

## Module 2 : Current and Voltage Transformers

### Lecture 9 : VT Tutorial

#### Objectives

In this lecture we will solve tutorial problems to:

- Design a CCVT.
- Find out the value of tuning inductance.
- Find out ratio error and phase angle error.
- Performance analysis of VT.

#### Example 1 :

Design a CCVT for a 132kV transmission line using the following data. Resistive Burden ( $3\phi$ ) = 150VA, frequency deviation to be subjected to  $\Delta f = 3\text{Hz}$ , phase angle error  $\beta = 40$  minutes. Consider four choices of  $V_2$  as 33 kV, 11 kV, 6.6 kV and 3.3 kV. Transmission line voltage  $V = 132$  kV. The standardized VT secondary voltage is 110 volts (L - L).

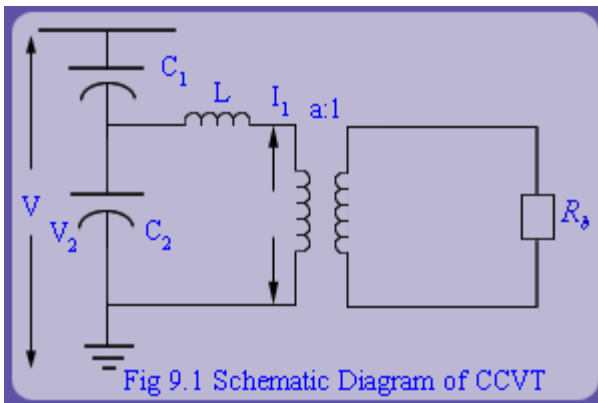


Fig 9.1 Schematic Diagram of CCVT

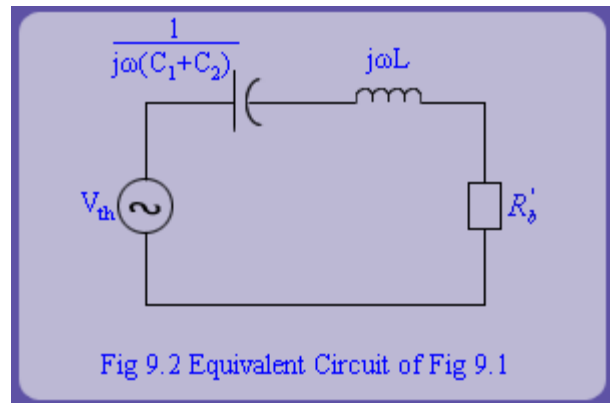


Fig 9.2 Equivalent Circuit of Fig 9.1

Answer:

Let  $V_2$  (L - N) be the voltage to be produced by the capacitive potential divider with capacitance values  $C_1$  and  $C_2$ . Let  $L$  be the value of tuning inductor. Our first task is to come up with a value of  $L$ . Here the specification for phase angle error  $\beta$  is 40 minutes. Variation in frequency can be upto  $\Delta f = 3\text{Hz}$  approximately. Phase angle error for change in  $\omega$  from  $\omega_0$  by  $\Delta\omega$  in the above equivalent circuit can be calculated as follows:

$$\begin{aligned} \Delta V_L - \Delta V_C &= jI \frac{d}{d\omega} \left( \omega L - \frac{1}{\omega C_{eq}} \right) \Delta\omega \\ &= I \left( L + \frac{1}{\omega_0^2 C_{eq}} \right) \Delta\omega \end{aligned}$$

At tuning frequency,

$$\omega_0^2 = \frac{1}{LC_{eq}}$$

Substituting  $\omega_0^2 = \frac{1}{LC}$

$$(\Delta V_L - \Delta V_C) = I(L+L)\Delta\omega$$

**Example 1: (contd..)**

From figure 9.3,  $\tan \beta = \frac{|V_L - V_C|}{|V_R|} = \frac{2LI\Delta\omega}{a^2 R_b I} = \frac{2L\Delta\omega}{a^2 R_b}$ . For small enough  $\beta$ ,  $\tan \beta = \beta$  and hence from

its % phase angle error  $\beta \approx \frac{2L\Delta\omega}{a^2 R_b} \times 100 \dots (1)$

Using this equation the value L for different values of  $V_2$  is found out.

(1) Let  $V_2$  be 33kV (L - N) Then;

$$\frac{3V_2^2}{R_b} = 150$$

$$R_b' = a^2 R_b = 217.8 \times 10^5 \Omega$$

$$\Delta\omega = 2\pi \times \Delta f = 2\pi \times 3$$

$$\beta = 40 \text{ min} = \frac{\pi \times 40}{180 \times 60} = 0.01164 \text{ rad}$$

From eqn (1)

$$L = \frac{\beta \times R_b'}{2 \times \Delta\omega} = \frac{0.01164 \times 217.8 \times 10^5}{2 \times 2\pi \times 3} = 6722.2 \text{ H}$$

$$C_1 + C_2 = \frac{1}{\omega^2 L} = 1.51 \times 10^{-9} \text{ F} = 1.51 \times 10^{-3} \mu\text{F}$$

**Example 1 : (contd..)**

(2)  $V_2 = 11 \text{ kV (L-N)}$

$$R_b' = \frac{3 \times (11 \times 10^3)^2}{150} = 242 \times 10^4 \Omega$$

$$L = \frac{\beta \times R_b'}{2 \times \Delta\omega} = \frac{0.01164 \times 242 \times 10^4}{2 \times 2\pi \times 3} = 747.2 \text{ H}$$

$$C_1 + C_2 = \frac{1}{\omega^2 L} = \frac{1}{(314)^2 \times 747.2}$$

$$= 1.36 \times 10^{-2} \mu\text{F}$$


(3)  $V_2 = 6.6 \text{ kV}$

$$R_b' = \frac{3 \times (6.6 \times 10^3)^2}{150}$$

$$= 87.12 \times 10^4 \Omega$$

$$L = \frac{\beta \times R_b'}{2 \times \Delta\omega} = \frac{0.01164 \times 87.12 \times 10^4}{2 \times 2\pi \times 3}$$

$$= 269 \text{ H,}$$

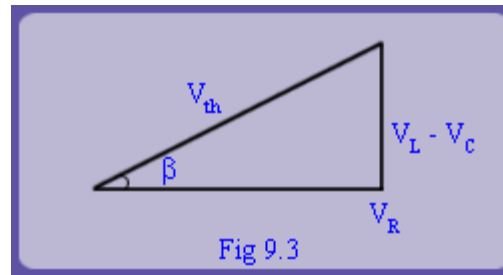

$$C_1 + C_2 = 3.77 \times 10^{-2} \mu F$$

$$(4) V_2 = 3.3 kV$$

$$R'_b = \frac{3 \times (3.3 \times 10^3)^2}{150}$$

$$= 21.78 \times 10^4 \Omega$$

$$L = \frac{\beta \times R'_b}{2 \times \Delta \omega} = \frac{0.01164 \times 21.78 \times 10^4}{2 \times 2\pi \times 3}$$

$$= 67.25 H$$

$$C_1 + C_2 = 0.151 \mu F$$

### Example 1 : (contd..)

The values of L,  $C_1 + C_2$  for different values of  $V_2$  are tabulated below.

$V_2$	L in H	$C_1 + C_2 \mu F$
33 kV	6722.2	0.00151
11 kV	747.2	0.0136
6.6 kV	269	0.0377
3.3 kV	67.25	0.151

From the above table it is clear that smaller the value of  $V_2$ , the smaller is the value of L and higher the value of  $C_1$  and  $C_2$  for tuning condition. If we select too low value of  $V_2$  and L then capacitance values will be beyond available limits, and if we select higher value of  $V_2$  and L, then CCVT's inductor will become bulky. So a compromise solution is necessary and let us select  $V_2 = 6.6 kV$

For  $V_2 = 6.6 kV$

$$L = 269 H$$

$$C_1 + C_2 = 0.0377 \mu F$$

$$\text{Now, } \frac{V}{V_2} = \frac{C_1 + C_2}{C_1}$$

$$\frac{132 \times 10^3}{\sqrt{3} \times 6.6 \times 10^3} = \frac{0.0377 \times 10^{-6}}{C_1}$$

$$C_1 = \frac{0.0377 \times \sqrt{3} \times 6.6 \times 10^3 \times 10^{-6}}{132 \times 10^3} \mu F$$


$$= 0.0033 \mu F$$

$$C_2 = 0.0344 \mu F$$

In this design, we have explained the basic concept for CCVT design and we assumed the transformer to be ideal. However in real life design, the value of magnetizing impedance of transformer, resistance of reactor etc have to be taken into account, as the ratio error  $\alpha$  and the phase angle error  $\beta$  will also get affected by these values. The next example brings out these issues.
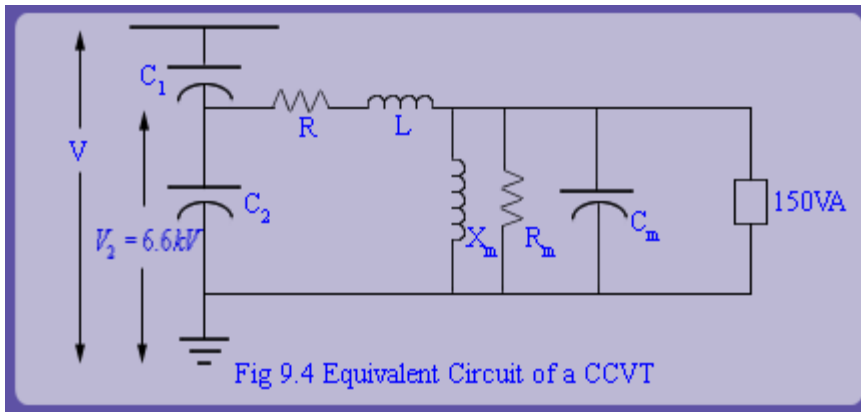
### Example 2:

The equivalent circuit of a CCVT is shown in fig 9.4. The values of  $C_1$  and  $C_2$  are  $0.0018 \mu F$  and  $0.0186 \mu F$  respectively. Tuning



inductor has an inductance of 497H and resistance of  $4620 \Omega$ .  $X_m$  of the VT referred to 6.6 kV side is  $1M\Omega$ , core loss = 20 watts per phase, VA burden = 150VA per phase. Value of  $C_m$  for compensating the current drawn by  $X_m$  is equal to  $3.183 \times 10^{-9} F$ .

- Verify the appropriateness of choice of L and  $C_m$ .
- Find out the nominal value of  $V/V_2$
- If the frequency drops from 50Hz to 47Hz, what would be the values of ratio error and phase angle error?

Answer (a):

If  $C_1 = 0.0018 \mu F$  and  $C_2 = 0.0186 \mu F$  then the value L of tuning inductor is given by

$$L = \frac{1}{\omega^2 (C_1 + C_2)}$$

where  $\omega = 2\pi f$  and  $f$  = nominal frequency. Thus,

$$L = \frac{1}{(2\pi \times 50)^2 (0.0018 + 0.0186) \times 10^{-6}}$$

= 496.7 H which is equal to the given value of L.

Now,  $X_m = 1 \times 10^6 \Omega$   $C_m$  has to be in parallel resonance with  $X_m$ . Therefore,

$$X_m = \frac{1}{\omega C_m}$$

$$C_m = \frac{1}{\omega X_m} = \frac{1}{(2\pi \times 50) \times 1 \times 10^6}$$

$$= 3.183 \times 10^{-9} F$$

The value is also same as the selected value of  $C_m$ . Hence, the selection of both L and  $C_m$  is appropriate.

Answer (b):

$$\frac{V}{V_2} = \frac{C_1 + C_2}{C_1} = \frac{0.0018 + 0.0186}{0.0018} = 11.33$$

$$V = 11.33 \times 6.6 = \frac{132}{\sqrt{3}} kV$$

Thus, this VT is connected to a 132 kV bus.

Example 2: (contd..)

Answer (c):

Core loss = 20 W

$$\frac{V_2^2}{R_m} = 20W$$

$$R_m = \frac{V_2^2}{20} = \frac{(6600)^2}{20}$$

$$= 2.18 \times 10^6 \Omega$$


VA burden = 150VA (resistive)

$$\frac{V_2^2}{R_b} = 150$$

$$R_b = \frac{V_2^2}{150} = \frac{(6600)^2}{150}$$

$$= 2.904 \times 10^5 \Omega$$

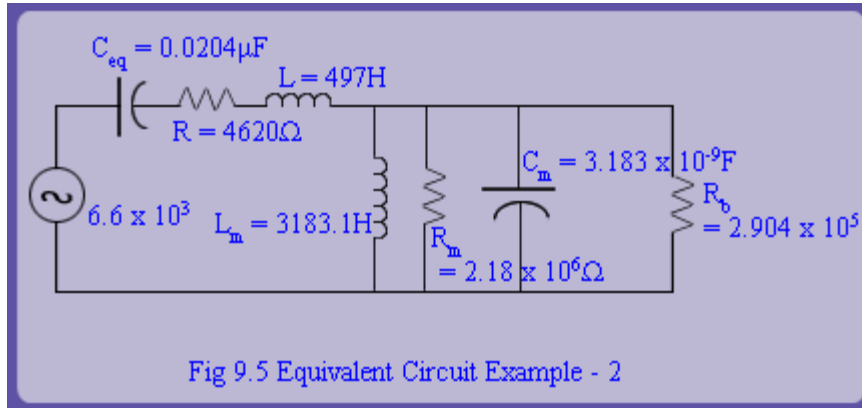
The equivalent circuit can be represented as shown below.



$$X_m = 10^6 \Omega \text{ at } f = 50 \text{ Hz}$$

$$2\pi f L_m = 10^6$$
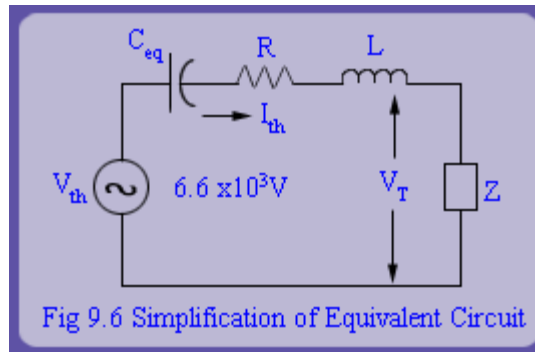
$$L_m = \frac{10^6}{2\pi} = 3183.1 \text{ H}$$



### Example 2 : (contd..)

The frequency of interest is 47Hz. Hence values of  $X_m$  and other impedance can be calculated at 47Hz. Figure 9.5 can be simplified as figure 9.6.

$$\text{Where } \frac{1}{Z} = \frac{1}{R_m} - \frac{j}{X_m} + j\omega C_m + \frac{1}{R_b}$$

$$= \frac{1}{2.18 \times 10^6} - \frac{j}{2\pi \times 47 \times 3183.1} + j2\pi \times 47 \times 3.183 \times 10^{-9} + \frac{1}{2.904 \times 10^5}$$

$$= 0.459 \times 10^{-6} - j1.064 \times 10^{-6} + j0.94 \times 10^{-6} + 3.44 \times 10^{-6}$$

$$= (3.902 - j0.124) \times 10^{-6} = 3.904 \times 10^{-6} \angle -1.82^\circ$$

$$Z = \frac{1}{3.904 \times 10^{-6} \angle -1.82^\circ} = 256147.5 \angle 1.82^\circ \Omega$$

$$= 256018.32 + j8135.15 \Omega$$

$$I_{th} = \frac{V_{th}}{R + j\omega L - \frac{j}{\omega C} + Z}$$

$$= \left[ \frac{6600 \angle 0^\circ}{4620 + j2\pi \times 47 \times 497 - \frac{j}{2\pi \times 47 \times 0.0204 \times 10^{-6}} + 256018.32 + j8135.15} \right]$$

$$\begin{aligned}
&= \frac{6600 \angle 0}{[4620 + j146768.9 - j165994 + 256018.32 + j8135.15]} \\
&= \frac{6600 \angle 0}{260638.32 - j11089.84} \\
&= \frac{6600 \angle 0}{260874.14 \angle -2.44^\circ} \text{ A} \\
V_T &= I_{th} \times Z \\
&= \frac{6600 \angle 0}{260874.14 \angle -2.44^\circ} \times 256147.5 \angle 1.82^\circ \\
&= 6480.42 \angle 4.26^\circ
\end{aligned}$$

Amplitude or ratio error of a CCVT is equal to  $\frac{V_{th} - V_T}{V_{th}} \times 100$  where  $V_{th}$  is the Thevenin equivalent voltage

source is nothing but open circuit emf.  $V_T$  is the terminal voltage on load. Hence % ratio error

$$= \frac{(6600 - 6480.42)}{6600} \times 100$$

$$= 1.81\%$$

Phase angle error =  $4.26^\circ$ .

Clearly, the phase angle error is on the higher side.

#### Review Questions

- Assume that the primary voltage of a CCVT is 400 kV and the voltage to be produced by the capacitive potential divider is 3.3 kV. If  $C_2$  is taken as  $0.02 \mu\text{F}$ , determine the value of tuning inductance at frequency of 50Hz.
- In figure 9.4 if  $V = 230 \text{ kV}$ ,  $V_2 = 6.6 \text{ kV}$  (L-N)  $C_1 = 0.001 \mu\text{F}$  and  $X_m = 1.2 \text{ M}\Omega$ , then find out the values of tuning inductance and capacitance to be connected across CCVT's secondary for compensating  $X_m$ . Standardized secondary voltage of a VT is 110V (L-L).
- Design a CCVT for a 400 kV transmission line using the following data. Secondary resistive burden ( $3 \phi$ ) = 300VA.  
Core loss ( $3 \phi$ ) = 50W.  $\Delta f = \pm 3 \text{ Hz}$ . Consider 3 choices of  $V_2 = 3.3 \text{ kV}$ ,  $6.6 \text{ kV}$ ,  $11 \text{ kV}$ . Take phase angle error  $\beta = 40 \text{ min.}$  and standard VT secondary voltage = 110 V (L-L).

#### Recap

In this lecture by solving the tutorial problems we have learnt the following:

- How to decide  $V_2$ .
- How to choose  $L$ .

- How to decide  $C_1$  and  $C_2$ .
- How to evaluate performance of VT.