

## LAB 4.1

# Diode I-V Transfer Curve

[See Section 4.2, p. 173 of Sedra/Smith]

### OBJECTIVES:

To study junction diode terminal characteristics by:

- Analyzing, simulating, and building a diode-based circuit.
- Taking measurements and applying transformations to obtain the diode I-V curve.

### MATERIALS:

- Laboratory setup, including breadboard
- One junction diode (e.g., 1N4003)
- Several wires and a resistor

### PART 1: SIMULATION

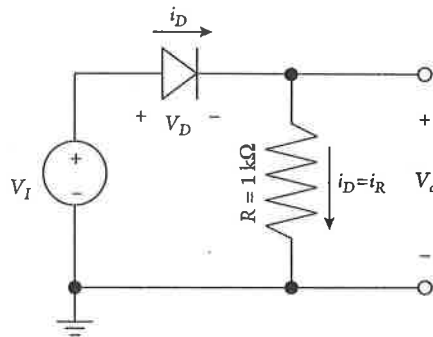


FIGURE L4.1: Circuit used to characterize junction diode terminal characteristics. Based on Fig. 4.21 p. 196 S&S.

Consider the circuit shown in Figure L4.1. Simulate the circuit by varying  $v_I$  from  $-3\text{ V}$  to  $+3\text{ V}$  in increments of  $0.1\text{ V}$ . Generate a plot of  $i_D$  vs.  $v_I$  and  $v_O$  vs.  $v_I$ . Do you see a resemblance between the two graphs?

## PART 2: MEASUREMENTS

Assemble the circuit onto a breadboard. Using a power supply, vary the input voltage from  $-3\text{ V}$  to  $+3\text{ V}$  in increments of  $0.25\text{ V}$ . For each point, measure the output voltage  $v_O$  using a digital multimeter, and report the current consumption  $i_D$  indicated by the power supply. Measure the value of the resistor.

## PART 3: POST-MEASUREMENT EXERCISE

- Generate a plot of  $v_O$  vs.  $v_I$  and a plot of  $i_D$  vs.  $v_I$ . Since  $i_D = v_O/R$ , do the two plots generally agree?
- Since the diode voltage is  $v_D = v_I - v_O$ , generate a new plot of  $i_D$  vs.  $v_D$ . Is it what you expect?

## PART 4 [OPTIONAL]: EXTRA EXPLORATION

- If you have access to a semiconductor parameter analyzer, generate the  $i_D$  vs.  $v_D$  curve using the analyzer. How does it compare to the curve you generated in Part 3?