

## LAB 4.2

# Fun with Diodes I: Rectifiers

[See Section 4.5, p. 194 of Sedra/Smith]

### OBJECTIVES:

To study diode-based rectifier circuits by:

- Analyzing, simulating, and building several rectifier circuits.
- Noting that many diode-based circuits are easy to assemble. In this lab, you will build several circuits that require only a few simple components.

### MATERIALS:

- Laboratory setup, including breadboard
- Several junction diodes (e.g., 1N4003)
- One 741-type operational amplifier
- Several wires, resistors, and capacitors of varying sizes

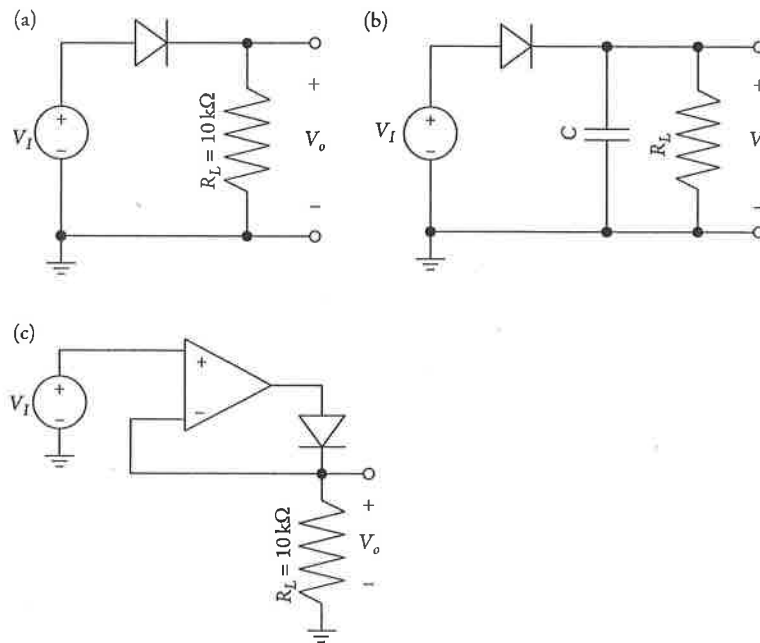


FIGURE L4.2: (a) Half-wave rectifier, (b) peak rectifier, and (c) precision rectifier. Circuits are based on Fig. 4.21 p. 196, Fig. 4.25 p. 202, and Fig. 4.27 p. 206 S&S.

**PART 1: SIMULATION****Half-wave rectifier**

Consider the half-wave rectifier shown in Figure L4.2(a). Simulate the circuit using a  $10\text{-V}_{\text{pk-pk}}$  1-kHz sinusoid and a 1N4003 diode. Provide a plot of  $v_I$  and  $v_O$  vs.  $t$ .

**Peak rectifier**

Consider the peak detector shown in Figure L4.2(b). Simulate the circuit using a  $10\text{-V}_{\text{pk-pk}}$  1-kHz input sinusoid for the two following sets of parameters. For both simulations, provide a plot of  $v_I$  and  $v_O$  vs.  $t$ , and report the peak voltage ( $V_p$ ) and the ripple voltage ( $V_r$ ).

- Peak detector I: Use  $R_L = 1\text{ k}\Omega$ ,  $C = 47\text{ }\mu\text{F}$ , 1N4003 diode
- Peak detector II: This time use  $R_L = 100\text{ }\Omega$ ,  $C = 47\text{ }\mu\text{F}$ , 1N4003 diode

**Precision rectifier**

Consider the precision rectifier shown in Figure L4.2(c). Simulate the circuit using a  $10\text{-V}_{\text{pk-pk}}$  1-kHz sinusoidal input, a 741 op-amp, and a 1N4003 diode. Provide a plot of  $v_I$  and  $v_O$  vs.  $t$ . Use  $R_L = 10\text{ k}\Omega$ .

**PART 2: MEASUREMENTS**

- For each circuit, assemble the circuit, apply the required waveform using a function generator, and capture the input and output voltage waveforms on an oscilloscope.
- For the peak rectifier, record the values of  $V_p$  and  $V_r$ .
- Using a digital multimeter, measure all resistors to three significant digits.

**PART 3: POST-MEASUREMENT EXERCISE**

- Using your measured resistor values, resimulate your circuits. How do the updated results compare with your simulations, and experiments? Explain any discrepancies.
- What conclusions do you draw from the two different peak rectifiers?

**PART 4 [OPTIONAL]: EXTRA EXPLORATION**

Can you turn the precision half-wave rectifier into a precision peak rectifier?