

Digital Circuit Design

Jeffrey N. Denenberg

Lecture #1

Introduction, Logic Circuits

Administrative

Handouts

Course Syllabus (readings due **before** lecture)

<http://DoctorD.WebHop.net>

Linked Resources on Syllabus

Grading

20% Homework (Due the week following the lecture on that topic)

2 midterms (40%) + cumulative final (40%)

all exams required; make arrangements in advance if you have a conflict.

Lab Note: You should prepare prior to Lab session

Paper design (if required)

Functioning simulation

Number Systems

Radix 10 Why? (0, 1, 9)

$$5,273 = 5 \cdot 10^3 + 2 \cdot 10^2 + 7 \cdot 10^1 + 3 \cdot 10^0$$

Binary Radix 2 (0,1)

On/off

$$153 = 2^7 + 2^3 + 2^0 = 10001001$$

Octal Radix 8 (0, 1, 7)

$$153 = 2 \cdot 8^2 + 3 \cdot 8^1 + 8^0 = 231$$

Hexadecimal Radix 16 (0, 1, 9, A, F)

$$153 = 9 \cdot 16^1 + 9 \cdot 16^0 = 99$$

Complements


(Representing Negative Numbers)

Signed-magnitude Binary

$$9 = \underline{0}0001001$$

↑
Sign bit

$$-9 = \underline{1}0001001$$

 


1 s complement (complement all bits)

$$-9 = 11110110$$

2 s complement (add 1 to the 1 s complement)

$$-9 = 11110111$$

 

Illustrative Example: 9 s Complement

Decimal Subtraction

$$\begin{array}{r} 575 \\ - 57 \\ \hline 518 \end{array}$$

9 s Complement

$$\begin{array}{r} -057 = 942 \\ \quad \quad \underline{575} \\ 1517 \end{array}$$

now wrap the overflow around and add for the answer

$$518$$

10 s Complement

$$\begin{array}{r} -057 = 942+1 = 943 \\ \quad \quad \underline{575} \\ 1518 \end{array}$$


Here ignore the overflow to get 518

Other Codes

BCD (10, 4-bit binary codes per digit)

Gray Code

 only one bit changes between adjacent Digits





ASCII

0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
0 NUL	SOH	STX	ETX	EOT	ENQ	ACK	BEL	BS	HT	LF	VT	FF	CR	SO	SI
1 DLE	DC1	DC2	DC3	DC4	NAK	SYN	ETB	CAN	EM	SUB	ESC	FS	GS	RS	US
2 SP	!	"	#	\$	%	&	'	()	*	+	,	-	.	/
3 0	1	2	3	4	5	6	7	8	9	:	;	<	=	>	?
4 @	A	B	C	D	E	F	G	H	I	J	K	L	M	N	O
5 P	Q	R	S	T	U	V	W	X	Y	Z	[\]	^	_
6 `	a	b	c	d	e	f	g	h	i	j	k	l	m	n	o
7 p	q	r	s	t	u	v	w	x	y	z	{		}	~	DEL

Digital Logic

Binary system -- 0 & 1, LOW & HIGH, negated and asserted.

Basic building blocks -- AND, OR, NOT

 
 


J. N. Denenberg

Lecture 1: Intro and Logic Circuits

7

Digital Logic Continued

  


J. N. Denenberg

Lecture 1: Intro and Logic Circuits

8

Many representations of digital logic

Transistor-level circuit diagrams

 


Gate symbols (for simple elements)


Truth tables

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Logic diagrams

 

 Prepackaged building blocks, e.g. multiplexer



$$\text{Equations: } Z = S' \cdot A + S \cdot B$$

Various hardware description languages

ABEL

```

module chap1mux
title 'Two-input multiplexer example'
CHAP1MUX device 'P16V8'

A, B, S      pin 1, 2, 3;
Z            pin 13 istype 'com';

equations

WHEN S == 0 THEN Z = A; ELSE Z = B;

end chap1mux
    
```

VHDL

```

library IEEE;
use IEEE.std_logic_1164.all;

entity Vchap1mux is
port ( A, B, S: in  STD_LOGIC;
      Z: out STD_LOGIC );
end Vchap1mux;


architecture Vchap1mux_arch of Vchap1mux is
begin
Z <= A when S = '0' else B;
end Vchap1mux_arch;
    
```

We'll start with gates and work our way up

Logic levels

Undefined region
is inherent

 digital, not analog
amplification,
weak => strong




Switching threshold varies with voltage, temp,
process, phase of the moon
need noise margin

The more you push the technology, the more
analog it becomes.

Logic voltage levels decreasing with process


5 -> 3.3 -> 2.5 -> 1.8 V

MOS Transistors

 

Voltage-controlled resistance


PMOS

 

Voltage-controlled resistance:
decrease $V_{gs} \implies$ decrease R_{ds}

Note: normally, $V_{gs} \leq 0$


NMOS

 

Voltage-controlled resistance:
increase $V_{gs} \implies$ decrease R_{ds}


Note: normally, $V_{gs} \geq 0$

CMOS Inverter

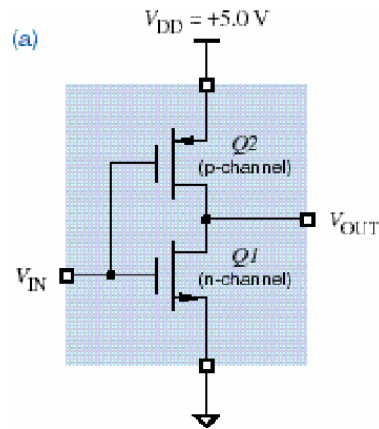



(b)

V_{IN}	$Q1$	$Q2$	V_{OUT}
0.0 (L)	off	on	5.0 (H)
5.0 (H)	on	off	0.0 (L)

 


Switch model

Simplified Inverter Model

  

Alternate transistor symbols

Inverter Again

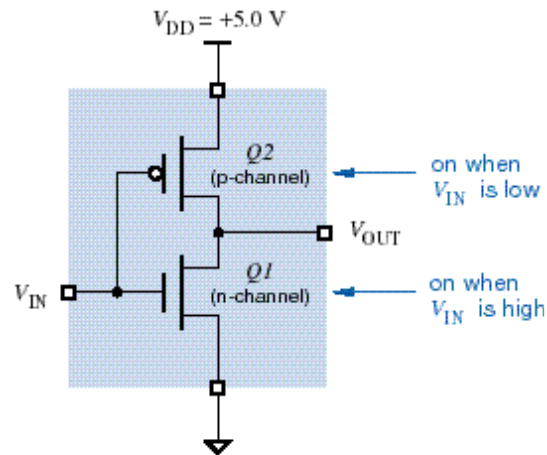

CMOS Gate Characteristics

No DC current flow into MOS gate terminal


However gate has capacitance \implies current required for switching (CV^2f power)

No current in output structure, except during switching

Both transistors partially on
Power consumption related to frequency

Slow input-signal rise times \implies more power

 Symmetric output structure \implies equally strong drive in LOW and HIGH states



This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.