

# Digital Design

## Lectures 11 & 12

Shift Registers and Counters

# Register with Parallel Load

- Register: Group of Flip-Flops
- Ex: D Flip-Flops
- Holds a Word (Nibble) of Data
- Loads in Parallel on Clock Transition
- Asynchronous Clear (Reset)

 


Fig. 6-1 4-Bit Register

# Register with Load Control

- Load Control = 1
  - New data loaded on next positive clock edge
- Load Control = 0
  - Old data reloaded on next positive clock edge

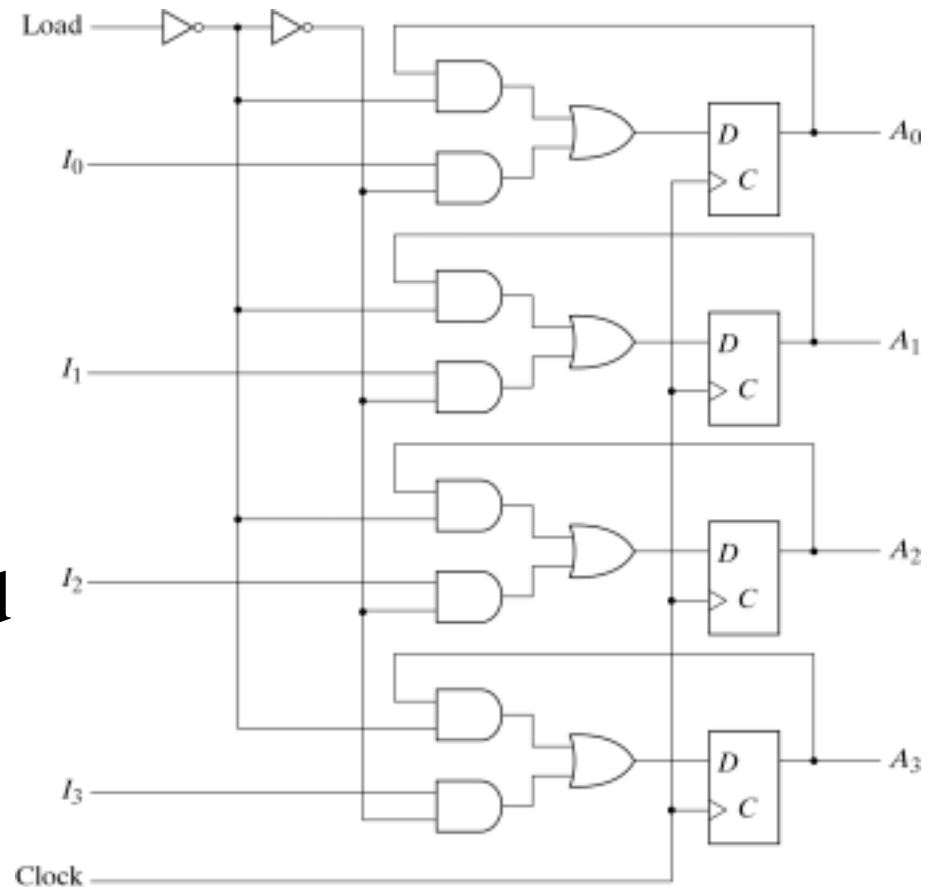


Fig. 6-2 4-Bit Register with Parallel Load

# Shift Registers

- Cascade chain of Flip-Flops
- Bits travel on Clock edges (Bucket Brigade)
- Serial in – Serial out, can also have parallel load / read

 


Fig. 6-3 4-Bit Shift Register

# Serial Transfer

Time	Reg A	Reg B
T0	1011	0011
T1	1101	1001
T2	1110	1100
T3	0111	0110
T4	1011	1011

 
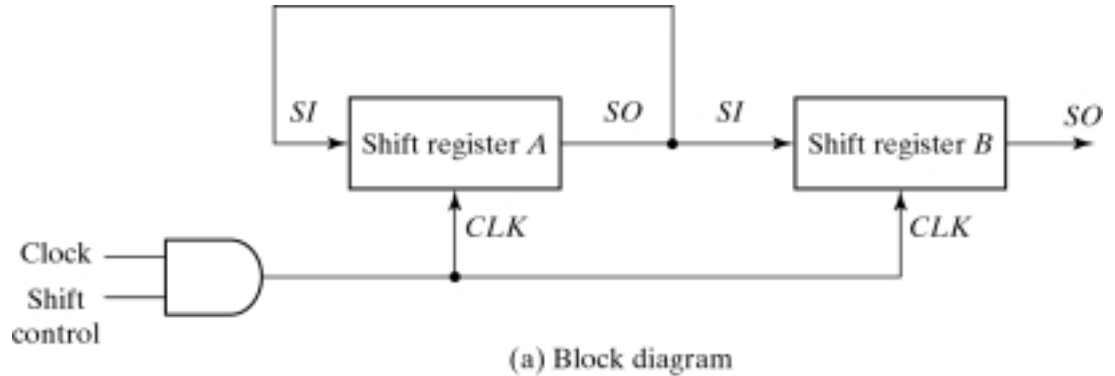


Fig. 6-4 Serial Transfer from Register A to register B

# Serial Addition (D Flip-Flop)

- Slower than parallel
- Low cost
- Share fast hardware on slow data
- Good for multiplexed data

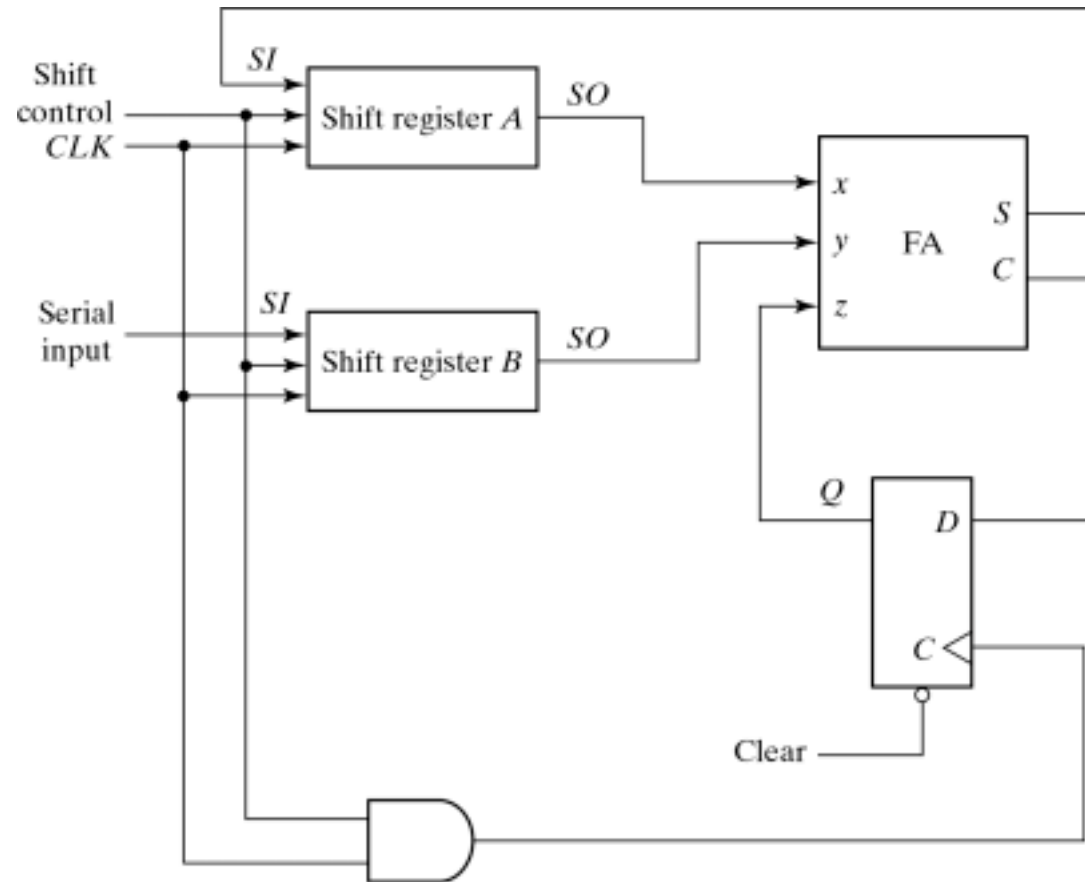


Fig. 6-5 Serial Adder

# Designing a JK Serial Adder

- $J_Q = x \cdot y$ ,  $K_Q = x' \cdot y' = (x+y)'$ ,  $S = x \oplus y \oplus Q$

Present State Q	Inputs x y		Next State Q	Output S	Flip_Flop Inputs J <sub>Q</sub> K <sub>Q</sub>	
0	0	0	0	0	0	x
0	0	1	0	1	0	x
0	1	0	0	1	0	x
0	1	1	1	0	1	x
1	0	0	0	1	x	1
1	0	1	1	0	x	0
1	1	0	1	0	x	0
1	1	1	1	1	x	0

Table 6-2

# New Serial Adder


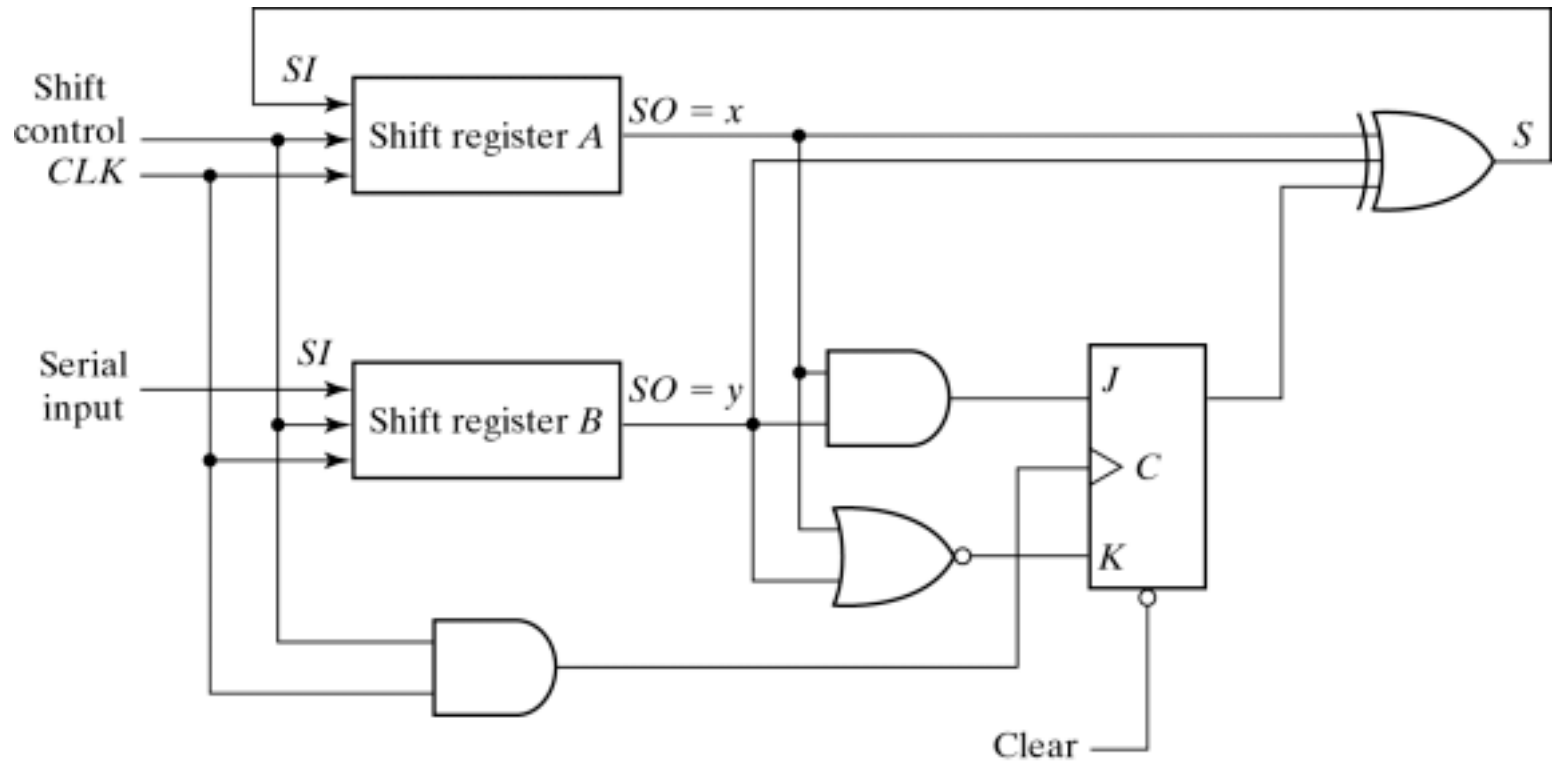


Fig. 6-6 Second form of Serial Adder

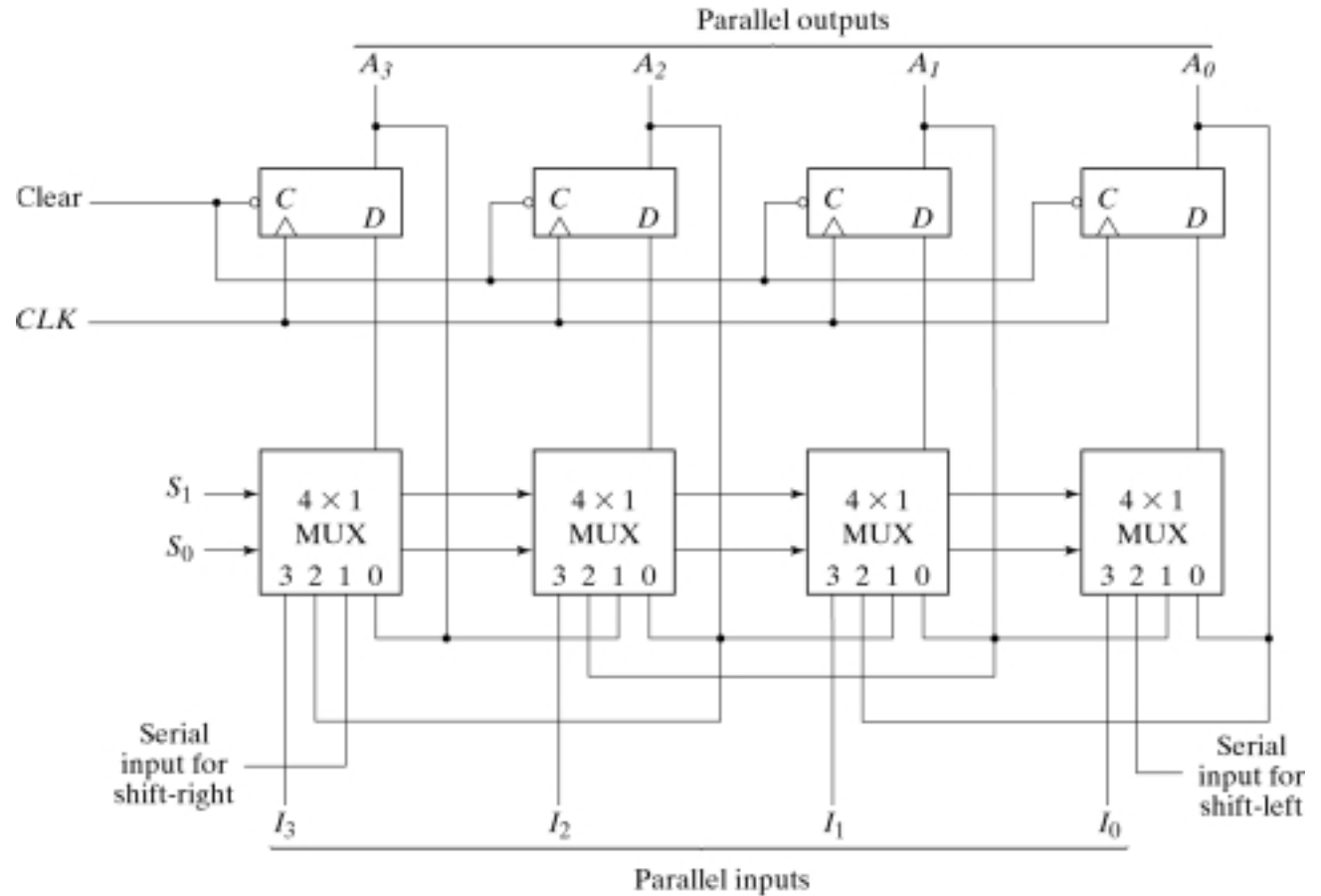

# Universal Shift Register

- Clear
- Clock
- Shift
  - Right
  - Left
- Load
- Read
- Control



S1  
0  
0  
1  
1

Fig. 6-7 4-Bit Universal Shift Register

# Binary Ripple Counter

- Asynchronous counter
- Changes “ripple” through the stages

Table 6-4

$A_3$	$A_2$	$A_1$	$A_0$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

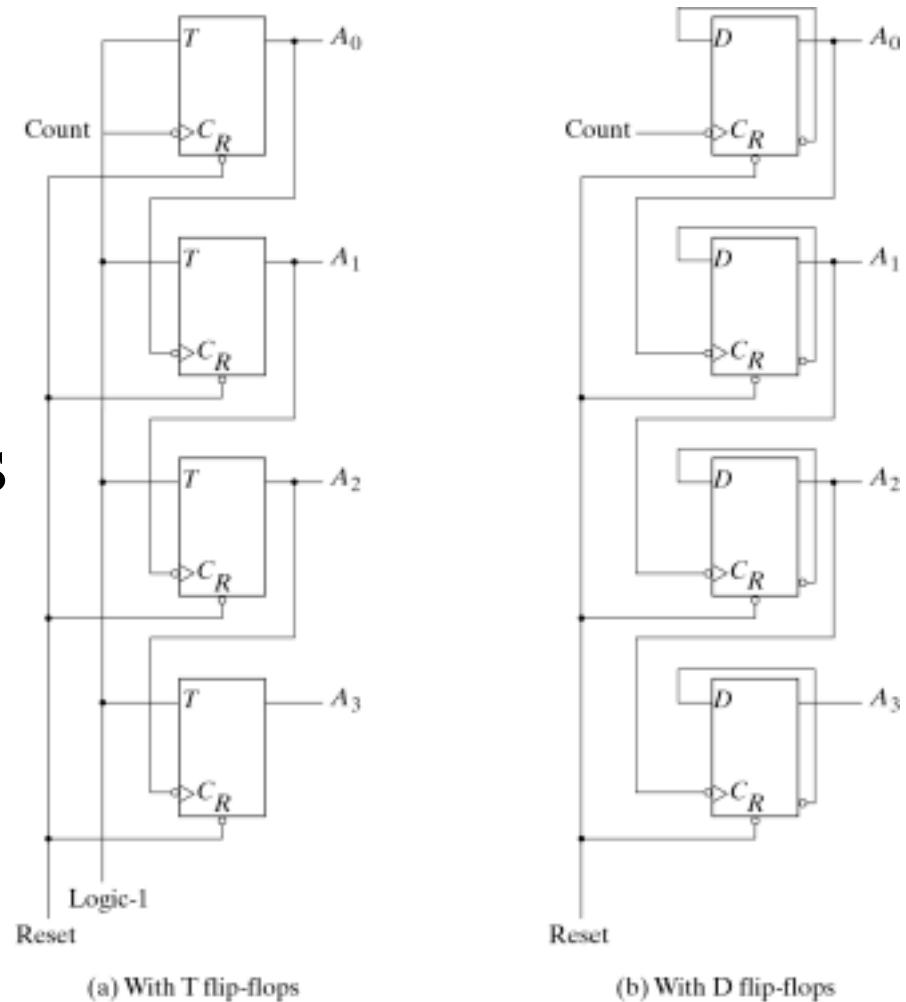


Fig. 6-8 4-Bit Binary Ripple Counter

# Decimal (BCD) Counter

 


Fig. 6-9 State Diagram of a Decimal BCD-Counter

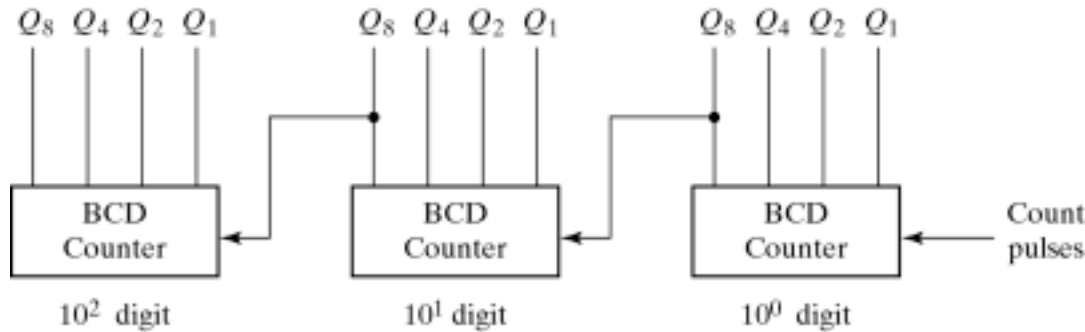


Fig. 6-11 Block Diagram of a Three-Decade Decimal BCD Counter

 


Fig. 6-10 BCD Ripple Counter

# Synchronous Binary Counter

- All transitions occur on clock pulse edges in parallel
- Faster results than ripple counters

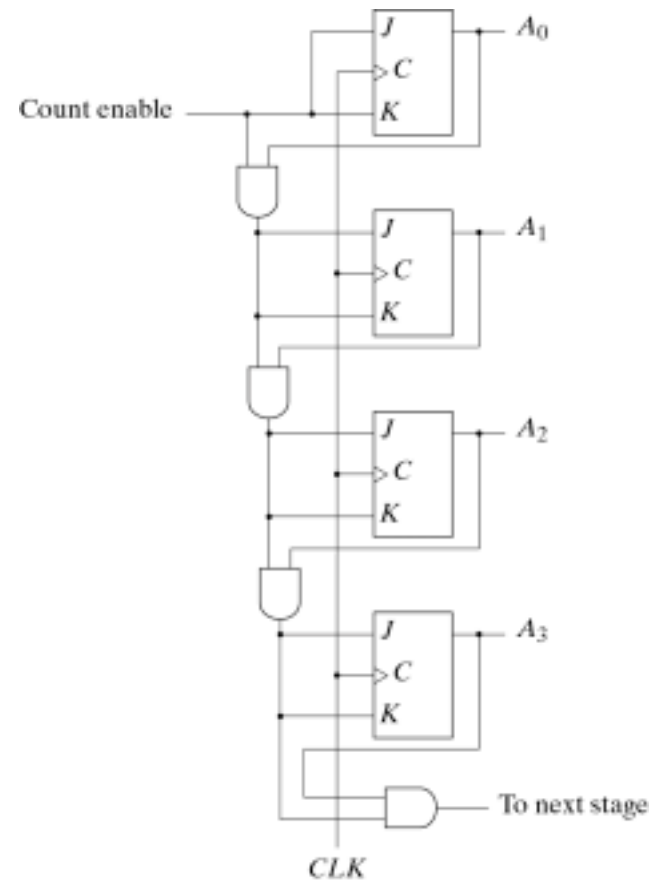


Fig. 6-12 4-Bit Synchronous Binary Counter

# Up-Down Synchronous Counter

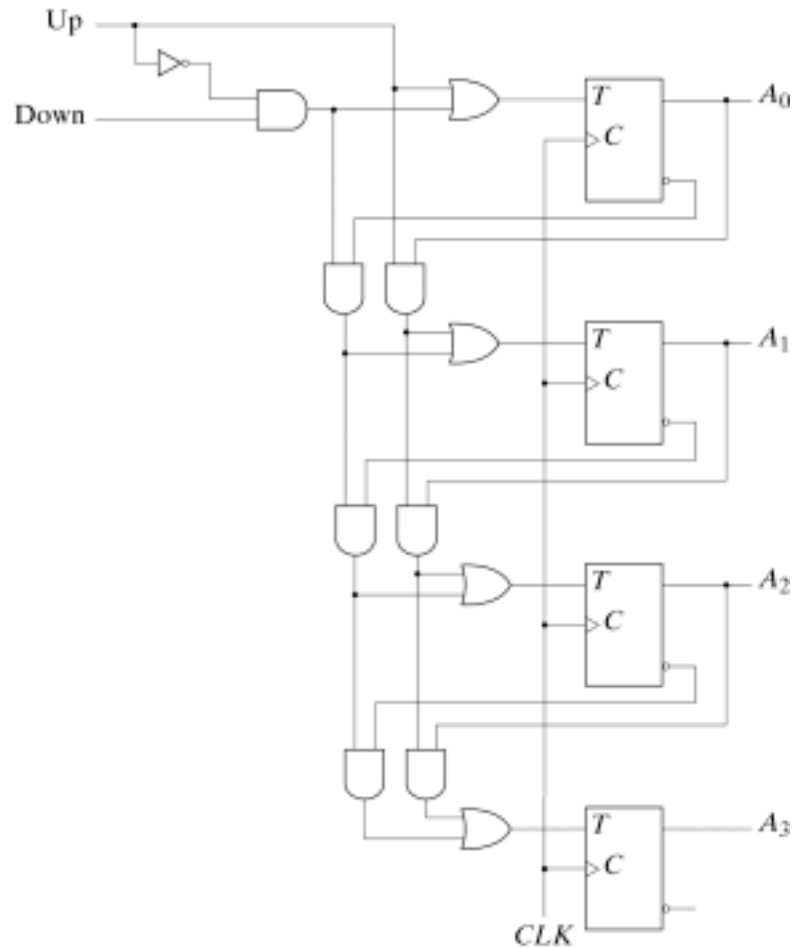


Fig. 6-13 4-Bit Up-Down Binary Counter

# Designing a Synchronous BCD Counter

Present State				Next State				Output	Next State			
Q <sub>8</sub>	Q <sub>4</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>8</sub>	Q <sub>4</sub>	Q <sub>2</sub>	Q <sub>1</sub>	y	TQ <sub>8</sub>	TQ <sub>4</sub>	TQ <sub>2</sub>	TQ <sub>1</sub>
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	1	0	0	1	1	0	0	0	0	1	1
0	1	0	1	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

$$TQ_1 = 1, \quad TQ_2 = Q'_8 Q_1, \quad TQ_4 = Q_2 Q_1, \quad TQ_8 = Q_8 Q_1 + Q_4 Q_2 Q_1, \quad y = Q_8 Q_1$$

# 4-bit Synchronous Counter with Parallel Load

Clear	Clk	Load	Count	Function
0	x	x	x	Clear
1	↑	1	x	Load
1	↑	0	1	Count
1	↑	0	0	No Change

Table 6-6

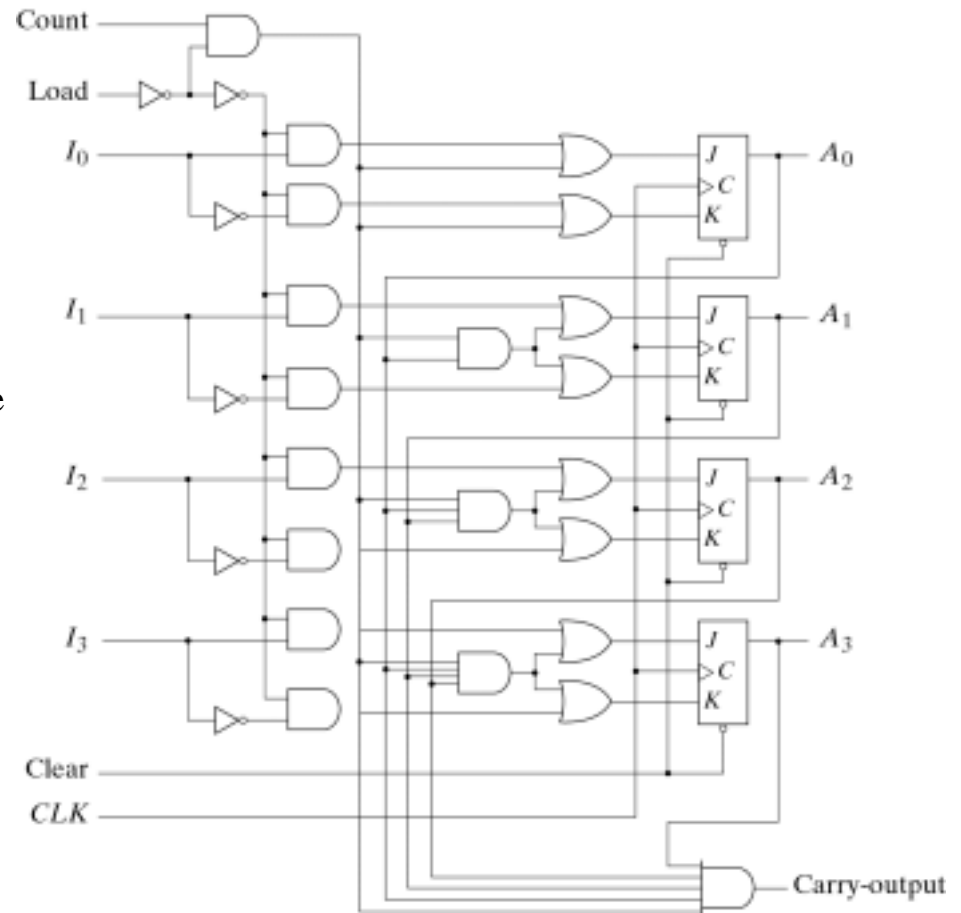


Fig. 6-14 4-Bit Binary Counter with Parallel Load

# More BCD Counters with Parallel Load

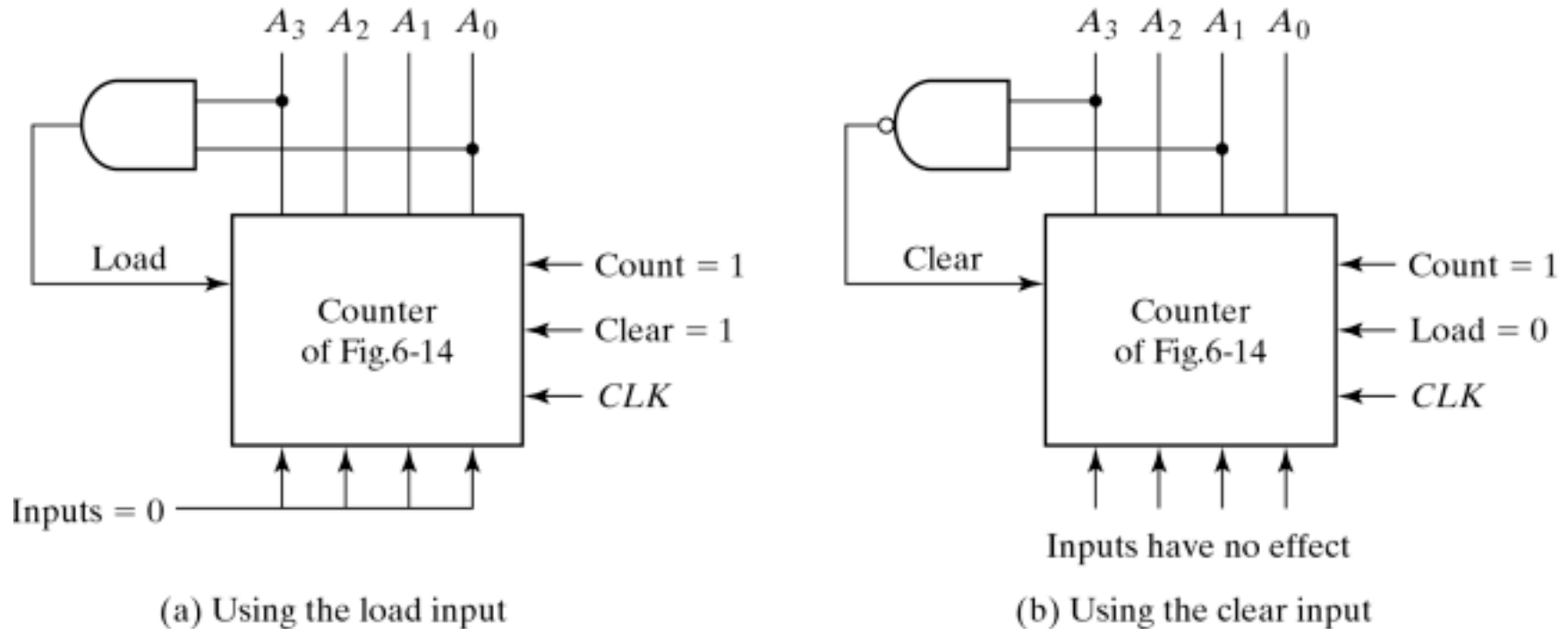


Fig. 6-15 Two ways to Achieve a BCD Counter Using a Counter with Parallel Load



# Counters with Unused States

- If in unused state
  - Ensure automatic return to a valid state
  - “Self-correcting”

 
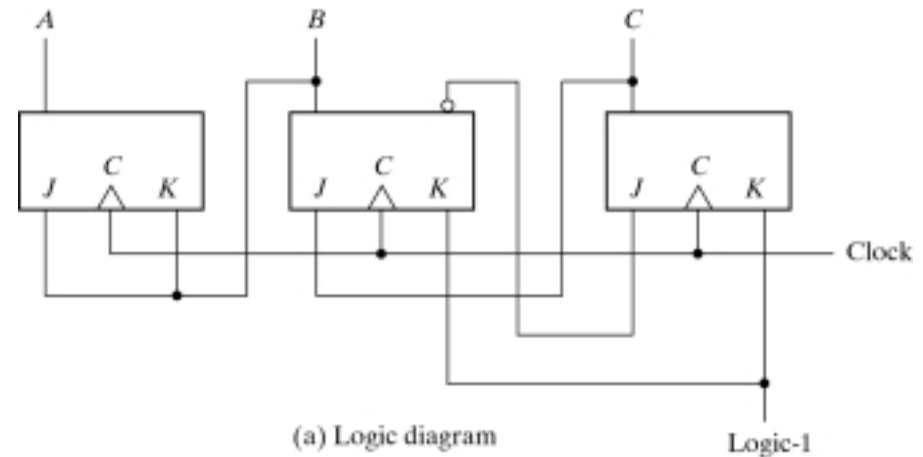


Fig. 6-16 Counter with Unused States

# Generating Timing Pulses

- Shift Register
  - Walk a 1
- Counter and decoder


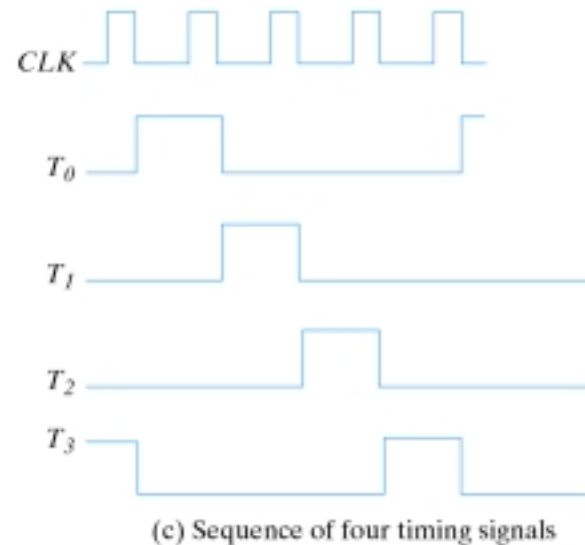
 


Fig. 6-17 Generation of Timing Signals
 
# Johnson Counter

- Shift register
- $2 \cdot k$  States
  - Walk 1s
  - Then walk 0s
- Only needs simple output logic for timing pulses (Mealy model)



(a) Four-stage switch-tail ring counter

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	$AB'$
3	1	1	0	0	$BC'$
4	1	1	1	0	$CE'$
5	1	1	1	1	$AE$
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

(b) Count sequence and required decoding

Fig. 6-18 Construction of a Johnson Counter