

## Notes on Phasor Notation and Diagrams

**Mathematically correct**  $V_m \dots$  Magnitude

Complex quantity  $\rightarrow \underline{V} = V_m e^{j\omega t} = V_m \cos(\omega t) + jV_m \sin(\omega t)$   
 ("underlined")

$$v(t) = \text{Re}(\underline{V}) = V_m \cos(\omega t)$$

or  $v(t) = \text{Im}(\underline{V}) = V_m \sin(\omega t)$

**Practical notation and usage**

Complex quantity, but underlining omitted  $\rightarrow I = 10 \text{ A} \angle 45^\circ$


RMS value instead of magnitude

For practical use phasor diagrams can be drawn with RMS values

RMS values are given if not noted otherwise. If in doubt, ask!
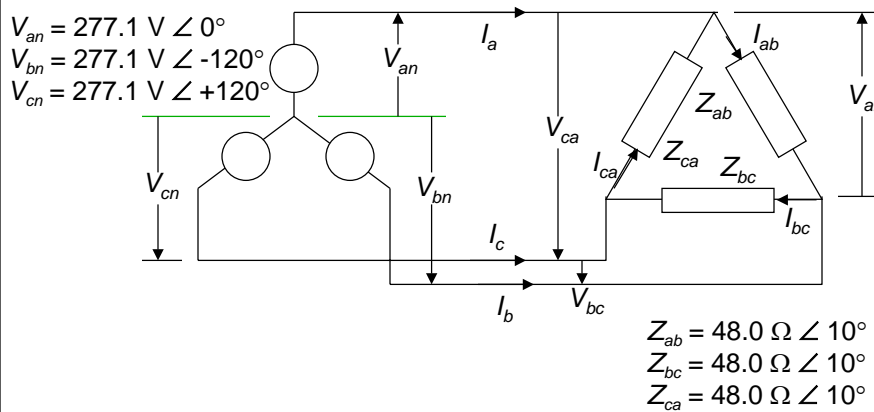
## Example: 3~ Balanced Circuit

For the following circuit, find all the voltage and current values and phasors and use them to find the power flowing in each part of the circuit



## Example: 3~ Balanced Circuit

$$V_{ab} = V_{an} - V_{bn} = 277.1\angle 0^\circ - 277.1\angle -120^\circ = 480\angle 30^\circ$$

$$|V_{L-L}| = 277.1 \cdot \sqrt{3} = 480V$$

$$I_{ab} = \frac{V_{ab}}{Z_{ab}} = \frac{480\angle 30^\circ}{48\angle 10^\circ} = 10A\angle 20^\circ$$

$$I_{bc} = I_{ab} \cdot 1\angle -120^\circ = 10A\angle -100^\circ$$

$$I_{ca} = I_{ab} \cdot 1\angle 120^\circ = 10A\angle 140^\circ$$


$$I_a = I_{ab} - I_{ca} = 10\sqrt{3}\angle -30^\circ + 20^\circ = 17.3A\angle -10^\circ$$

$$S = 3V_p I_p^* = 277.1 \cdot 17.3A\angle 0 + 10^\circ$$

$$= 4.8kVA\angle 10^\circ, PF = \cos(\phi) = 0.985, lag$$

$$P = S \cdot PF = 4.8 \cdot 0.985 = 4.72kW$$

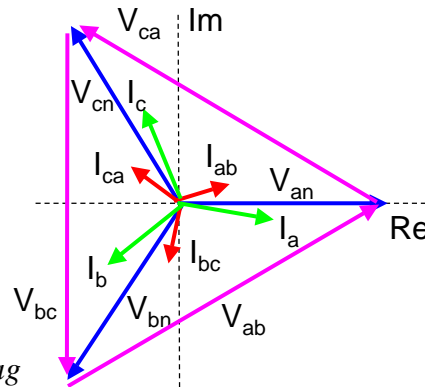
$$Q = S \cdot \sin(\phi) = 0.83kVAr \text{ delivered from source to load}$$



## Simplified Analysis, Balanced System

- **Single-phase analysis can be applied to balanced three-phase systems**
- **Convert a network into a wye-connected system**
  - ◆ Convert delta connected load and sources to wye connected equivalent
  - ◆ Connect a neutral conductor between all the neutral points of the wye connected loads and sources
- **Split the network into three equal single-phase equivalents**
- **Solve one of the single-phase equivalents**
- **Combine solutions of the three single-phase equivalents. Remember to adjust the phase angles of phase b and c.**
- **Compute the line voltages and currents**

## Δ-Y Transformation

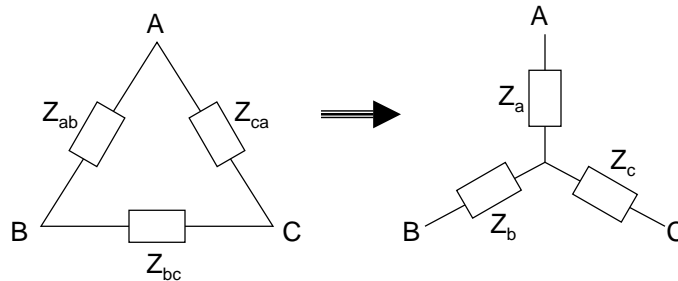


$$Z_a = \frac{Z_{ab} \cdot Z_{ca}}{Z_{ab} + Z_{bc} + Z_{ca}} \quad Z_b = \frac{Z_{ab} \cdot Z_{bc}}{Z_{ab} + Z_{bc} + Z_{ca}} \quad Z_c = \frac{Z_{bc} \cdot Z_{ca}}{Z_{ab} + Z_{bc} + Z_{ca}}$$

For  $Z_{ab} = Z_{bc} = Z_{ca}$

$$Z_Y = \frac{1}{3} Z_{\Delta}$$

## Y-Δ Transformation

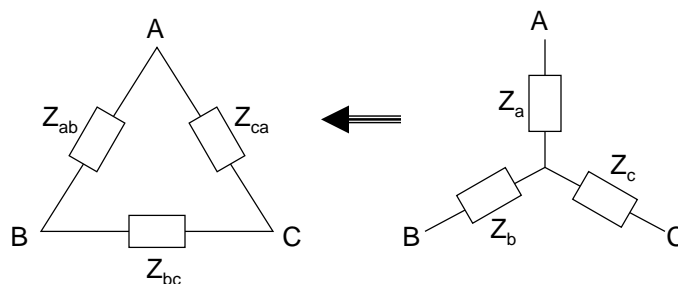

$$Z_{bc} = Z_b + Z_c + \frac{Z_b \cdot Z_c}{Z_a}$$


$$Z_{ab} = Z_a + Z_b + \frac{Z_a \cdot Z_b}{Z_c}$$

$$Z_{ca} = Z_c + Z_a + \frac{Z_c \cdot Z_a}{Z_b}$$


For  $Z_a = Z_b = Z_c$

$$Z_{\Delta} = 3 \cdot Z_Y$$
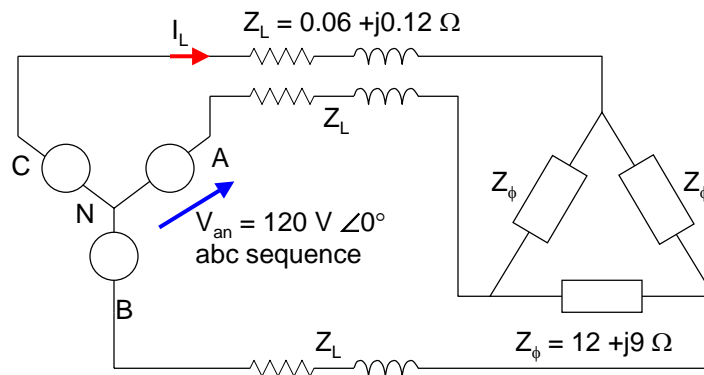
### Example: 3~ power system (book p.72, 2-2)



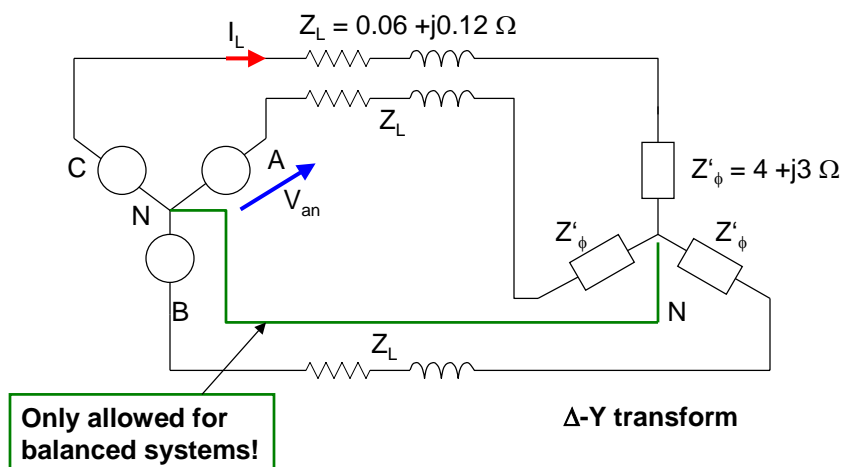
### Example: 3~ power system (book p.72, 2-2)



## Example: 3~ power system (book p.72, 2-2)

### Single phase equivalent

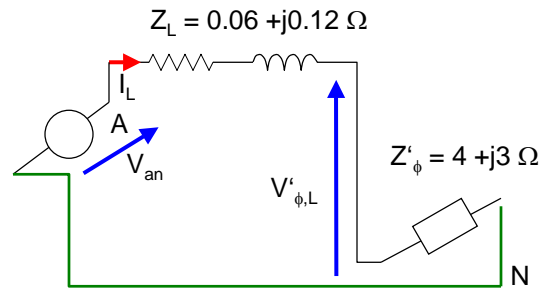

$$I_L = \frac{V_{an}}{Z_L + Z'_\phi} = \frac{120V}{4.06 + j3.12\Omega} = 23.4 A \angle -37.5^\circ$$

$$V'_{\phi,L} = I_L Z'_\phi = 117V \angle -0.6^\circ$$

## Homework 2


See web site

<http://www.eng.fsu.edu/~steuer/eel3216.html>

**IMPORTANT:**  
Change of homework policy


Homework solutions will **NOT** be accepted after the due date (see also updated policies on web site).

# Transformers

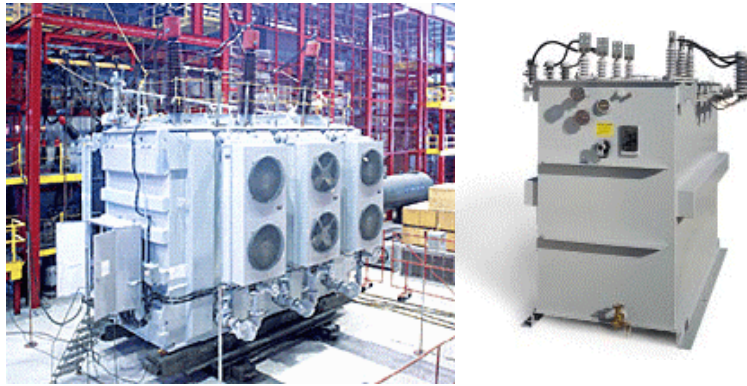

# Transformer Basics

**Figure 3-6** | Sketch of a real transformer with no load attached to its secondary.

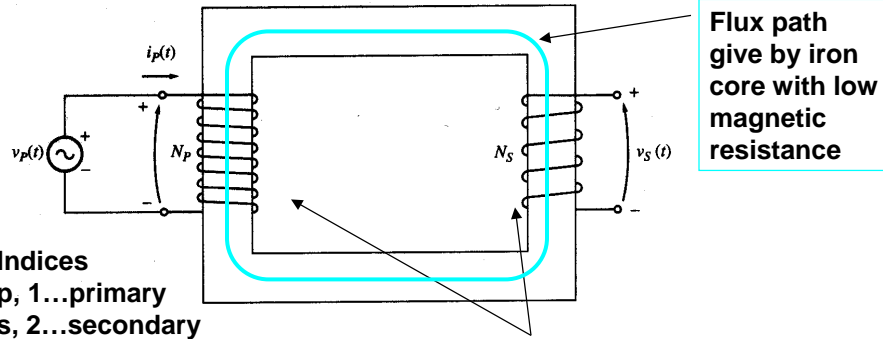

Indices  
 p, 1...primary  
 s, 2...secondary

Turns ratio

$$a = \frac{N_1}{N_2} = \frac{V_1}{V_2}$$

Real transformer typically has concentric windings for better coupling

## Why Power Transformers ?

---

- **By stepping up the voltage the current is reduced proportionally for the same power**

$$P_1 = V_1 I_1 \cos(\phi) \quad V_2 = a V_1 \quad P_2 = V_2 I_2 \cos(\phi) = P_1$$
$$I_2 = \frac{I_1}{a} \quad (\text{ideal transformer})$$

- **Smaller currents require less conductor material**
  - ♦ e.g. for same losses in transmission line conductors on primary and secondary side of transformer


$$P_{Loss,1} = I_1^2 R_1$$
$$P_{Loss,2} = I_2^2 R_2 = \left(\frac{I_1}{a}\right)^2 R_2 = I_1^2 R_1 \rightarrow R_2 = a^2 R_1$$

## Why Transformers ?

---

- **Galvanic isolation between sub-systems**
  - ♦ Reduce ground fault currents
- **Transition between 3 and 4 wire systems**
  - ♦ Delta-wye
- **Voltage regulation**
- **Instrumentation transformers**
  - ♦ Potential transformers (PT) to measure high voltages
  - ♦ Current transformers (CT) to measure high currents

## Faraday's Law

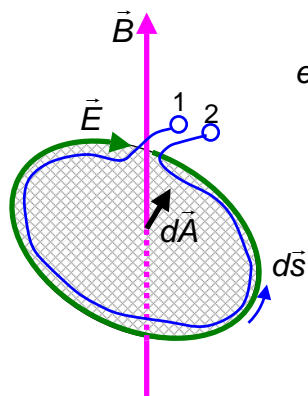

$$e_{ind,1-2} = \oint_S \vec{E} \cdot d\vec{s} = - \frac{d}{dt} \int_A \vec{B} \cdot d\vec{A} = - \frac{d\phi}{dt}$$

scalar      vectors      (!)      vectors      scalar

$d\vec{s}$  defines direction of  $d\vec{A}$

Conductor loop defines path of integration


$$\frac{d}{dt} \int_A \vec{B} \cdot d\vec{A} = \int_A \frac{\partial \vec{B}}{\partial t} \cdot d\vec{A}$$

Here: for  $\frac{\partial \vec{B}}{\partial t} > 0$ , polarity of "1" is positive

The voltage induced in a conductor loop is proportional to the negative rate of change of the magnetic flux through that loop.

## Lenz's Law


**Figure 1-14** | The meaning of Lenz's law: (a) A coil enclosing an increasing magnetic flux; (b) determining the resulting voltage polarity.

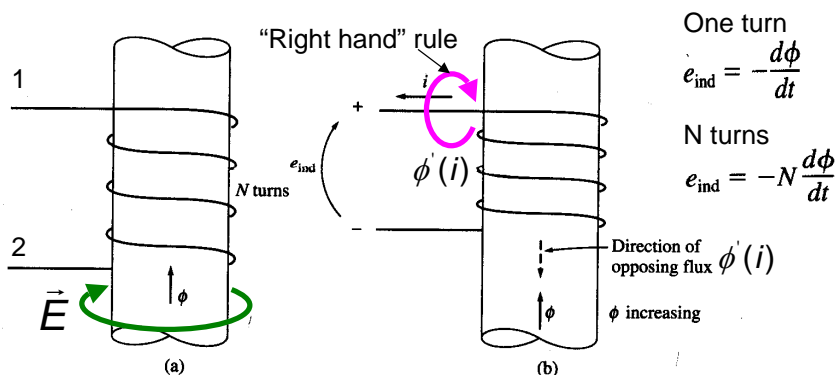

Polarity of  $e_{ind}$  is such that if the terminals were shorted a current  $i$  would flow which creates a flux  $\phi'(i)$  opposing the original flux  $\phi$ .  
 => minus sign often omitted for practical purpose



## Ideal 1~ Transformer Model

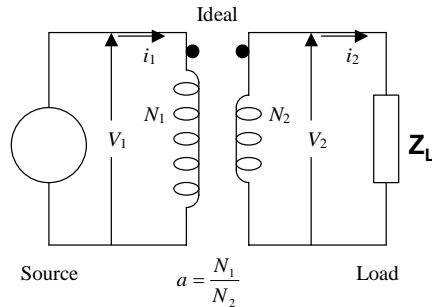

### Flux linkages (winding flux)

$$\lambda_1 = N_1\phi, \quad \lambda_2 = N_2\phi$$

$$v_1 = e_1, \quad v_2 = e_2$$

$$a = \frac{N_1}{N_2} = \frac{v_1}{v_2} = \frac{e_1}{e_2} = \frac{i_2}{i_1}$$

- **Dot convention**

- ◆ Current into dotted end produces positive MMF ( $N \cdot I$ ) or “ampere-turns”
- ◆ Therefore, orientation of  $i_1$  and  $i_2$  must be as shown to cancel MMF which is necessary to maintain a finite flux in an “ideal (iron) core”