

Voltage Regulation


Definition:

$$\text{percent regulation} = \frac{|V_{2,\text{no-load}}| - |V_{2,\text{full-load}}|}{|V_{2,\text{full-load}}|} \times 100$$

Practical Equation:

$$\text{percent regulation} = \frac{|V_1/a| - |V_2|}{|V_2|} \times 100$$

Voltage Regulation

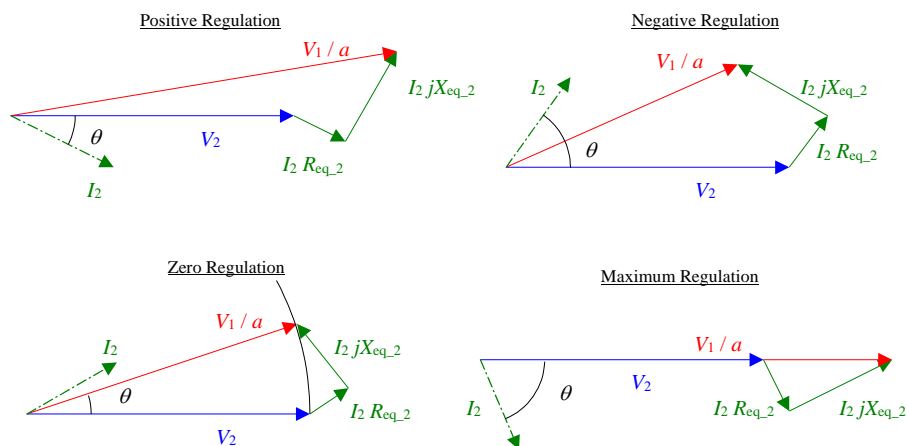

Transformer Efficiency

Definition:

$$\eta = \frac{\text{output power}}{\text{input power}} = \frac{P_2}{P_1}$$

Practical Equation:

$$\eta = \frac{P_1 - P_{\text{losses}}}{P_1} = \frac{P_2}{P_2 + P_{\text{losses}}} = \frac{P_2}{P_2 + P_{\text{copper}} + P_{\text{core}}}$$

Per Unit Equation:

$$\eta = \frac{|S_{2-pu}| \cos \phi}{|S_{2-pu}| \cos \phi + P_{\text{core-pu}} + |S_{2-pu}|^2 R_{\text{eq-pu}}}$$

Example: Voltage regulation

See Book, Example 3-5, p. 119

Per Unit System

- **From generation to the load centers, power systems have ratings and values that cover a large range**
 - ♦ e.g., 100 MVA of generation to 5 kVA loads;
765 kV transmission to 120 V utilization level
- **The per unit system of measurements simplifies the computation and analysis through a system**
- **Various electrical quantities are normalized with respect to a specific base value**
 - ♦ When working in a per unit system, it is important to specify the required base values
 - ♦ Electrical quantities such as voltage, current, power, and impedance are converted to per unit quantities

Per Unit (pu) System

$$pu \text{ value} = \frac{\text{actual value}}{\text{base value of the same dimension}}$$

$$\text{base current} = \frac{\text{base apparent power}}{\text{base voltage}}$$

$$\text{base impedance} = \frac{\text{base voltage}}{\text{base current}}$$

$$\text{per-unit voltage} = \frac{\text{actual voltage}}{\text{base voltage}}$$

$$\text{per-unit current} = \frac{\text{actual current}}{\text{base current}}$$

$$\text{per-unit impedance} = \frac{\text{actual impedance}}{\text{base impedance}}$$

Per Unit System – Y connections, Transmission lines

$$\text{base voltage, } V_{Base} = V_{p-Base} = V_{LL-Base} / \sqrt{3}$$

$$\text{base current, } I_{Base} = \frac{S_{1\phi-Base}}{V_{p-Base}} = \frac{S_{3\phi-Base}/3}{V_{LL-Base}/\sqrt{3}} = \frac{S_{3\phi-Base}}{\sqrt{3} \cdot V_{LL-Base}}$$

$$\text{base impedance, } Z_{Base} = \frac{V_{p-Base}}{I_{Base}} = \frac{V_{LL-Base}/\sqrt{3}}{I_{Base}}$$

$$Z_{Base} = \frac{(V_{p-Base})^2}{S_{1\phi-Base}} = \frac{(V_{LL-Base}/\sqrt{3})^2}{S_{3\phi-Base}/3} = \frac{(V_{LL-Base})^2}{S_{3\phi-Base}}$$

Per Unit System – Δ connection (less commonly used)

$$\text{base voltage, } V_{Base} = V_{LL-Base} = \sqrt{3} \cdot V_{p-Base}$$

$$\text{base current, } I_{Base} = \frac{S_{1\phi-Base}}{V_{LL-Base}} = \frac{S_{3\phi-Base}}{3 \cdot V_{LL-Base}} = \frac{1}{\sqrt{3}} I_{Base-Y}$$

$$\text{base impedance, } Z_{Base} = \frac{V_{LL-Base}}{I_{Base}} = \frac{\sqrt{3} V_{p-Base}}{I_{Base-Y}/\sqrt{3}} = 3 Z_{Base-Y}$$

$$Z_{Base} = \frac{(V_{LL-Base})^2}{S_{1\phi-Base}} = \frac{(V_{LL-Base})^2}{3 \cdot S_{3\phi-Base}} = 3 \cdot Z_{Base-Y}$$

Example

Find the pu impedances for the
Transformer of Example 3-5, p. 119

- a) For 15 kVA power base
- b) For 30 kVA power base

Example (primary side)

$$S_{\text{base}} = 15 \text{ kVA}$$

$$V_{\text{Base},P} = 2300 \text{ V}$$

$$S_{\text{base}} = 30 \text{ kVA}$$

$$Z_{\text{Base},P} = \frac{V_{\text{Base},P}^2}{S_{\text{Base}}} = \frac{2300^2}{15000} = 352.7 \Omega \quad Z_{\text{Base},P} = \frac{V_{\text{Base},P}^2}{S_{\text{Base}}} = \frac{2300^2}{30000} = 176.4 \Omega$$

$$R_{C,P,pu} = \frac{105.8 \text{ k}\Omega}{Z_{\text{Base},P}} = 300 \text{ pu}$$

S_{base} is
independent of
primary and
secondary side

$$R_{C,P,pu} = 600 \text{ pu}$$

$$X_{m,P,pu} = j \frac{11 \text{ k}\Omega}{Z_{\text{Base},P}} = j31 \text{ pu}$$

$$X_{m,P,pu} = j62 \text{ pu}$$

$$X_{eq,P,pu} = j \frac{6.45 \Omega}{Z_{\text{Base},P}} = j0.0183 \text{ pu} = j1.83\% \text{ pu} \quad X_{eq,P,pu} = j3.66\% \text{ pu}$$

$$R_{eq,P,pu} = \frac{4.45 \Omega}{Z_{\text{Base},P}} = 0.0126 \text{ pu} = 1.26\% \text{ pu}$$

$$R_{eq,P,pu} = 3.52\% \text{ pu}$$

Example (secondary side)

$S_{\text{base}} = 15 \text{ kVA}$	$V_{\text{Base},S} = 230 \text{ V}$	$S_{\text{base}} = 30 \text{ kVA}$
$Z_{\text{Base},S} = \frac{V_{\text{Base},S}^2}{S_{\text{Base}}} = \frac{230^2}{15000} = 3.527 \Omega$	$Z_{\text{Base},S} = \frac{V_{\text{Base},S}^2}{S_{\text{Base}}} = \frac{230^2}{30000} = 1.763 \Omega$	
$R_{C,S,pu} = \frac{1058 \Omega}{Z_{\text{Base},S}} = 300 \text{ pu}$	S_{base} is independent of primary and secondary side	$R_{C,S,pu} = 600 \text{ pu}$
$X_{m,S,pu} = j \frac{110 \Omega}{Z_{\text{Base},S}} = j31 \text{ pu}$		$X_{m,S,pu} = j62 \text{ pu}$
$X_{eq,S,pu} = j \frac{64.5 \text{ m}\Omega}{Z_{\text{Base},S}} = j0.0183 \text{ pu} = j1.83\% \text{ pu}$		$X_{eq,S,pu} = j3.66\% \text{ pu}$
$R_{eq,S,pu} = \frac{44.5 \text{ m}\Omega}{Z_{\text{Base},S}} = 0.0126 \text{ pu} = 1.26\% \text{ pu}$		$R_{eq,S,pu} = 3.52\% \text{ pu}$

Homework 3

See web site

<http://www.eng.fsu.edu/~steuerer/eel3216.html>

Problems 3-1 through 3-4 and 3-6 through 3-8 in book.