

## Changing Bases

---

- The impedances of generators, transformers, transmission lines, and loads are supplied by the manufacturers in per unit based on the equipment's own rating.
- When placing the equipment into a system, the impedance must be converted to the system base

$$Z_{pu} = \frac{Z_{p-Actual}}{Z_{Base}} = \frac{(Z_{p-Actual})(S_{3\phi-Base})}{(V_{LL-Base})^2}$$

$$Z_{new-pu} = Z_{old-pu} \left( \frac{S_{3\phi-Base-new}}{S_{3\phi-Base-old}} \right) \left( \frac{V_{LL-Base-old}}{V_{LL-Base-new}} \right)^2$$

**Only within one voltage zone!**

## Changing Bases

---

- Voltage, current, and impedance base values change at transformers as they step the voltage up or down.
- The power base remains the same across a transformer
- The pu values of impedance, voltage, and current across a transformer is independent of the reference side: primary or secondary

## Example

A one-line diagram of a three-phase power system is shown. Draw the impedance diagram of the power system, and mark all impedances in per unit. Use a base of 100 MVA and 138 kV for the transmission lines. All transformers are connected to step up the voltage of the generators to the transmission line voltages. Calculate the terminal voltage of G2 (in pu) if G1 is out of service and the motor draws 50 MW of power with 1 pu voltage at its terminals.

**Equipment Ratings:**

G1: 45 MVA 13.2 kV  $X_g = 0.15$  pu

G2: 55 MVA 18 kV  $X_g = 0.12$  pu

Motor : 75 MW, PF=1, 11.6 kV  $X_g = 0.23$  pu

T1: 50 MVA 13.8 / 138 kV  $X_t = 0.10$  pu


T2: 60 MVA 19.05 / 138 kV  $X_t = 0.10$  pu

T3: 70 MVA 138 / 11.6 kV  $X_t = 0.10$  pu


Line #1:  $Z_{TL} = j40 \Omega$

Line #2:  $Z_{TL} = j20 \Omega$

Line #3:  $Z_{TL} = j15 \Omega$

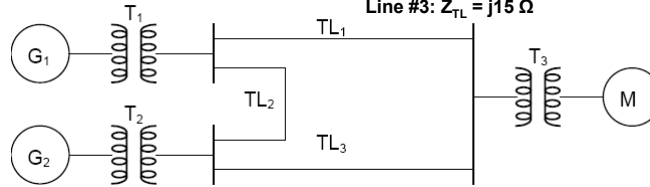

## Example (cont)

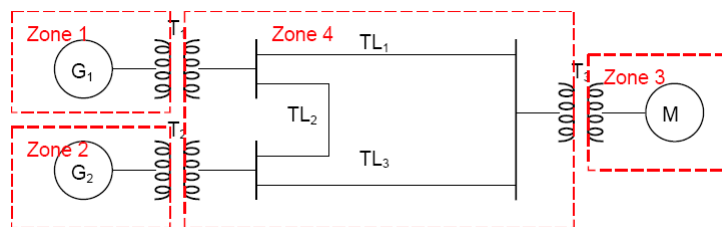

**Voltage Zones:**

Zone 1:  $V_{Base} = 13.8$  kV  $S_{Base} = 100$ MVA

Zone 2:  $V_{Base} = 19.05$  kV  $S_{Base} = 100$ MVA

Zone 3:  $V_{Base} = 11.6$  kV  $S_{Base} = 100$ MVA

Zone 4:  $V_{Base} = 138$  kV  $S_{Base} = 100$ MVA

## Example (cont)

Impedances:

$$Z_{G1} = j0.15 \left( \frac{100 \text{ MVA}}{45 \text{ MVA}} \right) \left( \frac{13.2 \text{ kV}}{13.8 \text{ kV}} \right)^2 = j0.305 \text{ pu}$$

$$Z_{G2} = j0.12 \left( \frac{100 \text{ MVA}}{55 \text{ MVA}} \right) \left( \frac{18 \text{ kV}}{19.05 \text{ kV}} \right)^2 = j0.195 \text{ pu}$$

$$Z_M = j0.23 \left( \frac{100 \text{ MVA}}{75 \text{ MVA}} \right) \left( \frac{11.6 \text{ kV}}{11.6 \text{ kV}} \right)^2 = j0.307 \text{ pu}$$

$$Z_{T1} = j0.10 \left( \frac{100 \text{ MVA}}{50 \text{ MVA}} \right) \left( \frac{138 \text{ kV}}{138 \text{ kV}} \right)^2 = j0.200 \text{ pu}$$

$$Z_{T2} = j0.10 \left( \frac{100 \text{ MVA}}{60 \text{ MVA}} \right) \left( \frac{138 \text{ kV}}{138 \text{ kV}} \right)^2 = j0.167 \text{ pu}$$

$$Z_{T3} = j0.10 \left( \frac{100 \text{ MVA}}{70 \text{ MVA}} \right) \left( \frac{138 \text{ kV}}{138 \text{ kV}} \right)^2 = j0.143 \text{ pu}$$


$$Z_{TL1} = \frac{j40 \Omega}{190.4 \Omega} = j0.210 \text{ pu}$$

$$Z_{TL2} = \frac{j20 \Omega}{190.4 \Omega} = j0.105 \text{ pu}$$


$$Z_{TL3} = \frac{j15 \Omega}{190.4 \Omega} = j0.0788 \text{ pu}$$

$$Z_{Base} = \frac{(138 \text{ kV})^2}{100 \text{ MVA}} = 190.4 \Omega$$

## Example (cont)

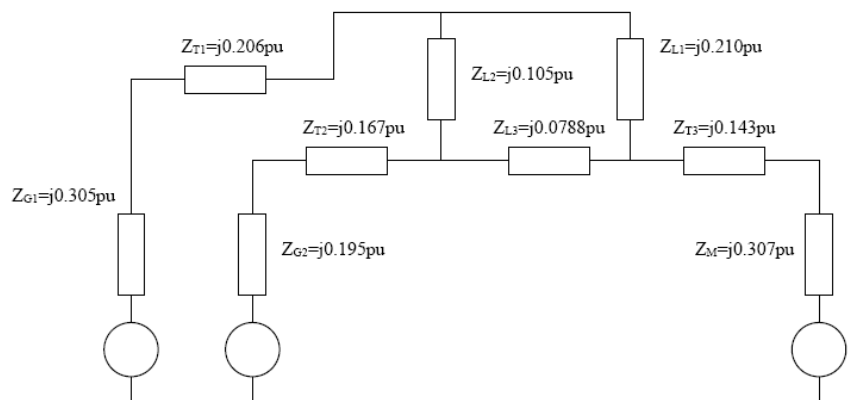

## Example (cont)

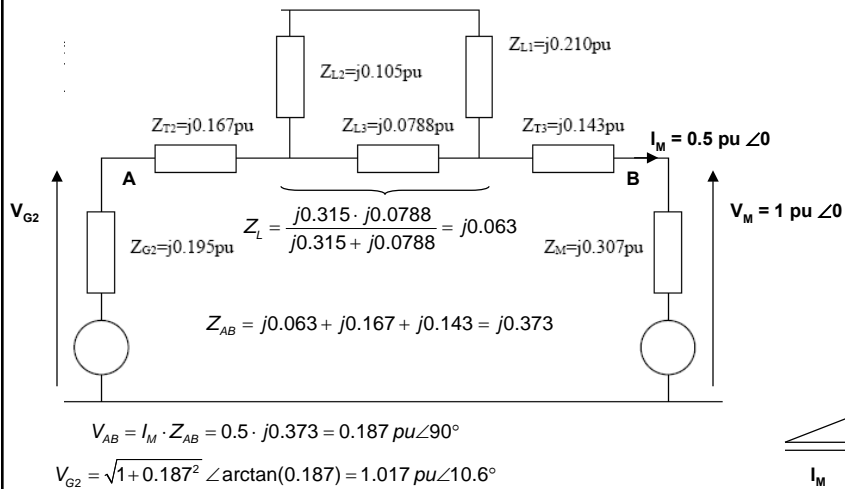


## Load Calculations and Transformer Sizing

- Load calculations determine the expected apparent power,  $S$ , of the load
- The expected load power is used to specify the power rating of the transformer
- Load balancing
  - ◆ Single phase systems
    - three wire - 120 / 240 V residential service
  - ◆ Three phase systems
    - grounded-wye connection, four wire service
    - floating-wye connection, three wire service
    - delta connection, three wire service



## Transformer Applications

- **Single-phase overhead transformers**

- ◆ single-bushing type

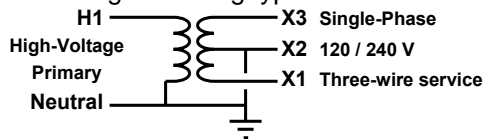


- ◆ two-bushing type

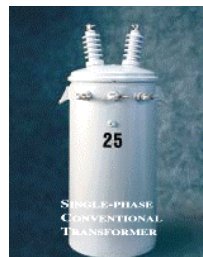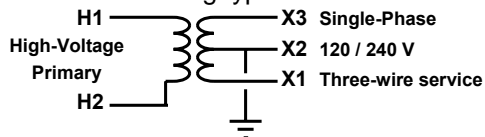
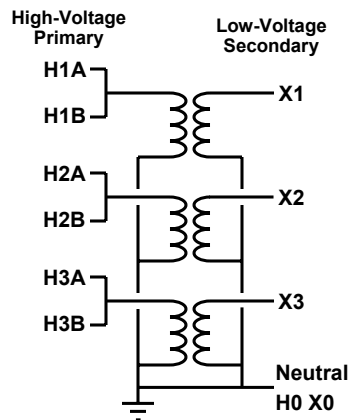
## Transformer Applications

- **Three-phase pad-mounted transformers**



## Standard Transformer Ratings

---

- Overhead pole-type transformers

Single-phase (kVA)	Three-phase (kVA)
10	30
25	45
37.5	75
50	112.5
75	150
100	225
167	300
250	500
333	
500	

## Example

---

A single-phase pole-mount transformer is to be used to supply the following estimated loads:

Load 1: 7 kW, 0.9 pf lagging, @ 120 V

Load 2: 12 kW, 0.9 pf lagging, @ 240 V

Load 3: 5 kW, 0.9 pf lagging, @ 120 V

Load 4: 23 kW, 0.8 pf lagging, @ 240 V

demand factor of all four loads: 0.72

The power distribution is one phase of a 12.47 kV, three-phase system. Specify the transformers voltage and power rating.

## Example

---

$$V_{LL} = 12,470 \text{ V} \quad E_1 = V_{LN} = \frac{V_{LL}}{\sqrt{3}} = \frac{12,470}{\sqrt{3}} = 7200 \text{ V}$$

$$E_2 = 120 / 240 \text{ V}$$

$$P_1 = 7 \text{ kW} \quad Q_1 = 3.4 \text{ kVAr} \quad Q = P \frac{\sqrt{1 - PF^2}}{PF} = P \sqrt{1 / PF^2 - 1}$$

$$P_2 = 12 \text{ kW} \quad Q_2 = 5.8 \text{ kVAr}$$

$$P_3 = 5 \text{ kW} \quad Q_3 = 2.4 \text{ kVAr}$$

$$P_4 = 23 \text{ kW} \quad Q_4 = 17.25 \text{ kVAr}$$

$$S_{load} = (S_1 + S_2 + S_3 + S_4) \cdot df = (47 + j28.9 \text{ kVA}) \cdot 0.72$$

$$S_{load} = (55.1 \text{ kVA}) \cdot 0.72 = 39.7 \text{ kVA}$$

$$S_{xfmr\_rating} > 39.7 \text{ kVA}$$

a 12,470GrdY / 7,200V : 120 / 240V,  
50 kVA transformer is required

## Homework 4

---

See web site

<http://www.eng.fsu.edu/~steuerer/eel3216.html>

Problems

3-10

3-22

in book

plus two extra problems