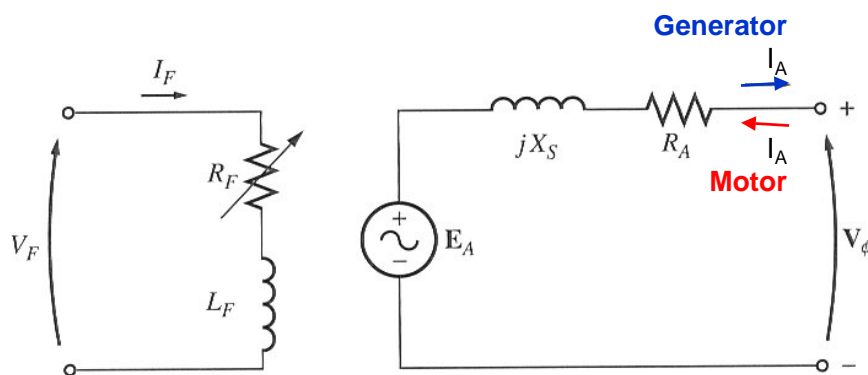


Electric Motors

- **Three basic types of motors**
 - ◆ Synchronous, SM
 - ◆ Induction (asynchronous), IM
 - ◆ DC motors
 - In the past: preferred for variable speed applications
 - Decreasing in popularity; replaced by combination of IM and power electronic variable speed drive (VSD)
- **Applications**
 - ◆ SM: largest power ratings, e.g. pumps for hydro power plant, electric ship propulsion, steel mills (with VSD)
 - ◆ IM: “workhorse” of the power industry, from fractional kW to MW ratings, e.g. air conditioner (compressor, fan), elevator, crane, electric vehicle (with VSD)
 - ◆ DC: low power, pure DC applications such as cars, also universal motor (for DC and AC),


Synchronous Motor (SM)




Generator: source convention, positive power leaves the machine

Motor: load convention, positive power enters the machine


Synchronous Motor (SM)

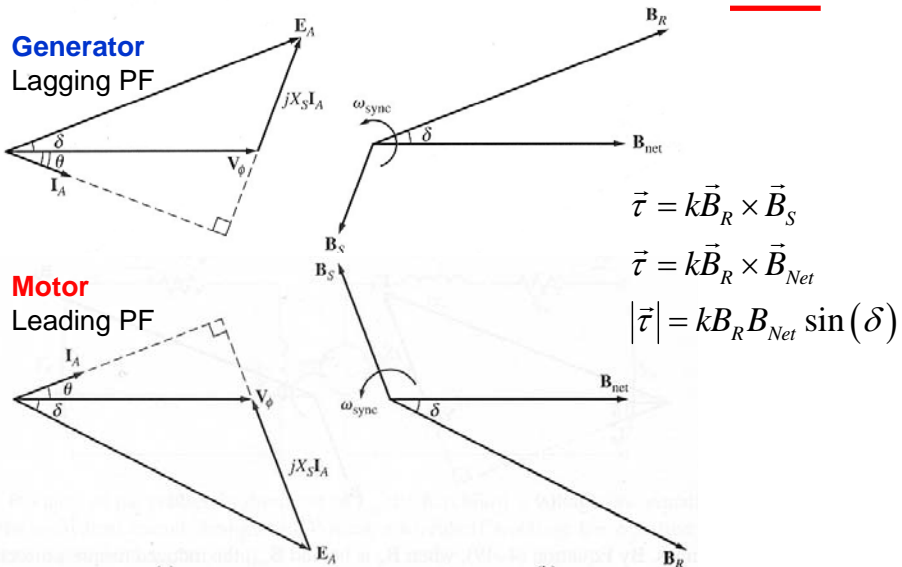

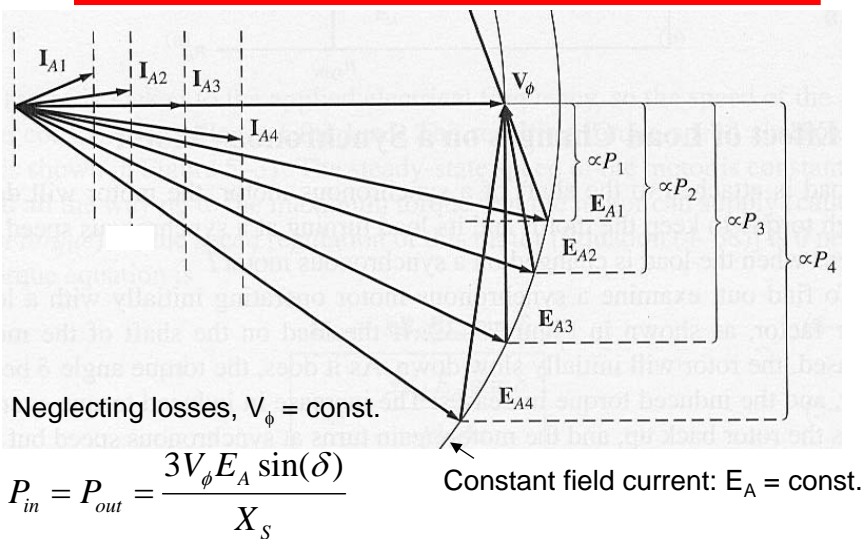
SM Loading Characteristic, $I_F = \text{const}$



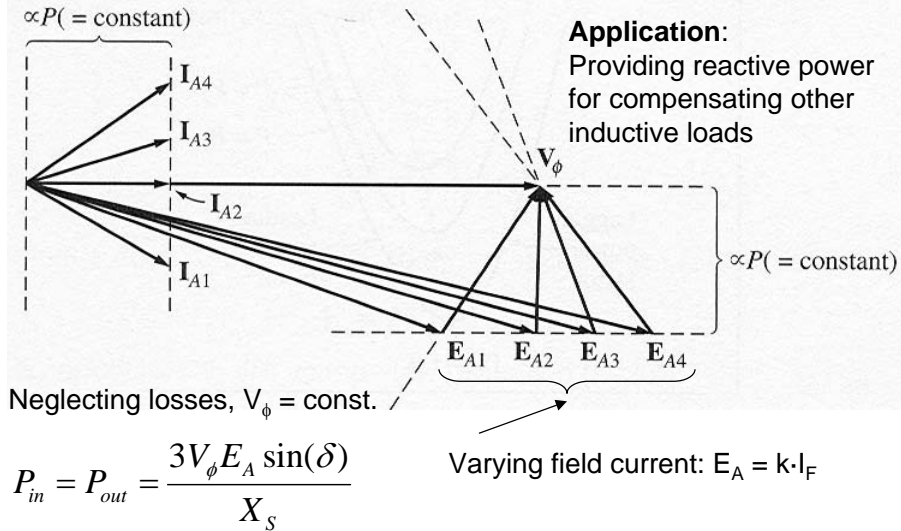
SM Reactive Power Characteristic, P = const



SM Torque-Speed Characteristic

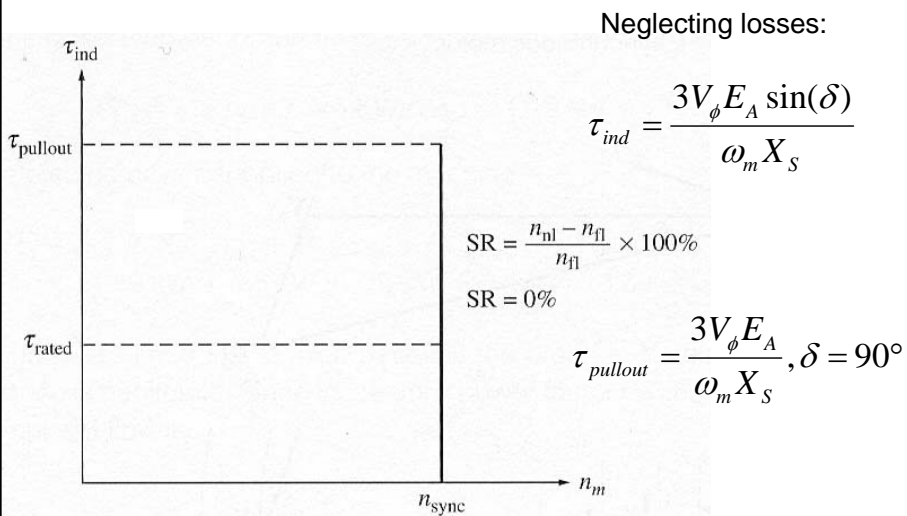

Induction (asynchronous) Motor (IM)

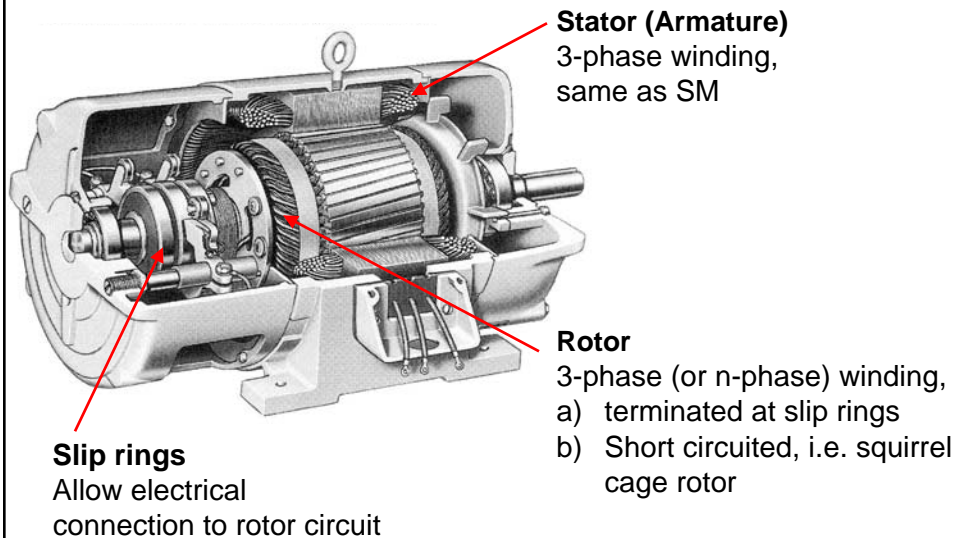

Fundamentals of Power Systems

Lecture 17

7

Induction (asynchronous) Motor (IM)

- Balanced 3-phase stator currents produce a magnetic field of constant magnitude B_S which rotates with the synchronous speed ω_{sync}
- If the rotor is not rotating (still stand, or locked rotor) a voltage E_{LR} of frequency

$$f_e = \frac{\omega_{sync}}{2\pi} \quad \text{Provided: same number of poles in stator and rotor}$$

is induced in the rotor winding

- If the rotor is rotating with a speed ω_m different from ω_{sync} a voltage

$$E_R = \frac{\omega_{sync} - \omega_m}{\omega_{sync}} E_{LR}$$

is with frequency

$$f_R = \frac{\omega_{sync} - \omega_m}{2\pi} = \frac{\omega_{sync} - \omega_m}{\omega_{sync}} f_{sync}$$


induced in the rotor winding

Fundamentals of Power Systems

Lecture 17

8

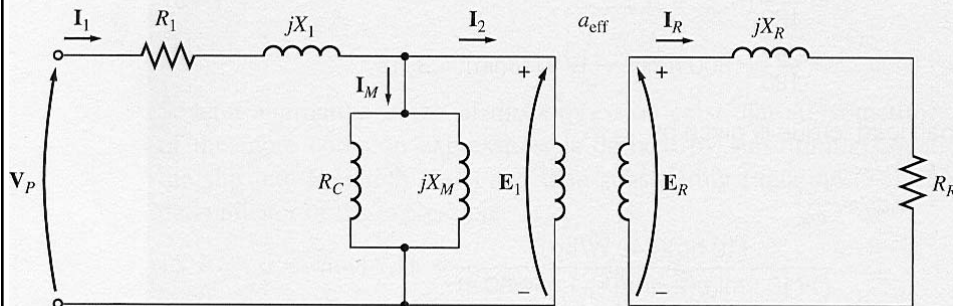IM – Developing a Single-phase Equivalent Circuit Model



Stator circuit

- Winding resistance and reactance
- Magnetizing branch (magnetization provided by stator only!)

Stator \leftrightarrow Rotor

- Effective turns ratio
 $E_{LR}/E_1 = a_{\text{eff}}$
- Ratio E_R/E_1 scales with rotor speed
- Change of frequency!

Rotor circuit

- Winding resistance and reactance

IM – The Concept of Slip

- The slip s is the relative (normalized) frequency in the rotor circuit

$$s = \frac{\omega_{\text{sync}} - \omega_m}{\omega_{\text{sync}}}$$

- Locked rotor: $s = 1$
- Rotor slower than synchronous speed: $1 > s > 0$
- Rotor at synchronous speed: $s = 0$
- Rotor faster than synchronous speed $s < 0$
- Rotor speed reversal: $s > 1$

- The electrical frequency in the rotor becomes


$$f_R = s \cdot f_e$$

- The mechanical speed of the rotor becomes


$$\omega_m = (1 - s)\omega_{\text{sync}}, \quad n_m = (1 - s)n_{\text{sync}}$$

IM – Equivalent rotor circuits (rotor short circuited)

Frequency of I_R : f_R , rotor

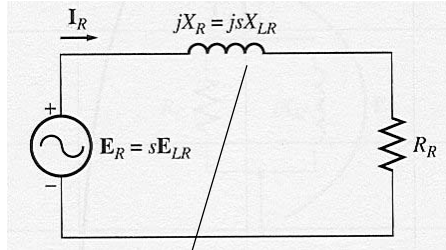


Frequency of I_R : f_e , stator

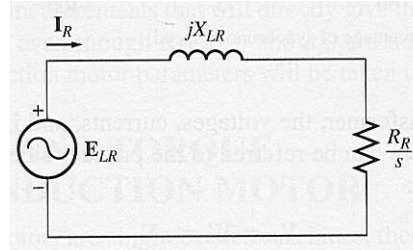

The **inductance** and **resistance** values are constant (independent of the rotor frequency, except for skin effects).

The rotor **reactance**, however, scales with the rotor frequency and thus with the slip!

IM – Equivalent Circuit Model

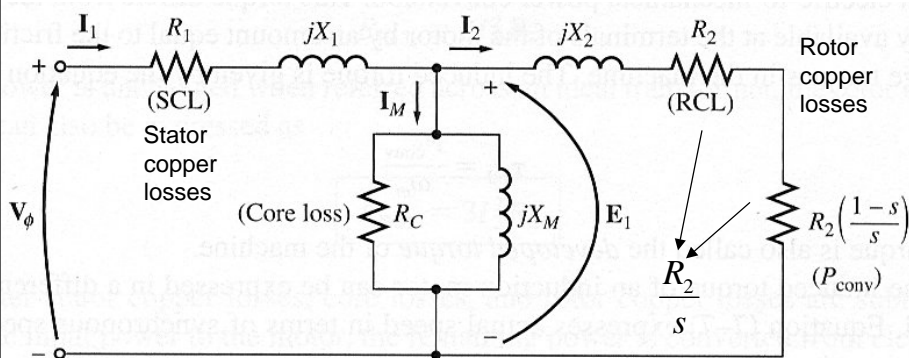

All rotor quantities are referred to the stator side

$$R_2 = a_{eff}^2 R_R$$


$$X_2 = a_{eff}^2 X_{LR}$$

$$P_{conv} = 3I_2^2 R_2 \left(\frac{1-s}{s} \right)$$


represents converted mechanical power

IM – Power Flow
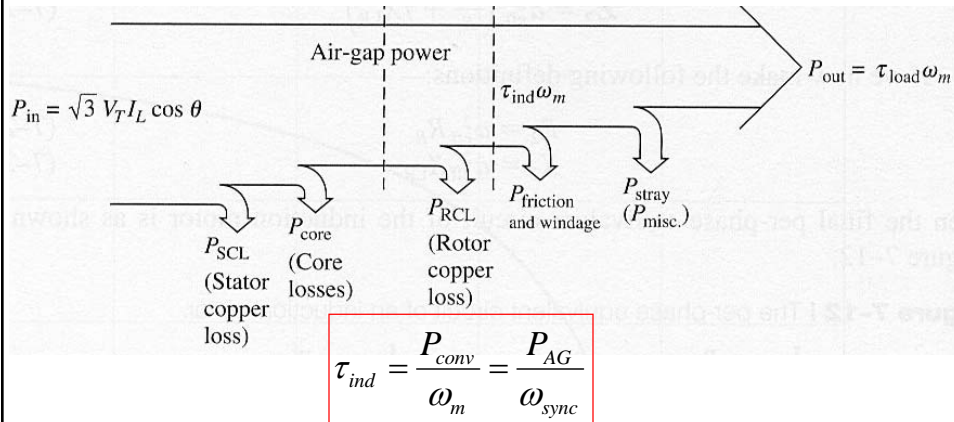
$$P_{AG} = 3I_2^2 R_2 \frac{1}{s} \quad P_{conv} = 3I_2^2 R_2 \left(\frac{1-s}{s} \right)$$



IM – Characteristics

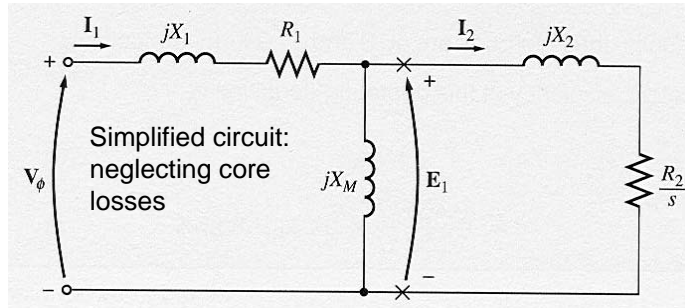

IM – Characteristics


$$\tau_{ind} = \frac{3V_{TH}^2}{\omega_{sync}} \frac{R_2/s}{(R_{TH} + R_2/s)^2 + (X_{TH} + X_2)^2}$$

$$\frac{R_2}{s_{max}} = |R_{TH} + j(X_{TH} + X_2)| = \sqrt{R_{TH}^2 + (X_{TH} + X_2)^2}$$


$$s_{max} = \frac{R_2}{\sqrt{R_{TH}^2 + (X_{TH} + X_2)^2}}$$

$$\tau_{max} = \frac{3V_{TH}^2}{2\omega_{sync}} \frac{1}{R_{TH} + \sqrt{R_{TH}^2 + (X_{TH} + X_2)^2}}$$

IM – Torque-Speed Characteristic

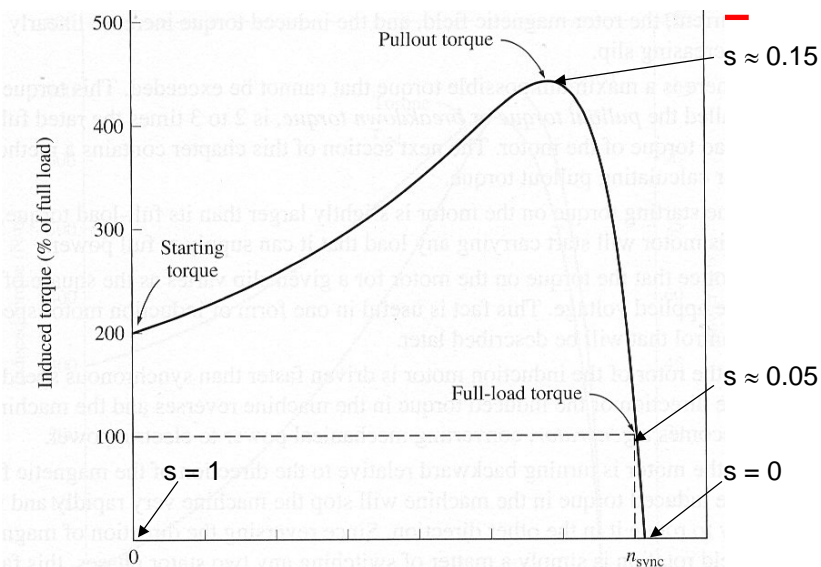

IM – Torque-Speed Characteristic

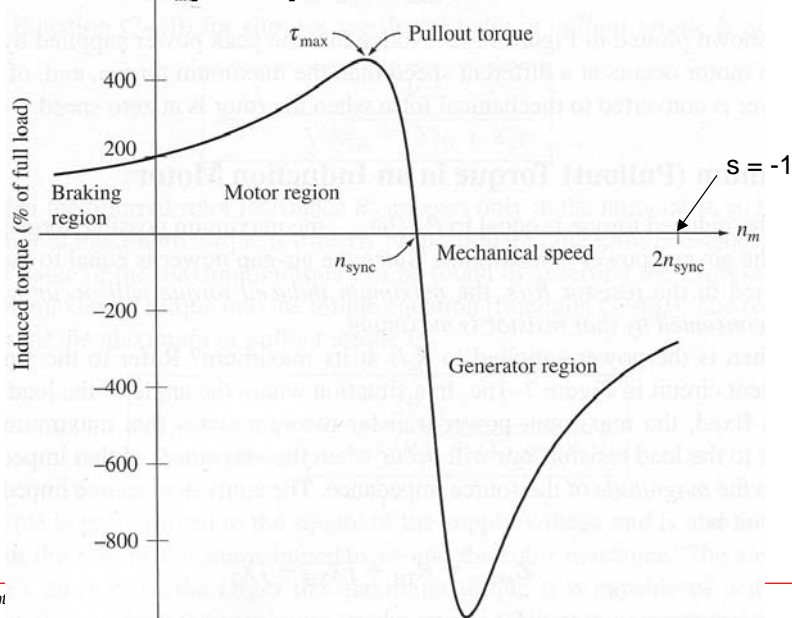

HW 10

Problem 5-29 in book