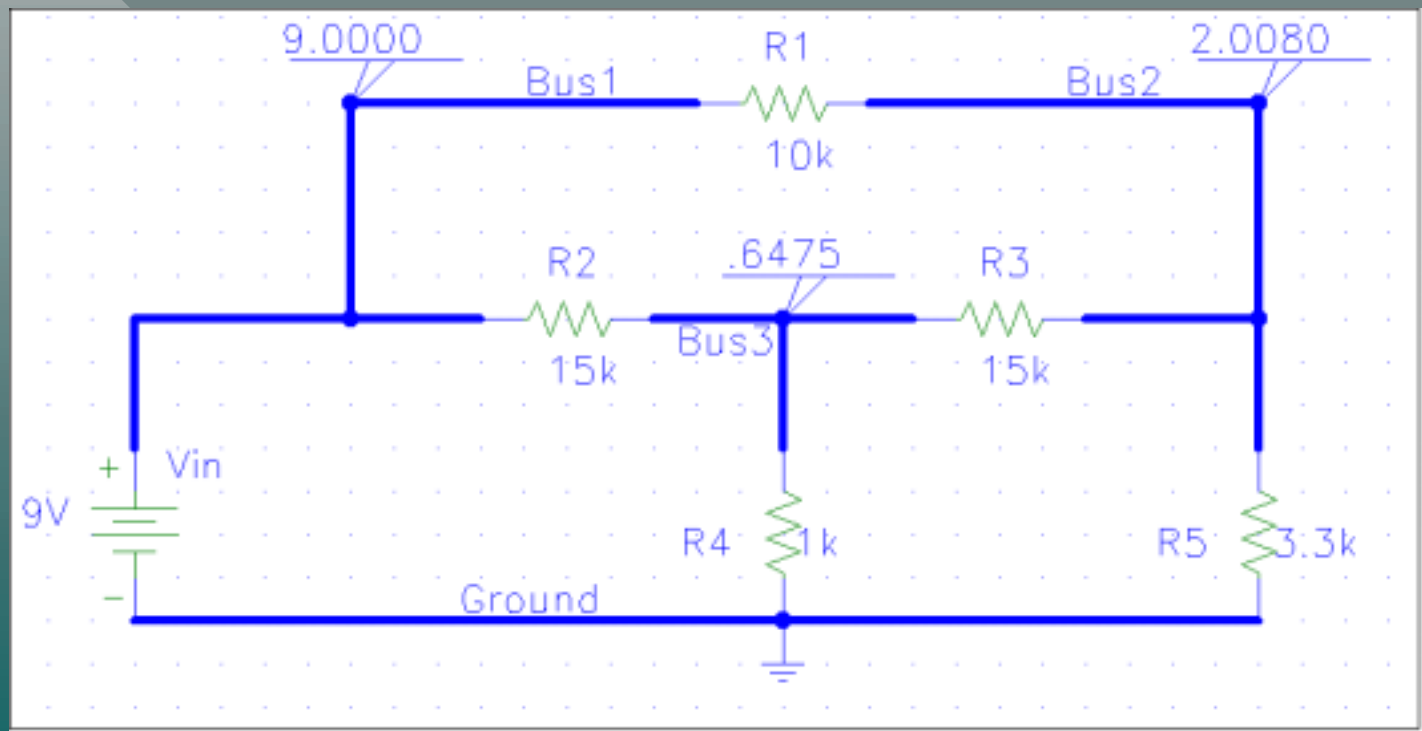


Introduction to MatLab: Circuit Analysis



Introduction


- MatLab can be a useful tool in many applications.
- We will learn how to analyze a simple electrical circuit, set the problem up as N equations in N unknowns, and transform the equations into a matrix formulation that MatLab can solve.

Topics

- Electrical Devices.
- Kirchhoff's Laws.
- Analyzing a Resistor Network.
- Inverting Matrices.
- A MatLab Solution.

Electrical Devices

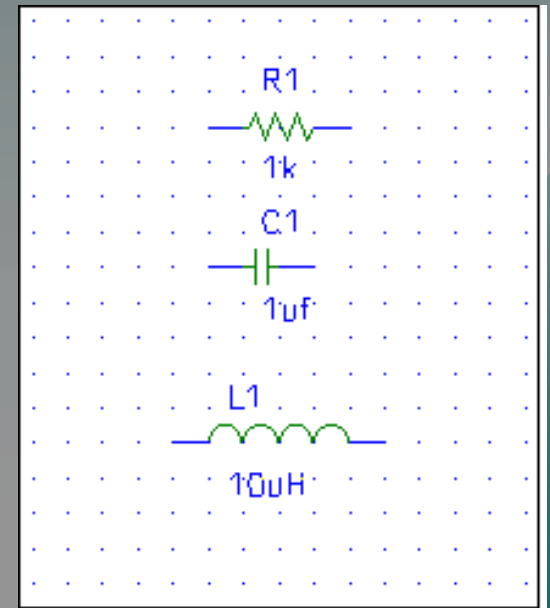- Voltage and Current.
- Sources.
- Resistors: Ohms Law.
- Capacitors: Charge Storage.
- Inductors: Current Storage.



Voltage and Current

- Voltage - the force that pushes electrical current around a circuit. (Sometimes called "potential" as in potential energy.)
- Current - the flow of electrical charge through a conductor. (Electrons flow backwards)
- Conductor - the "pipe" through which an electrical current flows.

Sources

- Voltage Source: Fixed Voltage waveform
 - Direct Current: A battery
 - Alternating Current: A generator (sine waves)
- Current Source: Fixed current waveform (AC or DC)

Resistors

- A constriction in the flow of current
- Analogous to a small orifice in a water pipe, it takes a high pressure (voltage) to force a flow of water (current) through the resistance.
- Ohm's Law
 $V = I * R$

Resistor Color Codes

- First two stripes: Digits
- Third stripe: Power of 10
- Fourth stripe: Precision
(none - 20%, silver - 10%, gold - 5%)

0 - Black

5 - Green

1 - Brown

6 - Blue

2 - Red

7 - Violet

3 - Orange

8 - Gray

4 - Yellow

9 - White

Capacitors

- A charge storage device
- Analogous to a water tank that is filled from the bottom. As the water level rises (charge divided by the cross sectional area – capacitance), the pressure (voltage) rises.
- Capacitor Law
 $V=Q/C$


Inductors

- A current storage device
- Analogous to the inertial effect of the flow of a fluid. The inductance is the mass that is moving.
- Inductor Law
 $V=L \cdot di/dt$ (di/dt is the “rate of change” in the current. This is analogous to velocity.)

Kirchhoff's Laws

- Conservation of Current:
The sum of all currents into a “node” equals zero.
- Loop Law:
The sum of all voltages around a loop equals zero.

A Resistor Network

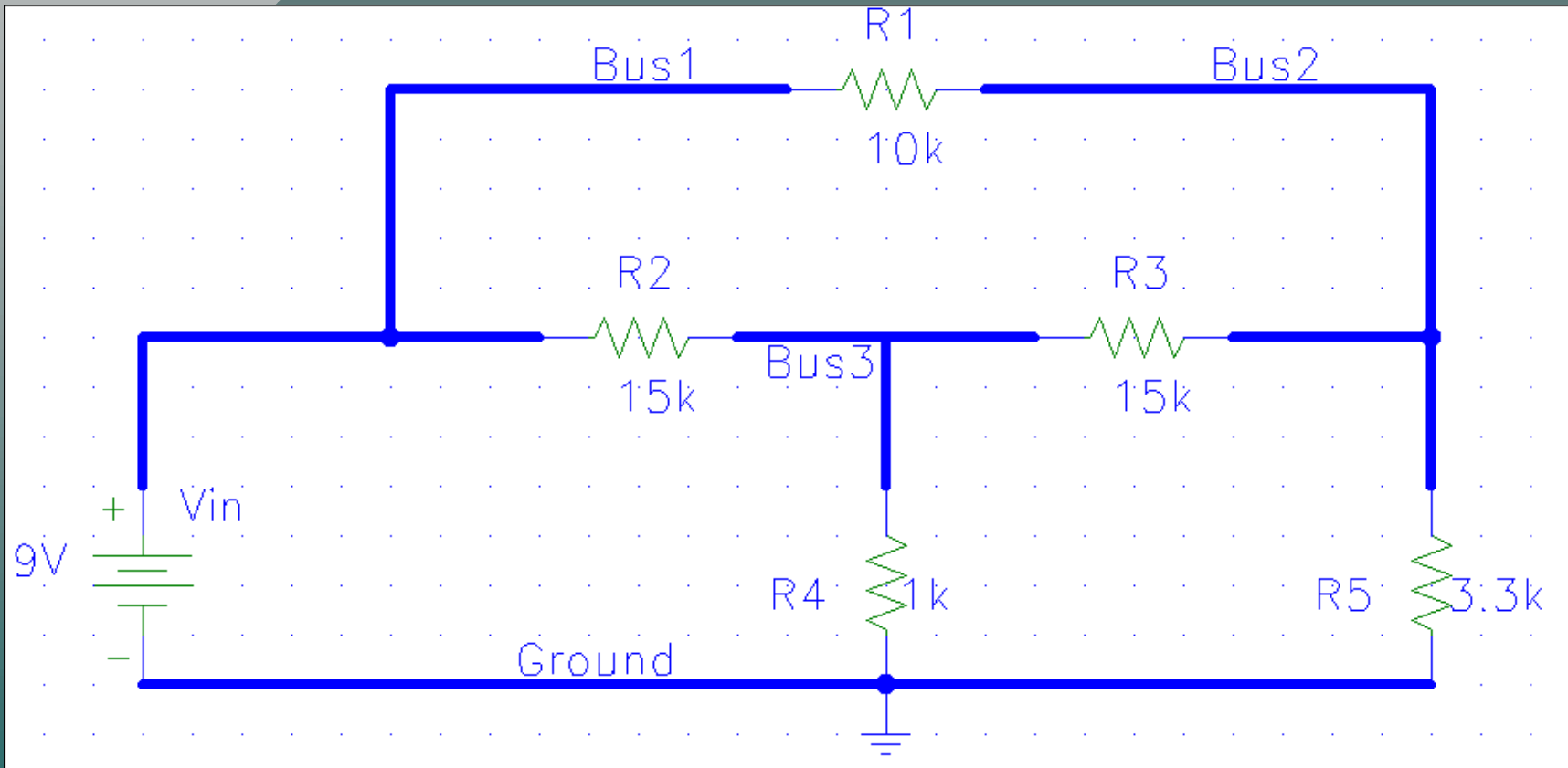

Measurements

- Multimeter (Analog and Digital)
- Voltage - measured relative to a reference, usually electrical ground.
- Resistance - meter puts a small current through the resistor and uses Ohm's law.
- Current - careful, the meter can be destroyed by an over-current.

Loop Equations

- Establish Independent Loop Currents
- Write Equation for Each Loop
 - Determine voltages in terms of the loop currents.
 - Sum to zero

(note: Alternative, use a set of "Node" equations)

Our Circuit – First Step

$$9v = 15k^*(I_1 - I_2) + 1k^*(I_1 - I_3)$$

$$0 = 10k^*I_2 + 15k^*(I_2 - I_1) + 15k^*(I_2 - I_3)$$

$$0 = 1k^*(I_3 - I_1) + 15k^*(I_3 - I_2) + 3.3k^*I_3$$

Our Circuit – Collecting Terms

$$9v = 16k \cdot I_1 - 15k \cdot I_2 - 1k \cdot I_3$$

$$0 = -15k \cdot I_1 + 40k \cdot I_2 - 15k \cdot I_3$$

$$0 = -1k \cdot I_1 - 15k \cdot I_2 + 19.3k \cdot I_3$$

Vectorizing N Equations

- Rewrite, ordering variables
- Formulate equivalent as an input column vector equals a coefficient matrix times an “unknowns” vector
- Solution: pre-multiply both sides by the inverse of the coefficient matrix.

Our Circuit – Vector Equation

$$\begin{bmatrix} 9\text{v} \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 16\text{k} & -15\text{k} & -1\text{k} \\ -15\text{k} & 40\text{k} & -15\text{k} \\ -1\text{k} & -15\text{k} & 19.3\text{k} \end{bmatrix} * \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

Inverting Matrices

- The inverse of a square matrix is that matrix which, when multiplied by the original matrix yields the Identity matrix
- In MatLab use "inv()".

Our Circuit – Inverse Matrix

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0.1396 & 0.0777 & 0.0676 \\ 0.0777 & 0.0785 & 0.0651 \\ 0.0676 & 0.0651 & 0.1059 \end{bmatrix} * \begin{bmatrix} 9 \\ 0 \\ 0 \end{bmatrix} * 10^{-3}$$

Our Circuit – Currents

I_1		1.256	
I_2	=	0.6992	* 10^{-3} amps
I_3		0.6085	

Intro To PSpice

- Originally from Microsim, now part of OrCad.
- Demo/student CDROM is free at www.orcad.com, current version is 9.2, Limited to small circuits and part library.
- Graphical simulation of circuits and automated Printed Circuit board layout.

Introduction to MatLab: Circuit Analysis

