

Electron Flow and Resistance: Ohm's (Ω) and Kirchoff's Laws

Session 1c of Basic Electricity
A Fairfield University E-Course
Powered by LearnLinc

Basic Electricity

Two Sections

- Electron Flow and Resistance
 - 5 on-line sessions
 - Lab
- Inductance and Capacitance
 - 5 on-line sessions
 - Lab

Mastery Test, Part 1

Basic Electricity (Continued)

- **Text:** “Electricity One-Seven,” Harry Mileaf, Prentice-Hall, 1996, ISBN 0-13-889585-6 (Covers several Modules and more)
- **References:**
 - “Digital Mini Test: Principles of Electricity Lessons One and Two,” SNET Home Study Coordinator, (203) 771-5400
 - [Electronics Tutorial](#) (Thanks to Alex Pounds at alex_tb@hotmail.com)
 - [Electronics Tutorial](#) (Thanks to Mark Sokos at sokos@desupernet.net)

Section 1:

Electron Flow and Resistance

- **OBJECTIVES:** This section introduces five basic electrical concepts as well as the underlying atomic structure of electrical materials.
 - Conductance(G),
 - Resistance (R),
 - Current (I),
 - Power (P), and
 - Electromotive force (E) or voltage (V).

Section 1 Schedule:


Session a – 03/04 <i>03/06 & 03/08 were Math Tutorials</i>	Atoms, Charge and Current Conductivity (G), Electric Fields and Electromotive Force (EMF)	Text 1.1 – 1.39 Text 1.40 – 1.68
Session b – 03/11	Resistance (R), Conductance (G), Ohms Law (Ω) & Power (Watts)	Text 2.1 – 2.52
Session c – 03/13 (lab - 03/16, sat.)	Resistors in Series and Parallel and Working with Equations	Text 2.53 – 2.98
Session d – 03/18	Series / Parallel Simplification Kirchoff, Thevenin & Norton	2.99 – 2.115 2.116 – 2.133
Session e – 03/20	Review: The Water Model	1.42, 1.63, 2.5, 2.129 Sokos

Session 1b Review

- Circuits
 - Open
 - Closed
- Switches
- Direct Current (DC) vs. Alternating Current (AC)
- Conductors
- Resistors and the Color Code
- Power (Voltage * Current)

Resistors in Series

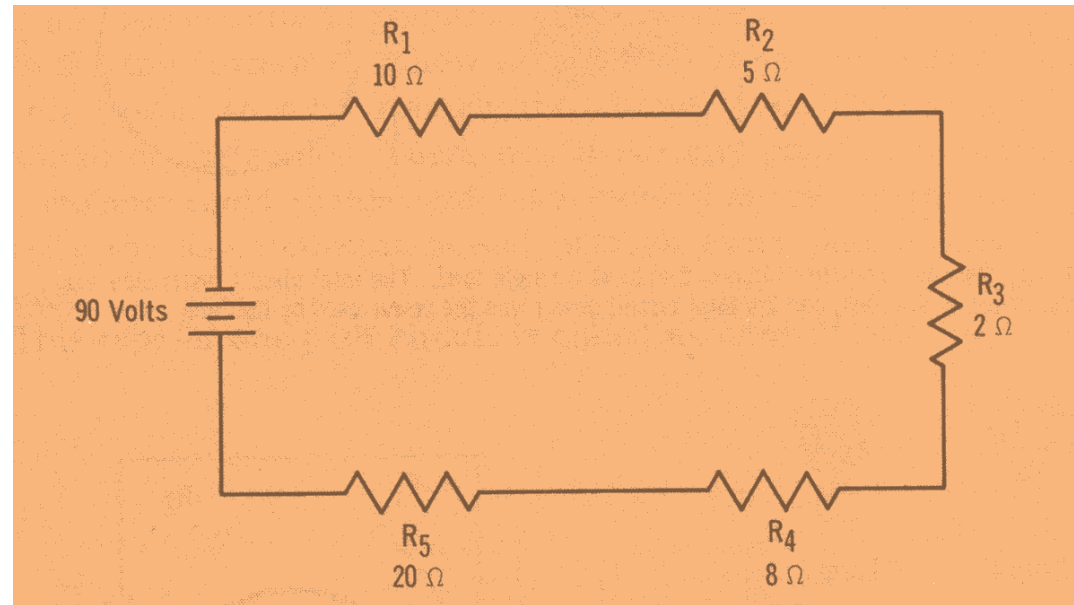- The same current passes through each series resistor
- The voltage “divides” among the resistors
- $90 = I * (10 + 5 + 2 + 8 + 20)$
- $R_{\text{total}} = 10 + 5 + 2 + 8 + 20$
- $R_{\text{total}} = 45$
- **Series resistors add**




Voltage Sources in Series

- Series voltages add (watch the \pm signs)




Adding up Total Power

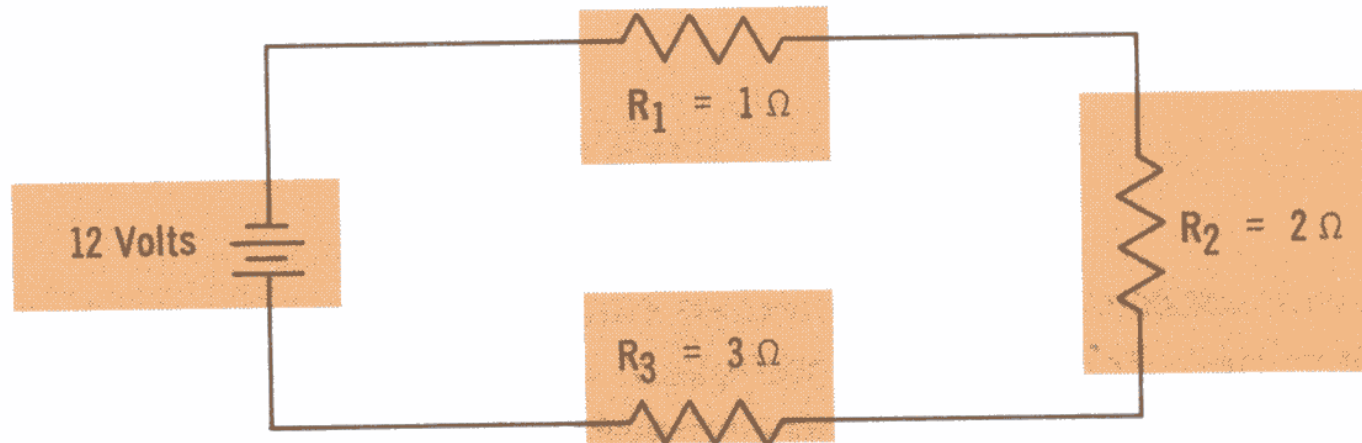- $P = P_1 + P_2 + P_3$
- $12 = I * 1 + I * 2 + I * 3$
- $12 = I * (1 + 2 + 3)$
- $12 = 6 * I$
- $I = 2$ amps
- $P_n = I * V_n = I^2 * R_n$
- $P = 2^2 * (1 + 2 + 3)$
- $P = 24$ watts




Voltage Drops

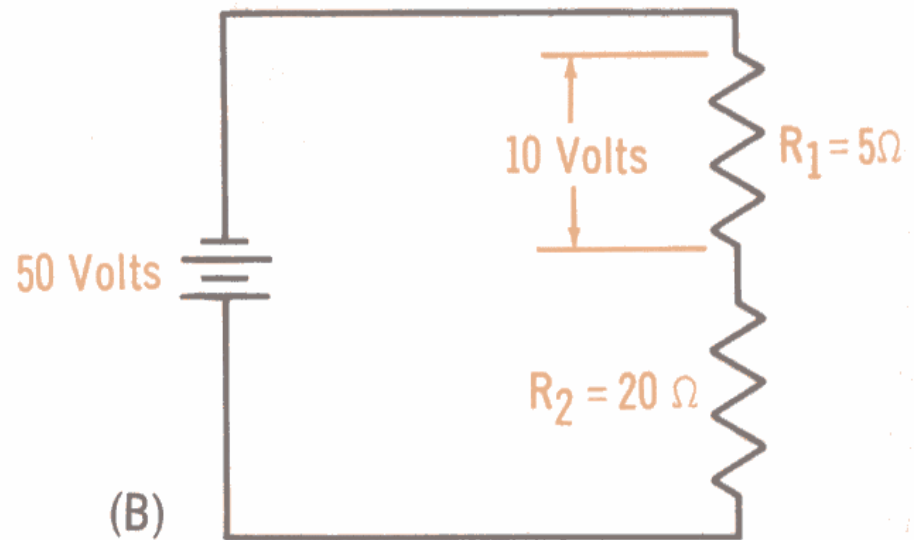- $R_{\text{total}} = 25\Omega$
- $I = 50/25 = 2$ amps
- $V_1 = 2 * 5 = 10$ volts
- $V_2 = 2 * 20 = 40$ volts
- **The voltage drops add to 50**



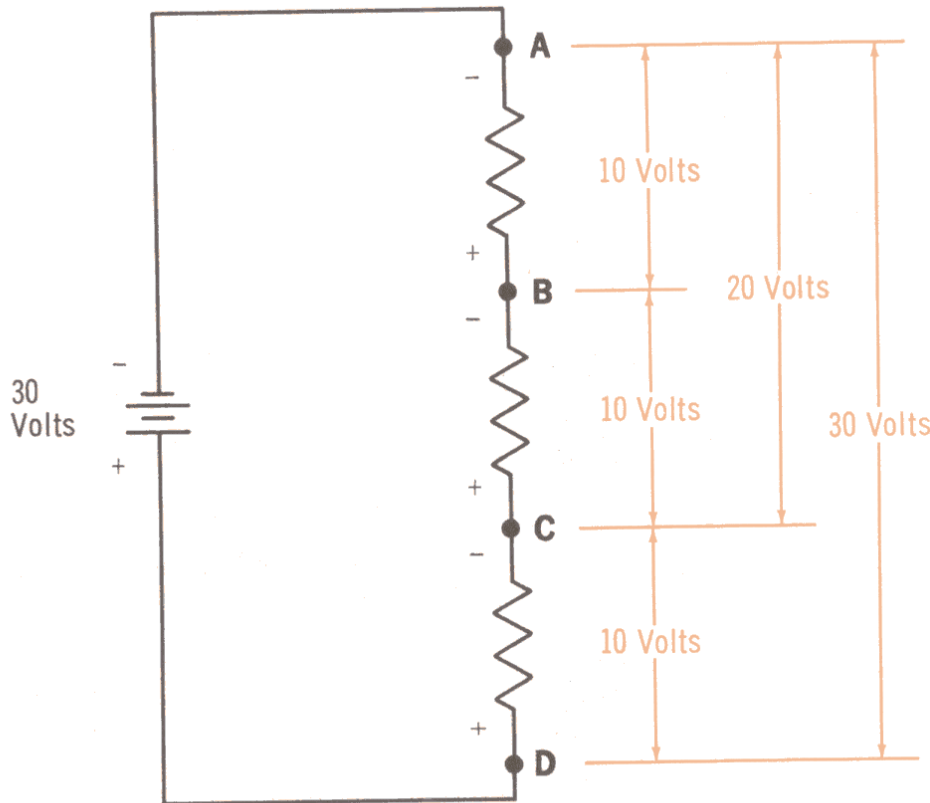Voltage is Relative (reference point / ground)




A voltage exists between two points. These points must be specified before you can determine the voltage



A point is positive or negative only in relation to another point. Very often, a point is positive with respect to one point, and at the same time, negative with respect to another

Potentiometers

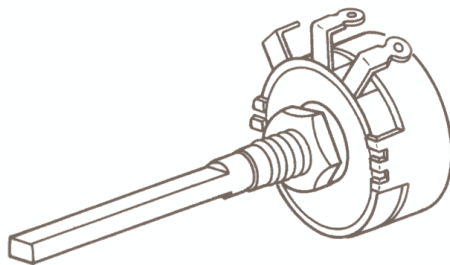- A variable resistor (Rheostat)
- 3 terminals
 - Top to bottom, fixed resistance
 - Wiper arm, variable resistance



This is a Variable Resistor

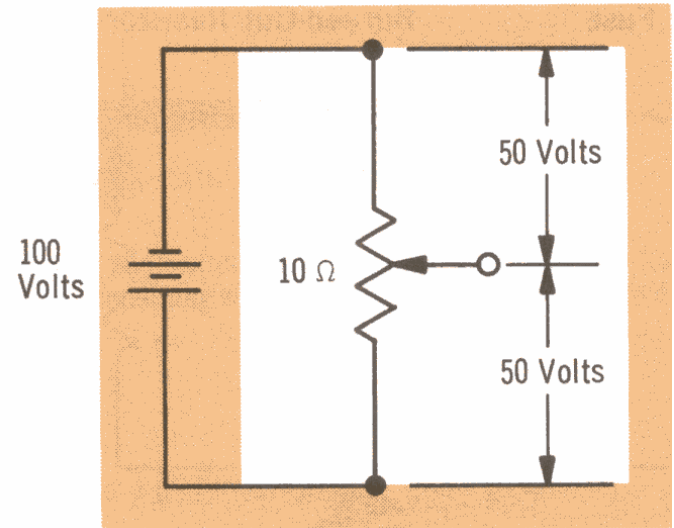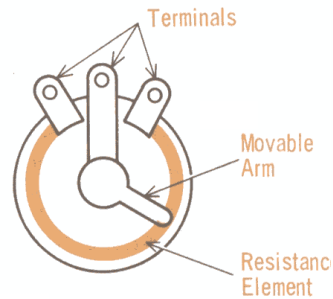

Potentiometer (continued)


- Effectively two variable resistors in series
 - Always add to same total resistance
 - Forms an adjustable “Voltage Divider”
- Voltage divider

$$I = V / (R_1 + R_2)$$

$$V_{\text{out}} = I * R_2$$

$$V_{\text{out}} = R_2 * V / (R_1 + R_2)$$
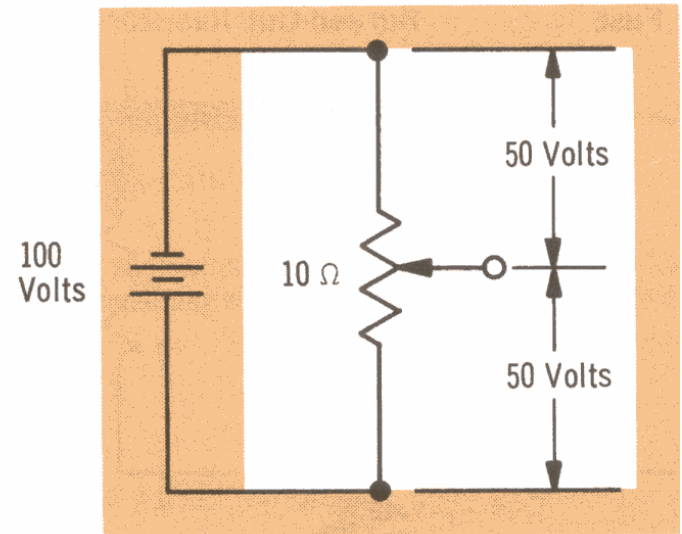
$$V_{\text{out}} / V = R_2 / (R_1 + R_2)$$



Parallel Resistors

- The same voltage is across each parallel resistor
- The current “divides” among the resistors


- $I_1 = 60/10$
= 6 amps

- $I_2 = 60/5$
= 12 amps

- $I_3 = 60/20$
= 3 amps


- $I_{\text{total}} = 6 + 12 + 3$

- $I_{\text{total}} = 21$ amps

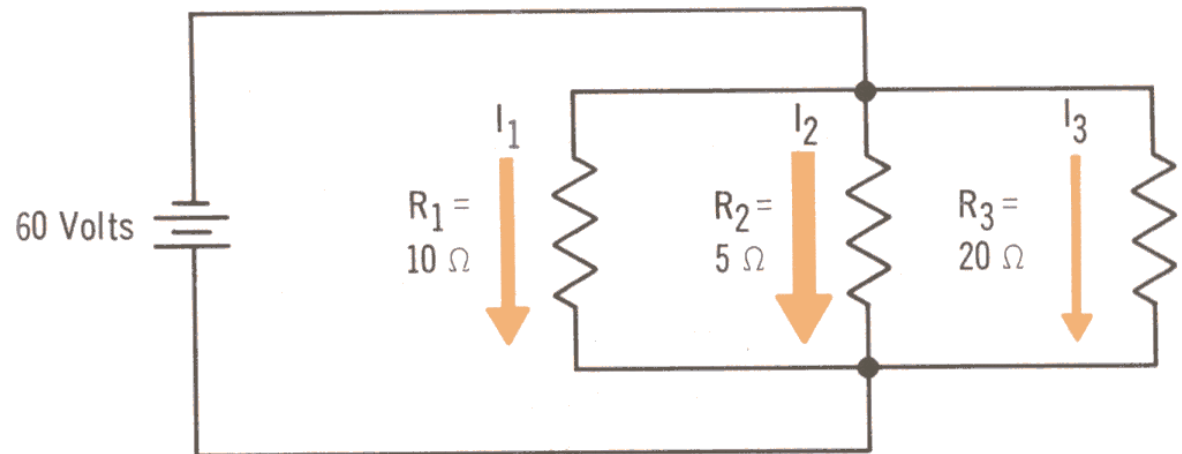


Adding Resistors in Parallel

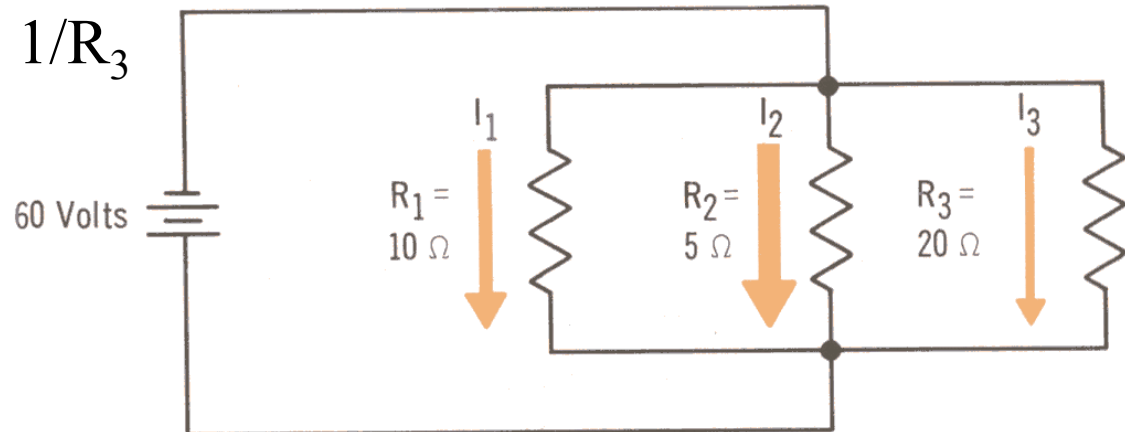- $V = I_{\text{total}} * R_{\text{total}}$ or $R_{\text{total}} = V / I_{\text{total}}$
- $I_{\text{total}} = V/R_1 + V/R_2 + V/R_3$
- $R_{\text{total}} = 1/(1/R_1 + 1/R_2 + 1/R_3)$
- $1 / R_{\text{total}} =$
 $1/R_1 + 1/R_2 + 1/R_3$




Parallel Practice

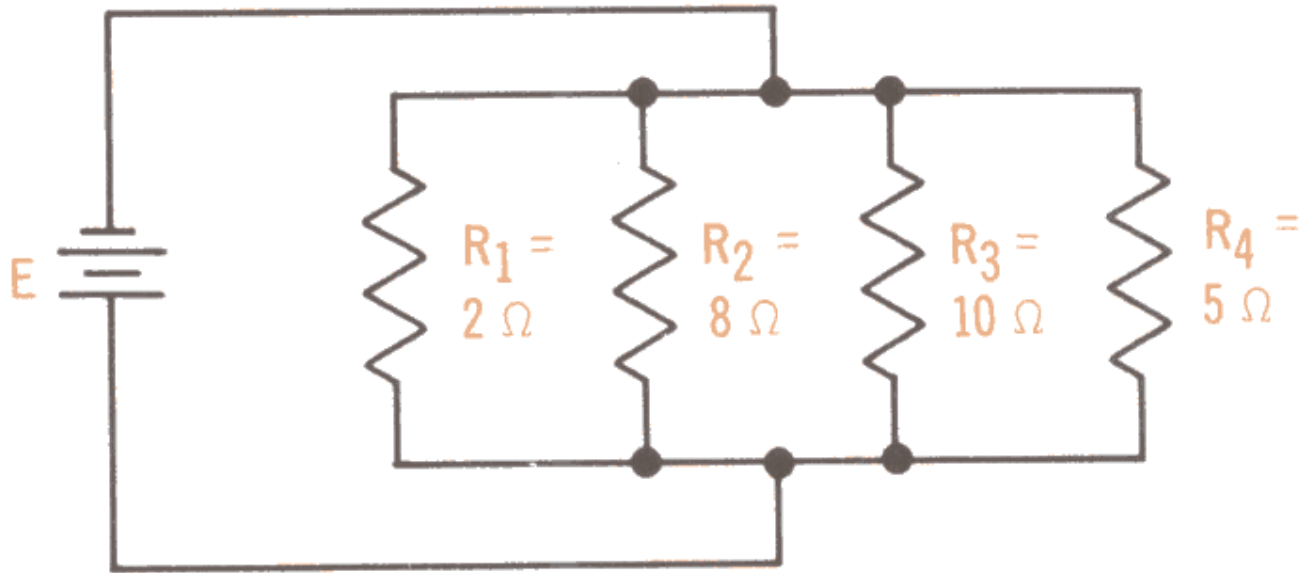


Problem 14

More Parallel Practice

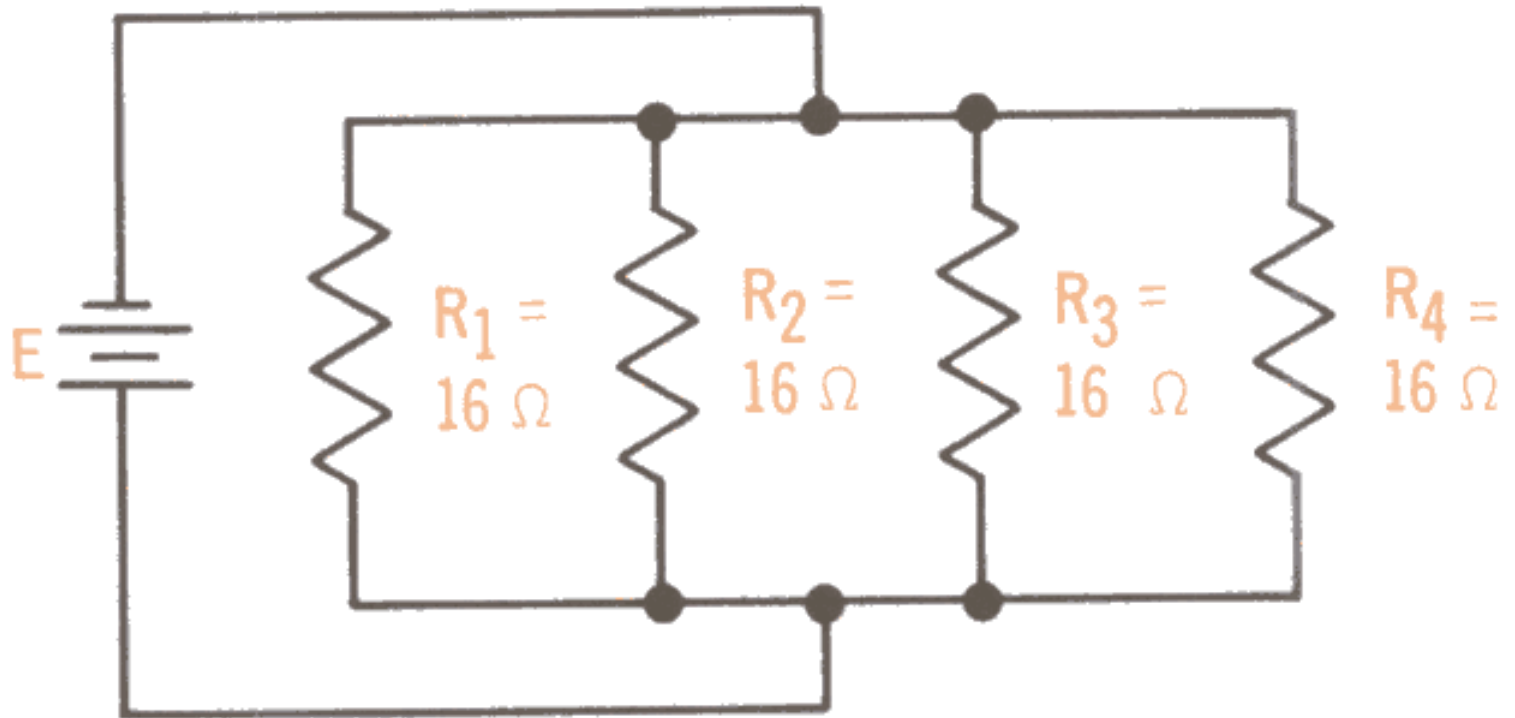

Problem 15

Still more Parallel Practice

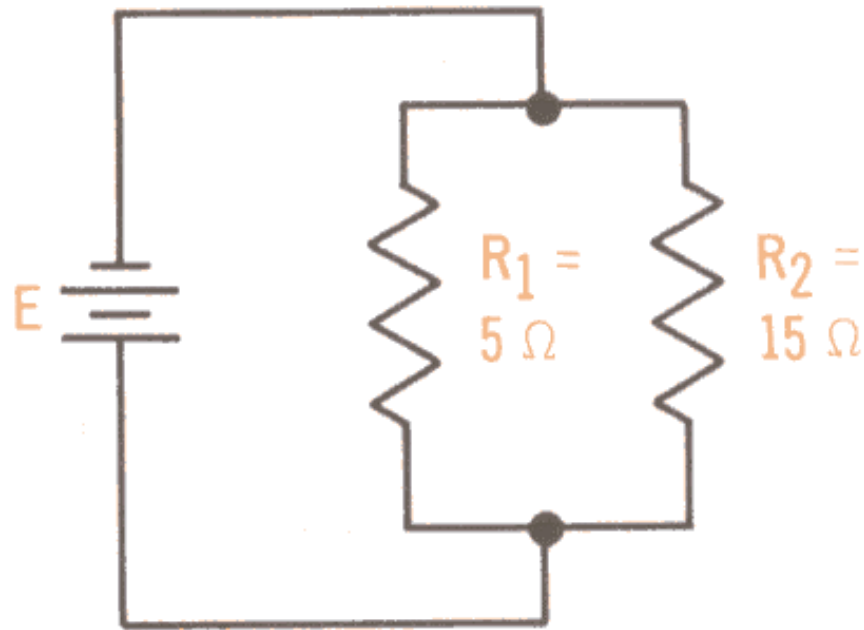

Problem 16

Section 1 Schedule:

Session a – 03/04 <i>03/06 & 03/08 were Math Tutorials</i>	Atoms, Charge and Current Conductivity (G), Electric Fields and Electromotive Force (EMF)	Text 1.1 – 1.39 Text 1.40 – 1.68
Session b – 03/11	Resistance (R), Conductance (G), Ohms Law (Ω) & Power (Watts)	Text 2.1 – 2.52
Session c – 03/13 (lab - 03/16, sat.)	Resistors in Series and Parallel and Working with Equations	Text 2.53 – 2.98
Session d – 03/18	Series / Parallel Simplification Kirchoff, Thevenin & Norton	2.99 – 2.115 2.116 – 2.133
Session e – 03/20	Review: The Water Model	1.42, 1.63, 2.5, 2.129 Sokos