

Resistor-Capacitor (RC) Circuits

Session 3c for Basic Electricity
A Fairfield University E-Course
Powered by LearnLinc

Module: Basic Electronics

(AC Circuits and Impedance: two parts)

- Text: “Electricity One-Seven,” Harry Mileaf, Prentice-Hall, 1996, ISBN 0-13-889585-6 (Covers much more material than this section)
- References:
 - “Digital Mini Test: Principles of Electricity Lessons One and Two,” SNET Home Study Coordinator, (203) 771-5400
 - [Electronics Tutorial](#) (Thanks to Alex Pounds)
 - [Electronics Tutorial](#) (Thanks to Mark Sokos)
 - [Basic Math Tutorial](#) (Thanks to George Mason University)
 - [Vector Math Tutorial](#) (Thanks to California Polytec at atom.physics.calpoly.edu)
- Alternating Current and Impedance
 - 5 on-line sessions plus one lab
- Resonance and Filters
 - 5 on-line sessions plus one lab

Section 3:

AC, Inductors and Capacitors

- **OBJECTIVES:** This section introduces AC voltage / current and their effects on circuit components (resistors, inductors, transformers and capacitors). The concept of impedance and the use of the vector analogy for computations is also introduced.

Section 3 Schedule:

Session 3a	– 05/13	Sine Waves, Magnitude, Phase and Vectors (again)	Text 4.1 – 4.24
3a continued	– 05/20	Complete 3a	
Session 3b	– 05/22	R-L Circuits (no class on 05/27)	Text 4.25 – 4.54
3b continued	– 05/29	Complete 3b	
Session 3c	– 06/03	R-C Circuits	Text 4.55 – 4.76
Session 3d	– 06/05	Series LC Circuits Series RLC Circuits	Text 4.77 – 4.88, 4.89 – 4.113
(lab - 06/08, Sat.)			
Session 3e	– 06/10	Parallel LC Circuits Parallel RLC Circuits	Text 4.114 – 4.122, 4.123 – 4.146
(Quiz 3 due 06/16)			
Session 3f	– 06/17	Review (Discuss Quiz 3)	

Session 3b (R-L) Review

- Inductive reactance $X_L = 2\pi fL$ at 90°
- Impedances (R , X_L) in series add as vectors (Phasors).
- Impedances in parallel add as inverses
- Multiplying Vectors
 - Multiply their magnitudes (lengths)
 - Add their phases
- Dividing Vectors
 - Divide their magnitudes (lengths)
 - Subtract their phases
- Ohm's and Kirchoff's laws still work


Session 3a (Vectors) Review

- Vector Analogy (frequency is not shown, corresponds to rotation)
 - Vector length corresponds to signal amplitude
 - Vector angle corresponds to phase (need a reference phase)
 - $\sin(2\pi f t)$: vertical vector (points up)
 - $\cos(2\pi f t)$: horizontal vector (points right)
- Vector Addition
 - Head-to-Tail
 - Parallelogram
- Vector Components (θ is the angle w.r.t. the horizontal axis)
 - Horizontal component: $A \cdot \cos(\theta)$
 - Vertical component : $A \cdot \sin(\theta)$
- You can add vectors by adding their corresponding components!


R-C Circuits

- 10:1 Ratio
 - If the effect of resistance (reactance) is 10 times larger than reactance (resistance), the smaller can be generally ignored in computations

RC Circuits

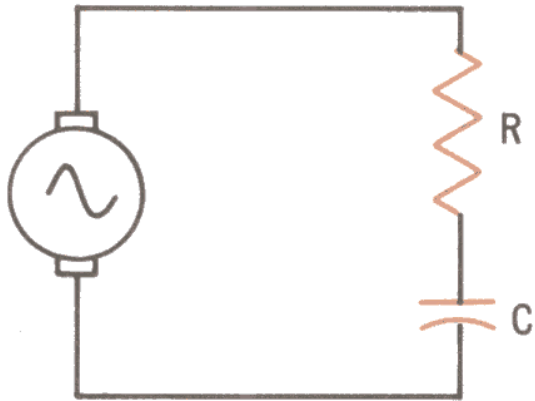


Series RC

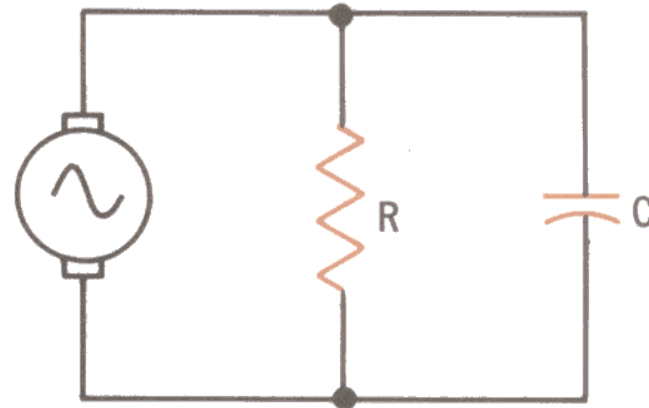

Parallel RC


Capacitor Leakage Resistance

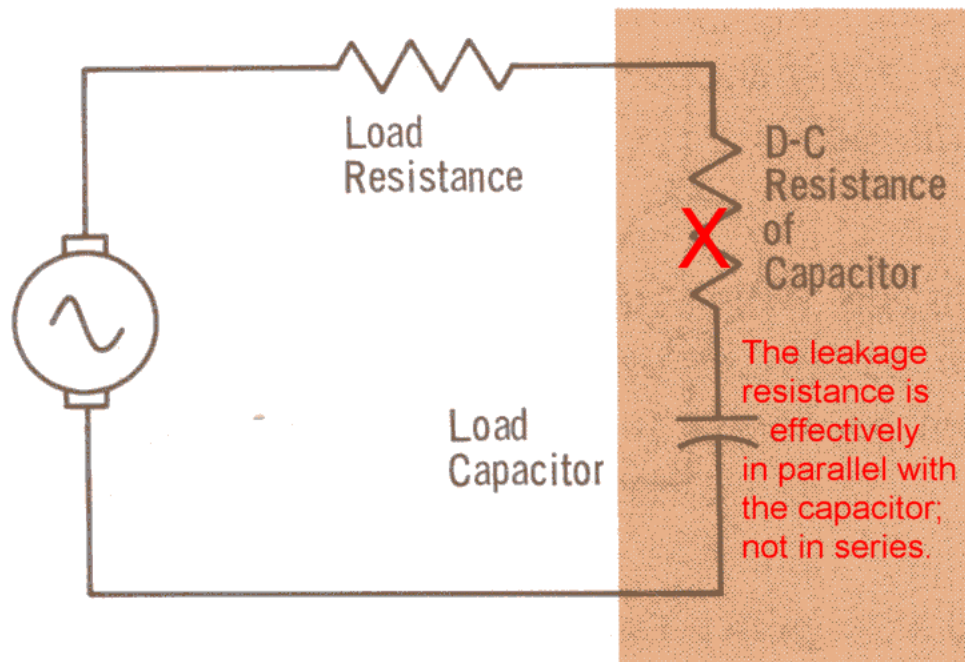- DC leakage resistance is in parallel with the capacitor. (**Text Error**)




Series RC Voltages

- Current is the same in all components; Use it as the reference.
- Voltage across the resistor is in phase with the current.
- Voltage across the capacitor lags (ICE) by 90° (*minus* $\pi/2$).
- E_{app} is the vector sum.
 - $|Z| = (180^2 + 240^2)^{1/2} = 300 \Omega$
 - $\angle Z = \arctan(-240/180) = \arctan(-1.33) = -0.93$ radians or -53.1°

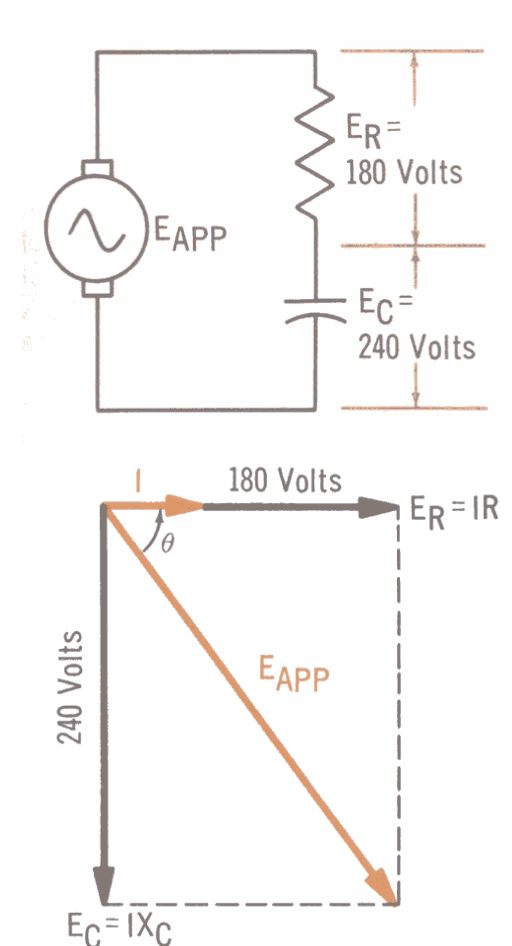

Series RC Voltage Waveforms

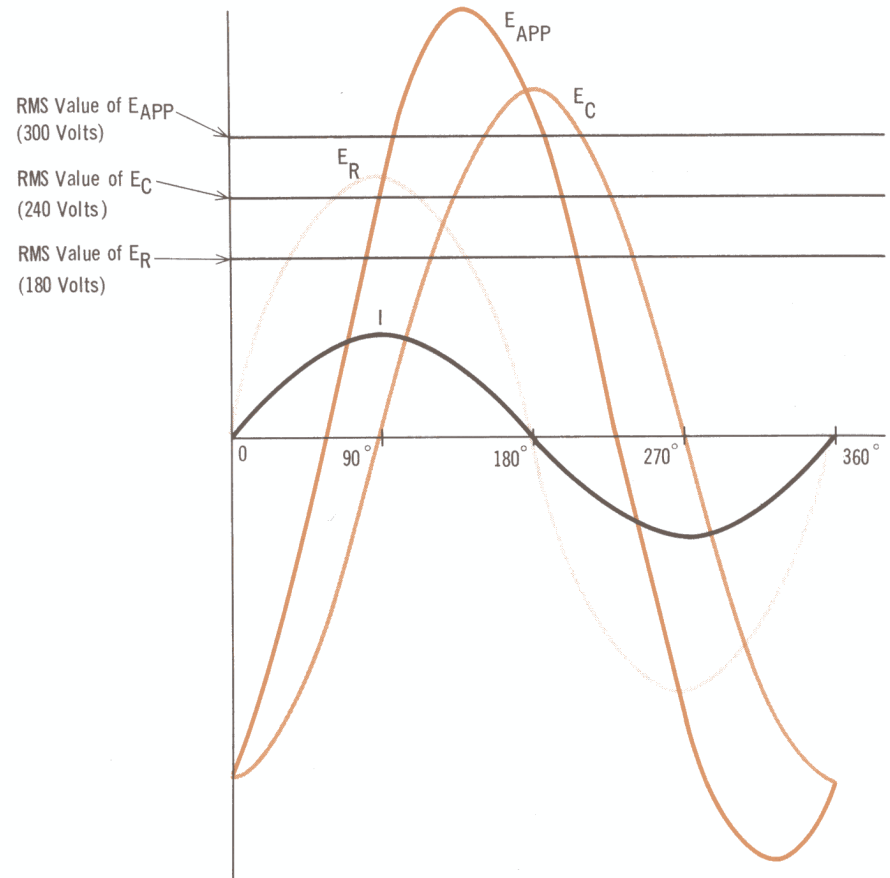
- Current is again the reference phase (shown as a sine wave).
- Capacitor voltage is $-\cos$ (lagging by 90°)
- Every point on E_{app} is the sum of the instantaneous values of E_R and E_C



Series RC Impedance


- Resistance is always treated as zero phase (to the right).
- Capacitive reactance, X_C , is then at -90° (down).
- Total impedance, Z , is then the vector sum of R and X_C .
 - $|Z| = (70^2 + 20^2)^{1/2} = 72.8 \Omega$
 - $\angle Z = \arctan(-20/70)$
 $= \arctan(-0.2857)$
 $= -0.2783$ radians or -16°

note: the picture shows θ backwards

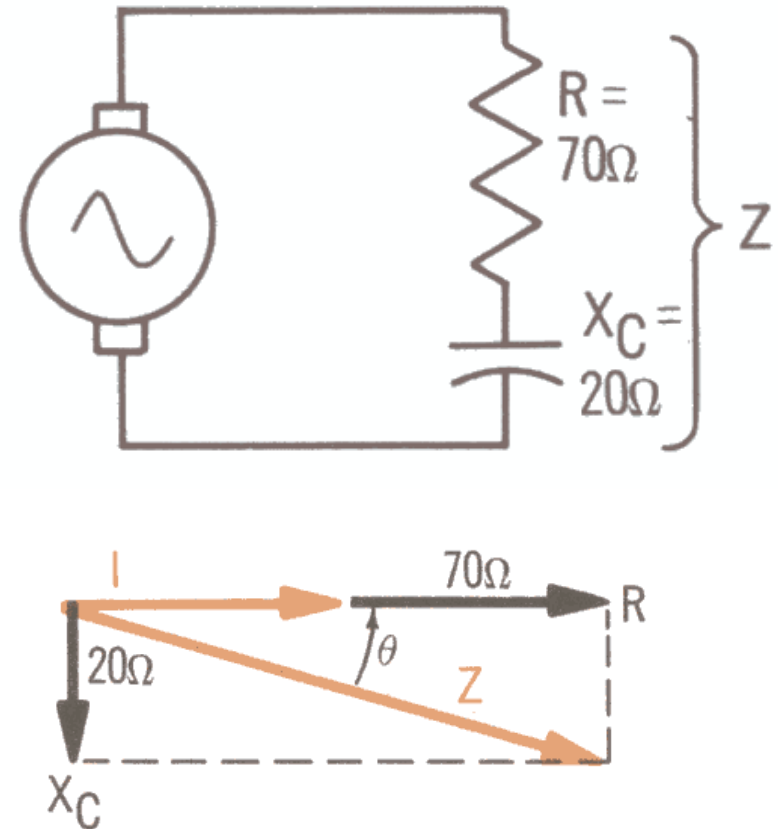


Ohm's Law Again

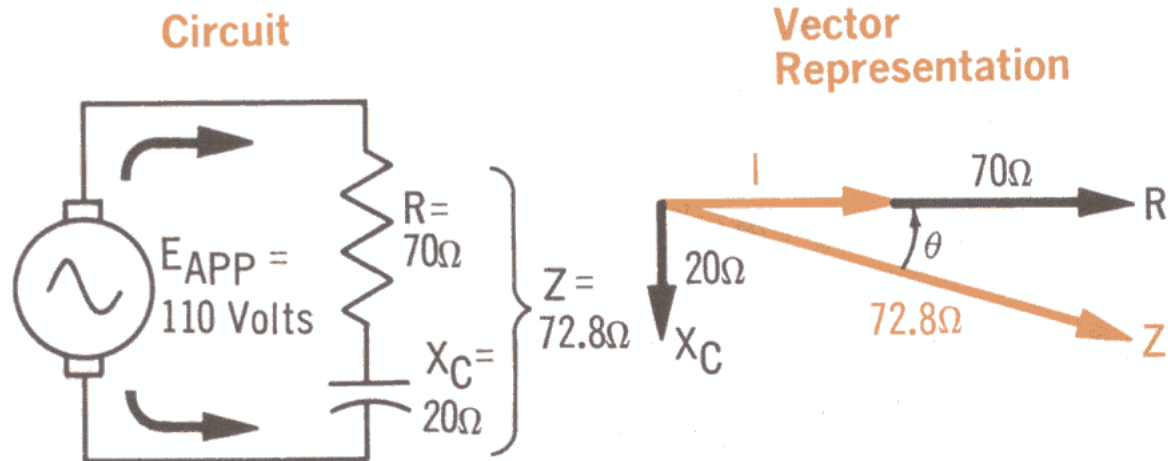- $Z = 72.8 \angle -16^\circ$
- $V = 110 \angle 0^\circ$ (using E_{app} as the reference phase)
(if I is the reference, then V is at -16°)
- $I = V / Z = 110 / 72.8 \angle 16^\circ = 1.51 \angle 16^\circ$




Effect of Changing Frequency

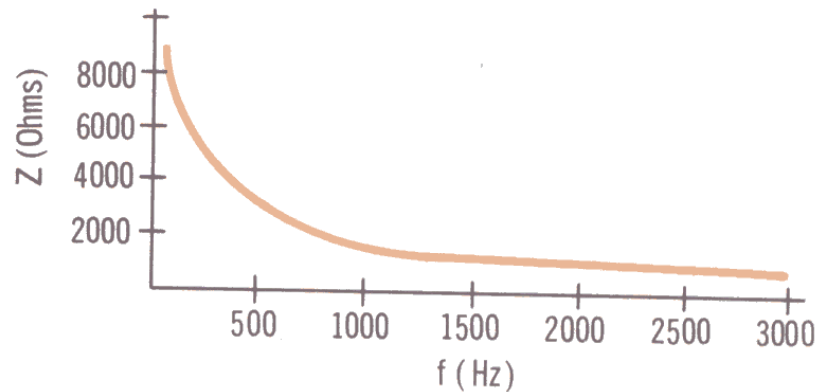- At low frequency the capacitive reactance is high and dominates the impedance.
- At high frequencies the capacitive reactance goes to zero and the resistor dominates the impedance.




Serial RC Exercise

- $X_C = E_C / I$
= 150Ω (at -90°)
- $|Z| = (100^2 + 150^2)^{1/2}$
= 180Ω
- $\angle Z = \arctan(-150/100)$
= $\arctan(-1.5)$
= -56.3°
- $E_{app} = I * Z = 90\angle-56.3^\circ$
- $f = 1/(2\pi CX_C)$
= $1/(6.28 * 0.00002 * 150)$
= 53 Hz

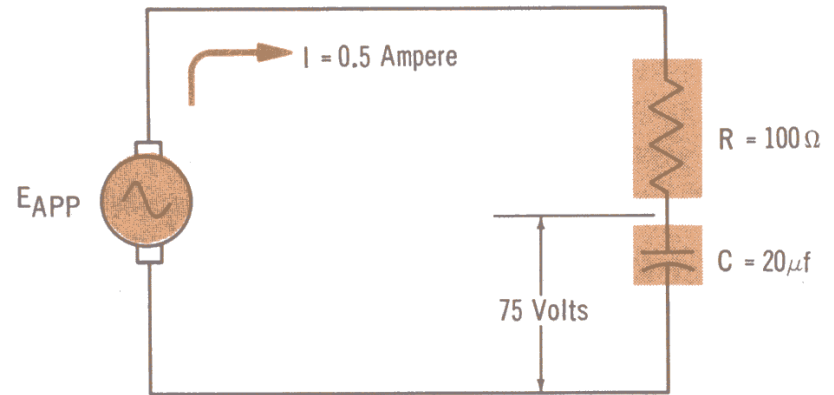


Parallel RC Circuits

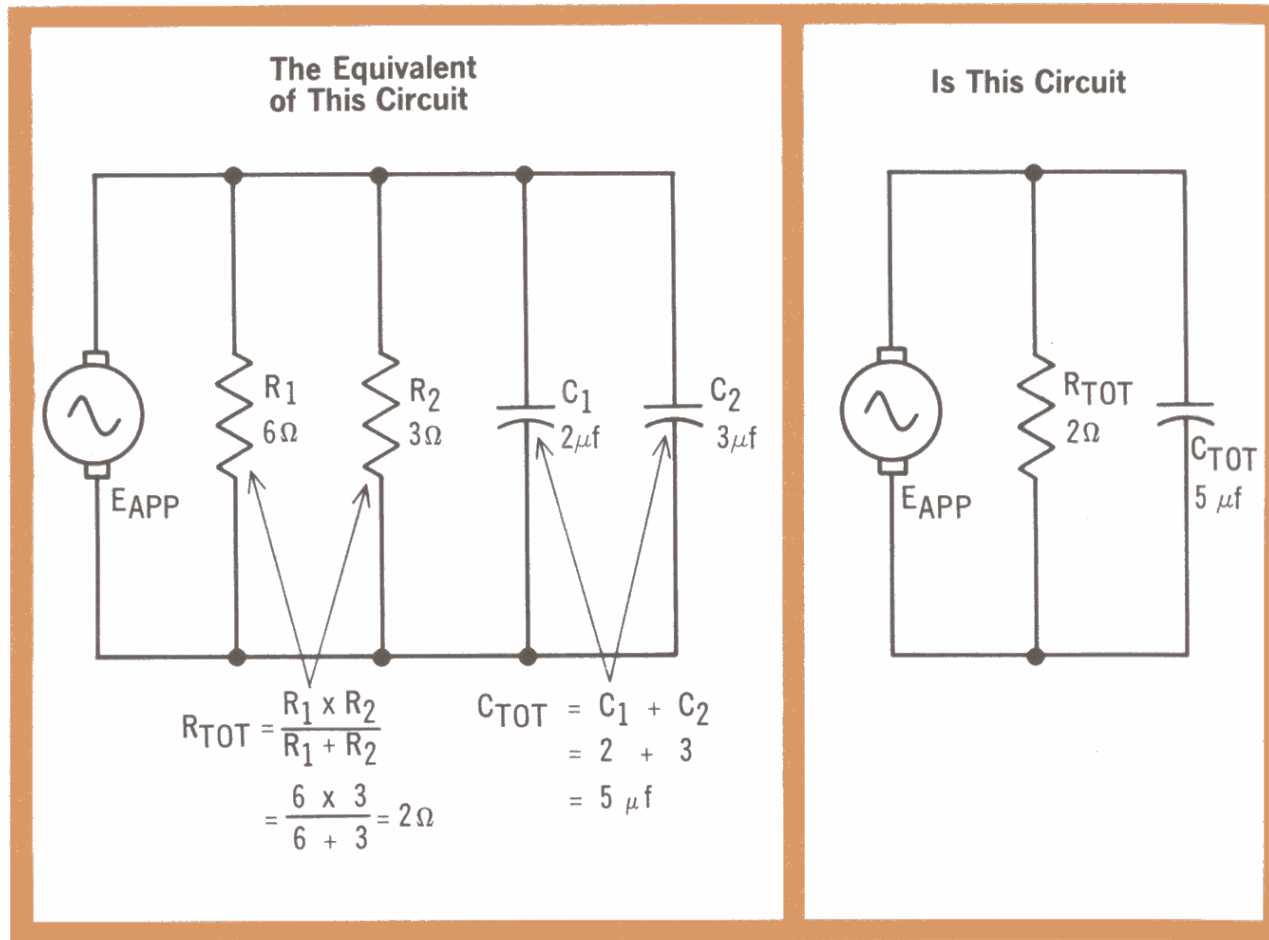


Branch Currents

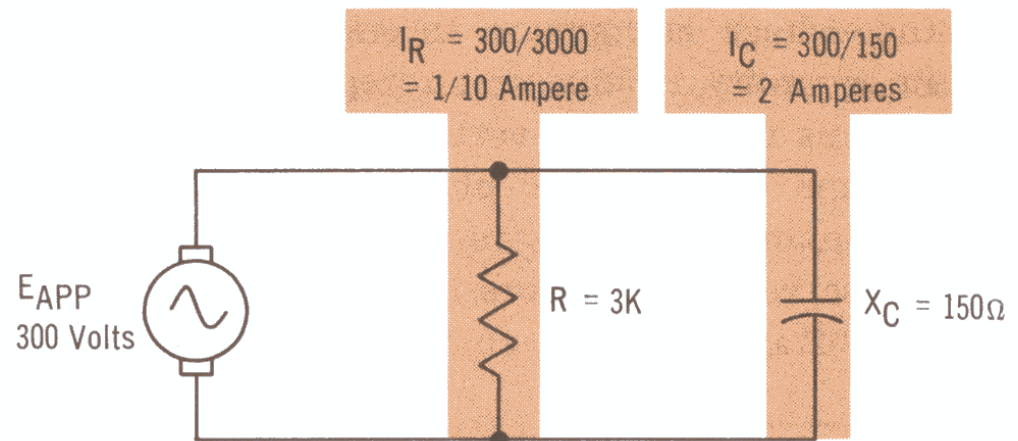- Voltages are the same across all branches.
- Calculate currents independently.
- Note that I_C is at 90° . (E_{app} is the reference phase)



Line Current

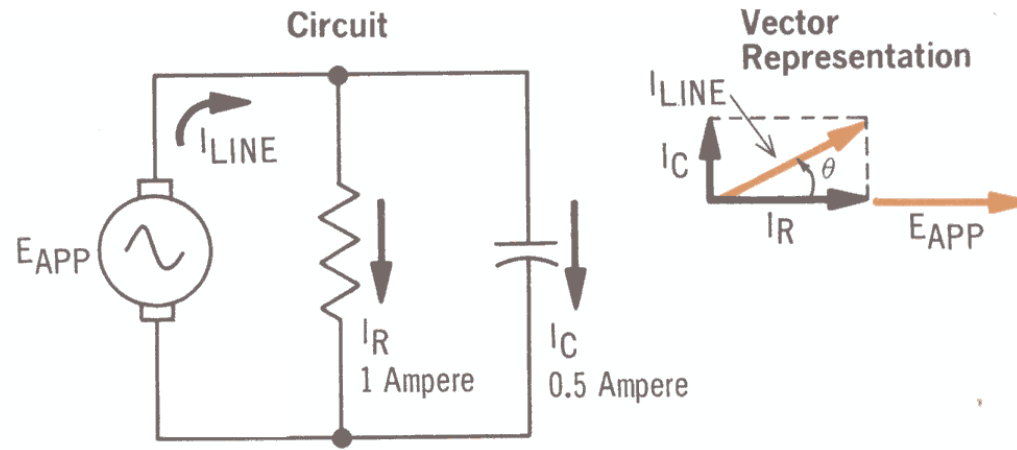- The total or Line current is the vector sum of the branch currents (Kirchoff's Current Law)



Parallel RC Impedance

- Impedances in parallel add as inverses


$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{X_C}$$

$$\frac{1}{Z} = \frac{1}{30} + \frac{1}{30\angle -90^0}$$

$$\frac{1}{Z} = .0333 + 0.0333\angle 90^0$$



$$\frac{1}{Z} = 0.047\angle 45^0$$

$$Z = 21\angle -45^0$$

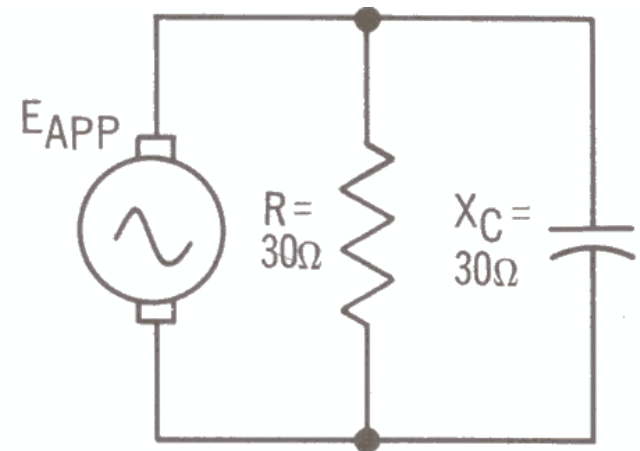

The Effect of Frequency

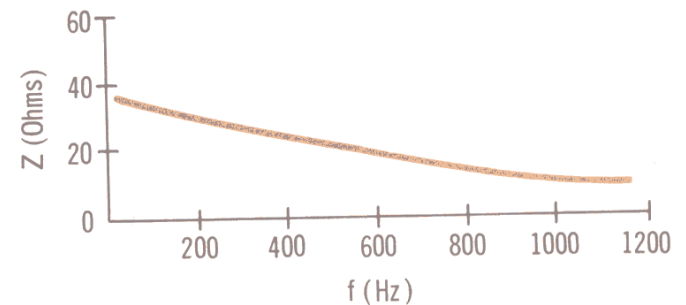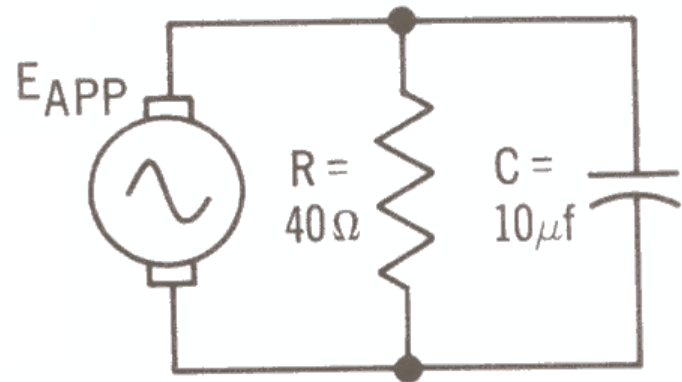- At low frequencies the capacitance is high so the resistance dominates.
- At high frequencies the capacitance goes to zero and dominates.



Section 3 Schedule:

Session 3a	– 05/13	Sine Waves, Magnitude, Phase and Vectors (again)	Text 4.1 – 4.24
3a continued	– 05/20	Complete 3a	
Session 3b	– 05/22	R-L Circuits (no class on 05/27)	Text 4.25 – 4.54
3b continued	– 05/29	Complete 3b	
Session 3c	– 06/03	R-C Circuits	Text 4.55 – 4.76
Session 3d (lab - 06/08, Sat.)	– 06/05	Series LC Circuits Series RLC Circuits	Text 4.77 – 4.88, 4.89 – 4.113
Can we do it Sunday?			
Session 3e (Quiz 3 due 06/16)	– 06/10	Parallel LC Circuits Parallel RLC Circuits	Text 4.114 – 4.122, 4.123 – 4.146
Session 3f	– 06/17	Review (Discuss Quiz 3)	