

Review for MT4: Digital Electronics

Part 8h of
“Electronics and Telecommunications”
A Fairfield University E-Course
Powered by LearnLinc

Module: Digital Electronics

(in two parts)

- Text: “[Digital Logic Tutorial](http://www.play-hookey.com/digital/),” [Ken Bigelow](#),
<http://www.play-hookey.com/digital/>
- References:
 - “[Electronics Tutorial](#)”, part 10 (Thanks to Alex Pounds)
http://doctord.dyndns.org:8000/courses/Topics/Electronics/Alex_Pounds/Index.htm
- Contents:
 - 7 – Digital Electronics 1
 - 5 on-line sessions plus one lab and a quiz
 - 8 – Digital Electronics 2
 - 5 on-line sessions plus one lab and a quiz
- Mastery Test part 4 follows this Module

Section 7: Digital Electronics 1

- Logic gates and Boolean algebra
- Truth Tables
- Binary numbers
- Memory
- Flip-Flops

Section 8: Digital Electronics 2

- Clocks and Counters
- Shift Registers
- Decoders
- Multiplexers & Demultiplexers
- Sampling

- **MT4**

Section 8 Schedule

Session 8a	04/02	Clocks and Counters	“Hookey”: “Counter” pages Alex Pounds: Part 27
Session 8b	04/09	Shift Registers	“Hookey”: “Register” pages
Session 8c	04/14	Decoders	“Hookey”: Decoders and Demultiplexers
Session 8d	04/16	Multiplexers and Demultiplexers	“Hookey”: Multiplexers, Decoders and Demultiplexers
Session 8e	04/21	Sampling (A/D & D/A)	Notes
Session 8f (Quiz 8 due 04/27)	04/23	Review for Quiz 8	
Session 8g	04/28	Quiz Results	
Session 8h (Lab - 05/03, Sat.)	04/30	MT4 Q&A	
MT4 (Sat, Cheshire)	05/10		
MT4 Results	05/12		

Digital Electronics Topics

- Logic Gates and Boolean Algebra
- Truth Tables
- Binary Numbers
- Memory
- Flip-Flops


Part 7

-
- Clocks and Counters
 - Shift Registers
 - Decoders
 - Multiplexers & Demultiplexers
 - Sampling and Nyquist

 Part 8

Logic Basics

- Binary: 1, 0; True, False; On, Off; High, Low; 5 volts, 0 volts
- Basic Logic Gates:
 - AND: $Q = A * B * C$
(Q is only true if all inputs are true)
 - OR: $Q = A + B + C$
(Q is only false if all inputs are false)
 - NOT: $Z = X'$
(Q is true if A is false, Q is false if A is true)
- Derived Logic Gates:
 - NAND
(Q is only false if all inputs are true)
 - NOR
(Q is only true if all inputs are false)
 - XOR
(Q is true if one of A or B is true but not both)



Truth Tables

- Truth Tables: Enumerate outputs for all input combinations
 - Example: 5 people are voting for one of two candidates
Let 0 represent Candidate A and 1 represent candidate B

Voter1	Voter2	Voter3	Winner
0	0	0	A
0	0	1	A
0	1	0	A
0	1	1	B
1	0	0	A
1	0	1	B
1	1	0	B
1	1	1	B

Boolean Algebra

- Named Variables

(T1)	$X + 0 = X$	(T1')	$X \cdot 1 = X$	(Identities)
------	-------------	-------	-----------------	--------------

- Operators

(T2)	$X + 1 = 1$	(T2')	$X \cdot 0 = 0$	(Null elements)
------	-------------	-------	-----------------	-----------------

- Expressions

(T3)	$X + X = X$	(T3')	$X \cdot X = X$	(Idempotency)
------	-------------	-------	-----------------	---------------

(T4)	$(X')' = X$			(Involution)
------	-------------	--	--	--------------

(T5)	$X + X' = 1$	(T5')	$X \cdot X' = 0$	(Complements)
------	--------------	-------	------------------	---------------

- Equations

(T6)	$X + Y = Y + X$	(T6')	$X \cdot Y = Y \cdot X$	(Commutativity)
------	-----------------	-------	-------------------------	-----------------

- Rules

(T7)	$(X + Y) + Z = X + (Y + Z)$	(T7')	$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$	(Associativity)
------	-----------------------------	-------	---	-----------------

(T8)	$X \cdot Y + X \cdot Z = X \cdot (Y + Z)$	(T8')	$(X + Y) \cdot (X + Z) = X + Y \cdot Z$	(Distributivity)
------	---	-------	---	------------------

(T9)	$X + X \cdot Y = X$	(T9')	$X \cdot (X + Y) = X$	(Covering)
------	---------------------	-------	-----------------------	------------

(T10)	$X \cdot Y + X \cdot Y' = X$	(T10')	$(X + Y) \cdot (X + Y') = X$	(Combining)
-------	------------------------------	--------	------------------------------	-------------

(T11)	$X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$			(Consensus)
-------	---	--	--	-------------

(T11')	$(X + Y) \cdot (X' + Z) \cdot (Y + Z) = (X + Y) \cdot (X' + Z)$			
--------	---	--	--	--

Binary Numbers:

– Based on powers of 2

$$\begin{array}{cccccccc} 0 & 1 & 1 & 0 & 1 & 1 & 0 & 1 \\ 128 & 64 & 32 & 16 & 8 & 4 & 2 & 1 \end{array} = 64 + 32 + 8 + 4 + 1 = 109$$


– k bits can count up to $2^k - 1$ (2^k values including zero)

- 8-bits \Rightarrow 256 values, 16-bits \Rightarrow 65536 values (64k binary)
- 10-bits \Rightarrow 1024 values (1k binary)
- 20-bits \Rightarrow 1,048,576 values (1 meg binary)
- Bits, Nibbles (4), Bytes (8), and Words
- Negative Numbers: Two's complement
- Binary Adders: half and full

$$\begin{array}{r} 01101101 = 109 \\ +00001011 = \underline{11} \\ \hline 01111000 = 120 \end{array}$$



Storage

 - The RS Latch (a “bit” of storage)
 - Set = 1: $Q=1$
 - Reset = 1: $Q=0$
- Register (n-bits of storage)
 - n latches (or flip-flops)
 - Stores a word (or byte) of data
- RAM (addressable words of memory)
 - Read / write
 - Volatile (data lost if power lost)
- ROMs, PROMs, EPROMs and EEROMS
 - Non-volatile memories



Pulses and Clocks

  
- Single Pulse
 - Signal normally low then high for a short time and goes back to low
- Clock
 - Signal alternates high-low at a regular rate



Positive going edge


Clocked Logic

 - Clock signal “enables Set and Reset pins
- Synchronous Logic
 - Slower than “ripple” logic
 - Gates have input to output “delay”
 - Delays build up as signals propagate through the logic
 - Predictable timing
 - Clocked (synchronous) logic prevents the build up of delays



The JK Flip-Flop

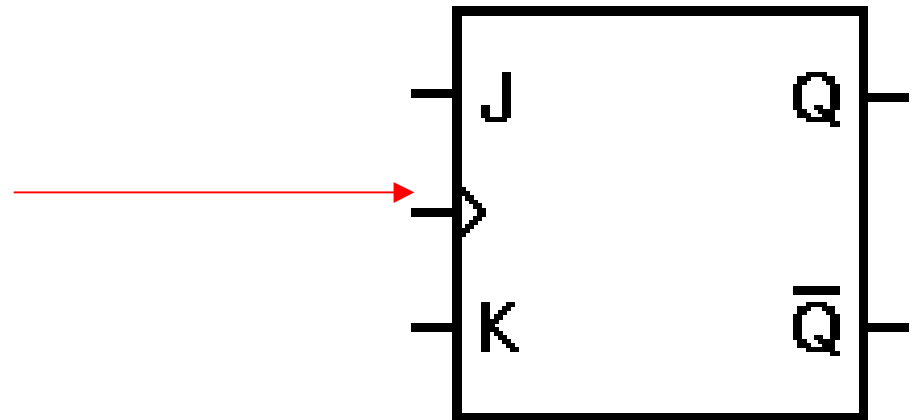- Edge Triggered Generic Flip-Flop
 - the triangle symbol
 - triangle: rising edge triggers change
 - Not then triangle: falling edge triggers change



- Truth Table
 - J and K determines state change


J	K	Q(t+1)
0	0	Q(t) – No change
0	1	0 – Reset
1	0	1 – Set
1	1	Q'(t) – Complement

The T Flip-Flop

- State toggles (flips) on each positive going clock edge


Triangle: edge triggered

T	$Q(t+1)$
0	$Q(t)$ – No change
1	$Q'(t)$ - Complement

 

The D Flip-Flop

 
- Simple triggered storage Flip-Flop
 - Note the half circle
 - It is controlled by clock level, not an edge



D	Q(t+1)
0	0 - Reset
1	1 - Set


Counter Review

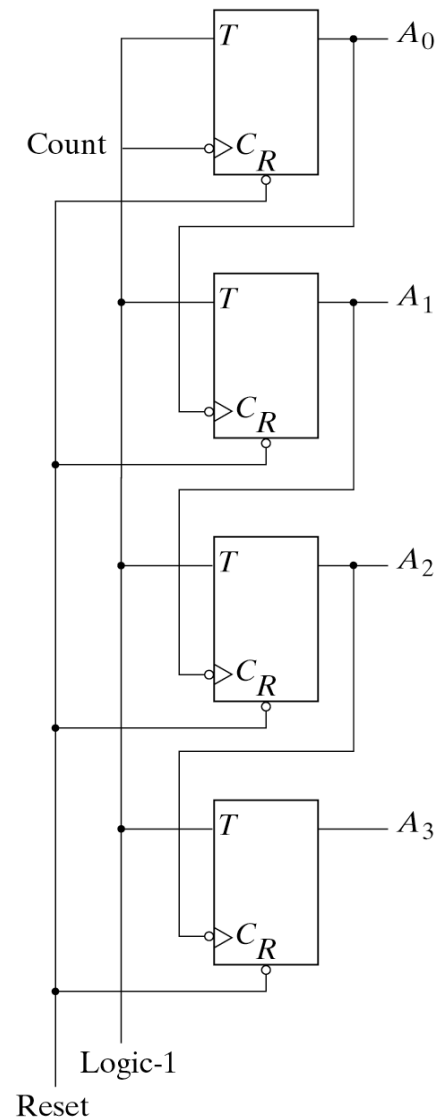- **Clock:** Sets system speed
- **Bit Storage:** Latch or Flip-Flop
- **Register** (n-bits of storage)
- **Counters**
 - Ripple Counter
 - Synchronous Counter
- **Frequency Divider:**
Counter Divides clock rate by an integer





Shift Register Review

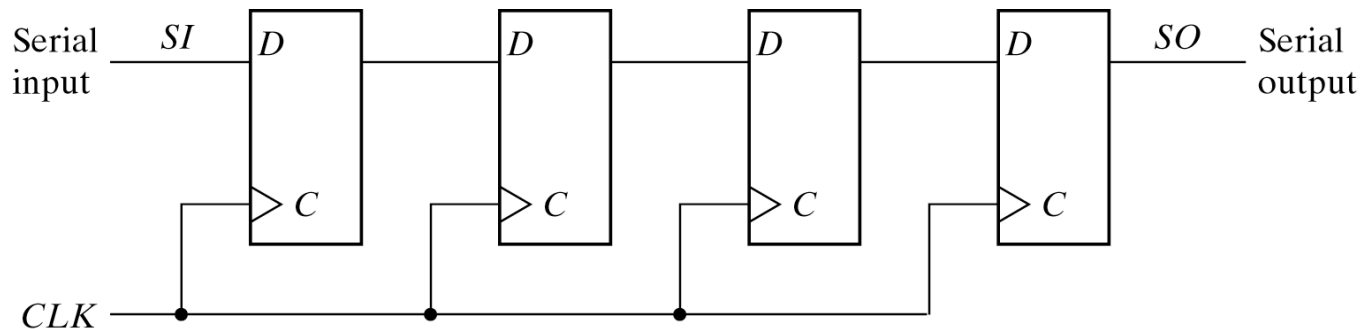- Cascade chain of Flip-Flops
- Data marches down the line at the beat of the clock
- Parallel or serial load, Parallel or serial read
- Applications:
 - Parallel to serial (serial transfer of data)
 - Serial to parallel (serial reception of data)
 - Feedback shift registers



Decoder Review

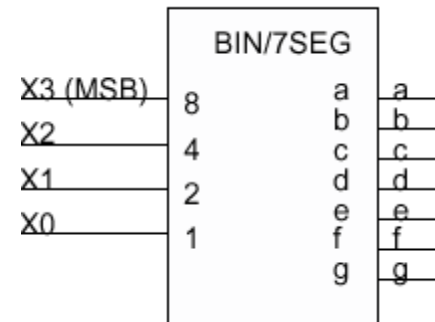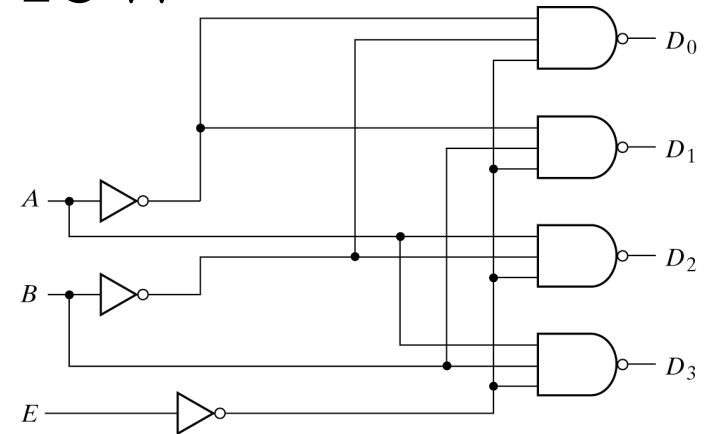
- A small number of input bits; treated as a binary number
- A larger set of output bits (up to 2^n)
- The output bit values are “decoded” from the combination of the input bits
- Examples:
 - 1 of N decoding
 - Line Decoder
 - Address Decoder
 - Seven segment display decoder
 - BCD to Decimal line decoder



Mux and Demux Review

 4.4 Multiplexer

- Multiplexer - A **data selector** that selects one of many inputs to appear on a single output line
- Demultiplexer - A **data distributor** that takes a single input line and routes it to one of several output lines




National Central University

www.ee.ncu.edu.tw/~ccsu

Introduction to Digital Systems


Chapter 4 P.25

Analog to Digital Conversion

 

- **Analog Signal:** A continuous electrical signal
- **Aliasing:** Confusion of high and low frequencies if sampling is too slow (filter ensures Nyquist criterion; Nyquist rate $f_s > 2 f_{\max}$ to avoid aliasing)
- **Sampling:** The process of approximating an analog signal by a sequence of narrow pulses
- **A/D:** Representing the “strength” of a pulse by a binary number (introduces an error due to word length)


Digital to Analog Conversion

 


- **Digital Signal:** A sequence of binary numbers representing an analog signal (approximate – digital “noise”)
- **PAM:** Pulse Amplitude Modulation - A sequence of pulses with strengths corresponding to the analog signal
- **Reconstruction Filter:** Averaging out the pulse sequence to reproduce the original analog signal (almost identical to the “anti-aliasing filter”)

Analog to Digital Conversion

- Flash (or parallel) A/D
 - Very fast
 - Either low resolution (8-bits) or very expensive
- Successive approximation A/D
 - Determines the MSB first
 - Repeatedly refines the representation
 - Accurate (high resolution) but slow
- Counting A/D: Uses a ramp signal and a high speed counter to determine the time that the ramp exceeds the signal value
- Over-Sampled (Sigma-Delta) A/D
 - Flash encodes a low-resolution value at high speeds
 - Uses a digital filter (anti-alias) to lower the bandwidth
 - Allows reduction of the sampling rate
 - Improves the resolution (number of bits)

 

Digital to Analog Conversion

 

- Reverses the A/D sequence
- D/A: generates a PAM pulse sequence where each pulse magnitude corresponds to the value of the corresponding digital number
- Reconstruction filter: Almost identical to the Anti-Aliasing filter used in A/D. Smooths out the pulse sequence to reproduce the original signal.

Applications

- North American Telephony (64 kbits/sec)
 - Sampling rate = 8 kHz (3 dB: 3.3 kHz , f_{\max} : 3.8 kHz)
 - μ 255 (logarithmic), 8-bit words (256 levels)
- CD Audio
 - Sampling rate = 44.1 kHz per channel (3 dB: 20 kHz, f_{\max} : 21 kHz)
(note: DAT = 48 kHz - Prof Audio = 96 kHz, 24 bit)
 - Linear 16-bit words
- PC sound card:
 - Sampling rate = 8, 16, 11.025, 22.05, 44.1 kHz
 - 8 or 16 bit word size

Section 8 Schedule

Session 8a	04/02	Clocks and Counters	“Hookey”: “Counter” pages Alex Pounds: Part 27
Session 8b	04/09	Shift Registers	“Hookey”: “Register” pages
Session 8c	04/14	Decoders	“Hookey”: Decoders and Demultiplexers
Session 8d	04/16	Multiplexers and Demultiplexers	“Hookey”: Multiplexers, Decoders and Demultiplexers
Session 8e	04/21	Sampling (A/D & D/A)	Notes
Session 8f (Quiz 8 due 04/27)	04/23	Review for Quiz 8	
Session 8g	04/28	Quiz Results	
Session 8h (Lab - 05/03, Sat.)	04/30	MT4 Q&A	
MT4 (Sat,Cheshire)	05/10		
MT4 Results	05/12		