

Fig. 4-1 Block Diagram of Combinational Circuit


 
 
 
 


Fig. 4-2 Logic Diagram for Analysis Example

 



 


Fig. 4-4 Logic Diagram for BCD to Excess-3 Code Converter

 


(a) $S = xy' + x'y$
 $C = xy$

 


(b) $S = x \oplus y$
 $C = xy$

Fig. 4-5 Implementation of Half-Adder

 

$$S = x'y'z + x'yz' + xy'z' + xyz$$

 

$$\begin{aligned} S &= xy + xz + yz \\ &= xy + xy'z + x'y'z \end{aligned}$$

Fig. 4-6 Maps for Full Adder

 
 


Fig. 4-7 Implementation of Full Adder in Sum of Products

 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

 


Fig. 4-9 4-Bit Adder

 


Fig. 4-10 Full Adder with P and G Shown

 


Fig. 4-11 Logic Diagram of Carry Lookahead Generator

 


Fig. 4-12 4-Bit Adder with Carry Lookahead

 


Fig. 4-13 4-Bit Adder Subtractor

 


Fig. 4-14 Block Diagram of a BCD Adder

$$\begin{array}{r}
 & B_1 & B_0 \\
 & A_1 & A_0 \\
 \hline
 & A_0B_1 & A_0B_0 \\
 \\
 A_1B_1 & A_1B_0 \\
 \hline
 C_3 & C_2 & C_1 & C_0
 \end{array}$$


 


Fig. 4-15 2-Bit by 2-Bit Binary Multiplier

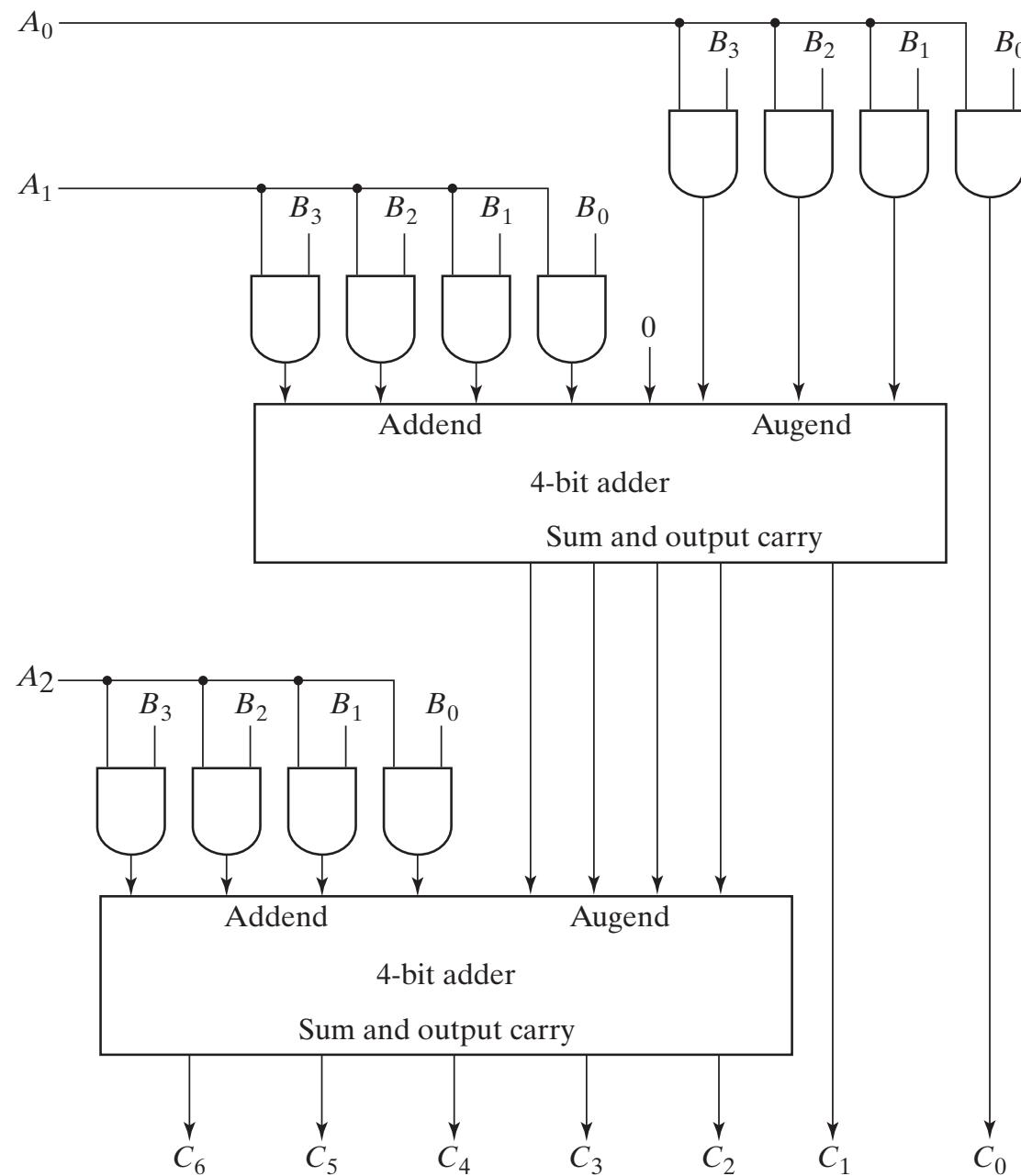



 


Fig. 4-17 4-Bit Magnitude Comparator

 

 

(a) Logic diagram

E	A	B	D_0	D_1	D_2	D_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table

Fig. 4-19 2-to-4-Line Decoder with Enable Input

 


Fig. 4-20 4×16 Decoder Constructed with Two 3×8 Decoders



 


Fig. 4-21 Implementation of a Full Adder with a Decoder

 

$$x = D_2 + D_3$$

 

$$y = D_3 + D_1 D'_2$$

Fig. 4-22 Maps for a Priority Encoder



 


Fig. 4-23 4-Input Priority Encoder

 


(a) Logic diagram

 

(b) Block diagram

Fig. 4-24 2-to-1-Line Multiplexer

 

(a) Logic diagram

s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table


 


Fig. 4-26 Quadruple 2-to-1-Line Multiplexer

x	y	z	F
0	0	0	0
0	0	1	1 $F = z$
0	1	0	1
0	1	1	0 $F = z'$
1	0	0	0
1	0	1	0 $F = 0$
1	1	0	1
1	1	1	1 $F = 1$

(a) Truth table

 

(b) Multiplexer implementation

Fig. 4-27 Implementing a Boolean Function with a Multiplexer

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

 


Fig. 4-28 Implementing a 4-Input Function with a Multiplexer



 


Fig. 4-29 Graphic Symbol for a Three-State Buffer

 


(a) 2-to-1- line mux

 


(b) 4 - to - 1 line mux


Fig. 4-30 Multiplexers with Three-State Gates

 


bufif1

 

bufif0

 

notif1

 

notif0

Fig. 4-31 Three-State Gates


 


Fig. 4-32 2-to-1-Line Multiplexer with Three-State Buffers

Stimulus module

 

Design module

 


Fig. 4-33 Stimulus and Design Modules Interaction

 


Fig. P4-1

 


Fig. P4-2



(a) Segment designation

(b) Numerical designation for display

Fig. P4-9

 


Fig. P4-17 First Stage of a Parallel Adder