 


(a) Conventional symbol



(b) Array logic symbol

Fig. 7-1 Conventional and Array Logic Diagrams for OR Gate


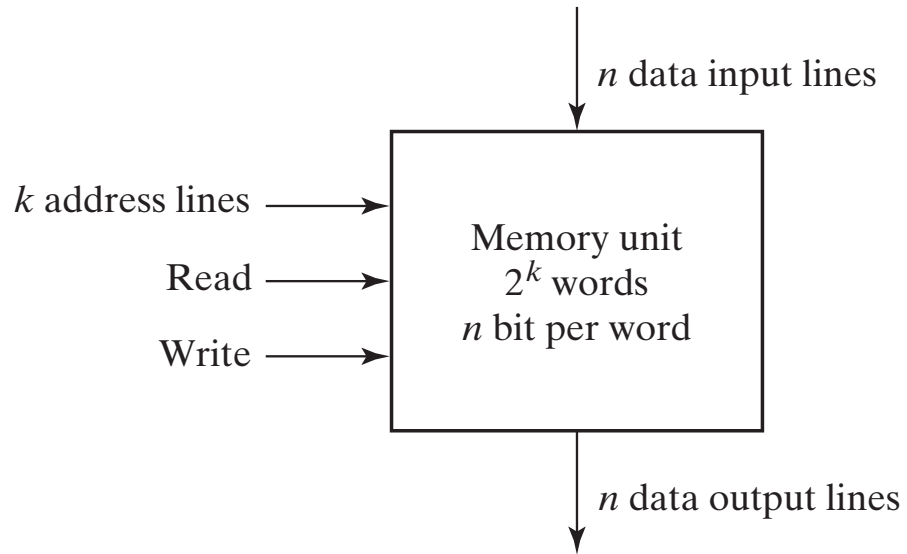



Fig. 7-2 Block Diagram of a Memory Unit

Memory address		
Binary	decimal	Memory content
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101

Fig. 7-3 Content of a  $1024 \times 16$  Memory

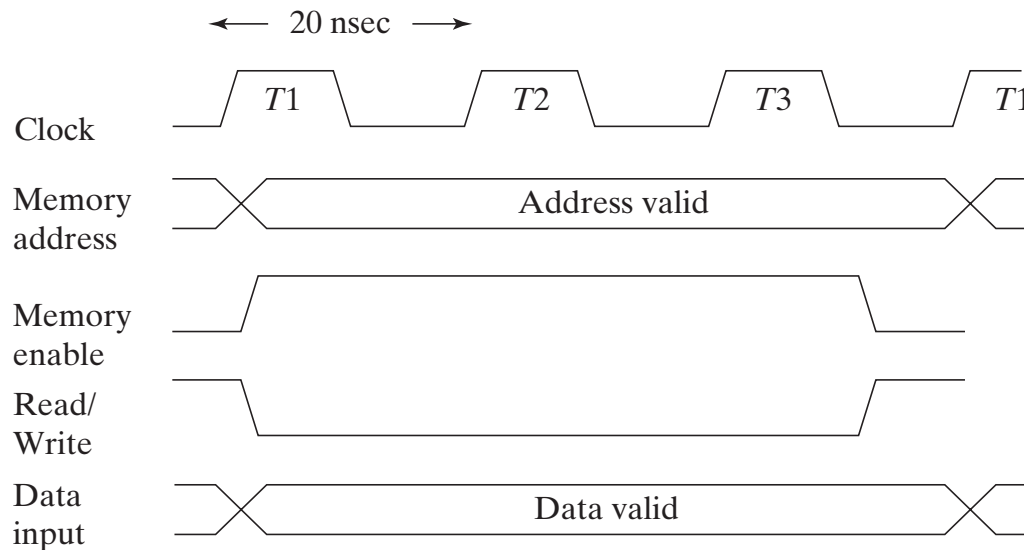


(a) Write cycle

 


(b) Read cycle

Fig. 7-4 Memory Cycle Timing Waveforms

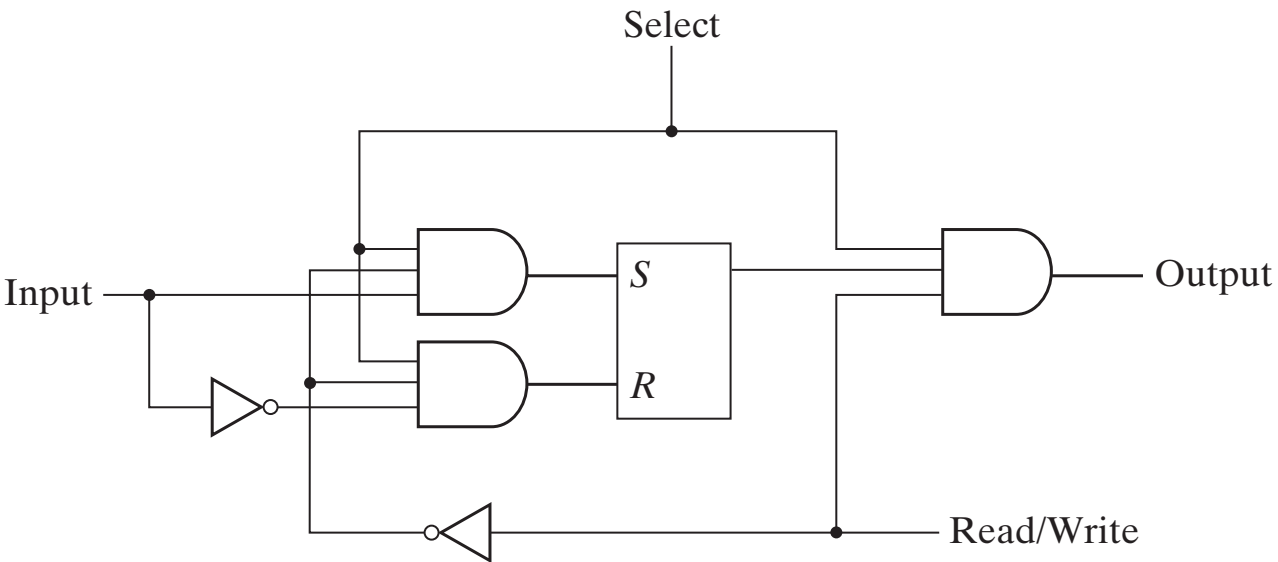

(a) Logic diagram

 

(b) Block diagram

Fig. 7-5 Memory Cell

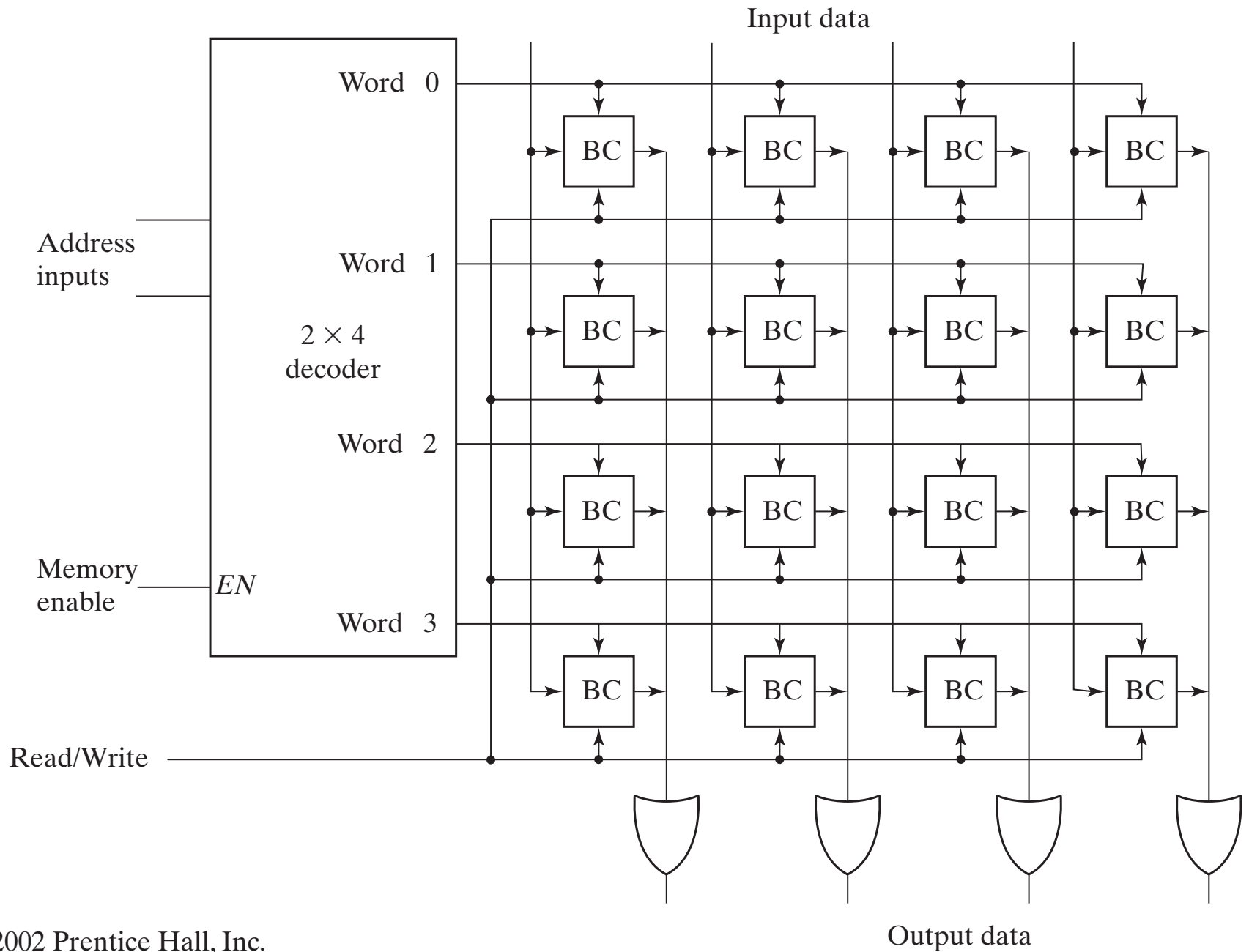


Fig. 7-6 Diagram of a  $4 \times 4$  RAM

 


Fig. 7-7 Two-Dimensional Decoding Structure for a 1K-Word Memory

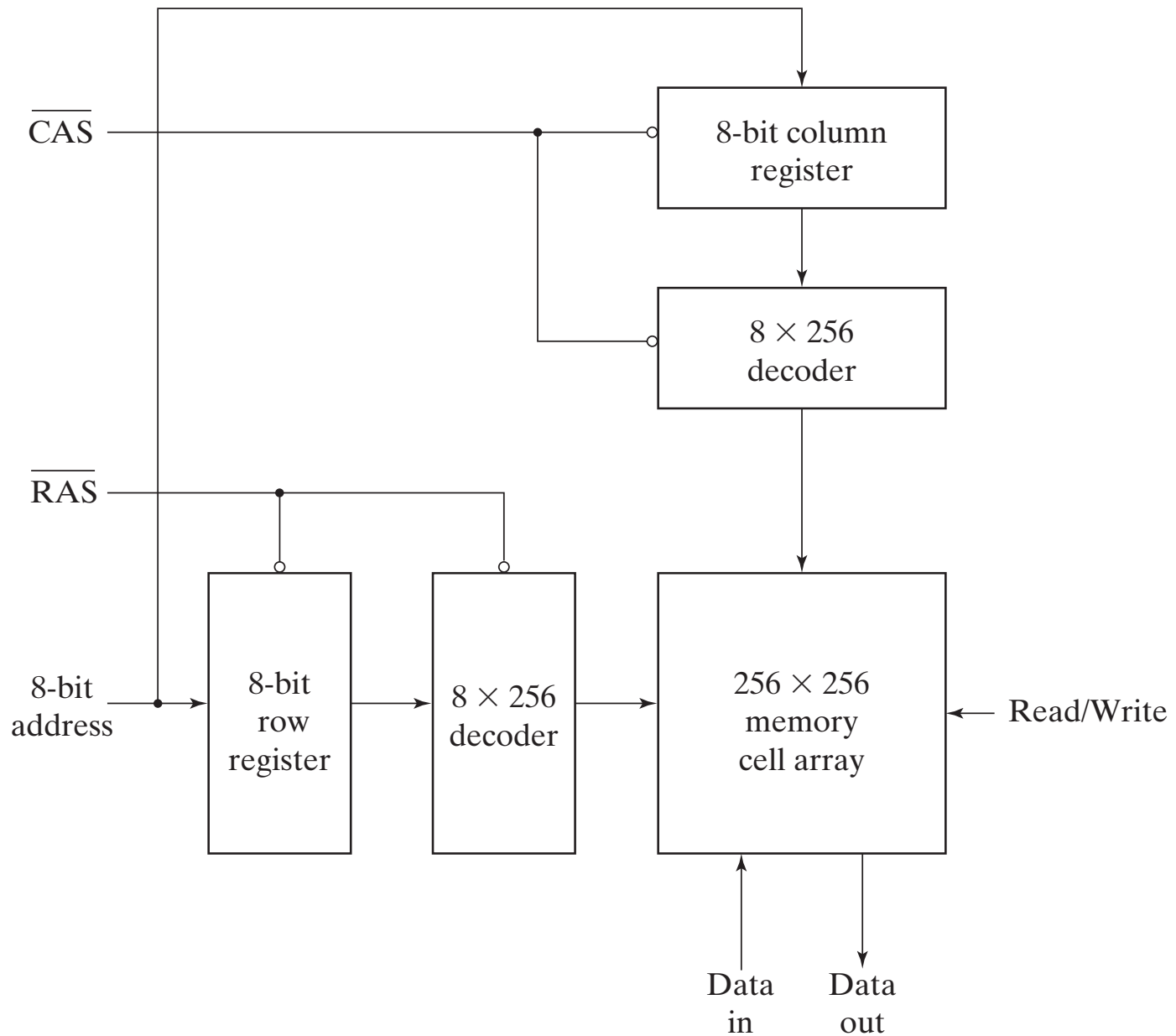


Fig. 7-8 Address Multiplexing for a 64K DRAM



 


Fig. 7-9 ROM Block Diagram

 


Fig. 7-10 Internal Logic of a  $32 \times 8$  ROM


 


Fig. 7-11 Programming the ROM According to Table 7-3

 


(a) Block diagram


$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

(b) ROM truth table


Fig. 7-12 ROM Implementation of Example 7-1

 

(a) Programmable read-only memory (PROM)

 

(b) Programmable array logic (PAL)

 

(c) Programmable logic array (PLA)

Fig. 7-13 Basic Configuration of Three PLDs

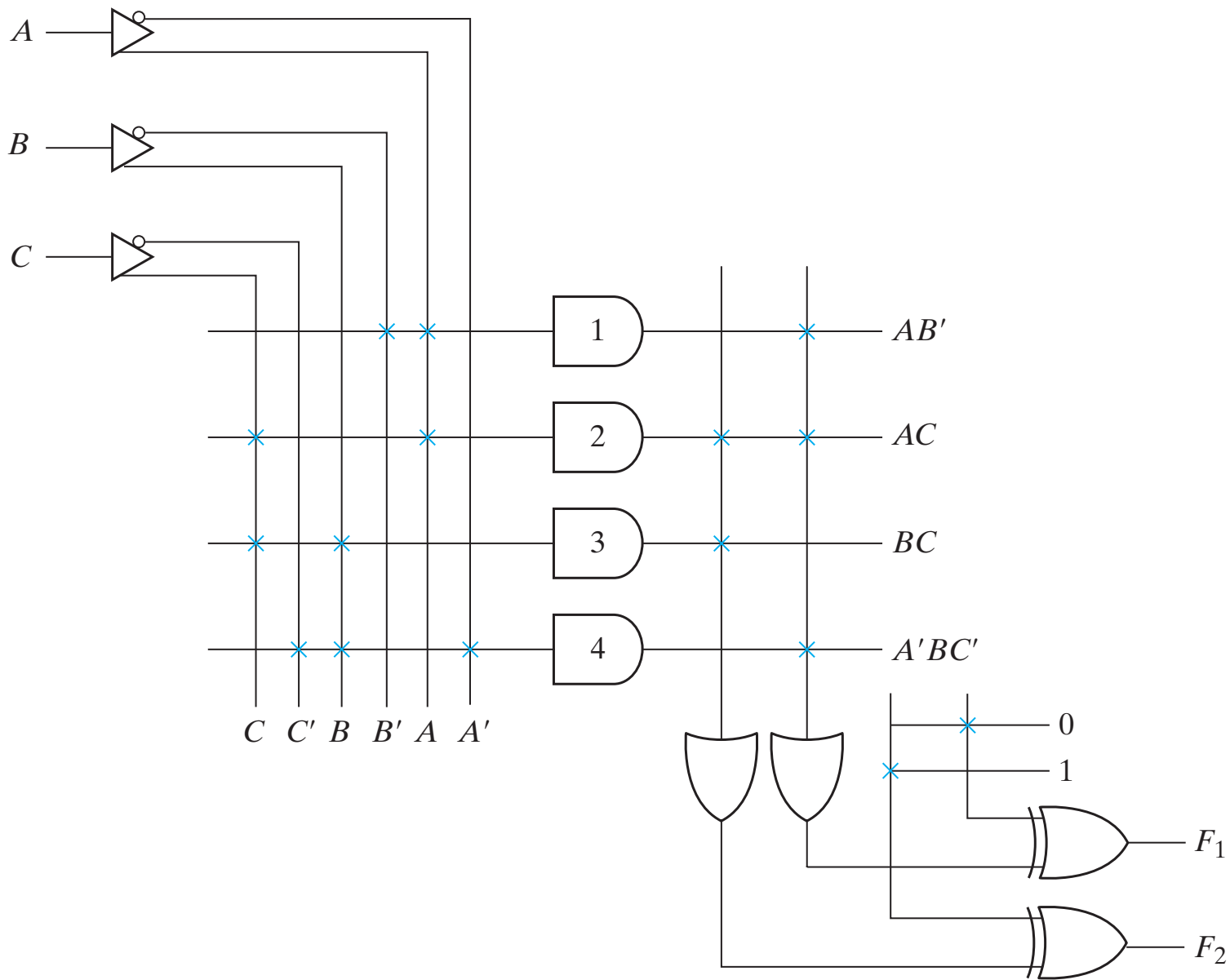


Fig. 7-14 PLA with 3 Inputs, 4 Product Terms, and 2 Outputs

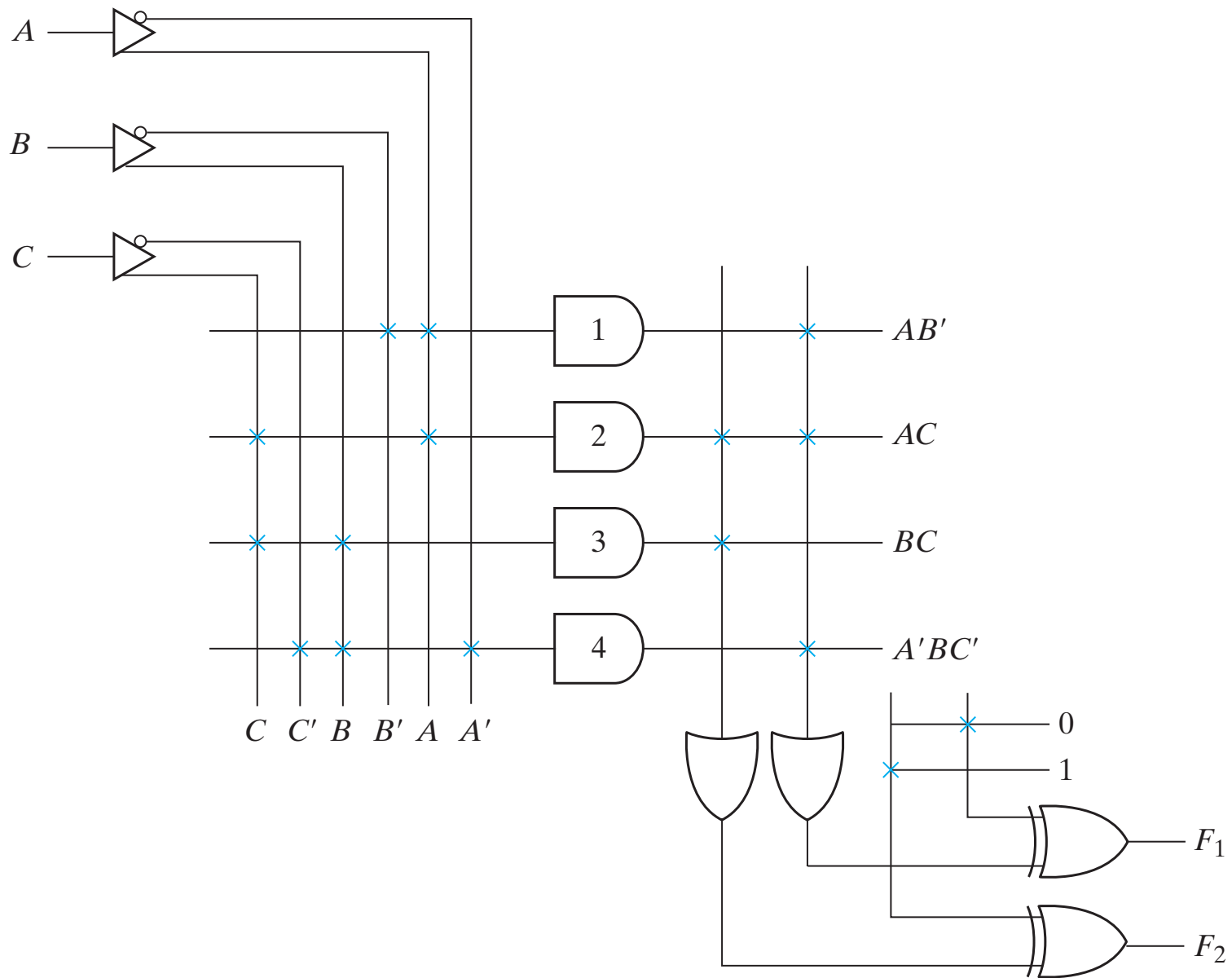


Fig. 7-14 PLA with 3 Inputs, 4 Product Terms, and 2 Outputs

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1	1	0	1
<i>A</i>	1	1	0	0	0
		<i>C</i>			

$$F_1 = A'B' + A'C' + B'C'$$

$$F_1 = (AB + AC + BC)'$$

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1	0	0	0
<i>A</i>	1	0	1	1	1
		<i>C</i>			

$$F_2 = AB + AC + A'B'C'$$

$$F_2 = (A'C + A'B + AB'C')'$$

PLA programming table

	Product term	Inputs			Outputs	
		<i>A</i>	<i>B</i>	<i>C</i>	(C)	(T)
					<i>F</i> <sub>1</sub>	<i>F</i> <sub>2</sub>
<i>AB</i>	1	1	1	–	1	1
<i>AC</i>	2	1	–	1	1	1
<i>BC</i>	3	–	1	1	1	–
<i>A'B'C'</i>	4	0	0	0	–	1

Fig. 7-15 Solution to Example 7-2



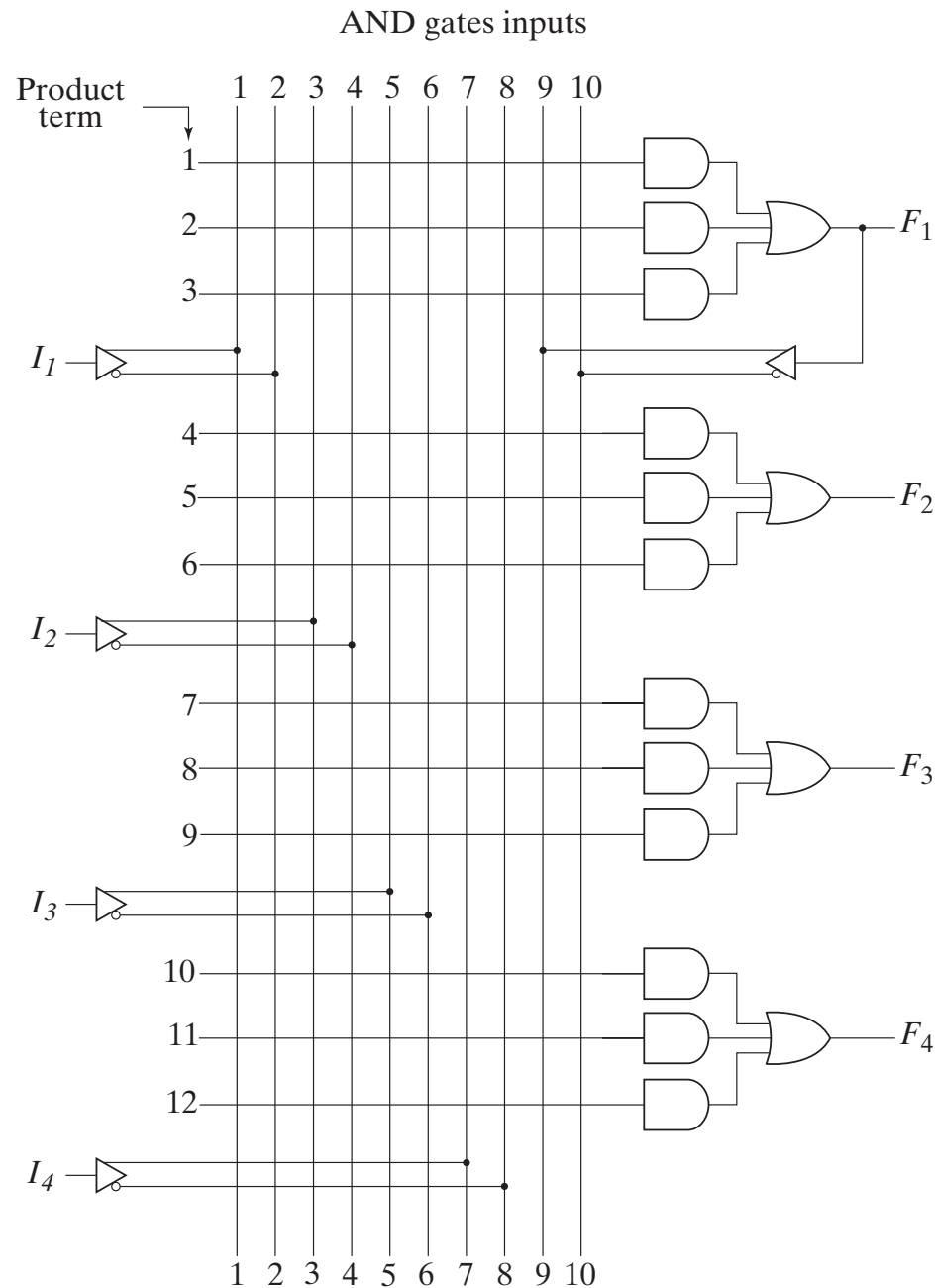


Fig. 7-16 PAL with Four Inputs, Four Outputs, and Three-Wide AND-OR Structure

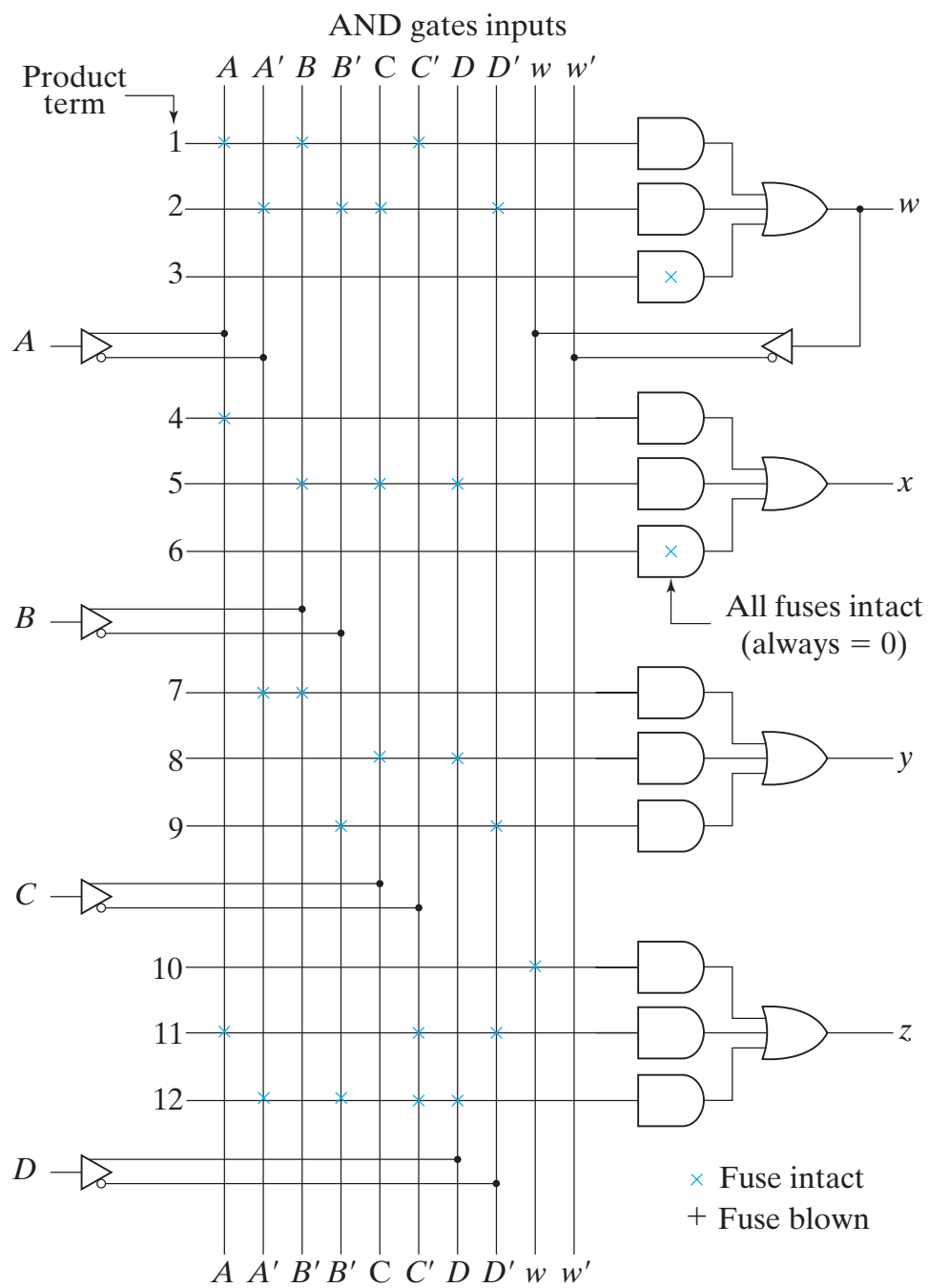


Fig. 7-17 Fuse Map for PAL as Specified in Table 7-6

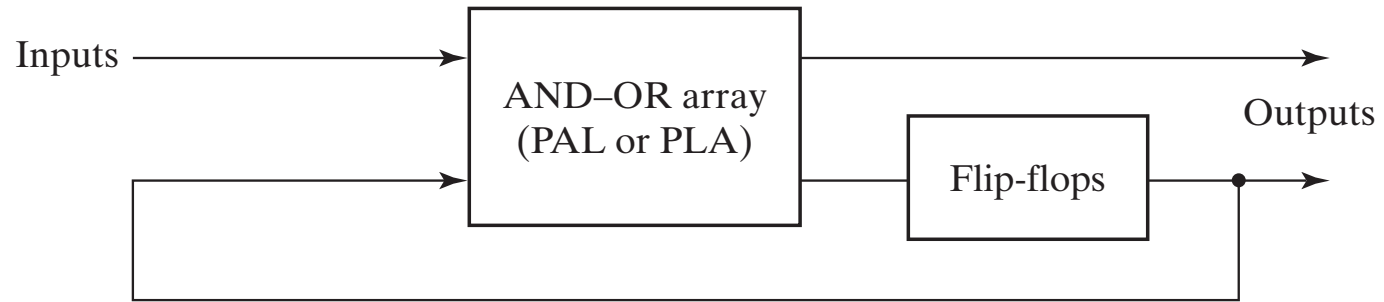


Fig. 7-18 Sequential Programmable Logic Device

 


Fig. 7-19 Basic Macrocell Logic

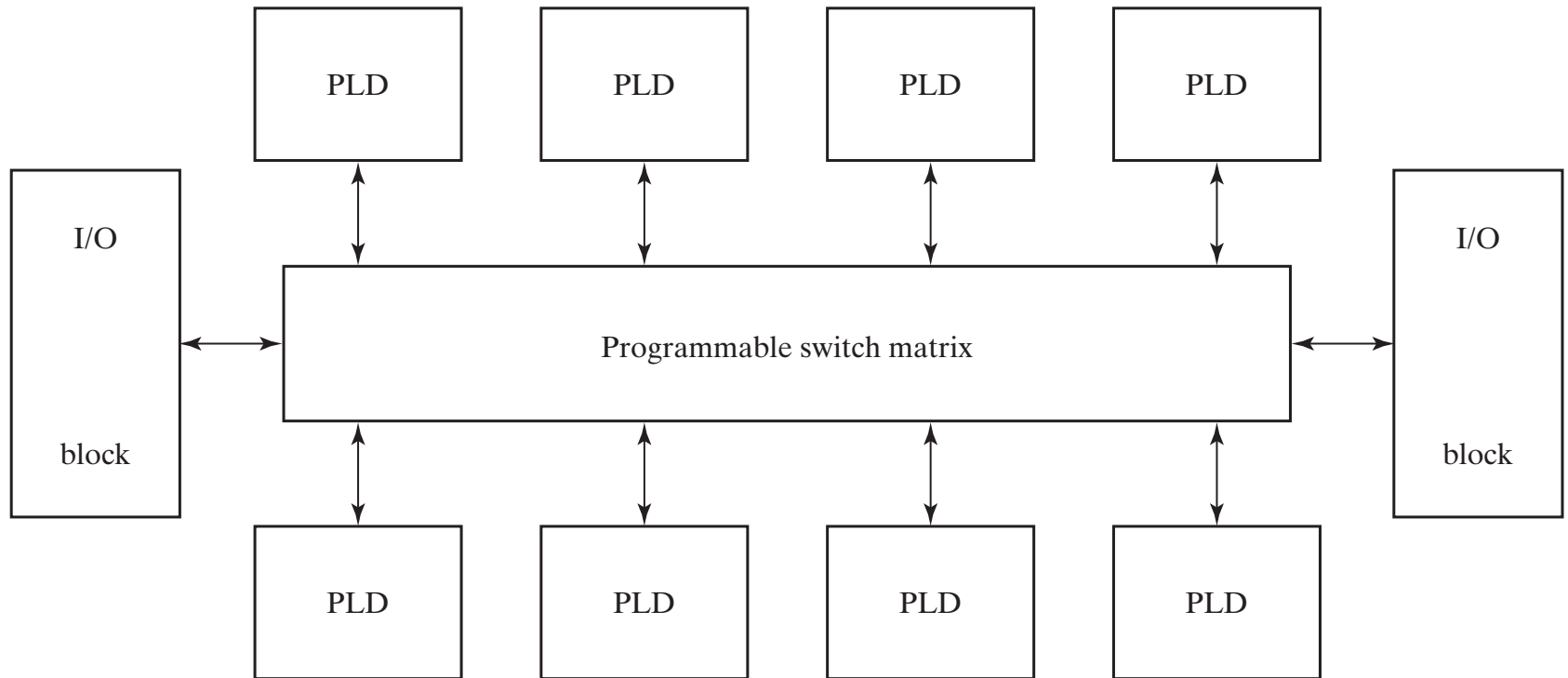


Fig. 7-20 General CPLD Configuration

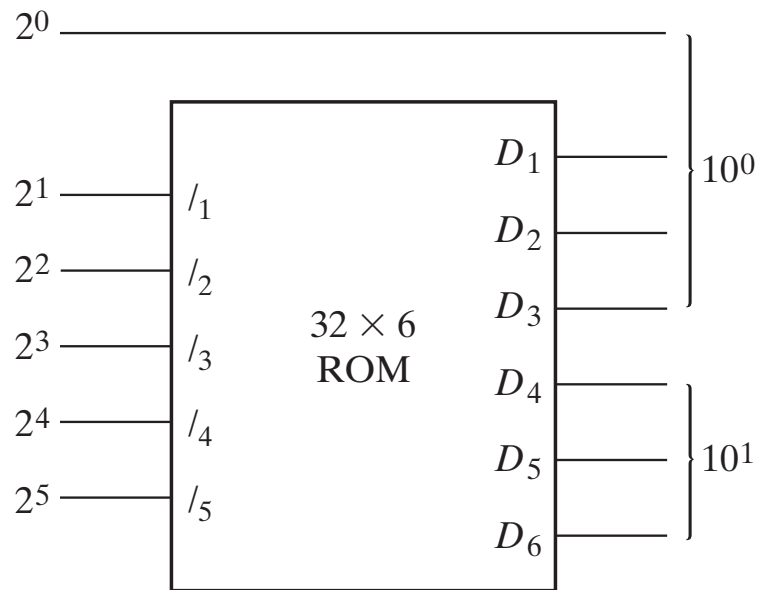


Fig. P7-17