

# Digital Design

## Lecture 9

### Sequential Logic

# A General Sequential Circuit


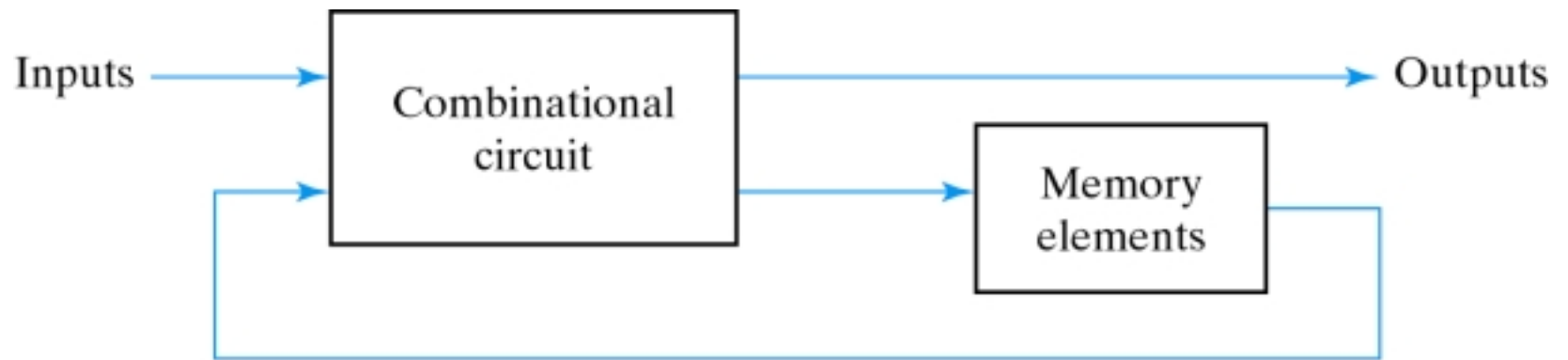


Fig. 5-1 Block Diagram of Sequential Circuit

# Synchronous Sequential Circuits

 

(a) Block diagram



(b) Timing diagram of clock pulses

Fig. 5-2 Synchronous Clocked Sequential Circuit

# Set/Reset Latch (NORs)


 


Fig. 5-3 SR Latch with NOR Gates

# Set/Reset Latch (NANDs)

 


(a) Logic diagram

(b) Function table

Fig. 5-4 SR Latch with NAND Gates

# SR Latch with Control

 


(a) Logic diagram

<i>C</i>	<i>S</i>	<i>R</i>	Next state of <i>Q</i>
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; Reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate

(b) Function table

Fig. 5-5 SR Latch with Control Input

# D Latch

 

(a) Logic diagram

$C$	$D$	Next state of $Q$
0	X	No change
1	0	$Q = 0$ ; Reset state
1	1	$Q = 1$ ; Set state

(b) Function table

Fig. 5-6 D Latch

# Latch Symbols

 


Fig. 5-7 Graphic Symbols for Latches



# Clock Response



(a) Response to positive level



(b) Positive-edge response



(c) Negative-edge response

Fig. 5-8 Clock Response in Latch and Flip-Flop

# Master-Slave D Flip-Flop

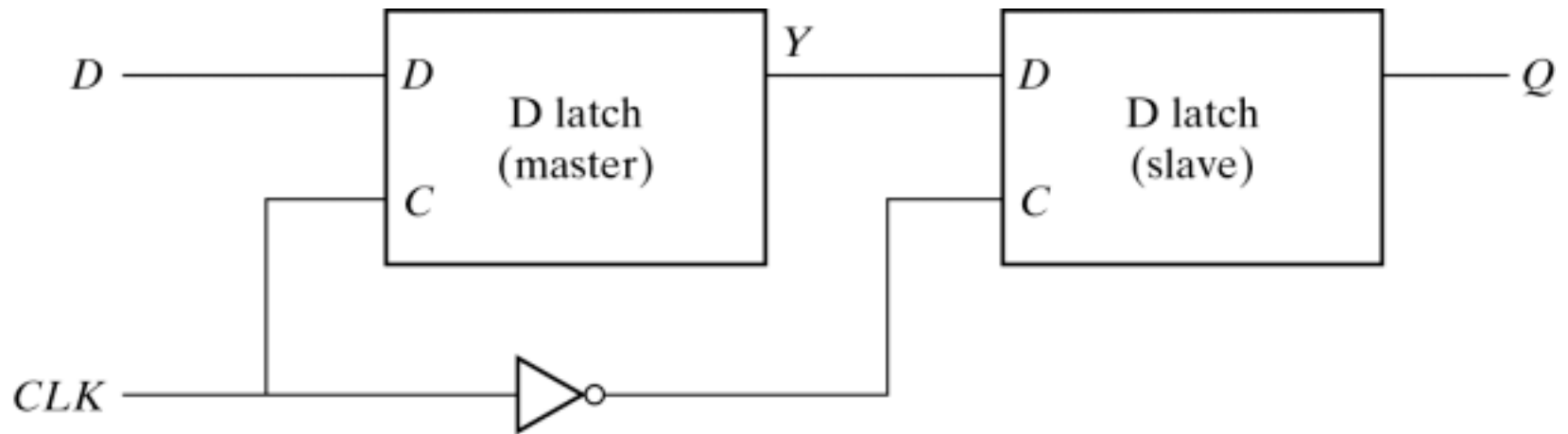


Fig. 5-9 Master-Slave  $D$  Flip-Flop

# D-Type Positive-Edge Triggered Flip-Flop



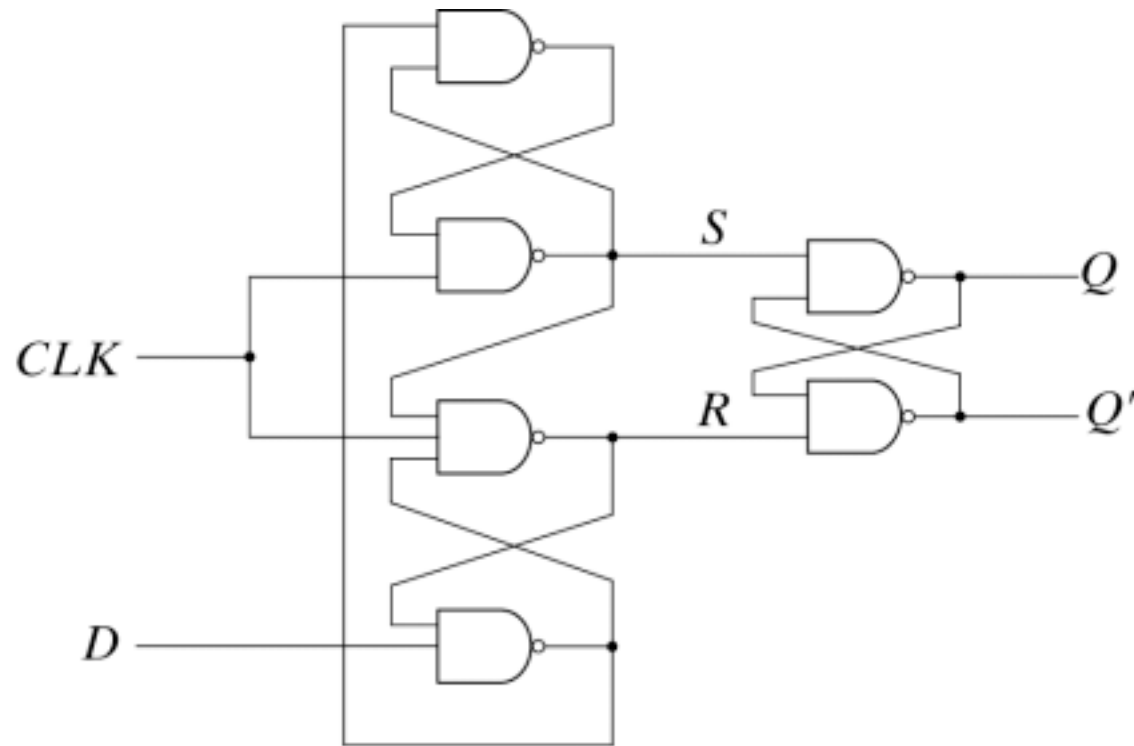


Fig. 5-10 *D*-Type Positive-Edge-Triggered Flip-Flop
 
# Edge-Triggered D Flip-Flop Graphic Symbol




(a) Positive-edge

 


(a) Negative-edge

Fig. 5-11 Graphic Symbol for Edge-Triggered *D* Flip-Flop

# JK Flip-Flop

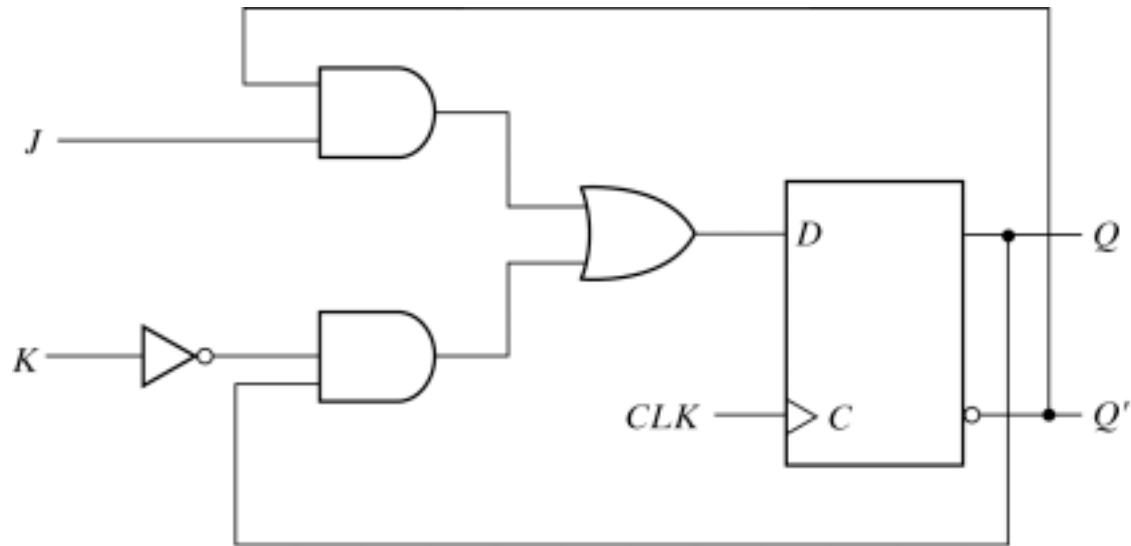

(a) Circuit diagram

 

(b) Graphic symbol

Fig. 5-12 JK Flip-Flop

# Flip-Flop Characteristic Tables

D – Flip-Flop

D	Q(t+1)
0	0 - Reset
1	1 - Set

T – Flip-Flop


T	Q(t+1)
0	Q(t) – No change
1	Q'(t) - Complement

JK – Flip-Flop


J	K	Q(t+1)
0	0	Q(t) – No change
0	1	0 – Reset
1	0	1 – Set
1	1	Q'(t) – Complement

Table 5.1


# T Flip-Flop

 

(a) From  $JK$  flip-flop

 


(b) From  $D$  flip-flop

 


(c) Graphic symbol

Fig. 5-13 T Flip-Flop

# D Flip-Flop with Reset

 

(a) Circuit diagram

 

(b) Graphic symbol

$R$	$C$	$D$	$Q$	$Q'$
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

(b) Function table

Fig. 5-14 D Flip-Flop with Asynchronous Reset



# Sequential Circuit Analysis

 


Fig. 5-15 Example of Sequential Circuit

# State Diagrams


 


Fig. 5-16 State Diagram of the Circuit of Fig. 5-15

# Sequential Circuit: D Flip-Flop

 

(a) Circuit diagram

Present state	Inputs		Next state
$A$	$x$	$y$	$A$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(b) State table



(c) State diagram

Fig. 5-17 Sequential Circuit with  $D$  Flip-Flop

# Sequential Circuit: JK Flip-Flop

 


Fig. 5-18 Sequential Circuit with JK Flip-Flop

# State Diagram for JK Circuit

 


Fig. 5-19 State Diagram of the Circuit of Fig. 5-18

# Sequential Circuit: T Flip-Flop

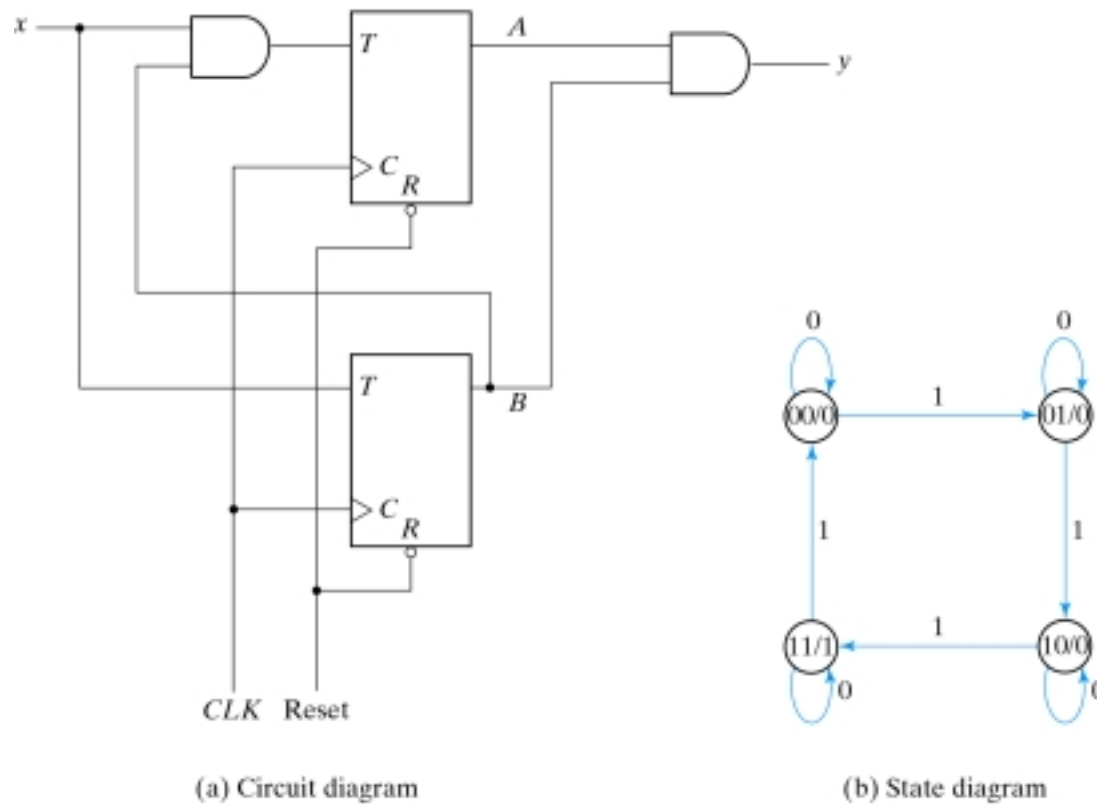


Fig. 5-20 Sequential Circuit with  $T$  Flip-Flops

# Mealy and Moore Models

## Finite State Machines

- Mealy
  - Output is a function of both the present state and the present input
  - See Figure 5-15 (Slide 16: Sequential Analysis)
- Moore
  - Output is only a function of the current state
  - See Figure 5-18 (Slide 19: JK Flip-Flop)