



Alexander-Sadiku

Fundamentals of Electric Circuits

Chapter 10

Sinusoidal Steady-State Analysis

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

1



Sinusoidal Steady-State Analysis

Chapter 10


- 10.1 Basic Approach
- 10.2 Nodal Analysis
- 10.3 Mesh Analysis
- 10.4 Superposition Theorem
- 10.5 Source Transformation
- 10.6 Thevenin and Norton Equivalent Circuits

2

10.1 Basic Approach (1)

Steps to Analyze AC Circuits:

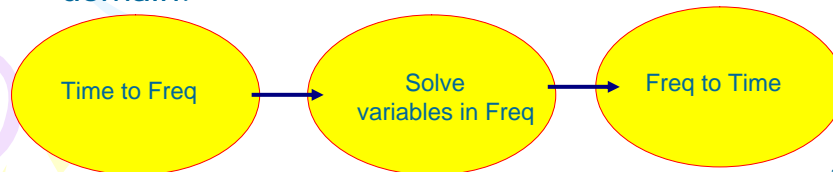1. **Transform** the circuit to the **phasor or frequency domain**.
2. **Solve** the problem using circuit techniques (nodal analysis, mesh analysis, superposition, etc.).
3. **Transform** the resulting phasor to the time domain.




3

10.2 Nodal Analysis (1)

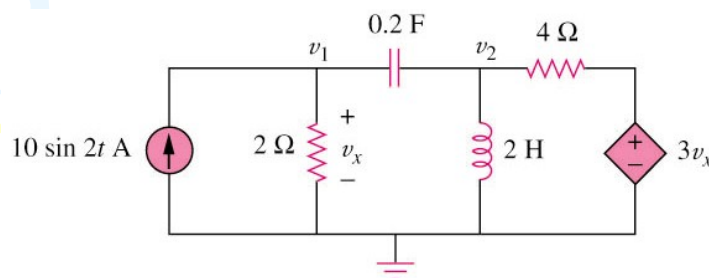Example 1

Using nodal analysis, find v_1 and v_2 in the circuit of figure below.



Answer:


$$v_1(t) = 11.32 \sin(2t + 60.01^\circ) \text{ V}$$

$$v_2(t) = 33.02 \sin(2t + 57.12^\circ) \text{ V}^4$$

10.3 Mesh Analysis (1)

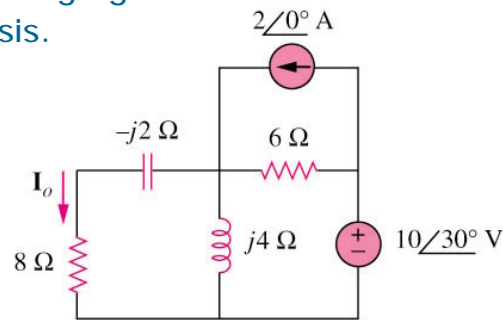Example 2

Find I_o in the following figure using mesh analysis.



Answer: $I_o = 1.194 \angle 65.44^\circ \text{ A}$

5

10.4 Superposition Theorem (1)

When a circuit has sources operating at different frequencies,

The separate phasor circuit for each frequency must be solved independently, and


The total response is the sum of time-domain responses of all the individual phasor circuits.

6

10.4 Superposition Theorem (2)

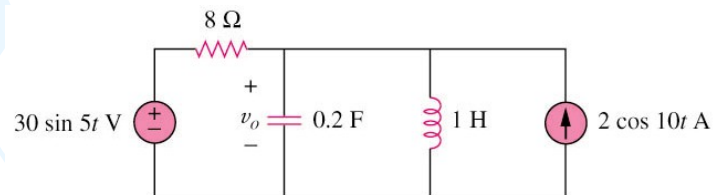Example 3


Calculate v_o in the circuit of figure shown below using the superposition theorem.



$$V_o = 4.631 \sin(5t - 81.12^\circ) + 1.051 \cos(10t - 86.24^\circ) \text{ V}$$

7

10.5 Source Transformation (1)

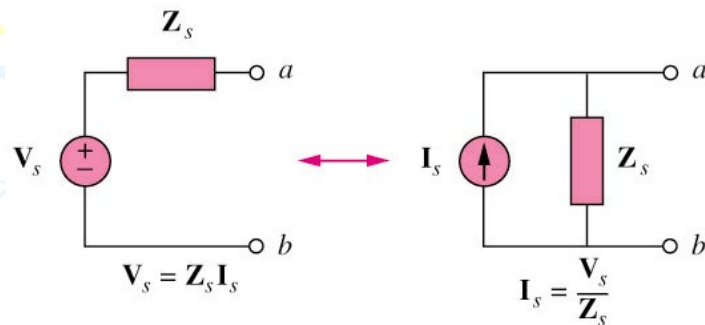


8

10.5 Source Transformation (2)

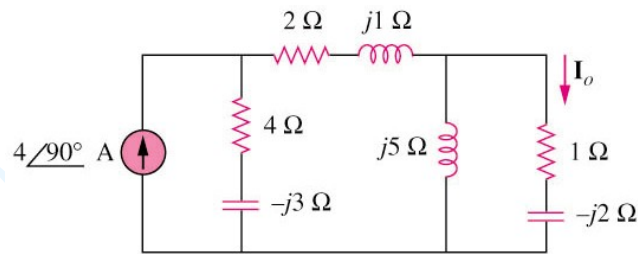Example 4


Find I_o in the circuit of figure below using the concept of source transformation.



$$I_o = 3.288 \angle 99.46^\circ \text{ A}$$

9

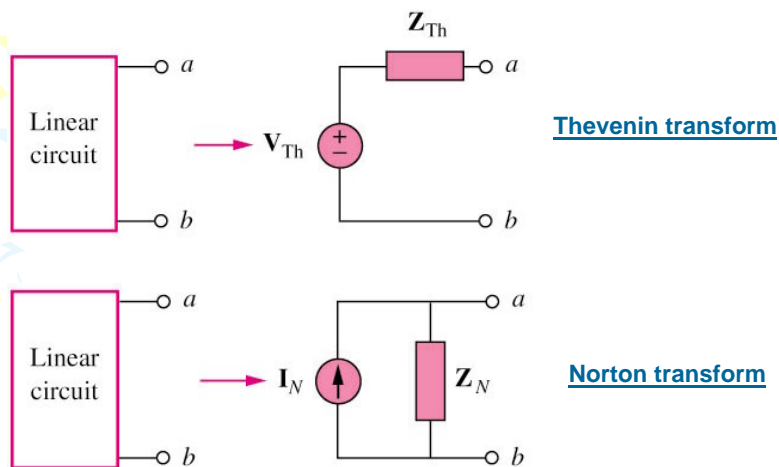10.6 Thevenin and Norton Equivalent Circuits (1)




10

10.6 Thevenin and Norton Equivalent Circuits (2)

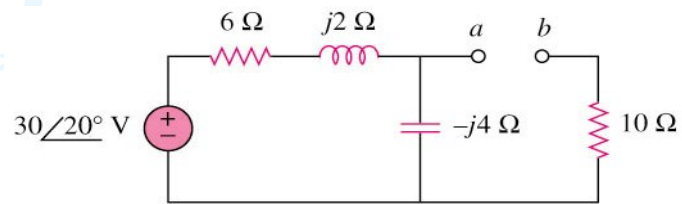Example 5

Find the Thevenin equivalent at terminals a b of the circuit below.



$$Z_{th} = 12.4 - j3.2\ \Omega$$

$$V_{TH} = 18.97\angle -51.57^\circ\text{ V}$$

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.