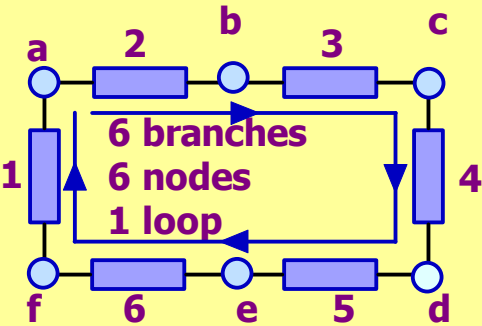


SINGLE LOOP CIRCUITS


BACKGROUND: USING KVL AND KCL WE CAN WRITE ENOUGH EQUATIONS TO ANALYZE ANY LINEAR CIRCUIT. WE NOW START THE STUDY OF SYSTEMATIC, AND EFFICIENT, WAYS OF USING THE FUNDAMENTAL CIRCUIT LAWS



ALL ELEMENTS IN SERIES
ONLY ONE CURRENT

WRITE 5 KCL EQS OR DETERMINE THE ONLY CURRENT FLOWING

VOLTAGE DIVISION: THE SIMPLEST CASE

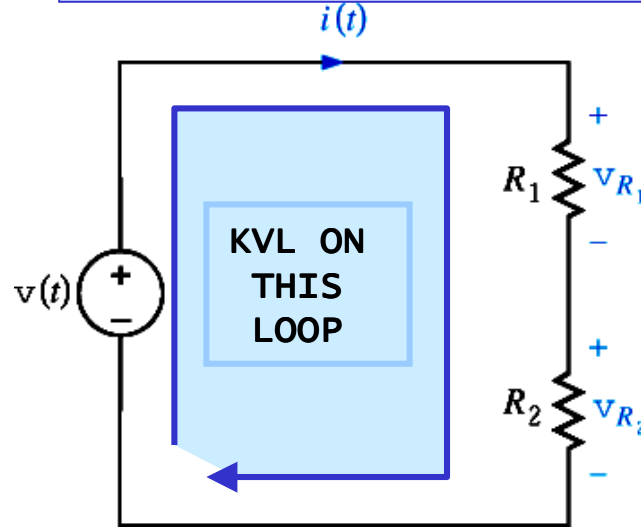

$$\text{KVL} \quad -v(t) + v_{R_1} + v_{R_2} = 0$$

OHM'S LAW

$$v_{R_1} = R_1 i(t)$$

$$v_{R_2} = R_2 i(t)$$

$$\text{SUBSTITUTION} \quad v(t) = R_1 i(t) + R_2 i(t)$$

$$i(t) = \frac{v(t)}{R_1 + R_2}$$

$$v_{R_1} = R_1 i(t)$$


$$= R_1 \left[\frac{v(t)}{R_1 + R_2} \right]$$

$$v_{R_2} = \frac{R_2}{R_1 + R_2} v(t)$$


IMPORTANT VOLTAGE DIVIDER EQUATIONS

$$= \frac{R_1}{R_1 + R_2} v(t)$$

SUMMARY OF BASIC VOLTAGE DIVIDER

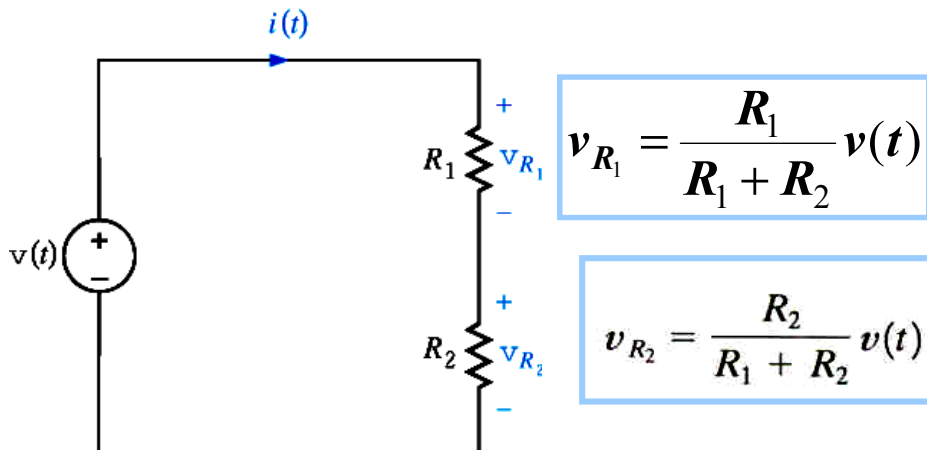

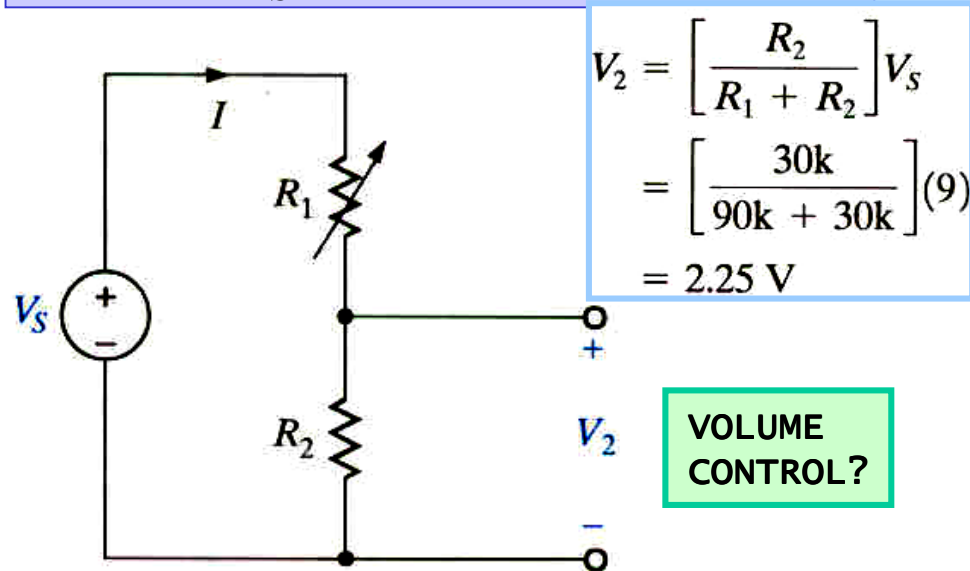EXAMPLE: $V_S = 9V$, $R_1 = 90k\Omega$, $R_2 = 30k\Omega$





VOLUME CONTROL?

$R_1 = 15k\Omega \Rightarrow$

$$V_2 = \left[\frac{30k}{30k + 15k} \right] 9$$

$$= 6 V$$

A "PRACTICAL" POWER APPLICATION

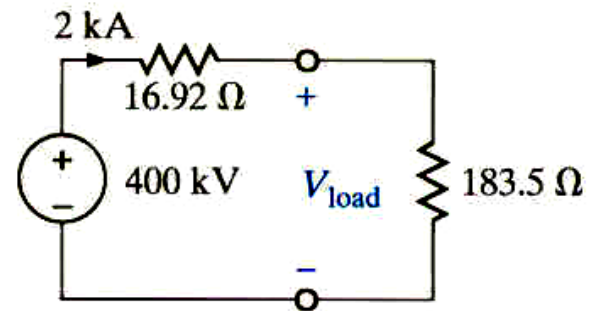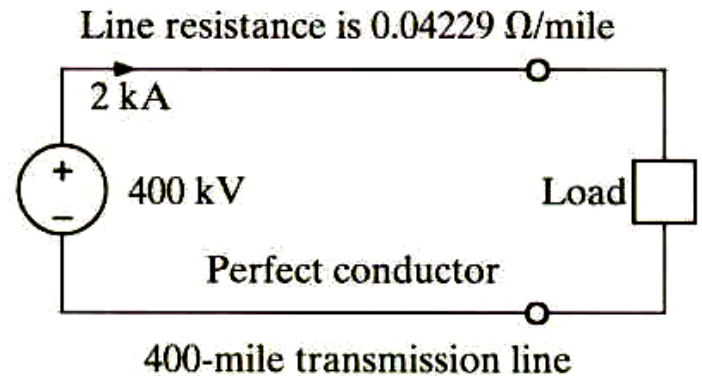

$$V_{load} = \left[\frac{183.5}{183.5 + 16.92} \right] 400k$$

$$= 366.24 kV$$

$$P_{load} = I^2 R_{load}$$

$$= 734 MW$$

$$P_{line} = P_{in} - P_{load} = I^2 R_{line}$$


$$= 66 MW \quad \text{LOSSES!!!}$$

HOW CAN ONE REDUCE THE LOSSES?




THE CONCEPT OF EQUIVALENT CIRCUIT

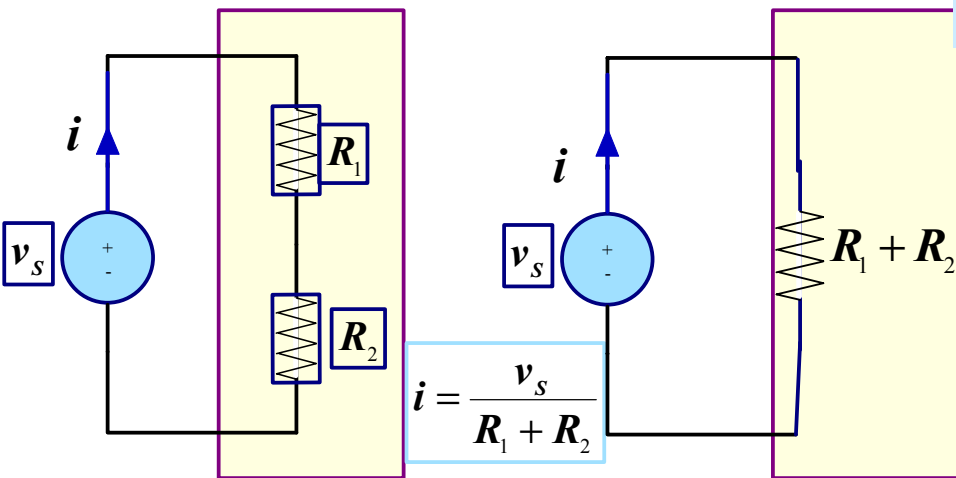THIS CONCEPT WILL OFTEN BE USED TO SIMPLIFY THE ANALYSIS OF CIRCUITS. WE INTRODUCE IT HERE WITH A VERY SIMPLE VOLTAGE DIVIDER






AS FAR AS THE CURRENT IS CONCERNED BOTH CIRCUITS ARE EQUIVALENT. THE ONE ON THE RIGHT HAS ONLY ONE RESISTOR

SERIES COMBINATION OF RESISTORS

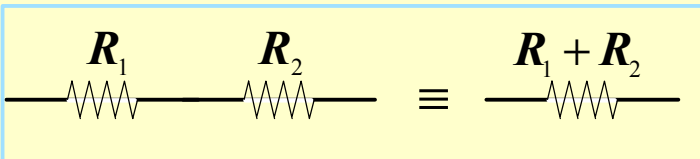

THE DIFFERENCE BETWEEN ELECTRIC CONNECTION AND PHYSICAL LAYOUT

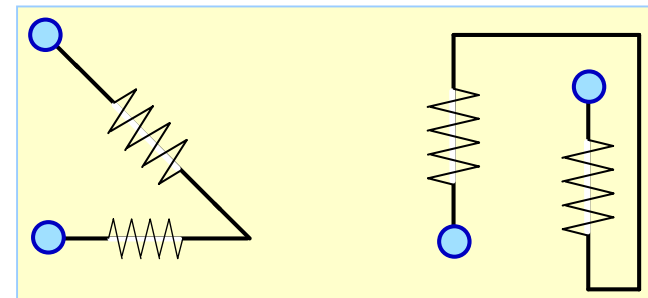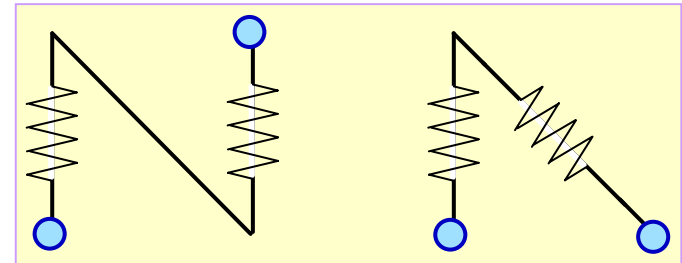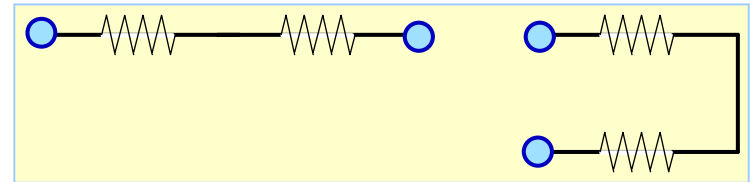SOMETIMES, FOR PRACTICAL CONSTRUCTION REASONS, COMPONENTS THAT ARE ELECTRICALLY CONNECTED MAY BE PHYSICALLY QUITE APART



IN ALL CASES THE RESISTORS ARE CONNECTED IN SERIES



CONNECTOR SIDE


ILLUSTRATING THE DIFFERENCE BETWEEN PHYSICAL LAYOUT AND ELECTRICAL CONNECTIONS

- PHYSICAL NODE
- PHYSICAL NODE

SECTION OF 14.4 KB VOICE/DATA MODEM

CORRESPONDING POINTS


COMPONENT SIDE

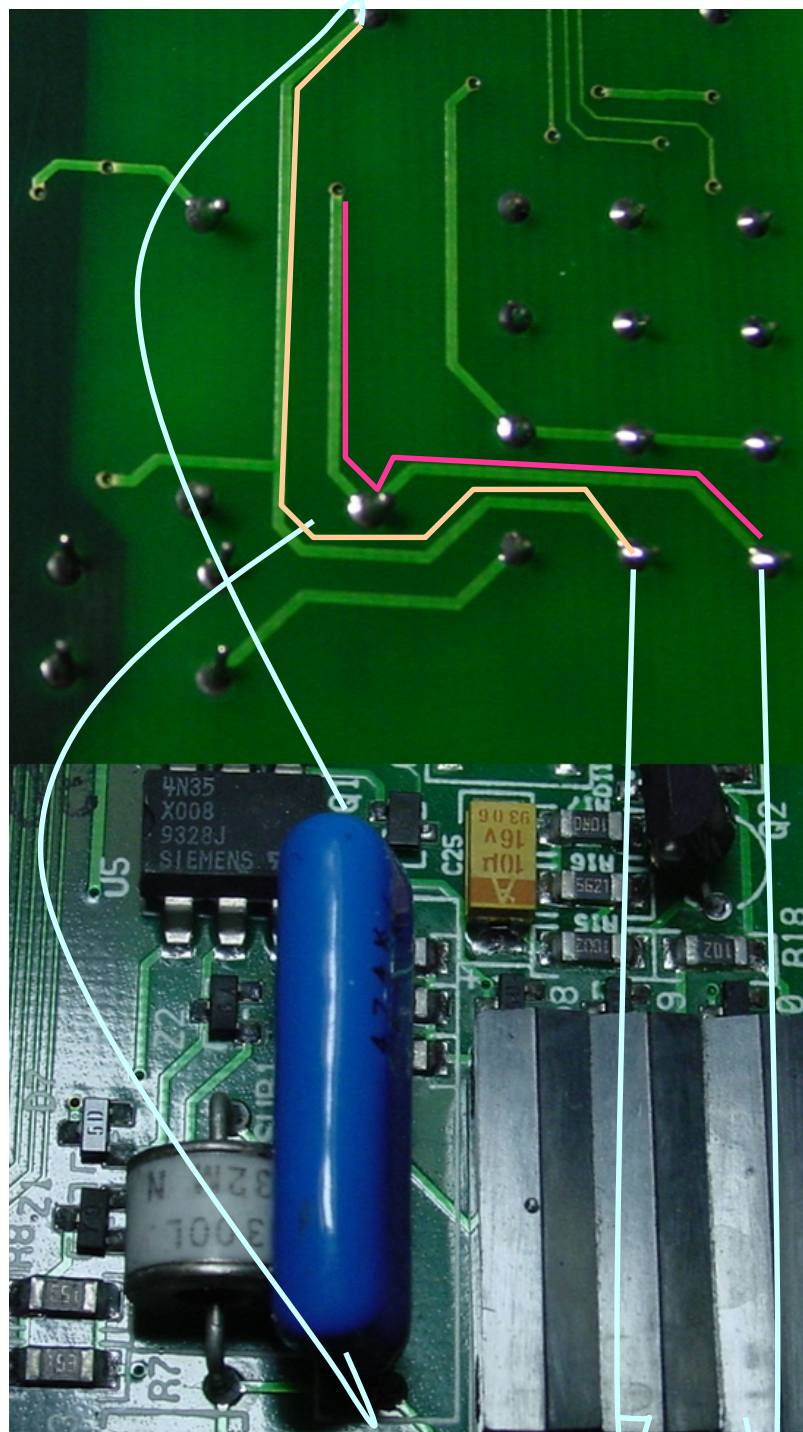

FIRST GENERALIZATION: MULTIPLE SOURCES

Voltage sources in series can be algebraically added to form an equivalent source.

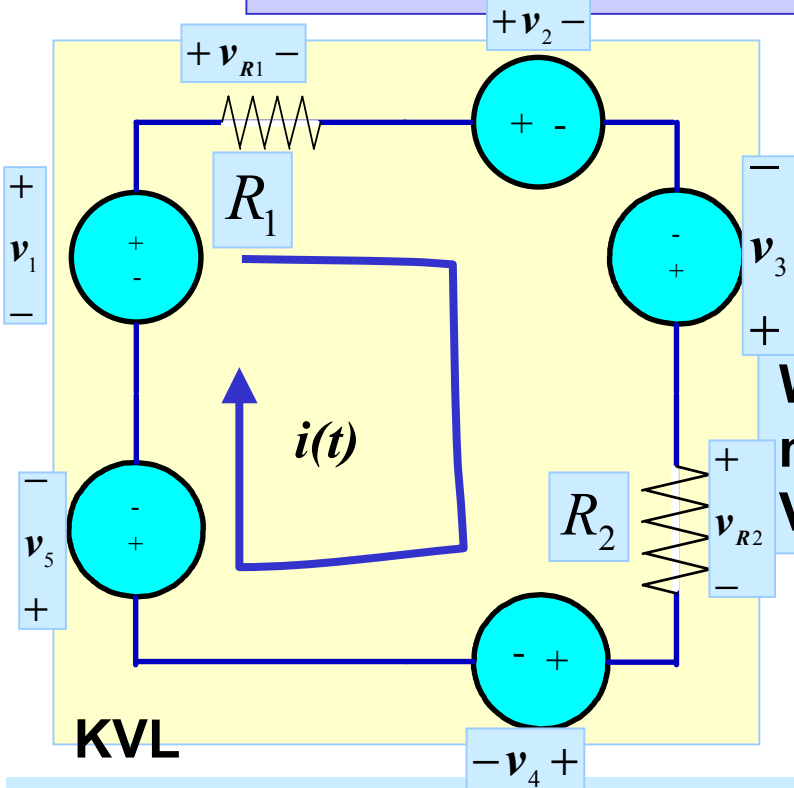We select the reference direction to move along the path.
Voltage drops are subtracted from rises




KVL

$$v_{R1} + v_2 - v_3 + v_{R2} + v_4 + v_5 - v_1 = 0$$


Collect all sources on one side

$$\underline{(v_1 - v_2 + v_3 - v_4 - v_5)} = v_{R1} + v_{R2}$$
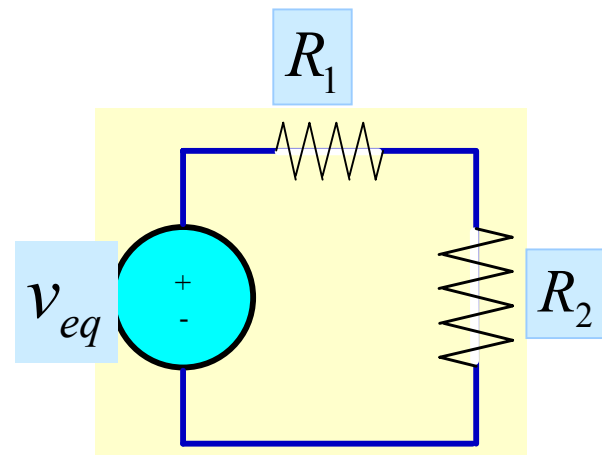
$$\underline{(v_{eq})} = v_{R1} + v_{R2}$$



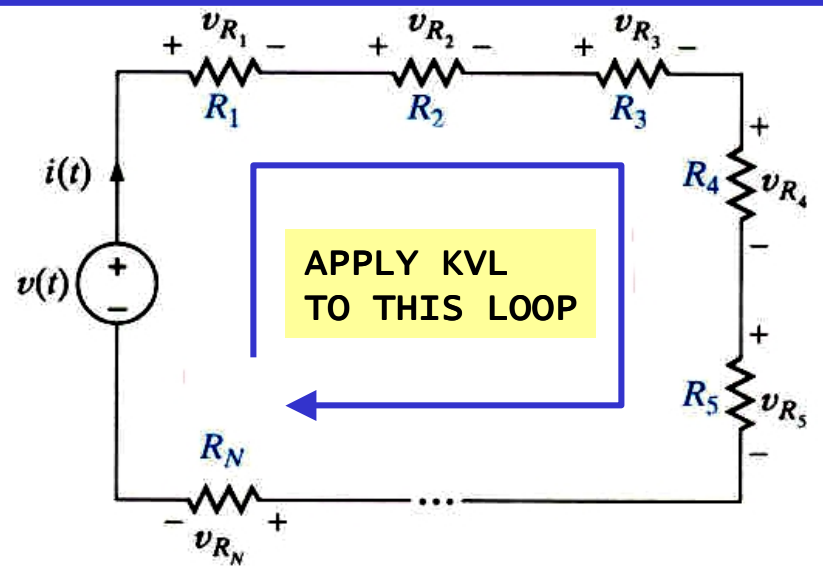SECOND GENERALIZATION: MULTIPLE RESISTORS



$$v(t) = v_{R_1} + v_{R_2} + \dots + v_{R_N}$$

AND OHM'S LAW
 $= R_1 i(t) + R_2 i(t) + \dots + R_N i(t)$


$$R_S = R_1 + R_2 + \dots + R_N$$

$$i(t) = \frac{v(t)}{R_S}$$

$$v_{R_i} = R_i i \Rightarrow v_{R_i} = \frac{R_i}{R_S} v(t)$$

VOLTAGE DIVISION FOR MULTIPLE RESISTORS

FIND $I, V_{bd}, P(30k)$

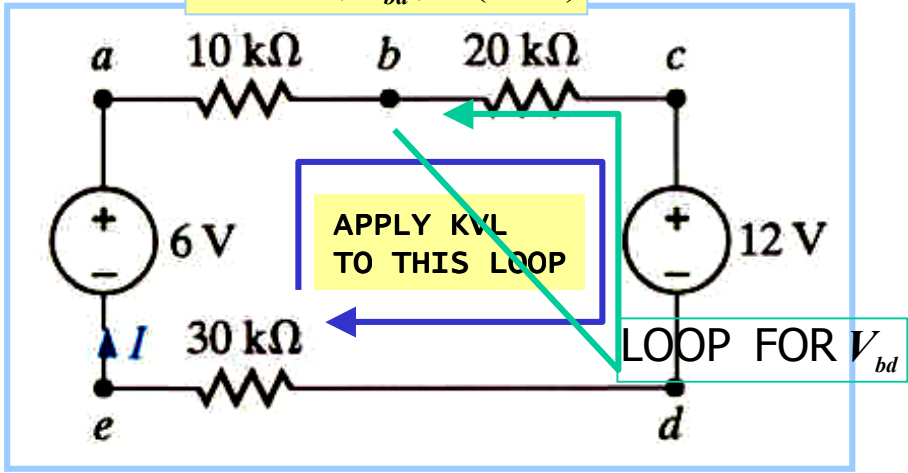

$$10kI + 20kI + 12 + 30kI - 6 = 0$$


$$I = -0.1 \text{ mA}$$

$$V_{bd} - 12 - 20[k\Omega]I = 0 \text{ (KVL)} \Rightarrow V_{bd} = 10V$$

POWER ON 30kΩ RESISTOR
 $P = I^2 R = (-10^{-4} \text{ A})^2 (30 * 10^3 \Omega) = 30 \text{ mW}$



THE "INVERSE" VOLTAGE DIVIDER

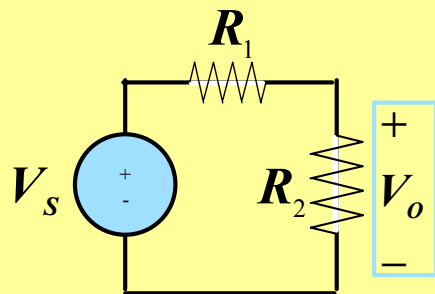


VOLTAGE DIVIDER

"INVERSE" DIVIDER

$$V_o = \frac{R_2}{R_1 + R_2} V_s$$

$$V_s = \frac{R_1 + R_2}{R_2} V_o$$


Find I and V_{bd} in the circuit

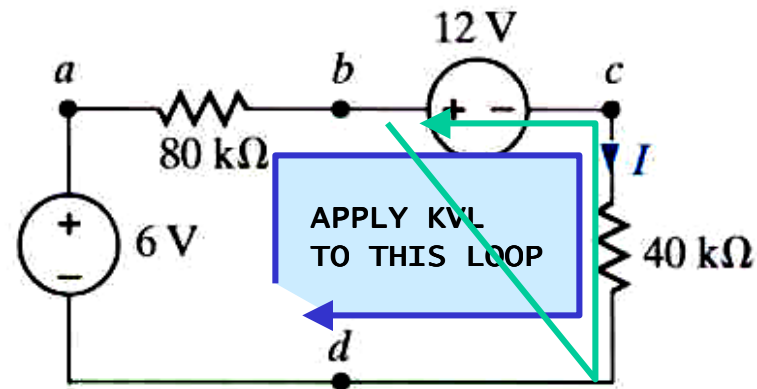

$$-6 + 80kI + 12 + 40kI = 0 \Rightarrow I = -0.05mA$$

$$V_{bd} = -40kI - 12V = 0 \Rightarrow V_{bd} = 10V$$


COMPUTE V_s

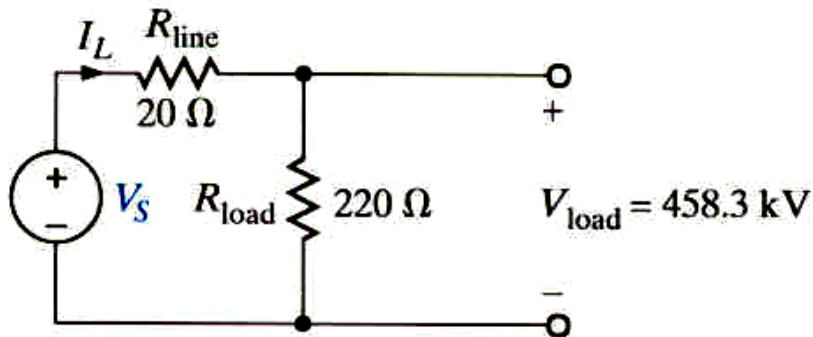

"INVERSE" DIVIDER

$$V_s = \frac{220 + 20}{220} 458.3 = 500kV$$

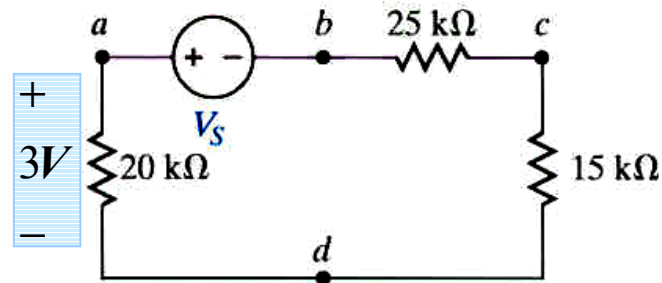
In the network in Fig. E2.11, if V_{ad} is 3 V, find V_s .




INVERSE DIVIDER PROBLEM

$$V_s = \frac{25 + 15 + 20}{20} 3 = 9V$$



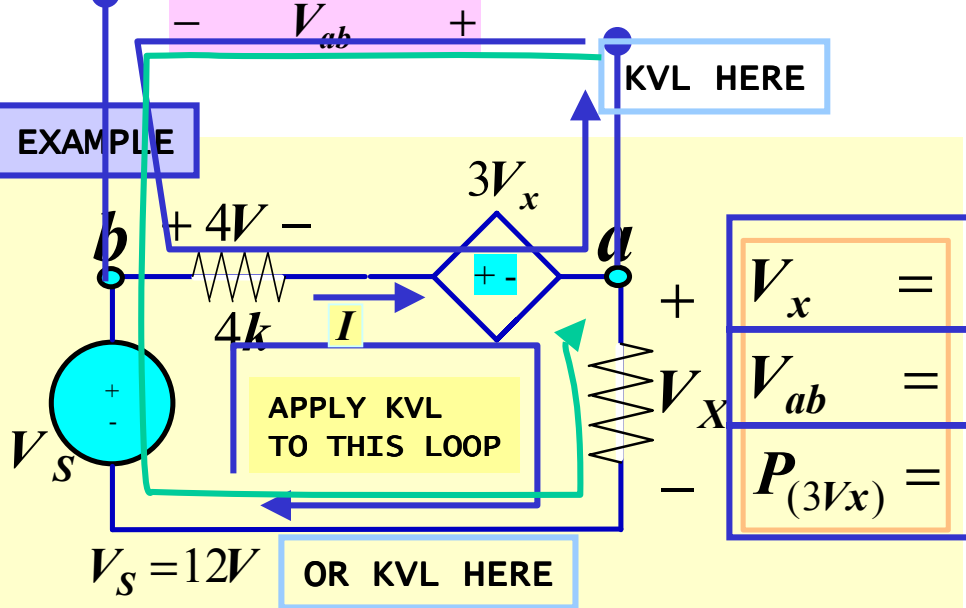

EXAMPLE

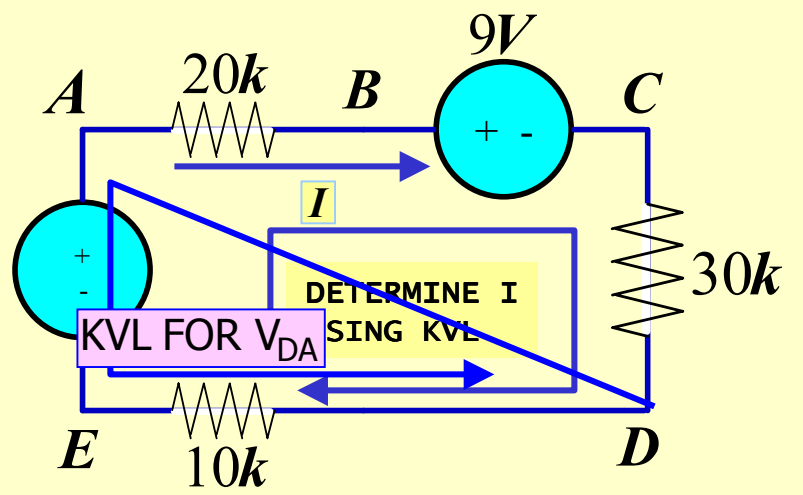

$P_{(3V_x)}$ is the power absorbed or supplied by the dependent source

KVL: $-12 + 4 + 3V_x + V_x = 0 \Rightarrow V_x = 2V$

KVL: $V_{ab} + 4 + 3V_x = 0 \Rightarrow V_{ab} = -10V$

KVL: $V_{ab} + V_s - V_x = 0$

$P_{(3V_x)} = 3V_x I$ (PASSIVE SIGN CONVENTION)

OHMS' LAW: $I = \frac{4V}{4k} = 1mA$

$P_{(3V_x)} = 2[V] * 1[mA] = 2mW$

$V_{DA} =$

$V_{CD} = 30k * I = 1.5V$

$I_{DE} = 0.05mA$

KVL: $-12 + 20k * I + 9 + 30k * I + 10k * I = 0$

$I = \frac{3V}{60k\Omega} = 0.05mA$

KVL: $V_{DA} + 12 - 10k * I = 0$

$V_{DA} = -11.5V$

