

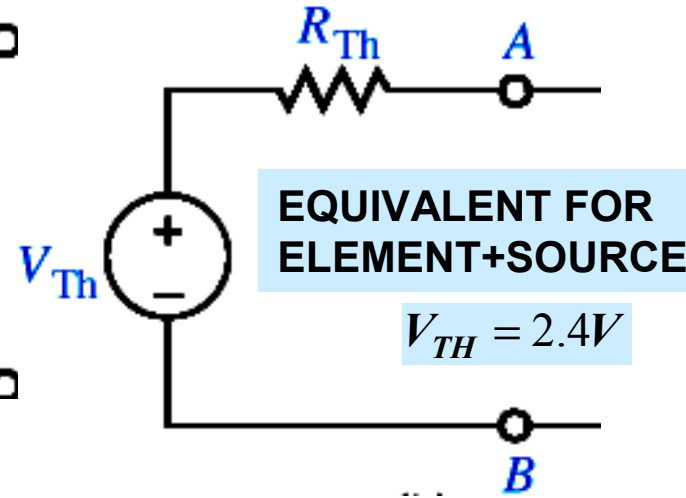
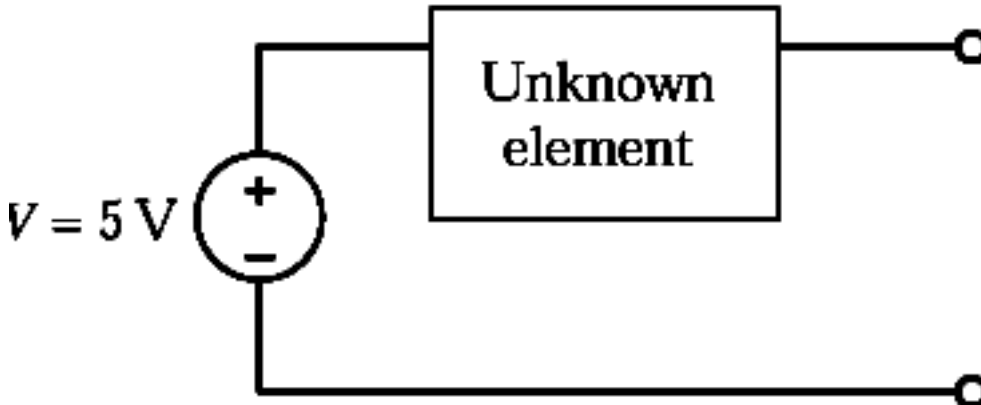



LEARNING BY APPLICATION

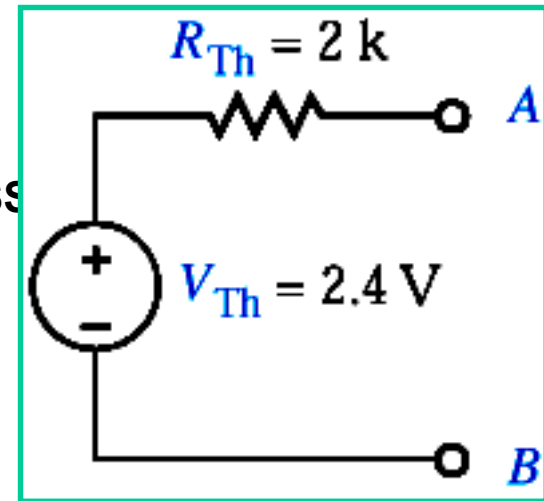FIND THE THEVENIN EQUIVALENT FOR THE UNKNOWN ELEMENT USING A RESISTOR AND A VOLTMETER



+
2.4V
-
(measured in open circuit)

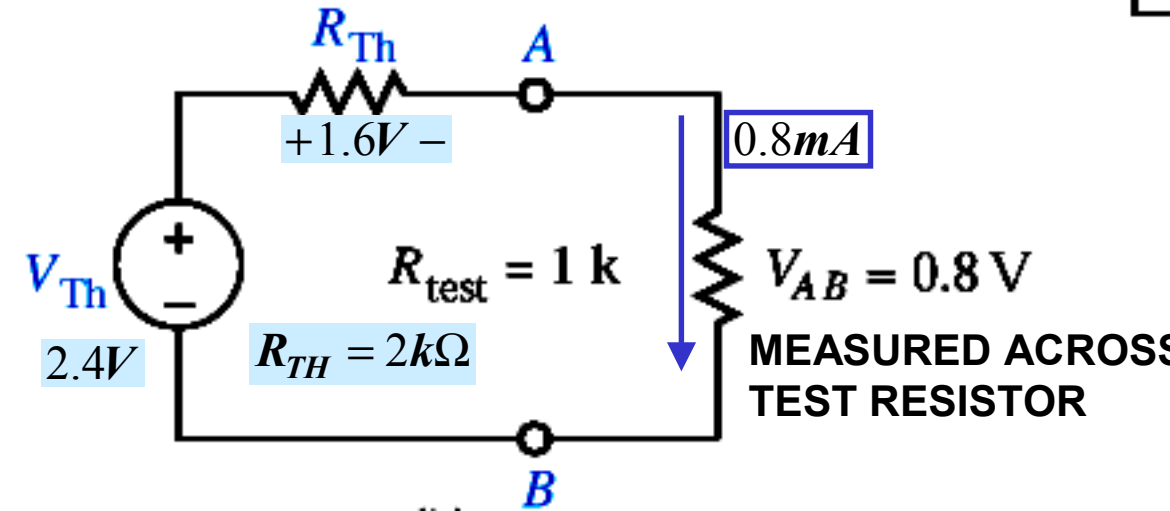

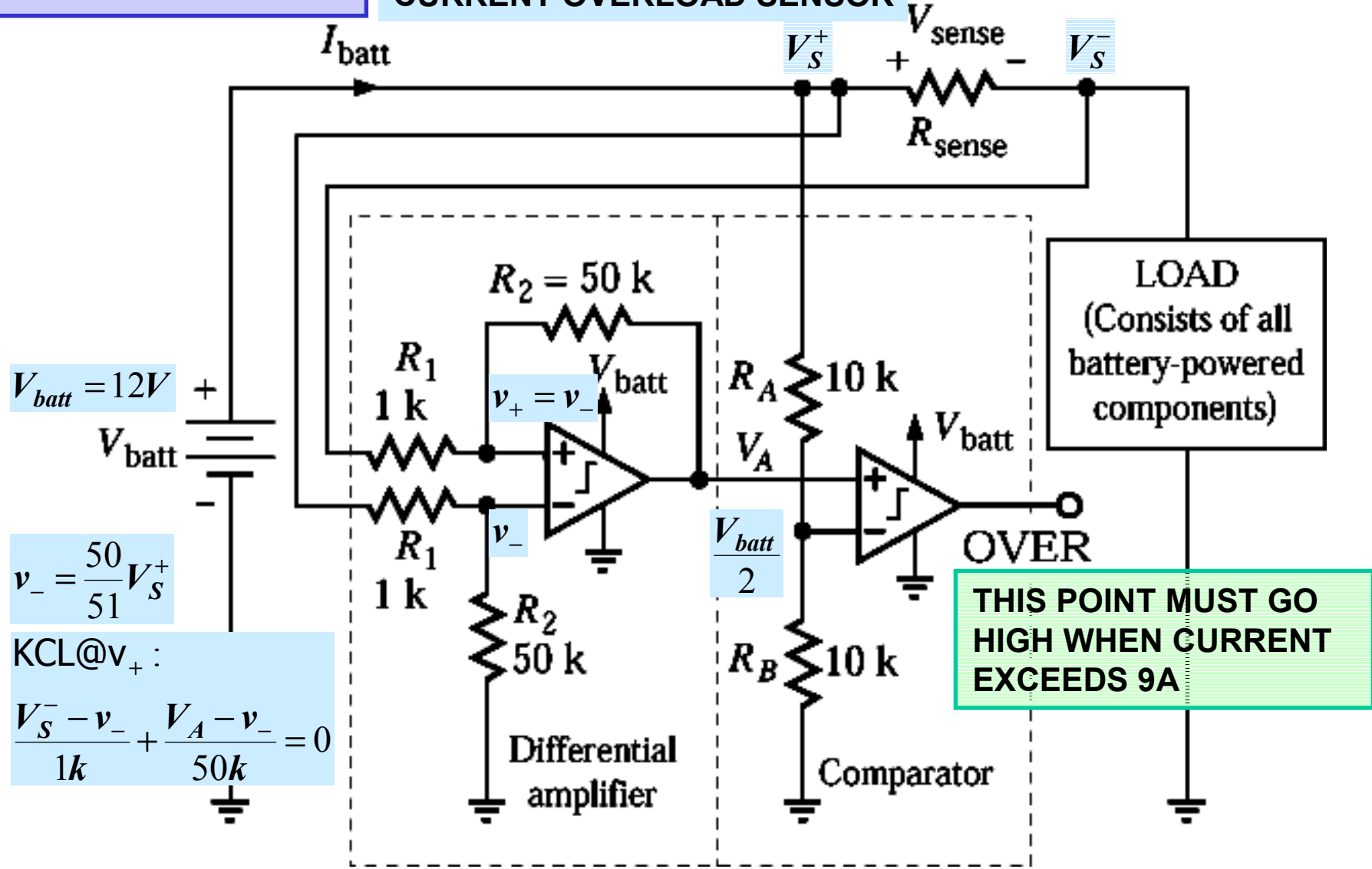

$V_{batt} = 12V$

$v_- = \frac{50}{51} V_s^+$

KCL@ v_+ :

$$\frac{V_s^- - v_-}{1k} + \frac{V_A - v_-}{50k} = 0$$

$V_A = 50(V_s^+ - V_s^-) = 50V_{sense}$ $50 \times R_{sense} \times 9(A) = 6V \Rightarrow R_{sense} = 0.0133\Omega$

DESIGN REQUIREMENT


$I_{batt} \geq 9A \Rightarrow V_A \geq 6V$

THIS POINT MUST GO HIGH WHEN CURRENT EXCEEDS 9A



LEARNING BY DESIGN

DESIGN EQUATIONS

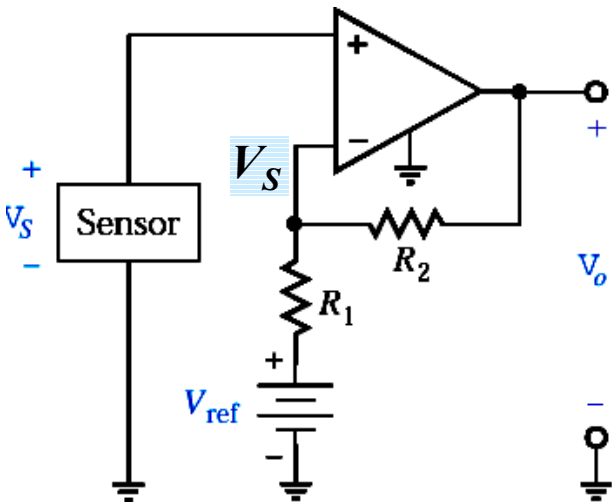

$$0 = \left[1 + \frac{R_2}{R_1} \right] (0.5) - \frac{R_2}{R_1} V_{ref} \Rightarrow \frac{R_1}{R_2} = 9$$

$$5 = \left[1 + \frac{R_2}{R_1} \right] (1.0) - \frac{R_2}{R_1} V_{ref} \Rightarrow V_{ref} = \frac{5}{9} V$$

CHOOSE $R_1 = 10k\Omega$


DESIGN REQUIREMENT	
INPUT	OUTPUT
$0.5 \leq V_S \leq 1.0V$	$0 \leq V_O \leq 5V$

DETERMINE V_{ref}, R_1, R_2


KCL @ v_-

$$\frac{V_O - V_S}{R_2} + \frac{V_{ref} - V_S}{R_1} = 0$$
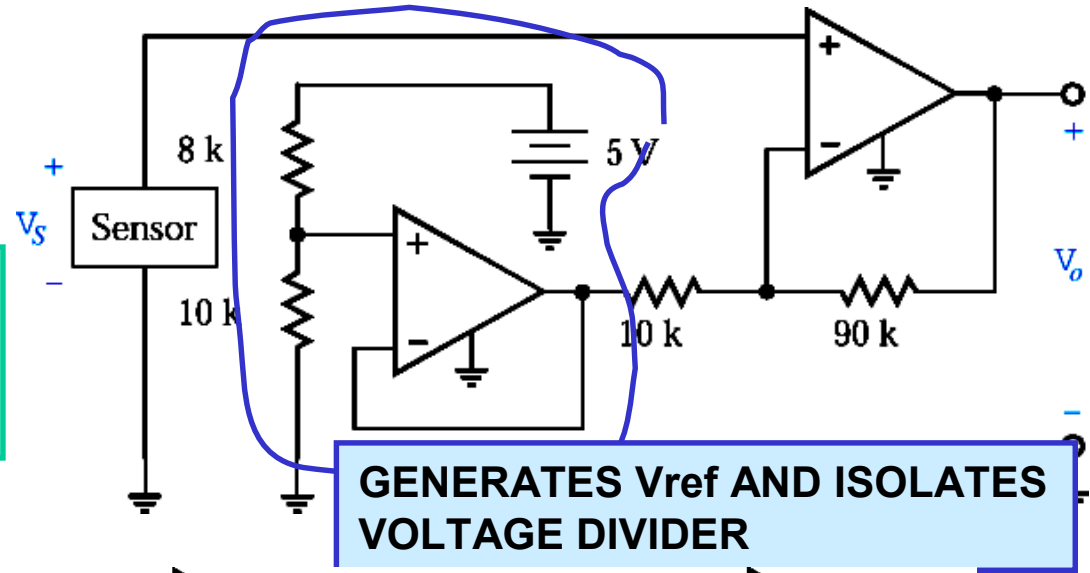
$$V_O = \left[1 + \frac{R_2}{R_1} \right] V_S - \frac{R_2}{R_1} V_{ref}$$



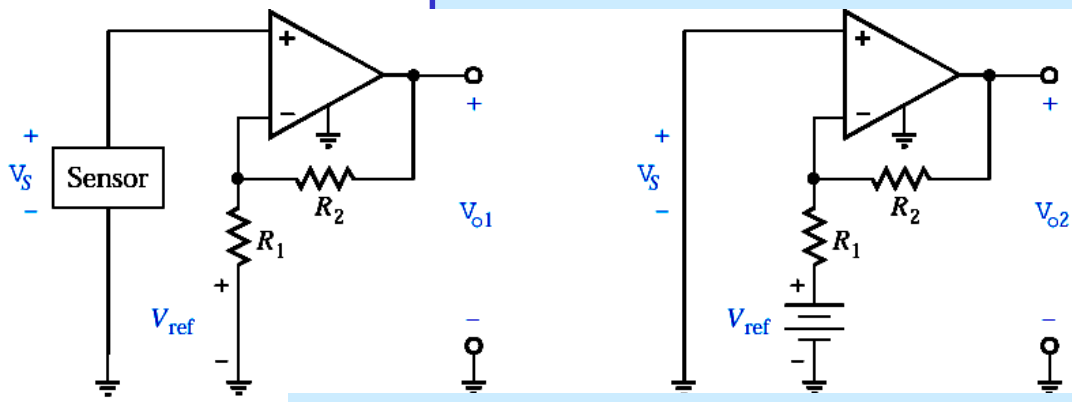GENERATES V_{ref} AND ISOLATES VOLTAGE DIVIDER



Analyzing circuit using superposition

