

POLYPHASE CIRCUITS

LEARNING GOALS

Three Phase Circuits

Advantages of polyphase circuits

Three Phase Connections

Basic configurations for three phase circuits

Source/Load Connections

Delta-Y connections

Power Relationships



Study power delivered by three phase circuits

Power Factor Correction

Improving power factor for three phase circuits



THREE PHASE CIRCUITS

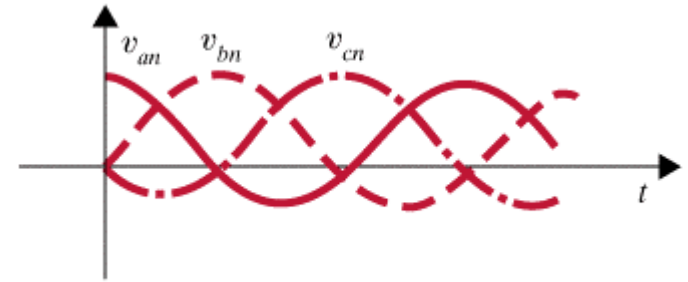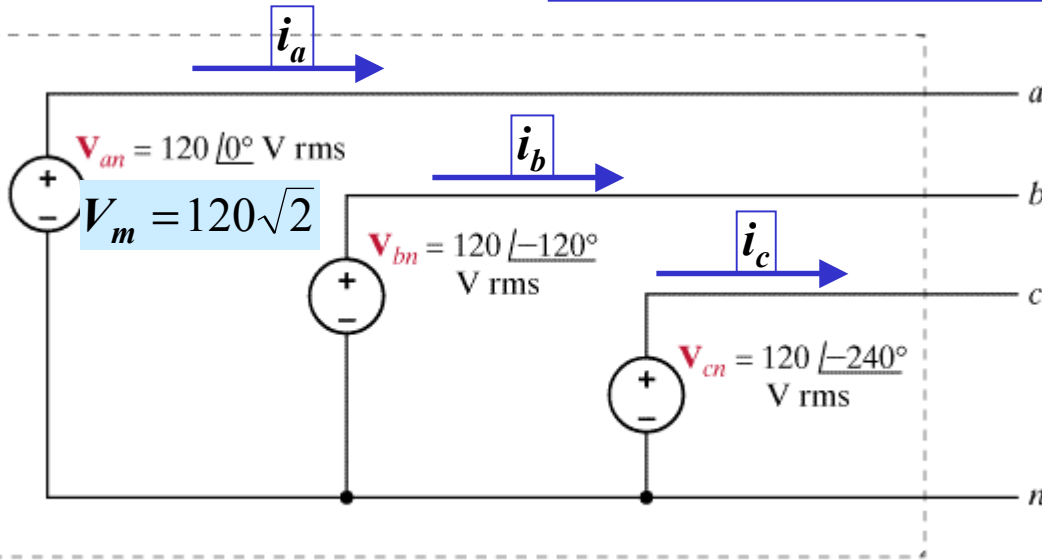

Instantaneous Phase Voltages

$$v_{an}(t) = V_m \cos(\omega t)(V)$$

$$v_{bn}(t) = V_m \cos(\omega t - 120^\circ)(V)$$

$$v_{cn}(t) = V_m \cos(\omega t - 240^\circ)(V)$$

Balanced Phase Currents

$$i_a(t) = I_m \cos(\omega t - \theta)$$

$$i_b(t) = I_m \cos(\omega t - \theta - 120^\circ)$$

$$i_c(t) = I_m \cos(\omega t - \theta - 240^\circ)$$

Instantaneous power

$$p(t) = v_{an}(t)i_a(t) + v_{bn}(t)i_b(t) + v_{cn}(t)i_c(t)$$

Theorem

For a balanced three phase circuit the instantaneous power is constant

$$p(t) = 3 \frac{V_m I_m}{2} \cos \theta (W)$$



Proof of Theorem

For a balanced three phase circuit the instantaneous power is constant

$$p(t) = 3 \frac{V_m I_m}{2} \cos \theta \text{ (W)}$$

Instantaneous power

$$p(t) = v_{an}(t)i_a(t) + v_{bn}(t)i_b(t) + v_{cn}(t)i_c(t)$$

$$p(t) = V_m I_m \left[\begin{array}{l} \cos \omega t \cos(\omega t - \theta) \\ + \cos(\omega t - 120) \cos(\omega t - 120 - \theta) \\ + \cos(\omega t - 240) \cos(\omega t - 240 - \theta) \end{array} \right]$$

$$\cos \alpha \cos \beta = \frac{1}{2} [\cos(\alpha - \beta) + \cos(\alpha + \beta)]$$

$$p(t) = V_m I_m \left[\begin{array}{l} 3 \cos \theta + \cos(2\omega t - \theta) \\ + \cos(2\omega t - 240 - \theta) \\ + \cos(2\omega t - 480 - \theta) \end{array} \right]$$

$$\phi = \omega t - \theta$$

$$\cos(\phi - 240) = \cos(\phi + 120)$$

$$\cos(\phi - 480) = \cos(\phi - 120)$$

$$\cos(120) = -0.5$$

Lemma

$$\cos \phi + \cos(\phi - 120) + \cos(\phi + 120) = 0$$

Proof

$$\cos \phi = \cos \phi$$




$$\cos(\phi - 120) = \cos \phi \cos(120) + \sin \phi \sin(120)$$

$$\cos(\phi + 120) = \cos \phi \cos(120) - \sin \phi \sin(120)$$


$$\cos \phi + \cos(\phi - 120) + \cos(\phi + 120) = 0$$




THREE-PHASE CONNECTIONS

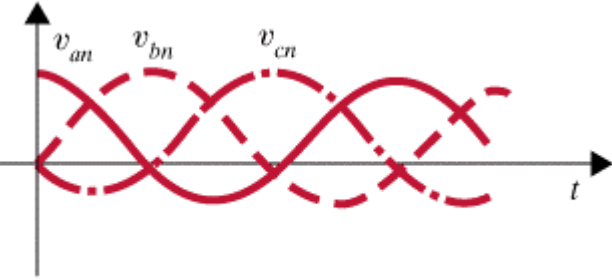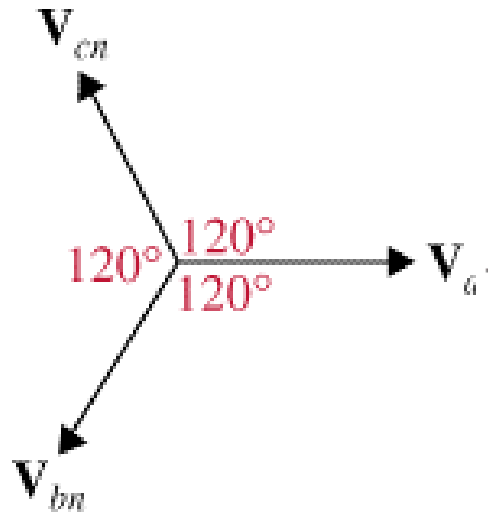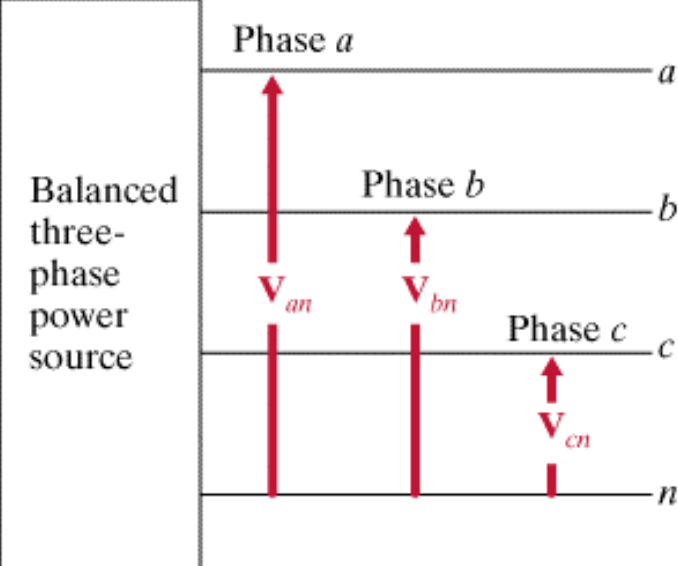


Positive sequence a-b-c

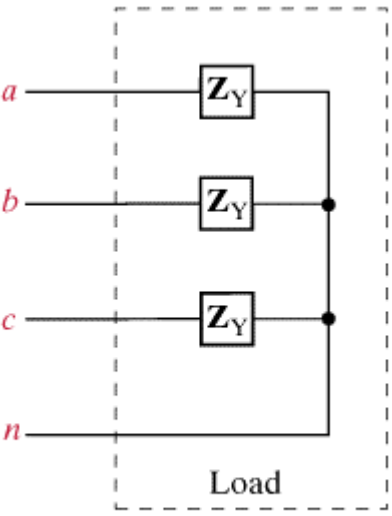


Y-connected loads

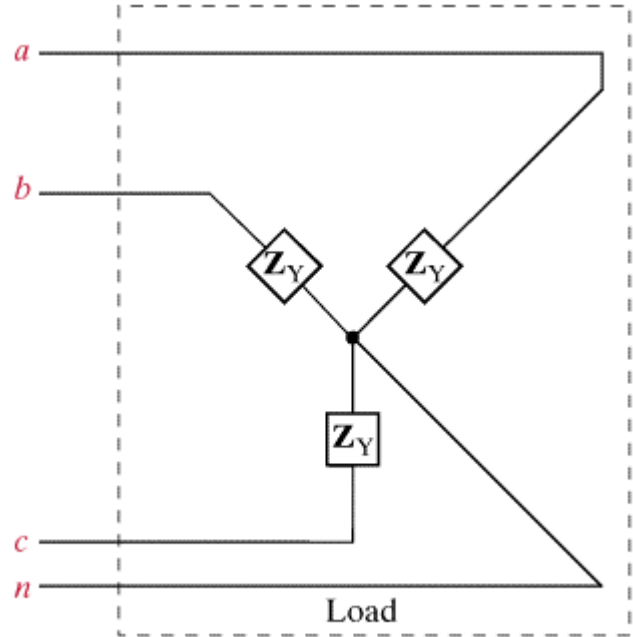

(b) ◀ ▶

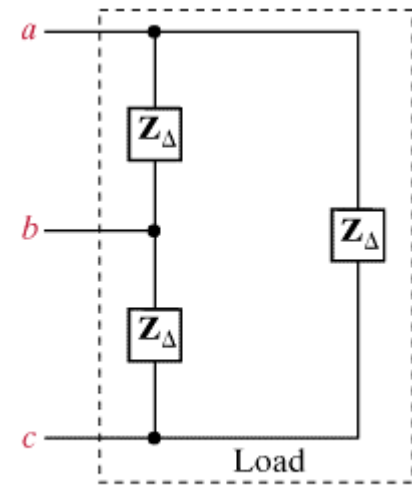


Delta connected loads

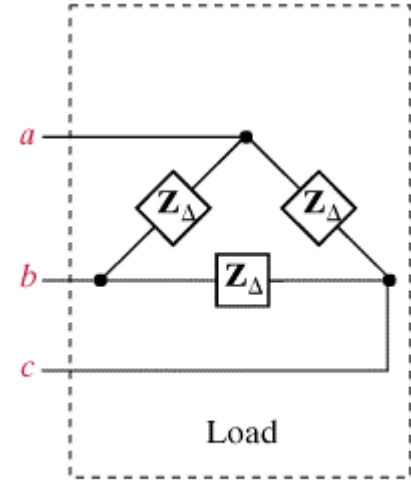

SOURCE/LOAD CONNECTIONS

BALANCED Y-Y CONNECTION

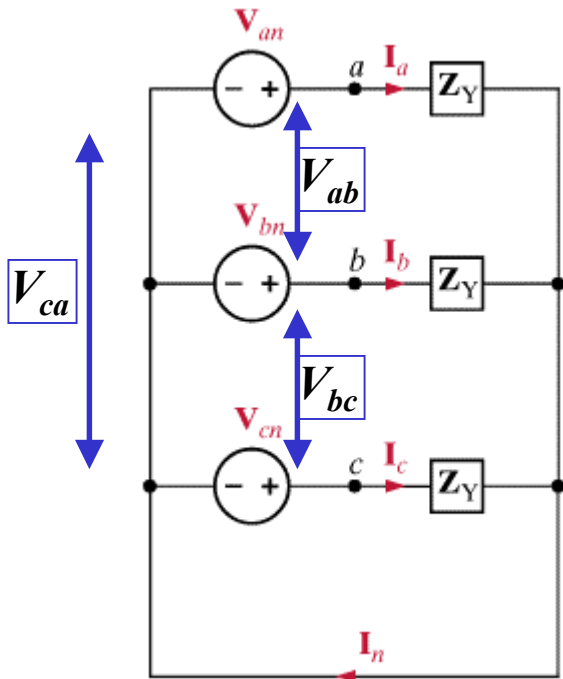


$$V_{an} = |V_p| \angle 0^\circ$$

$$V_{bn} = |V_p| \angle -120^\circ$$

$$V_{cn} = |V_p| \angle 120^\circ$$

Positive sequence phase voltages

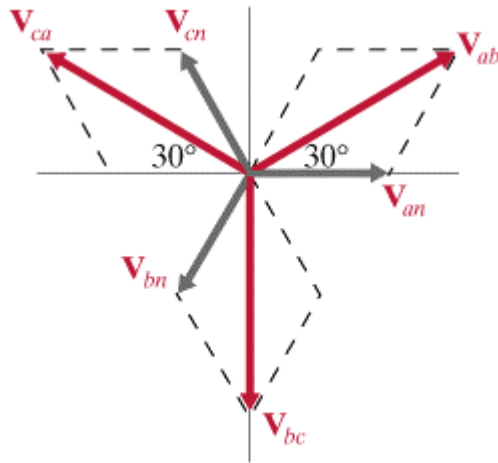


$$I_a = \frac{V_{an}}{Z_Y}; I_b = \frac{V_{bn}}{Z_Y}; I_c = \frac{V_{cn}}{Z_Y}$$

$$I_a = |I_L| \angle \theta^\circ; I_b = |I_L| \angle \theta - 120^\circ; I_c = |I_L| \angle \theta + 120^\circ$$

$$I_a + I_b + I_c = I_n = 0$$

For this balanced circuit it is enough to analyze one phase

Line voltages

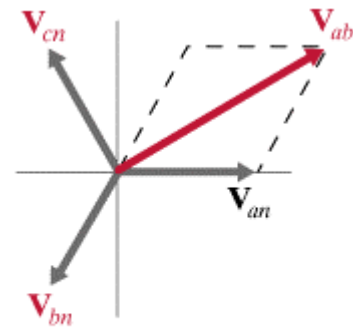

(a)

$$V_{ab} = V_{an} - V_{bn}$$

$$= |V_p| \angle 0^\circ - |V_p| \angle -120^\circ$$

$$= |V_p| (1 - (\cos 120 - j \sin 120))$$

$$= |V_p| \left(\frac{1}{2} - j \frac{\sqrt{3}}{2} \right)$$

$$= \sqrt{3} |V_p| \angle 30^\circ$$

$$V_{bc} = \sqrt{3} |V_p| \angle -90^\circ$$

$$V_{ca} = \sqrt{3} |V_p| \angle -210^\circ$$

$$V_L = \sqrt{3} |V_p| = \text{Line Voltage}$$




LEARNING EXAMPLE

For an abc sequence, balanced Y - Y three phase circuit


$$V_{ab} = 208 \angle -30^\circ$$

Determine the phase voltages

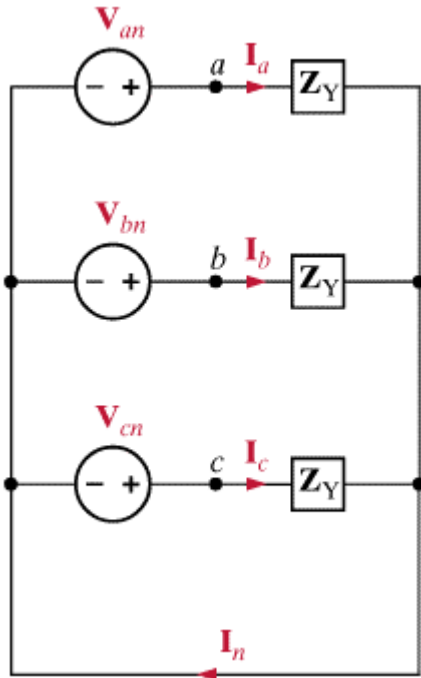

Balanced Y - Y

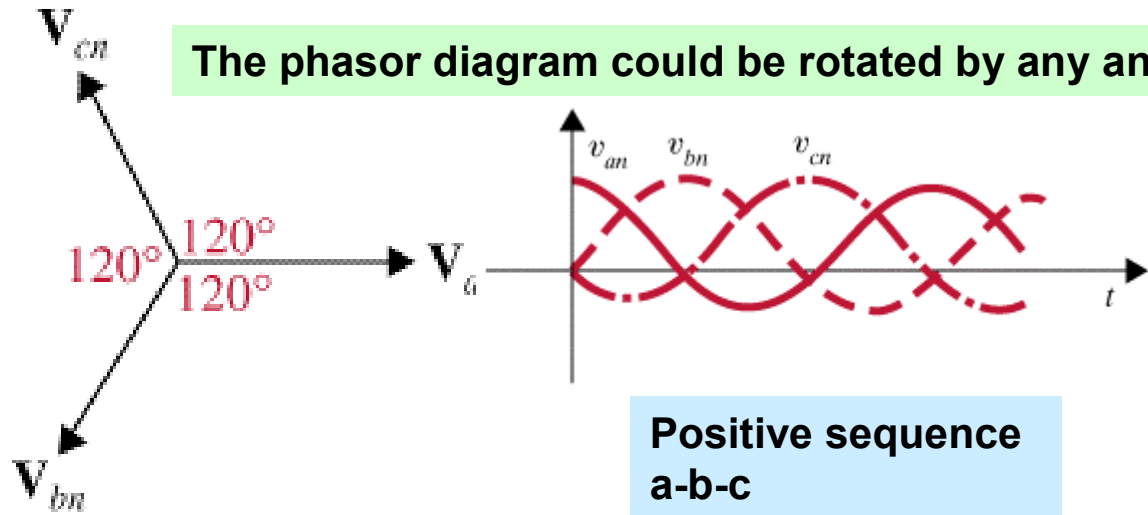The phasor diagram could be rotated by any angle




Positive sequence
a-b-c

$$V_{an} = |V_p| \angle 0^\circ$$

$$V_{bn} = |V_p| \angle -120^\circ$$

$$V_{cn} = |V_p| \angle 120^\circ$$

Positive sequence
phase voltages

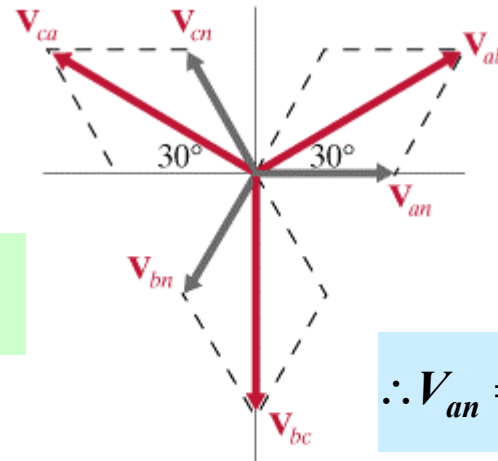

$$V_{ab} = \sqrt{3} |V_p| \angle 30^\circ$$

V_{an} lags V_{ab} by 30°

$$V_{ab} = 208 \angle -30^\circ$$

$$V_{an} = 120 \angle -60^\circ$$

$$V_{bn} = 120 \angle -180^\circ$$

$$V_{cn} = 120 \angle 60^\circ$$

$$\therefore V_{an} = \frac{|V_{ab}|}{\sqrt{3}} \angle (-30^\circ - 30^\circ)$$

Relationship between
phase and line voltages




LEARNING EXAMPLE

For an abc sequence, balanced Y - Y three phase circuit

source $|V_{phase}| = 120(V)_{rms}$, $Z_{line} = 1 + j1\Omega$, $Z_{phase} = 20 + j10\Omega$

Because circuit is balanced data on any one phase are sufficient

Determine line currents and load voltages

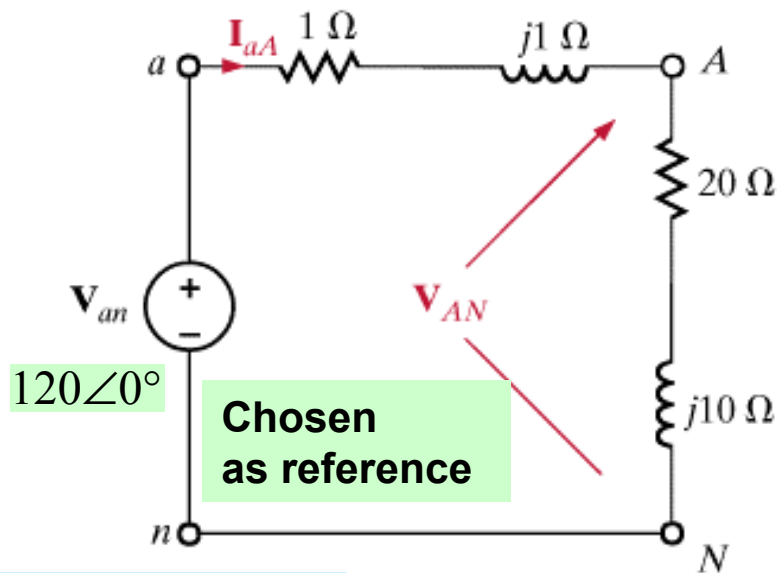 $120\angle 0^\circ$

Chosen as reference

$$V_{an} = 120\angle 0^\circ$$

$$V_{bn} = 120\angle -120^\circ$$

$$V_{cn} = 120\angle 120^\circ$$

Abc sequence

$$I_{aA} = \frac{V_{an}}{21 + j11} = \frac{120\angle 0^\circ}{23.71\angle 27.65^\circ} = 5.06\angle -27.65^\circ (A)_{rms}$$

$$I_{bB} = 5.06\angle -120 - 27.65^\circ (A)_{rms}$$

$$I_{cC} = 5.06\angle 120 - 27.65^\circ (A)_{rms}$$

$$V_{AN} = I_{aA} \times (20 + j10) = I_{aA} \times 22.36\angle 26.57^\circ$$

$$V_{AN} = 113.15\angle -1.08^\circ (V)_{rms}$$

$$V_{BN} = 113.15\angle -121.08^\circ (V)_{rms}$$

$$V_{CN} = 113.15\angle 118.92^\circ (V)_{rms}$$



LEARNING EXTENSION


For an abc sequence, balanced Y - Y three phase circuit

 $V_{an} = 120 \angle 90^\circ (V)_{rms}$. Find the line voltages V_{ab} leads V_{an} by 30°

$$V_{ab} = \sqrt{3} \times 120 \angle 120^\circ (V)_{rms}$$

$$V_{bc} = \sqrt{3} \times 120 \angle 0^\circ (V)_{rms}$$
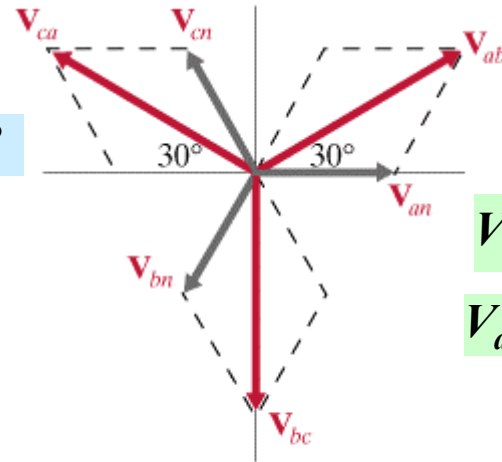
$$V_{ca} = \sqrt{3} \times 120 \angle 240^\circ (V)_{rms}$$



$$V_{ab} = \sqrt{3} |V_p| \angle 30^\circ$$

 V_{an} lags V_{ab} by 30°

Relationship between phase and line voltages

 $V_{ab} = 208 \angle 0^\circ (V)_{rms}$. Find the phase voltages V_{an} lags V_{ab} by 30°

$$V_{an} = \frac{208}{\sqrt{3}} \angle -30^\circ (V)_{rms}$$

$$V_{bn} = \frac{208}{\sqrt{3}} \angle -150^\circ (V)_{rms}$$

$$V_{cn} = \frac{208}{\sqrt{3}} \angle 90^\circ (V)_{rms}$$




LEARNING EXTENSION

For an abc sequence, balanced Y - Y three phase circuit

load, $|V_{phase}| = 104.02 \angle 26.6^\circ (V)_{rms}$, $Z_{line} = 1 + j1 \Omega$, $Z_{phase} = 8 + j3 \Omega$

Determine source phase voltages

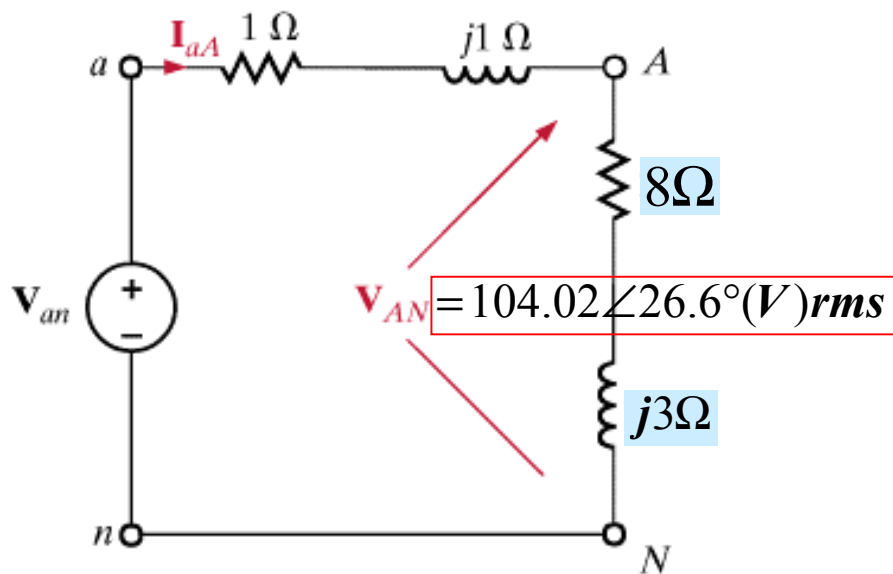

Currents are not required. Use inverse voltage divider


$$V_{an} = \frac{(8 + j3) + (1 + j1)}{8 + j3} V_{AN}$$

$$\frac{9 + j4}{8 + j3} \times \frac{8 - j3}{8 - j3} = \frac{84 + j5}{73} = 1.15 \angle 3.41^\circ$$

$$V_{an} = 120 \angle 30^\circ$$

$$V_{bn} = 120 \angle -90^\circ$$


$$V_{cn} = 120 \angle 150^\circ$$

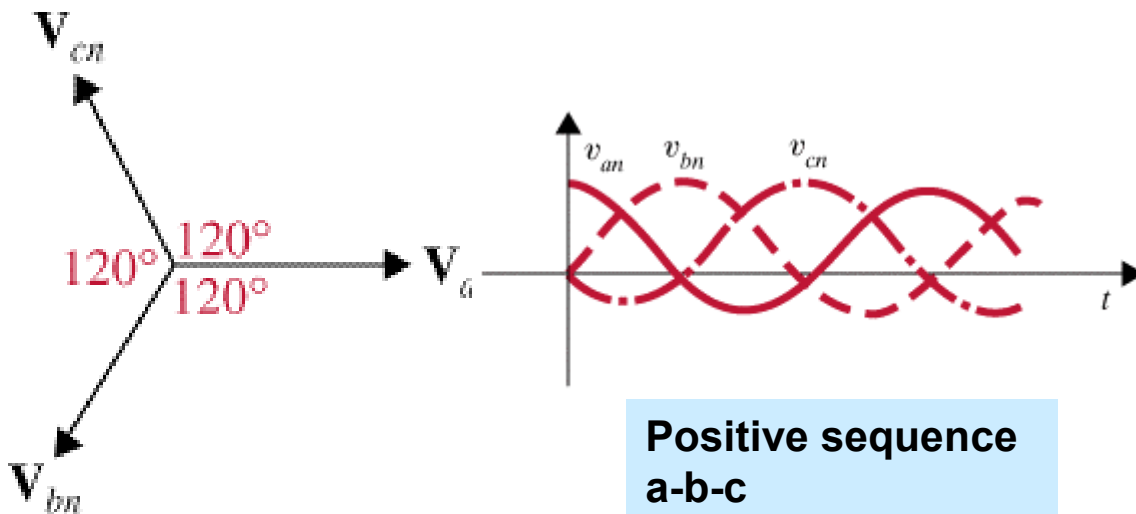


Positive sequence a-b-c



DELTA CONNECTED SOURCES

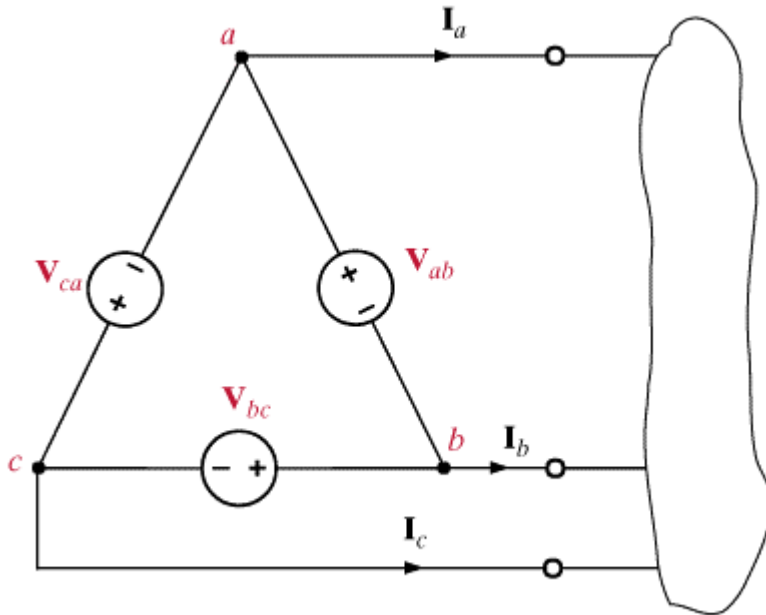

(a)

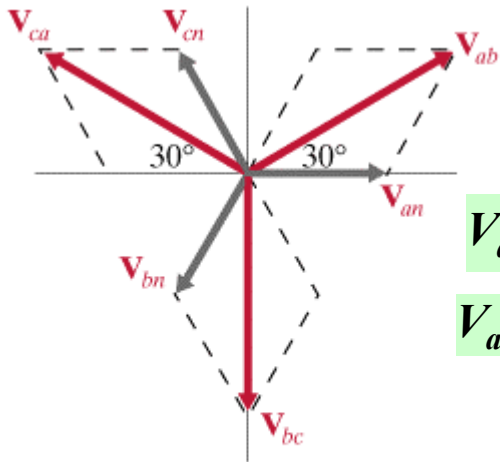


$$V_{ab} = \sqrt{3} |V_p| \angle 30^\circ$$

V_{an} lags V_{ab} by 30°

Relationship between phase and line voltages

Convert to an equivalent Y connection

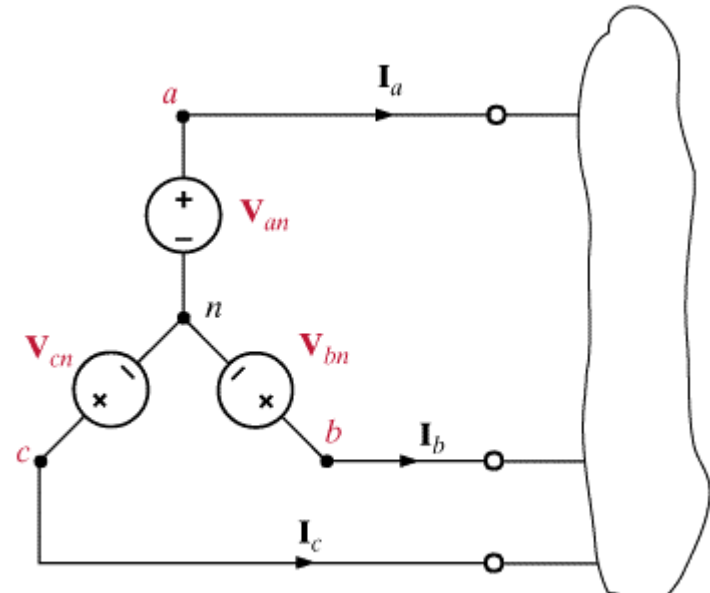

$$\left. \begin{aligned} V_{ab} &= V_L \angle 0^\circ \\ V_{bc} &= V_L \angle -120^\circ \\ V_{ca} &= V_L \angle 120^\circ \end{aligned} \right\} \Rightarrow \left\{ \begin{aligned} V_{an} &= \frac{V_L}{\sqrt{3}} \angle -30^\circ \\ V_{bn} &= \frac{V_L}{\sqrt{3}} \angle -150^\circ \\ V_{cn} &= \frac{V_L}{\sqrt{3}} \angle 90^\circ \end{aligned} \right.$$


Example

$$\left. \begin{aligned} V_{ab} &= 208 \angle 60^\circ \\ V_{bc} &= 208 \angle -60^\circ \\ V_{ca} &= 208 \angle 180^\circ \end{aligned} \right\} \Rightarrow \left\{ \begin{aligned} V_{an} &= 120 \angle 30^\circ \\ V_{bn} &= 120 \angle -90^\circ \\ V_{cn} &= 120 \angle 150^\circ \end{aligned} \right.$$



LEARNING EXAMPLE

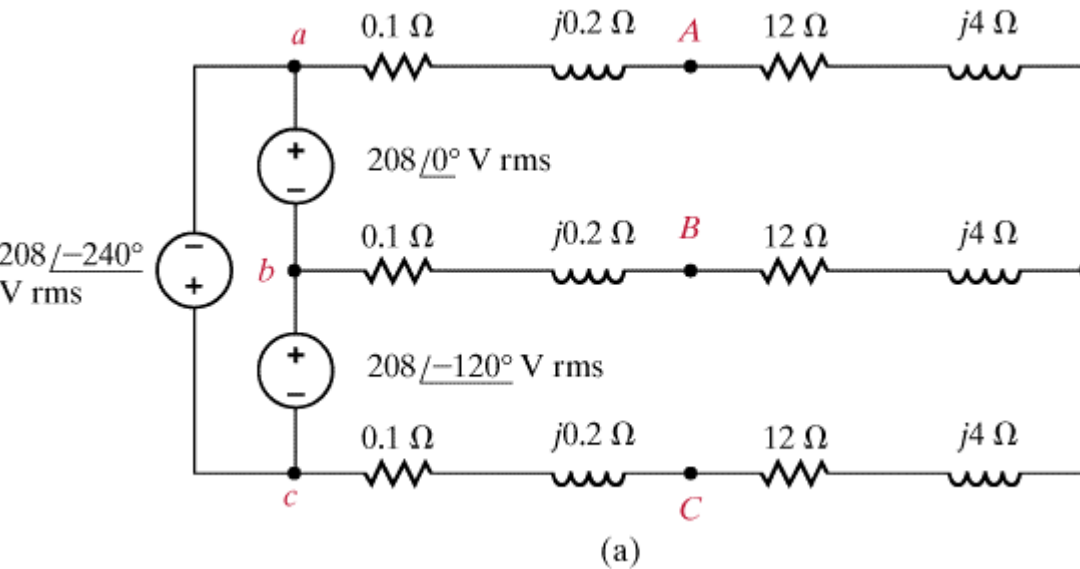
Determine line currents and line voltages at the loads



Source is Delta connected.
Convert to equivalent Y

$$\left. \begin{aligned} V_{ab} &= V_L \angle 0^\circ \\ V_{bc} &= V_L \angle -120^\circ \\ V_{ca} &= V_L \angle 120^\circ \end{aligned} \right\} \Rightarrow \begin{cases} V_{an} = \frac{V_L}{\sqrt{3}} \angle -30^\circ \\ V_{bn} = \frac{V_L}{\sqrt{3}} \angle -150^\circ \\ V_{cn} = \frac{V_L}{\sqrt{3}} \angle 90^\circ \end{cases}$$

Analyze one phase

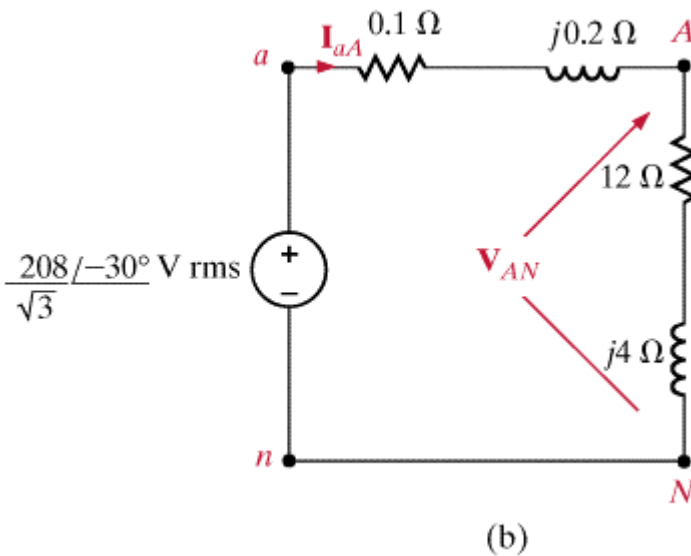

$$I_{aA} = \frac{(208/\sqrt{3}) \angle -30^\circ}{12.1 + j4.2} = 9.38 \angle -49.14^\circ (A) rms$$

$$V_{AN} = (12 + j4) \times 9.38 \angle -49.19^\circ = 118.65 \angle -30.71^\circ (V) rms$$

$$V_{ab} = \sqrt{3} |V_p| \angle 30^\circ \quad V_{AB} = \sqrt{3} \times 118.65 \angle 0.71^\circ$$

Determine the other phases using the balance


$$I_{bB} = 9.38 \angle -169.14^\circ (A) rms \quad V_{BC} = \sqrt{3} \times 118.65 \angle -119.29^\circ$$

$$I_{cC} = 9.38 \angle -71.86^\circ (A) rms \quad V_{CA} = \sqrt{3} \times 118.65 \angle 120.71^\circ$$



LEARNING EXTENSION

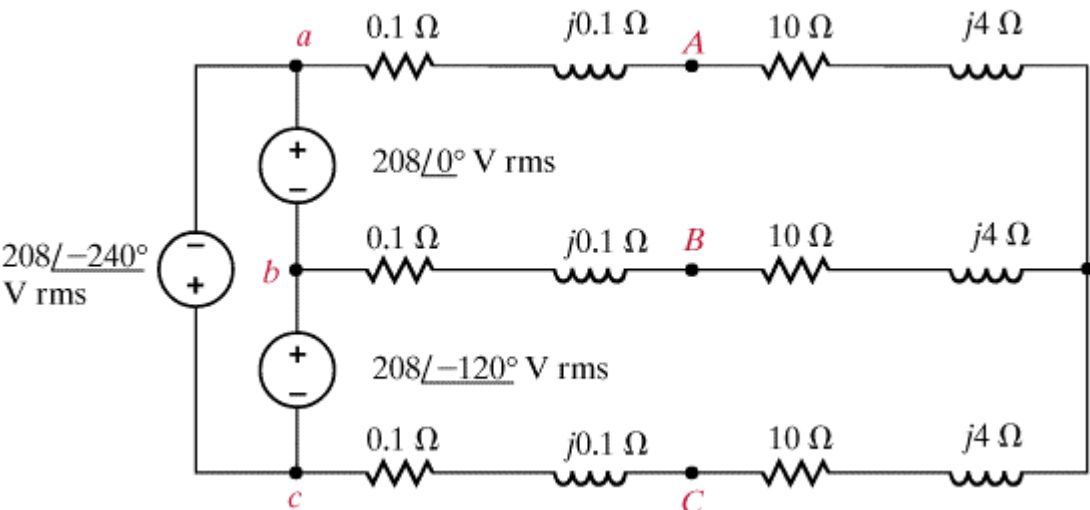
Compute the magnitude of the line voltage at the load



Source is Delta connected.
Convert to equivalent Y

$$\left. \begin{aligned} V_{ab} &= V_L \angle 0^\circ \\ V_{bc} &= V_L \angle -120^\circ \\ V_{ca} &= V_L \angle 120^\circ \end{aligned} \right\} \Rightarrow \begin{cases} V_{an} = \frac{V_L}{\sqrt{3}} \angle -30^\circ \\ V_{bn} = \frac{V_L}{\sqrt{3}} \angle -150^\circ \\ V_{cn} = \frac{V_L}{\sqrt{3}} \angle 90^\circ \end{cases}$$

Analyze one phase

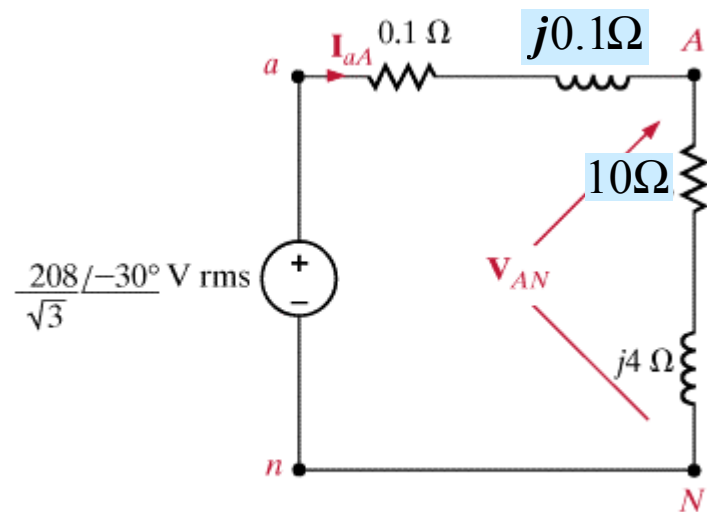

$$V_{AN} = \frac{10 + j4}{10.1 + j4.1} 120 \angle -30^\circ$$

Only interested in magnitudes!

$$|V_{AN}| = 120 \frac{10.77}{10.90} = 118.57 (V)_{rms}$$


$$V_{ab} = \sqrt{3} |V_p| \angle 30^\circ$$

$$|V_{AB}| = 205.4 (V)_{rms}$$

(b)



DELTA-CONNECTED LOAD

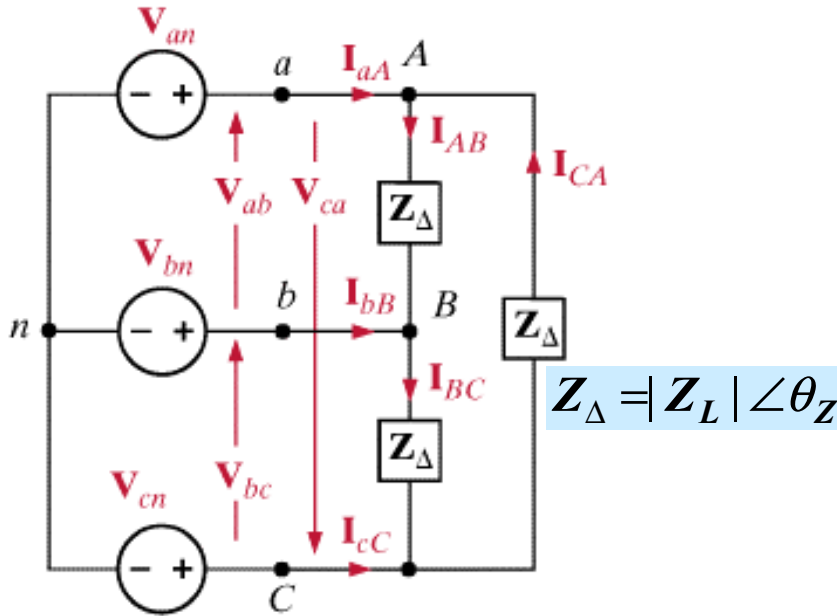

Method 1: Solve directly

$$V_{an} = |V_p| \angle 0^\circ$$

$$V_{bn} = |V_p| \angle -120^\circ$$

$$V_{cn} = |V_p| \angle 120^\circ$$

$$V_{ab} = \sqrt{3} |V_p| \angle 30^\circ$$

$$V_{bc} = \sqrt{3} |V_p| \angle -90^\circ$$

$$V_{ca} = \sqrt{3} |V_p| \angle -210^\circ$$

$$|I_{line}| = \sqrt{3} |I_\Delta|$$

$$\theta_{line} = \theta_\Delta - 30^\circ$$

Line-phase current relationship

Load phase currents

$$I_{AB} = \frac{V_{AB}}{Z_\Delta} = |I_\Delta| \angle \theta_\Delta$$

$$I_{BC} = \frac{V_{BC}}{Z_\Delta} = |I_\Delta| \angle \theta_\Delta - 120^\circ$$

$$I_{CA} = \frac{V_{CA}}{Z_\Delta} = |I_\Delta| \angle \theta_\Delta + 120^\circ$$

$$\theta_\Delta = 30^\circ - \theta_Z$$

Line currents

$$I_{aA} = I_{AB} - I_{CA}$$

$$I_{bB} = I_{BC} - I_{AB}$$

$$I_{cC} = I_{CA} - I_{BC}$$

Method 2: We can also convert the delta connected load into a Y connected one. The same formulas derived for resistive circuits are applicable to impedances





Balanced case $Z_Y = \frac{Z_\Delta}{3}$

$$I_{aA} = \frac{V_{an}}{Z_Y} = |I_{aA}| \angle \theta_L \Rightarrow \begin{cases} |I_{aA}| = \frac{|V_{AB}| / \sqrt{3}}{|Z_\Delta| / 3} \\ \theta_L = -\theta_Z \end{cases}$$



REVIEW OF
 $\Delta \leftrightarrow Y$
 Transformations

$$R_{ab} = R_2 \parallel (R_1 + R_3)$$

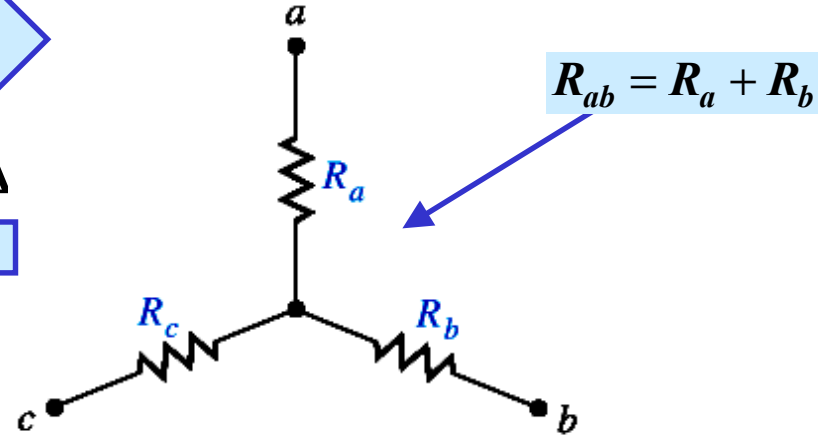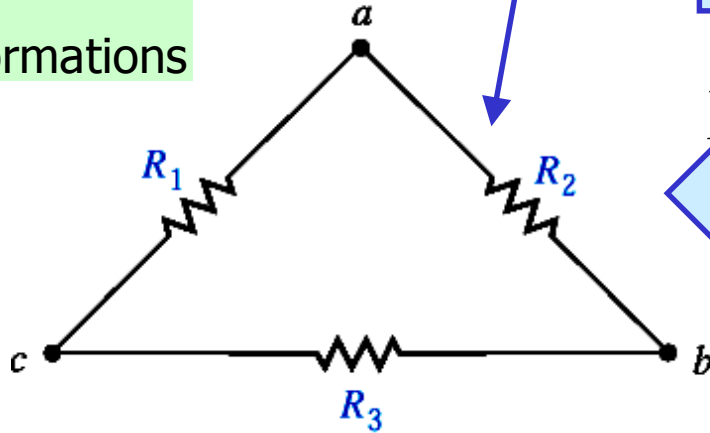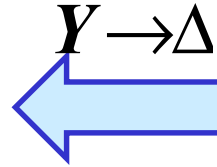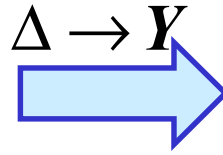

$$R_{ab} = R_a + R_b$$

$$R_a + R_b = \frac{R_2(R_1 + R_3)}{R_1 + R_2 + R_3}$$

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$\frac{R_a}{R_b} = \frac{R_1}{R_3} \Rightarrow R_3 = \frac{R_b R_1}{R_a}$$

$$\frac{R_b}{R_c} = \frac{R_2}{R_1} \Rightarrow R_2 = \frac{R_b R_1}{R_c}$$

REPLACE IN THE THIRD AND SOLVE FOR R1

$$R_b + R_c = \frac{R_3(R_1 + R_2)}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

$Y - \Delta$

$$R_c + R_a = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3}$$


$$R_c = \frac{R_3 R_1}{R_1 + R_2 + R_3}$$

$\Delta \rightarrow Y$


SUBTRACT THE FIRST TWO THEN ADD TO THE THIRD TO GET Ra
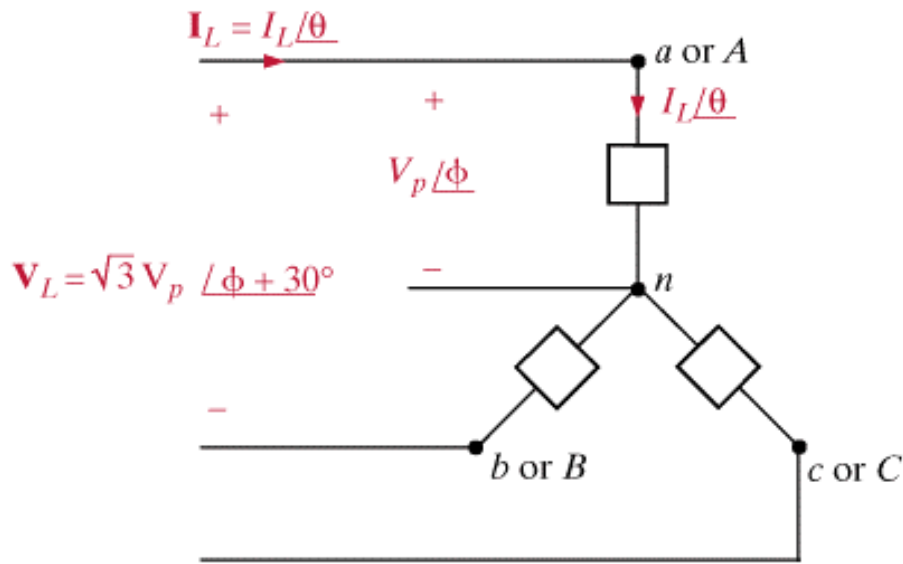
$$R_{\Delta} = R_1 = R_2 = R_3 \Rightarrow R_Y = \frac{R_{\Delta}}{3}$$






(a)

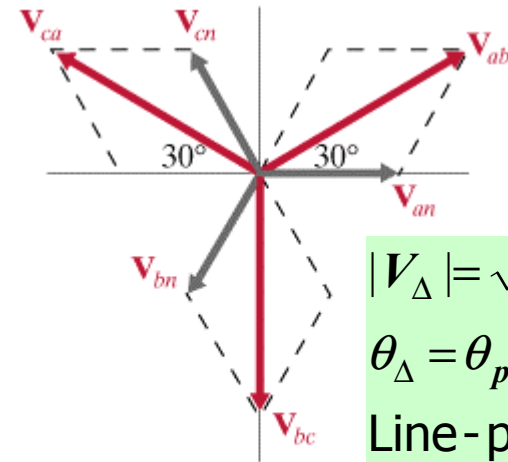

(b)

$|V_\Delta| = \sqrt{3} |V_{phase}|$
 $\theta_\Delta = \theta_{phase} + 30^\circ$
 Line-phase voltage relationship

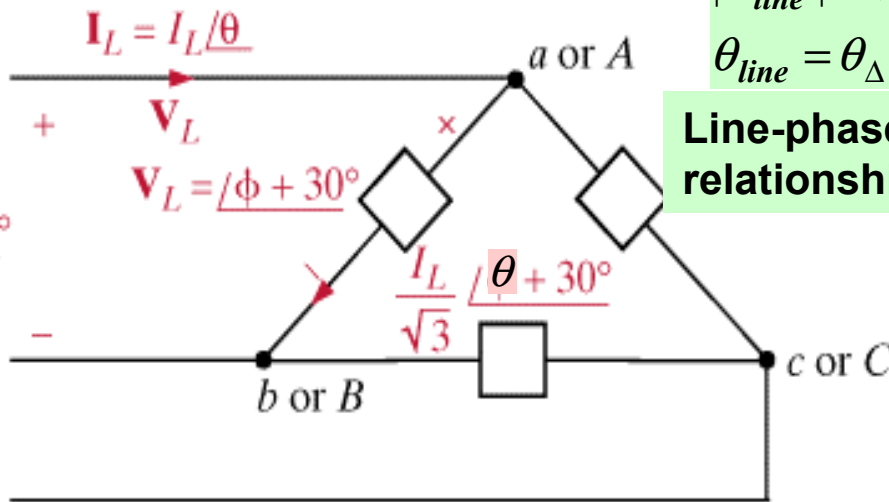

(a)

$|I_{line}| = \sqrt{3} |I_\Delta|$
 $\theta_{line} = \theta_\Delta - 30^\circ$

Line-phase current relationship

LEARNING EXTENSION

$I_{aA} = 12 \angle 40^\circ$

Find the phase currents

$I_{AB} = 6.93 \angle 70^\circ$


$I_{BC} = 6.93 \angle -50^\circ$

$I_{CA} = 6.93 \angle 190^\circ$



LEARNING EXAMPLE

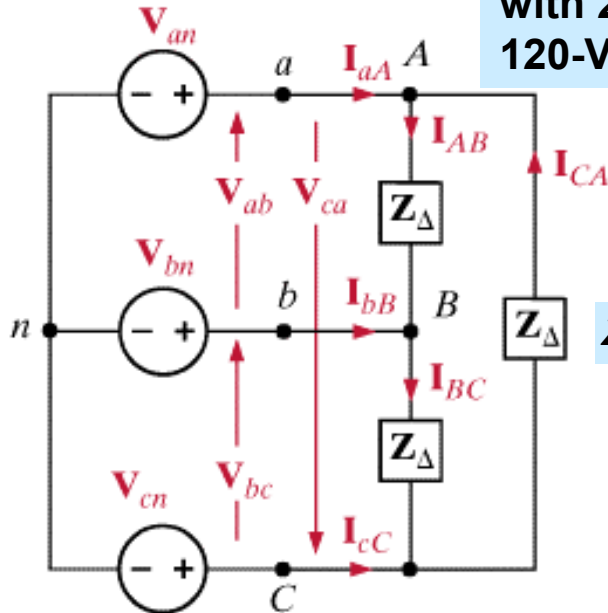Delta-connected load consists of 10-Ohm resistance in series with 20-mH inductance. Source is Y-connected, abc sequence, 120-V rms, 60Hz. Determine all line and phase currents



$$V_{an} = 120 \angle 30^\circ (V)_{rms}$$

$$Z_{\text{inductance}} = 2\pi \times 60 \times 0.020 = 7.54 \Omega$$

$$Z_{\Delta} = 10 + j7.54 \Omega = 12.52 \angle 37.02^\circ \Rightarrow Z_Y = 4.17 \angle 37.02^\circ$$

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{120\sqrt{3} \angle 60^\circ}{10 + j7.54} = 16.60 \angle 22.98^\circ (A)_{rms}$$

$$I_{BC} = 16.60 \angle -97.02^\circ (A)_{rms}$$

$$I_{CA} = 16.60 \angle 142.98^\circ (A)_{rms}$$

$$I_{aA} = 28.75 \angle -7.02^\circ (A)_{rms}$$

$$I_{bB} = 28.75 \angle -127.02^\circ (A)_{rms}$$

$$I_{cC} = 28.75 \angle 112.98^\circ (A)_{rms}$$

Alternatively, determine first the line currents and then the delta currents

$$|V_{\Delta}| = \sqrt{3} |V_{\text{phase}}|$$

$$\theta_{\Delta} = \theta_{\text{phase}} + 30^\circ$$

Line-phase voltage relationship


$$|I_{\text{line}}| = \sqrt{3} |I_{\Delta}|$$

$$\theta_{\text{line}} = \theta_{\Delta} - 30^\circ$$

Line-phase current relationship



POWER RELATIONSHIPS

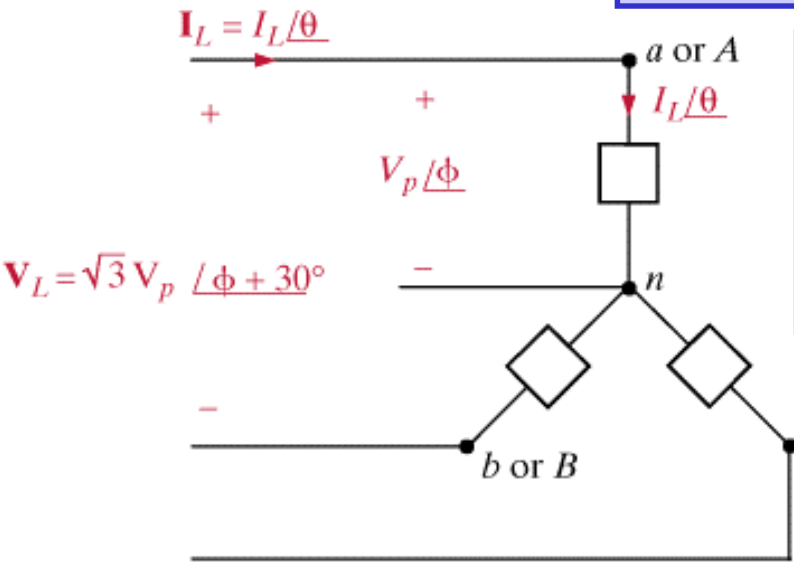


(a)

$|V_{\Delta}| = \sqrt{3} |V_{phase}|$
 $\theta_{\Delta} = \theta_{phase} + 30^{\circ}$
 Line-phase voltage relationship

$S_{Total} = 3 \times V_{phase} \times I_{phase}^*$

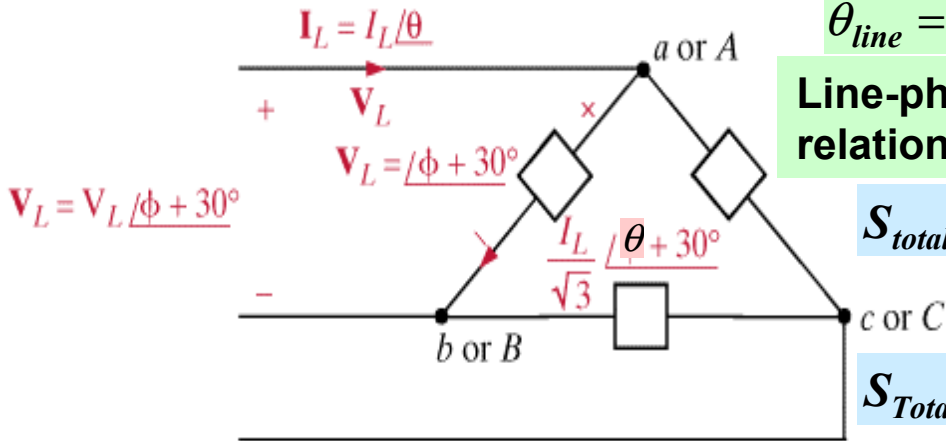$S_{Total} = \sqrt{3} V_{line} I_{line}^*$




(b)

$|I_{line}| = \sqrt{3} |I_{\Delta}|$
 $\theta_{line} = \theta_{\Delta} - 30^{\circ}$
 Line-phase current relationship

$S_{total} = 3 V_{line} \times I_{\Delta}^*$

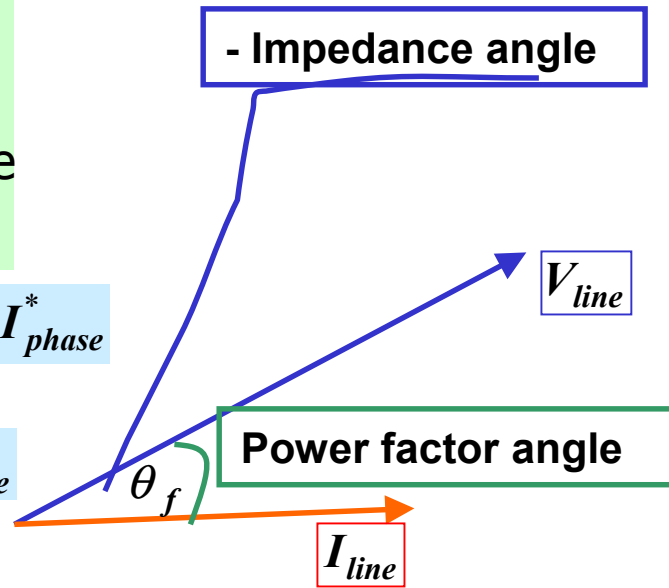$S_{Total} = \sqrt{3} V_{line} I_{line}^*$



$P_{total} = \sqrt{3} |V_{line}| |I_{line}| \cos \theta_f$

$Q_{total} = \sqrt{3} |V_{line}| |I_{line}| \sin \theta_f$




LEARNING EXAMPLE

$$|V_{line}| = 208(V)_{rms}$$

$$P_{total} = 1200W$$

power factor angle = 20° lagging

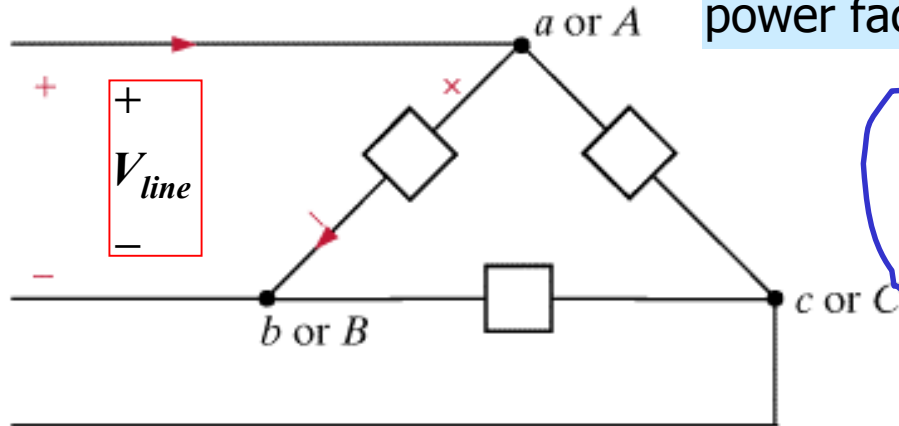

Determine the magnitude of the line currents and the value of load impedance per phase in the delta

$$P_{total} = \sqrt{3} |V_{line}| |I_{line}| \cos \theta_f$$

$$Q_{total} = \sqrt{3} |V_{line}| |I_{line}| \sin \theta_f$$

$$\frac{P_{total}}{3} = \frac{|V_{line}| |I_{line}|}{\sqrt{3}} \cos \theta_f \Rightarrow |I_{line}| = 3.54(A)_{rms}$$

$$|I_{line}| = \sqrt{3} |I_{\Delta}|$$

$$\theta_{line} = \theta_{\Delta} - 30^\circ$$


Line-phase current relationship

$$\Rightarrow |I_{\Delta}| = 2.05(A)_{rms}$$

$$\Rightarrow |Z_{\Delta}| = \frac{|V_{line}|}{|I_{\Delta}|} = 101.46\Omega$$


$$Z_{\Delta} = 101.46 \angle 20^\circ$$

- Impedance angle

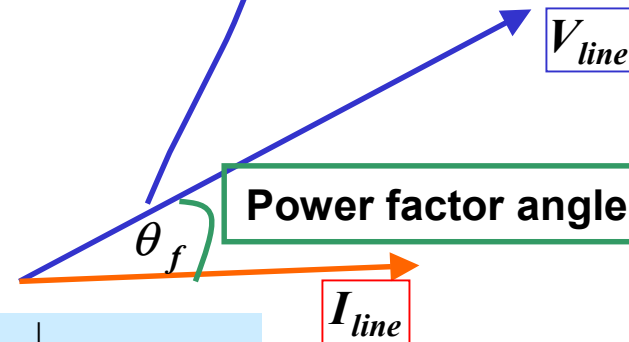

LEARNING EXAMPLE

For an abc sequence, balanced Y - Y three phase circuit

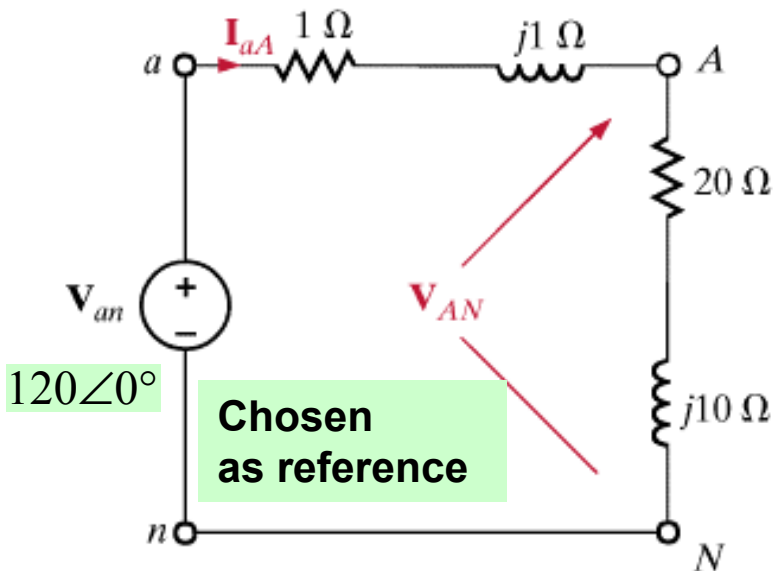source $|V_{phase}| = 120(V)_{rms}$, $Z_{line} = 1 + j1\Omega$, $Z_{phase} = 20 + j10\Omega$ **Determine real and reactive power per phase at the load and total real, reactive and complex power at the source**

$$V_{AN} = I_{aA} \times (20 + j10) = I_{aA} \times 22.36 \angle 26.57^\circ$$

$$V_{AN} = 113.15 \angle -1.08^\circ (V)_{rms}$$

$$S_{phase} = V_{AN} I_{aA}^* = 113.15 \angle -1.08^\circ \times 5.06 \angle 27.65^\circ$$

$$S_{phase} = 572.54 \angle 26.57^\circ = 512 + j256.09 (VA)_{rms}$$

 $P_{per\ phase}$ $Q_{per\ phase}$

$$S_{source\ phase} = V_{an} \times I_{aA}^* = 120 \angle 0^\circ \times 5.06 \angle 27.65^\circ$$

$$V_{an} = 120 \angle 0^\circ$$

$$V_{bn} = 120 \angle -120^\circ$$

$$V_{cn} = 120 \angle 120^\circ$$

Because circuit is balanced data on any one phase are sufficient**Abc sequence**

$$I_{aA} = \frac{V_{an}}{21 + j11} = \frac{120 \angle 0^\circ}{23.71 \angle 27.65^\circ} = 5.06 \angle -27.65^\circ (A)_{rms}$$

$$S_{source\ phase} = 607.2 \angle 27.65^\circ$$

$$= 537.86 + j281.78 VA$$

$$P_{total\ source} = 3 \times 537.86 (W)$$

$$Q_{total\ source} = 3 \times 281.78 (VA)$$

$$S_{total\ source} = P_{total\ source} + Q_{total\ source} = 1613.6 + j845.2 (VA)$$

$$|S_{total\ source}| = 1821.6 (VA)$$

LEARNING EXAMPLE


Determine the line currents and the combined power factor

Circuit is balanced

Load 1: 24kW at pf = 0.6 lagging

Load 2: 10kW at pf = 1

Load 3: 12kVA at pf = 0.8 leading

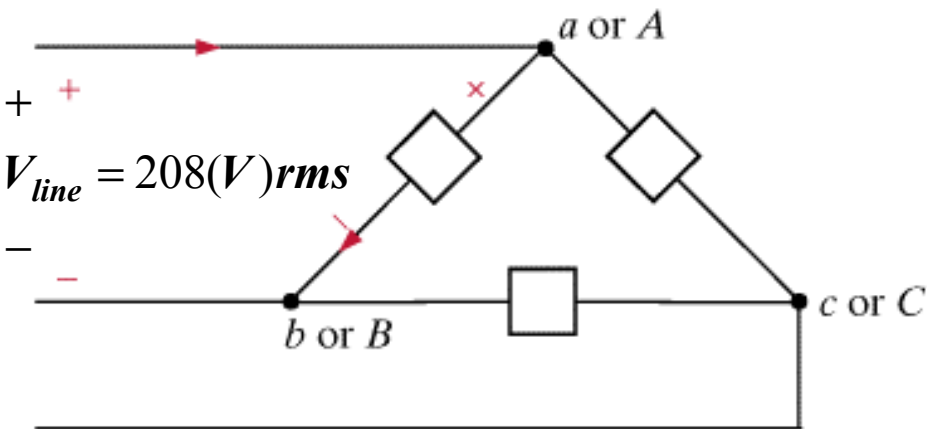

$$\left. \begin{array}{l} P_1 = 24kW \\ pf = 0.6 \text{ lagging} \end{array} \right\} \Rightarrow |S_1| = 40kVA$$

$$|Q_1| = \sqrt{|S_1|^2 - |P_1|^2} = 32kVA$$

lagging \Rightarrow inductive $\therefore S_1 = 24 + j32 kVA$

Load 2

$$\left. \begin{array}{l} P_2 = 10kW \\ pf = 1 \end{array} \right\} \Rightarrow S_2 = 10 + j0 kVA$$

Load 3

$$\left. \begin{array}{l} |S_3| = 12kVA \\ pf = 0.8 \end{array} \right\} \Rightarrow \begin{cases} P_3 = 9.6kW \\ |Q_3| = 7.2kVA \end{cases}$$

leading pf \Rightarrow capacitive $\therefore S_3 = 9.6 - j7.2 kVA$


$$S = P + jQ$$

$$P = |S| \cos \theta_f$$

$$Q = |S| \sin \theta_f$$

$$pf = \cos \theta_f$$

$$S_{total} = S_1 + S_2 + S_3$$

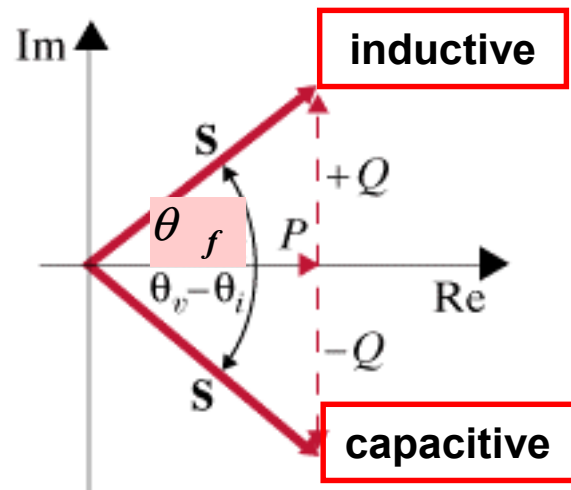

$$S_{TOTAL} = S_1 + S_2 + S_3 = 43.6 + j24.8 kVA = 50.160 \angle 29.63^\circ kVA$$

$$P_{total} = \sqrt{3} |V_{line}| |I_{line}| \cos \theta_f$$

$$Q_{total} = \sqrt{3} |V_{line}| |I_{line}| \sin \theta_f$$

$$\Rightarrow \begin{cases} |S_{total}| = \sqrt{3} |V_{line}| \times |I_{line}| \\ \theta_f = 29.63^\circ \end{cases}$$

pf = 0.869 lagging



$$|I_{line}| = 139.23(A)rms$$

Continued ...



LEARNING EXAMPLE
continued

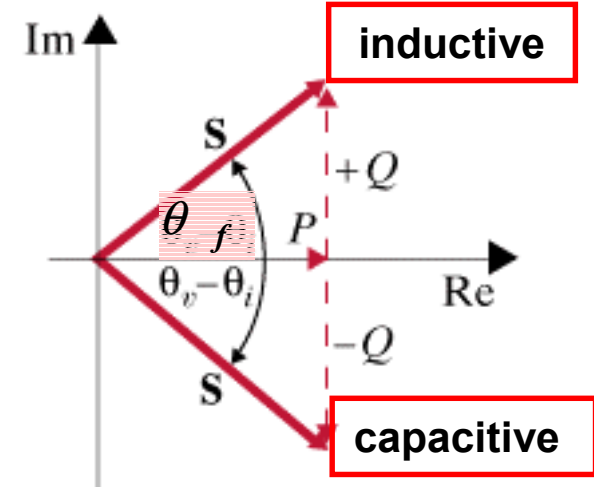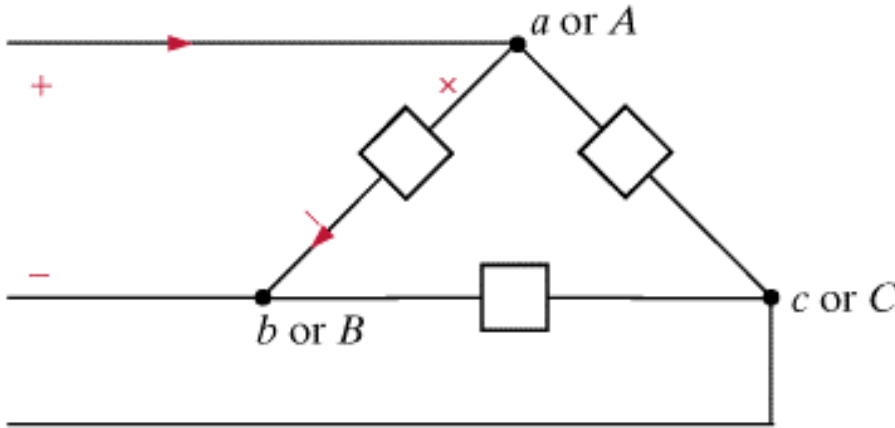If the line impedances are $Z_{line} = 0.05 + j0.02\Omega$
determine line voltages and power factor at the source



$$|I_{line}| = 139.23(A)_{rms}$$

$$S_{line} = 3 \times (Z_{line} I_{line}) I_{line}^* = 3 \times Z_{line} |I_{line}|^2$$

$$S_{line} = 2908 + j1163(VA)$$

$$S_{load\ total} = 43.6 + j24.8kVA = 50.160 \angle 29.63^\circ kVA$$

$$S_{source\ total} = 46.508 + j25.963 = 53.264 \angle 29.17^\circ kVA$$

$$\begin{cases} |S_{total}| = \sqrt{3} |V_{line}| \times |I_{line}| \\ \theta_f = 29.17^\circ \end{cases}$$


$$V_{line} = \frac{53,264}{\sqrt{3} \times 139.13} = 220.87(V)_{rms}$$

$$pf = \cos \theta_f = \cos(29.17^\circ) = 0.873 \text{ lagging}$$



LEARNING EXTENSION

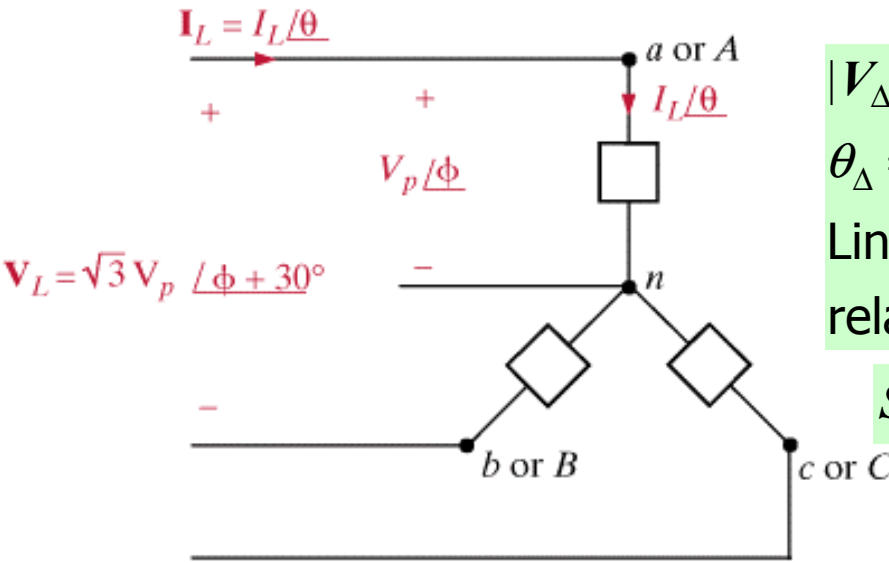A Y-Y balanced three-phase circuit has a line voltage of 208-Vrms. The total real power absorbed by the load is 12kW at pf=0.8 lagging. Determine the per-phase impedance of the load



$|V_{\Delta}| = \sqrt{3} |V_{phase}|$
 $\theta_{\Delta} = \theta_{phase} + 30^{\circ}$
 Line-phase voltage relationship


$$S_{Total} = 3 \times V_{phase} \times I_{phase}^*$$

$$S = P + jQ$$

$$P = |S| \cos \theta_f$$

$$Q = |S| \sin \theta_f$$

$$pf = \cos \theta_f$$

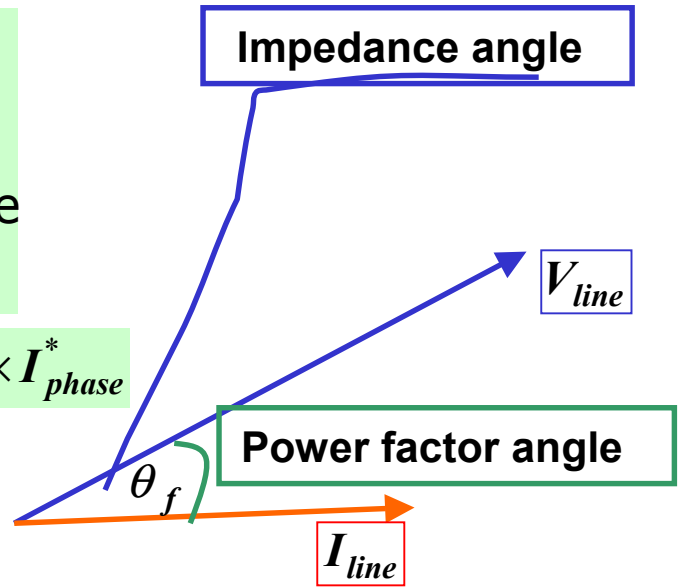

$$\Rightarrow |V_{phase}| = \frac{208}{\sqrt{3}} = 120(V)_{rms}$$

$$S_{total} = 3V_{phase} \times \left(\frac{V_{phase}}{Z_{phase}} \right)^* = 3 \times \frac{|V_{phase}|^2}{Z_{phase}^*}$$

$$|Z_{phase}| = \frac{3 \times |V_{phase}|^2}{|S_{total}|} = 2.88 \Omega$$

$$pf = 0.8 = \cos \theta_f \Rightarrow \theta_f = 36.87^{\circ}$$

$$|S_{total}| = \frac{P_{total}}{pf} = 15kVA$$

$$Z_{pahse} = 2.88 \angle 36.87^{\circ} \Omega$$





LEARNING EXTENSION

Determine real, reactive and complex power at both load and source

Source is Delta connected. Convert to equivalent Y

Analyze one phase

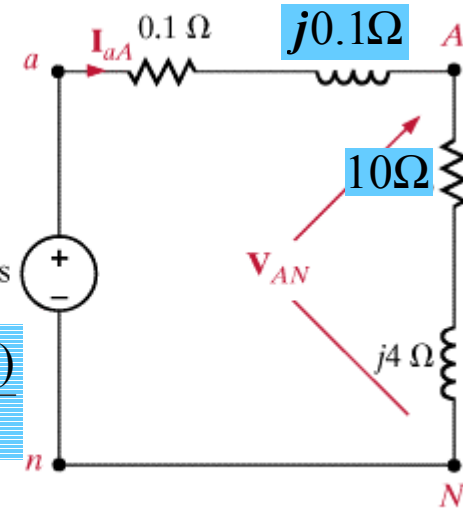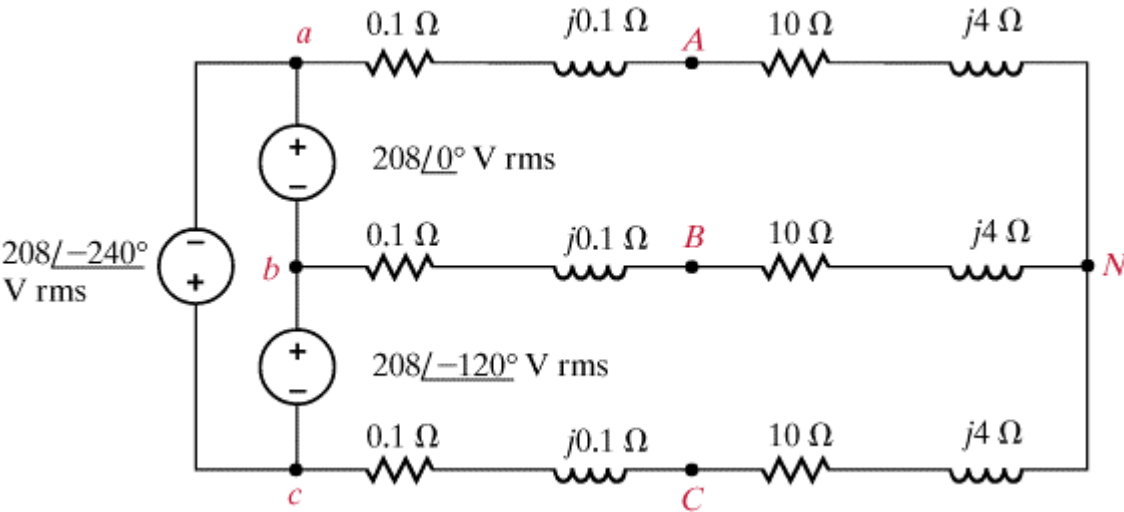

$$S_{load} = 3 \times V_{AN} I_{aA}^* = 3 \times \frac{|V_{AN}|^2}{Z_{phase}^*} = \frac{3 \times |118.57|^2}{10 - j4} = \frac{3 \times |118.57|^2 (10 + j4)}{10^2 + 4^2}$$

$$S_{source} = 3 \times V_{an} I_{aA}^* = 3 \times \frac{|V_{an}|^2}{Z_{total\ phase}^*} = \frac{3 \times |120|^2}{10.1 - j4.1} = \frac{3 \times |120|^2 (10.1 + j4.1)}{(10.1)^2 + (4.1)^2}$$

$$V_{AN} = \frac{10 + j4}{10.1 + j4.1} 120 \angle -30^\circ$$

$$|V_{AN}| = 120 \frac{10.77}{10.90} = 118.57 (V)_{rms}$$

$$S_{load} = 3 \times (1,212.0 + j484.8)$$

$$S_{source} = 3 \times (1224.1 + j496)$$

(b)



LEARNING EXTENSION

A 480-V rms line feeds two balanced 3-phase loads.
 The loads are rated
 Load 1: 5kVA at 0.8 pf lagging
 Load 2: 10kVA at 0.9 pf lagging.

Determine the magnitude of the line current from the 408-V rms source

$$|S_1| = 5kVA = \frac{P}{0.8} \Rightarrow P_1 = 4kW$$

$$Q_1 = \sqrt{|S_1|^2 - P_1^2} = 3.0kVA$$

$$pf \text{ lagging} \Rightarrow S_1 = 4 + j3kVA$$

$$|S_2| = 10kVA = \frac{P}{0.9} \Rightarrow P = 9kW$$

$$Q_2 = \sqrt{|S_2|^2 - P_2^2} = 4.36kVA$$

$$S_2 = 9 + j4.36kVA$$

$$S_{total} = 13 + j7.36kVA$$

$$S = P + jQ$$

$$P = |S| \cos \theta_f$$

$$Q = |S| \sin \theta_f$$

$$pf = \cos \theta_f$$

$$S_{total} = S_1 + S_2$$

$$P_{total} = \sqrt{3} |V_{line}| |I_{line}| \cos \theta_f$$


$$Q_{total} = \sqrt{3} |V_{line}| |I_{line}| \sin \theta_f$$

$$|S_{total}| = \sqrt{3} |V_{line}| |I_{line}|$$

$$|I_{lineq}| = \frac{|S_{total}|}{\sqrt{3} \times |V_{line}|} = \frac{14,939}{706.68} = 21.14(A)_{rms}$$



POWER FACTOR CORRECTION

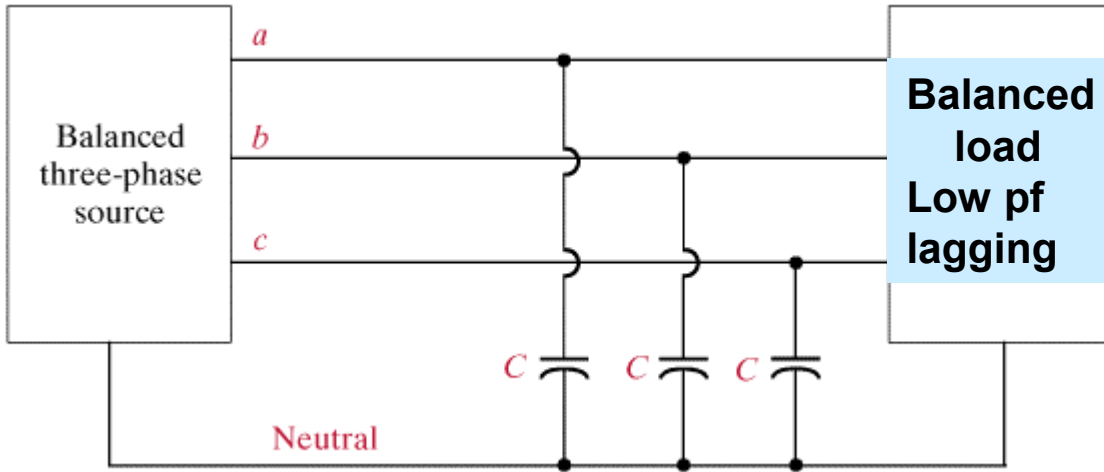

Similar to single phase case.
Use capacitors to increase the power factor

Keep clear about total/phase power, line/phase voltages

$$\left. \begin{matrix} S_{old} \\ pf_{old} \end{matrix} \right\} \rightarrow Q_{old}$$

$$\Delta Q = Q_{new} - Q_{old}$$

$$\left. \begin{matrix} P_{old} \\ pf_{new} \end{matrix} \right\} \rightarrow Q_{new}$$

Reactive Power to be added

To use capacitors this value should be negative

$$Q_{\text{per capacitor}} = -\omega CV^2$$

The voltage depends on how the capacitors are connected

$$S = P + jQ$$

$$P = |S| \cos \theta_f$$

$$Q = |S| \sin \theta_f$$

$$pf = \cos \theta_f$$

$$pf = \cos \theta_f \Rightarrow \sin \theta_f = \sqrt{1 - pf^2}$$

$$Q = P \tan \theta_f$$


lagging $\Rightarrow Q > 0$

$$\tan \theta_f = \frac{pf}{\sqrt{1 - pf^2}}$$



LEARNING EXAMPLE

$f = 60\text{Hz}$, $|V_{line}| = 34.5\text{kV rms}$. Required $pf = 0.94\text{leading}$

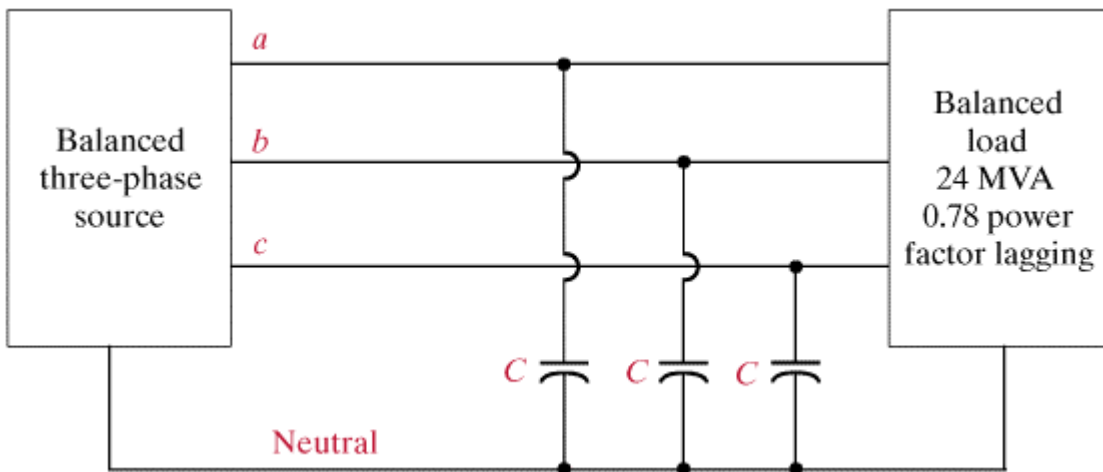

$$S = P + jQ$$

$$P = |S| \cos \theta_f$$

$$Q = |S| \sin \theta_f$$

$$pf = \cos \theta_f$$

$$Q = P \tan \theta_f$$

$$\tan \theta_f = \frac{pf}{\sqrt{1 - pf^2}}$$

$$\text{lagging} \Rightarrow Q_{old} > 0$$

$$pf = \cos \theta_f \Rightarrow \sin \theta_f = \sqrt{1 - pf^2} = 0.626$$

$$|Q_{old}| = 15.02\text{MVA}$$

$$P_{old} = 18.72\text{MW}$$

$$\left. \begin{array}{l} P_{old} = 18.72\text{MW} \\ pf_{new} = 0.94\text{leading} \end{array} \right\} \Rightarrow Q_{new} = -6.8\text{MVA}$$

$$\Delta Q = -6.8 - 15.02 = -21.82\text{MVA}$$

$$Q_{\text{per capacitor}} = -7.273\text{MVA}$$

$$Y\text{-connection} \Rightarrow V_{\text{capacitor}} = \frac{34.5}{\sqrt{3}}\text{kV rms}$$


$$-7.273 \times 10^6 = -2\pi \times 60 \times C \times \left(\frac{34.5 \times 10^3}{\sqrt{3}} \right)^2$$

$$C = 48.6\mu\text{F}$$



LEARNING EXAMPLE

$f = 60\text{Hz}$, $|V_{line}| = 34.5\text{kV rms}$. Required $pf = 0.90\text{lagging}$

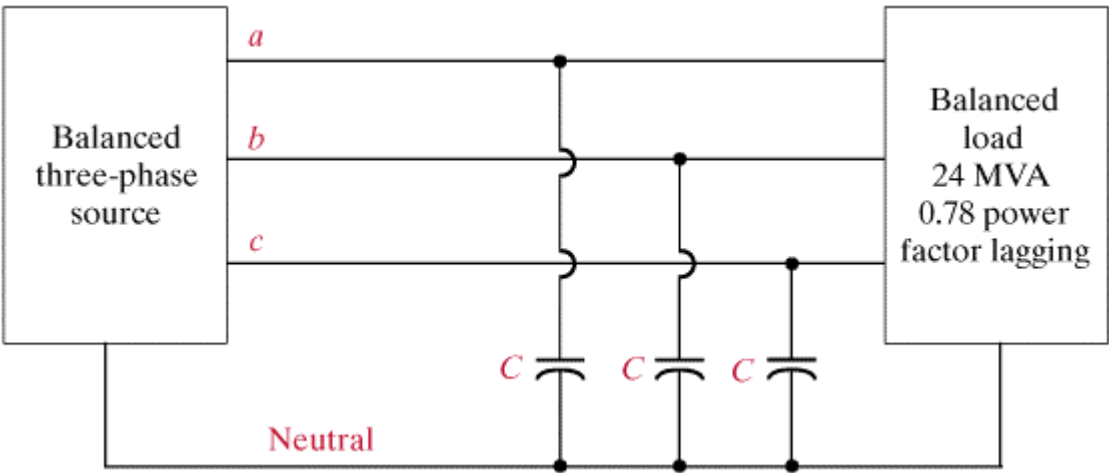

$S = P + jQ$
 $P = |S| \cos \theta_f$
 $Q = |S| \sin \theta_f$
 $pf = \cos \theta_f$

$Q = P \tan \theta_f$

$\tan \theta_f = \frac{pf}{\sqrt{1 - pf^2}}$

lagging $\Rightarrow Q_{old} > 0$

$pf = \cos \theta_f \Rightarrow \sin \theta_f = \sqrt{1 - pf^2} = 0.626$

$|Q_{old}| = 15.02\text{MVA}$
 $P_{old} = 18.72\text{MW}$

$P_{old} = 18.72\text{MW}$
 $pf_{new} = 0.90\text{lagging}$

$\Rightarrow Q_{new} = -9.067\text{MVA}$

$\Delta Q = 9.067 - 15.02 = -5.953\text{MVA}$

$Q_{\text{per capacitor}} = -1.984\text{MVA}$

Y-connection $\Rightarrow V_{\text{capacitor}} = \frac{34.5}{\sqrt{3}}\text{kV rms}$


$-1.984 \times 10^6 = -2\pi \times 60 \times C \times \left(\frac{34.5 \times 10^3}{\sqrt{3}} \right)^2$

$C = 13.26\mu\text{F}$




LEARNING EXAMPLE

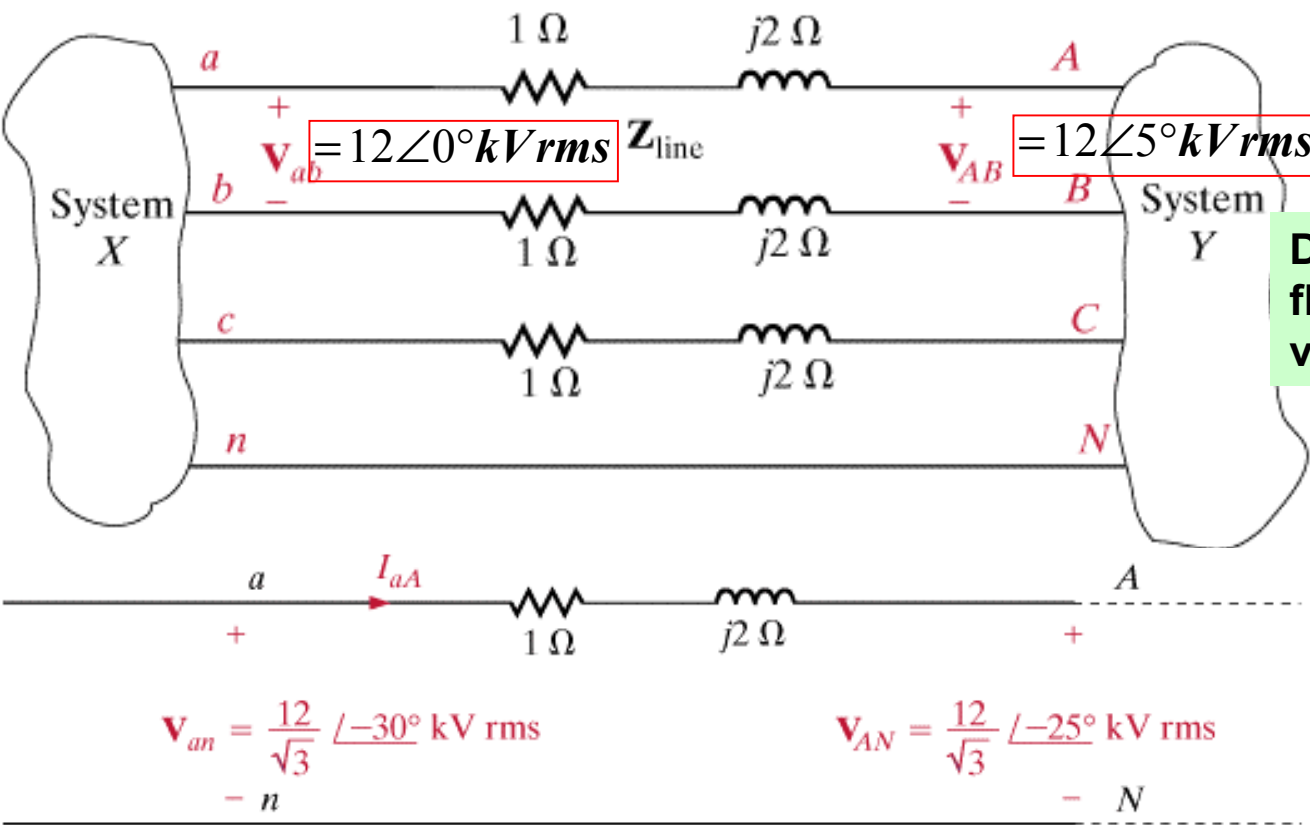MEASURING POWER FLOW Which circuit is the source and what is the average power supplied?



Phase differences determine direction of power flow!

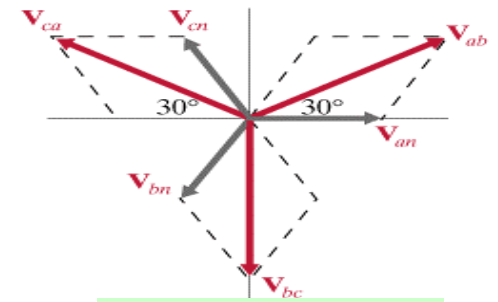Determine the current flowing. Convert line voltages to phase voltages



$$S_Y = 3V_{AN} \times I_{aA}^*$$

$$S_X = 3V_{an} (-I_{aA})^*$$

Equivalent 1-phase circuit

$$I_{aA} = \frac{V_{an} - V_{AN}}{1 + j2} = \frac{\frac{12000}{\sqrt{3}} \angle -30^\circ - \frac{12000}{\sqrt{3}} \angle -25^\circ}{1 + j2}$$

$$I_{aA} = 270.30 \angle -180.93 (A) rms$$

$$S_Y = \sqrt{3} \times 12 \times 0.2703 \angle (-25 + 180.93)^\circ MVA$$

$$S_X = -\sqrt{3} \times 12 \times 0.2703 \angle (-30 + 180.93)^\circ MVA$$

$$P_Y = -5.13 MW$$

$$P_X = 4.91 MW$$

$$S = P + jQ$$

$$P = |S| \cos \theta_f$$

System Y is the source

$$P_{loss} = -(P_X + P_Y)$$



CAPACITOR SPECIFICATIONS

Capacitors for power factor correction are normally specified in VARs

$$|Q_{\text{per capacitor}}| = \omega CV^2$$


The voltage and frequency must be given in order to know the capacitance

Assume 60Hz unless other value is given.

LEARNING EXAMPLE

For pf = 0.94 leading one needs

$$C = 48.6 \mu F$$

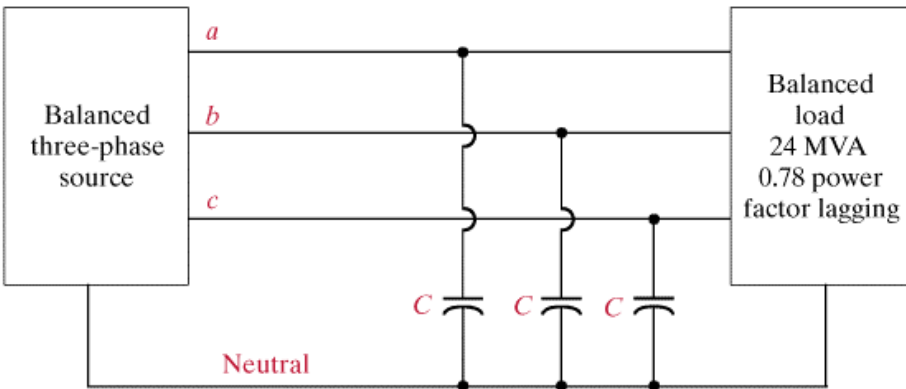

$$V_{\text{line}} = 34.5 \text{ kV} \Rightarrow V_{\text{phase}} = 19.9 \text{ kV}$$

Capacitor 1 is not rated at high enough voltage!

Choices available

Capacity	Rated Voltage (kV)	Rated Q (Mvar)
1	10	4
2	50	25
3	20	7.5

$$C_1 = \frac{4 \times 10^6}{2\pi \times 60 \times (10 \times 10^3)^2} = 106.1 \mu F$$


$$C_2 = \frac{25 \times 10^6}{2\pi \times 60 \times (50 \times 10^3)^2} = 26.53 \mu F$$

$$C_3 = \frac{7.5 \times 10^6}{2\pi \times 60 \times (20 \times 10^3)^2} = 49.7 \mu F$$

Capacitor 3 is the best alternative



LEARNING BY DESIGN

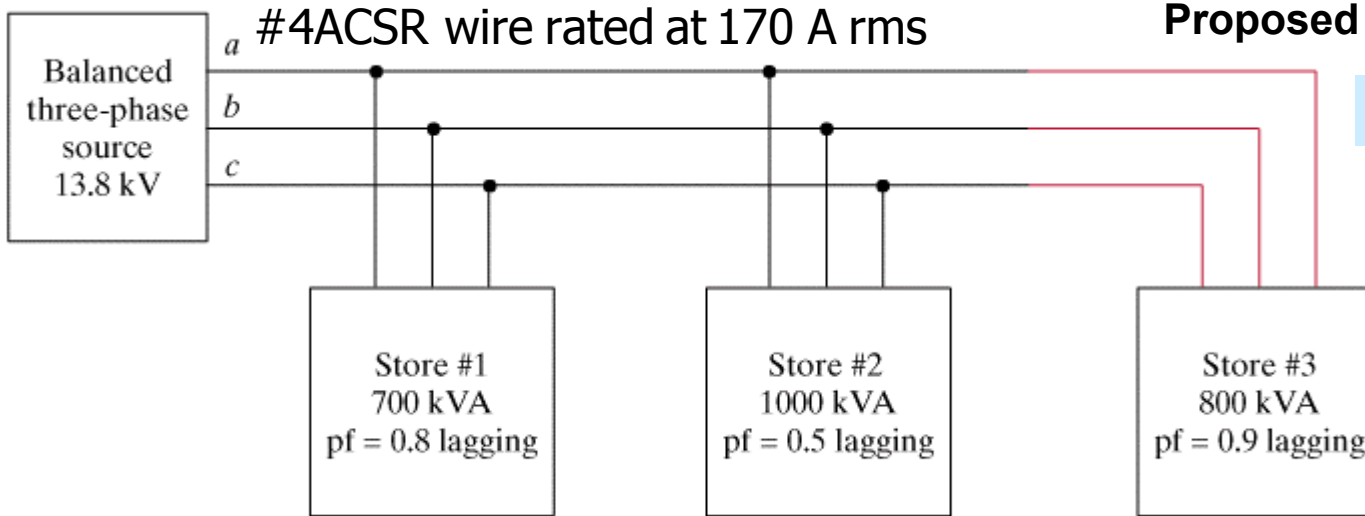

1. Is the wire suitable?
 2. What capacitance would be required to have a composite pf = 0.92 lagging
- Capacitors are to be Y - connected

$$S_1 = 700 \angle 36.9^\circ = 560 + j420 \text{ kVA}$$

$$S_2 = 1000 \angle 60^\circ \text{ kVA} = 500 + j866 \text{ kVA}$$

$$S_3 = 800 \angle 25.8^\circ \text{ kVA} = 720 + j349 \text{ kVA}$$

$$S_{total} = 1780 + j1635 \text{ kVA} = 2417 \angle 42.57^\circ \text{ kVA}$$

$$S_{total} = S_1 + S_2 + S_3$$

$$S = P + jQ$$

$$P = |S| \cos \theta_f$$

$$Q = |S| \sin \theta_f$$

$$pf = \cos \theta_f$$

$$|I_{line}| = \frac{|S_{total}|}{\sqrt{3} \times V_{line}} = \frac{2.417 \times 10^6}{\sqrt{3} \times 13.8 \times 10^3} = 101.1 \text{ Arms}$$

Wire is OK

$$\left. \begin{matrix} P_{old} \\ pf_{new} \end{matrix} \right\} \rightarrow Q_{new} = P \tan \theta_{f(new)} = 758.28 \text{ kVA}$$

$$S_{Total} = 3 \times V_{phase} \times I_{phase}^*$$

$$= \sqrt{3} \times V_{line} \times I_{line}^*$$

$$\Delta Q = Q_{new} - Q_{old} = -876.72 \text{ kVA}$$

Polyphase

$$|Q_{per capacitor}| = \omega C V^2$$

$$V = |V_{phase}| = \frac{13.8 \text{ kV}}{\sqrt{3}}$$

$$C = \frac{(876.72 \times 10^3 / 3)}{2\pi \times 60 \times (13.8 \times 10^3)^2 / 3} = 12.2 \mu F$$

