

ADDITIONAL ANALYSIS TECHNIQUES

LEARNING GOALS

REVIEW LINEARITY

The property has two equivalent definitions.
We show and application of homogeneity

APPLY SUPERPOSITION

We discuss some implications of the superposition property in linear circuits

DEVELOP THEVENIN'S AND NORTON'S THEOREMS

These are two very powerful analysis tools that allow us to focus on parts of a circuit and hide away unnecessary complexities

MAXIMUM POWER TRANSFER

This is a very useful application of Thevenin's and Norton's theorems



THE METHODS OF NODE AND LOOP ANALYSIS PROVIDE POWERFUL TOOLS TO DETERMINE THE BEHAVIOR OF EVERY COMPONENT IN A CIRCUIT









The techniques developed in chapter 2; i.e., combination series/parallel, voltage divider and current divider are special techniques that are more efficient than the general methods, but have a limited applicability. It is to our advantage to keep them in our repertoire and use them when they are more efficient.

In this section we develop additional techniques that simplify the analysis of some circuits.

In fact these techniques expand on concepts that we have already introduced: linearity and circuit equivalence



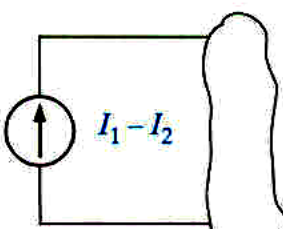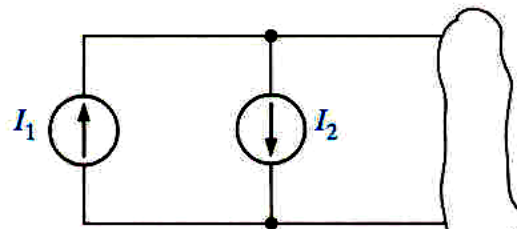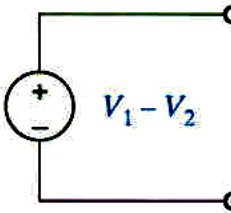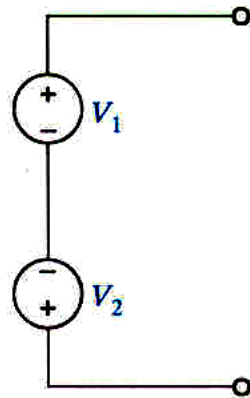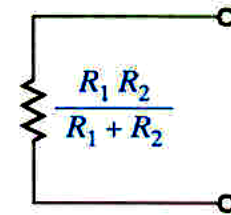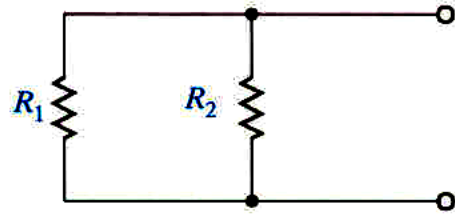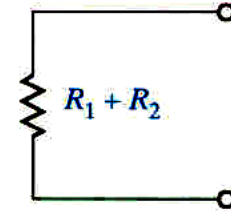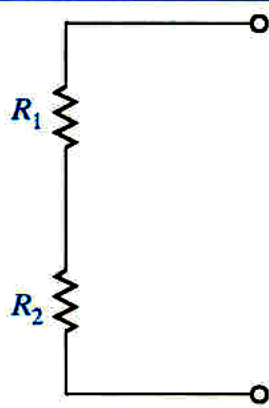**SOME EQUIVALENT CIRCUITS
ALREADY USED**



LINEARITY

THE MODELS USED ARE ALL LINEAR. MATHEMATICALLY THIS IMPLIES THAT THEY SATISFY THE PRINCIPLE OF SUPERPOSITION

THE MODEL $y = Tu$ IS LINEAR IFF

$$T(\alpha_1 u_1 + \alpha_2 u_2) = \alpha_1 T u_1 + \alpha_2 T u_2$$

for all possible input pairs u_1, u_2

and all possible scalars α_1, α_2

AN ALTERNATIVE, AND EQUIVALENT, DEFINITION OF LINEARITY SPLITS THE SUPERPOSITION PRINCIPLE IN TWO.

THE MODEL $y = Tu$ IS LINEAR IFF

1. $T(u_1 + u_2) = T u_1 + T u_2, \forall u_1, u_2$ additivity
2. $T(\alpha u) = \alpha T u, \forall \alpha, \forall u$ homogeneity

NOTICE THAT, TECHNICALLY, LINEARITY CAN NEVER BE VERIFIED EMPIRICALLY ON A SYSTEM. BUT IT COULD BE DISPROVED BY A SINGLE COUNTER EXAMPLE. IT CAN BE VERIFIED MATHEMATICALLY FOR THE MODELS USED.

USING NODE ANALYSIS FOR RESISTIVE CIRCUITS ONE OBTAINS MODELS OF THE FORM $Av = f$

v IS A VECTOR CONTAINING ALL THE NODE VOLTAGES AND f IS A VECTOR DEPENDING ONLY ON THE INDEPENDENT SOURCES. IN FACT THE MODEL CAN BE MADE MORE DETAILED AS FOLLOWS

$$Av = Bs$$

HERE, A, B , ARE MATRICES AND s IS A VECTOR OF ALL INDEPENDENT SOURCES


FOR CIRCUIT ANALYSIS WE CAN USE THE LINEARITY ASSUMPTION TO DEVELOP SPECIAL ANALYSIS TECHNIQUES

FIRST WE REVIEW THE TECHNIQUES CURRENTLY AVAILABLE




A CASE STUDY TO REVIEW PAST TECHNIQUES


DETERMINE V_0

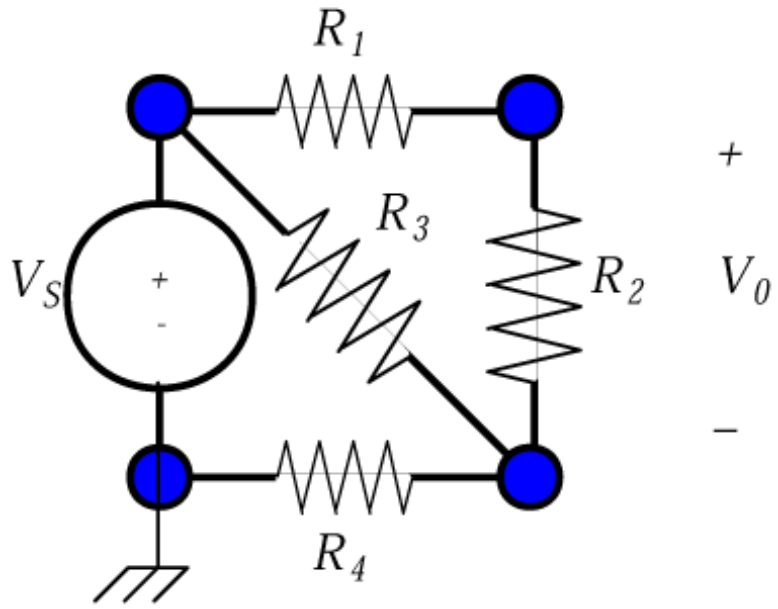


SOLUTION TECHNIQUES AVAILABLE??

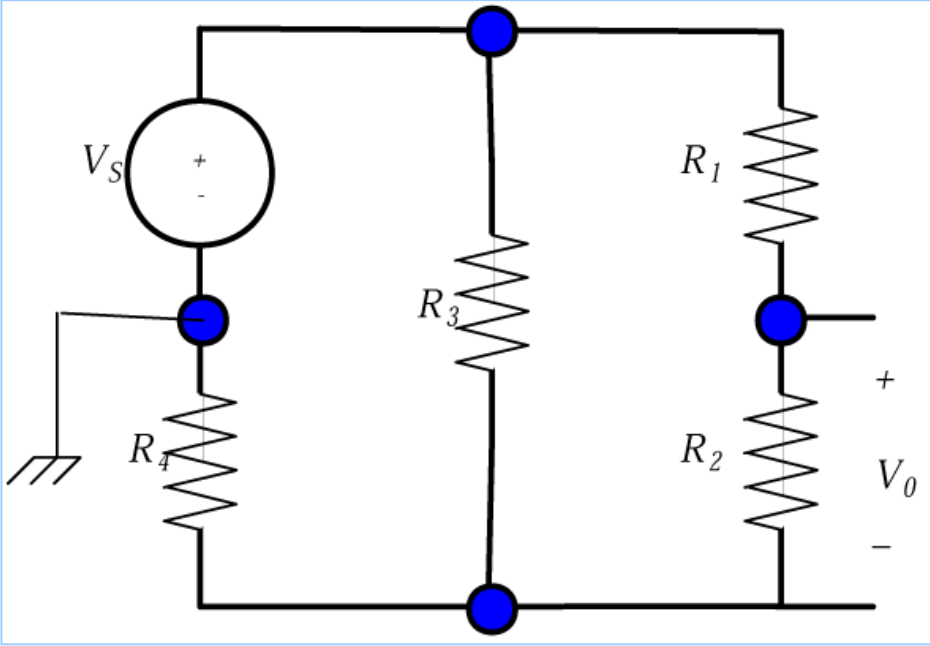Redrawing the circuit may help us in recognizing special cases



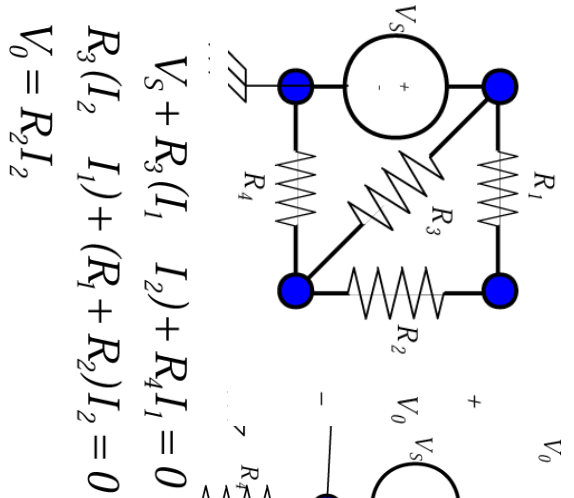

LOOP ANALYSIS

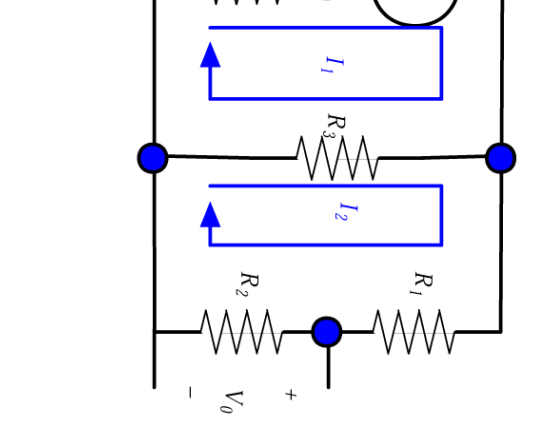

NODE ANALYSIS

$$V_1 = V_S$$

$$\frac{V_2}{R_1} + \frac{V_2}{R_4} + \frac{V_2}{R_2} - \frac{V_0}{R_2} = 0$$


$$\frac{V_0}{R_2} + \frac{V_0}{R_1} - \frac{V_1}{R_1} = 0$$

$$V_S + R_3(I_1 - I_2) + R_4 I_1 = 0$$

$$R_3(I_2 - I_1) + (R_1 + R_2)I_2 = 0$$

$$V_0 = R_2 I_2$$

COMBINATION SERIES/PARALLEL

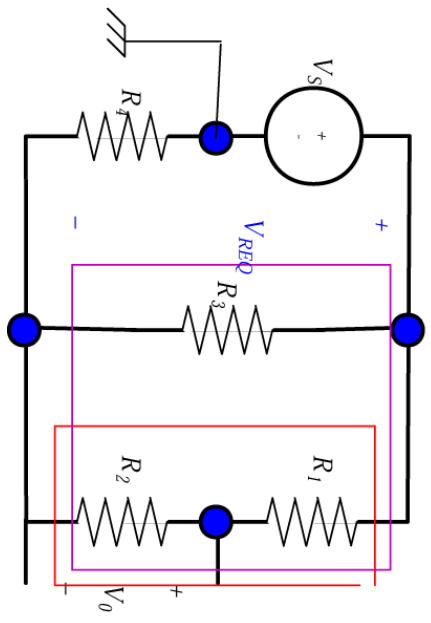

$$R_{EQ} = \frac{R_3(R_1 + R_2)}{R_1 + R_2 + R_3}$$

$$R_{EQ} = \parallel R_3, (R_1 + R_2) \parallel$$


$$V_{REQ} = \frac{R_{REQ}}{R_{REQ} + R_4} V_S$$

VOLTAGE DIVIDER

$$V_0 = \frac{R_2}{R_2 + R_3} V_{REQ}$$



USING HOMOGENEITY

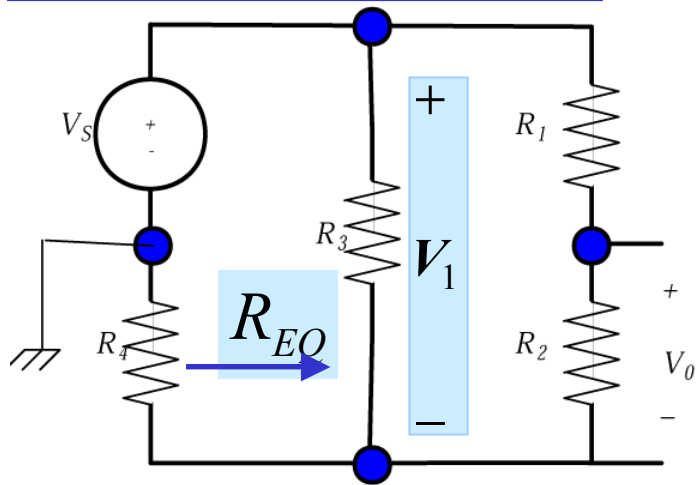

The procedure can be made entirely algorithmic

1. Give to V_0 any arbitrary value (e.g., $V'_0 = 1$)
2. Compute the resulting source value and call it V'_s
3. Use linearity. $V'_s \rightarrow V'_0 \Rightarrow kV'_s \rightarrow kV'_0, \forall k$
4. The given value of the source (V_s) corresponds to

$$k = \frac{V_s}{V'_s}$$

Hence the desired output value is

$$V_0 = kV'_0 = \frac{V_s}{V'_s} V'_0$$

Assume that the answer is known. Can we Compute the input in a very easy way ?!!

If V_0 is given then V_1 can be computed using an inverse voltage divider.

$$V_1 = \frac{R_1 + R_2}{R_2} V_0$$

... And V_s using a second voltage divider


$$V_s = \frac{R_4 + R_{EQ}}{R_{EQ}} V_1 = \frac{R_4 + R_{EQ}}{R_{EQ}} \frac{R_1 + R_2}{R_2} V_0$$

Solve now for the variable V_0

This is a nice little tool for special problems. Normally when there is only one source and when in our judgement solving the problem backwards is actually easier



SOLVE USING HOMOGENEITY

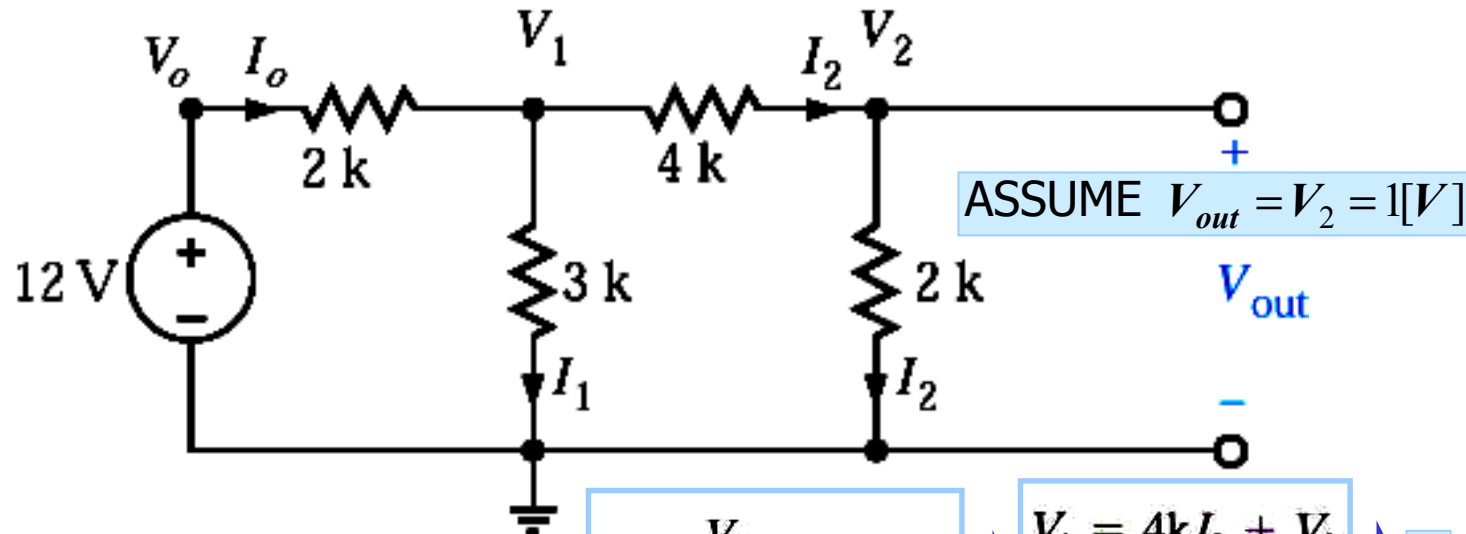

$$I_2 = \frac{V_2}{2k} = 0.5 \text{ mA}$$

$$V_1 = 4kI_2 + V_2 = 3 \text{ V}$$

$$I_1 = \frac{V_1}{3k} = 1 \text{ mA}$$

$$I_o = I_1 + I_2 = 1.5 \text{ mA}$$

$$V_o = 2kI_o + V_1 = 6 \text{ V}$$

NOW USE HOMOGENEITY

$$V_o = 6[V] \rightarrow V_{out} = 1[V]$$


$$V_o = 12[V] \rightarrow V_{out} = 2[V]$$



LEARNING EXTENSION

COMPUTE I_o USING HOMOGENEITY. USE $I = 6mA$
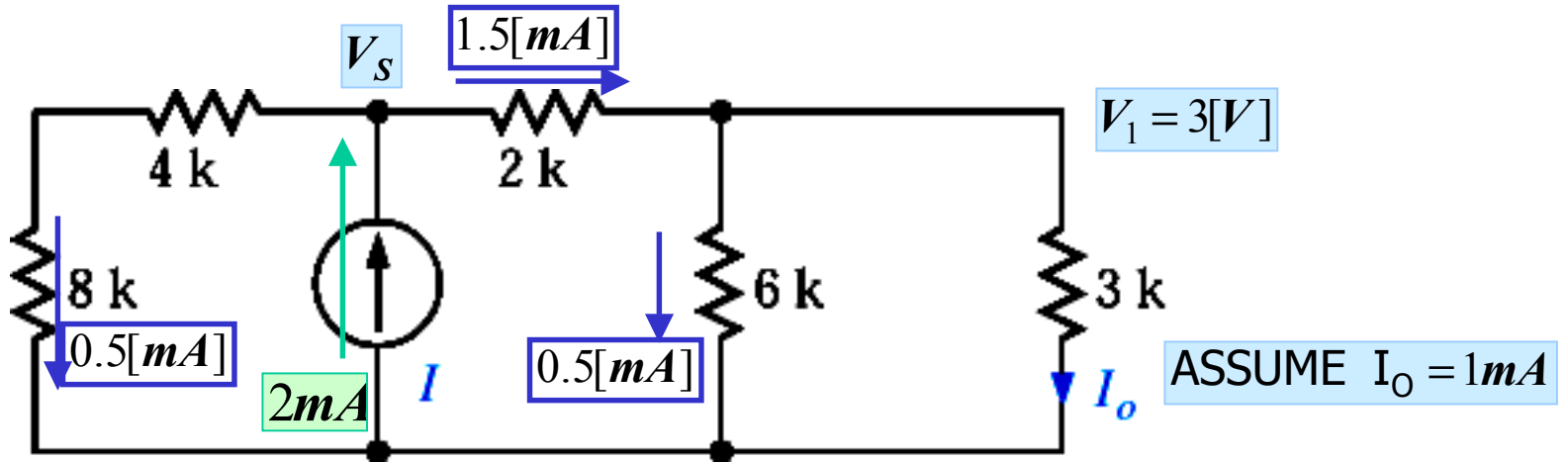
$$V_s = 1.5[mA] \times 2k\Omega + V_1 = 6[V]$$



USE HOMOGENEITY

$$I = 2mA \rightarrow I_o = 1mA$$

$$I = 6mA \rightarrow I_o = \underline{\quad}$$



Source Superposition

This technique is a direct application of linearity.

It is normally useful when the circuit has only a few sources.



FOR CLARITY WE SHOW A CIRCUIT WITH ONLY TWO SOURCES

Due to Linearity


$$V_L = a_1 V_S + a_2 I_S$$

CONTRIBUTION BY V_S

$$V_L^1$$

CONTRIBUTION BY I_S

$$V_L^2$$

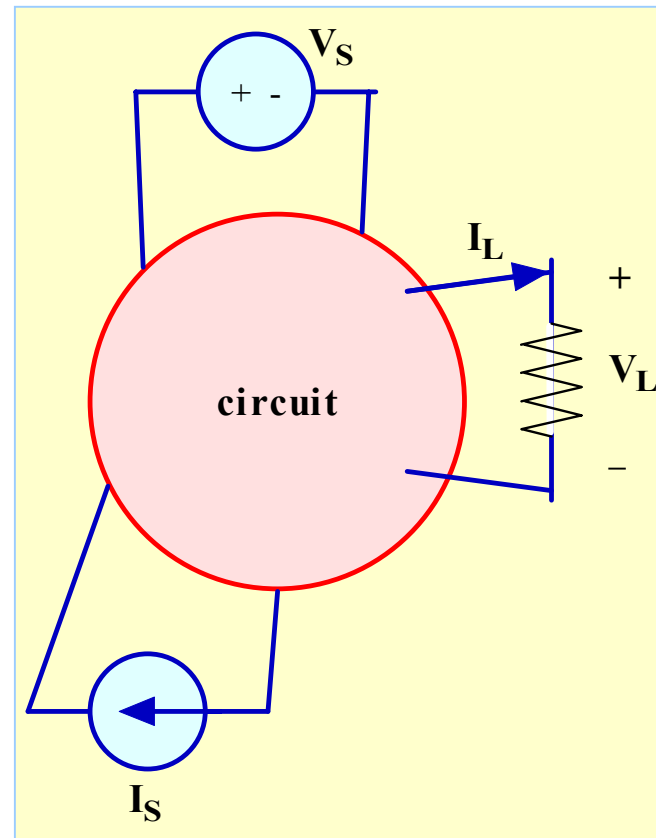

$$V_L^1$$


Can be computed by setting the current source to zero and solving the circuit

$$V_L^2$$


Can be computed by setting the voltage source to zero and solving the circuit



SOURCE SUPERPOSITION

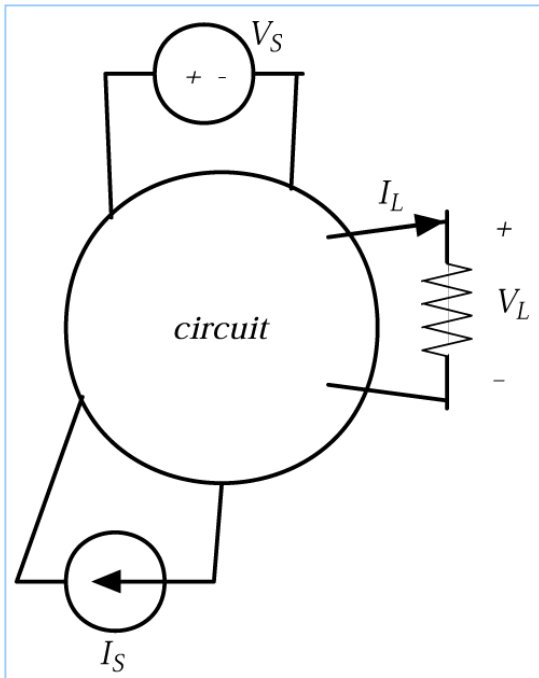


=

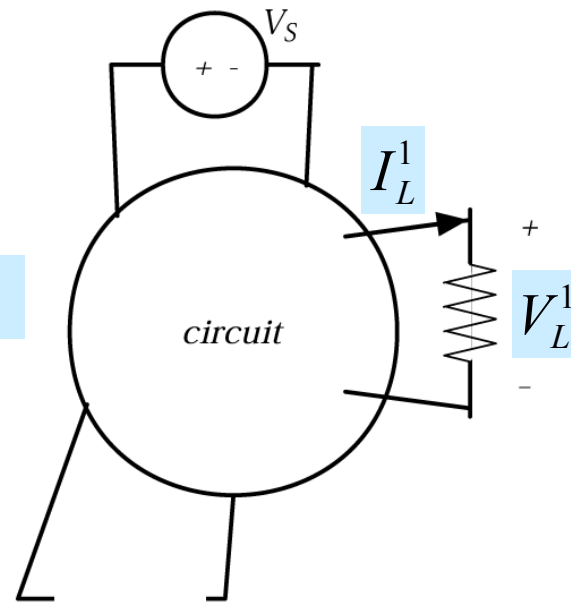

Circuit with current source set to zero (OPEN)

+

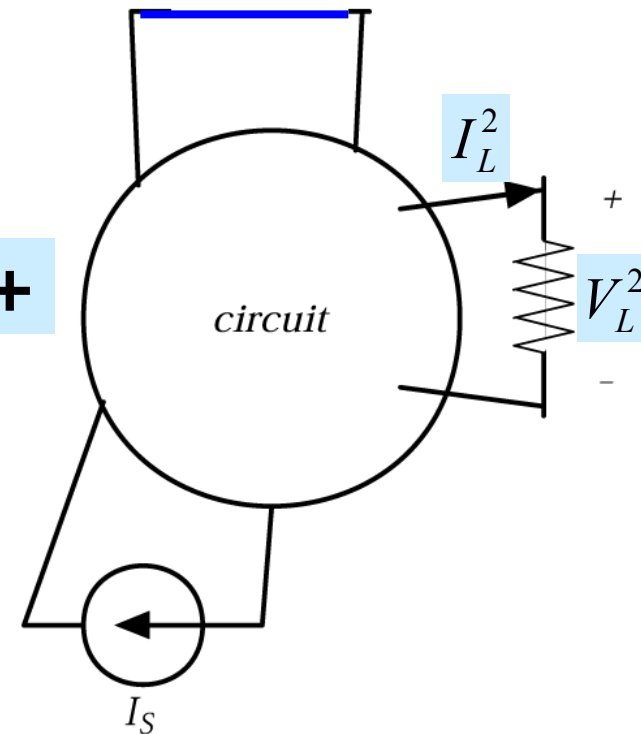

Due to the linearity of the models we must have

$$I_L = I_L^1 + I_L^2 \quad V_L = V_L^1 + V_L^2$$

Principle of Source Superposition


The approach will be useful if solving the two circuits is simpler, or more convenient, than solving a circuit with two sources

We can have any combination of sources. And we can partition any way we find convenient




LEARNING EXAMPLE


WE WISH TO COMPUTE THE CURRENT i_1

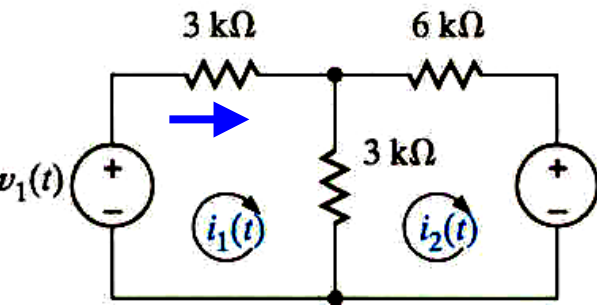

=

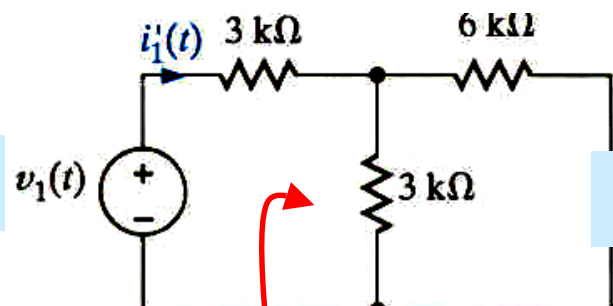

+

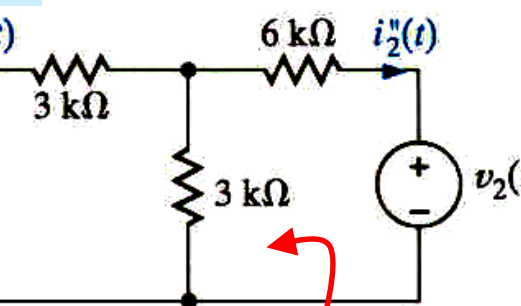

$$6ki_1(t) - 3ki_2(t) = v_1(t)$$

$$-3ki_1(t) + 9ki_2(t) = -v_2(t)$$

Loop equations

$$R_{eq} = 3 + 3 \parallel 6 [k]$$

$$R_{eq} = 6 + (3 \parallel 3) [k]$$

$$i_1'(t) = \frac{v_1(t)}{3k + \frac{(3k)(6k)}{3k + 6k}}$$

$$= \frac{v_1(t)}{5k}$$

Contribution of v1

$$i_2'' = \frac{v_2}{R_{eq}}$$

$$i_1''(t) = \frac{-2v_2(t)}{15k} \left(\frac{3k}{3k + 3k} \right)$$

$$= \frac{-v_2(t)}{15k}$$


Contribution of v2

Once we know the "partial circuits" we need to be able to solve them in an efficient manner




LEARNING EXAMPLE

Compute V_0 using source superposition

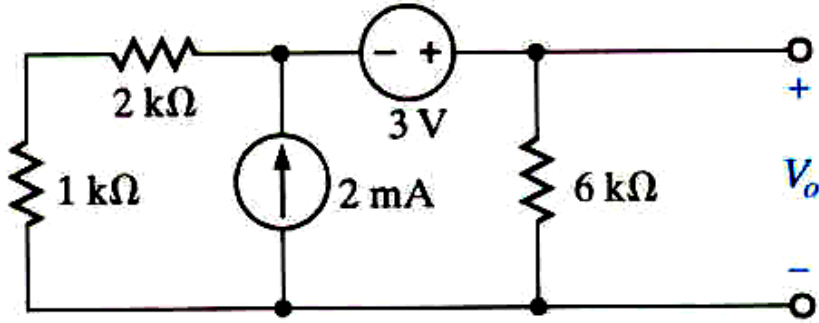

We set to zero the voltage source

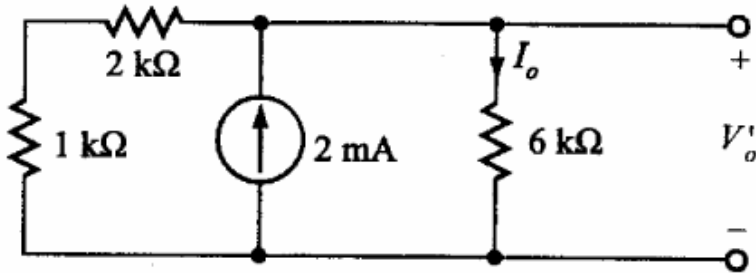


$$I_o = (2 \times 10^{-3}) \left(\frac{1k + 2k}{1k + 2k + 6k} \right)$$

Current division


$$V'_0 = I_o(6k) = 4 V$$

Ohm's law

Now we set to zero the current source

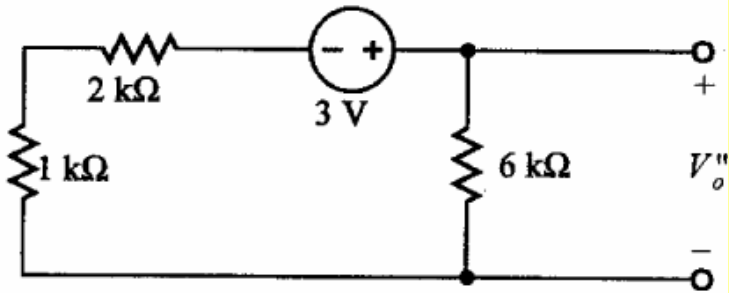

Voltage Divider

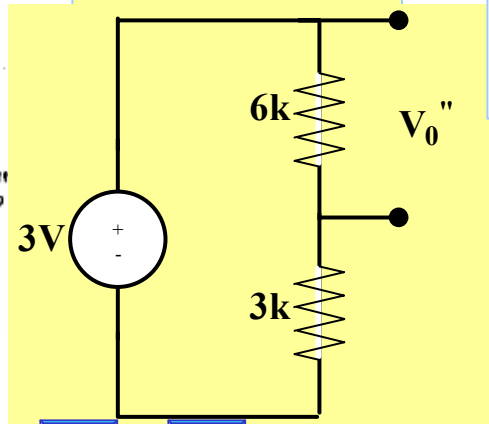


$$V''_0 = 3 \left(\frac{6k}{1k + 2k + 6k} \right) = 2[V]$$

$$V_0 = V'_0 + V''_0 = 6[V]$$

LEARNING EXAMPLE

Compute V_o using source superposition


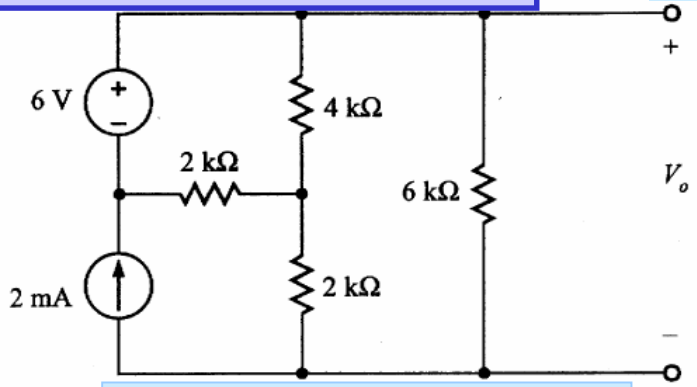
We must be able to solve each circuit in a very efficient manner!!!




If V_1 is known then V'_o is obtained using a voltage divider

V_1 can be obtained by series parallel reduction and divider

Set to zero current source

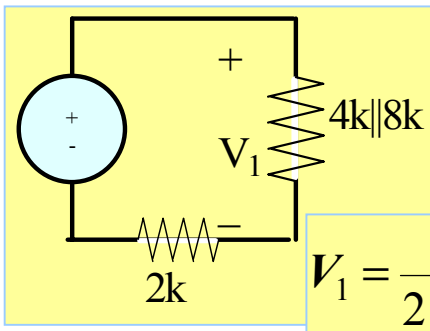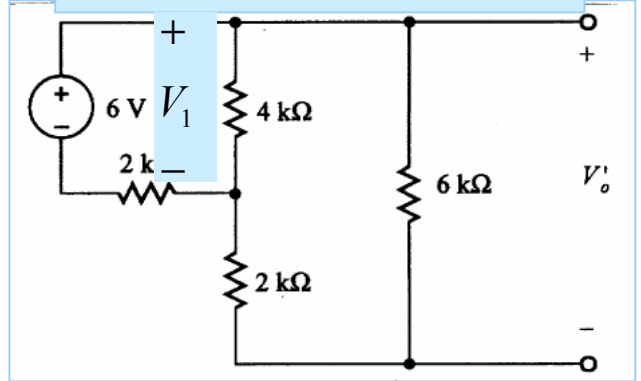


$$V_1 = \frac{8/3}{2 + 8/3} (6)$$

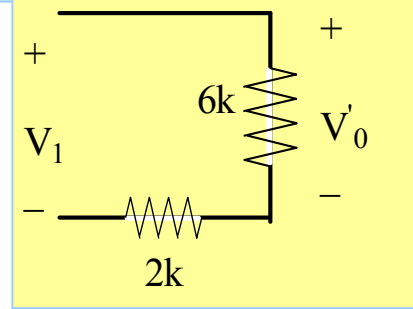


$$V'_o = \frac{6k}{6k + 2k} V_1 = \frac{18}{7} [V]$$

Set to zero voltage source

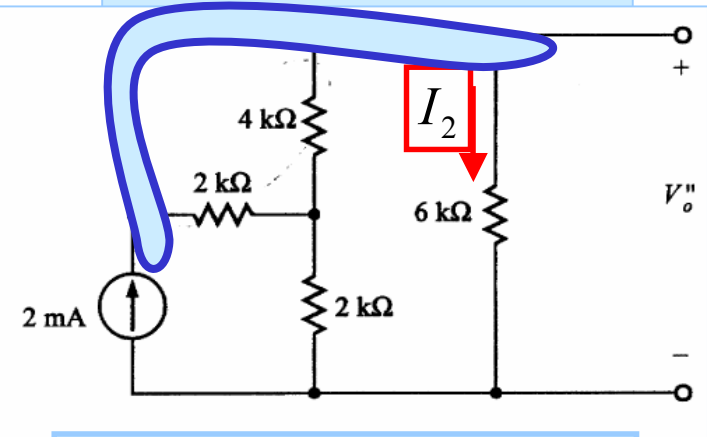

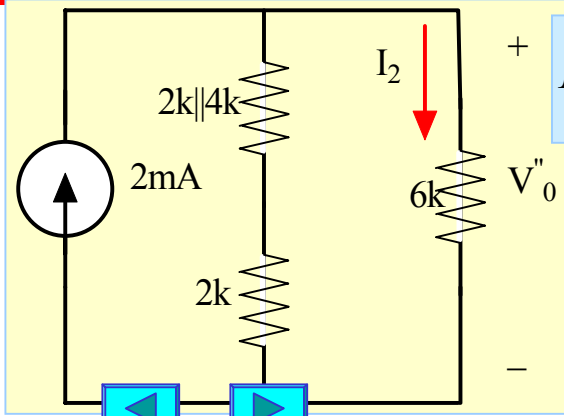The current I_2 can be obtained using a current divider and V''_o using Ohm's law



$$I_2 = \frac{2k + (2k \parallel 4k)}{2k + 6k + (2k \parallel 4k)} (2)mA$$


$$V''_o = 6kI_2$$

$$V_o = V'_o + V''_o$$


WHEN IN DOUBT... REDRAW!



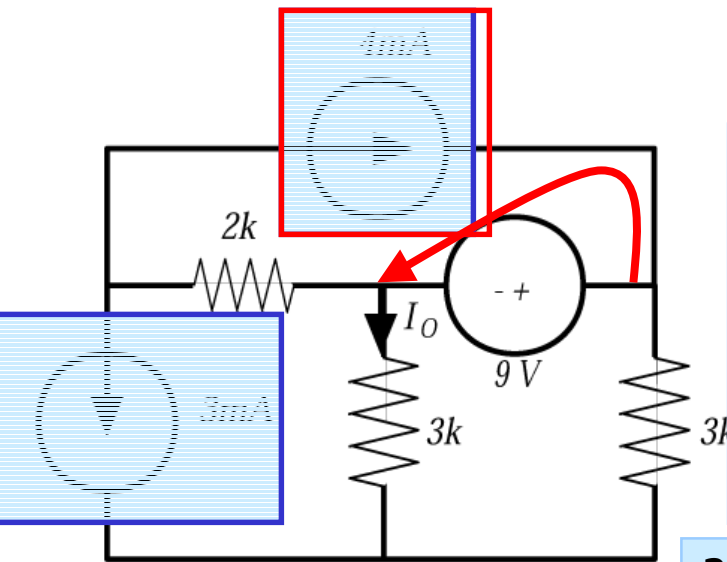Sample Problem COMPUTE I_0 USING SOURCE SUPERPOSITION



1. Consider only the voltage source

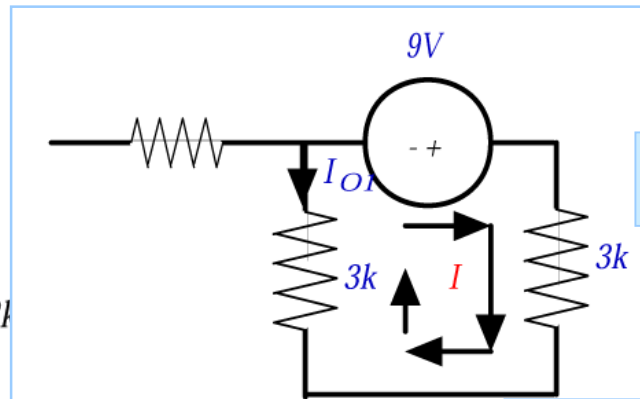


$$I_{01} = -1.5mA$$


2. Consider only the 3mA source

Current divider

$$I_{02} = -1.5mA$$

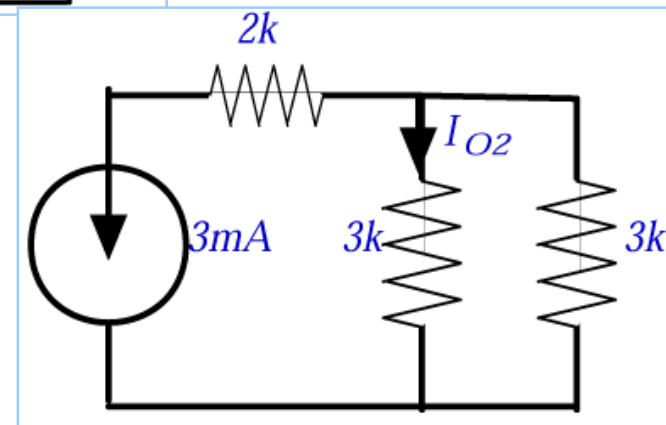

3. Consider only the 4mA source

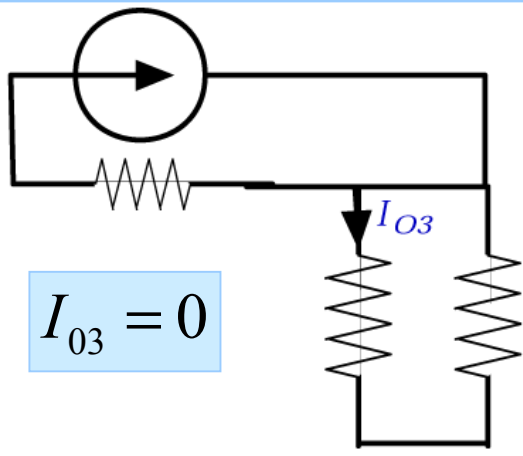


$$I_{03} = 0$$

Using source superposition


$$I_0 = I_{01} + I_{02} + I_{03} = -3mA$$



USE SOURCE SUPERPOSITION TO COMPUTE I_O

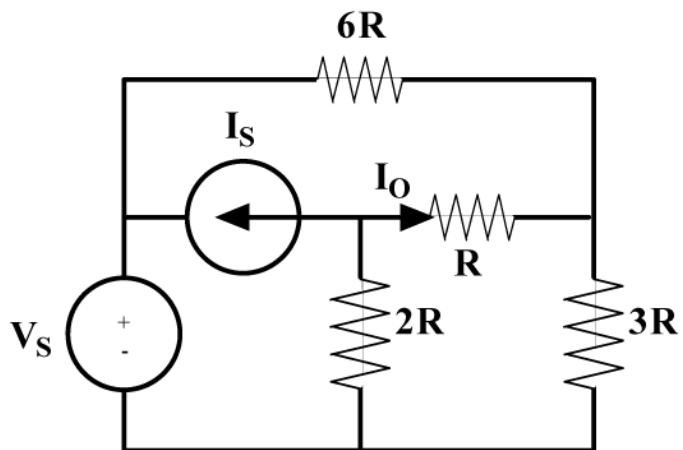


open current source

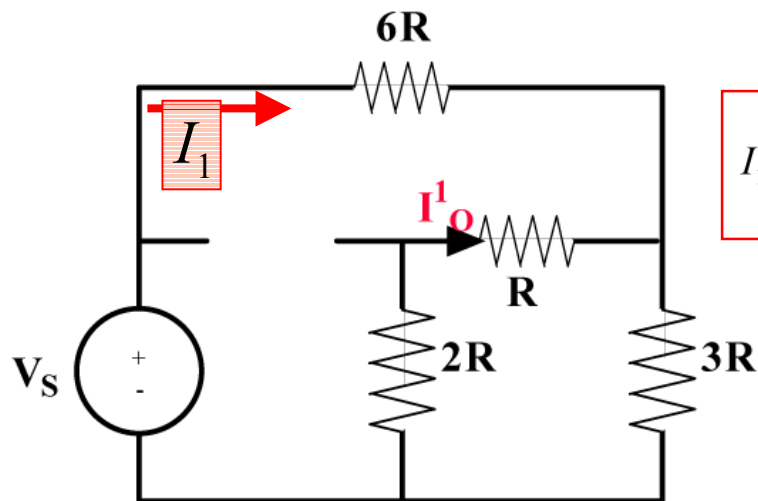


$$I_1 = \frac{V_s}{6R + \parallel 3R, 3R \parallel}$$

$$I_o^1 = -\frac{I_1}{2}$$

short circuit voltage source

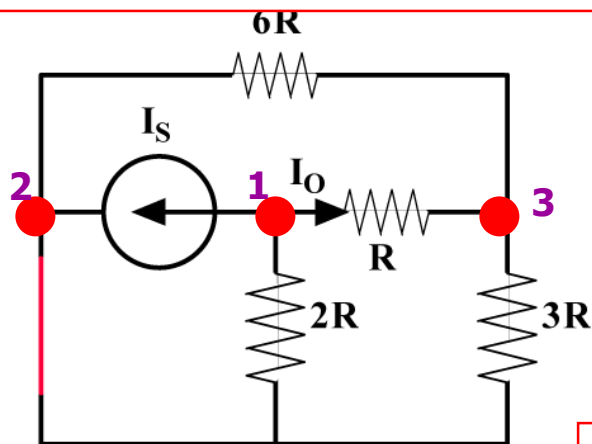

in case of doubt: REDRAW CIRCUIT!

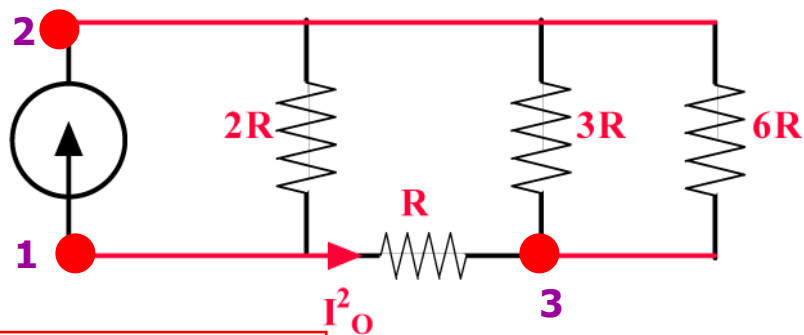

NOW USE CURRENT DIVIDER

$$I_o^2 = -\frac{2R}{2R + R + \parallel 3R, 6R \parallel} I_s$$

$$I_o^2 = -\frac{2}{5} I_s$$

$$I_o = I_o^1 + I_o^2$$

$$I_o = -\frac{V_s}{15R} - \frac{2}{5} I_s$$

Linearity

