

# THEVENIN'S AND NORTON'S THEOREMS

These are some of the most powerful analysis results to be discussed.


They permit to hide information that is not relevant and concentrate in what is important to the analysis



# Low distortion audio power amplifier

**TO MATCH SPEAKERS AND AMPLIFIER ONE SHOULD ANALYZE THIS CIRCUIT**

From PreAmp (voltage)

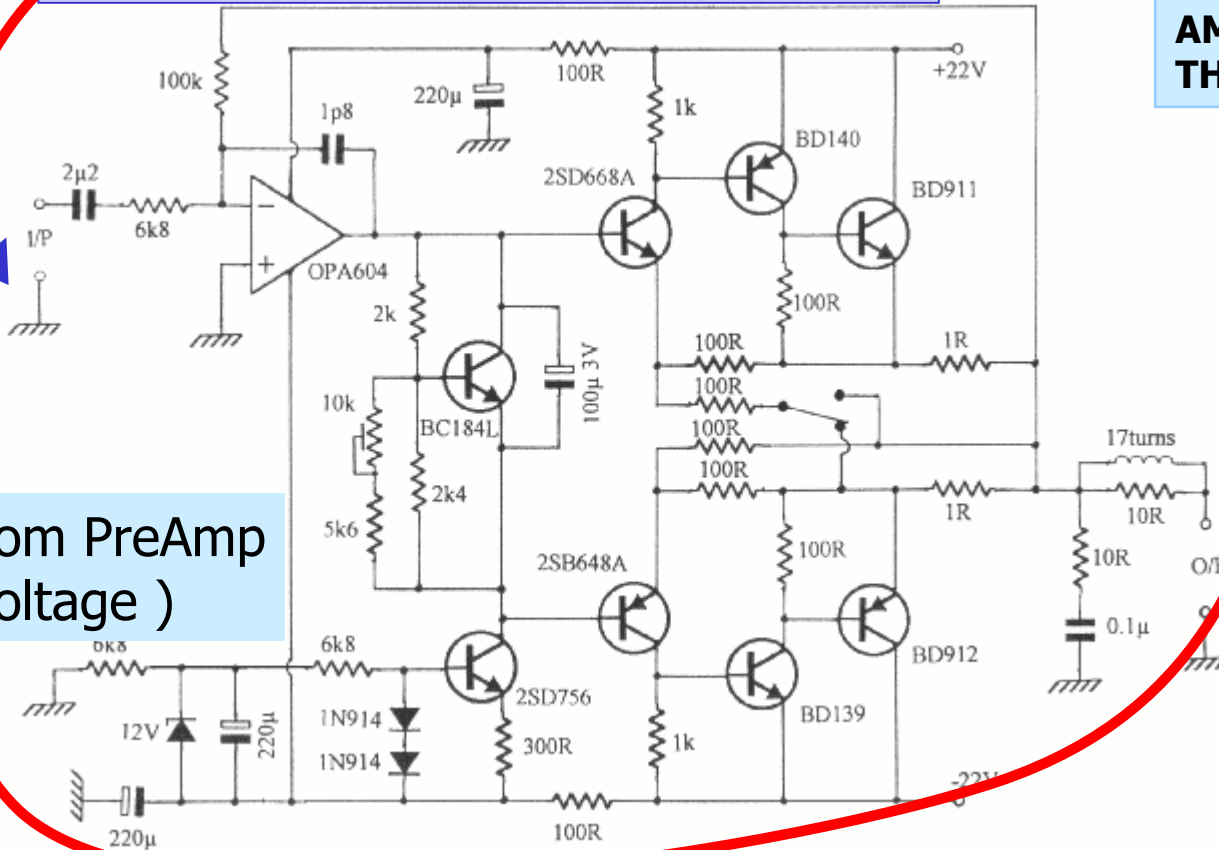


To speakers

Courtesy of M.J. Renardson

<http://angelfire.com/ab3/mjramp/index.html>


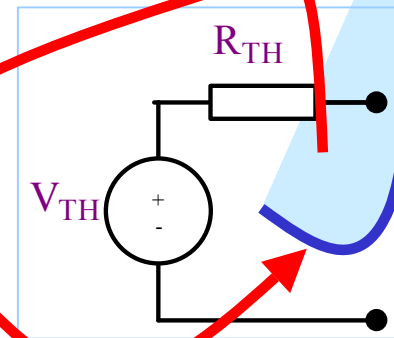
**TO MATCH SPEAKERS AND AMPLIFIER IT IS MUCH EASIER TO CONSIDER THIS EQUIVALENT CIRCUIT!**



**REPLACE AMPLIFIER BY SIMPLER "EQUIVALENT"**



# THEVENIN'S EQUIVALENT THEOREM

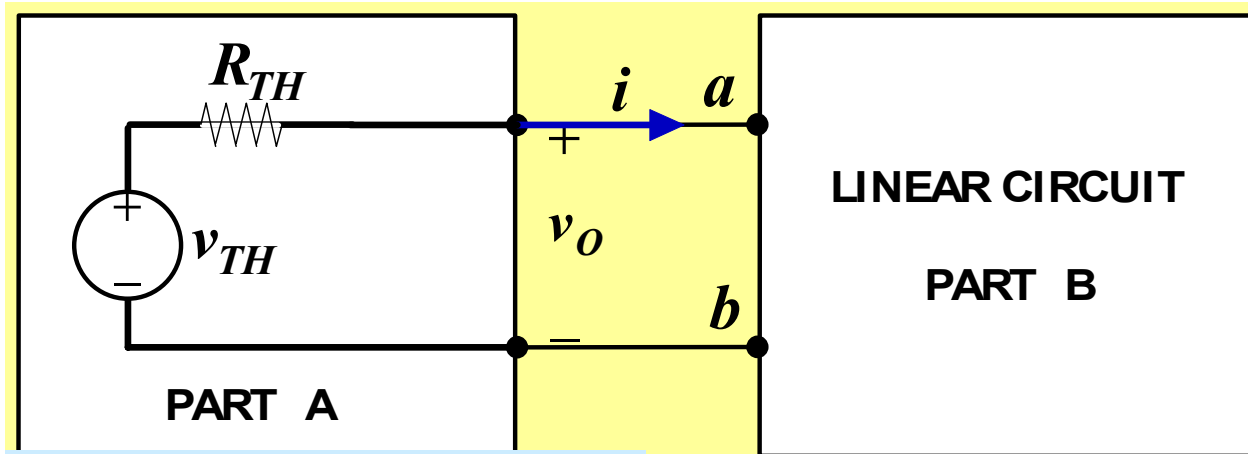
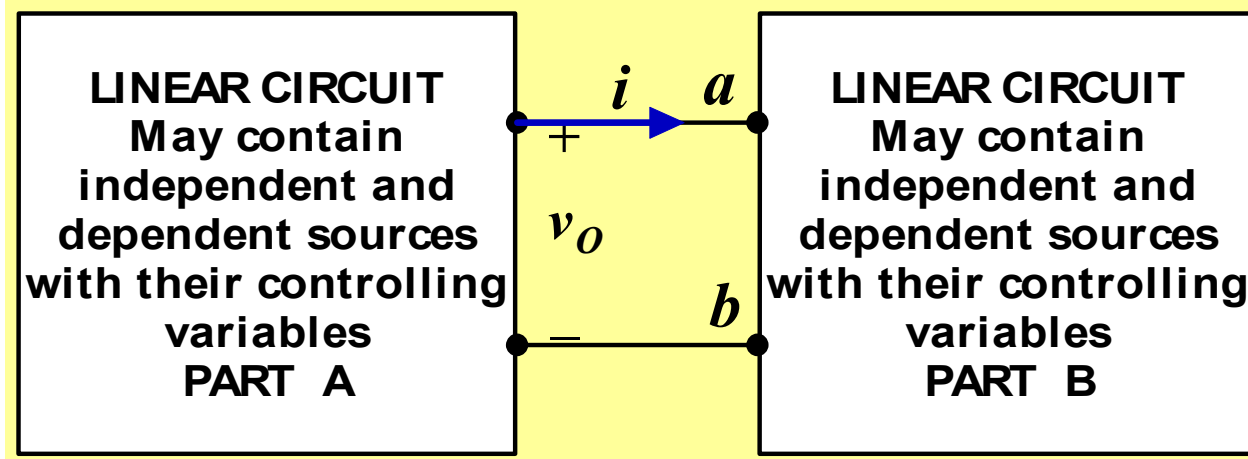


**Thevenin Equivalent Circuit for PART A**

$v_{TH}$  Thevenin Equivalent Source  
 $R_{TH}$  Thevenin Equivalent Resistance



# NORTON'S EQUIVALENCE THEOREM

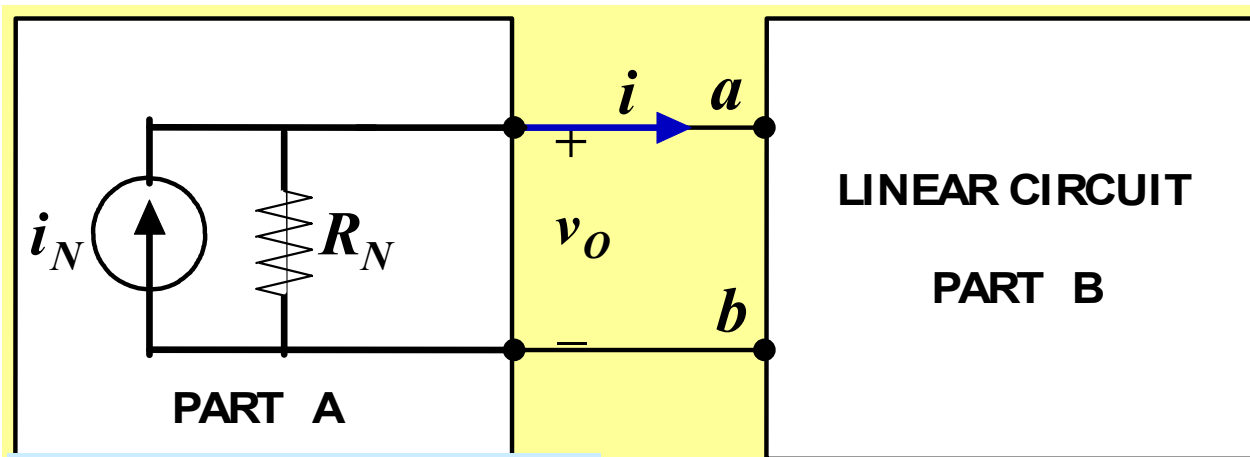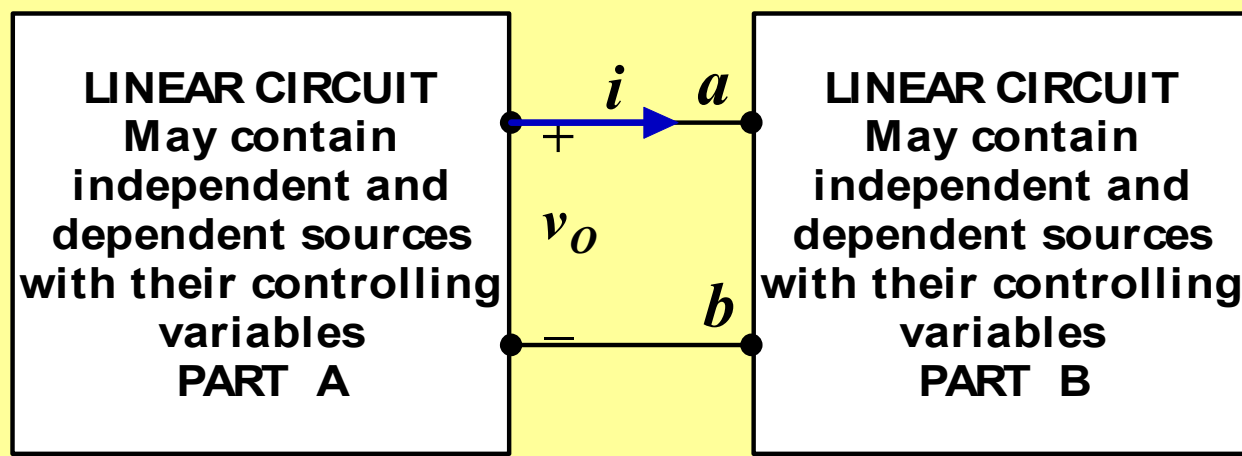


**Norton Equivalent Circuit  
for PART A**


$i_N$  Thevenin Equivalent Source  
 $R_N$  Thevenin Equivalent Resistance


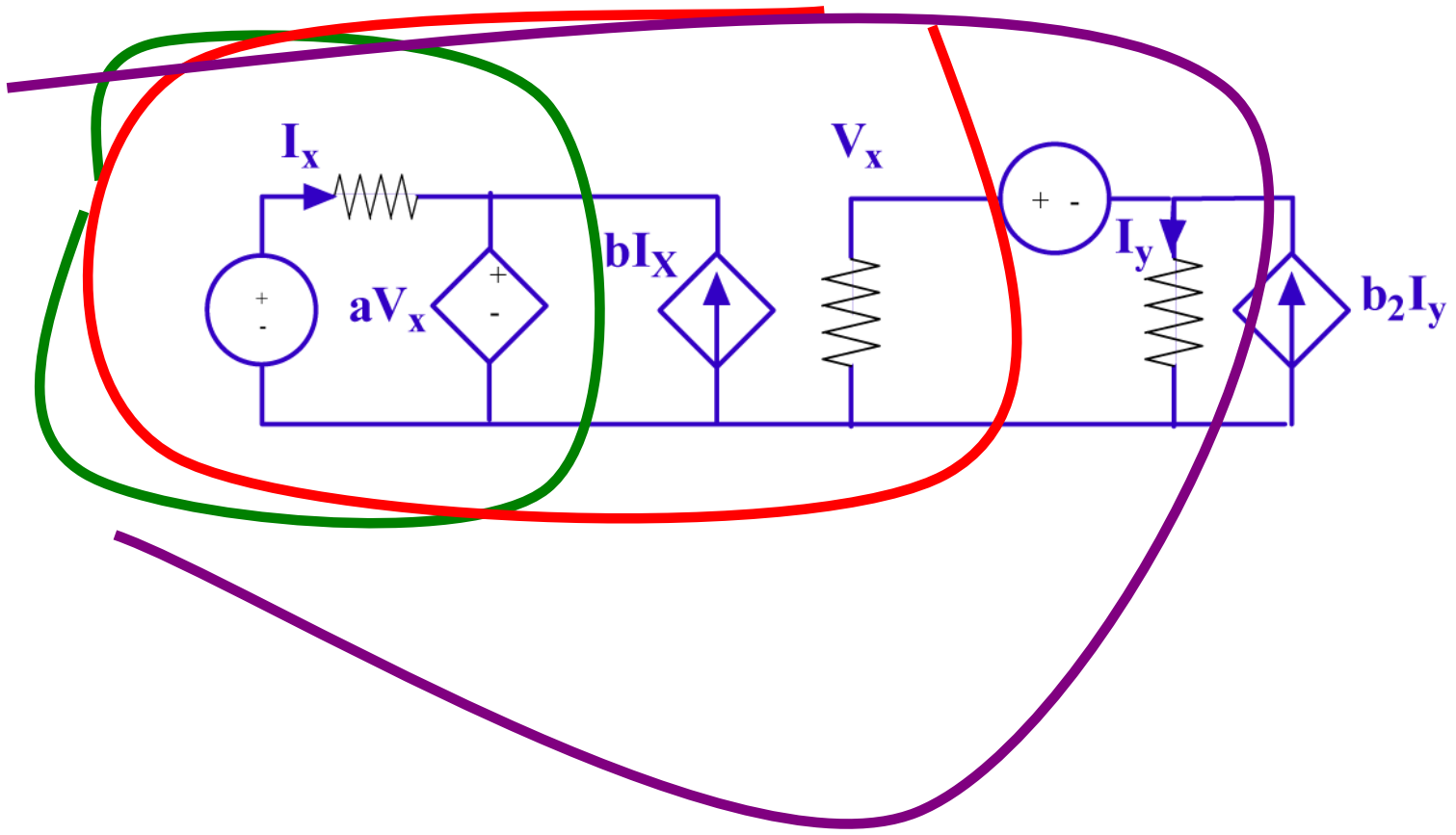
# Examples of Valid and Invalid Partitions




# OUTLINE OF PROOF - version 1

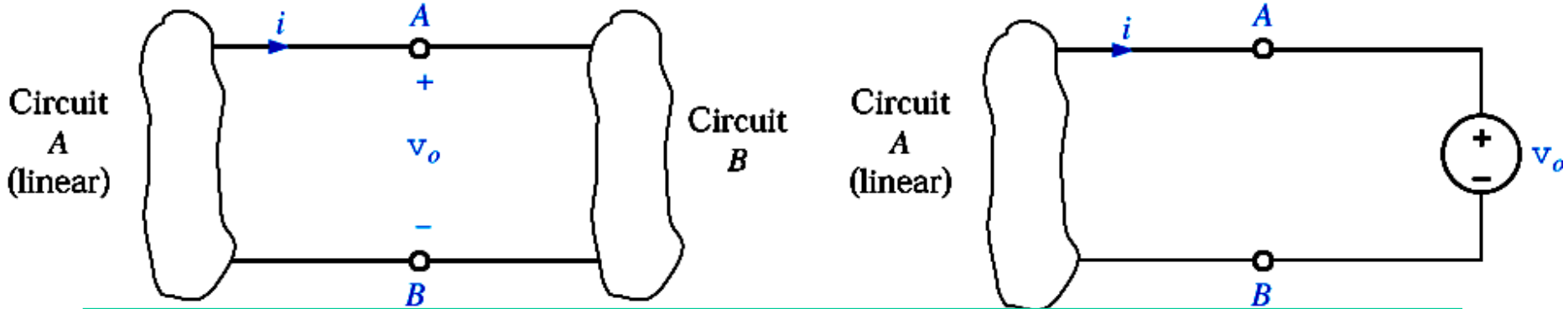

If Circuit A is unchanged then the current should be the same FOR ANY  $v_o$

## USE SOURCE SUPERPOSITION

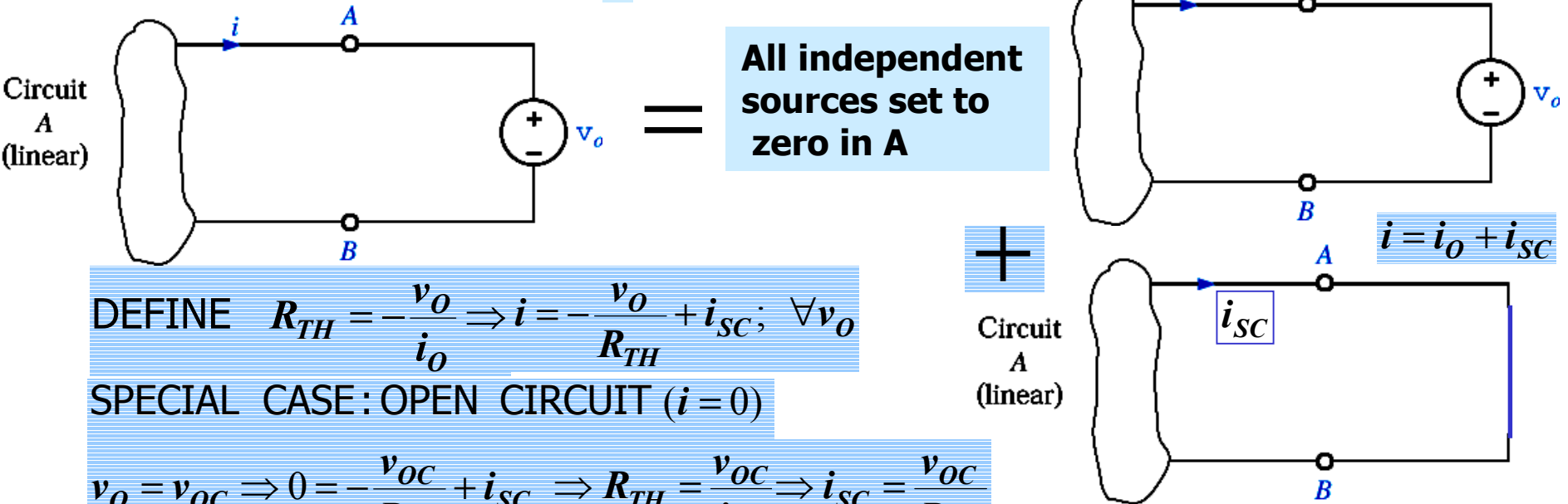

DEFINE  $R_{TH} = -\frac{v_o}{i_o} \Rightarrow i = -\frac{v_o}{R_{TH}} + i_{SC}; \forall v_o$

SPECIAL CASE: OPEN CIRCUIT ( $i = 0$ )


$v_o = v_{OC} \Rightarrow 0 = -\frac{v_{OC}}{R_{TH}} + i_{SC} \Rightarrow R_{TH} = \frac{v_{OC}}{i_{SC}} \Rightarrow i_{SC} = \frac{v_{OC}}{R_{TH}}$

$i = -\frac{v_o}{R_{TH}} + i_{SC} \Rightarrow v_o = v_{OC} - R_{TH}i$

HOW DO WE INTERPRET THIS RESULT?



# OUTLINE OF PROOF - version 2

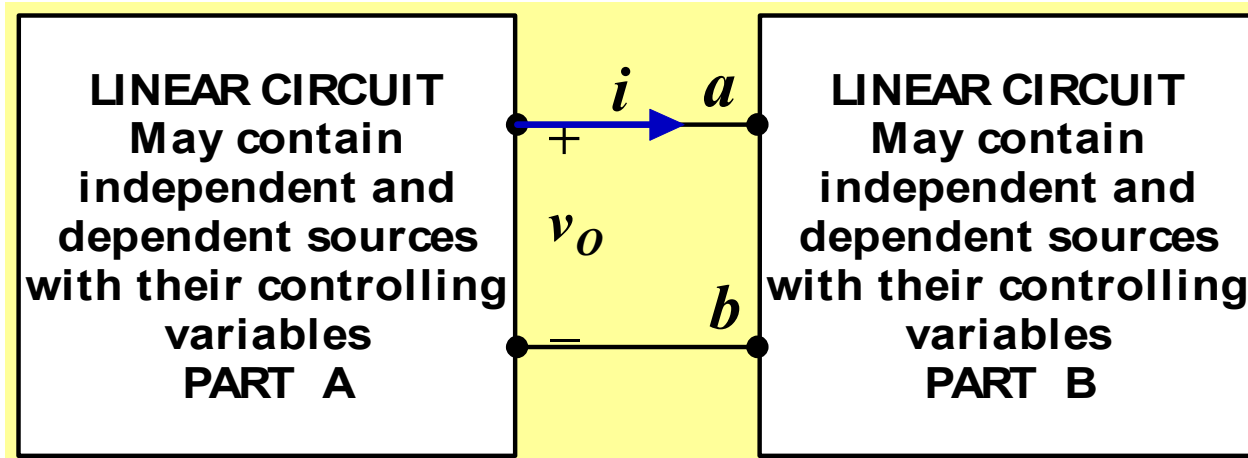

1. Because of the linearity of the models, for any Part B the relationship between  $v_o$  and the current,  $i$ , has to be of the form  $v_o = m * i + n$

2. Result must hold for "every valid Part B" that we can imagine

3. If part B is an open circuit then  $i=0$  and...  $n = v_{OC}$

4. If Part B is a short circuit then  $v_o$  is zero. In this case


$$0 = m * i_{SC} + v_{OC} \Rightarrow m = -\frac{v_{OC}}{i_{SC}} = -R_{TH}$$

$$v_o = -R_{TH} i + v_{OC}$$

How do we interpret this?




# THEVENIN APPROACH

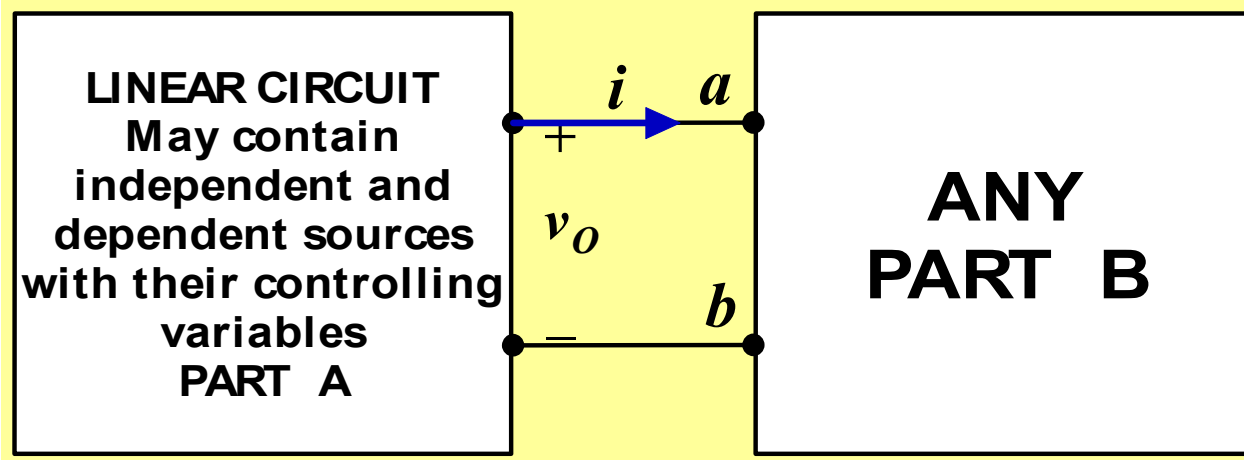

$$v_o = -R_{TH}i + v_{OC}$$

For ANY circuit in Part B

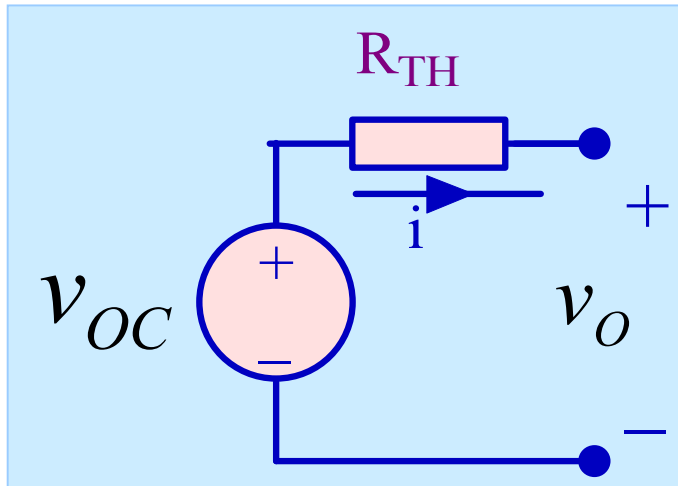

**PART A MUST BEHAVE LIKE THIS CIRCUIT**

This is the Thevenin equivalent circuit for the circuit in Part A

The voltage source is called the **THEVENIN EQUIVALENT SOURCE**

The resistance is called the **THEVENIN EQUIVALENT RESISTANCE**







# Norton Approach

$$v_o = v_{OC} - R_{TH}i \Rightarrow i = \frac{v_{OC}}{R_{TH}} - \frac{v_o}{R_{TH}}$$

$$\frac{v_{OC}}{R_{TH}} = i_{SC}$$

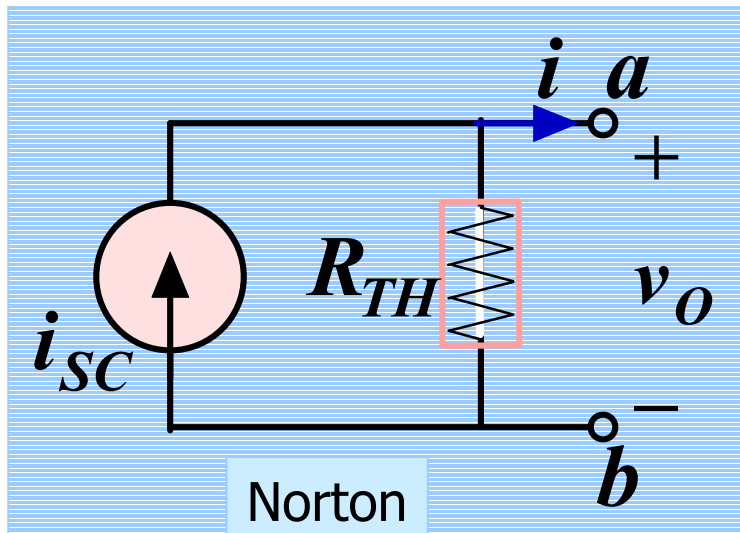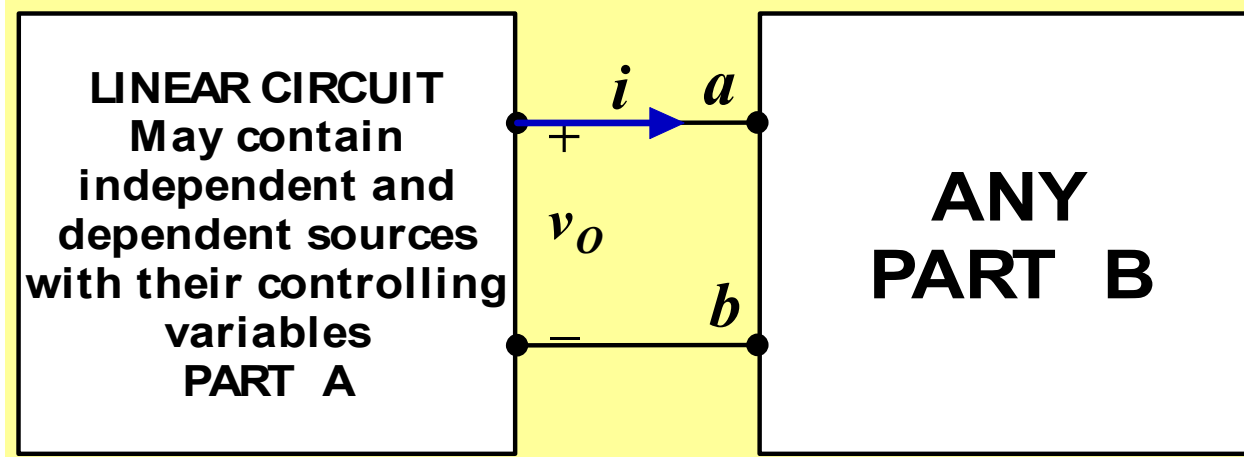


Norton Equivalent Representation for Part A


$i_{SC}$  Norton Equivalent Source


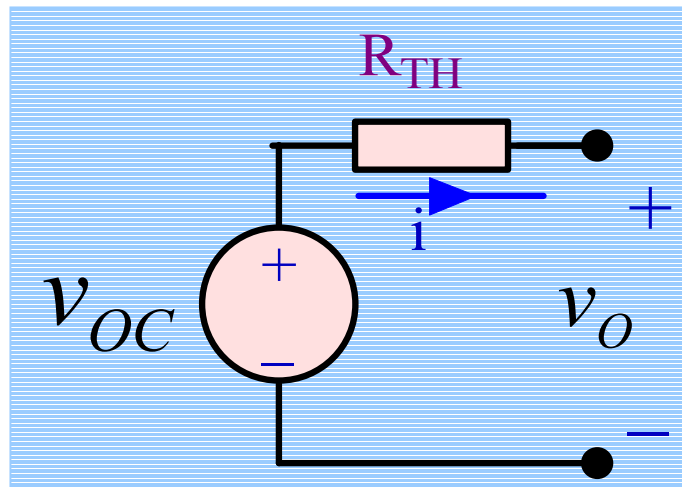
## ANOTHER VIEW OF THEVENIN'S AND NORTON'S THEOREMS



Thevenin

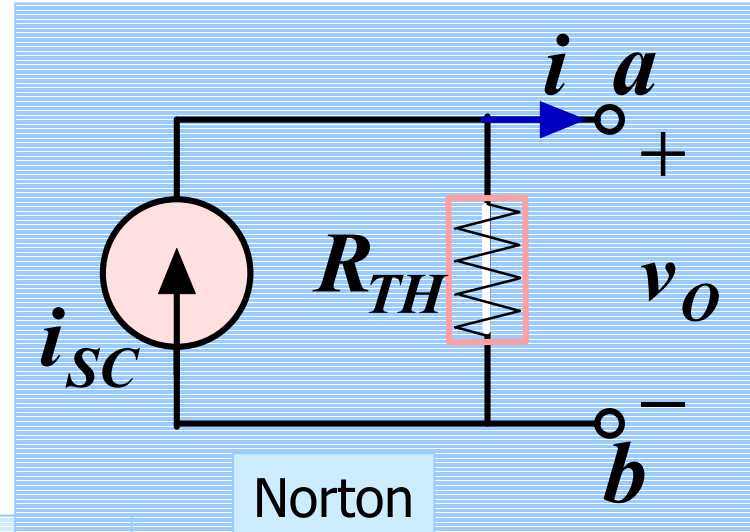

Norton

$$i_{SC} = \frac{v_{OC}}{R_{TH}}$$

This equivalence can be viewed as a source transformation problem. It shows how to convert a voltage source in series with a resistor into an equivalent current source in parallel with the resistor.


**SOURCE TRANSFORMATION CAN BE A GOOD TOOL TO REDUCE THE COMPLEXITY OF A CIRCUIT**

Source transformation is a good tool to reduce complexity in a circuit ...

WHEN IT CAN BE APPLIED!!

“ideal sources” are not good models for real behavior of sources

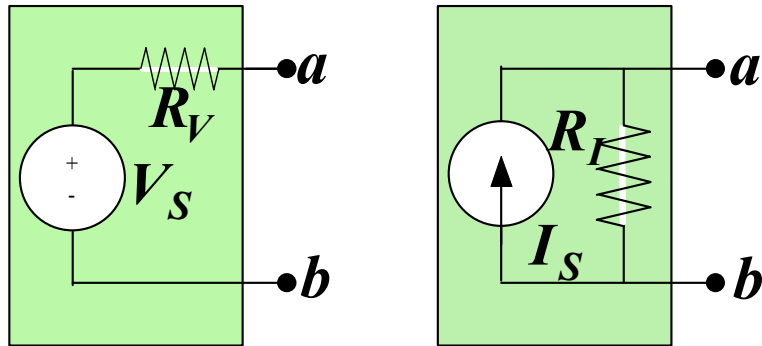A real battery does not produce infinite current when short-circuited



THE MODELS ARE EQUIVALENTS WHEN

$$R_V = R_I = R$$

$$V_S = R I_S$$

Improved model  
for voltage source


Improved model  
for current source

Source Transformation can be used to determine the Thevenin or Norton Equivalent...

BUT THERE MAY BE MORE EFFICIENT TECHNIQUES



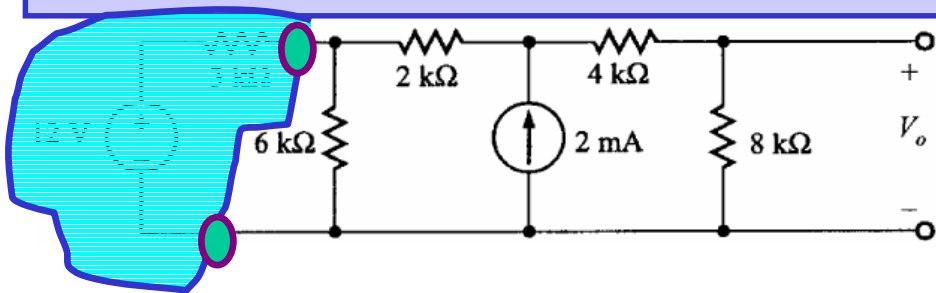
# EXAMPLE: SOLVE BY SOURCE TRANSFORMATION



In between the terminals we connect a current source and a resistance in parallel

The equivalent current source will have the value  $12V/3k$

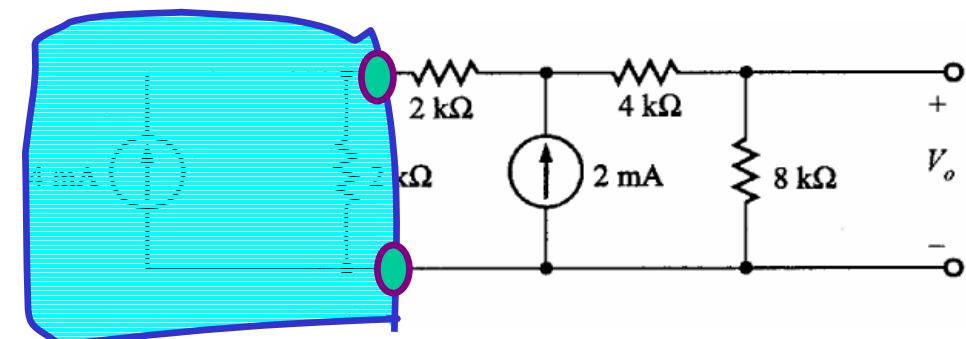
The 3k and the 6k resistors now are in parallel and can be combined



In between the terminals we connect a voltage source in series with the resistor

The equivalent source has value  $4mA * 2k$

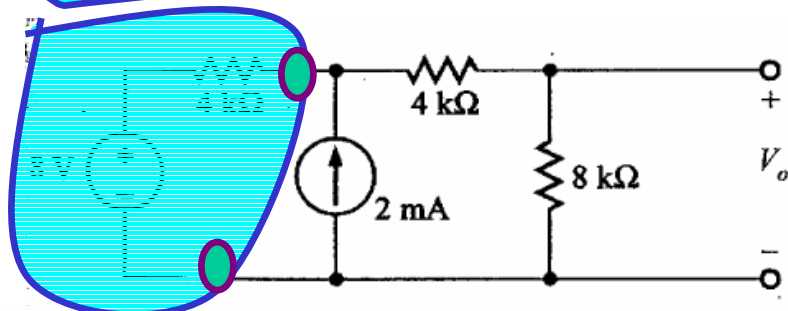The 2k and the 2k resistor become connected in series and can be combined




After the transformation the sources can be combined

The equivalent current source has value  $8V/4k$  and the combined current source has value 4mA


## Options at this point

1. Do another source transformation and get a single loop circuit



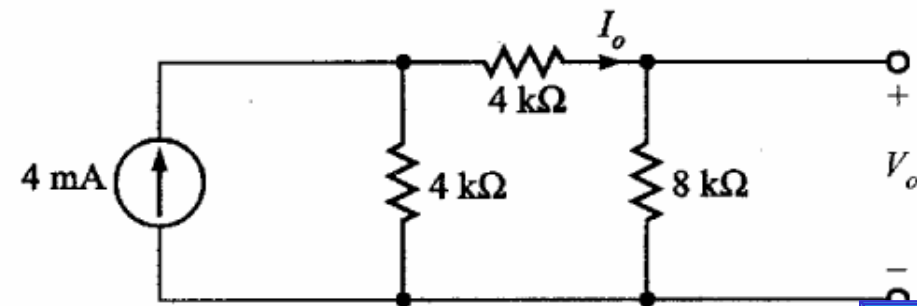
2. Use current divider to compute  $I_o$  and then compute  $V_o$  using Ohm's law



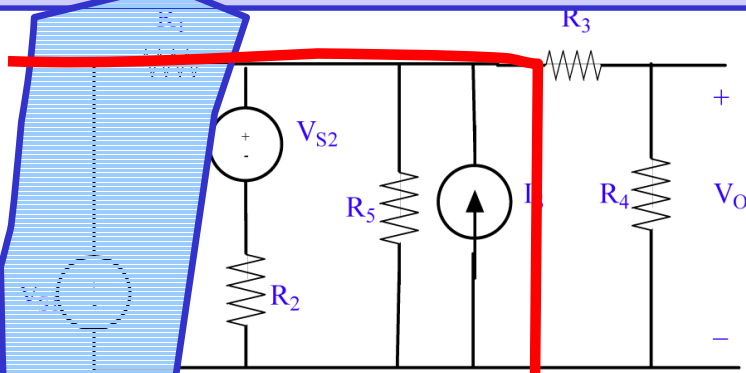
**PROBLEM Compute  $V_0$  using source transformation**



**EQUIVALENT CIRCUITS**

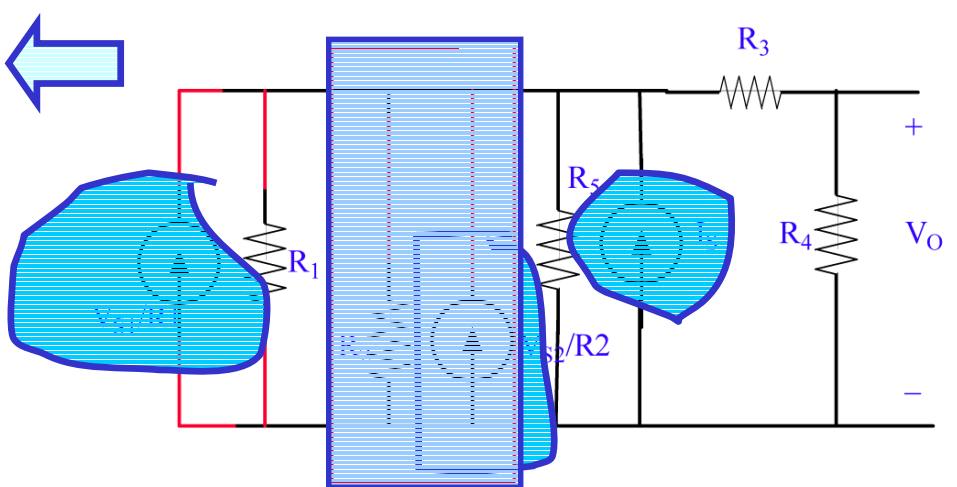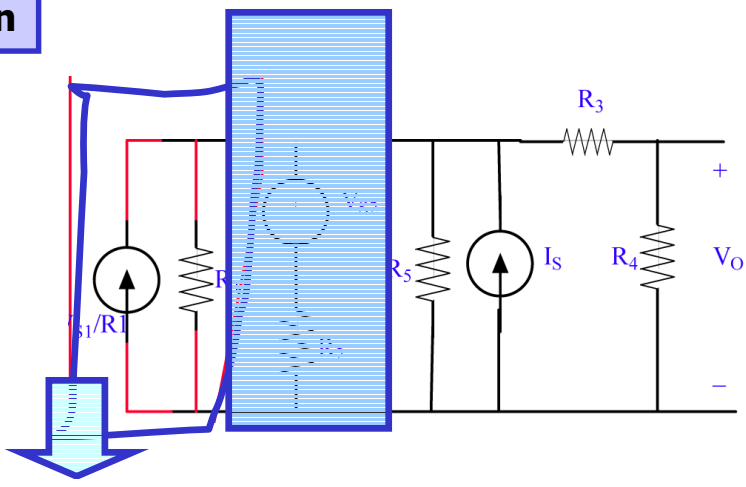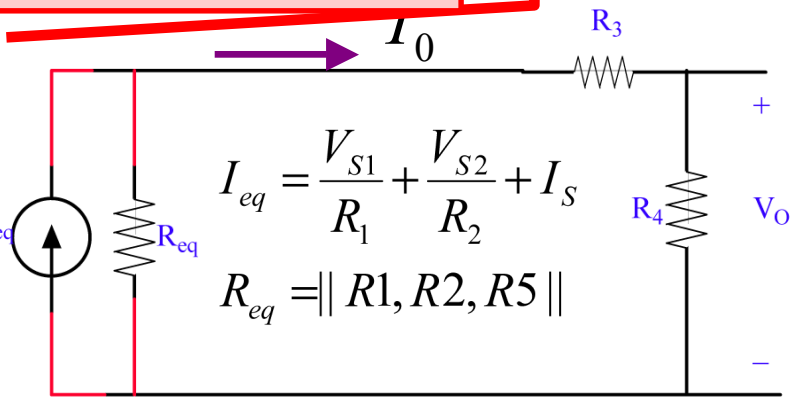

**Or one more source transformation**

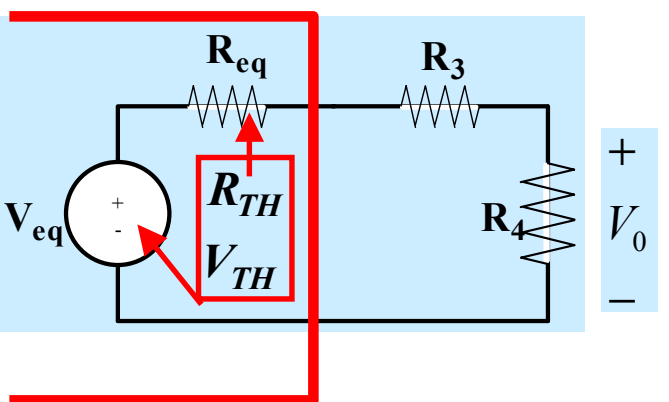


**3 current sources in parallel and three resistors in parallel**

$$V_{eq} = R_{eq} I_{eq}$$


$$V_0 = \frac{R_4}{R_4 + R_3 + R_{eq}} V_{eq}$$



## RECAP OF SOURCE TRANSFORMATION

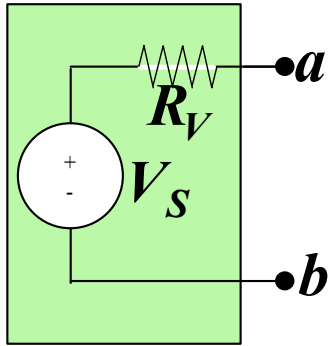

Improved model  
for voltage source

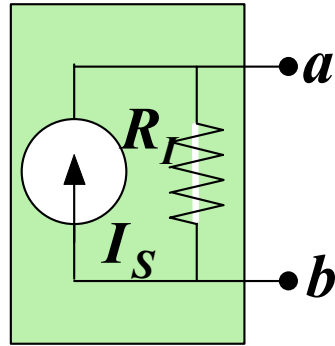

Improved model  
for current source

THE MODELS ARE EQUIVALENTS WHEN  
 $R_V = R_I = R$   
 $V_S = R I_S$

Source Transformation can be used to determine the Thevenin or Norton Equivalent...

WE NOW REVIEW SEVERAL EFFICIENT APPROACHES  
TO DETERMINE THEVENIN OR NORTON EQUIVALENT  
CIRCUITS



# A General Procedure to Determine the Thevenin Equivalent

$v_{TH}$  Open Circuit voltage  
voltage at a - b if Part B is removed


$i_{SC}$  Short Circuit Current  
current through a - b if Part B is replaced  
by a short circuit

$R_{TH} = \frac{v_{TH}}{i_{SC}}$  Thevenin Equivalent Resistance

1. Determine the  
Thevenin equivalent  
source

Remove part B and  
compute the OPEN  
CIRCUIT voltage  $V_{ab}$


One circuit problem

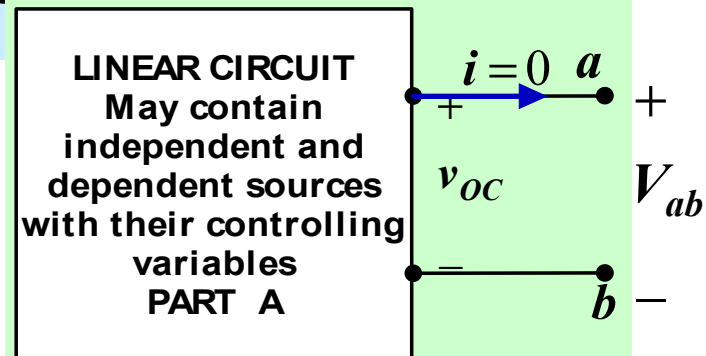

2. Determine the  
SHORT CIRCUIT  
current

Remove part B and  
compute the SHORT  
CIRCUIT current  $I_{ab}$


Second circuit problem

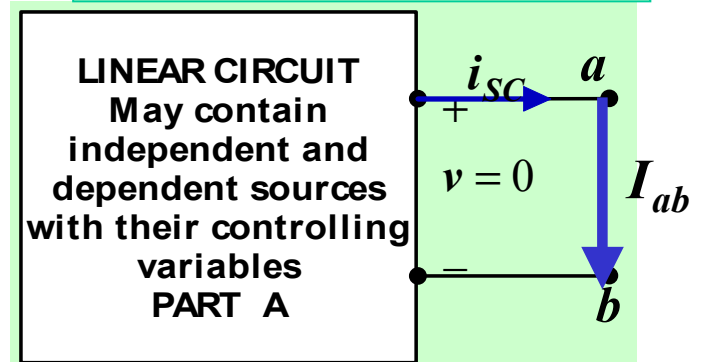

$$v_{TH} = v_{OC}, R_{TH} = \frac{v_{OC}}{i_{SC}}$$


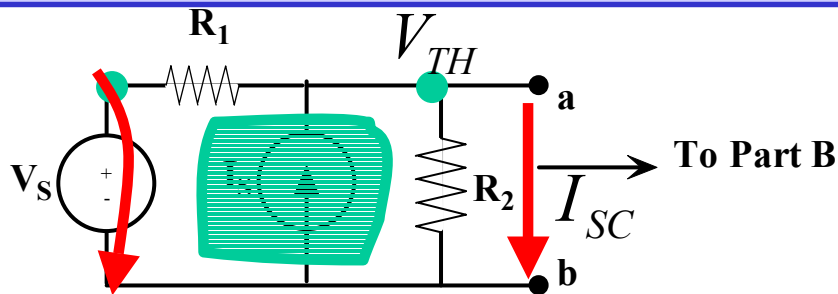
# AN EXAMPLE OF DETERMINING THE THEVENIN EQUIVALENT



Part B is irrelevant.

The voltage  $V_{ab}$  will be the value of the Thevenin equivalent source.

What is an efficient technique to compute the open circuit voltage?

Now for the short circuit current  
Let's try source superposition

When the current source is open the current through the short circuit is

$$I_{SC}^1 = \frac{V_S}{R_1}$$

**NODE ANALYSIS**

$$\frac{V_{TH}}{R_2} + \frac{V_{TH} - V_S}{R_1} - I_S = 0$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2}\right)V_{TH} = \frac{V_S}{R_1} + I_S$$

$$V_{TH} = \frac{R_2}{R_1 + R_2}V_S + \frac{R_1 R_2}{R_1 + R_2}I_S$$

$$V_{TH} = \frac{R_1 R_2}{R_1 + R_2} \left( \frac{V_S}{R_1} + I_S \right)$$

When the voltage source is set to zero, the current through the short circuit is

$$I_{SC}^2 = I_S$$

$$I_{SC} = I_S + \frac{V_S}{R_1}$$

To compute the Thevenin resistance we use

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_{TH} = \frac{V_{TH}}{I_{SC}}$$

For this case the Thevenin resistance can be computed as the resistance from a - b when all independent sources have been set to zero

Is this a general result?








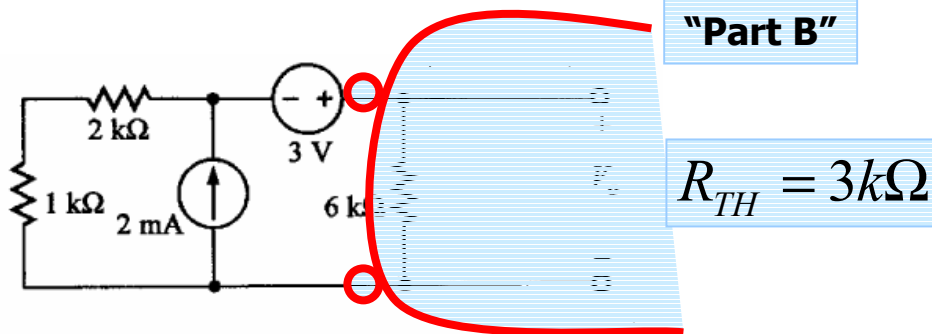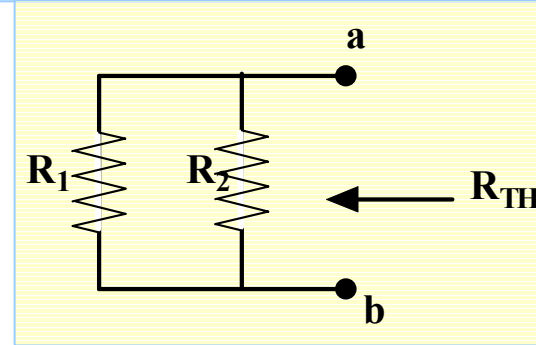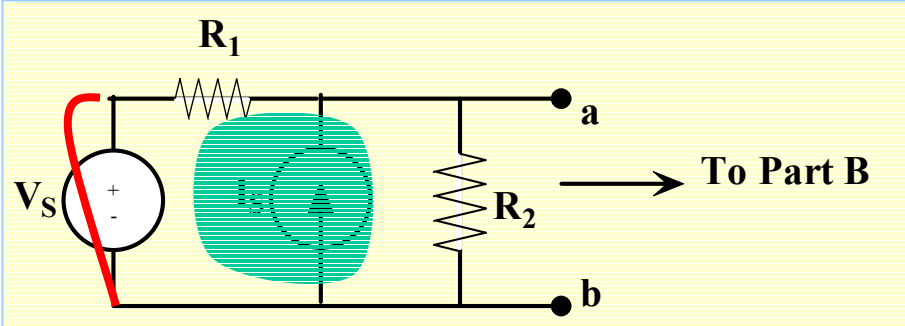
# Determining the Thevenin Equivalent in Circuits with Only INDEPENDENT SOURCES

The Thevenin Equivalent Source is computed as the open loop voltage

The Thevenin Equivalent Resistance **CAN BE COMPUTED** by setting to zero all the sources and then determining the resistance seen from the terminals where the equivalent will be placed







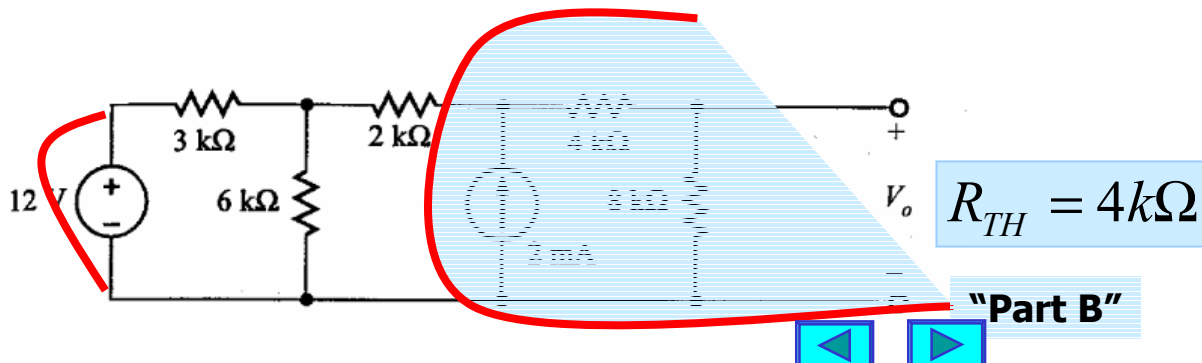Since the evaluation of the Thevenin equivalent can be very simple, we can add it to our toolkit for the solution of circuits!!



Find  $V_o$  in the following network using Thévenin's theorem.

LEARNING BY DOING

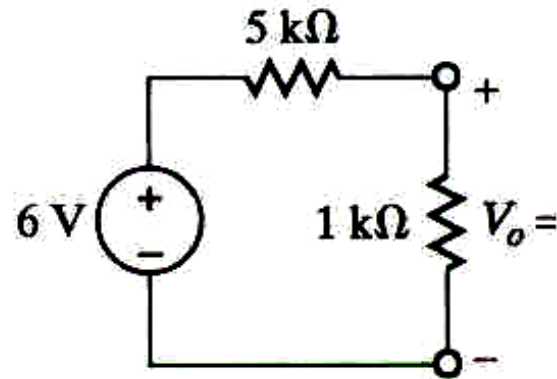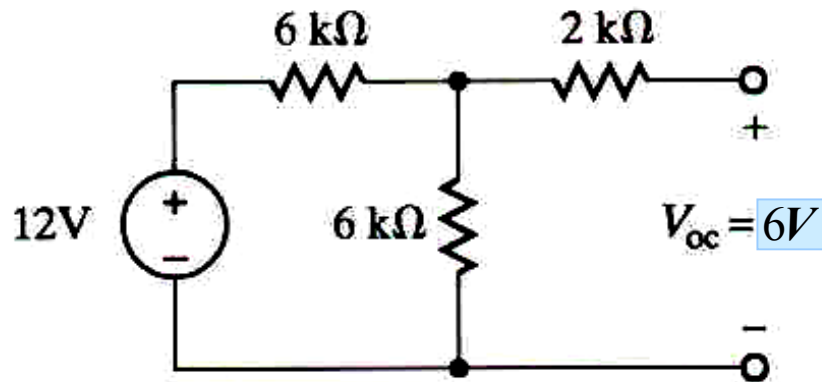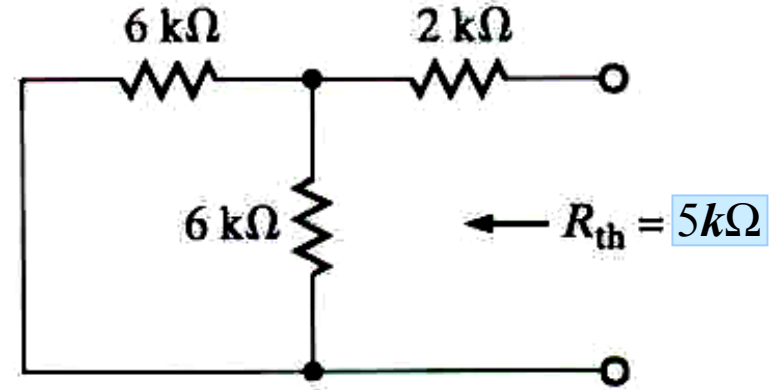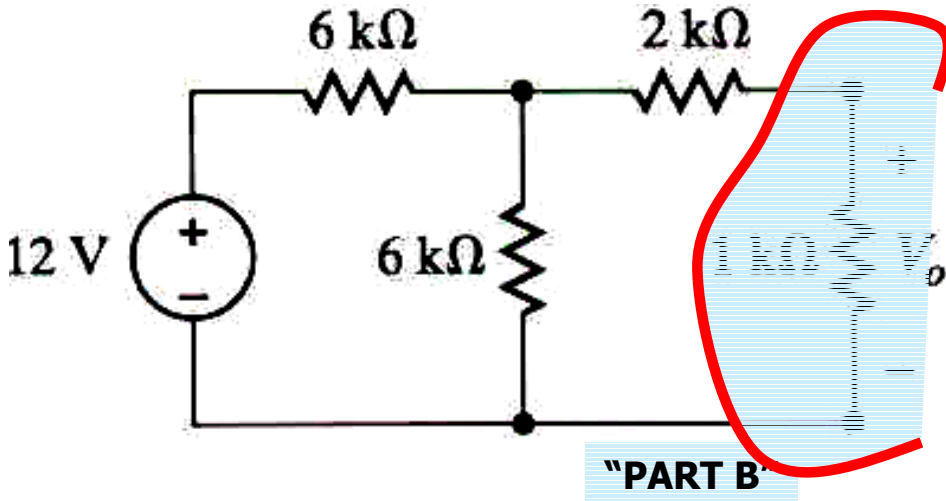


$$V_o = \frac{1k}{1k + 5k} (6V) = 1[V]$$



# LEARNING EXAMPLE

# COMPUTE $V_o$ USING THEVENIN

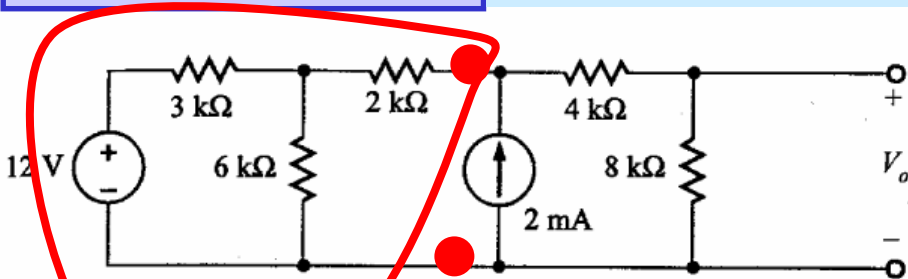

In the region shown, one could use source transformation twice and reduce that part to a single source with a resistor.

... Or we can apply Thevenin Equivalence to that part (viewed as "Part A")

$$R_{TH} = 4k\Omega$$

For the open loop voltage the part outside the region is eliminated

$$V_{TH} = \frac{6}{3+6} 12[V] = 8[V]$$


The original circuit becomes...

And one can apply Thevenin one more time!


For open loop voltage use KVL

$$R_{TH}^1 = 4k\Omega$$

$$V_{TH}^1 = 4k * 2mA + 8V = 16V$$

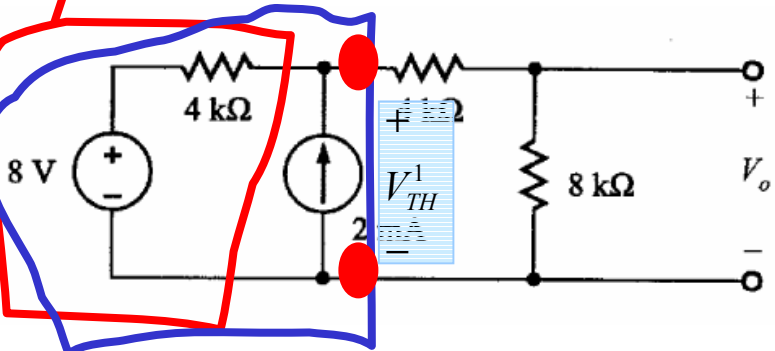

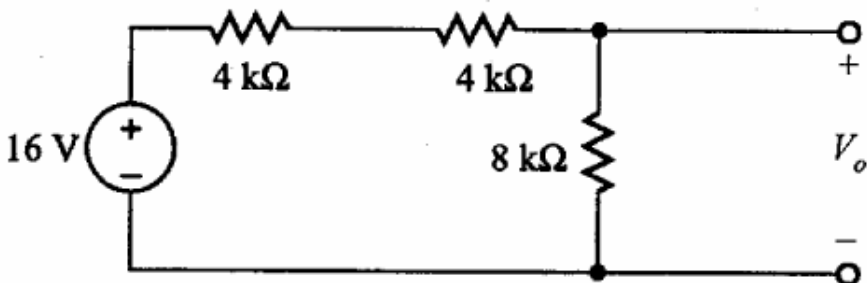
...and we have a simple voltage divider!!



$$V_o = \frac{8}{8+8} 16[V] = 8V$$



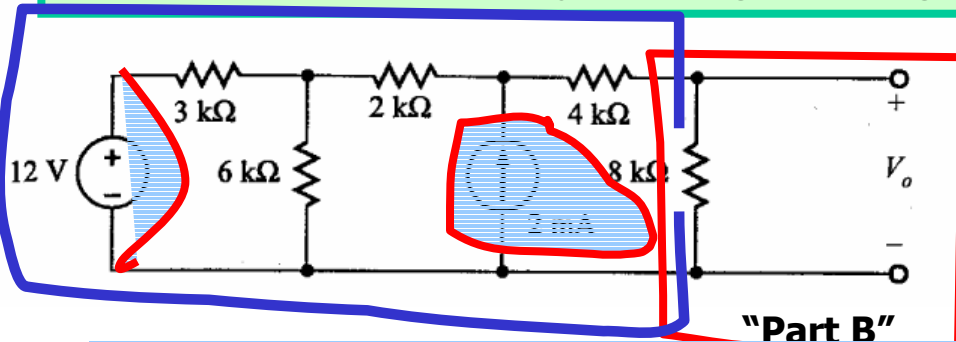
Or we can use Thevenin only once to get a voltage divider




"Part B"

For the Thevenin voltage we have to analyze the following circuit

METHOD??

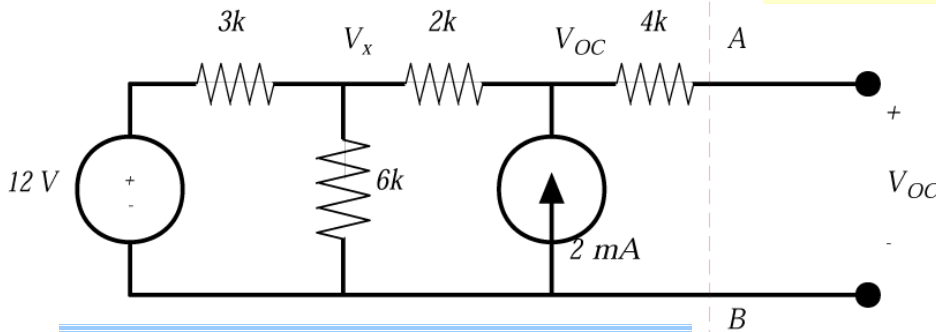


Thevenin Equivalent of "Part A"

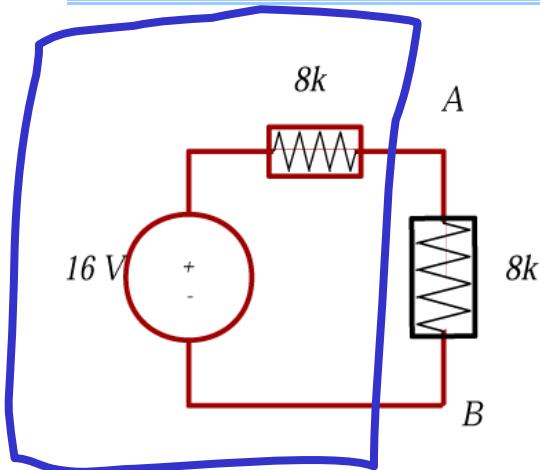

Simple Voltage Divider

For the Thevenin resistance

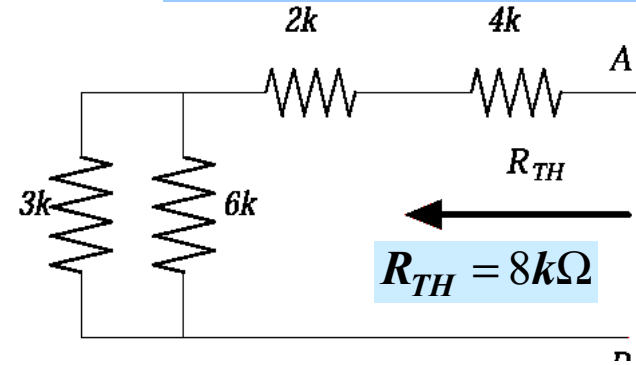

Source superposition, for example

Contribution of the voltage source


$$V_{OC}^1 = \frac{6}{3+6} 12V = 8V$$

Contribution of the current source

$$V_{OC}^2 = (2k + 2k) * (2mA) = 8V$$

# LEARNING EXAMPLE


# USE THEVENIN TO COMPUTE $V_o$

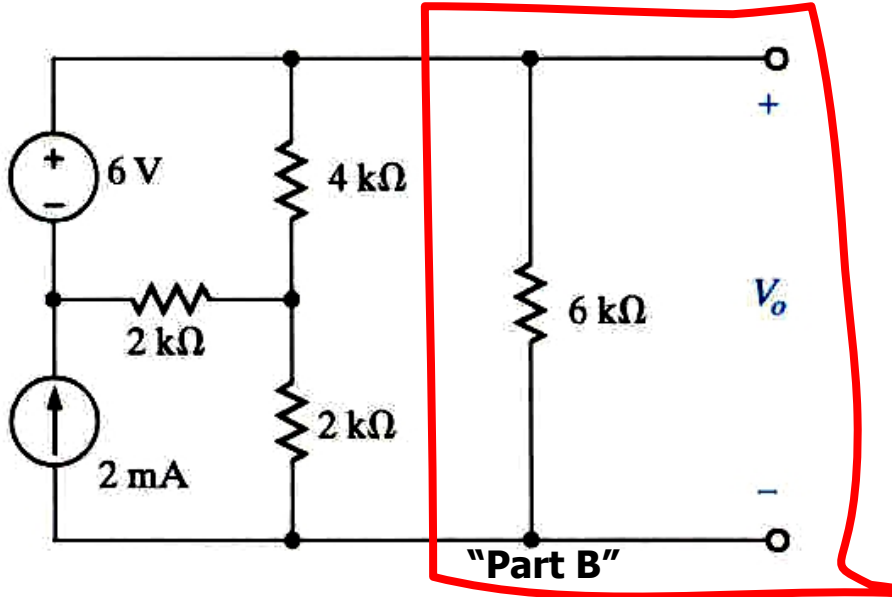

You have the choice on the way to partition the circuit.

Make "Part A" as simple as possible

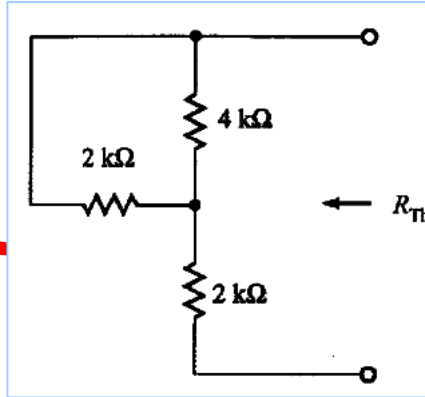
Since there are only independent sources, for the Thevenin resistance we set to zero all sources and determine the equivalent resistance



$$R_{TH} = 2 + (2 || 4) [k\Omega]$$

$$R_{TH} = \frac{10}{3} k\Omega$$

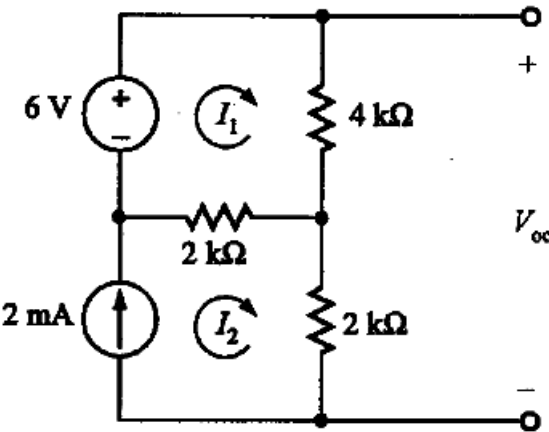For the open circuit voltage we analyze the following circuit ("Part A") ...



*Loop Analysis*


$$I_2 = 2mA$$

$$-6V + 4kI_1 + 2k(I_1 - I_2) = 0$$



$$I_1 = \frac{6 + 2I_2}{6} mA = \frac{5}{3} mA$$

$$V_{OC} = 4k * I_1 + 2k * I_2 = 20/3 + 4V = 32/3 [V]$$

The circuit becomes...

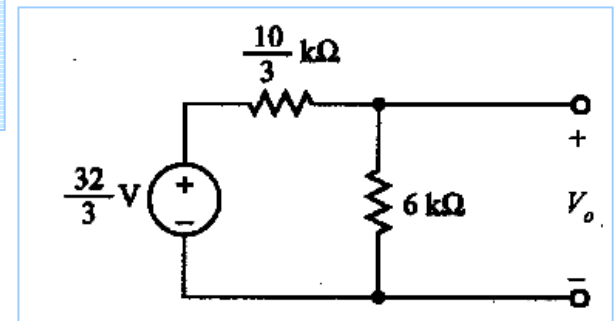


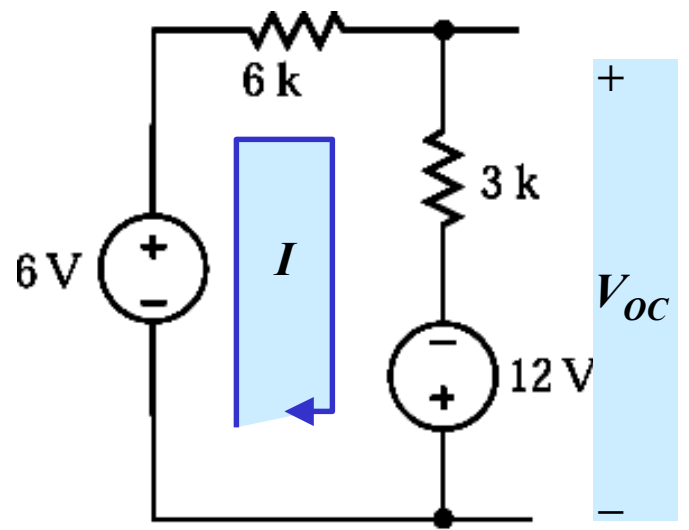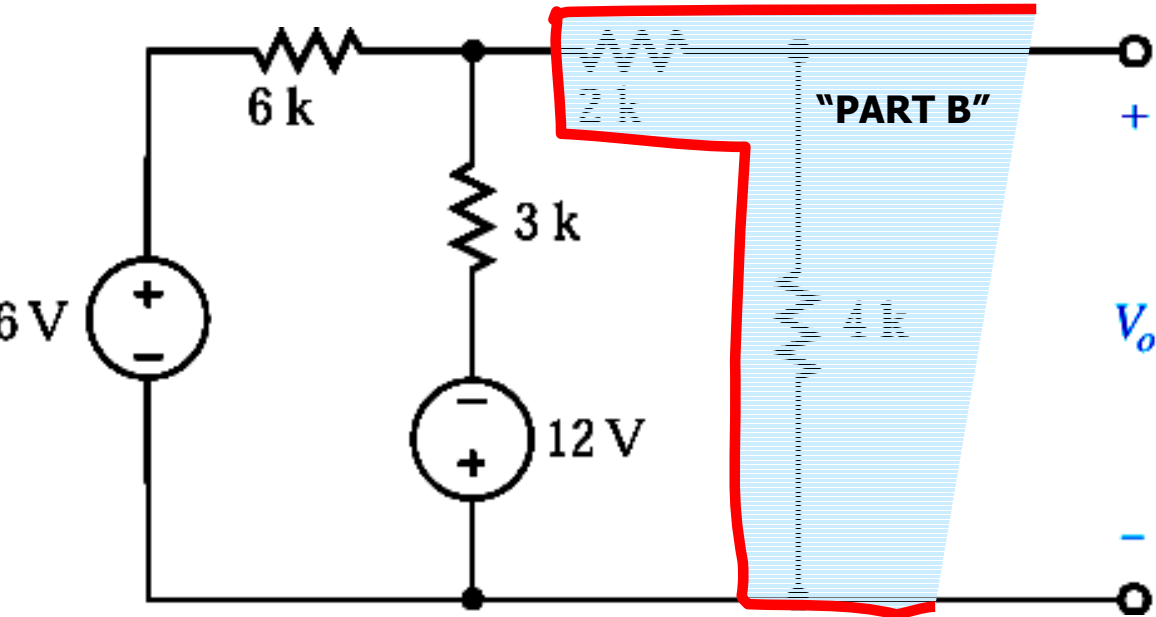**LEARNING EXTENSION: USE THEVENIN TO COMPUTE  $V_o$**




$9kI = 18[V] \Rightarrow I = 2mA$

$V_{OC} = 3kI - 12 = -6[V]$

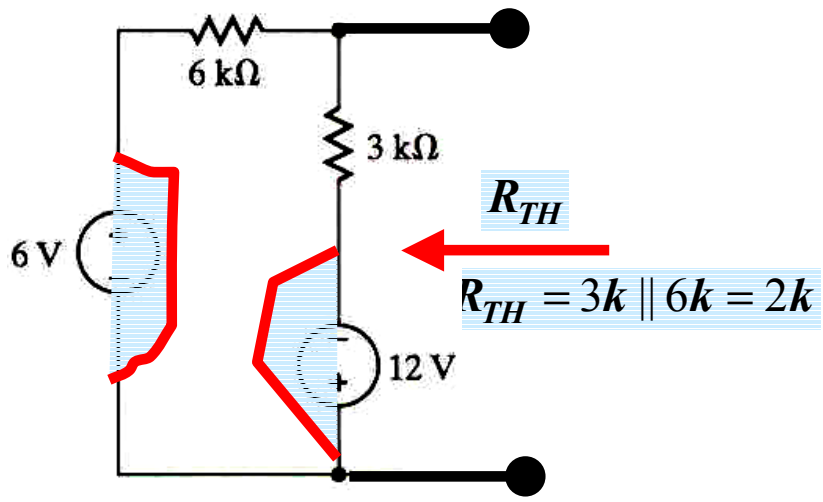


**RESULTING EQUIVALENT CIRCUIT**

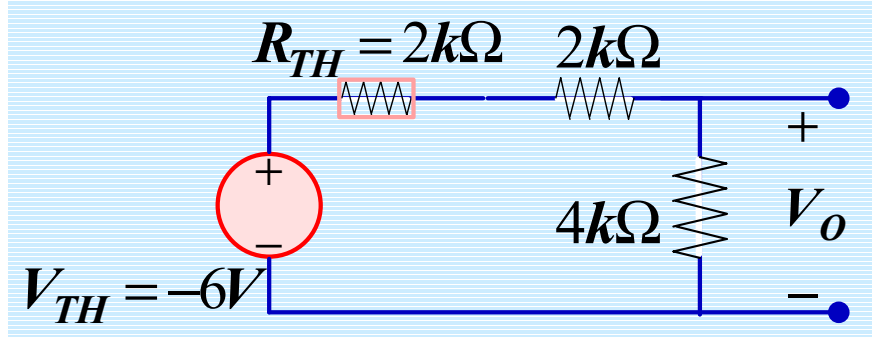

$V_o = \frac{4}{4+4}(-6V) = -3[V]$



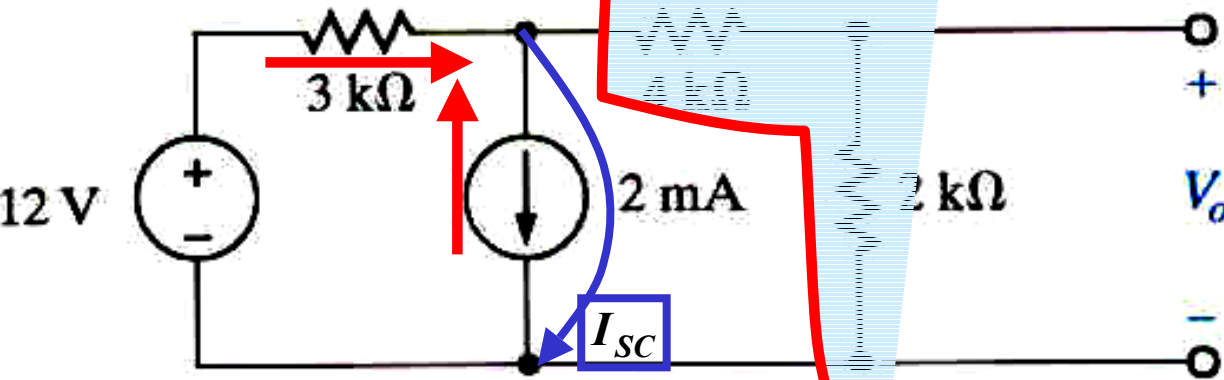
# LEARNING EXTENSION: COMPUTE $V_o$ USING NORTON



$$R_N = R_{TH} = 3k\Omega$$

$$I_{SC} = I_N = \frac{12V}{3k} - 2mA = 2mA$$


PART B

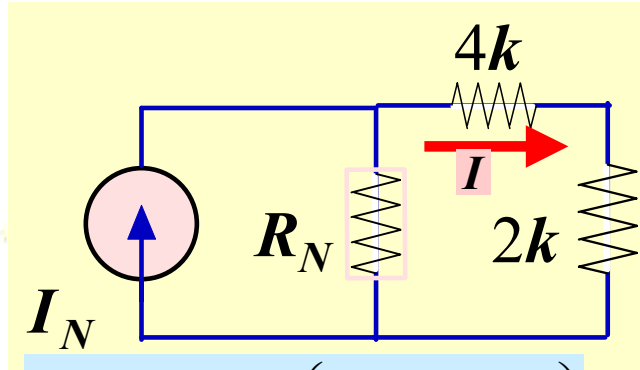

$$V_o = 2kI = 2k \left( \frac{R_N}{R_N + 6k} I_N \right)$$


$$V_o = 2 \frac{3}{9} (2) = \frac{4}{3} [V]$$

# COMPUTE $V_o$ USING THEVENIN PART B

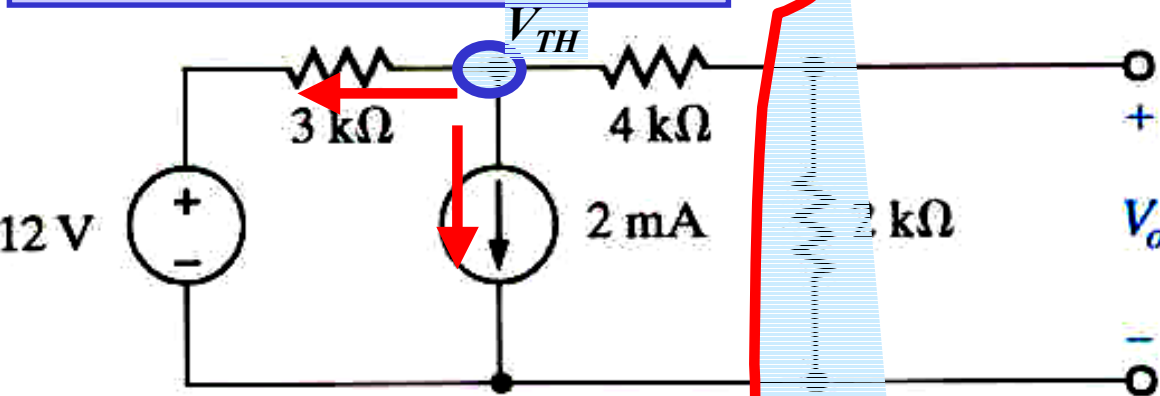

$$\frac{V_{TH} - 12}{3k} + 2mA = 0$$

$$R_{TH} = 3k + 4k$$


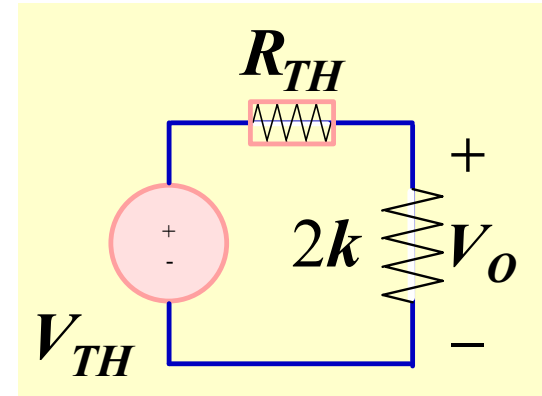


$$V_o = \frac{2}{2+7} (6V) = \frac{4}{3} [V]$$




# SAMPLE PROBLEM

FIND THE THEVENIN EQUIVALENT AT a - b

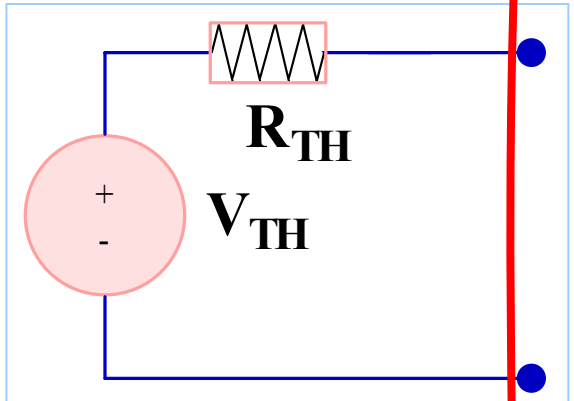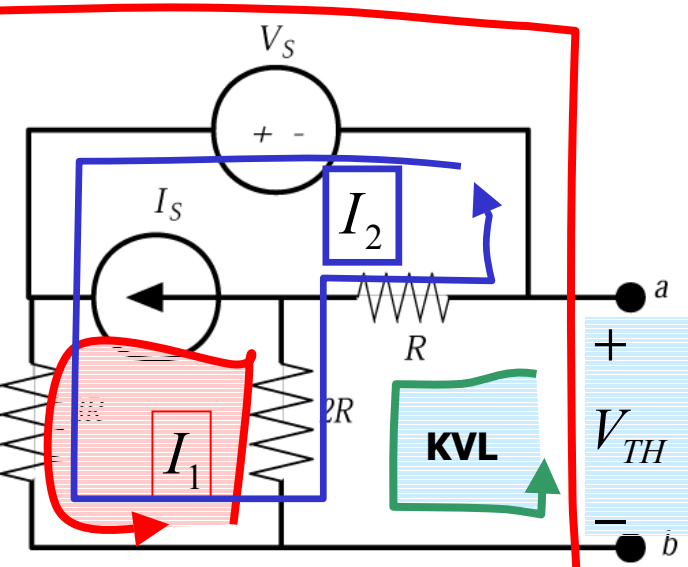

This is what we need to get
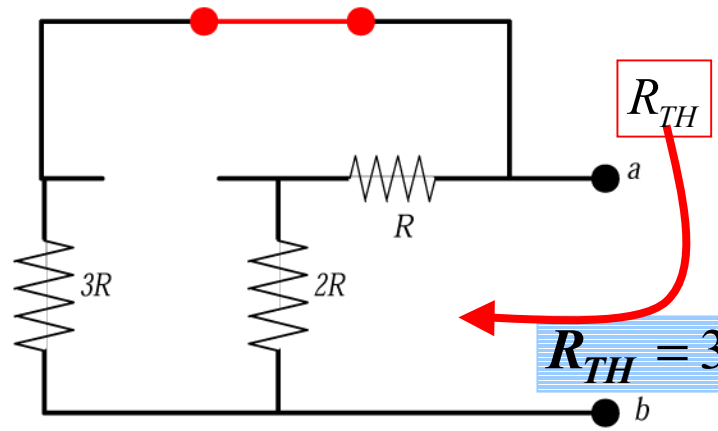
## Equivalent Resistance: Independent sources only



$$R_{TH} = 3R \parallel 3R = 1.5R$$

## Equivalent Voltage: Node, loop, superposition... Do loops

$$I_1 = I_S \quad -V_S + 5R(I_1 + I_2) + RI_2 = 0$$


$$V_{TH} = -RI_2 - 2R(I_1 + I_2)$$

## How about source superposition?

Opening the current source:

$$V_{TH}^1 = -\frac{V_S}{2}$$

Short circuiting the voltage source

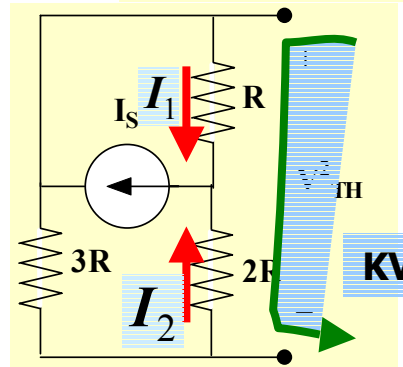


$$I_1 = \frac{5}{6}I_S \quad I_2 = \frac{1}{6}I_S$$

$$V_{TH}^2 = RI_1 - 2RI_2 = \frac{1}{2}RI_S$$

$$V_{TH} = V_{TH}^1 + V_{TH}^2$$




# SAMPLE PROBLEM

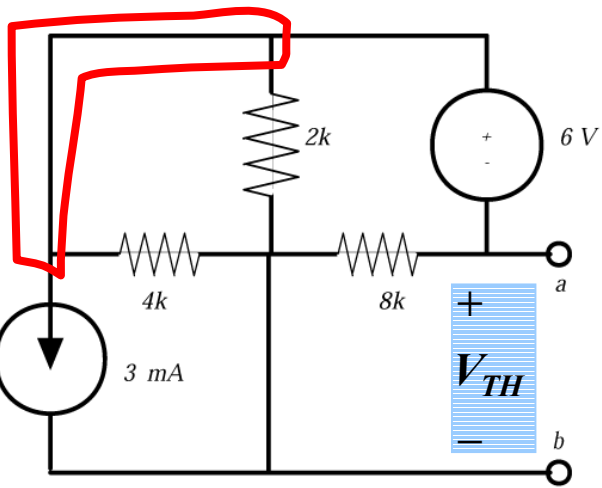

FIND THE THEVENIN EQUIVALENT CIRCUIT FROM TERMINALS a - b  
SHOW ALL YOUR WORK


## All independent sources

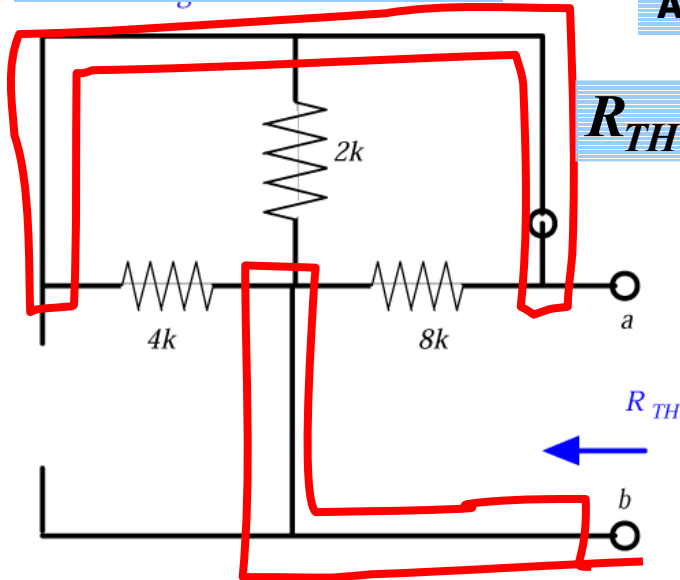


All resistors are in parallel!!  
 $R_{TH} = || 2k, 4k, 8k || = 8/7k$

## The circuit can be simplified
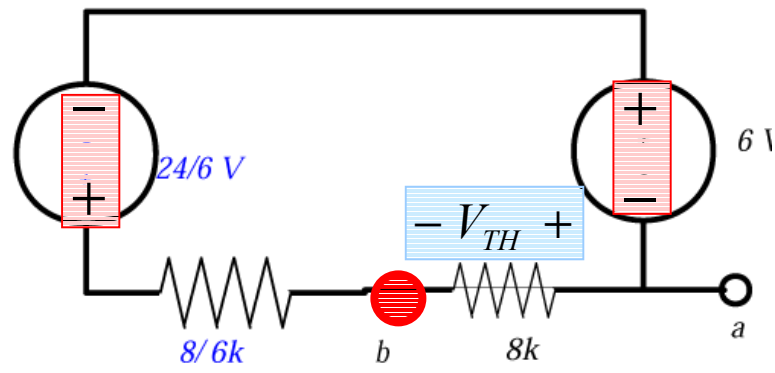
### ... An to compute Equivalent Source...



### SOURCE TRANSFORMATION

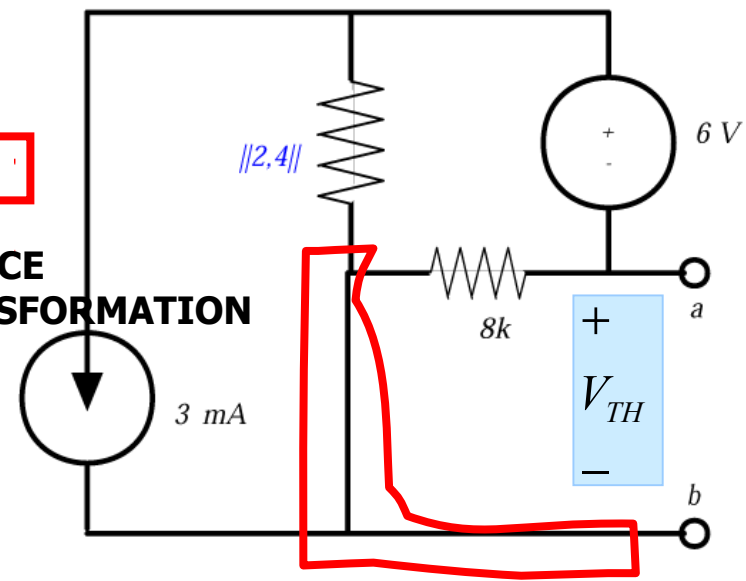


### Voltage divider

$$V_{TH} = - \frac{8k}{8k + (8/6)k} (6 + 24/6) [V]$$


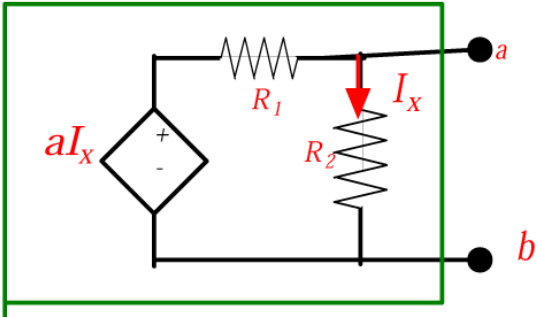
# THEVENIN EQUIVALENT FOR CIRCUITS WITH ONLY DEPENDENT SOURCES



$$-aI_x + (R_1 + R_2)I_x = 0$$

$$(-a + R_1 + R_2)I_x = 0$$

$$-a + R_1 + R_2 \neq 0 \Rightarrow I_x = 0$$


**A circuit with only dependent sources cannot self start.**

**(actually that statement has to be qualified a bit. What happens if  $a = R_1 + R_2$ ?)**

**FOR ANY PROPERLY DESIGNED CIRCUIT WITH ONLY DEPENDENT SOURCES  $V_{OC} = 0, I_{SC} = 0$**

**This is a big simplification!!**

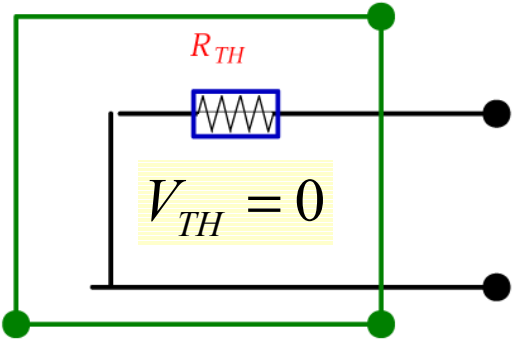**But we need a special approach for the computation of the Thevenin equivalent resistance**



**Since the circuit cannot self start we need to probe it with an external source**


**The source can be either a voltage source or a current source and its value can be chosen arbitrarily!**

**Which one to choose is often determined by the simplicity of the resulting circuit**



**IF WE CHOOSE A VOLTAGE PROBE...**

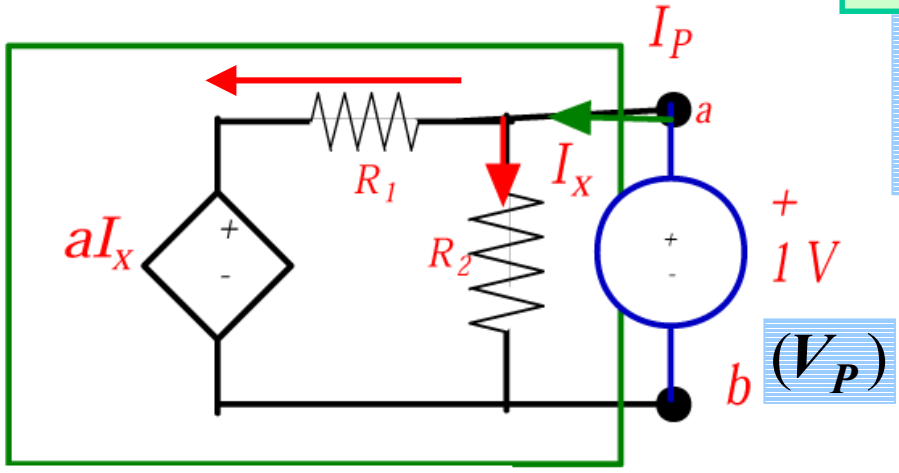
**WE MUST COMPUTE CURRENT SUPPLIED BY PROBE SOURCE**



$$I_P = I_X + \frac{V_P - aI_X}{R_1}$$

$$I_X = \frac{V_P}{R_2}$$
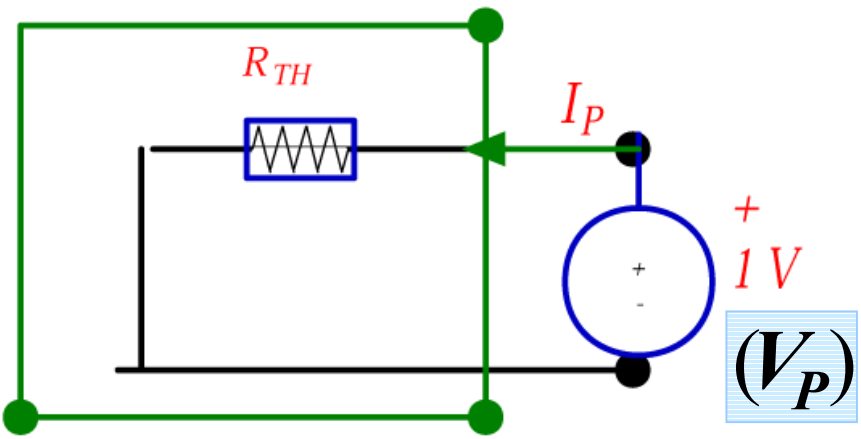
$$I_P = \left( \frac{1}{R_2} + \frac{1}{R_1} - \frac{a}{R_1 R_2} \right) V_P$$



$$R_{TH} = \frac{V_P}{I_P}$$


$$R_{TH} = \frac{V_P}{\left( \frac{1}{R_2} + \frac{1}{R_1} - \frac{a}{R_1 R_2} \right) V_P}$$

**The value chosen for the probe voltage is irrelevant. Oftentimes we simply set it to one**



# IF WE CHOOSE A CURRENT SOURCE PROBE

We must compute the node voltage  $V_p$


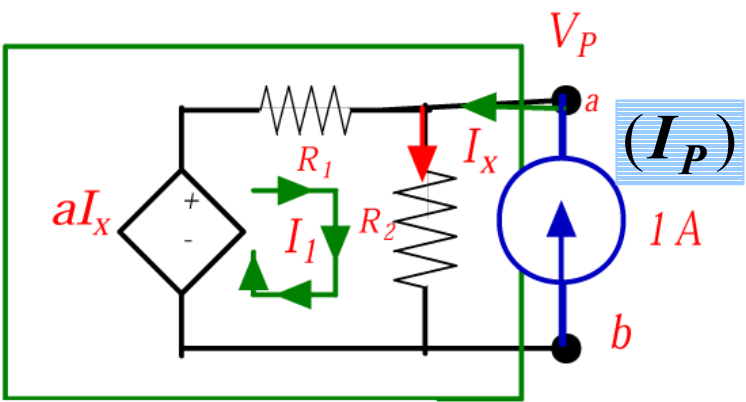


**KCL**

$$\frac{V_P}{R_2} + \frac{V_P - aI_X}{R_1} - I_P = 0$$

$$I_X = \frac{V_P}{R_2}$$
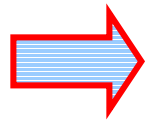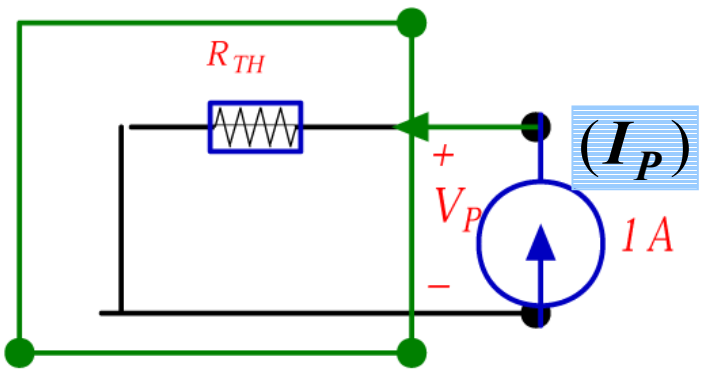
$$\left( \frac{1}{R_2} + \frac{1}{R_1} - \frac{a}{R_1 R_2} \right) V_P = I_P$$




$$R_{TH} = \frac{V_P}{I_P}$$

The value of the probe current is irrelevant. For simplicity it is often chosen as one.



**LEARNING EXAMPLE**

**FIND THE THEVENIN EQUIVALENT**

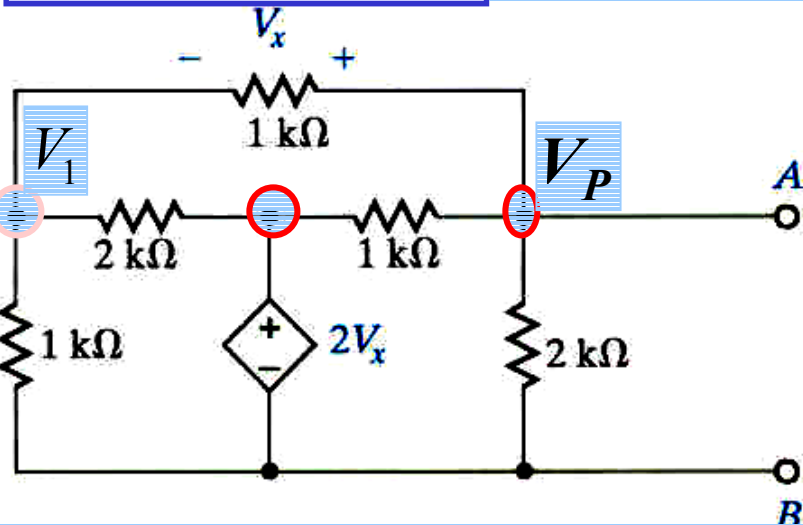

$$KCL@V_1: \frac{V_1}{1k} + \frac{V_1 - 2V_x}{2k} + \frac{V_1 - V_P}{1k} = 0$$

Controlling variable:  $V_x = V_P - V_1$

SOLVING THE EQUATIONS


$$V_1 = \frac{4}{7}V_P, \quad V_x = \frac{3}{7}V_P$$

$$I_P = \frac{V_P}{2k} + \frac{V_P - 2V_x}{1k} + \frac{V_x}{1k}$$

$$I_P = \frac{15V_P}{14k}$$

Do we use current probe or voltage probe?

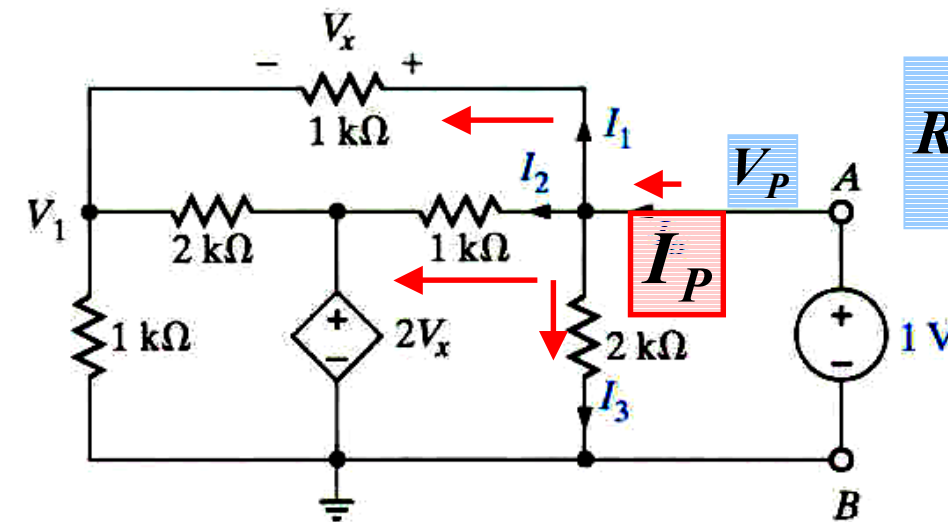If we use voltage probe there is only one node not connected through source




$$R_{TH} = \frac{V_P}{I_P} = \frac{14}{15}k\Omega$$

Using voltage probe. Must compute current supplied



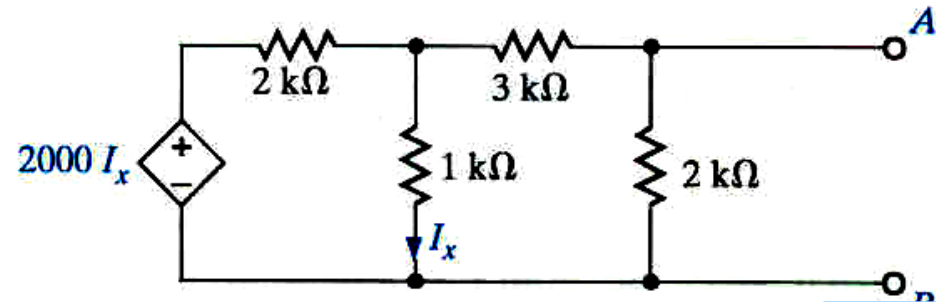
# LEARNING EXAMPLE Find the Thevenin Equivalent circuit at A - B



Only dependent sources. Hence  $V_{th} = 0$   
 To compute the equivalent resistance we must apply an external probe

We choose to apply a current probe

$$R_{TH} = \frac{V_P}{I_P}$$

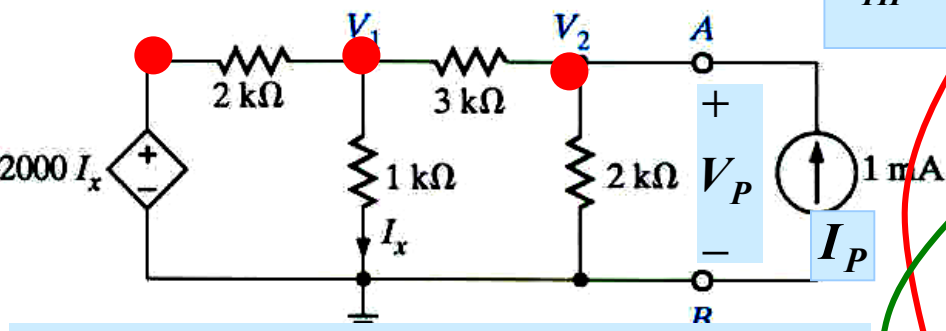

@V\_1

$$\frac{V_1 - 2000I_x}{2k} + \frac{V_1}{1k} + \frac{V_1 - V_2}{3k} = 0$$

@V\_2

$$\frac{V_2 - V_1}{3k} + \frac{V_2}{2k} = 1 \times 10^{-3} \quad (I_P)$$

Controlling variable

$$I_x = \frac{V_1}{1k}$$

"Conventional" circuit with dependent sources - use node analysis

$$3(V_1 - 2V_1) + 6V_1 + 2(V_1 - V_2) = 0$$


$$2(V_2 - V_1) + 3V_2 = 6[V]$$

$$5V_1 - 2V_2 = 0 \quad */2$$

$$-2V_1 + 5V_2 = 6 \quad */5$$

$$V_2 = \frac{30}{21} = \frac{10}{7}$$

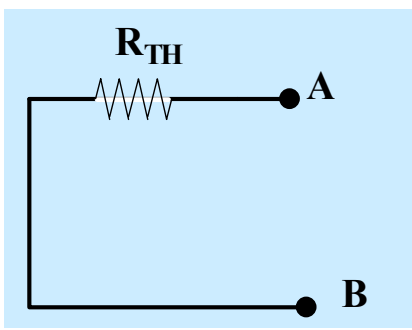
$$(V_P = V_2) \cap (I_P = 1mA) \Rightarrow R_{TH} = \frac{V_2}{1mA} = (10/7)k\Omega$$




Thevenin equivalent




# SAMPLE PROBLEM

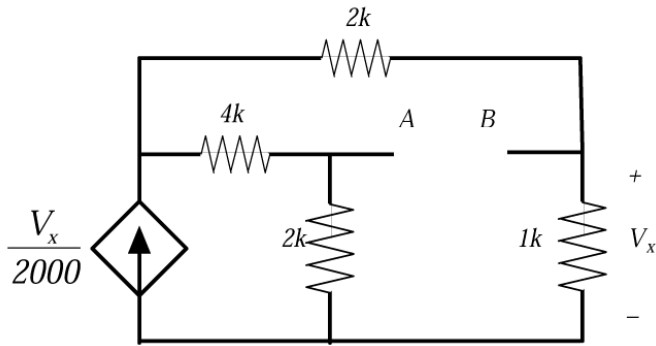

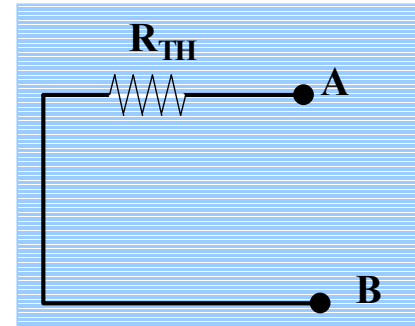FIND THE THEVENIN EQUIVALENT AT TERMINALS A - B USING A 1mA SOURCE



Thevenin equivalent

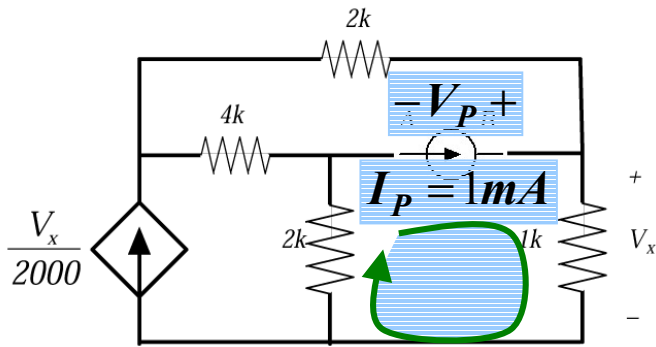


$$\begin{aligned} I_1 &= I_p/2 \\ I_3 &= 0 \\ R_{th} &= 2k\Omega \end{aligned}$$

$$R_{TH} = \frac{V_P}{I_P} = \frac{V_P}{1mA}$$

The resistance is numerically equal to  $V_p$  but with units of  $k\Omega$

MUST FIND  $V_{AB} = V_P$ . METHOD?

Loop analysis

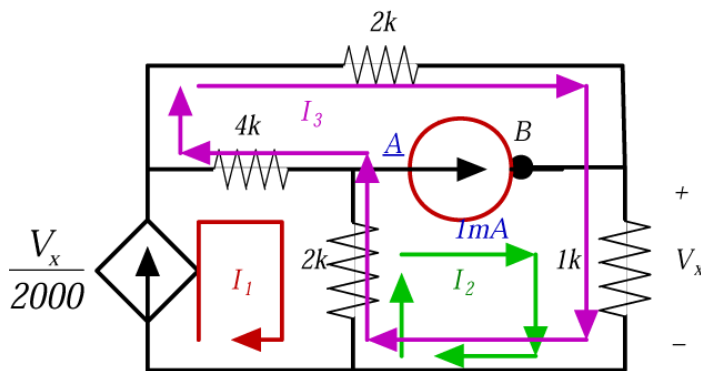

$$I_1 = \frac{V_X}{2000}; I_2 = I_P$$

$$2k * I_3 + 1k * (I_2 + I_3) + 2k * (I_3 + I_2 - I_1) + 4k * (I_3 - I_1) = 0$$

Controlling variable  $V_X = 1k * (I_3 + I_2)$

Voltage across current probe

$$-V_P + 1k * (I_3 + I_2) + 2k * (I_3 + I_2 - I_1) = 0$$



# Thevenin Equivalent

## Circuits with both Dependent and Independent Sources


We will compute open circuit voltage and short circuit current

For each determination of a Thevenin equivalent we will solve two circuits


Any and all the techniques discussed should be readily available; e.g., KCL, KVL, combination series/parallel, node, loop analysis, source superposition, source transformation, homogeneity

The approach of setting to zero all sources and then combining resistances to determine the Thevenin resistance is in general not applicable!!

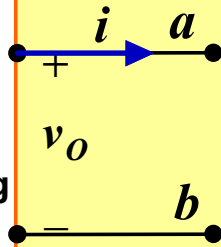LINEAR CIRCUIT  
May contain independent and dependent sources with their controlling variables  
PART A



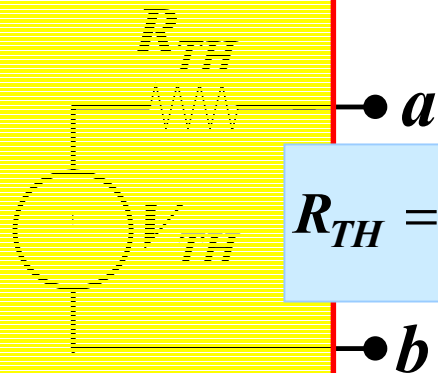Any and all the techniques discussed should be readily available; e.g., KCL, KVL, combination series/parallel, node, loop analysis, source superposition, source transformation, homogeneity



$$R_{TH} = \frac{V_{OC}}{I_{SC}}$$

$$V_{TH} = V_{OC}$$




**EXAMPLE Use Thevenin to determine  $V_o$**

**Guidelines to partition:**

**"Part A" should be as simple as possible.**

**After "Part A" is replaced by the Thevenin equivalent we should have a very simple circuit**

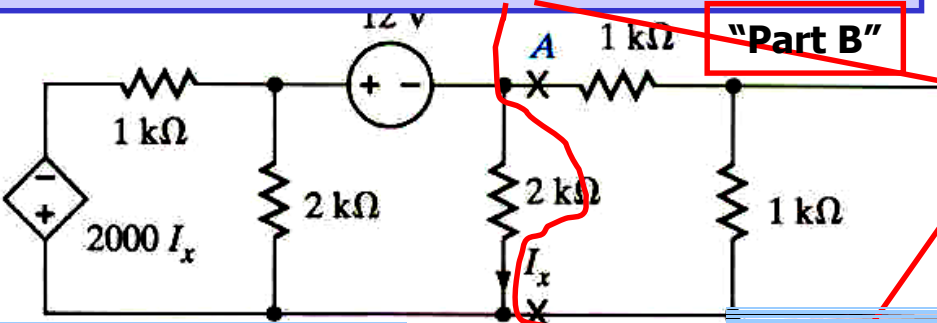**The dependent sources and their controlling variables must remain together**



**Open circuit voltage**

**Options???**

**Constraint at super node  $V_1 - V_{OC} = 12 \Rightarrow V_1 = 12 + V_{OC}$**

**KCL at super node**


$$\frac{(12 + V_{OC}) - (-aI_X)}{1k} + \frac{12 + V_{OC}}{2k} + \frac{V_{OC}}{2k} = 0$$

**Equation for controlling variable**

$$I_X^1 = \frac{V_{OC}}{2k}$$


**Solve**

$$V_{OC} = -\frac{36}{4 + (a/1k)}$$

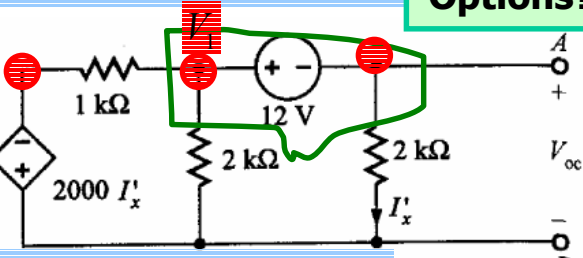

**Short circuit current**

$$I_X'' = \frac{V_A}{2k} = 0$$

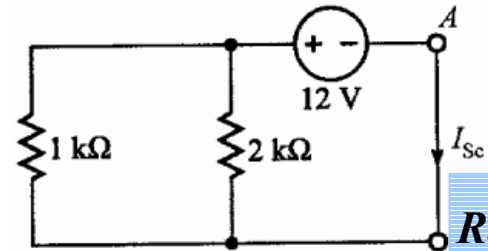


$$I_{SC} = -\frac{12V}{1k \parallel 2k} = -18mA$$

$$R_{TH} = \frac{V_{OC}}{I_{SC}} = \frac{2}{4 + (a/1k)} [k\Omega]$$

**Solution to the problem**

**Negative resistances for some "a's"**

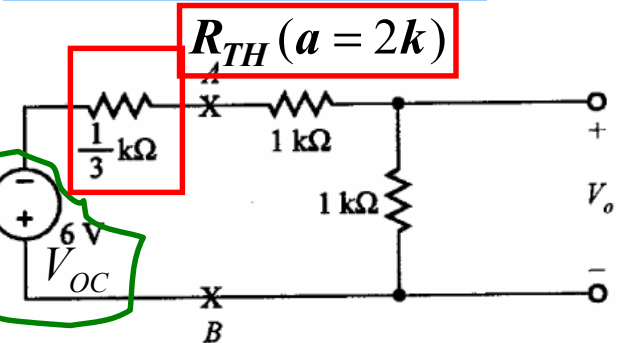
**Setting all sources to zero and combining resistances will yield an incorrect value!!!!**




$$V_o = \frac{1k}{1k + 1k + R_{TH}} V_{TH}$$



# Find $V_o$ using Thevenin

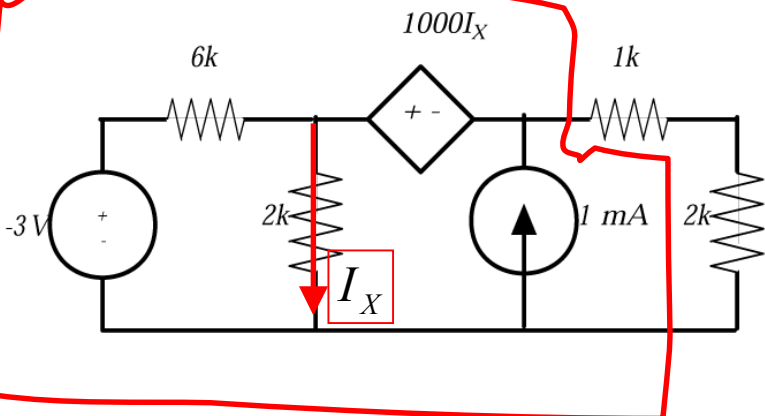

## Short Circuit Current

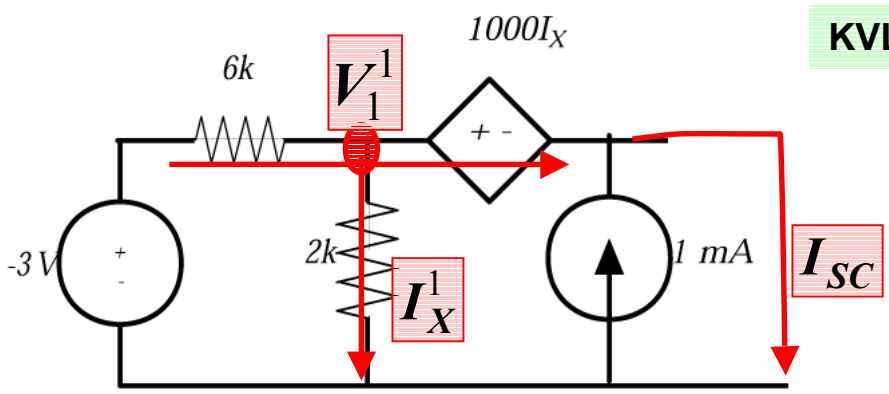

$$V_1^1 = 1000 I_X^1$$


$$I_X^1 = \frac{V_1^1}{2k} \Rightarrow V_1^1 = 0 \Rightarrow I_X^1 = 0$$

### KCL

$$I_{SC} = 1mA + (-3V)/(6k) = 0.5mA$$

$$R_{TH} = \frac{V_{OC}}{I_{SC}} = (3/4)k$$

## Open circuit voltage

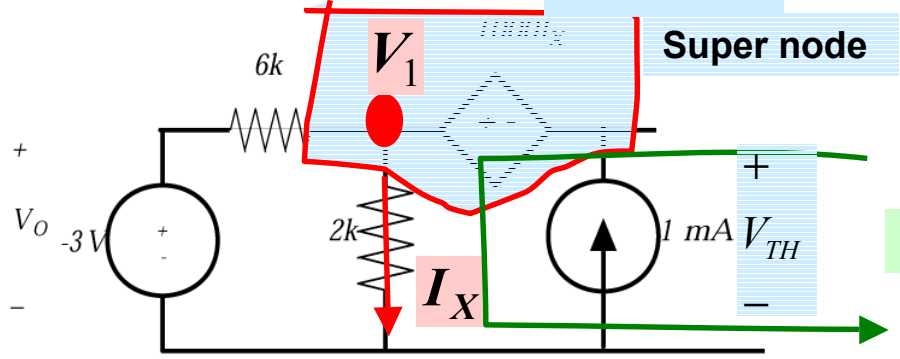

### Method???

### Super node

### KVL

$$\frac{V_1}{2k} - 1mA + \frac{V_1 - (-3V)}{6k} = 0$$

$$V_1 = (3/4)[V]$$

### KVL


$$-V_{TH} - 1000 I_X + V_1 = 0$$

### Controlling variable

$$I_X = \frac{V_1}{2k}$$


$$V_{TH} = (3/8)[V]$$

## The equivalent circuit

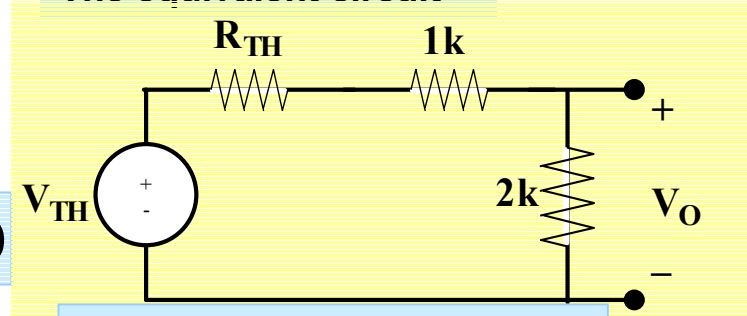

$$V_o = \frac{2}{2+1+(3/4)} (3/8)[V]$$

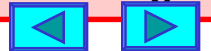
The equivalent resistance cannot be obtained by short circuiting the sources and determining the resistance of the resulting interconnection of resistors




**EXAMPLE: Use Thevenin to compute  $V_o$**

**DON'T PANIC!!**

**Select your partition**

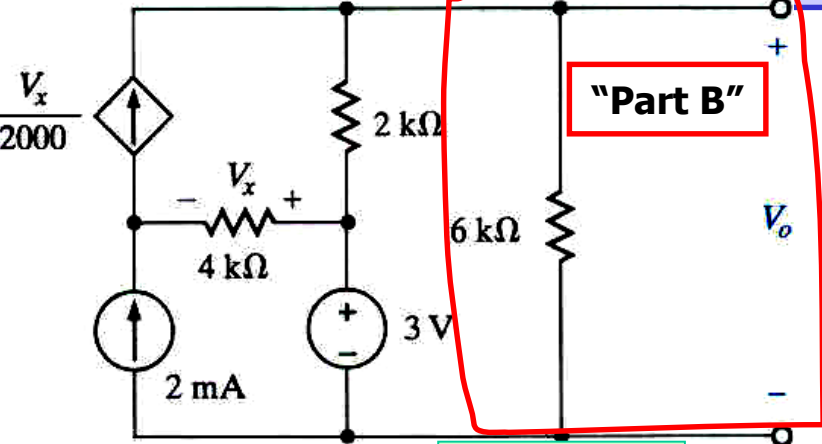

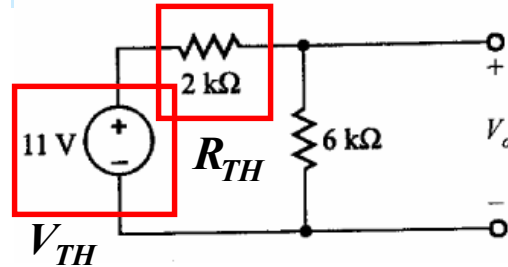**Now compute  $V_o$  using the Thevenin equivalent**



$$V_o = \frac{6k}{6k + 8k} 11[V]$$

**Open Circuit Voltage**

**Use loops**

**Loop equations**

$$I_1 = \frac{V_X^1}{2000}; I_2 = 2mA$$

**Controlling variable**

$$V_X^1 = 4k(I_1 - I_2)$$

$$V_X^1 = 2kI_1 \Rightarrow 2kI_1 = 4k(I_1 - I_2) \Rightarrow I_1 = 4mA$$

$$V_{OC} = 2k * I_1 + 3[V] = 2k * 4mA + 3V = 11V$$

**KVL for  $V_{oc}$**

**Loop equations**

$$I_1 = 4mA \text{ Same as before}$$

$$I_{SC} = \frac{3V + 2k * I_1}{2k} = \frac{11}{2} mA$$

**Short circuit current**

$$I_1 = \frac{V_x''}{2000}; I_2 = 2mA$$



$$-3V + 2k(I_{SC} - I_1) = 0$$

**Controlling variable**

$$V_X'' = 4k * (I_1 - I_2)$$

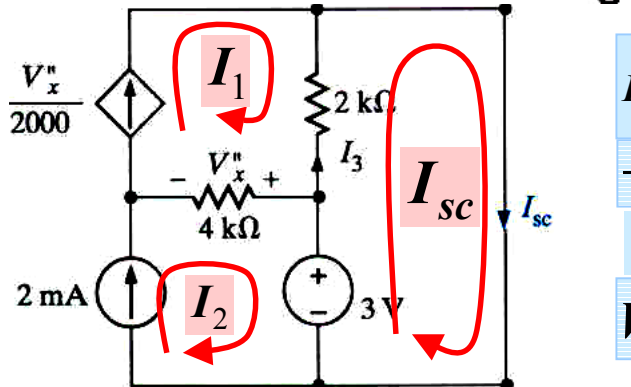
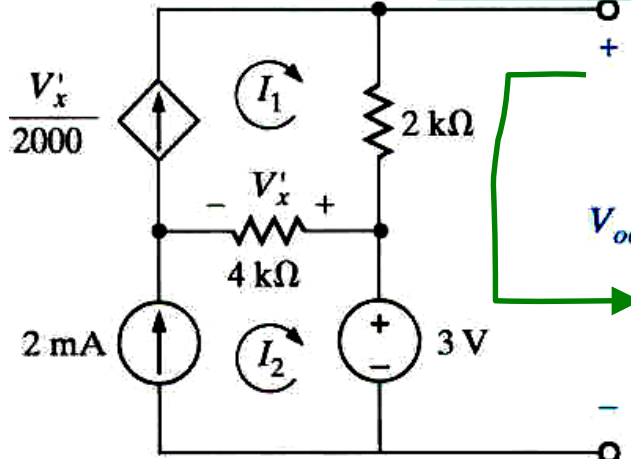
**Thevenin resistance**

$$R_{TH} = \frac{V_{oc}}{I_{SC}} = \frac{11[V]}{(11/2)mA} = 2k\Omega$$



# EXAMPLE

## Linear Model for Transistor

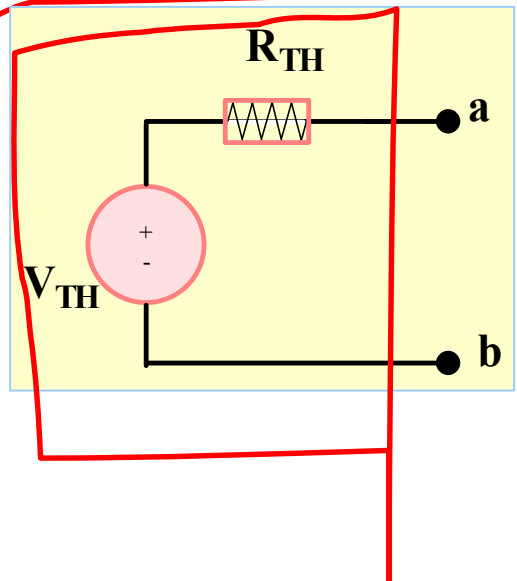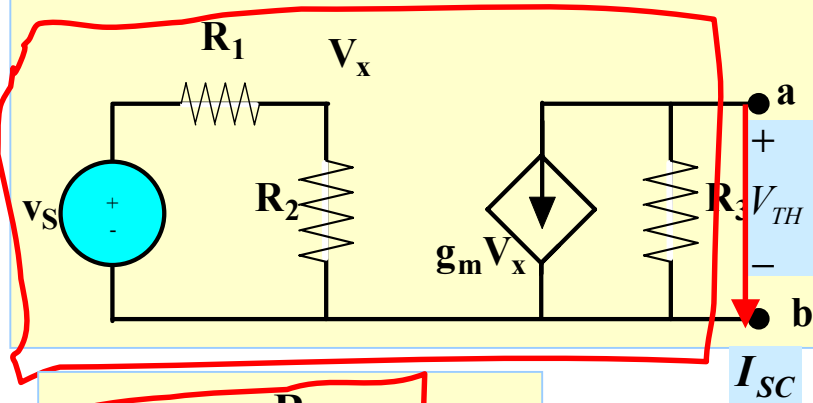

### The alternative for mixed sources

$$V_{TH} = V_{OC}, \quad R_{TH} = \frac{V_{OC}}{I_{SC}}$$

### Open circuit voltage

$$V_{TH} = -g_m R_3 V_x$$

$$V_x = \frac{R_2}{R_1 + R_2} v_S \Rightarrow V_{TH} = -g_m \frac{R_3 R_2}{R_1 + R_2} v_S$$

### Short circuit current

$$I_{SC} = -g_m V_x = -g_m \frac{R_2}{R_1 + R_2} v_S$$


### Equivalent Resistance

$$R_{TH} = \frac{V_{OC}}{I_{SC}} = R_3$$



# SAMPLE PROBLEM

supernode

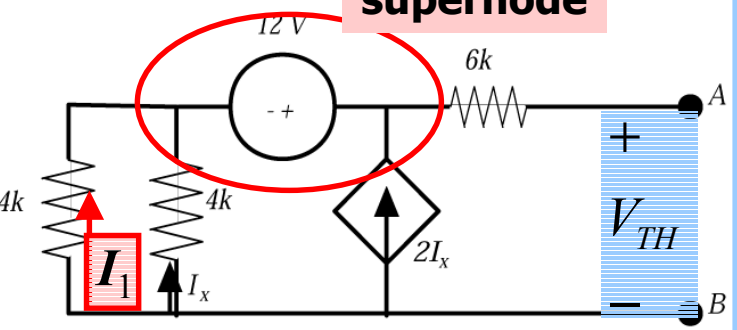

FIND THE THEVENIN EQUIVALENT AT THE TERMINALS A - B

Mixed sources. Must compute Voc and Isc

Open circuit voltage

KCL at super node  $I_1 + I_X + 2I_X = 0$

The two 4k resistors are in parallel  $I_1 = I_X$

$I_X = 0 \Rightarrow V_{TH} = 12[V]$

KCL at supernode


$I_{SC} = 4I_X$

$4k * (I_{SC} / 4) - 12[V] + 6k * I_{SC} = 0$


$R_{TH} = \frac{V_{TH}}{I_{SC}} = \frac{12V}{(12/7)mA} = 7k\Omega$

$I_{SC} = \frac{12}{7} mA$

Short circuit current

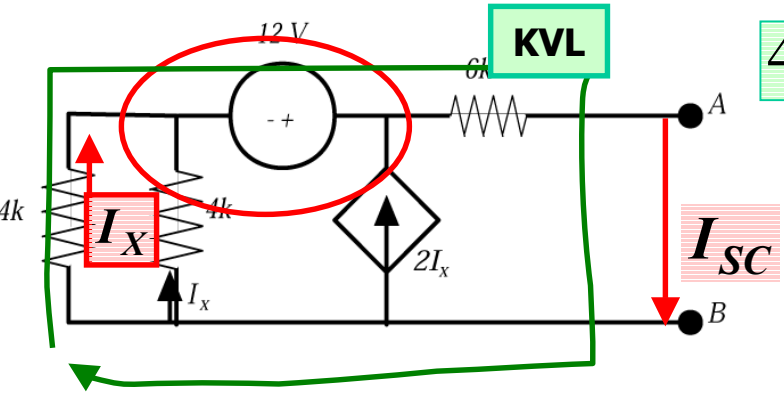


FINAL ANSWER

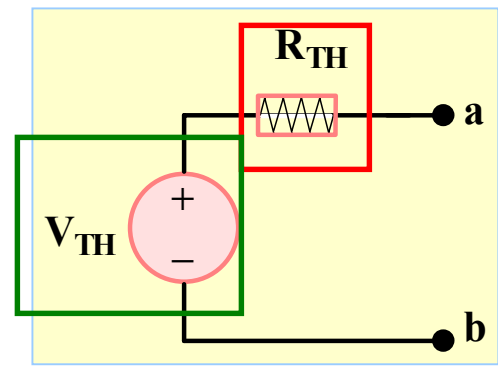

# SAMPLE PROBLEM

FIND THE THEVENIN EQUIVALENT AT a - b

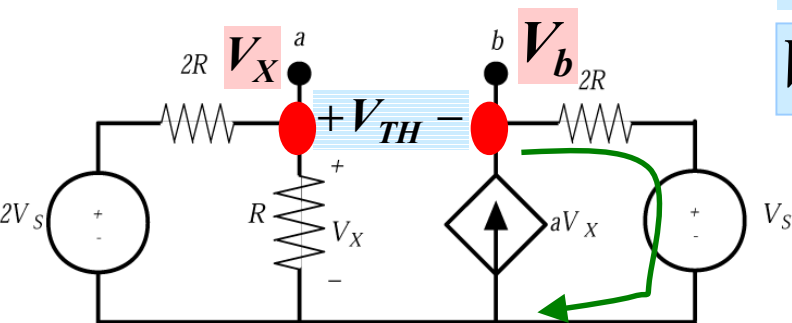

Mixed sources! Must compute open loop voltage and short circuit current

Open circuit voltage

$$V_{TH} = V_X - V_b$$

For V<sub>x</sub> use voltage divider


$$V_X = \frac{R}{R + 2R} (2V_S) = \frac{2}{3} V_S$$

For V<sub>b</sub> use KVL

$$V_b = 2R(aV_X) + V_S = (1 + 4aR/3)V_S$$

$$V_{TH} = V_X - (2RaV_X + V_S) = (1 - 2Ra)(2V_S/3) - V_S$$

Short circuit current

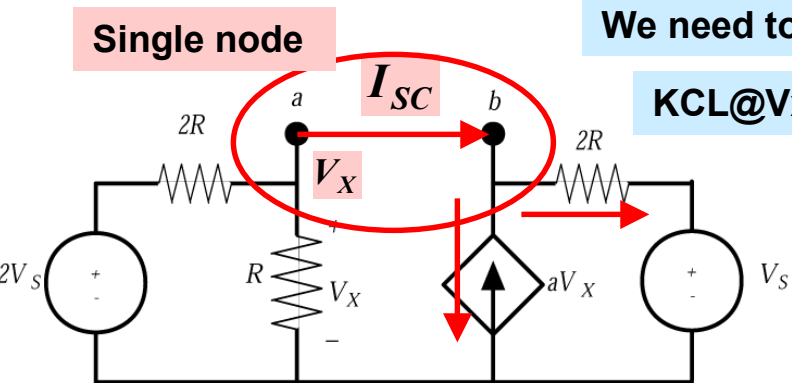

Single node

We need to compute V<sub>x</sub>

KCL@V<sub>x</sub>

$$\frac{V_x^1 - 2V_S}{2R} + \frac{V_x^1}{R} - aV_x^1 + \frac{V_x^1 - V_S}{2R} = 0 \Rightarrow V_x^1 = \frac{3V_S}{4 - 2aR}$$


$$V_{TH} = -\frac{1 + 4aR}{3} V_S$$

KCL again can give the short circuit current

$$I_{SC} = -aV_x^1 + \frac{V_x^1 - V_S}{2R}$$


$$I_{SC} = -\frac{1 + 4aR}{4R(1 - 2aR)} V_S$$
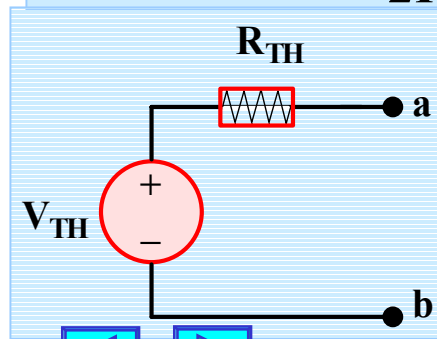
$$R_{TH} = \frac{V_{OC}}{I_{SC}} = \frac{V_{TH}}{I_{SC}} = \frac{4R(1 - 2aR)}{3}$$



FINAL ANSWER
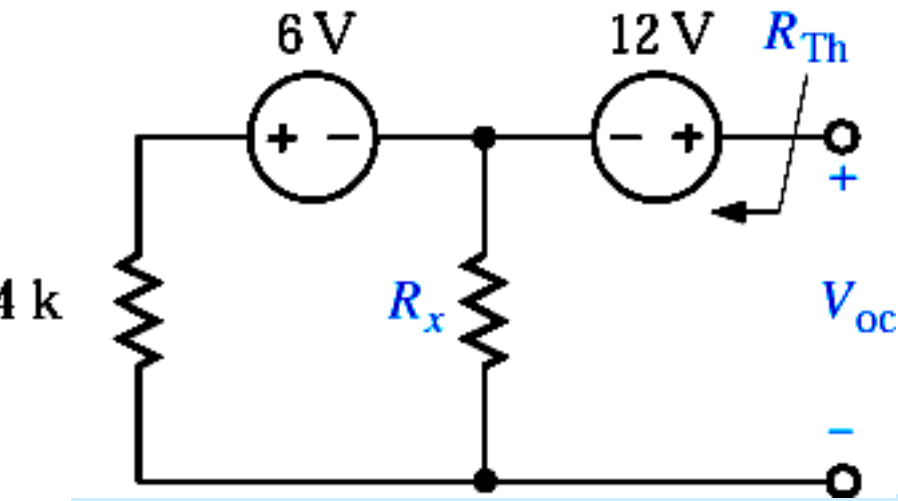
# LEARNING EXAMPLE FIND AND PLOT $R_{TH}$ , $V_{OC}$ , WHEN $0 \leq R_X \leq 10k\Omega$




## DATA TO BE PLOTTED


$$R_{TH} = 4k \parallel R_X = \frac{4R_X}{4 + R_X} \quad V_{OC} = 12 - 6 \left[ \frac{R_X}{4k + R_X} \right]$$

Using EXCEL to generate and plot data


### THEVENIN EQUIVALENT EXAMPLE

Rx[kOhm]	Voc[V]	Rth[kOhm]
0	12	0
0.1	11.8537	0.097560976
0.2	11.7143	0.19047619
0.3	11.5814	0.279069767
0.4	11.4545	0.363636364
0.5	11.3333	0.444444444
0.6	11.2174	0.52173913
0.7	11.1064	0.595744681
0.8	11	0.666666667
0.9	10.898	0.734693878
1	10.8	0.8
1.1	10.7059	0.862745098
1.2	10.6154	0.923076923
1.3	10.5283	0.981132075
1.4	10.4444	1.037037037
1.5	10.3636	1.090909091
1.6	10.2857	1.142857143
1.7	10.2105	1.192982456
1.8	10.1379	1.24137931
1.9	10.0678	1.288135593

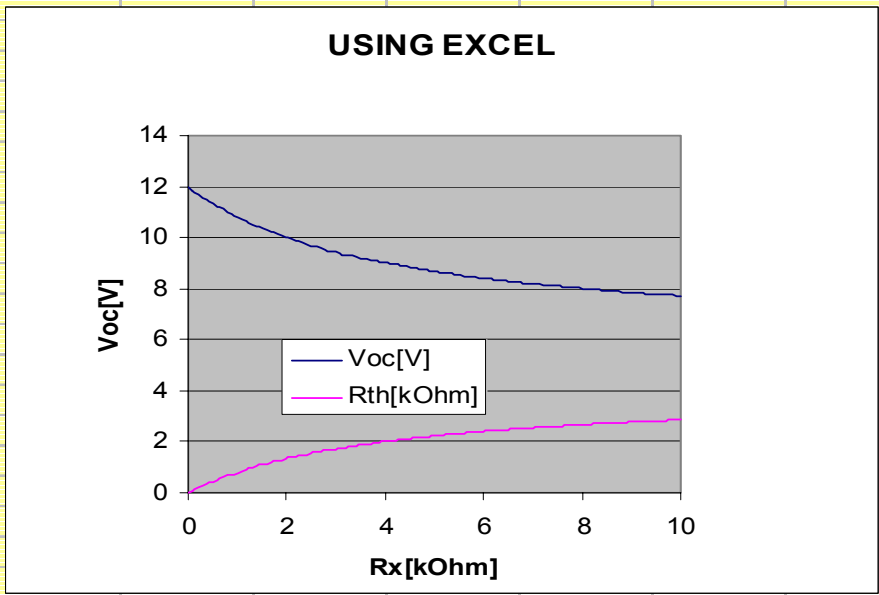


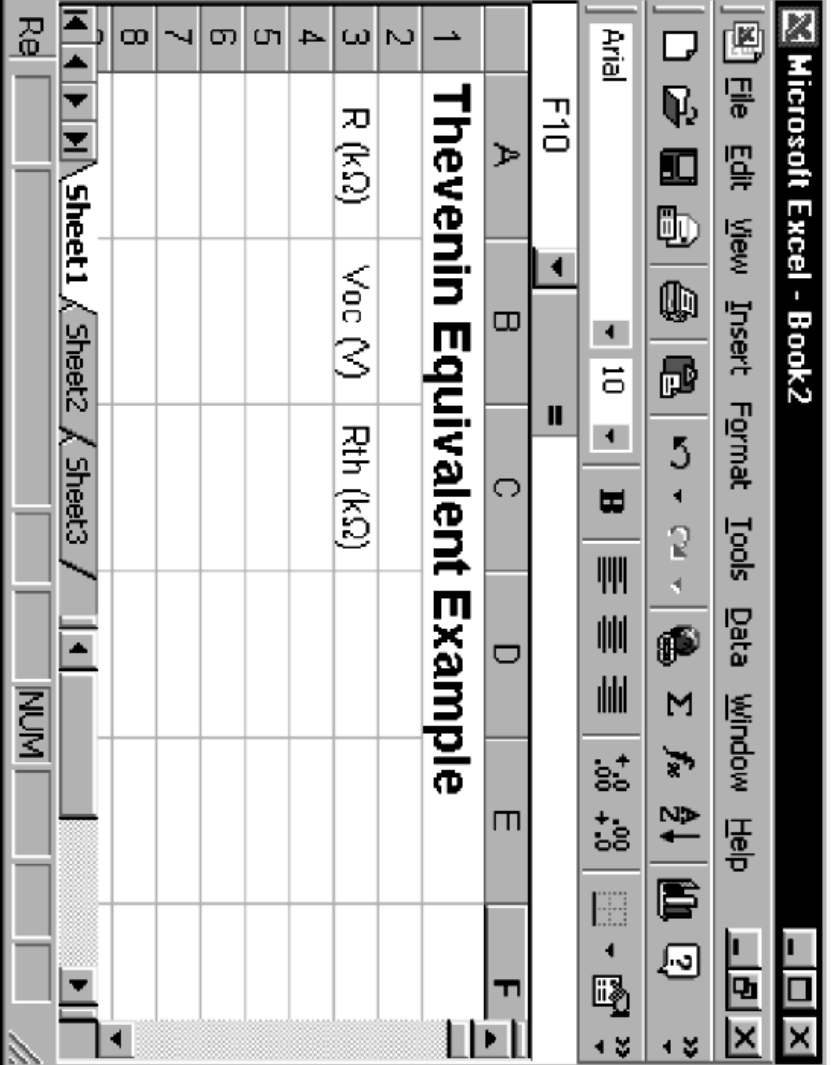

(a)

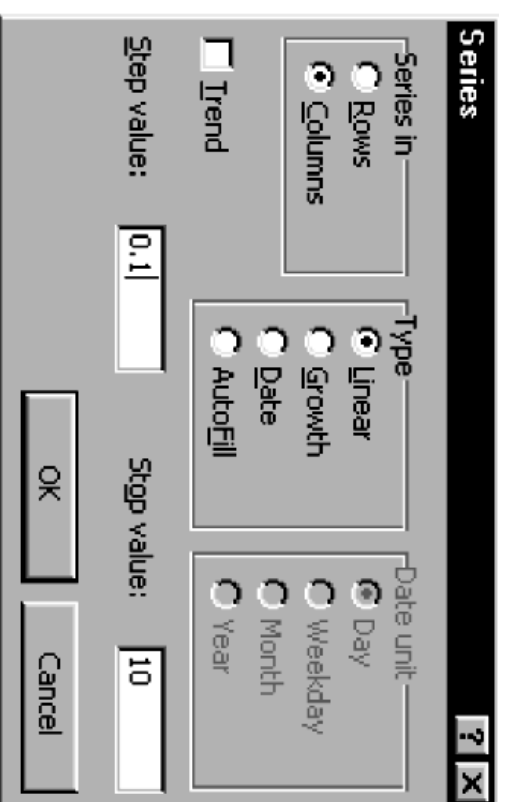

(b)

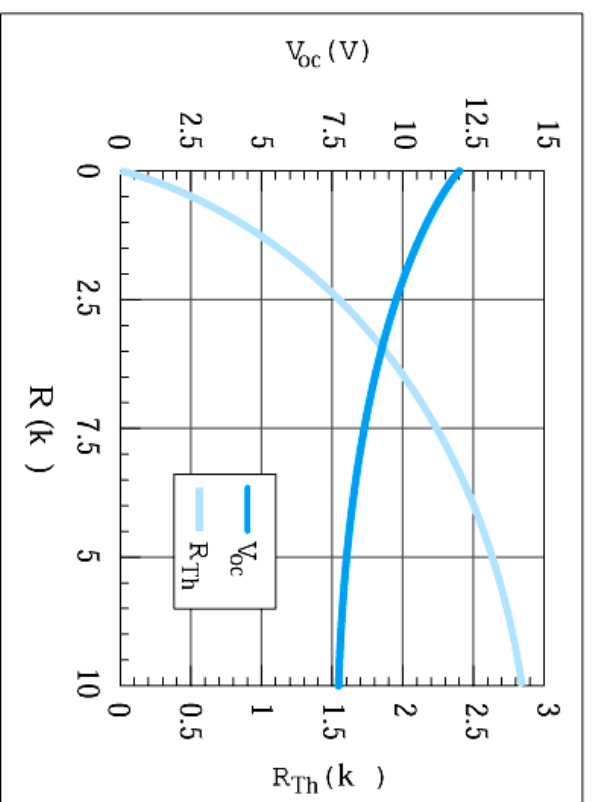

(c)



# LEARNING EXAMPLE FIND AND PLOT $R_{TH}$ , $V_{OC}$ , WHEN $0 \leq R_X \leq 10k\Omega$


## DATA TO BE PLOTTED

$$R_{TH} = 4k \parallel R_X = \frac{4R_X}{4 + R_X} \quad V_{OC} = 12 - 6 \left[ \frac{R_X}{4k + R_X} \right]$$

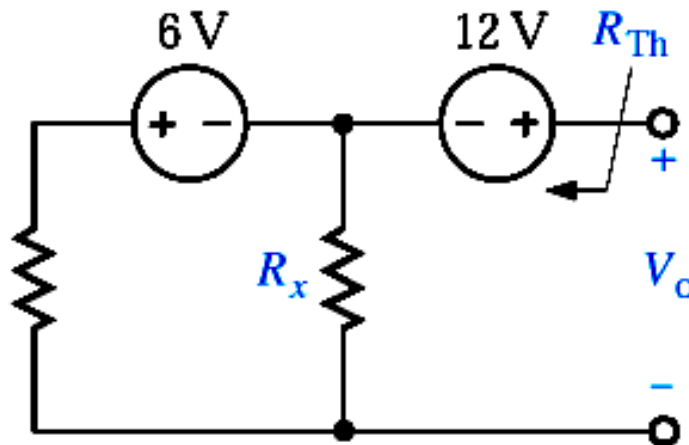
## Using MATLAB to generate and plot data

```



» Rx=[0:0.1:10]'; %define the range of resistors to use
» Voc=12-6*Rx./(Rx+4); %the formula for Voc. Notice "./"
» Rth=4*Rx./(4+Rx); %formula for Thevenin resistance.
» plot(Rx,Voc,'bo', Rx,Rth,'md')
» title('USING MATLAB'), %proper graphing tools
» grid, xlabel('Rx(kOhm)'), ylabel('Volts/kOhms')
» legend('Voc[V]', 'Rth[kOhm]')
    
```






USING MATLAB

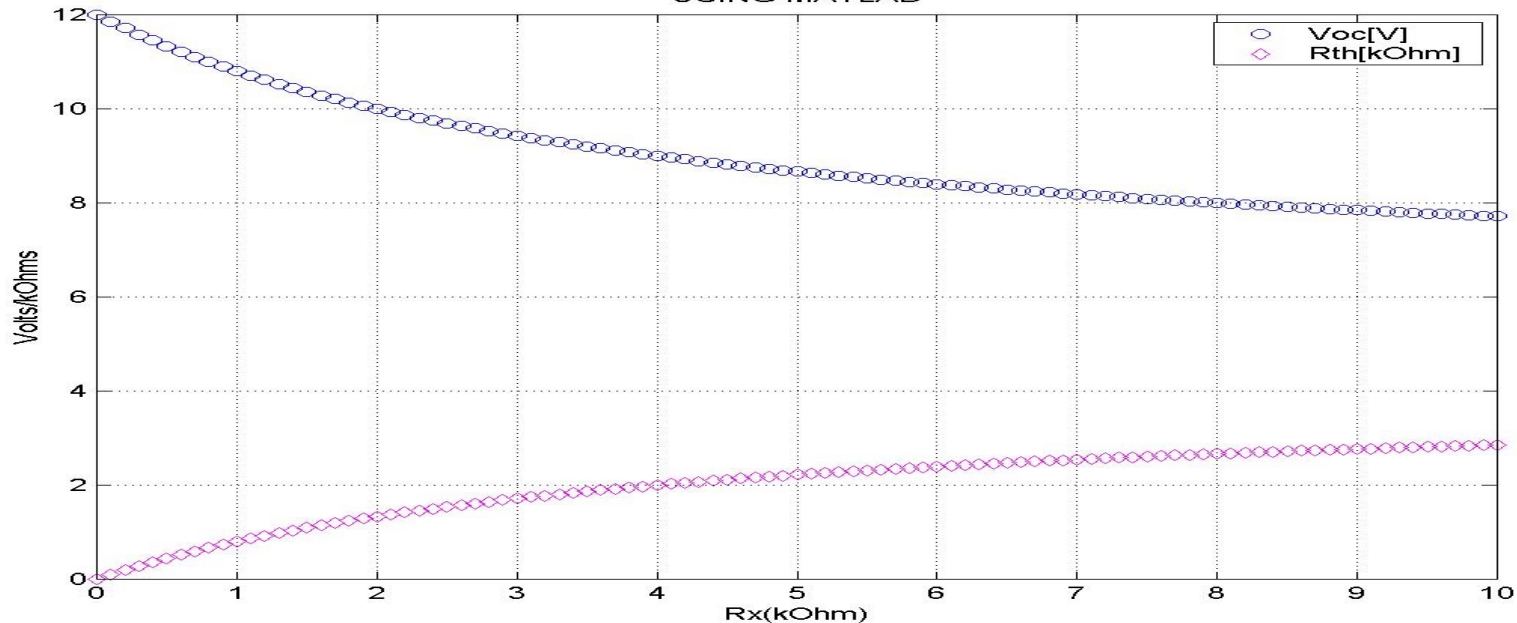
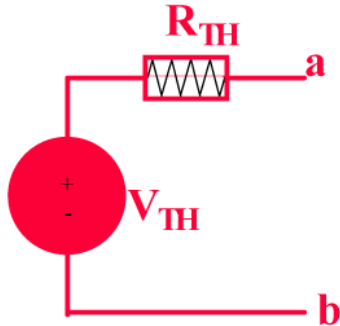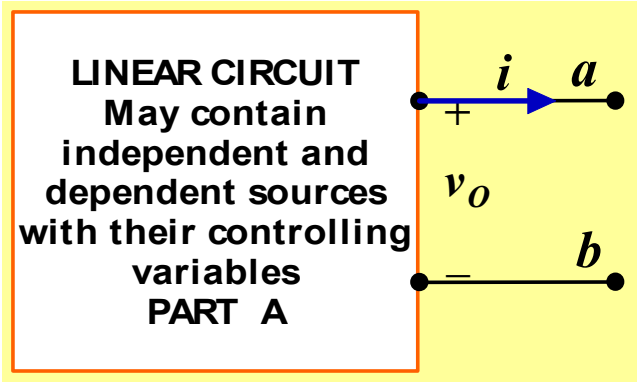
# A MORE GENERAL VIEW OF THEVENIN THEOREM



## USUAL INTERPRETATION

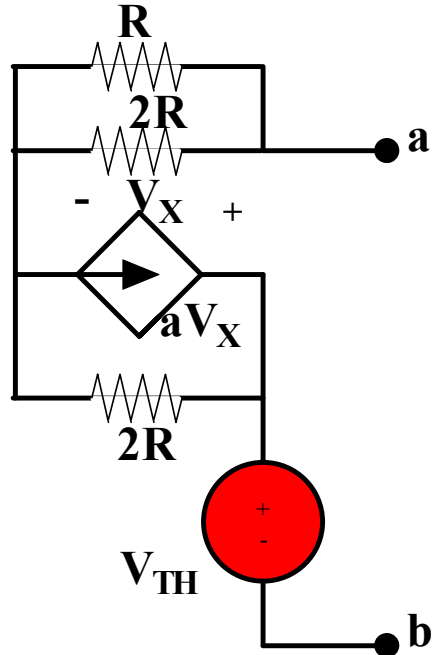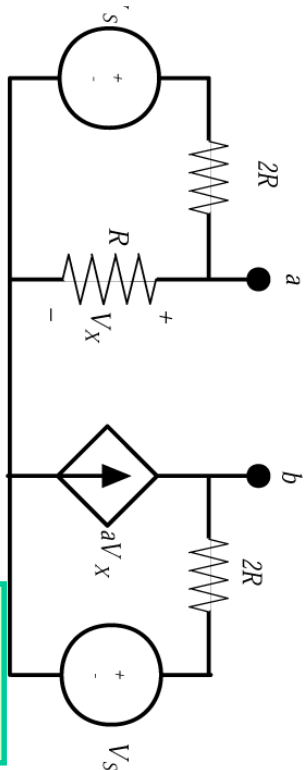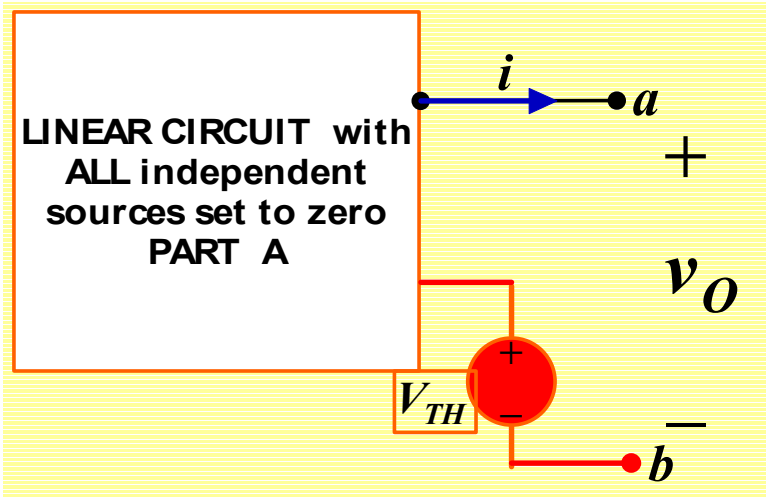

Thevenin



**THIS INTERPRETATION APPLIES EVEN WHEN THE PASSIVE ELEMENTS INCLUDE INDUCTORS AND CAPACITORS**



# MAXIMUM POWER TRANSFER



Courtesy of M.J. Renardson

<http://angelfire.com/ab3/mjramp/index.html>

From PreAmp  
(voltage)


To speakers

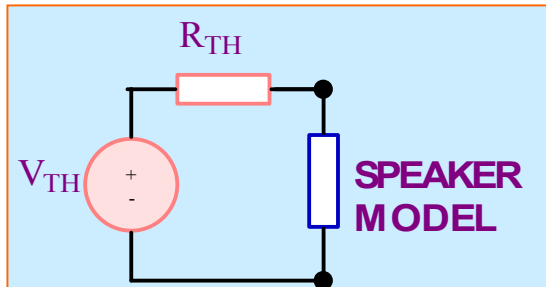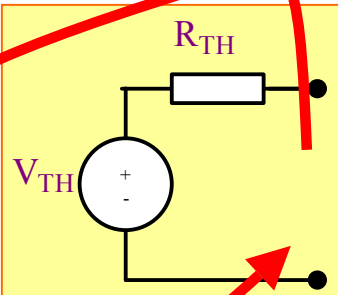The simplest model for a  
speaker is a resistance...



**BASIC MODEL FOR THE  
ANALYSIS OF POWER  
TRANSFER**

# MAXIMUM POWER TRANSFER

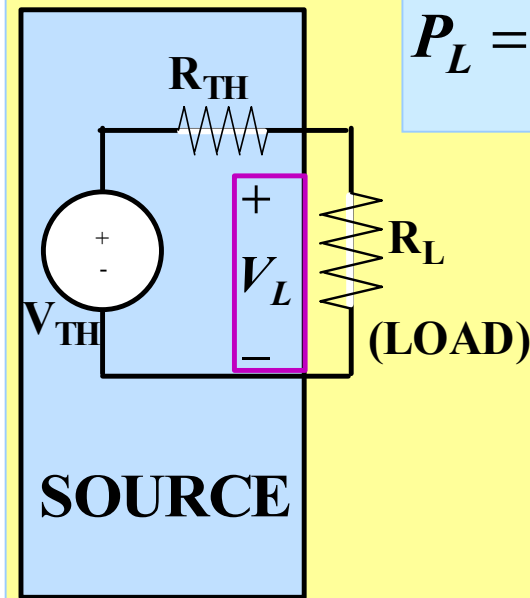

$$P_L = \frac{V_L^2}{R_L}; V_L = \frac{R_L}{R_{TH} + R_L} V_{TH}$$

$$P_L = \frac{R_L}{(R_{TH} + R_L)^2} V_{TH}^2$$

For every choice of  $R_L$  we have a different power. How do we find the maximum value?

Consider  $P_L$  as a function of  $R_L$  and find the maximum of such function

$$\frac{dP_L}{dR_L} = V_{TH}^2 \left( \frac{(R_{TH} + R_L) - 2R_L}{(R_{TH} + R_L)^3} \right)$$

Technically we need to verify that it is indeed a maximum

Set the derivative to zero to find extreme points. For this case we need to set to zero the numerator

$$R_{TH} + R_L - 2R_L = 0 \Rightarrow R_L^* = R_{TH}$$

The maximum power transfer theorem

The value of the maximum power that can be transferred is


The load that maximizes the power transfer for a circuit is equal to the Thevenin equivalent resistance of the circuit.

$$P_L(\max) = \frac{V_{TH}^2}{4R_{TH}}$$

ONLY IN THIS CASE WE NEED TO COMPUTE THE THEVENIN VOLTAGE


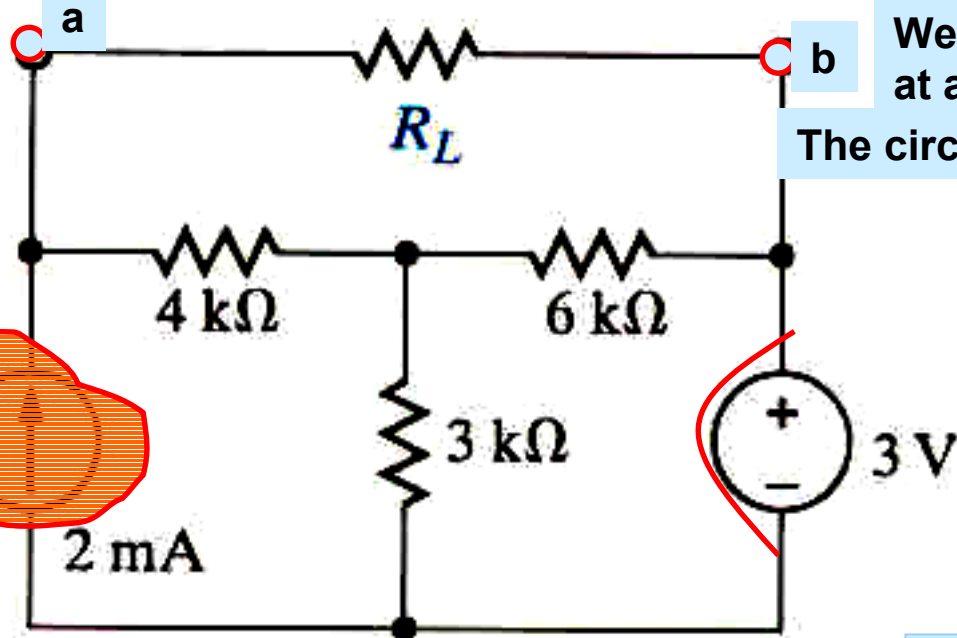
# LEARNING EXAMPLE DETERMINE $R_L$ FOR MAXIMUM POWER TRANSFER



We need to find the Thevenin resistance at a - b.

The circuit contains only independent sources ...

$$R_{TH} = 4k + \parallel 3k, 6k \parallel = 6k$$

Resistance for maximum power transfer


If we MUST find the value of the power that can be transferred THEN we need the Thevenin voltage!!!

*loop1*:  $I_1 = 2mA$

*loop2*:  $3k * (I_2 - I_1) + 6k * I_2 + 3[V] = 0$

$$I_2 = -\frac{3[V]}{9k} + \frac{1}{3}I_1 = \frac{1}{3}[mA]$$

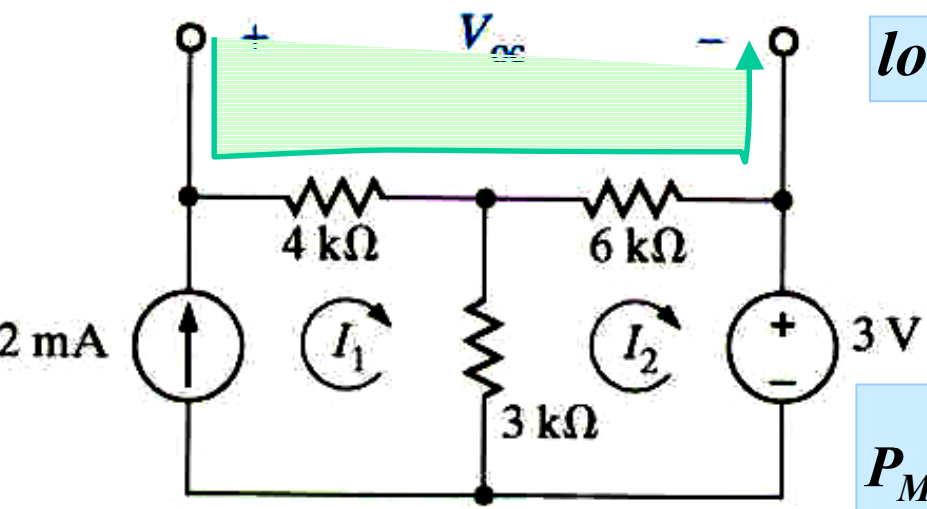**KVL**:  $V_{OC} = 4k * I_1 + 6k * I_2 = 10[V]$




$$P_{MX} = \frac{V_{TH}^2}{4R_{TH}}$$

$$P_{MX} = \frac{100[V^2]}{4 * 6k} = \frac{25}{6}[mW]$$



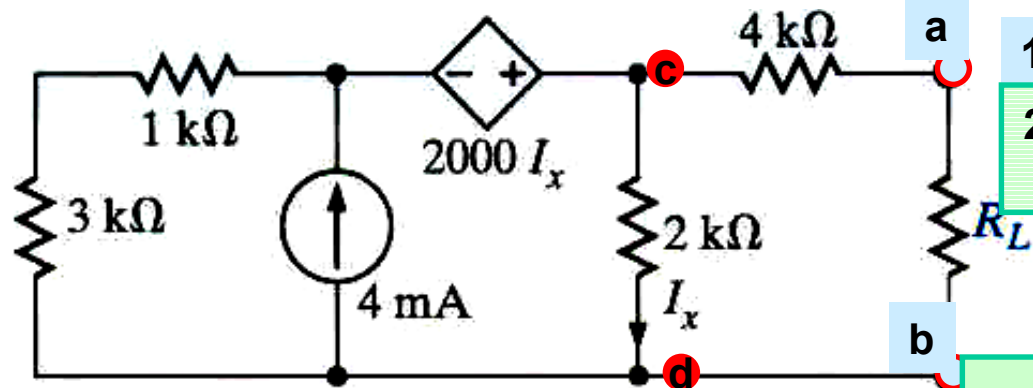
# LEARNING EXAMPLE DETERMINE $R_L$ AND MAXIMUM POWER TRANSFERRED




This is a mixed sources problem

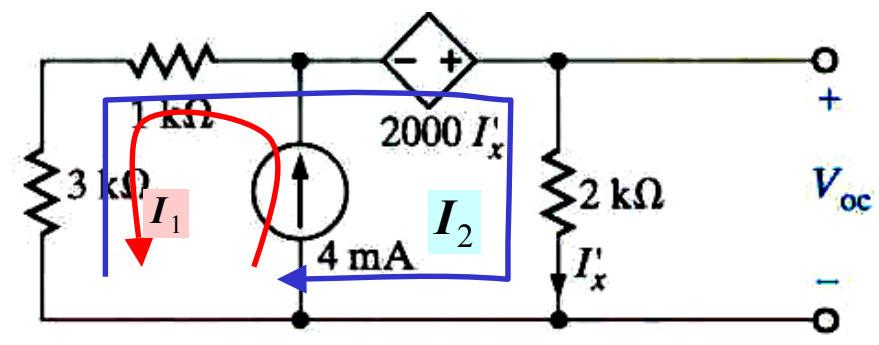1. Find the Thevenin equivalent at a - b
2. Remember that for maximum power transfer  $R_L = R_{TH}$   $P_{MX} = \frac{V_{TH}^2}{4R_{TH}}$

.... And it is simpler if we do Thevenin at c - d and account for the 4k at the end



Now the short circuit current

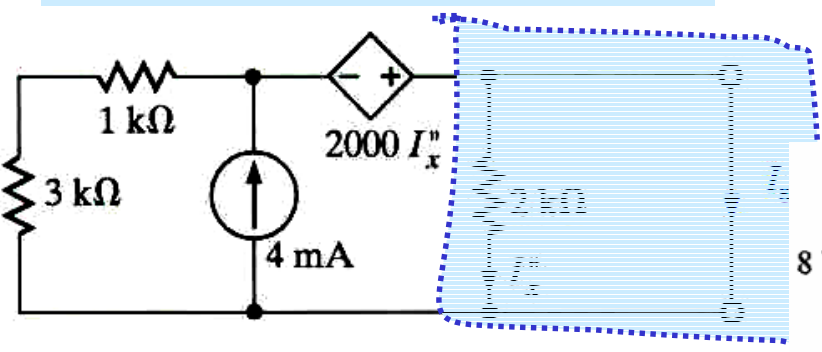

loop1:  $I_1 = 4mA$

loop2:  $-2kI'_x + 2kI_2 + 4k(I_2 - I_1) = 0$


Controlling variable:  $I'_x = I_2$

$I_2 = I_1 = 4mA \Rightarrow V_{OC} = 8[V]$

$R_{TH} = 2k$

$I''_x = 0 \Rightarrow I_{SC} = 4mA$

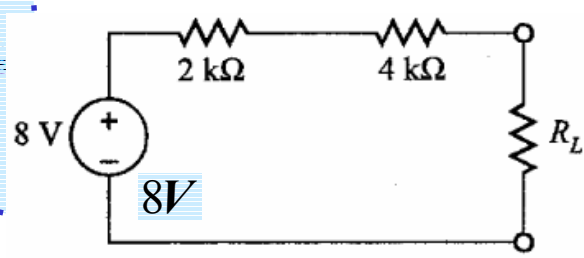Remember now where the partition was made



$R_L = 6k$

$P_{MX} = \frac{8^2}{4 * 6} [mW] = \frac{8}{3} [mW]$

