

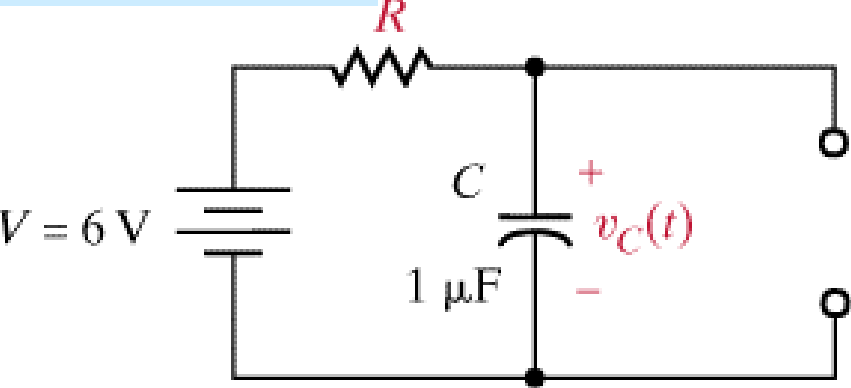


Find R so that the SCR is ready to fire after one second of capacitor charging

Charging phase

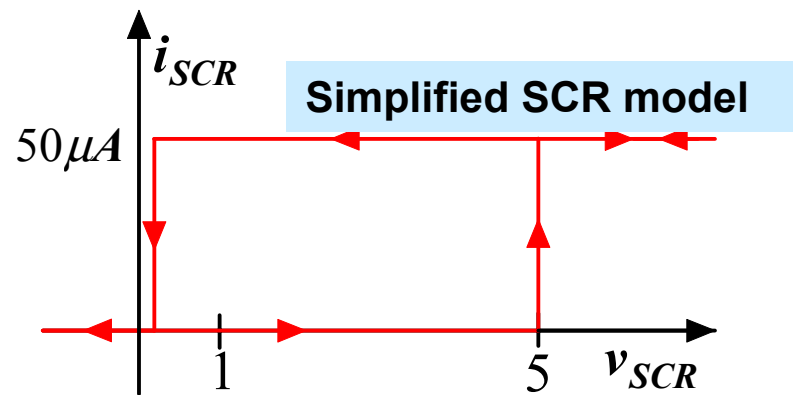

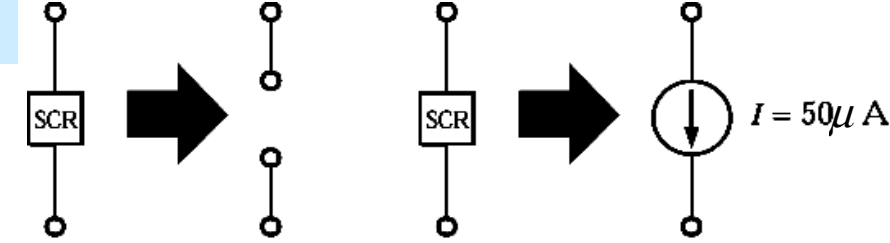As soon as the SCR switches off the capacitor starts charging. Hence, assume $v_C(0) = 0.2$



SCR "fires"

$$v_C(t) = K_1 + K_2 e^{-\frac{t}{\tau}}, t > 0$$

$$\tau = RC = 10^{-6} R$$

$$v_C(\infty) = 6V = K_1$$

$$v_C(0) = 0.2V = K_1 + K_2$$

$$K_1 = 6$$

$$K_2 = 5.8$$

$$v_C(t) = 6 - 5.8 e^{-\frac{t}{RC}}, t > 0$$


Required: $v_C(1) = 5V = 6 - 5.8 e^{-\frac{1}{RC}}$

$$e^{\frac{1}{RC}} = 5.8 \Rightarrow \frac{1}{RC} = 1.758 \Rightarrow R = 569k\Omega$$

$$\tau = RC = .569$$



THE DISCHARGE STAGE

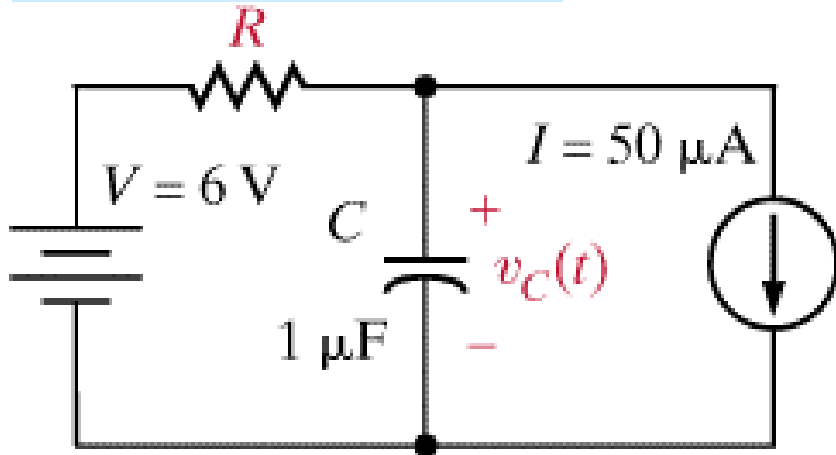

With the chosen resistor discharge starts after one second and the capacitor voltage is 5V

$$v_C(t) = K_1 + K_2 e^{-\frac{(t-1)}{\tau}}, \quad t > 1 \quad \tau = 0.569\text{s} \quad v_C(1) = 5\text{V}$$

$$v_C(\infty) = 6 - RI = 6 - 0.569 \times 10^6 (\Omega) \times 50 \times 10^{-6} (\text{A})$$

$$K_1 = -22.45$$

$$K_1 + K_2 = 5 \Rightarrow K_2 = 27.45$$

$$v_C(t) = -22.45 + 27.45 e^{-\frac{(t-1)}{0.569}} \quad t > 1$$

For SCR turn off $v_C(1 + T_{\text{off}}) = 0.2$

$$e^{0.569} = \frac{27.45}{22.65} \Rightarrow T_{\text{off}} = 0.11\text{s}$$

```
%example6p12
```

```
%visualizes one cycle of pacemaker
```

```
%charge cycle
```

```
tau=0.569;
```

```
tc=linspace(0,1,200);
```

```
vc=6-5.8*exp(-tc/tau);
```

```
%discharge cycle. SCR on
```

```
td=linspace(1,1.11,25);
```


```
vcd=-22.45+27.45*exp(-(td-1)/tau);
```

```
plot(tc,vc,'bd',td,vcd,'ro'),grid,
```

```
title('PACEMAKER CYCLE')
```

```
xlabel('time(s)'), ylabel('voltage(V)')
```


```
legend('SCR off', 'SCR on')
```

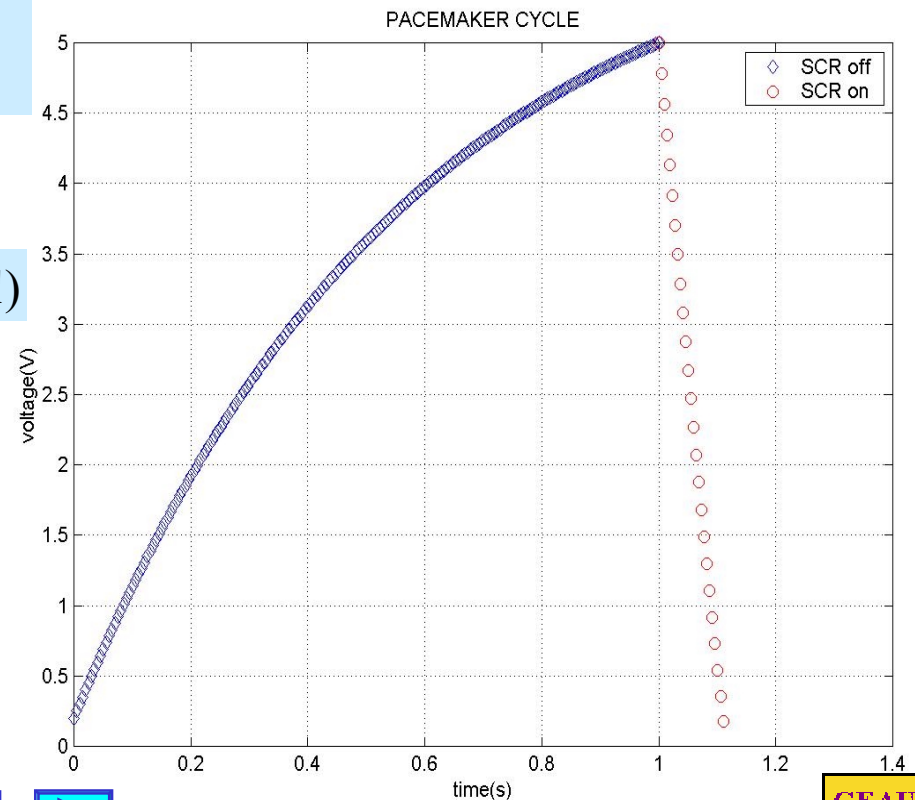

LEARNING EXAMPLE


BOOSTER CONVERTER

AC voltage waveform

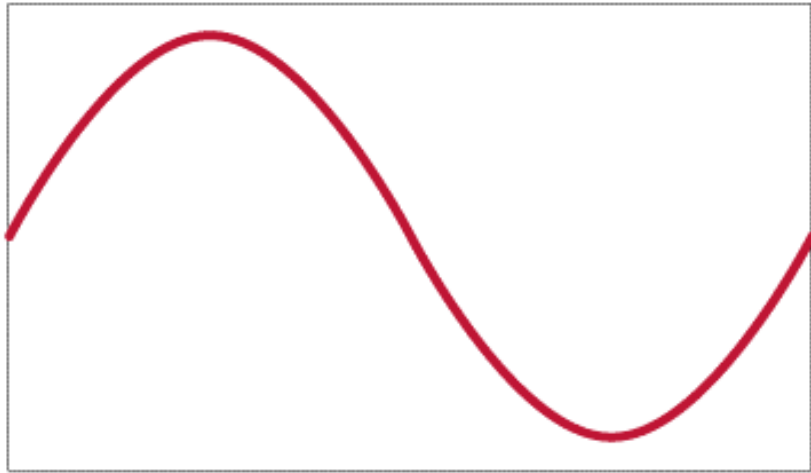


Time


e.g. booster

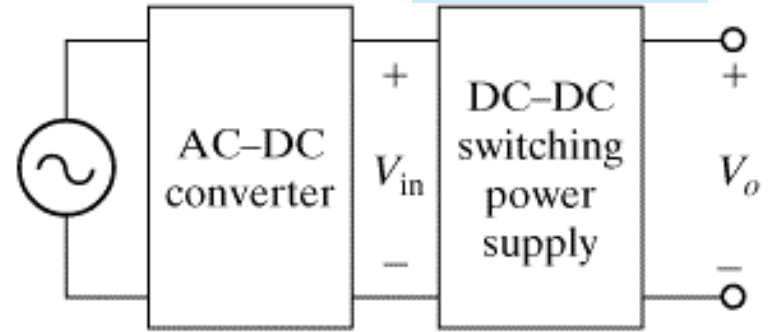

STANDARD DC POWER SUPPLY

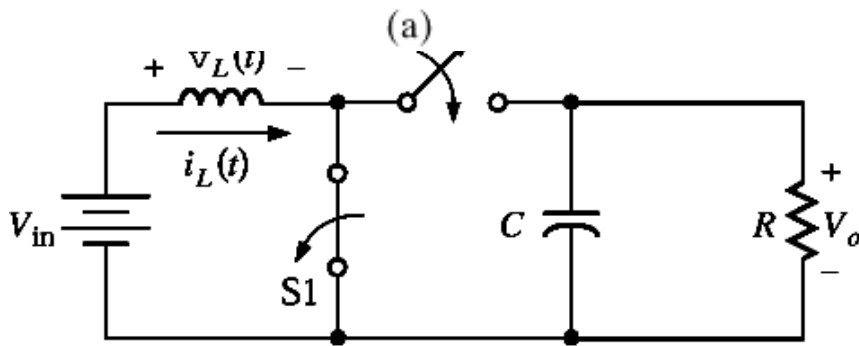

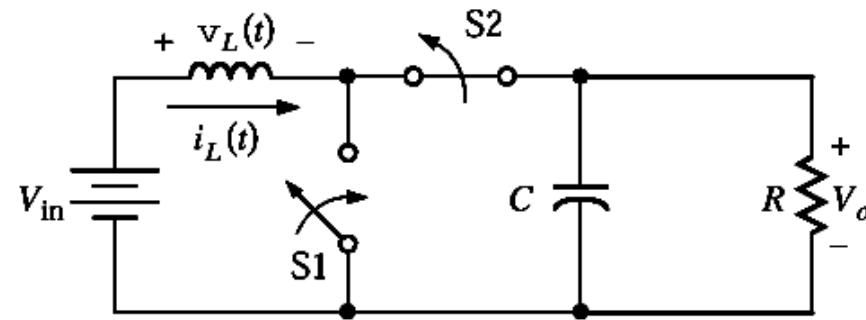BOOSTER "ON" PERIOD
Energy is stored in inductor.
Capacitor discharges




BOOSTER "OFF" PERIOD
Inductor releases energy.
Capacitor charges

Inductor current at the beginning of ON period MUST be the same than the current at the end of OFF period




THE "ON" CYCLE

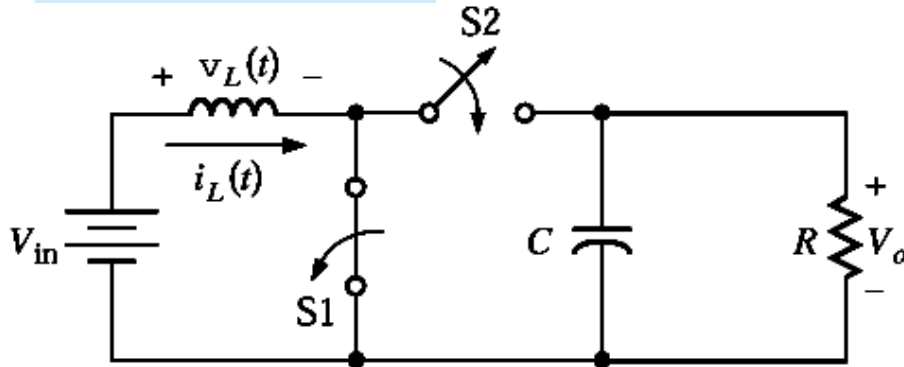

$$i_L(t_{on}) = i(0) + \frac{1}{L} \int_0^{t_{on}} v_L(x) dx = I_0 + \frac{V_{in}}{L} t_{on}$$

THE "OFF" CYCLE $t > t_{on}$

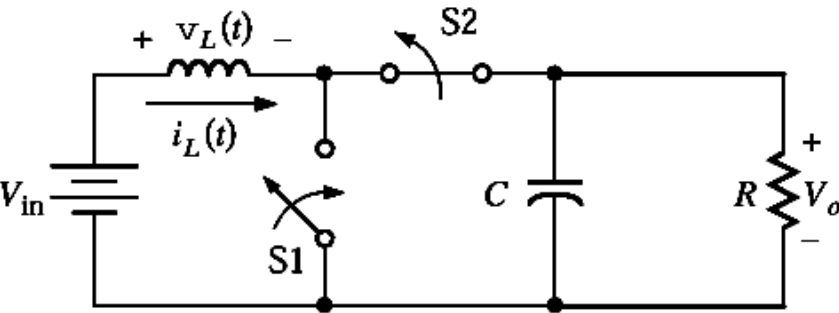

$$i_L(t_{on} + t_{off}) = i(t_{on}) + \frac{1}{L} \int_{t_{on}}^{t_{on} + t_{off}} v_L(x) dx$$

SIMPLIFYING ASSUMPTION: THE OUTPUT VOLTAGE (V_o) IS CONSTANT

$$v_L = V_{in} - V_o$$

$$I_0 = i(t_{on}) + \frac{V_{in} - V_o}{L} t_{off}$$

$$I_o = I_0 + \frac{V_{in}}{L} t_{on} + \frac{V_{in} - V_o}{L} t_{off}$$

$$V_o = \frac{t_{on} + t_{off}}{t_{off}} V_{in} \quad V_o > V_{in} \text{ (hence booster)}$$

Period: $T = t_{on} + t_{off}$

Duty cycle: $D = \frac{t_{on}}{T}$



$$V_o = V_{in} \frac{1}{1 - D}$$

By adjusting the duty cycle one can adjust the output voltage level



LEARNING BY DESIGN FIND C SUCH THAT $i(t)$ IS OVERDAMPED, AND SATISFIES:

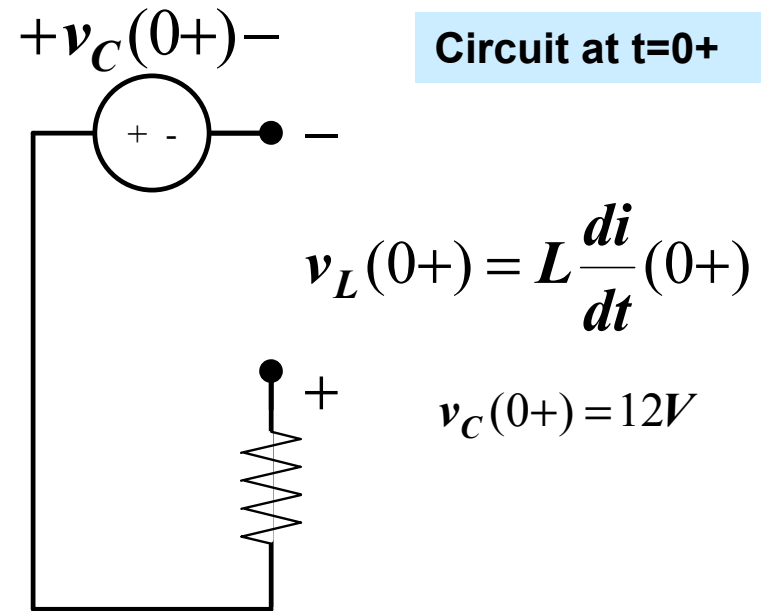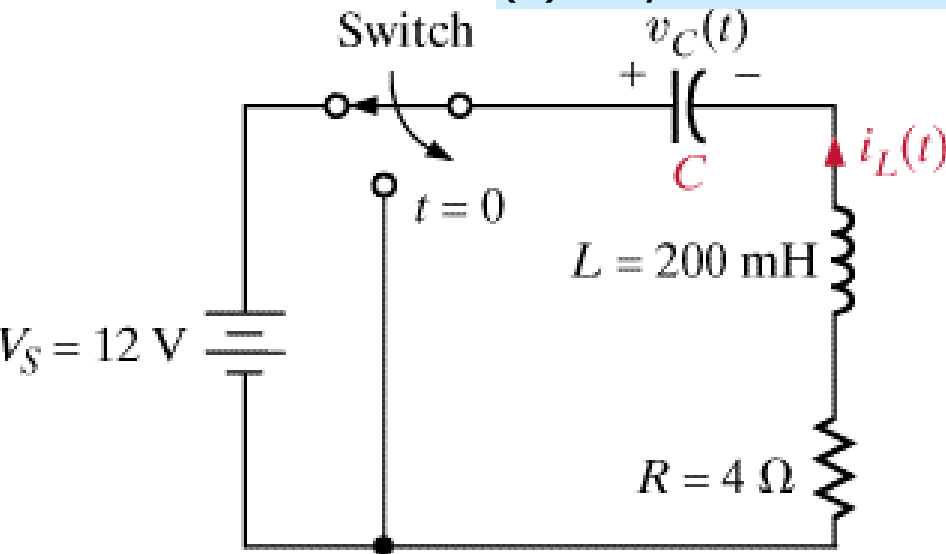- (1) Reaches 1A within 100ms;
- (2) Stays above 1A between 1s and 1.5s



AFTER SWITCHING WE HAVE RLC SERIES

$$\frac{d^2 i_L(t)}{dt^2} + \frac{R}{L} \frac{di_L(t)}{dt} + \frac{1}{LC} i_L(t) = 0$$

DESIRED RESPONSE: $i(t) = K_1 e^{-s_1 t} + K_2 e^{-s_2 t}; t > 0$

Ch. Eq.: $s^2 + 20s + 5/C = (s + s_1)(s + s_2) = 0$
 $\therefore s_1 + s_2 = 20; s_1 s_2 = 5/C$

INITIAL CONDITIONS:

$$i_L(0) = 0; v_L(0) = L \frac{di_L}{dt}(0) = 12$$

$$K_1 + K_2 = 0$$

$$-s_1 K_1 - s_2 K_2 = 60$$

For the initial conditions analyze circuit at $t=0+$. Assume the circuit was in steady state prior to the switching




$$i_L(t) = \frac{60}{s_2 - s_1} (e^{-s_1 t} - e^{-s_2 t})$$

NOW ONE CAN USE TRIAL AND ERROR OR CAN ATTEMPT TO ESTIMATE THE REQUIRED CAPACITANCE

IF FEASIBLE, GET AN IDEA OF THE FAMILY OF SOLUTIONS

Mesh plot
obtained with
MATLAB

CURRENT AS FUNCTION OF MODES

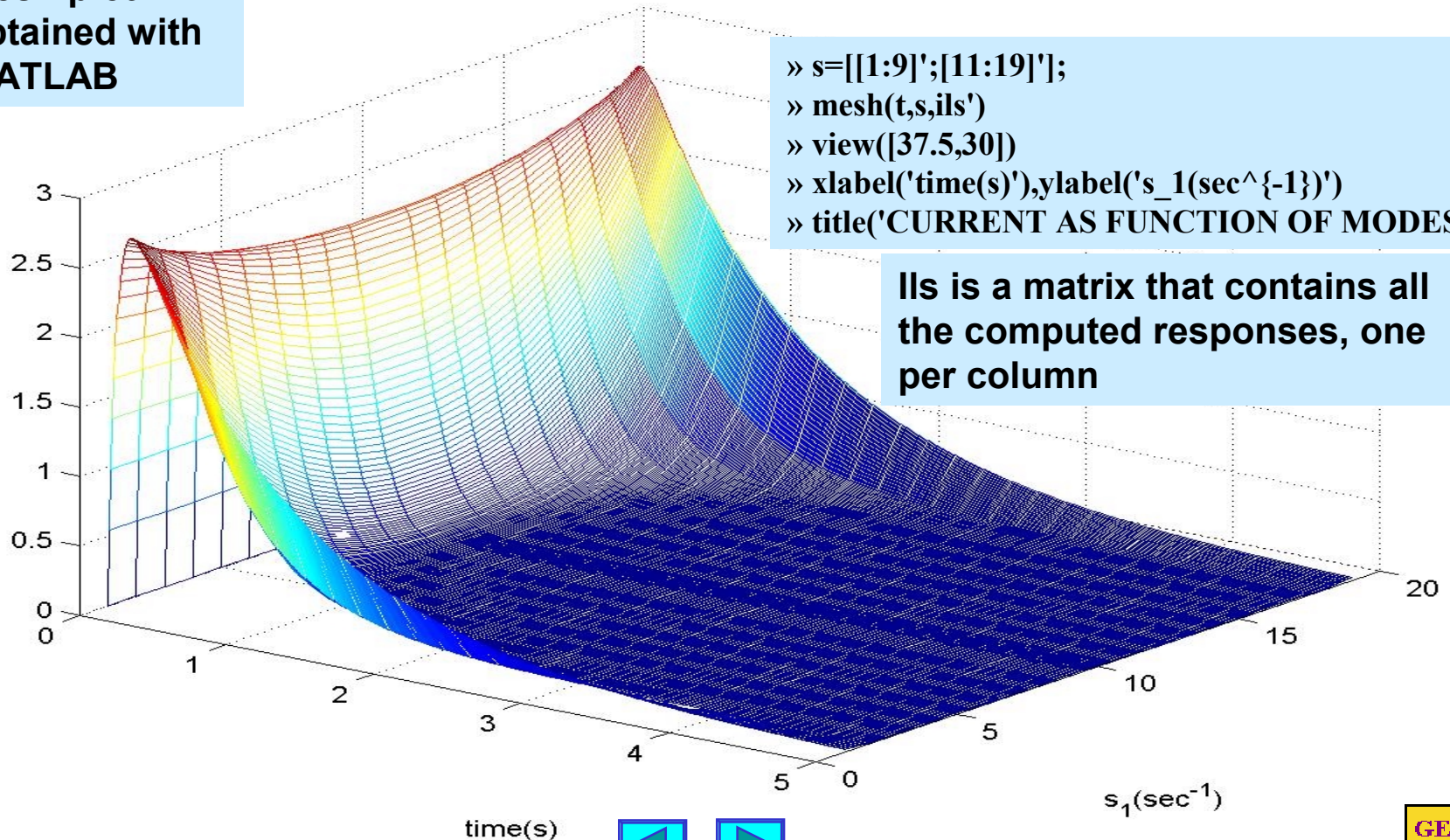

Estimate charge by estimating area under the curve

```
%example6p14.m
```

```
%displays current as function of roots in characteristic equation
```

```
% il(t)=(60/(s2-s1))*(exp(-s1*t)-exp(s2*t));
```

```
% with restriction s1+s2=20, s1~s2.
```

```
t=linspace(0,5,500)'; %set display interval as a column vector
```

```
ils=[]; %reserve space to store curves
```

```
for s1=1:19
```

```
    s2=20-s1;
```

```
    if s1~=s2
```

```
        il=(60/(s2-s1))*(exp(-s1*t)-exp(-s2*t));
```

```
        ils=[ils il]; %save new trace as a column in matrix
```


```
    end
```

```
end
```

```
%now with one command we plot all the columns as functions of time
```

```
plot(t,ils), grid, xlabel('Time(s)'),ylabel('i(A)')
```
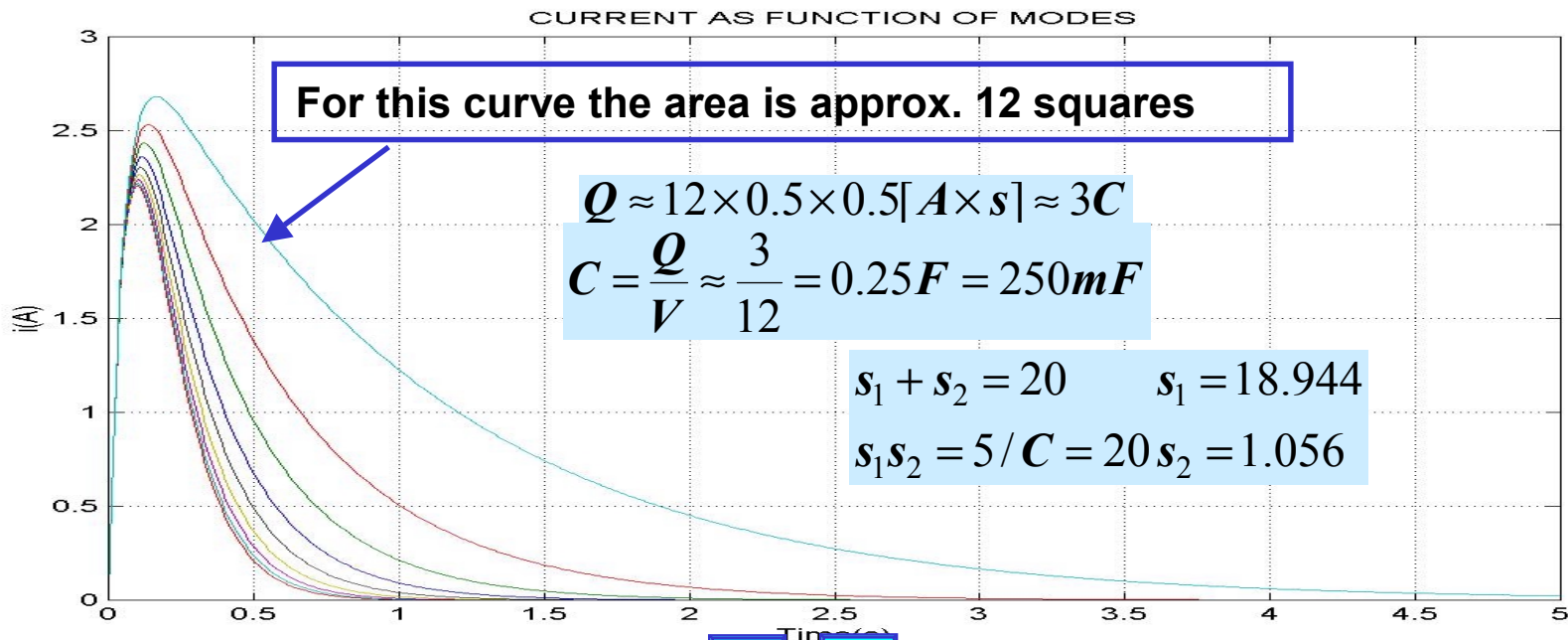
```
title('CURRENT AS FUNCTION OF MODES')
```



```
%verification
```


```
s1=18.944;
```

```
s2=20-s1;
```

```
il=(60/(s2-s1))*(exp(-s1*t)-exp(-s2*t));
```

```
plot(t,il,'rd',t,il,'b'), grid, xlabel('time(s)'), ylabel('i(A)')
```

```
title('VERIFICATION OF DESIGN')
```

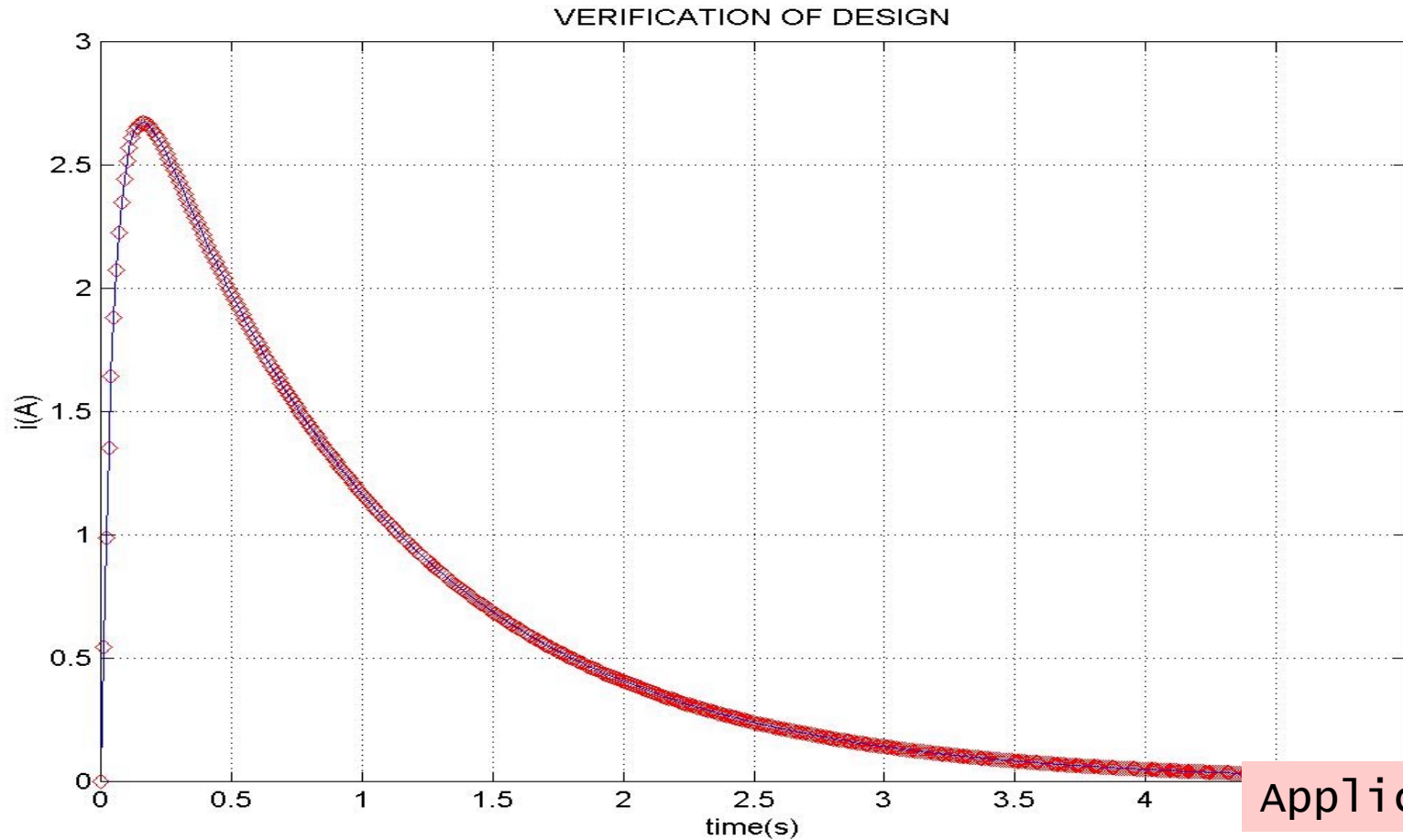

Applications

