

Answers to Selected Problems

CHAPTER 1

1.1 $I = 2 \text{ A}$

1.7 $W = 1440 \text{ J}$

1.11 (a) 5 V, + top

(b) 5 V, + bottom

(c) 5 V, + bottom

(d) 5 V, + top

1.14 (a) $I = -2 \text{ A}$

(b) $V_1 = -12 \text{ V}$

1.18 (a) $P_1 = 12 \text{ W}$

$P_2 = 24 \text{ W}$

(b) $P_1 = -72 \text{ W}$

$P_2 = 48 \text{ W}$

1.21 $P_2 = 48 \text{ W absorbed}$

1.24 (a) $P_1 = 16 \text{ W absorbed}$

$P_2 = 8 \text{ W absorbed}$

$P_{12\text{V}} = 24 \text{ W supplied}$

(b) $P_1 = 40 \text{ W absorbed}$

$P_2 = 24 \text{ W absorbed}$

$P_3 = 16 \text{ W supplied}$

$P_{24\text{V}} = 48 \text{ W supplied}$

1.28 $P_1 = 48 \text{ W absorbed}$

$P_2 = 48 \text{ W absorbed}$

$P_3 = 56 \text{ W absorbed}$

$P_{36\text{V}} = 144 \text{ W supplied}$

$P_{\text{D.S.}} = 8 \text{ W}$

CHAPTER 2

2.2 $R_x = 5 \text{ k}\Omega$

2.6 $G_x = 200 \text{ }\mu\text{S}$

2.11 $I_1 = 6 \text{ mA}$

$I_2 = 3 \text{ mA}$

2.15 $I_x = -3 \text{ mA}$

2.19 $V_{da} = -9 \text{ V}$

$V_{be} = 9 \text{ V}$

2.25 $V_x = 10 \text{ V}$

2.30 $V_S = -2 \text{ V}$

2.39 $V_o = 36 \text{ V}$

2.45 $I_L = 2.4 \text{ mA}$

2.49 $R_{AB} = 12 \text{ k}\Omega$

2.53 $R_{AB} = 2 \text{ k}\Omega$

2.57 $I_{\text{max}} = 18.22 \text{ mA}$ $P_{\text{max}} = 182.2 \text{ mW}$

$I_{\text{min}} = 17.51 \text{ mA}$ $P_{\text{min}} = 175.1 \text{ mW}$

2.64 $I_1 = -3 \text{ mA}$

2.68 $I_o = 0.33 \text{ mA}$

2.72 $V_S = -92.4 \text{ V}$

2.77 $V_o = -12 \text{ V}$

2.82 $V_o = 3 \text{ V}$

2.87 $V_S = 41 \text{ V}$

2.92 $V_S = 30 \text{ V}$

2.98 $I_o = -4 \text{ mA}$

2.103 $g = 4$

2.109 $I_o = 2 \text{ A}$

2.113 $I_o = 0.67 \text{ A}$

CHAPTER 3

3.1 $I_o = 1 \text{ mA}$

3.5 $I_o = 0.6 \text{ mA}$

3.9 $V_o = -3.6 \text{ V}$

3.14 $I_o = -1 \text{ mA}$

3.20 $V_A = 2.5 \text{ V}$

$V_B = -0.33 \text{ V}$

A2 ANSWERS TO SELECTED PROBLEMS

3.27 $V_o = 2 \text{ V}$

3.32 $V_o = 5 \text{ V}$

3.36 $V_1 = 11.5 \text{ V}$

$V_2 = 12 \text{ V}$

$V_3 = 12 \text{ V}$

$V_4 = 6.5 \text{ V}$

3.41 $V_o = 8 \text{ V}$

3.46 $V_o = 1.33 \text{ V}$

3.49 $V_o = 15 \text{ V}$

3.54 $V_o = -5 \text{ V}$

3.59 $I_o = 2.88 \text{ mA}$

3.63 $V_o = 6.67 \text{ V}$

3.69 $I_o = 2.67 \text{ mA}$


3.73 $I_o = 1.64 \text{ mA}$

3.79 $V_o = 7.57 \text{ V}$

3.84 $V_o = 6 \text{ V}$

3.89 $V_o = -3.33 \text{ V}$

3.95 $I_o = 2.88 \text{ mA}$

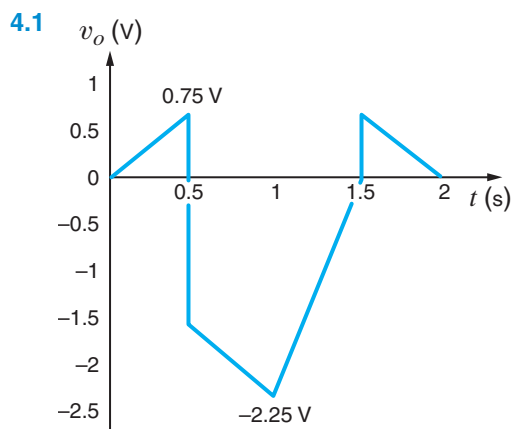CHAPTER 4

4.9 $\frac{V_o}{V_{in}} = 7.06$

$I_o = 606 \mu\text{A}$

4.12 $I_1 = 1 \text{ mA}$ $I_2 = 0 \text{ A}$ $I_3 = 1 \text{ mA}$

4.17 (a) $V_o = 4V_1 - V_2$

(b) $V_o = 2 \text{ V}$

(c) $4 \text{ V} \leq V_2 \leq 28 \text{ V}$

4.21 $\frac{i_o}{v_1} = -\frac{1}{R_f}$

4.25 $V_o = 0 \text{ V}$

4.30 $V_o = -11.2 \text{ V}$

4.35 $V_o = -11.43 \text{ V}$

4.38 $v_o = v_1 \left[1 + \frac{R_3}{R_2} + \frac{R_3}{R_4} \right] \left(-\frac{R_2}{R_1} \right)$

CHAPTER 5

5.1 $I_o = 1.14 \text{ mA}$

5.5 $I_o = -3.2 \text{ mA}$

5.9 $I_o = -2 \text{ mA}$

5.14 $V_o = 14.4 \text{ V}$

5.19 $I_o = 0.909 \text{ mA}$

5.22 $I_o = 1.6 \text{ mA}$

5.28 $V_o = 4.8 \text{ V}$

5.33 $I_o = 5 \text{ mA}$

5.37 $V_o = 65.79 \text{ V}$

5.44 $I_o = 1.6 \text{ mA}$

5.50 $I_o = 2.57 \text{ mA}$

5.55 $I_o = 0.909 \text{ mA}$

5.59 $R_{Th} = 400 \Omega$

5.65 $V_o = -0.316 \text{ V}$

5.70 $V_o = -5 \text{ V}$

5.76 $P_{2 \text{ mA}} = 12 \text{ mW}$

5.81 $V_o = 2 \text{ V}$

5.85 $I_o = -0.5 \text{ mA}$

5.94 $I_o = 1.6 \text{ mA}$

5.98 $R_L = 99.0 \Omega$

CHAPTER 6

6.3 $v = 40 \text{ V}$

6.6 $i(t) = 9.23 \cos 377t \text{ A}$


6.9
$$v(t) = \begin{cases} 0 \text{ V} & t < 0 \\ 100t \text{ V} & 0 < t < t_1 \\ 0.2 \text{ V} & t > t_1 \end{cases}$$

6.13
$$i(t) = \begin{cases} 0 & t < 0 \\ -12 \text{ mA} & 0 < t < t_1 \\ 0 & t_1 < t < t_2 \\ 8 \text{ mA} & t_2 < t < t_3 \\ 0 & t > t_3 \end{cases}$$

6.17
$$v(t) = \begin{cases} 0 & t < 0 \\ 2500t^2 \text{ V} & 0 < t < t_1 \\ 4 \text{ V} & t > t_1 \end{cases}$$

6.22 (a) $v(t) = 75.4 \cos 377t \text{ V}$

(b) $w(t) = 0.2 \sin^2 377t \text{ J}$

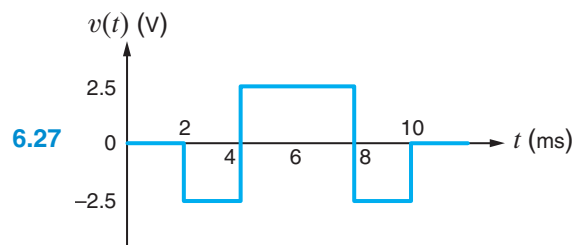

6.33
$$i(t) = \begin{cases} 0 \text{ A} & t < 0 \\ t/2 \text{ A} & 0 \leq t \leq 2 \text{ ms} \\ (3 \times 10^{-3} - t) \text{ A} & 2 \text{ ms} \leq t \leq 3 \text{ ms} \\ 0 \text{ A} & t \geq 3 \text{ ms} \end{cases}$$

6.38 (a) $L = 10 \text{ mH} \pm 10\%$ $9 \text{ mH} \leq L \leq 11 \text{ mH}$

(b) $L = 2 \text{ nH} \pm 5\%$ $1.9 \text{ nH} \leq L \leq 2.1 \text{ nH}$

(c) $L = 68 \text{ } \mu\text{H} \pm 10\%$ $61.2 \text{ } \mu\text{H} \leq L \leq 74.8 \text{ } \mu\text{H}$

6.43 $P_{R_2} = 21.33 \text{ W}$ $w_C = 144 \text{ J}$

6.49 $V_2 = 8 \text{ V}$ $V_1 = 4 \text{ V}$

6.54 $C_T = 2 \text{ } \mu\text{F}$

6.60 $C_{\text{eq}} = 3.18 \text{ } \mu\text{F}$


6.67 $L_{AB} = 6 \text{ mH}$

6.73 $v_o(t) = 3.81 \cos(377t) \text{ V}$


CHAPTER 7

7.3 $v_C(t) = 12 - 8e^{-\frac{t}{0.6}} \text{ V}$

7.8 $v_o(t) = 4 + 50e^{-7.5t} \text{ V}$

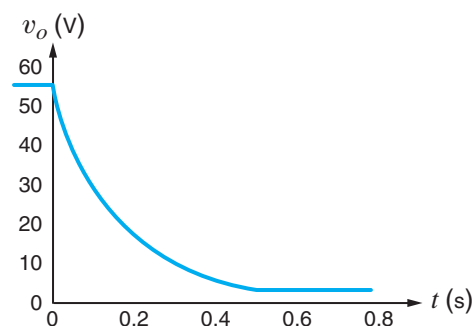

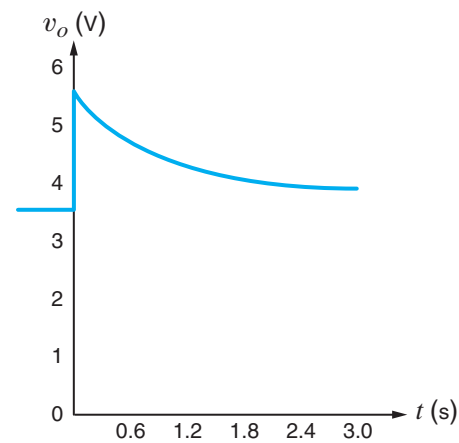
7.12 $v_o(t) = 4 + 1.6e^{-\frac{t}{0.6}} \text{ V}$



A4 ANSWERS TO SELECTED PROBLEMS

7.19 $i_o(t) = 0.67e^{-5t}$ A

7.23 $i_o(t) = 0.375 - 1.125e^{-8t}$ A

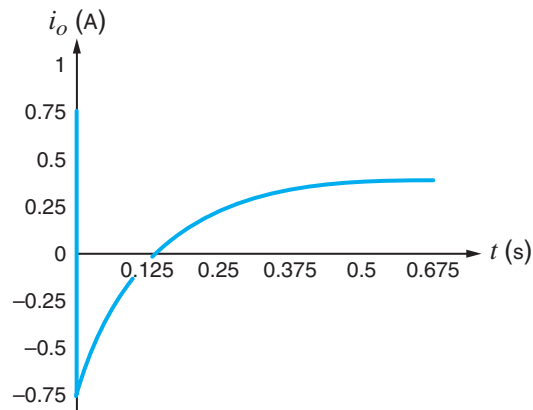

7.28 $i_o(t) = 2 + 0.5e^{-3.75t}$ mA

7.33 $v_o(t) = 4.36e^{-2.73t}$ V

7.37 $i_o(t) = 3 + 0.33e^{-1.67t}$ mA

7.41 $i_o(t) = 2.4 - 2.4e^{-2.5 \times 10^5 t}$ mA

7.47 $v_o(t) = 12 - 3e^{-6t}$ V

7.52 $i(t) = -5 + 2.5e^{-4t}$ A

7.57 $v_o(t) = 16 - 2.8e^{-1.5t}$ V

$$7.63 \quad v_o(t) = \begin{cases} 8 - 8e^{-1.25t} \text{ V} & 0 \leq t \leq 1 \\ 5.71e^{-1.25(t-1)} \text{ V} & t > 1 \end{cases}$$

7.68 $v_R(0^+) = -8$ V

$i_2(0^+) = 0$ A

$i_1(\infty) = 0$ A

7.72 $L = 2$ H

$R_1 = 3 \Omega$

$R_2 = 5 \Omega$

7.75 (a) $s^2 + 2s + 5 = 0$


(b) $s_{1,2} = \frac{-2 \pm \sqrt{4 - 20}}{2} = -1 \pm j2$ rad/s

(c) underdamped!

$$v_1(t) = e^{-t}[A_1 \cos 2t + A_2 \sin 2t]$$

7.80 $v(t) = e^{-4t}[10 \cos 2t + 40 \sin 2t]$ V

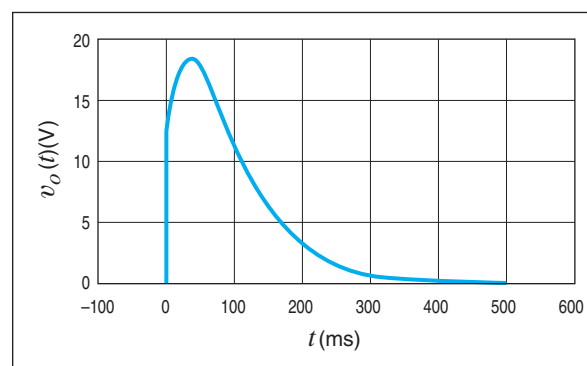7.85 $v_o(t) = 12e^{-20t} + 720te^{-20t}$ V



7.90 $i(t) = (4.04e^{-T_1 t} - 1.54e^{T_1 t})$ A $T_1 = 0.08$ s
 $T_2 = 12.42$ s

7.95 $i(t) = e^{-3t}[3 \cos t + 5.4 \sin t]$ A

CHAPTER 8

8.1 $f = 63.7$ Hz $T = 15.7$ ms

8.5 (a) $i = v/R$ $i(t) = 5 \cos(377t + 180^\circ)$ A

$\mathbf{I} = 5 \angle 180^\circ$ A

(b) $i(t) = 6 \sin(377t + 45^\circ) = 6 \cos(377t - 45^\circ)$ A

$\mathbf{I} = 6 \angle -45^\circ$


8.9 $\mathbf{Z} = 1.00 + j3.77 \Omega$

8.14 $\mathbf{Z} = 2.83 \angle 16.9^\circ \Omega$

8.18 $v(t) = 5.16 \cos(377t + 45.1^\circ)$ V

8.23 $L = 10$ mH

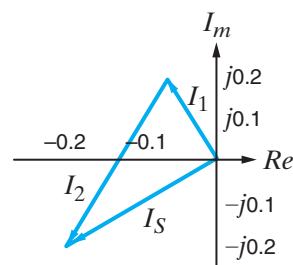8.29 $v_o(t) = 7.08 \cos(10^4 t + 36.8^\circ)$ V



8.36 $\mathbf{V}_o = 45 \angle -23.1^\circ$ V

8.41 $\mathbf{I}_o = 2.83 \angle 45^\circ$ A

8.46 $\mathbf{Z} = -0.508 + j0.586 \Omega$

$\mathbf{Z} = 0.776 \angle 130.9^\circ \Omega$

8.52 $\mathbf{V}_o = 3.58 \angle 153.4^\circ$ V

8.58 $\mathbf{V}_o = 4.56 \angle 37.9^\circ$ V

8.64 $\mathbf{V}_o = 5.55 \angle 86.8^\circ$ V

8.69 $\mathbf{V}_o = 2.53 \angle 71.6^\circ$ V

8.73 $\mathbf{V}_o = 4.71 \angle -98.1^\circ$ V

8.77 $\mathbf{I}_o = 2 \angle -36.9^\circ$ A

8.82 $\mathbf{V}_o = 5.55 \angle 86.8^\circ$ V

8.88 $\mathbf{V}_{oc} = -4 + j4$ V $\mathbf{Z}_{Th} = 2.24 \angle 117^\circ \Omega$

8.93 $\mathbf{V}_o = 4 \angle 90^\circ$ V

8.98 $\mathbf{V}_o = 37.6 \angle -60.7^\circ$ V

8.103 $\mathbf{I}_o = 17.7 \angle -137^\circ$ A

CHAPTER 9

$$9.2 \quad v(t) = 20 \cos(\omega t + 66.9^\circ) \text{ V}$$

$$p(t) = 40 \cos(2\omega t + 96.9^\circ) + 32.0 \text{ W}$$

$$9.8 \quad P = 4.31 \text{ W}$$

$$9.13 \quad P_{1\Omega} = 2.25 \text{ W}$$

$$9.18 \quad P_{I_s} = 0.660 \text{ W supplied}$$

$$P_{V_s} = 0.394 \text{ W supplied}$$

$$9.23 \quad P_{R_L} = 9.92 \text{ W}$$

$$9.28 \quad \mathbf{Z}_L = 2 + j2 \Omega$$

$$P_L = 1.05 \text{ W}$$

$$9.34 \quad \mathbf{Z}_L = 2.8 + j0.4 \Omega$$

$$P_L = 1.32 \text{ W}$$

$$9.39 \quad \mathbf{Z}_L = 4 + j1 \Omega$$

$$P_L = 5.00 \text{ W}$$

$$9.43 \quad V_{\text{rms}} = 1.87 \text{ V}$$

$$9.49 \quad I_{\text{rms}} = 3.27 \text{ A}$$

$$9.53 \quad \text{pf} = 0.833$$

$$9.57 \quad \text{pf} = 0.65 \text{ lagging}$$

$$9.63 \quad \mathbf{V}_S = 303 \angle 11.1^\circ \text{ V}_{\text{rms}}$$

$$\text{pf}_S = 0.73 \text{ lagging}$$

$$9.67 \quad \text{pf}_S = 0.72 \text{ lagging}$$

$$\mathbf{S}_{V_s} = 46.3 \angle 43.8^\circ \text{ kVA}$$

$$9.73 \quad C = 563 \mu\text{F}$$

$$9.79 \quad |\mathbf{I}_{\text{man}}| = \begin{cases} 238 \text{ mA} & \text{dry skin} \\ 14.4 \text{ A} & \text{wet skin} \end{cases}$$

CHAPTER 10

$$10.5 \quad \frac{V_o}{V_s} = 0.140 \angle 24.8^\circ$$

$$10.11 \quad V_o = 10.15 \angle 10.8^\circ \text{ V}$$

$$10.15 \quad V_o = 2.17 \angle 5.19^\circ \text{ V}$$

$$10.18 \quad I_o = 3.25 \angle 66.0^\circ \text{ A}$$

$$10.25 \quad V_o = 1.24 \angle -120^\circ \text{ V}$$

$$10.31 \quad V_o = 12.2 \angle 15.0^\circ \text{ V}$$

$$10.36 \quad V_o = 2.5 \angle 36.9^\circ \text{ V}$$

$$10.40 \quad \mathbf{Z}_{\text{in}} = 4.6 + j3.2 \Omega$$

$$10.47 \quad w(t = 1 \text{ ms}) = 94.1 \mu\text{J}$$

$$10.52 \quad V_1 = 5.36 \angle 3.4^\circ \text{ V}$$

$$V_2 = nV_1 = 10.72 \angle 3.4^\circ \text{ V}$$

$$I_2 = -I_1/n = 1.90 \angle 138^\circ \text{ A}$$

$$10.57 \quad I_1 = -1.84 \angle 0^\circ \text{ A} \quad V_1 = 6.48 \angle 0^\circ \text{ V}$$

$$I_2 = 0.46 \angle 0^\circ \text{ A} \quad V_2 = 25.9 \angle 0^\circ \text{ V}$$

$$10.63 \quad V_o = 1.80 \angle -140^\circ \text{ V}$$

$$10.69 \quad V_s = 14.14 \angle 165^\circ \text{ V}$$

$$10.73 \quad V_s = 30.9 \angle 153^\circ \text{ V}$$

CHAPTER 11

$$11.2 \quad V_{an} = 100 \angle 45^\circ \text{ V rms}$$


$$V_{bn} = 100 \angle -75^\circ \text{ V rms}$$

$$V_{cn} = 100 \angle 165^\circ \text{ V rms}$$

$$V_{ab} = 100\sqrt{3} \angle 75^\circ \text{ V rms} = 171 \angle 75^\circ \text{ V rms}$$

$$V_{bc} = 171 \angle -45^\circ \text{ V rms}$$
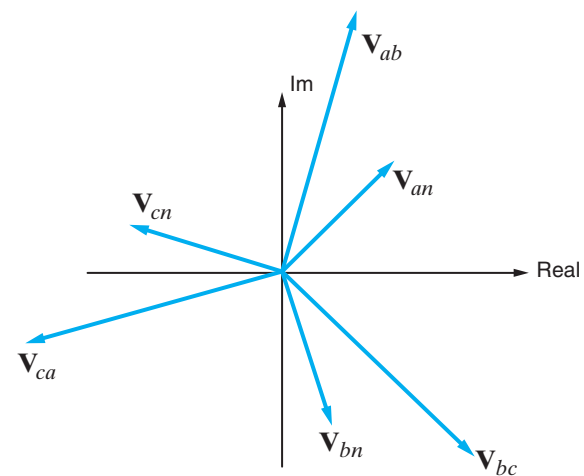
$$V_{ca} = 171 \angle -165^\circ \text{ V rms}$$



A6 ANSWERS TO SELECTED PROBLEMS

$$11.9 \mathbf{I}_{aA} = 2.00 \angle -73.6^\circ \text{ A rms}$$

$$\mathbf{I}_{bB} = 2.00 \angle 166^\circ \text{ A rms}$$

$$\mathbf{I}_{cC} = 2.00 \angle 46.4^\circ \text{ A rms}$$

$$11.13 \mathbf{Z} = 3.5 - j1 \Omega$$

$$11.16 \mathbf{V}_{ab} = 217 \angle 40^\circ \text{ V rms}$$

$$11.23 \mathbf{Z}_L = 10 + j12 \Omega$$

$$11.29 |\mathbf{V}_{AB}| = 199 \text{ V rms}$$

$$11.34 \mathbf{V}_{AB} = 208 \angle 60^\circ \text{ V rms}$$

$$11.37 \mathbf{V}_{an} = 103 \angle 43.7^\circ \text{ V rms}$$

$$\mathbf{V}_{bn} = 103 \angle -76.3^\circ \text{ V rms}$$

$$\mathbf{V}_{cn} = 103 \angle 163.7^\circ \text{ V rms}$$

$$11.41 \mathbf{I}_{AN1} = 9.38 \angle -4.39^\circ \text{ A rms}$$

$$\mathbf{I}_{BN1} = 9.38 \angle -124.4^\circ \text{ A rms}$$

$$\mathbf{I}_{CN1} = 9.38 \angle 115.6^\circ \text{ A rms}$$

$$11.47 \mathbf{Z}_L = 12 \angle 25^\circ \Omega$$

$$11.54 \mathbf{S}_3 = 18.4 \angle 49.4^\circ \text{ kVA}$$

$$11.59 \text{ pf}_{\text{new}} = 0.966 \text{ lagging}$$


$$11.63 C = 16.4 \mu\text{F}$$

CHAPTER 12

$$12.1 \mathbf{Z} = R \left[\frac{s^2 + \frac{s}{RC} + \frac{1}{LC}}{s^2 + \frac{1}{LC}} \right]$$


$$12.5 \mathbf{Z}_i = \frac{1.8s + 1}{s}$$
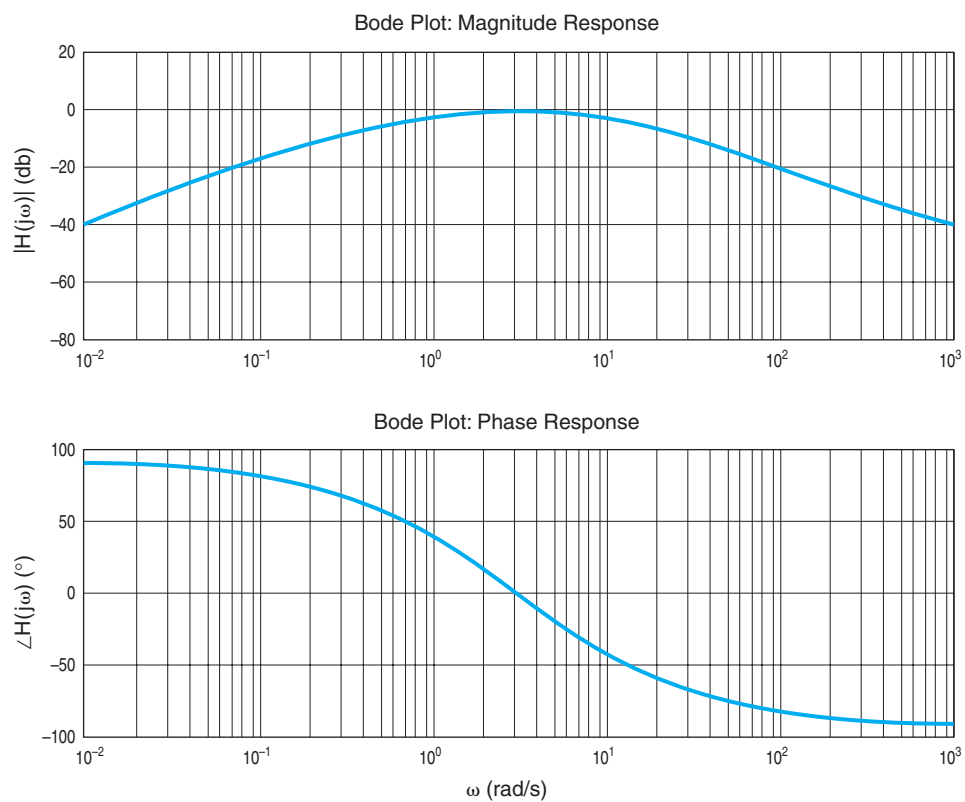
$$12.9 \mathbf{H}(j\omega) = \frac{10(j\omega)}{(j\omega + 1)(j\omega + 10)}$$




$$12.13 \quad \mathbf{H}(j\omega) = \frac{100(j\omega)}{(j\omega + 1)(j\omega + 10)(j\omega + 50)}$$


$$|\mathbf{H}|_{\omega=\frac{1}{100}} \approx 2 \times 10^{-3} = -54 \text{ dB}$$

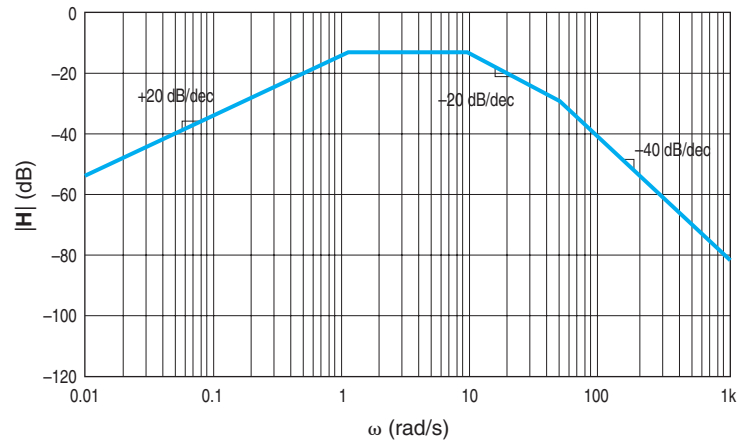

$$12.17 \quad |\mathbf{G}|_{\omega=0.1} \approx \frac{10(0.1)}{1(10)^2} = \frac{1}{100} = -40 \text{ dB}$$

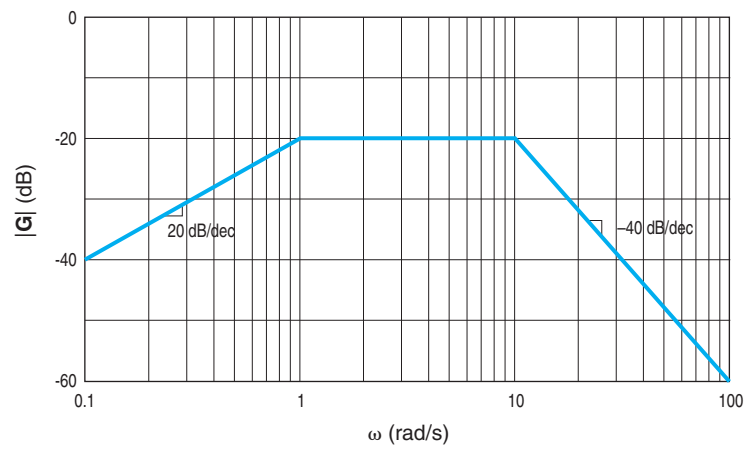

$$12.23 \quad |\mathbf{G}|_{\omega=0.1} \approx \frac{10(2)(100)}{(0.1)(100)} = 200 = 46 \text{ dB}$$

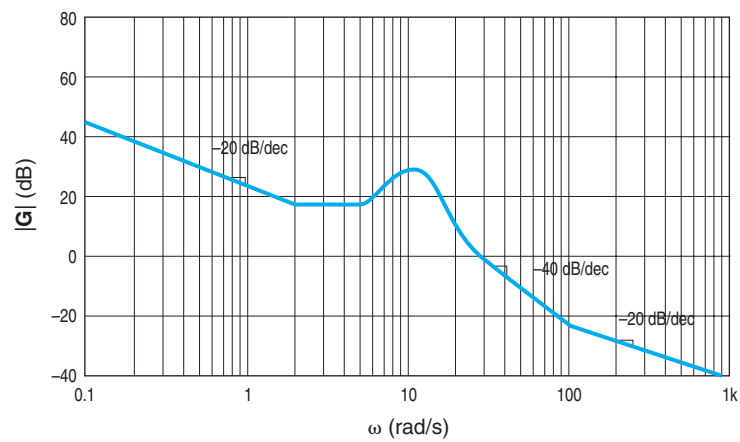

A8 ANSWERS TO SELECTED PROBLEMS

$$12.29 \quad \mathbf{H}(j\omega) = \frac{5.33 \times 10^4(j\omega + 1)(j\omega + 120)}{(j\omega + 10)(j\omega + 80)^2}$$

$$12.34 \quad \mathbf{G}(j\omega) = \frac{288(j\omega + 100)^2}{j\omega(j\omega + 900)[(j\omega)^2 + j4\omega + 400]}$$

$$12.39 \quad \omega_o = 7.07 \text{ krad/s}$$

$$Q = 14.14$$

$$\omega_{\max} = 7.06 \text{ krad/s}$$

$$|V_{o\max}| = 84.9 \text{ V}$$

$$12.44 \quad Q = 3.33$$

$$C = 100 \text{ } \mu\text{F}$$

$$\text{BW} = 300 \text{ rad/s}$$

$$12.49 \quad R = 2000 \text{ } \Omega$$

$$C = 25 \text{ } \mu\text{F}$$

$$L = 10 \text{ nH}$$

$$12.53 \quad L_{\text{new}} = 50 \text{ } \mu\text{H}$$

$$C_{\text{new}} = 12.5 \text{ } \mu\text{F}$$

$$R = 2 \text{ } \Omega$$

12.57 Filter is highpass

$$12.63 \quad \text{(a)} \quad I_{ABC} = 50 \text{ } \mu\text{A}$$

$$R_G = 100 \text{ k}\Omega$$

$$\text{(b)} \quad 0.952 \text{ mS} \leq g_m \leq 1.053 \text{ mS}$$

$$12.69 \quad \text{(a)} \quad R_G = 100 \text{ M}\Omega$$

$$\text{(b)} \quad R = 500 \text{ } \Omega$$

12.75 Arbitrarily select $C = 1 \text{ nF}$, yields $R = 6.87 \text{ k}\Omega$

CHAPTER 13

$$13.1 \quad \mathcal{L}[f(t)] = e^{-(s+a)}$$

$$13.5 \quad \mathbf{F}(s) = e^{-(s+a)} \left\{ \frac{\omega \cos \omega}{(s+a)^2 + \omega^2} + \frac{(s+a) \sin \omega}{(s+a)^2 + \omega^2} \right\}$$

$$13.8 \quad \mathbf{F}(s) = \frac{e^{-(s+a)}}{s+1}$$

$$13.12 \quad \text{(a)} \quad f(t) = \frac{1}{6} [1 + 3e^{-2t} - 4e^{-3t}]u(t)$$

$$\text{(b)} \quad f(t) = \frac{1}{2} [1 - 2e^{-t} + 3e^{-2t}]u(t)$$

$$13.16 \quad \text{(a)} \quad f(t) = 10e^{-t} \cos(t - 90^\circ)u(t)$$

$$\text{(b)} \quad f(t) = 10e^{-2t} \cos(t)u(t)$$

$$13.21 \quad \text{(a)} \quad f(t) = \left[-\frac{1}{2}e^{-2t} + 1.58e^{-t} \cos(t - 18.4^\circ) \right]u(t)$$

$$\text{(b)} \quad f(t) = [\delta(t) - e^{-2t} \cos(t + 90^\circ)]u(t)$$

$$13.27 \quad \text{(a)} \quad f(t) = [te^{-t} - 3e^{-t} + 4e^{-2t}]u(t)$$

$$\text{(b)} \quad f(t) = \frac{1}{16} [t - 4te^{-4t} - e^{-4t}]u(t)$$

$$13.32 \quad f(t) = 2e^{-8(t-1)} - e^{-4(t-1)}u(t-1)$$

$$13.37 \quad y(t) = [e^{-t} - e^{-2t}]u(t)$$

13.41 Initial values

$$\text{(a)} \quad \lim_{t \rightarrow 0} f(t) = 2$$

$$\text{(b)} \quad \lim_{t \rightarrow 0} f(t) = 2$$

$$\text{(c)} \quad \lim_{t \rightarrow 0} f(t) = 2$$

Final values

$$\text{(a)} \quad \lim_{t \rightarrow \infty} f(t) = 4$$

$$\text{(b)} \quad \lim_{t \rightarrow \infty} f(t) = 0$$

$$\text{(c)} \quad \lim_{t \rightarrow \infty} f(t) = 0$$

$$13.45 \quad i(t) = 2e^{-4.5t}u(t) \text{ A}$$

$$13.48 \quad v_o(t) = 2.67e^{-1.67t}u(t) \text{ V}$$

CHAPTER 14

$$14.1 \quad \mathbf{Z}_{(s)} = \frac{6s + 8}{6s^2 + 16s + 11}$$

$$14.6 \quad v_o(t) = [4\sqrt{2}e^{-t} \cos(t - 45^\circ)]u(t) \text{ V}$$

$$14.11 \quad v_o(t) = [2\sqrt{2}e^{-t} \cos(t - 45^\circ)]u(t) \text{ V}$$

$$14.16 \quad v_o(t) = [2(1 - e^{-t})]u(t) \text{ V}$$

$$14.21 \quad v_o(t) = [4 - 5e^{-t} + 2e^{-2t}]u(t) \text{ V}$$

$$14.25 \quad v_o(t) = [1.5(1 - e^{-4t})]u(t) \text{ V}$$

$$14.30 \quad v_o(t) = 9.6e^{-t}u(t) \text{ V}$$

$$14.35 \quad v_o(t) = 1.15[e^{-0.42t} - e^{-1.58t}]u(t) \text{ V}$$

$$14.38 \quad v_o(t) = 12e^{-2t}u(t) \text{ V}$$

$$14.42 \quad v_o(t) = \left(4 - \frac{4}{3}e^{-4t} \right)u(t) - \left(4 - \frac{4}{3}e^{-4(t-1)} \right)u(t-1) \text{ V}$$

$$14.45 \quad \frac{V_o}{V_i} = \frac{s+1}{14s+6}$$

$$14.51 \quad \frac{V_o}{V_s} = \frac{-s}{s^2 + 2s + 2} \quad \text{Roots at } s = \frac{-2 \pm \sqrt{4 - 8}}{2} = -1 \pm j1 \quad \left\{ \begin{array}{l} \text{Complex conjugate poles.} \\ \text{Network is} \\ \text{underdamped!} \end{array} \right.$$

$$14.54 \quad \omega_o = \sqrt{40} \text{ rad/s}$$

$$2\zeta\omega_o = 22 \Rightarrow \zeta = 1.74 \quad \text{overdamped}$$

$$14.59 \quad v_o(t) = 4.71 \cos(t - 45^\circ) \text{ V}$$

$$14.63 \quad v_o(t) = 5.22 \cos(2t + 97.8^\circ) \text{ V}$$

CHAPTER 15

$$15.3 \quad f(t) = \sum_{\substack{n=-\infty \\ n \text{ odd}}}^{\infty} \frac{2}{jn\pi} e^{jn\omega_o t}$$

$$15.8 \quad v(t) = \frac{2}{\pi} \sum_{\substack{n=1 \\ n \text{ odd}}}^{\infty} \frac{3}{n} \sin(n\pi t/2) - \frac{1}{n} \cos(n\pi t/2) \text{ V}$$

$$15.13 \quad a_n = \frac{4}{(n\pi)^2} (\cos(n\pi/2) - 1) + \frac{4}{n\pi} \sin(n\pi/2)$$

$$a_o = -\frac{1}{4} \quad b_n = 0$$

$$15.18 \quad v(t) = -\frac{\pi}{4} + \sum_{n=1}^{\infty} \frac{1}{\pi n^2} (\cos(n\pi) - 1) \cos(nt) + \frac{1}{n} (1 - 2 \cos(n\pi)) \sin(nt) \text{ V}$$

$$15.24 \quad f(t) = -4 \sin(20\pi t) - 5 \sin(40\pi t) - 3 \sin(60\pi t) - 2 \sin(80\pi t) - \sin(100\pi t)$$

$$15.29 \quad v_o(t) = \frac{1}{4} + 0.285 \cos(t + 26.6^\circ) +$$

$$0.023 \cos(t - 49^\circ) \text{ V}$$

$$15.32 \quad P = 127.6 \text{ W}$$

$$15.37 \quad v_o(t) = 1.27 \cos(4t - 58^\circ) \text{ V}$$

$$15.41 \quad w = 0.106 \text{ J}$$

CHAPTER 16

$$16.1 \quad (\text{a}) \quad y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{1}{Z_L} \quad y_{21} = -\frac{1}{Z_L}$$


$$y_{12} = -\frac{1}{Z_L} \quad y_{22} = \frac{1}{Z_L}$$

$$(\text{b}) \quad z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = Z_L \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = Z_L$$

$$z_{12} = Z_L \quad z_{22} = Z_L$$

$$16.7 \quad y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{1}{Z_1} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{1}{Z_2}$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \frac{\gamma}{Z_2} \quad y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = 0$$

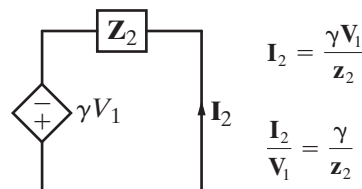For y_{21} 

$$I_2 = \frac{\gamma V_1}{Z_2}$$

$$\frac{I_2}{V_1} = \frac{\gamma}{Z_2}$$

$$16.11 \quad \frac{V_2}{V_1} = -438$$

$$16.18 \quad h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = R_1 // R_2 = \frac{2}{3} \Omega$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = \frac{-R_1}{R_1 + R_2} = -\frac{1}{3}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{R_1}{R_1 + R_2} = \frac{1}{3}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{1}{R_3 // (R_1 + R_2)} = \frac{2}{3} \text{ S}$$

$$16.22 \quad (\text{a}) \quad A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 1 \quad B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} = Z_L$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = 0 \quad D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} = 1$$

$$(\text{b}) \quad A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 1 \quad B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} = 0$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{Z_L} \quad D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} = 1$$

A10 ANSWERS TO SELECTED PROBLEMS

$$16.26 \mathbf{A} = \left. \frac{\mathbf{V}_1}{\mathbf{V}_2} \right|_{\mathbf{I}_2=0} = \frac{R_1 + R_2}{\gamma + R_1}$$

$$\mathbf{B} = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3 - \gamma R_2}{\gamma + R_2}$$

$$\mathbf{C} = \left. \frac{\mathbf{I}_1}{\mathbf{V}_2} \right|_{\mathbf{I}_2=0} = \frac{1}{\gamma + R_2}$$

$$\mathbf{D} = \left. \frac{\mathbf{I}_1}{-\mathbf{I}_2} \right|_{\mathbf{V}_2=0} = \frac{R_2 + R_3}{\gamma + R_2}$$

$$16.32 \mathbf{z}_{11} = \frac{\mathbf{y}_{22}}{\Delta \mathbf{y}} = 3\Omega$$

$$\mathbf{z}_{12} = \frac{-\mathbf{y}_{12}}{\Delta \mathbf{y}} = 2\Omega$$

$$16.37 \mathbf{Y}_{\text{in}} = \frac{2 + j2}{1 + j2} \text{ S}$$

$$16.42 \mathbf{V}_o = 2.32 \angle 157^\circ \text{ V}$$

$$\mathbf{z}_{21} = \frac{-\mathbf{y}_{21}}{\Delta \mathbf{y}} = 2\Omega$$

$$\mathbf{z}_{22} = \frac{\mathbf{y}_{11}}{\Delta \mathbf{y}} = 5\Omega$$