

Chapter Seven:

First- and Second-Order Transient Circuits

7.1 Use the differential equation approach to find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.1 and plot the response including the time interval just prior to switch action.

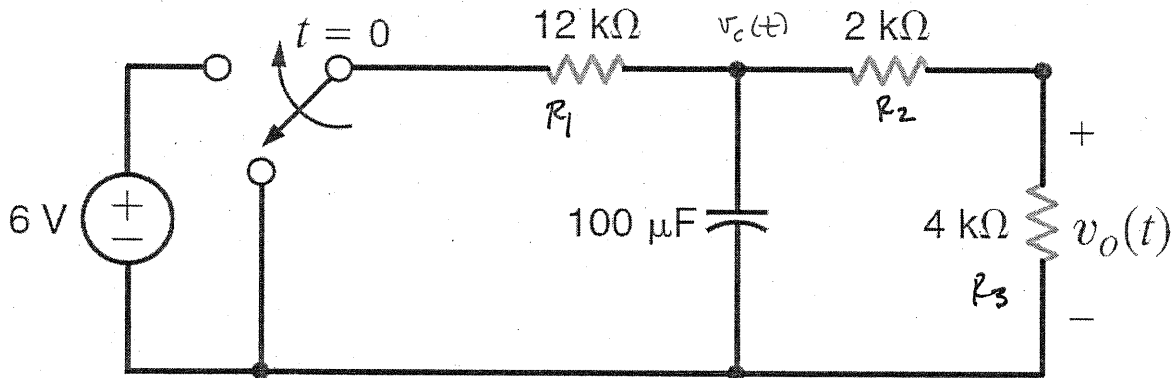


Figure P7.1

SOLUTION:

$$v_c(0^-) = 0V \quad \text{for } t > 0: \quad \frac{6 - v_c}{R_1} + \frac{v_o - v_c}{R_2} - C \frac{dv_c}{dt} = 0 \quad v_o = \frac{v_c R_3}{R_2 + R_3} = \alpha v_c$$

$$\text{Multiply by } \alpha \Rightarrow \frac{6\alpha}{R_1} + \frac{v_o}{R_2} [\alpha - 1] - \frac{v_o}{R_1} - \frac{C}{\alpha} \frac{dv_o}{dt} = 0$$

$$\frac{dv_o}{dt} + v_o \left[\frac{1}{R_1 C} + \frac{1 - \alpha}{R_2 C} \right] - \frac{6\alpha}{R_1 C} = 0 \quad \text{let } \frac{1}{R_1 C} + \frac{1 - \alpha}{R_2 C} = B$$

$$\text{assume } v_o(t) = K_1 + K_2 e^{-t/\tau} \quad \left\{ \begin{array}{l} \tau = 1/B = C \left[\frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3} \right] \\ K_1 = \frac{6\alpha}{R_1 B C} = \frac{6R_3}{R_1 + R_2 + R_3} \end{array} \right.$$

$$-\frac{K_2}{\tau} e^{-t/\tau} + K_1 B + K_2 B e^{-t/\tau} - \frac{6\alpha}{R_1 C} = 0$$


$$\tau = 0.4s \quad K_1 = 1.33V$$

$$v_o(0) = v_c(0) \alpha = 0 = K_1 + K_2 \Rightarrow K_2 = -1.33V$$

$$v_o(t) = 1.33 - 1.33 e^{-2.5t} V$$

$t = 0^+$: $v_c(0^+) = 0$ $v_o(0^+) = \frac{6R_3}{R_1 + R_2 + R_3} = 1.33V$

$t = 0^-$ $v_o(t) = 0$

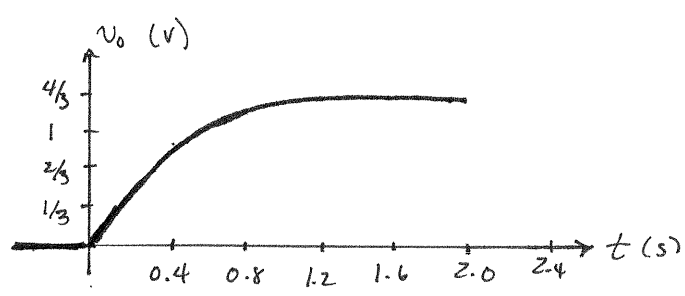

7.2 Use the differential equation approach to find $v_C(t)$ for $t > 0$ in the circuit in Fig. P7.2 and plot the response including the time interval just prior to closing the switch.

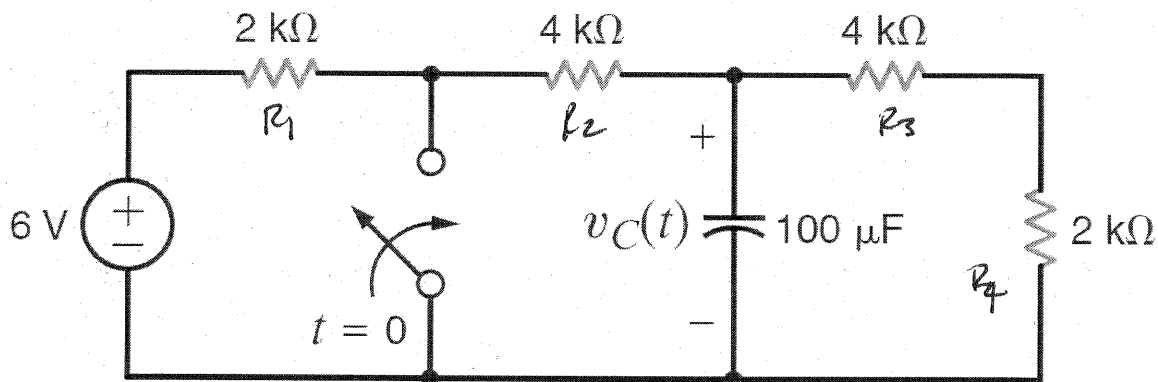


Figure P7.2

SOLUTION:
$$v_C(0^+) = v_C(0^-) = \frac{6(R_3 + R_4)}{R_1 + R_2 + R_3 + R_4} = 3V$$

for $t > 0$:
$$\frac{v_C}{R_2} + \frac{v_C}{R_3 + R_4} + C \frac{dv_C}{dt} = 0 \quad \text{let } v_C(t) = k_1 + k_2 e^{-t/\tau}$$


$$k_1 \left(\frac{1}{R_2} + \frac{1}{R_3 + R_4} \right) + k_2 \left(\frac{1}{R_2} + \frac{1}{R_3 + R_4} \right) e^{-t/\tau} - \frac{k_2 C}{\tau} e^{-t/\tau} = 0$$

yields $k_1 = 0$ $\tau = C \left\{ \frac{R_2(R_3 + R_4)}{R_2 + R_3 + R_4} \right\} = 0.24s$

$$v_C(0^+) = 3 = k_1 + k_2 \Rightarrow k_2 = 3V$$

$$v_C(t) = 3 e^{-t/0.24} \text{ V}$$

for $t=0^-$: $v_C(0^-) = 3V$

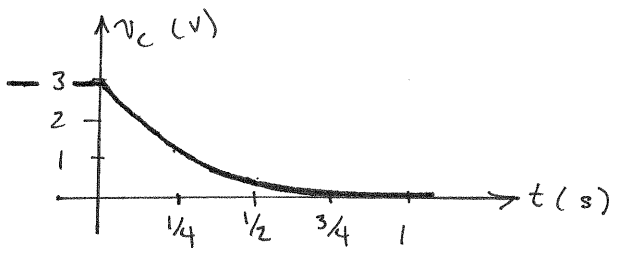

7.3 Use the differential equation approach to find $v_C(t)$ for $t > 0$ in the circuit in Fig. P7.3. CS

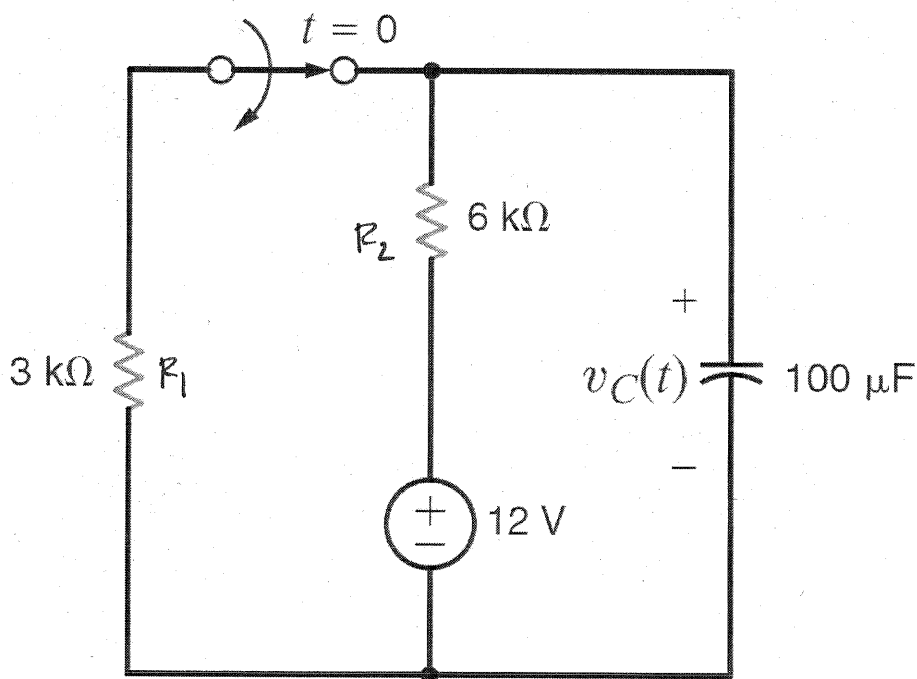


Figure P7.3


SOLUTION: $v_C(0^+) = v_C(0^-) = \frac{12(R_1)}{R_1 + R_2} = 4V$ $v_C(t) = K_1 + K_2 e^{-t/\tau}$

for $t > 0$,

$$\frac{v_C - 12}{R_2} + C \frac{dv_C}{dt} = 0 \Rightarrow \frac{dv_C}{dt} + \frac{v_C}{R_2 C} - \frac{12}{R_2 C} = 0 = \frac{-K_2}{\tau} e^{-t/\tau} + \frac{K_1}{R_2 C} + \frac{K_2}{R_2 C} e^{-t/\tau} - \frac{12}{R_2 C} = 0$$

yields: $\tau = R_2 C = 0.6s$ $K_1 = 12$ $v_C(0^+) = 4 = K_1 + K_2 \Rightarrow K_2 = -8V$

$$v_C(t) = 12 - 8e^{-\frac{t}{0.6}} V$$

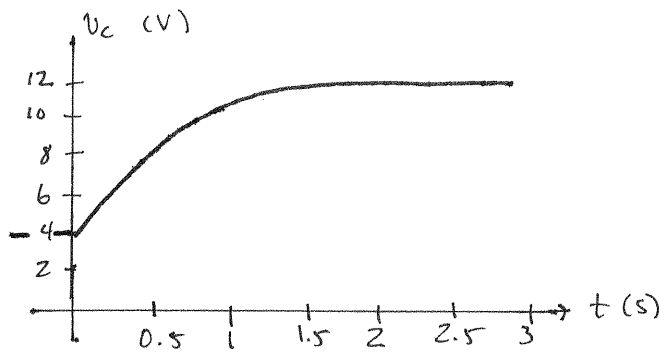

7.4 Use the differential equation approach to find $v_C(t)$ for $t > 0$ in the circuit in Fig. P7.4.

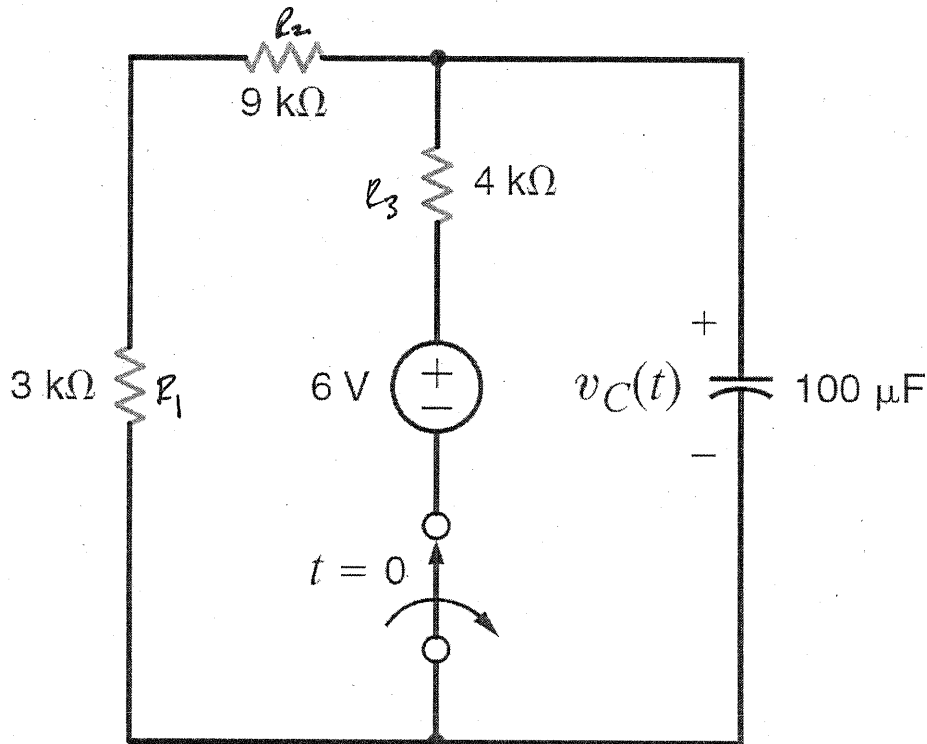


Figure P7.4


SOLUTION: $v_C(0^+) = v_C(0^-) = \frac{6(R_1 + R_2)}{R_1 + R_2 + R_3} = 4.5 \text{ V}$ $v_C(t) = K_1 + K_2 e^{-t/\tau}$

for $t > 0$: $\frac{C dv_C(t)}{dt} + \frac{v_C(t)}{R_1 + R_2} = 0 \Rightarrow \frac{dv_C}{dt} + \frac{v_C}{C(R_1 + R_2)} = 0 = \frac{dv_C}{dt} + \frac{v_C}{\tau}$

$\tau = C(R_1 + R_2) = 1.2 \text{ s}$ $-\frac{K_2}{\tau} + \frac{K_1}{\tau} + \frac{K_2}{\tau} = 0 \Rightarrow K_1 = 0$

$v_C(0^+) = 4.5 = K_1 + K_2 \Rightarrow K_2 = 4.5$

$$v_C(t) = 4.5 e^{-t/1.2} \text{ V}$$

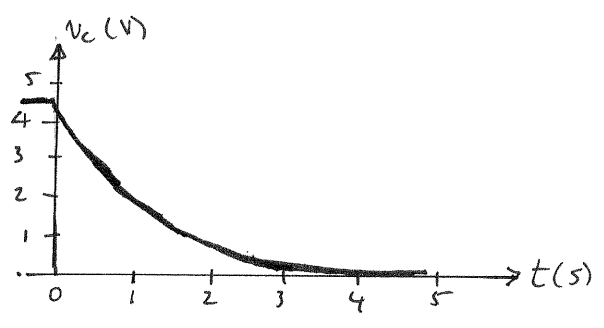

7.5 Use the differential equation approach to find $v_C(t)$ for $t > 0$ in the circuit in Fig. P7.5 and plot the response including the time interval just prior to opening the switch. **CS**

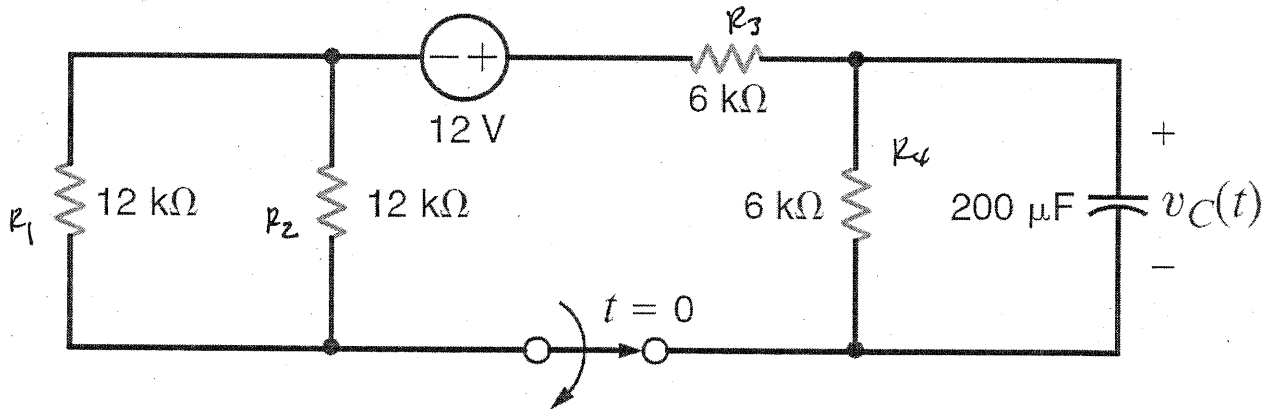


Figure P7.5


SOLUTION: $v_C(0^-) = v_C(0^+) = \frac{12 R_4}{R_3 + R_4 + R_A} \quad R_A = R_1 // R_2 = 6 \text{ k}\Omega \quad v_C(0^+) = 4 \text{ V}$

for $t > 0$; $\frac{v_C}{R_4} + C \frac{dv_C}{dt} = 0 \Rightarrow \frac{dv_C}{dt} + \frac{v_C}{R_4 C} = 0$

$v_C(t) = K_1 + K_2 e^{-t/\tau} \Rightarrow \frac{dv_C}{dt} + \frac{v_C}{\tau} = 0$

$\tau = R_4 C \quad K_1 = 0 \quad v_C(0^+) = 4 = K_1 + K_2 \Rightarrow K_2 = 4 \text{ V}$

$$v_C(t) = 4 e^{-t/1.2} \text{ V}$$

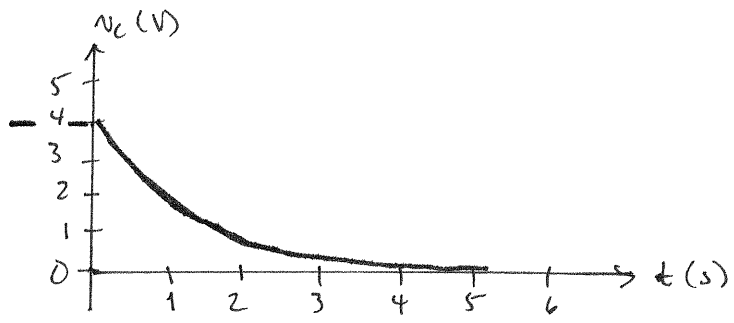

7.6 Use the differential equation approach to find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.6 and plot the response including the time interval just prior to opening the switch. **CS**

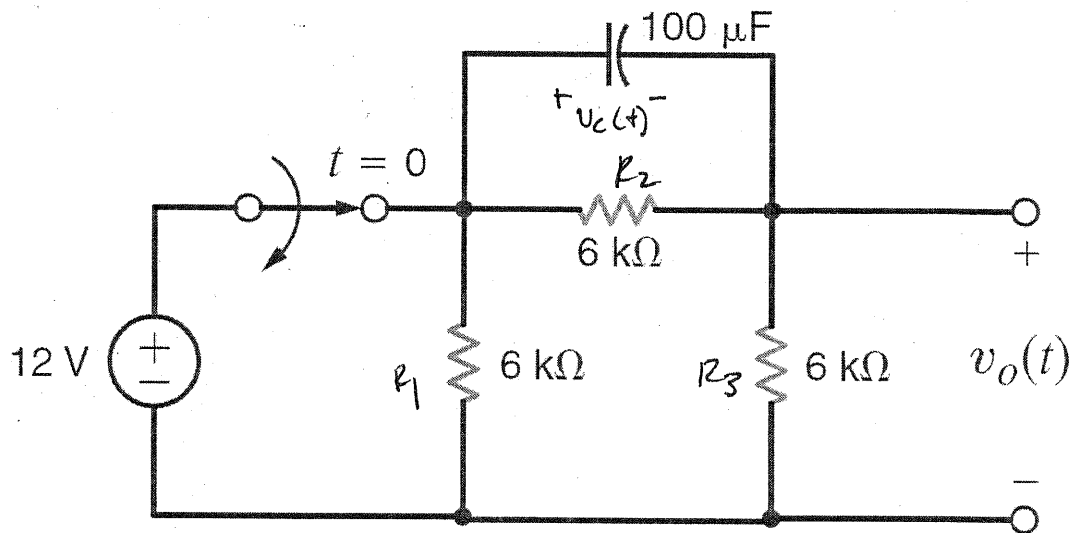


Figure P7.6

SOLUTION: $v_c(t^+) = v_c(t^-) = \frac{12 R_2}{R_2 + R_3} = 6V$ $v_o(t) = K_1 + K_2 e^{-t/\tau}$

For $t > 0$: $v_o = \frac{v_c (-R_3)}{R_1 + R_3} = -\alpha v_c$ $\frac{v_c}{R_2} + C \frac{dv_c}{dt} = \frac{v_o}{R_3}$


Eliminate v_c : $\frac{dv_o}{dt} + v_o \left[\frac{1}{R_2 C} + \frac{\alpha}{R_3 C} \right] = 0 = \frac{dv_o}{dt} + \frac{v_o}{\tau}$

$\tau = C \left[\frac{R_2 (R_1 + R_3)}{R_2 + R_1 + R_3} \right] = 0.4s$ $K_1 = 0$

$v_o(t^+) = v_c(t^+) \alpha = -3V = K_1 + K_2 \Rightarrow K_2 = -3V$

$$v_o(t) = -3 e^{-2.5t} \text{ V}$$

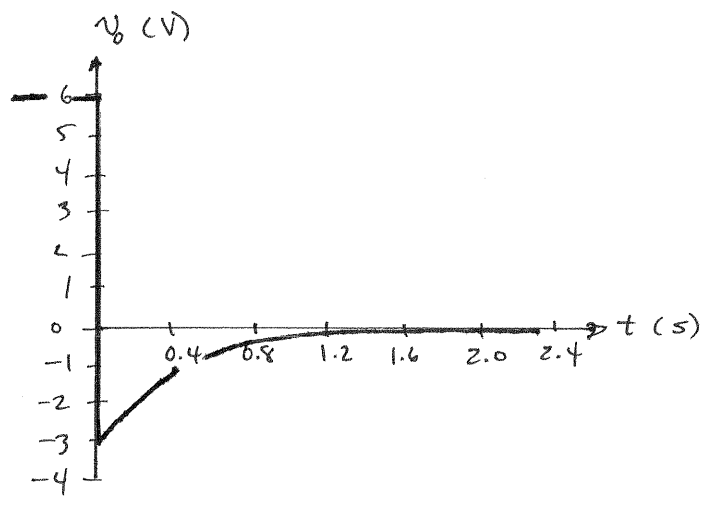$t = 0^-$: $v_c(0^-) = 6V$ $v_o(0^-) = 12 - v_c = 6V$



7.7 Use the differential equation approach to find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.7 and plot the response including the time interval just prior to closing the switch.

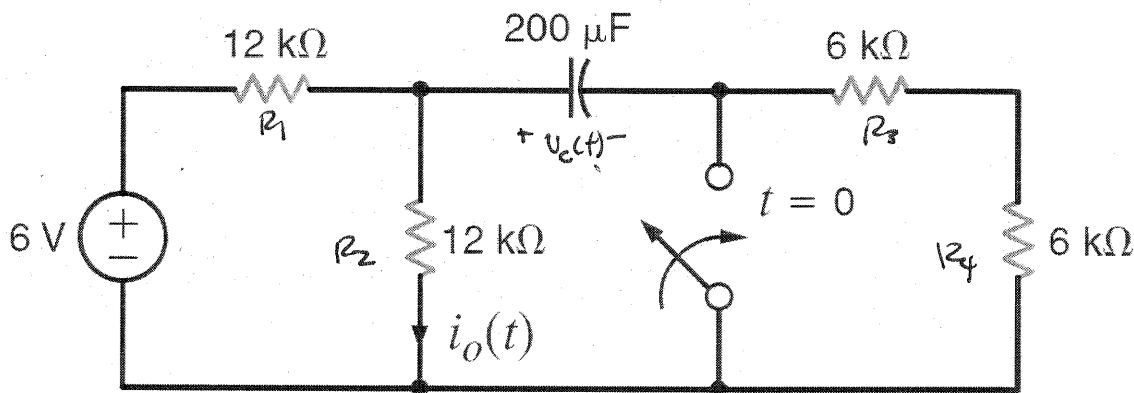


Figure P7.7

SOLUTION: $v_c(0^-) = v_c(0^+) = \frac{6R_2}{R_1 + R_2} = 3V$ $i_o(t) = \frac{v_c(t)}{R_2}$ for $t > 0$.

For $t > 0$: $\frac{6 - v_c}{R_1} = \frac{v_c}{R_2} + C \frac{dv_c}{dt} \Rightarrow \frac{dv_c}{dt} + v_c \left[\frac{1}{R_1 C} + \frac{1}{R_2 C} \right] - \frac{6}{R_1 C} = 0$

Convert to i_o : $\frac{di_o}{dt} + i_o \left[\frac{1}{R_1 C} + \frac{1}{R_2 C} \right] - \frac{6}{R_1 R_2 C} = 0$


$i_o(t) = k_1 + k_2 e^{-t/\tau} \Rightarrow -\frac{k_2}{\tau} e^{-t/\tau} + (k_1 + k_2 e^{-t/\tau}) \left[\frac{1}{R_1 C} + \frac{1}{R_2 C} \right] - \frac{6}{R_1 R_2 C} = 0$

yields $\tau = C \frac{R_1 R_2}{R_1 + R_2} = 1.25$ $k_1 = \frac{6}{R_1 + R_2} = 0.25 \text{ mA}$

$i_o(0^+) = k_1 + k_2 = v_c(0^+) / R_2 = 0.25 \text{ mA} \Rightarrow k_2 = 0$

$i_o(t) = 0.25 \text{ mA}$

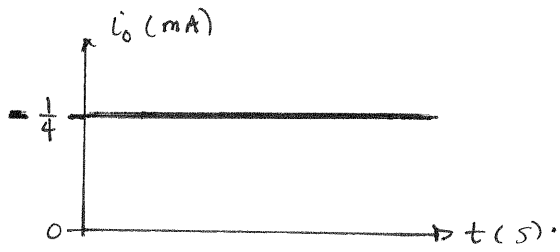$t=0^- : v_c(0^-) = 3V \quad i_c(0^-) = 0 \quad i_o(0^-) = \frac{6}{R_1 + R_2} = 0.25mA$



7.8 Use the differential equation approach to find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.8 and plot the response including the time interval just prior to closing the switch.

CS


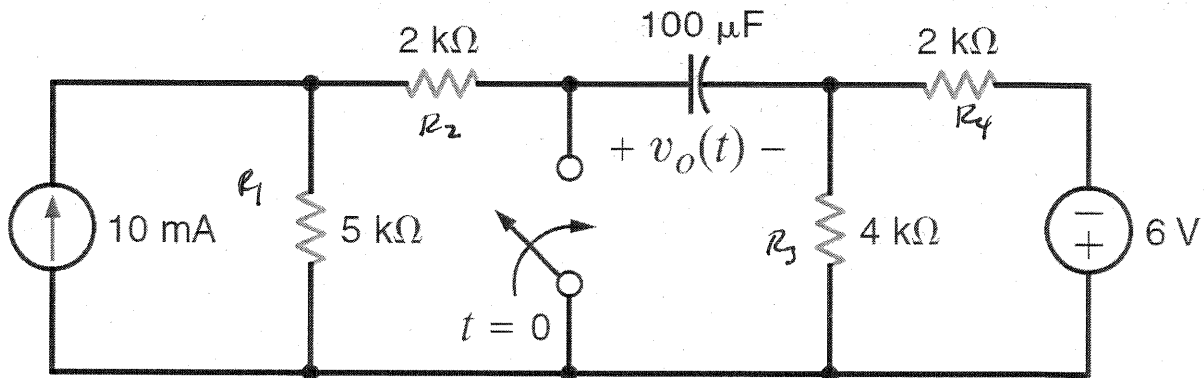


Figure P7.8

SOLUTION: Using source transformation:

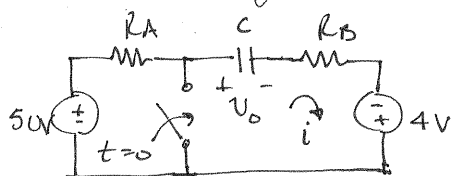

$$R_A = R_1 + R_2 = 7 \text{ k}\Omega$$

$$R_B = R_3 \parallel R_4 = 1.33 \text{ k}\Omega$$


$$v_o(0^+) = v_o(0^-) = 54 \text{ V}$$

$$\text{For } t > 0: 4 = v_o + i R_B \text{ \& } i = C dv_o/dt \Rightarrow \frac{dv_o}{dt} + \frac{v_o}{R_B C} - \frac{4}{R_B C} = 0$$

$$v_o = K_1 + K_2 e^{-t/\tau} \Rightarrow \tau = R_B C \text{ \& } K_1 = 4 \quad \tau = 0.133 \text{ s}$$

$$v_o(0^+) = 54 = K_1 + K_2 \Rightarrow K_2 = 50 \text{ V}$$

$$v_o = 4 + 50 e^{-7.5t} \text{ V}$$

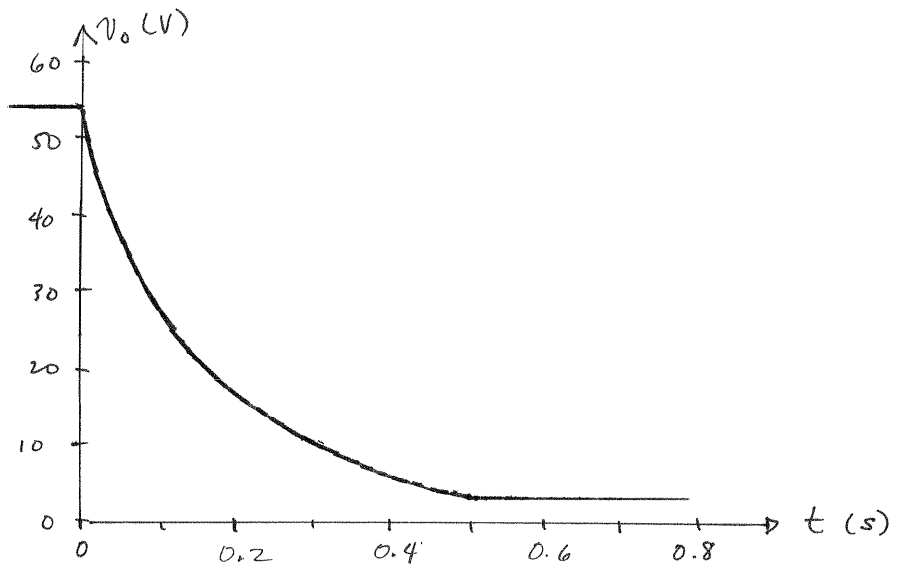

7.9 Use the differential equation approach to find $v_C(t)$ for $t > 0$ in the circuit in Fig. P7.9 and plot the response including the time interval just prior to opening the switch.


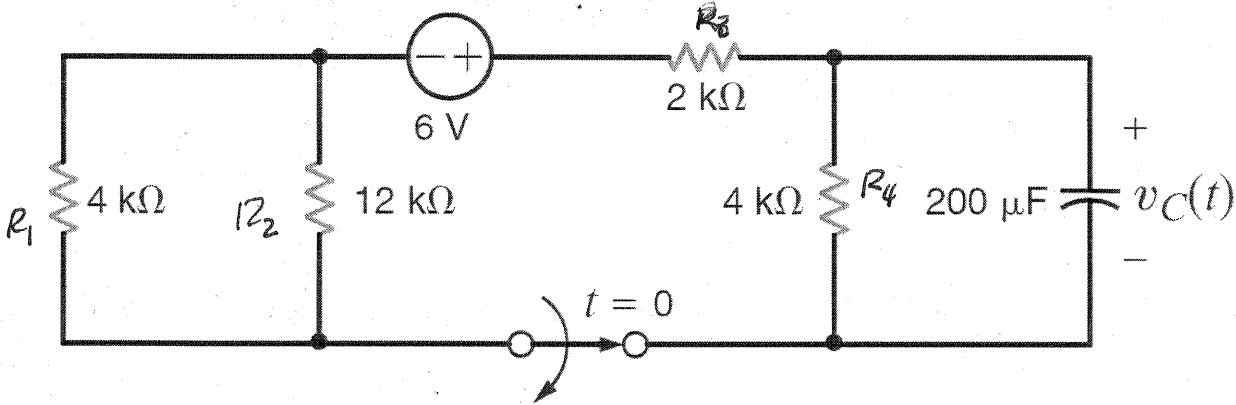


Figure P7.9

SOLUTION: $R_A = R_1 // R_2 = 3k\Omega$

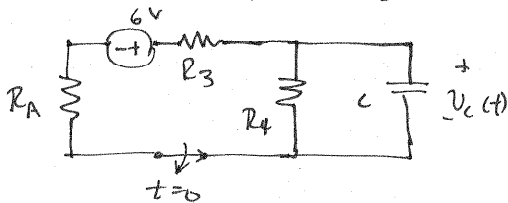

$$v_C(t^+) = v_C(t^-) = \frac{6 R_4}{R_A + R_3 + R_4} = \frac{8}{3} \text{ V}$$


for $t > 0$,

$$\frac{v_C}{R_4} + C \frac{dv_C}{dt} = 0 \Rightarrow \frac{dv_C}{dt} + \frac{v_C}{R_4 C} = 0$$

$$v_C = K_1 + K_2 e^{-t/\tau} \Rightarrow \tau = R_4 C = 0.85 \text{ s} \quad K_1 = 0$$

$$v_C(t^+) = \frac{8}{3} = K_1 + K_2 \Rightarrow K_2 = 2.67 \text{ V}$$

$$v_C(t) = 2.67 e^{-1.25t} \text{ V}$$

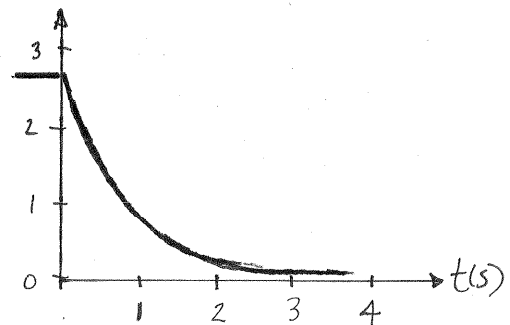

7.10 Use the differential equation approach to find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.10 and plot the response including the time interval just prior to opening the switch. **CS**


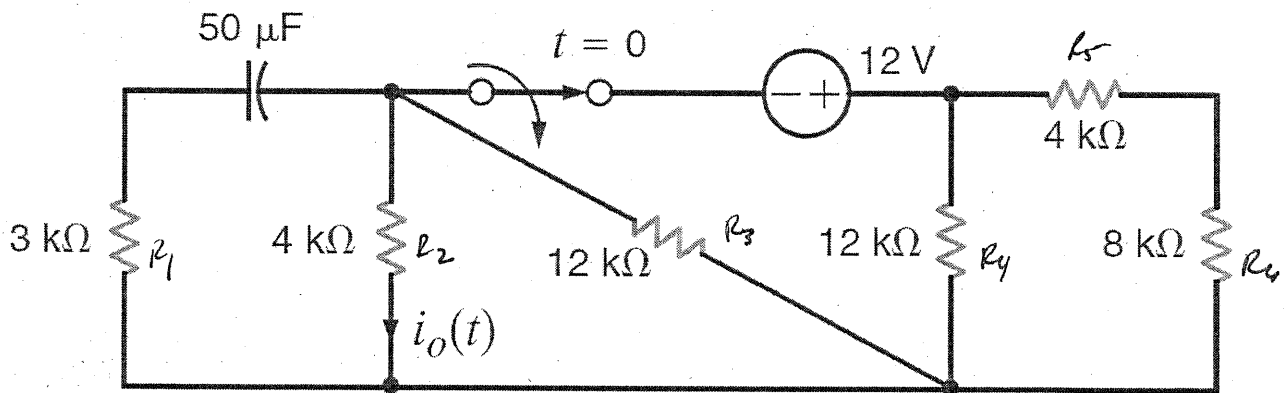


Figure P7.10

SOLUTION:

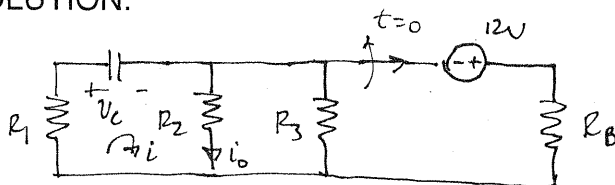

$$R_B = R_4 \parallel (R_5 + R_6) = 6 \text{ k}\Omega$$

$$R_A = R_2 \parallel R_3 = 3 \text{ k}\Omega$$

$$v_C(0^+) = v_C(0^-) = \frac{12 R_A}{R_A + R_B} = 4 \text{ V}$$

$$i_o(0^-) = \frac{-v_C(0^-)}{R_2} = -1 \text{ mA} \quad \checkmark$$

$$\text{For } t > 0, \quad v_C + i R_A + i R_1 = 0 \quad \& \quad i = C \frac{dv_C}{dt} \quad \& \quad i_o = \frac{R_3}{R_2 + R_3} i = \alpha i$$

$$\text{yields,} \quad \frac{dv_C}{dt} + \frac{v_C}{C(R_1 + R_A)} = 0$$


$$\text{or,} \quad \frac{di_o}{dt} + \frac{i_o}{C(R_1 + R_A)} = 0 \quad \text{where } i_o = K_1 + K_2 e^{-t/\tau}$$

$$\text{yields,} \quad \tau = C[R_1 + R_A] = 0.3 \text{ s} \quad K_1 = 0$$


$$i_o(0^+) = \frac{-v_C(0^+)}{R_1 + R_A} \frac{R_3}{R_3 + R_2} = -0.5 \text{ mA} = K_1 + K_2 \Rightarrow K_2 = -0.5 \text{ mA}$$

$$i_o(t) = -0.5 e^{-t/0.3} \text{ mA}$$

$t = 0^-$:

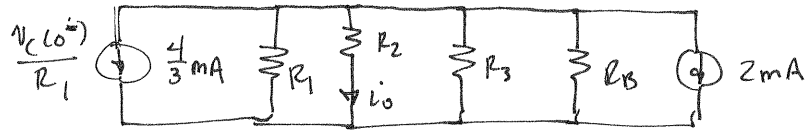
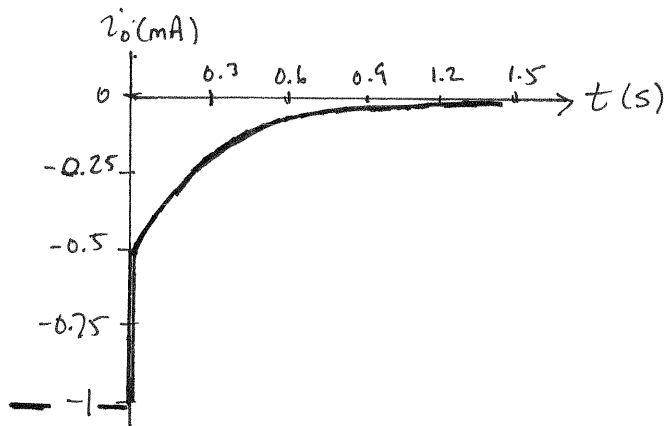
$$i_o(0^-) = - \frac{(2 + 4/3) \times 10^{-3} (1/R_2)}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_B}} = -1 \text{ mA}$$



7.11 Use the differential equation approach to find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.11 and plot the response including the time interval just prior to opening the switch.


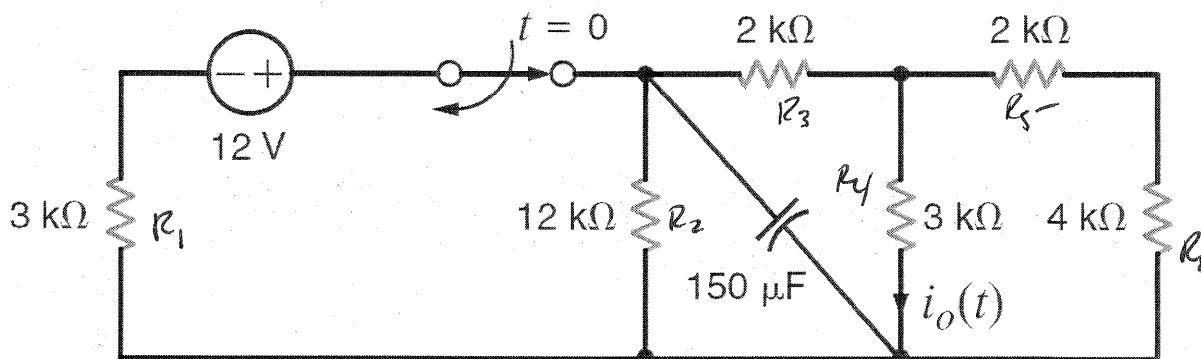


Figure P7.11

SOLUTION:

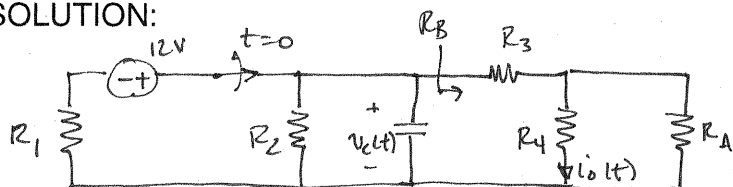

$$R_A = R_5 + R_6 = 6 \text{ k}\Omega$$

$$R_B = R_3 + (R_4 // R_A) = 4 \text{ k}\Omega$$

$$R_C = R_2 // R_B = 3 \text{ k}\Omega$$

$$v_c(0^+) = v_c(0^-) = \frac{12 R_C}{R_1 + R_C} = 6 \text{ V}$$

$$i_o(t) = \frac{v_c(t)}{R_B} \frac{R_A}{R_A + R_4} = \frac{v_c(t)}{6000} \quad i_o(0^-) = i_o(0^+) = 1 \text{ mA}$$


$$\text{For } t > 0, \quad \frac{v_c}{R_C} + C \frac{dv_c}{dt} = 0 \Rightarrow \frac{di_o}{dt} + \frac{i_o}{CR_C} = 0$$

$$i_o = K_1 + K_2 e^{-t/\tau} \Rightarrow \tau = CR_C = 0.45 \text{ s} \quad K_1 = 0$$

$$K_1 + K_2 = i_o(0^+) = 1 \text{ mA} \Rightarrow K_2 = 1 \text{ mA}$$

$$i_o(t) = e^{-t/0.45} \text{ mA}$$

$t=0^-$:

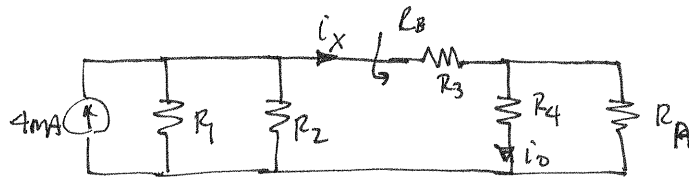


$$R_B = 4k\Omega$$

$$R_A = 6k\Omega$$

$$i_x = \frac{4 \times 10^{-3} \left(\frac{1}{R_B} \right)}{\frac{1}{R_B} + \frac{1}{R_1} + \frac{1}{R_2}} = 1.5 \text{ mA}$$
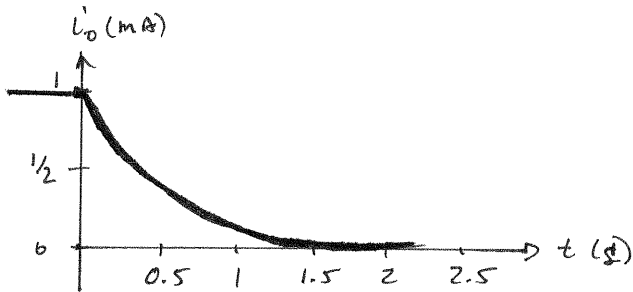
$$i_o = \frac{i_x R_A}{R_A + R_4} = 1 \text{ mA}$$



7.12 Use the differential equation approach to find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.12 and plot the response including the time interval just prior to opening the switch.

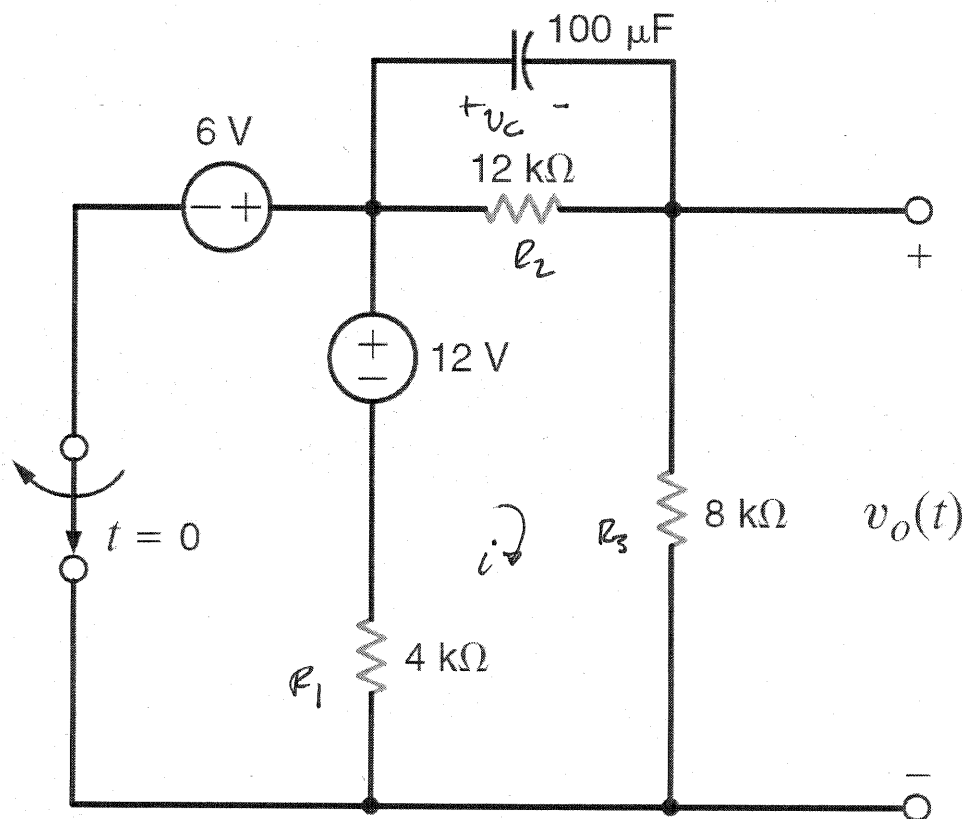


Figure P7.12

SOLUTION: $v_c(0^+) = v_c(0^-) = \frac{6R_2}{R_2 + R_3} = 3.6\text{V}$ $v_o(0^-) = \frac{6R_3}{R_2 + R_3} = 2.4\text{V}$

For $v_o(0^+)$: $\left[12 - v_c(0^+)\right] \frac{R_3}{R_1 + R_3} = v_o(0^+) = 5.6\text{V}$

For $t > 0$: $12 = v_c(t) + i(R_1 + R_3)$ $v_o = iR_3$

and $C \frac{dv_c}{dt} + \frac{v_c}{R_2} = \frac{v_o}{R_3}$

yields $\frac{dv_o}{dt} + v_o \left[\frac{1}{R_2 C} + \frac{\alpha}{R_3 C} \right] - \frac{12\alpha}{R_2 C} = 0$ $\alpha = \frac{R_3}{R_1 + R_3}$


$$\tau = C [R_2 \parallel (R_1 + R_3)] = 0.6 \text{ s}$$

$$K_1 = \frac{12 R_3}{R_1 + R_2 + R_3} = 4 \text{ V}$$

$$v_o(0^+) = K_1 + K_2 = 5.6 \text{ V} \Rightarrow K_2 = 1.6 \text{ V}$$

$$v_o(t) = 4 + 1.6 e^{-t/0.6} \text{ V}$$
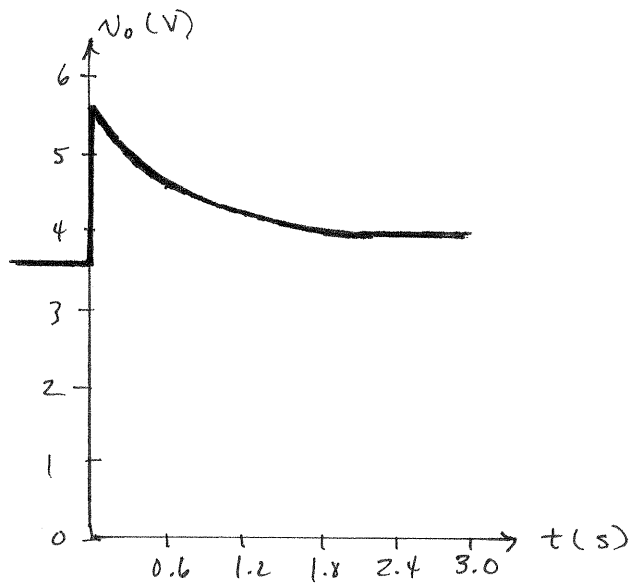
$$t=0^-: v_o(0^-) = 6 - v_c(0^-) = 3.6 \text{ V}$$



7.13 Use the differential equation approach to find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.13 and plot the response including the time interval just prior to opening the switch.


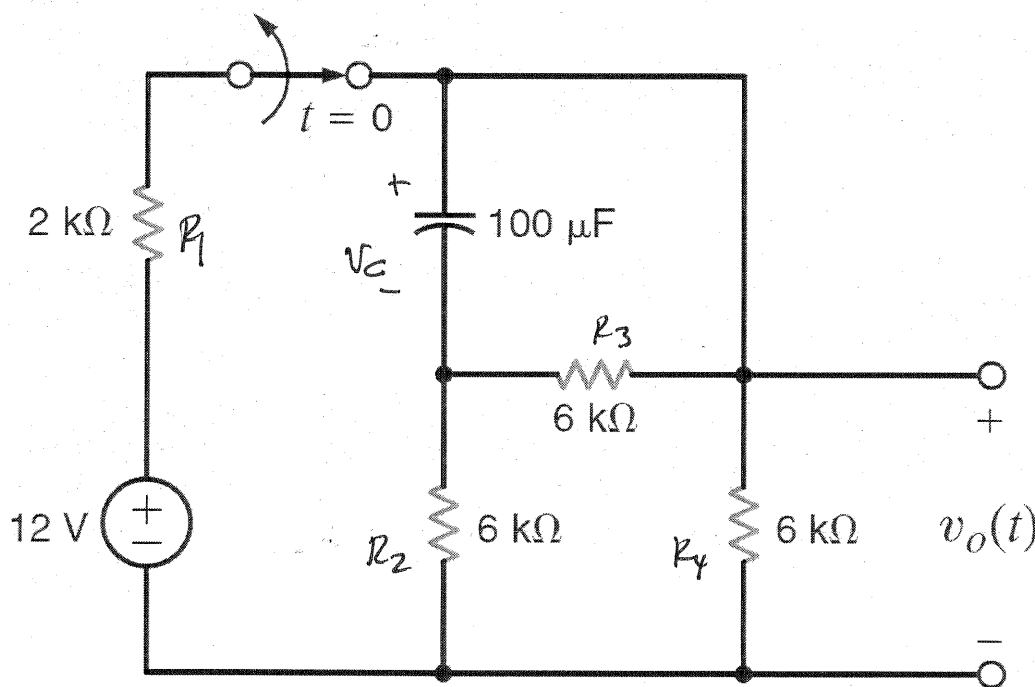


Figure P7.13

SOLUTION:

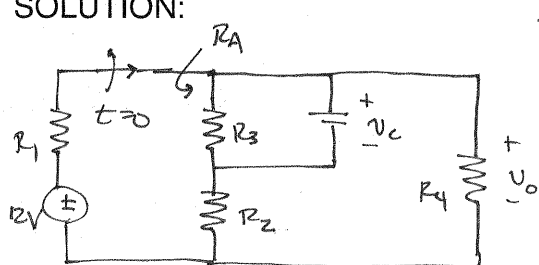

$t < 0$

$$R_A = R_3 \parallel (R_2 + R_4) = 4 \text{ k}\Omega$$

$$v_o(t=0^-) = \frac{12 R_A}{R_A + R_1} = 8 \text{ V}$$

$$v_C(t=0^-) = v_C(t=0^+) = \frac{v_o(t=0^-) R_3}{R_2 + R_3} = 4 \text{ V}$$

$$t = 0^+ \quad v_o(t=0^+) = \frac{v_C(t=0^+) R_4}{R_2 + R_4} = 2 = K_1 + K_2$$

$$t > 0 \quad C \frac{dv_C}{dt} + \frac{v_C}{R_3} + \frac{v_o}{R_4} = 0 \quad \text{and} \quad v_o = \frac{v_C R_4}{R_2 + R_4} = \alpha v_C$$

yields
$$\frac{dv_C}{dt} + v_C \left[\frac{1}{CR_3} + \frac{\alpha}{CR_4} \right] = 0$$


$$\tau = C [R_3 // (R_2 + R_4)] = 0.4 \text{ s}$$

$$K_1 = 0$$

$$v_o(0^+) = z = K_1 + K_2 \Rightarrow K_2 = z$$

$$v_o(t) = z e^{-2.5t} \text{ V}$$

$$t = 0^- : v_o(0^-) = 8 \text{ V}$$

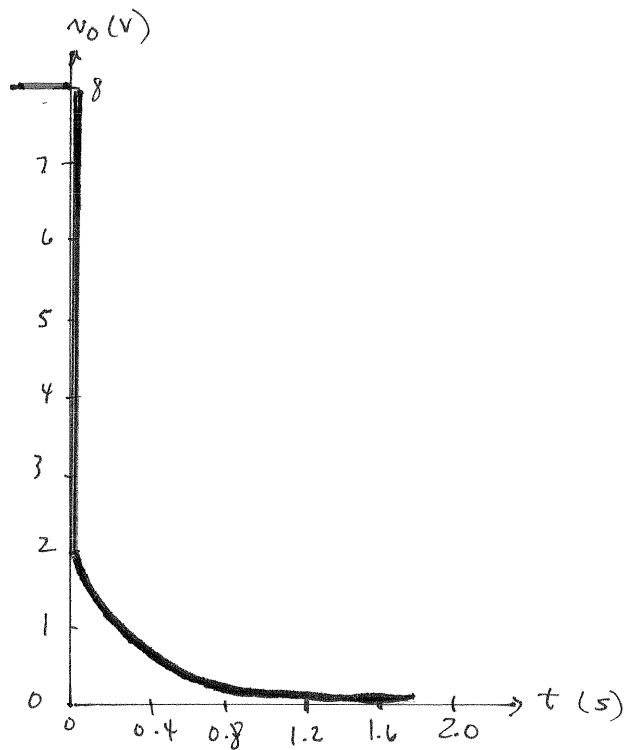

7.14 Use the differential equation approach to find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.14 and plot the response including the time interval just prior to closing the switch. **PSV**


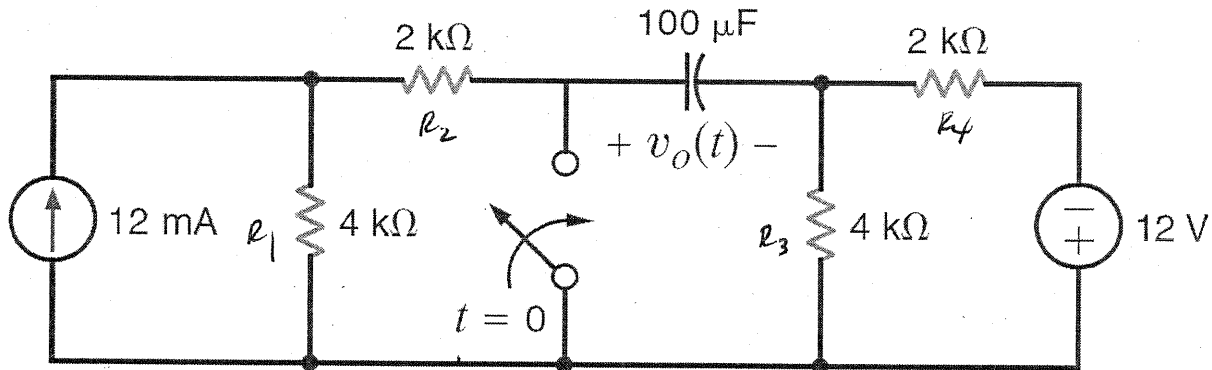


Figure P7.14

SOLUTION: By source transformation:

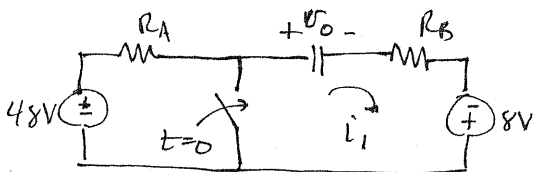

$$R_A = R_1 + R_2 = 6 \text{ k}\Omega$$

$$R_B = R_3 \parallel R_4 = \frac{4}{3} \text{ k}\Omega$$

$$t < 0 \quad v_o(0^-) = v_o(0^+) = 56 \text{ V} \quad \text{Note: } v_o(t) = v_c(t)$$


$$t = 0^+ \quad v_o(0^+) = 56 \text{ V}$$

$$t > 0 \quad 8 = v_o + i_1 R_B \quad \& \quad i_1 = C \frac{dv_c}{dt} \Rightarrow \frac{dv_o}{dt} + \frac{v_o}{R_B C} - \frac{8}{R_B C} = 0$$

$$v_o = K_1 + K_2 e^{-t/\tau} \Rightarrow \tau = R_B C = 0.133 \mu\text{s} \quad K_1 = 8 \text{ V}$$

$$K_2 = v_o(0^+) - K_1 = 48 \text{ V}$$

$$v_o(t) = 8 + 48 e^{-7.5t} \text{ V}$$

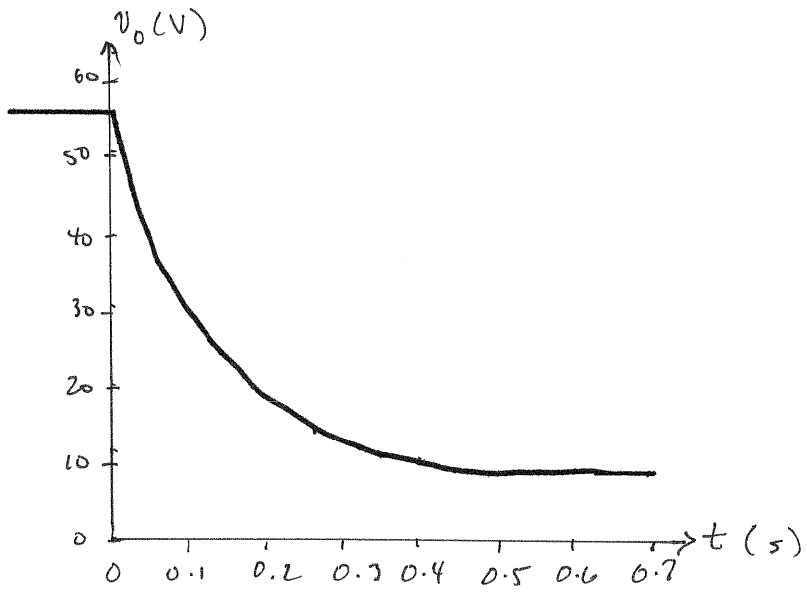

7.15 Use the differential equation approach to find $i(t)$ for $t > 0$ in the network in Fig. P7.15.

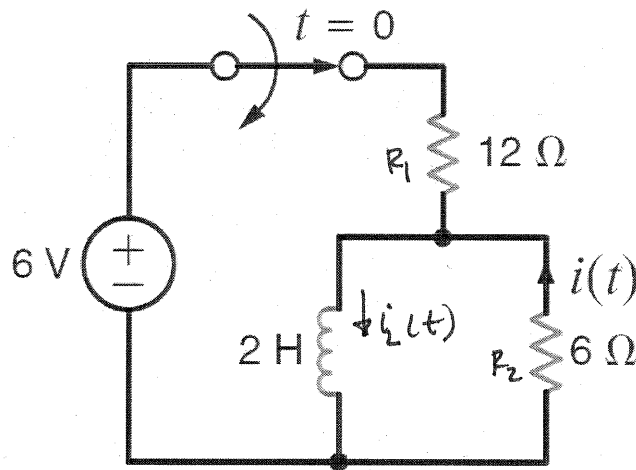


Figure P7.15

SOLUTION: $t=0^-$: $i_L(0^-) = 6/R_1 = 0.5 \text{ A} = i_L(0^+)$


$t=0^+$: $i(0^+) = i_L(0^+) = 0.5 \text{ A} = k_1 + k_2$

$t > 0$: $L \frac{di}{dt} + R_2 i = 0 \Rightarrow \frac{di}{dt} + \left(\frac{R_2}{L}\right) i = 0$

$i = k_1 + k_2 e^{-t/\tau} \Rightarrow \tau = \frac{L}{R_2} = \frac{1}{3} \text{ s} \quad k_1 = 0$

$k_2 = i(0^+) - k_1 = 0.5 \text{ A}$

$i(t) = 0.5 e^{-3t} \text{ A}$

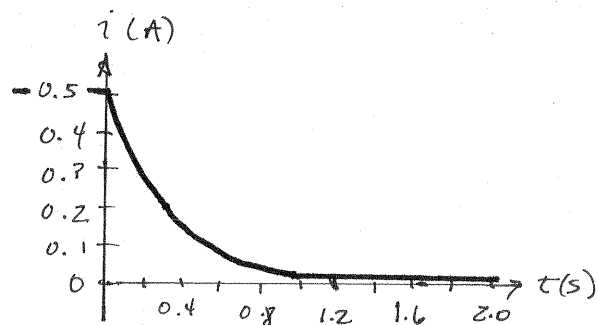

7.16 Use the differential equation approach to find $i(t)$ for $t > 0$ in the circuit in Fig. P7.16 and plot the response including the time interval just prior to switch movement.

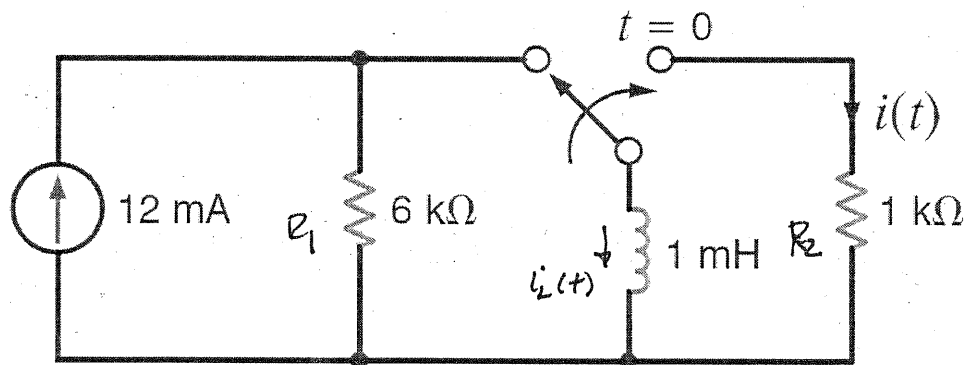


Figure P7.16

SOLUTION:

$$\underline{t=0^-} \quad i_L(0^-) = 12 \text{ mA} = i_L(0^+)$$


$$\underline{t=0^+} \quad i = -i_L = -12 \text{ mA}$$

$$\underline{t > 0} \quad L \frac{di_L}{dt} = R_2 i \quad \& \quad i = -i_L \Rightarrow \frac{di}{dt} + \left(\frac{R_2}{L}\right) i = 0$$

$$i = K_1 + K_2 e^{-t/\tau} \Rightarrow \tau = \frac{L}{R_2} = 1 \mu\text{s} \quad K_1 = 0$$

$$K_2 = i(0^+) - K_1 = -12 \text{ mA}$$

$$i(t) = -12 e^{-10^6 t} \text{ mA}$$

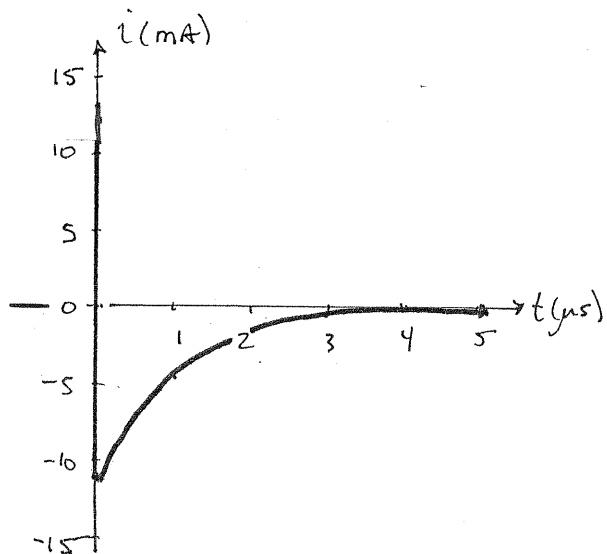

7.17 In the circuit in Fig. 7.17, find $i_o(t)$ for $t > 0$ using the differential equation approach.

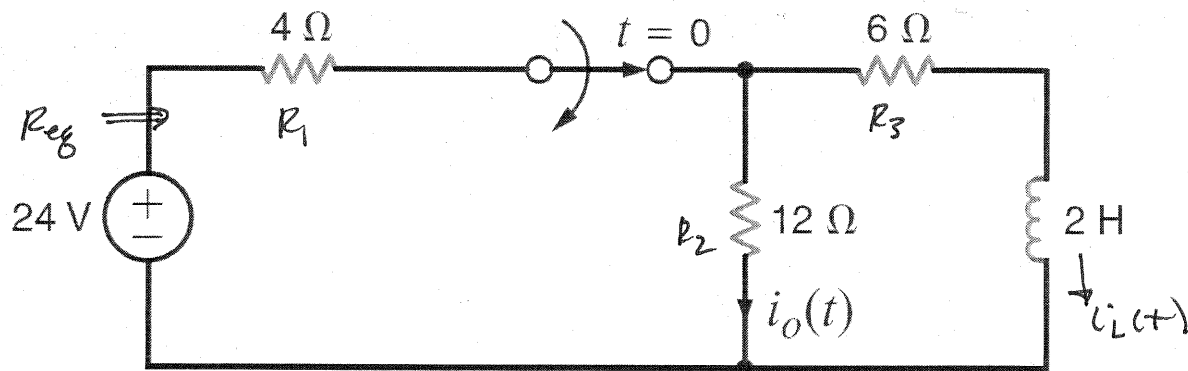


Figure P7.17

SOLUTION:

$$\underline{t=0^-} \quad i_o + i_L = \frac{24}{R_{eq}} = 3 \quad R_{eq} = R_1 + [R_2 \parallel R_3] = 8\Omega$$

$$\frac{i_o}{i_L} = \frac{R_3}{R_2} = \frac{1}{2} \Rightarrow i_L(0^-) = 2A = i_L(0^+)$$

$$\underline{t=0^+} \quad i_L(0^+) = 2A = -i_o(0^+)$$


$$\underline{t>0} \quad L \frac{di_L}{dt} = i_o (R_2 + R_3) \quad \& \quad i_o = -i_L \Rightarrow \frac{di_o}{dt} + i_o \left(\frac{R_2 + R_3}{L} \right) = 0$$

$$i_o = K_1 + K_2 e^{-t/\tau} \Rightarrow \tau = \frac{L}{R_2 + R_3} = \frac{1}{9} s \quad K_1 = 0$$


$$K_2 = i_o(0^+) - K_1 = -2A$$

$$i_o(t) = -2 e^{-9t} A$$

$t=0^-: i_L(0^-) = 2A$

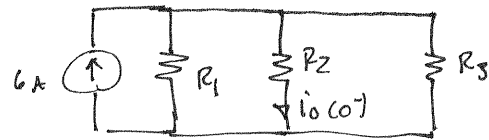
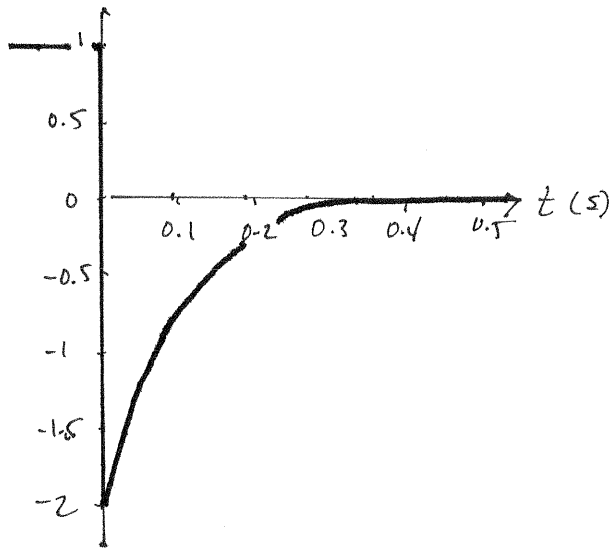
$$i_0(0^-) = \frac{6 \left(\frac{1}{R_2} \right)}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = 1A$$



7.18 Use the differential equation approach to find $i(t)$ for $t > 0$ in the circuit in Fig. P7.18 and plot the response including the time interval just prior to opening the switch.


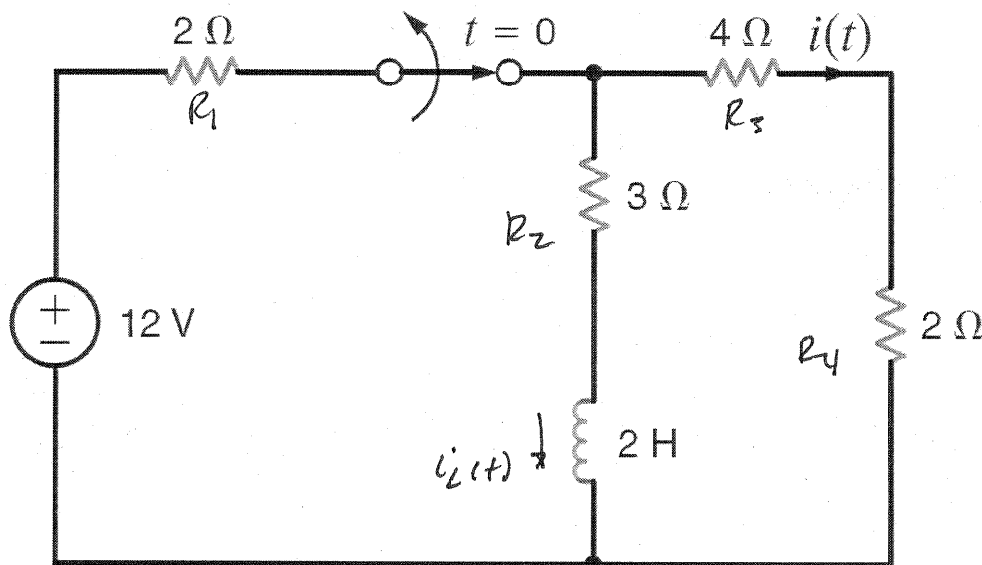


Figure P7.18

SOLUTION: By source transformation:

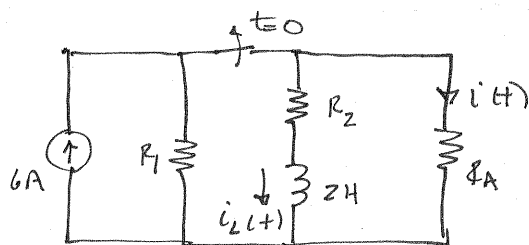

$$R_A = R_3 + R_4 = 6\Omega$$

$$t = 0^- : i_L = \frac{6 \left(\frac{1}{R_2} \right)}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_A}} = 2\text{A}$$

$$i(0^-) = \frac{6 \left(\frac{1}{R_A} \right)}{\frac{1}{R_A} + \frac{1}{R_1} + \frac{1}{R_2}} = 1\text{A}$$

$$t = 0^+ \quad i_L(0^+) = i_L(0^-) = 2\text{A}$$


$$i(0^+) = -i_L(0^+) = -2\text{A}$$

$$t > 0 : L \left(\frac{di_L}{dt} \right) = i(R_A + R_2) \quad \& \quad i = -i_L \Rightarrow \frac{di}{dt} + \left(\frac{R_A + R_2}{L} \right) i = 0$$

$$i = K_1 + K_2 e^{-t/\tau}$$

$$\text{yields } \tau = \frac{L}{R_A + R_2} = \frac{2}{9} \text{ s} \quad i(0) = 0 \quad K_2 = -2$$

$$i = -2e^{-4.5t} \text{ A}$$

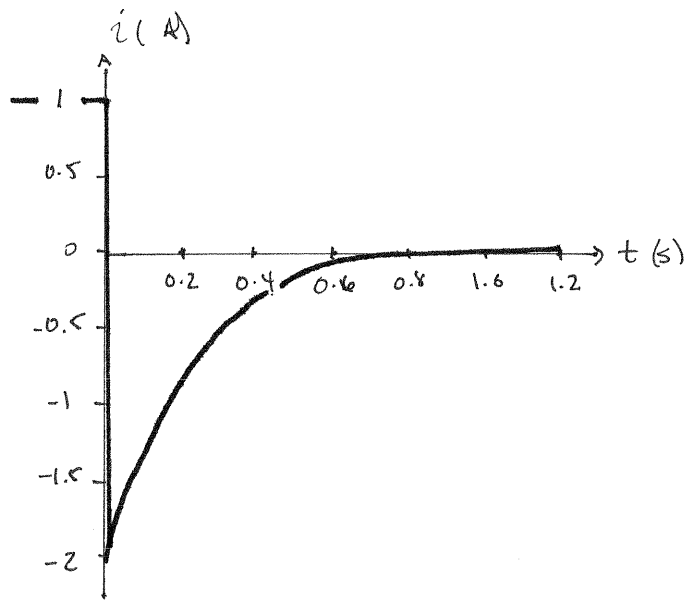

7.19 In the network in Fig. 7.19, find $i_o(t)$ for $t > 0$ using the differential equation approach. CS

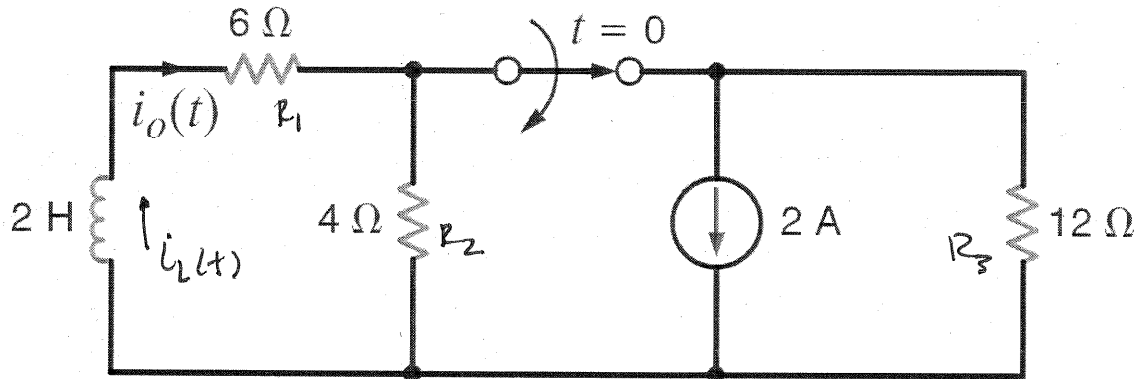


Figure P7.19

SOLUTION: $t = 0^-$: $i_L(0^-) = \frac{2 \left(\frac{1}{R_1} \right)}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{2}{3} \text{ A}$


$t = 0^+$ $i_o = i_L = \frac{2}{3} \text{ A}$

$t > 0$ $L \frac{di_L}{dt} + i_o (R_1 + R_2) = 0$ & $i_L = i_o \Rightarrow \frac{di_o}{dt} + \frac{(R_1 + R_2)}{L} i_o = 0$

$i_o = k_1 + k_2 e^{-t/\tau} \Rightarrow \tau = \frac{L}{R_1 + R_2} = \frac{1}{5} \text{ s}$ $k_1 = 0$

$k_2 = i_o(0^+) - k_1 = \frac{2}{3} \text{ A}$

$i_o(t) = 0.67 e^{-5t} \text{ A}$

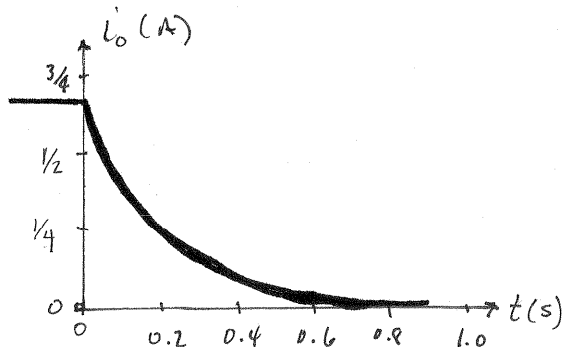

7.20 Use the differential equation approach to find $i(t)$ for $t > 0$ in the circuit in Fig. P7.20 and plot the response including the time interval just prior to switch movement. **PSV**

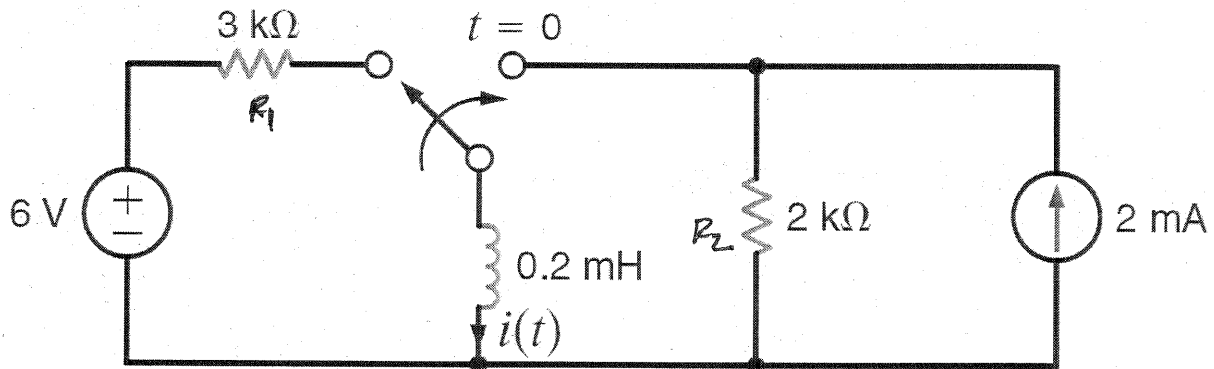


Figure P7.20

SOLUTION:

$$t=0^- : i(0^-) = \frac{6}{R_1} = 2 \text{ mA} = i(0^+)$$

$$t=0^+ : i(0^+) = 2 \text{ mA}$$



$$t > 0 : 4 = R_2 i + L \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{R_2}{L} i - \frac{4}{L} = 0 \quad i = k_1 + k_2 e^{-t/\tau}$$


$$\tau = L/R_2 = 0.1 \mu\text{s} \quad K_1 = 4/R_2 = 2 \text{ mA}$$

$$K_2 = i(0^+) - K_1 = 0$$


$$i(t) = 2 \text{ mA}$$

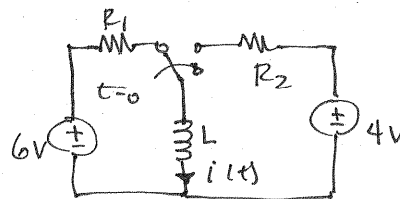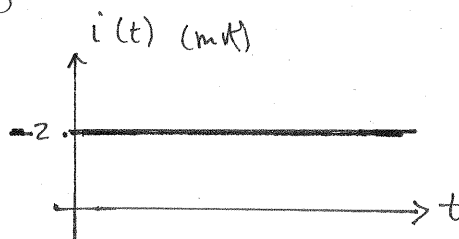

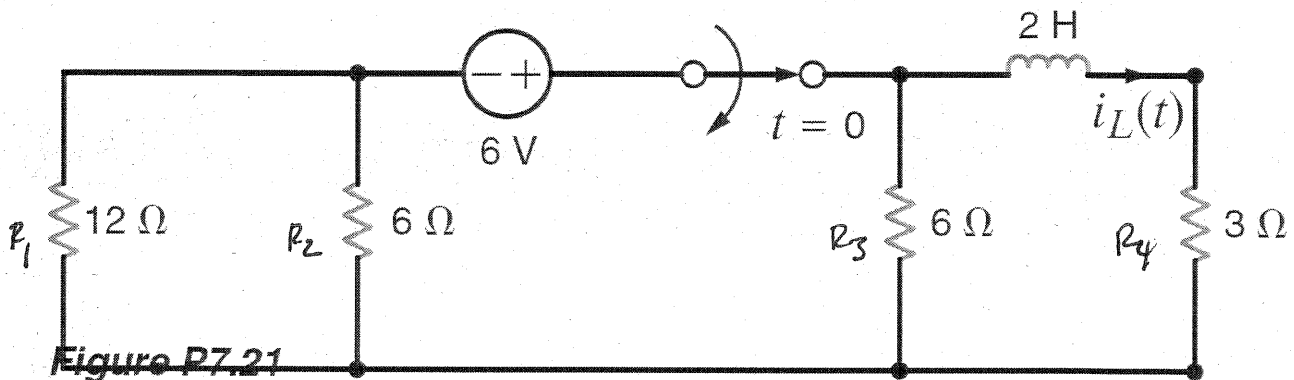7.21 Use the differential equation approach to find $i_L(t)$ for $t > 0$ in the circuit in Fig. P7.21 and plot the response including the time interval just prior to opening the switch.



SOLUTION:

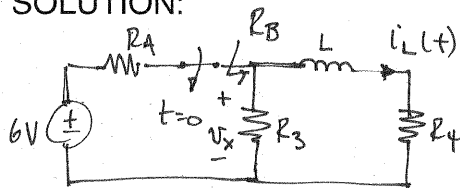

$$R_A = R_1 // R_2 = 4\Omega$$

$$R_B = R_3 // R_4 = 2\Omega$$

$$t = 0^- : \quad i_L(0^-) = v_x(0^-) / R_4 \quad v_x = \frac{6 R_B}{R_B + R_A} = 2V \quad i_L(0^-) = \frac{2}{3}A$$


$$t = 0^+ \quad i_L(0^+) = i_L(0^-) = \frac{2}{3}A$$

$$t > 0 : \quad L \frac{di_L}{dt} + i_L (R_3 + R_4) = 0 \Rightarrow \frac{di_L}{dt} + \left(\frac{R_3 + R_4}{L} \right) i = 0$$

$$i = K_1 + K_2 e^{-t/\tau} \Rightarrow \tau = \frac{L}{R_3 + R_4} = \frac{2}{9} s \quad K_1 = 0$$

$$K_2 = i_L(0^+) - K_1 = \frac{2}{3}A$$

$$i_L(t) = 0.67 e^{-4.5t} A$$

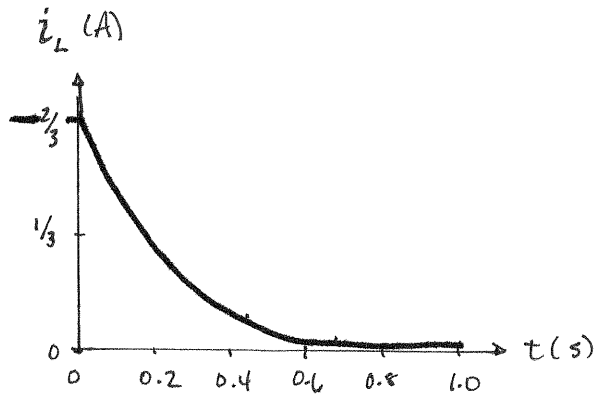

7.22 Use the differential equation approach to find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.22 and plot the response including the time interval just prior to opening the switch.


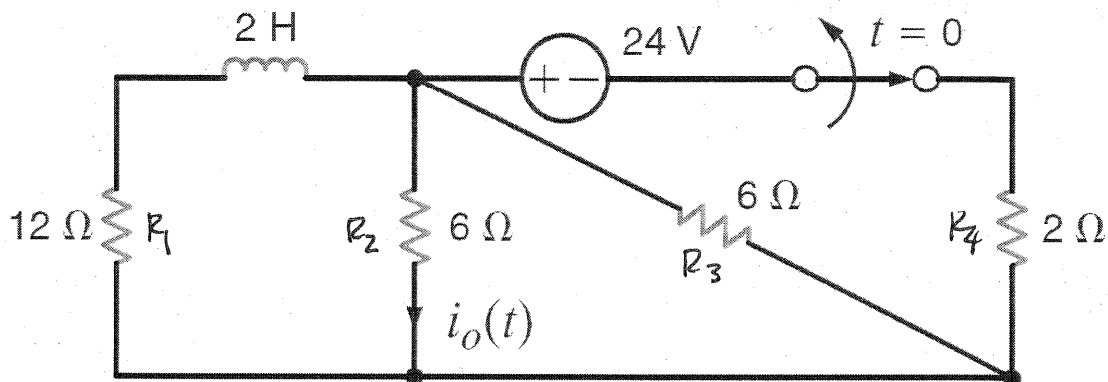


Figure P7.22

SOLUTION:

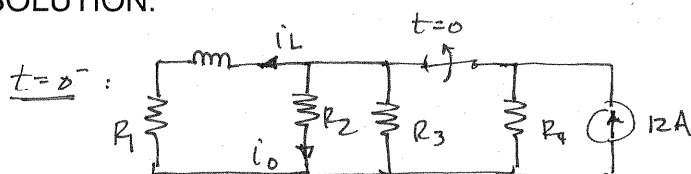

$$i_L(0^-) = \frac{12 \left(\frac{1}{R_1} \right)}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} = \frac{12}{11} \text{ A}$$

$$i_o(0^-) = \frac{12 \text{ A} \left(\frac{1}{R_2} \right)}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} = \frac{24}{11} \text{ A}$$

$$t = 0^+ \quad i_L(0^+) = \frac{12}{11} \text{ A}$$


$$i_o(0^+) = \frac{-i_L(0^+) R_3}{R_2 + R_3} = -\frac{6}{11} \text{ A}$$

$$t > 0: \quad L \frac{di_L}{dt} + i_L (R_1 + R_B) = 0 \quad R_B = R_2 // R_3 \quad i_o = \frac{-i_L R_3}{R_2 + R_3}$$

$$\frac{di_o}{dt} + \left(\frac{R_1 + R_B}{L} \right) i_o = 0 \quad \& \quad i_o(t) = K_1 + K_2 e^{-t/\tau}$$

$$\tau = \frac{L}{R_1 + R_B} = \frac{2}{15} \text{ s} \quad K_1 = 0 \quad K_2 = i_o(0^+) - K_1 = -\frac{6}{11} \text{ A}$$

$$i_o(t) = -0.545 e^{-7.5t} \text{ A}$$

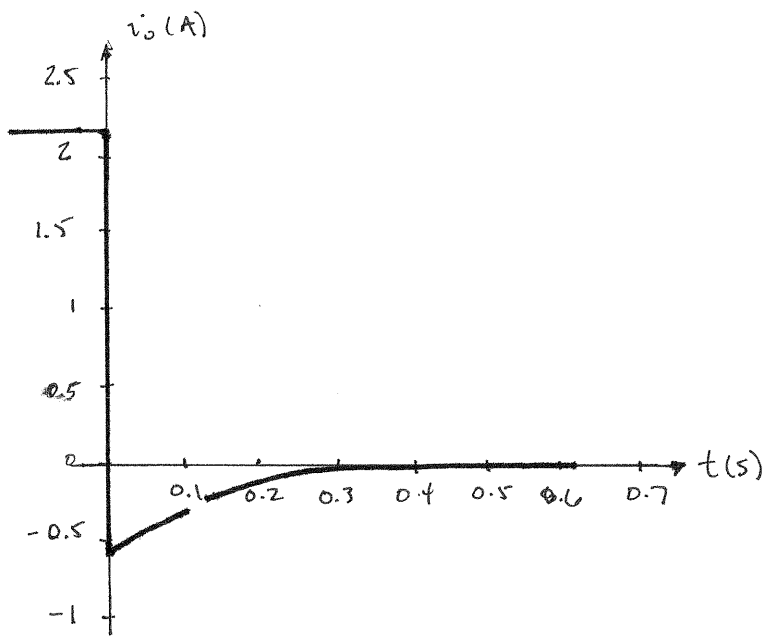

7.23 Using the differential equation approach, find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.23 and plot the response including the time interval just prior to opening the switch.


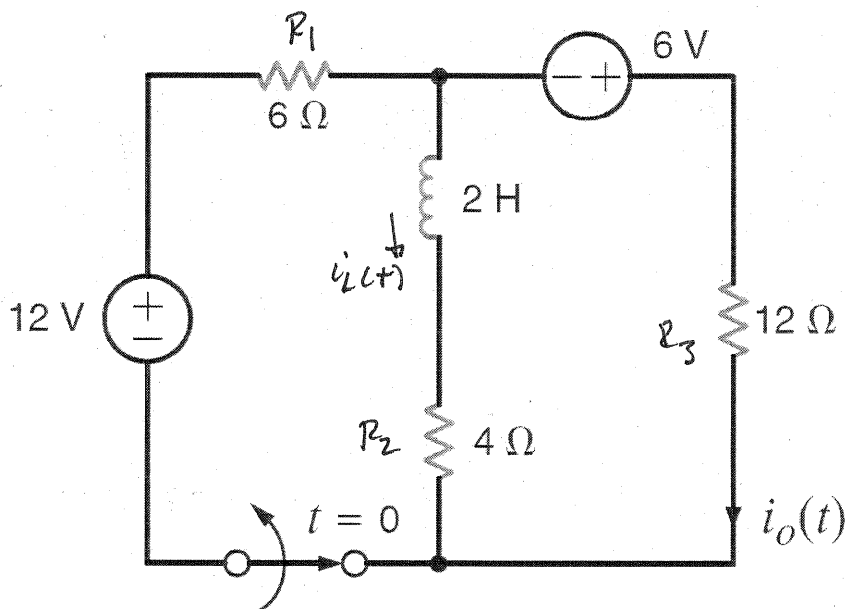


Figure P7.23

SOLUTION: By source transformation:

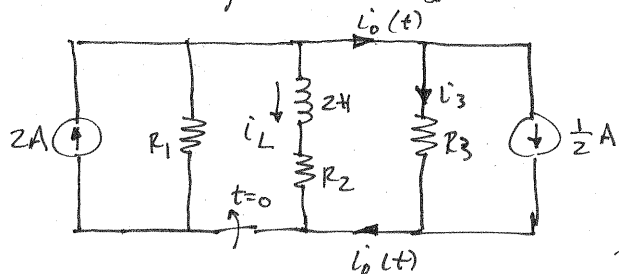

$$t=0^- \quad i_L(0^-) = \frac{(2-0.5) \frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{3}{4} \text{ A}$$

$$i_o(0^-) = i_3(0^-) + 0.5$$

$$i_3(0^-) = \frac{1.5 \left(\frac{1}{R_3}\right)}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{4} \text{ A} \quad i_o(0^-) = \frac{3}{4} \text{ A}$$


$$t=0^+: \quad i_o(0^+) = -i_L(0^+) = -\frac{3}{4} \text{ A}$$

$$t > 0: \quad 6 = R_3 i_o + R_2 i_o + L \frac{di_o}{dt} \Rightarrow \frac{di_o}{dt} + i_o \frac{(R_2 + R_3)}{L} - \frac{6}{L} = 0$$


$$i_o = k_1 + k_2 e^{-t/\tau} \Rightarrow \tau = \frac{L}{R_2 + R_3} = \frac{1}{8} \text{ s} \quad k_1 = \frac{6}{R_2 + R_3} = \frac{3}{8} \text{ A}$$

$$k_2 = i_o(0^+) - k_1 = -9/8 \text{ A}$$
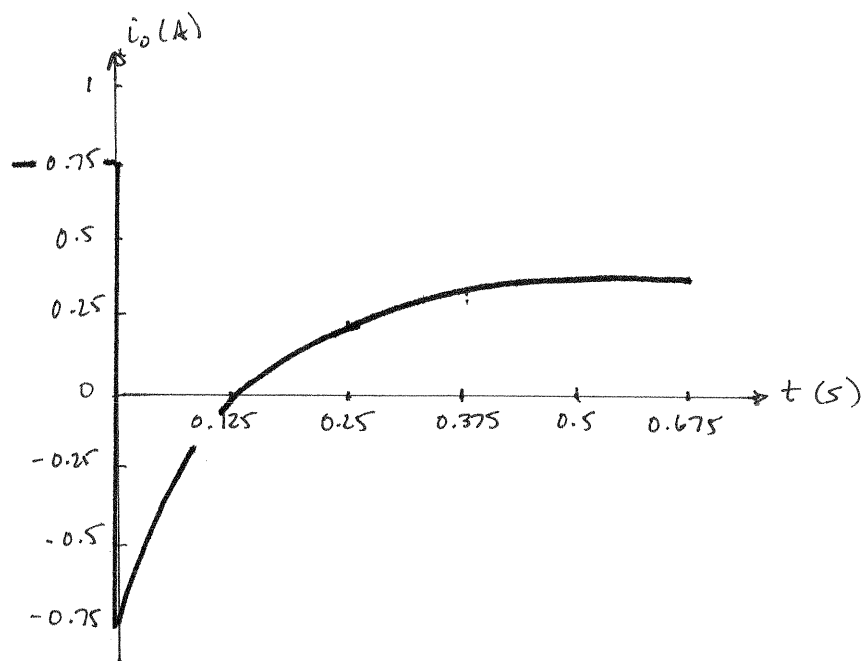
$$i_o(t) = 0.375 - 1.125 e^{-8t} \text{ A}$$



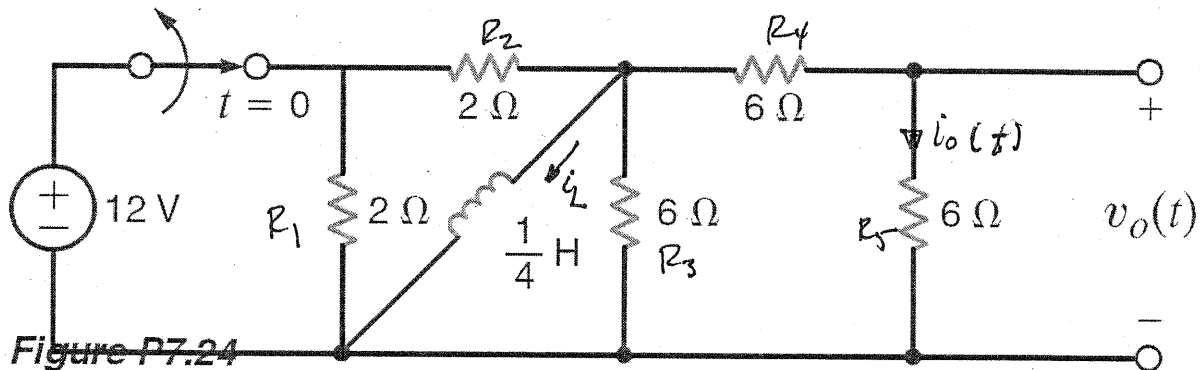7.24 Use the differential equation approach to find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.24 and plot the response including the time interval just prior to opening the switch.



SOLUTION:


$$t=0^-: i_L(0^-) = 12/R_2 = 6A \quad v_o(0^-) = 0V$$

$$t=0^+ \quad i_L(0^+) = 6A \quad v_o(0^+) = i_o R_5$$

$$v_o(0^+) = -6V$$

$$i_o = \frac{-i_L R_c}{R_A + R_c} \quad \left\{ \begin{array}{l} R_A = R_4 + R_5 = 12\Omega \\ R_c = R_3 \parallel [R_1 + R_2] \\ R_c = 2.4\Omega \end{array} \right.$$

$t > 0$

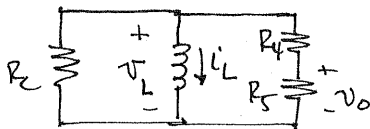

$$i_L + \frac{v_L}{R_c} + \frac{v_L}{R_A} = 0 \quad \& \quad v_L = L \frac{di_L}{dt}$$


$$\frac{di_L}{dt} + \frac{R_A R_c}{(R_A + R_c)L} i_L = 0$$

$$\text{But } v_o = -\left(\frac{i_L R_c}{R_c + R_A}\right) R_5 \Rightarrow \frac{dv_o}{dt} + \frac{R_A R_c}{(R_A + R_c)L} v_o = 0$$

$$v_o = K_1 + K_2 e^{-t/\tau} \Rightarrow \tau = \frac{L(R_A + R_c)}{R_A R_c} = \frac{1}{8} s \quad K_1 = 0$$

$$K_2 = v_o(0^+) - K_1 = -6V$$

$$v_o = -6e^{-8t} V$$

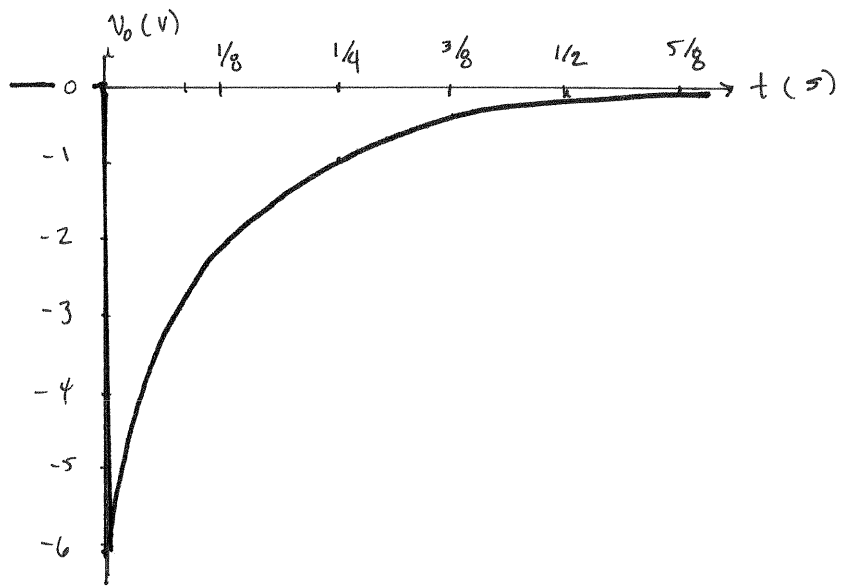

7.25 Use the differential equation approach to find $i(t)$ for $t > 0$ in the circuit in Fig. P7.25 and plot the response including the time interval just prior to opening the switch.

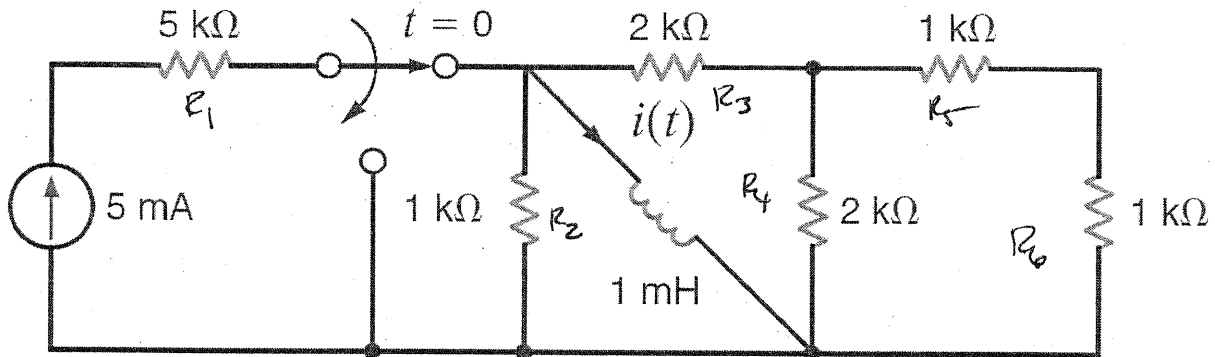



Figure P7.25

SOLUTION:

$$t=0^-: i(0^-) = 5 \text{ mA}$$

$$t=0^+: i(0^+) = i(0^-) = 5 \text{ mA}$$

$t > 0$:

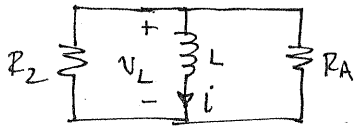

$$R_A = R_3 + \{R_4 \parallel [R_5 + R_6]\}$$

$$R_A = 3 \text{ k}\Omega$$

$$\tau = \frac{L(R_A + R_2)}{R_A R_2} = \frac{4}{3} \mu\text{s}$$


$$i + \frac{v_L}{R_2} + \frac{v_L}{R_A} = 0 \quad \& \quad v_L = L \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{R_A R_2}{(R_A + R_2)L} i = 0$$

$$i = K_1 + K_2 e^{-t/\tau}$$

$$K_1 = 0 \quad K_2 = i(0^+) - K_1 = 5 \text{ mA}$$
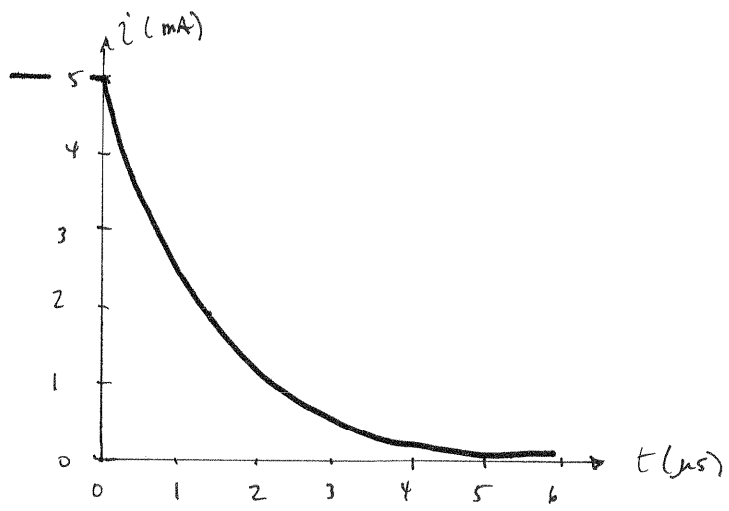
$$i(t) = 5 e^{-2.5 \times 10^5 t} \text{ mA}$$



7.26 Find $v_C(t)$ for $t > 0$ in the network in Fig. P7.26 using the step-by-step method. CS


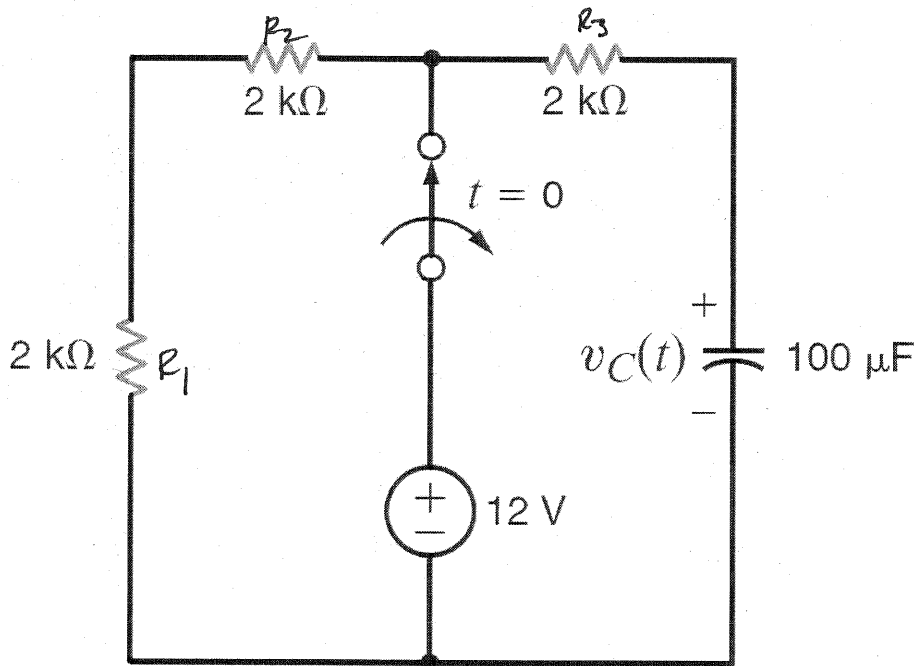
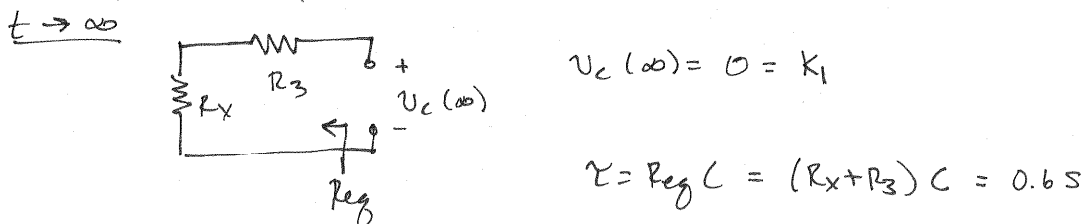
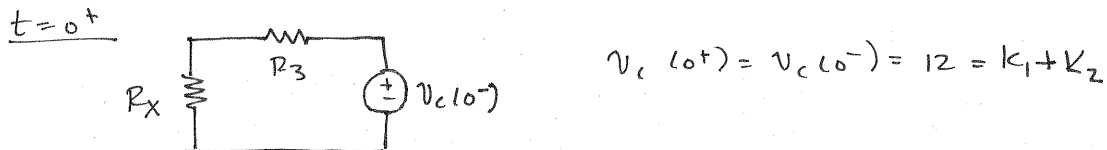


Figure P7.26

SOLUTION:

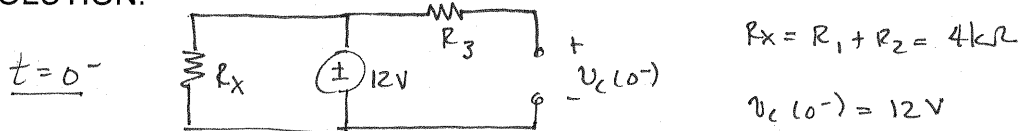

$$v_C(t) = K_1 + K_2 e^{-t/\tau}$$

$$v_C(t) = 12e^{-1.67t} \text{ V}$$

7.27 Use the step-by-step method to find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.27.


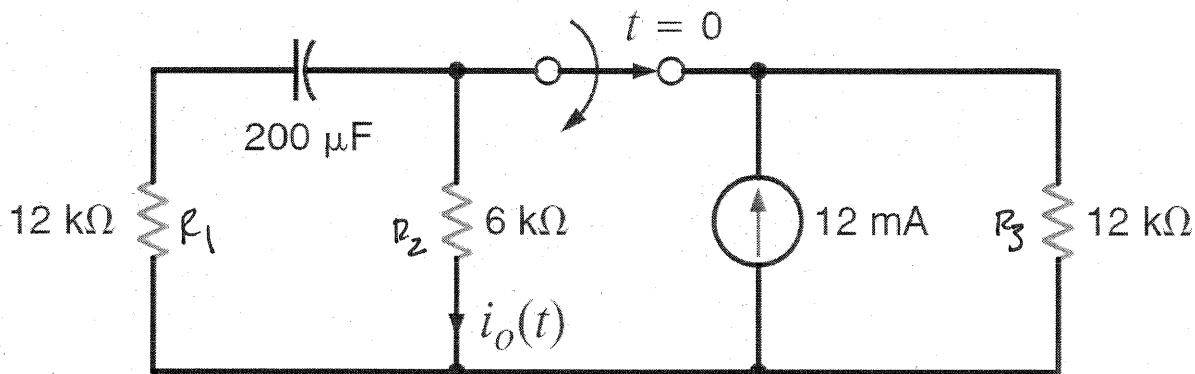



Figure P7.27

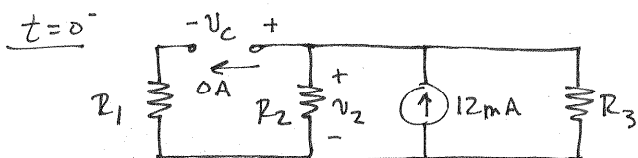SOLUTION: $i_o(t) = k_1 + k_2 e^{-t/\tau}$




$$v_2 = v_c = 12 \times 10^{-3} \left[\frac{R_3 R_2}{R_3 + R_2} \right]$$

$$v_c(0^-) = 48 \text{ V}$$

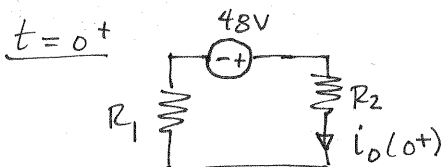
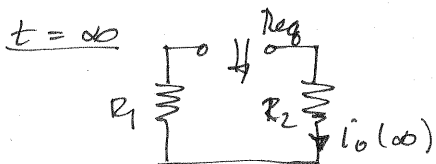
$$i_o(0^+) = \frac{48}{R_1 + R_2} = 2.67 \text{ mA} = k_1 + k_2$$



$$i_o(\infty) = 0 = k_1$$

$$\tau = C R_{eq} \quad R_{eq} = R_1 + R_2 = 18 \text{ k}\Omega$$

$$\tau = 3.6 \text{ s}$$

$$i_o(t) = 2.67 e^{-t/3.6} \text{ mA}$$

7.28 Use the step-by-step technique to find $i_o(t)$ for $t > 0$ in the network in Fig. P7.28. **CS**


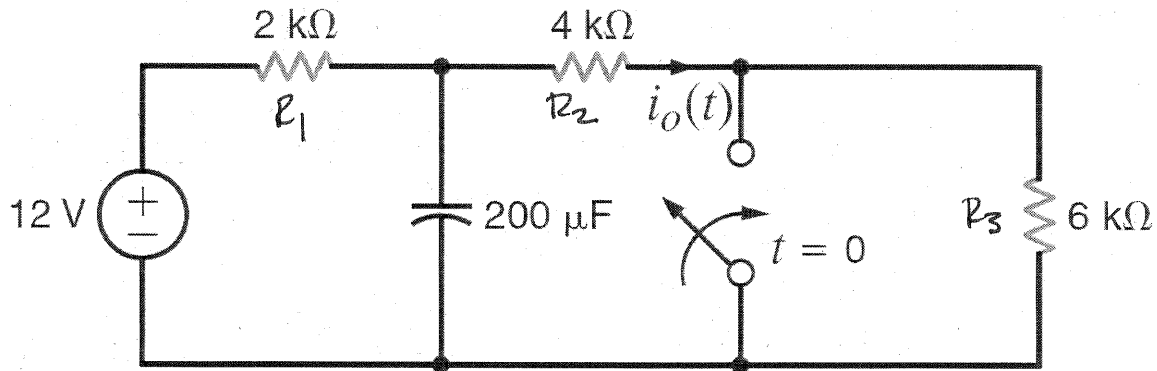



Figure P7.28

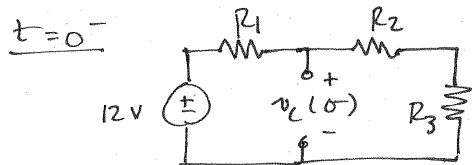SOLUTION: $i_o(t) = k_1 + k_2 e^{-t/\tau}$




By voltage division: $v_c(0^-) = \frac{12(R_2 + R_3)}{R_1 + R_2 + R_3}$


$$v_c(0^-) = 10\text{V}$$

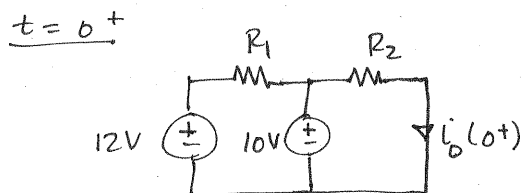
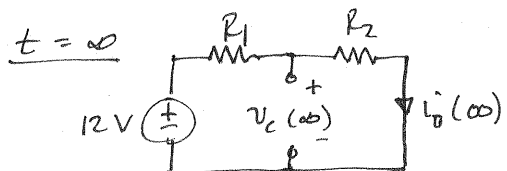
$$i_o(0^+) = 10/R_2 = 2.5\text{mA} = k_1 + k_2$$


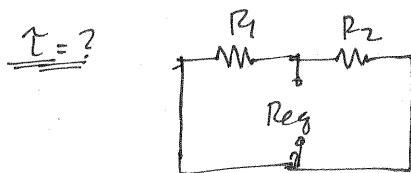
$$i_o(\infty) = \frac{12}{R_1 + R_2} = 2\text{mA} = k_1$$



$$\tau = C R_{eq} \quad R_{eq} = R_1 // R_2 = \frac{4}{3}\text{k}\Omega$$

$$\tau = 0.267\text{s}$$

$$i_o(t) = 2 + 0.5 e^{-3.75t} \text{ mA}$$

7.29 Use the step-by-step method to find $v_o(t)$ for $t > 0$ in the network in Fig. P7.29.



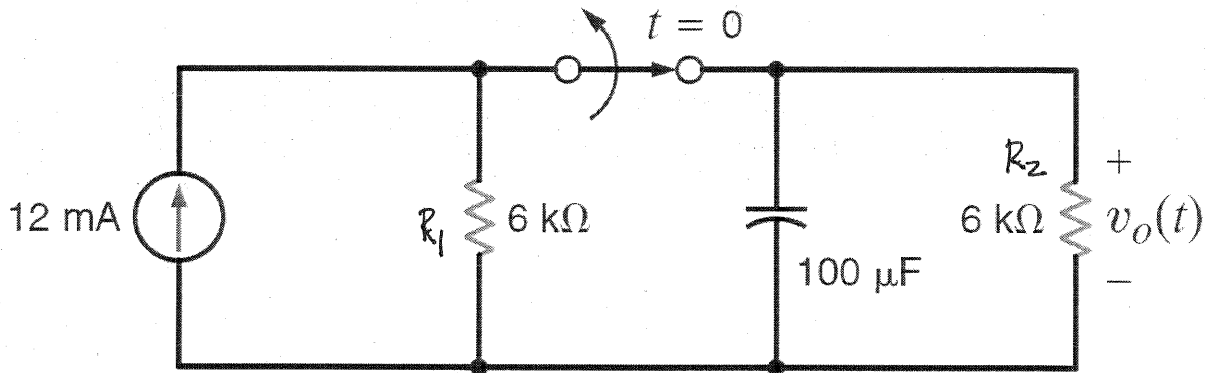


Figure P7.29

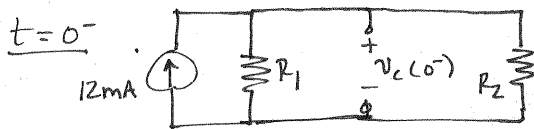
SOLUTION: $v_o(t) = K_1 + K_2 e^{-t/\tau}$


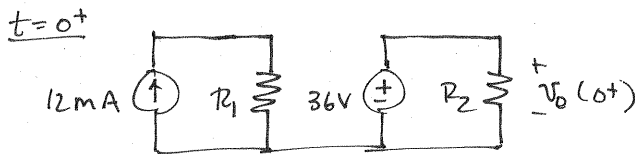
$$v_c(0^-) = 12 \times 10^{-3} \frac{(R_1 R_2)}{R_1 + R_2} = 36 \text{ V}$$



$$v_o(0^+) = 36 = K_1 + K_2$$

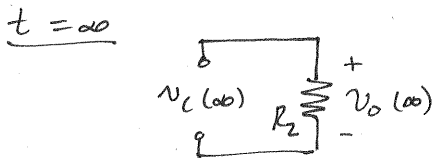

$$v_o(\infty) = 0 = K_1$$

$\tau = ?$ $\tau = R_{eq} C$ $R_{eq} = R_2 = 6 \text{ k}\Omega$ $\tau = 0.6 \text{ s}$

$$v_o(t) = 36 e^{-t/0.6} \text{ V}$$

7.30 Use the step-by-step method to find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.30.


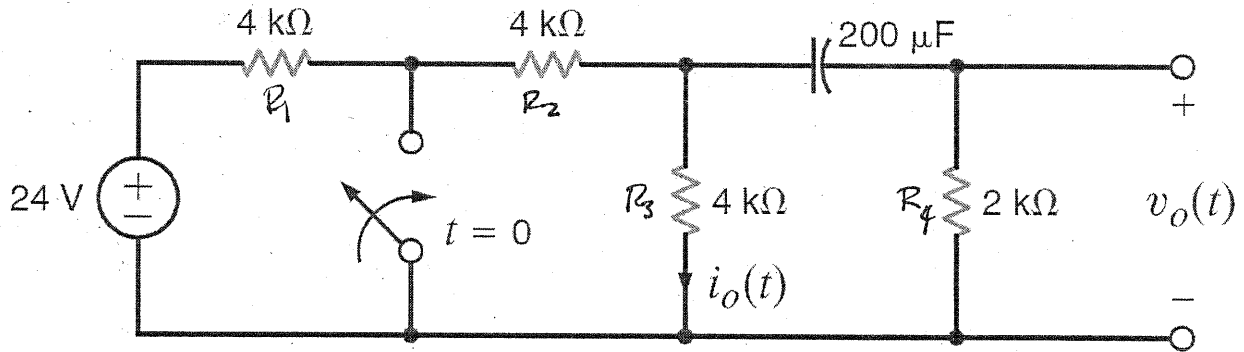


Figure P7.30

SOLUTION:


$$i_o(t) = K_1 + K_2 e^{-t/\tau}$$

$t = 0^-$

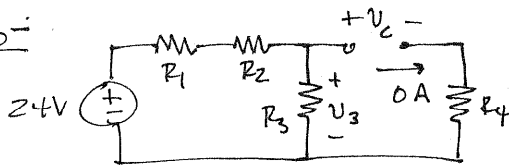

$$v_c = v_3 = \frac{24 R_3}{R_1 + R_2 + R_3} = 8V$$


$t = 0^+$

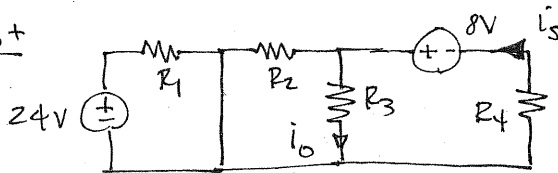

$$i_s = \frac{8}{R_4 + R_x} \quad R_x = \frac{R_2 R_3}{R_2 + R_3} = 2k\Omega$$


$$i_o = \frac{i_s R_2}{R_2 + R_3} = 1mA = K_1 + K_2$$

$t = \infty$

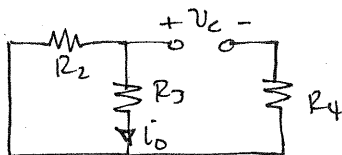

$$i_o(\infty) = 0 = K_1$$

$\tau = ?$

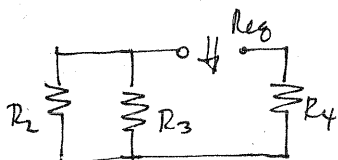

$$\tau = R_{eq} C$$

$$R_{eq} = \frac{R_2 R_3}{R_2 + R_3} + R_4 = 4k\Omega$$

$$\tau = 0.8s$$


$$i_o(t) = e^{-1.25t} \text{ mA}$$

7.31 Find $v_o(t)$ for $t > 0$ in the network in Fig. P7.30 using the step-by-step technique.


SOLUTION:

$$v_o(t) = K_1 + K_2 e^{-t/\tau}$$
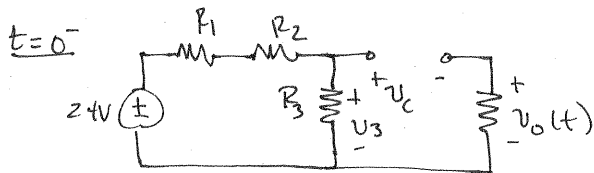
$$R_1 = R_2 = R_3 = 4\text{ k}\Omega \quad R_4 = 2\text{ k}\Omega$$



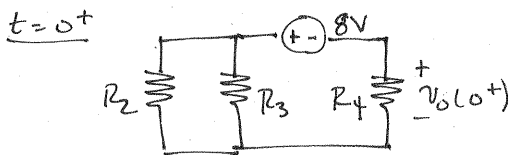
$$v_c = v_3 = \frac{24 R_3}{R_1 + R_2 + R_3} = 8\text{ V}$$




$$R_x = R_2 \parallel R_3 = 2\text{ k}\Omega$$
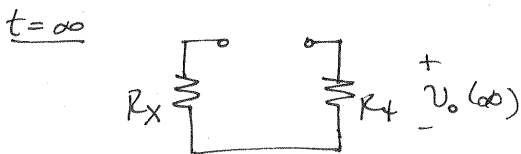
$$v_o(0^+) = \frac{-8 R_4}{R_4 + R_x} = -4\text{ V} = K_1 + K_2$$



$$v_o(\infty) = 0 = K_1$$

$\tau = ?$

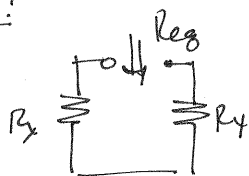

$$\tau = R_{\text{Th}} C \quad R_{\text{Th}} = R_x + R_4 = 4\text{ k}\Omega$$

$$\tau = 0.8\text{ s}$$

$$v_o(t) = -4 e^{-1.25t} \text{ V}$$

7.32 Use the step-by-step technique to find $i_o(t)$ for $t > 0$ in the network in Fig. P7.32.


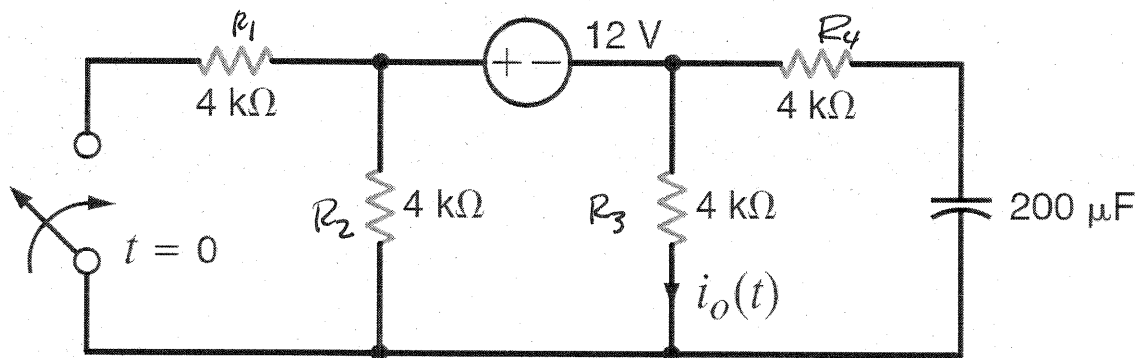


Figure P7.32

SOLUTION:


$$i_o(t) = K_1 + K_2 e^{-t/\tau}$$

$t = 0^-$


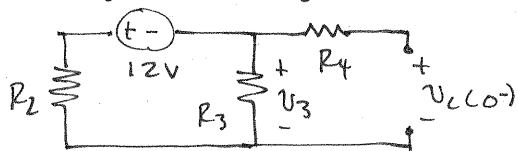


$$U_C(0^-) = U_3 = -\frac{12 R_3}{R_2 + R_3} = -6V$$

$t = 0^+$

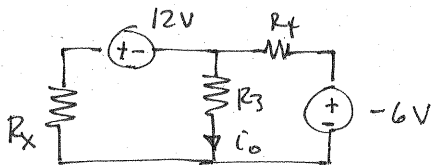


$$R_x = R_1 // R_2 = 2k\Omega$$

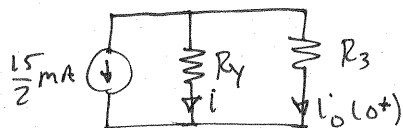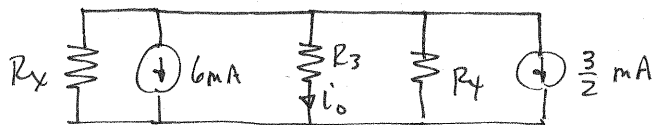


$$R_y = R_x // R_4 = \frac{4}{3} k\Omega$$

$$i_o(0^+) = \frac{-15}{2000} \frac{R_y}{R_y + R_3} = -1.875 mA = K_1 + K_2$$

$t = \infty$

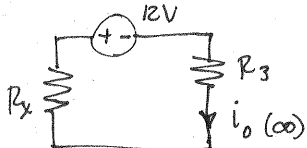
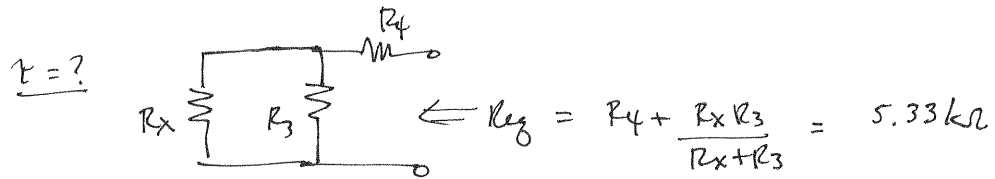
$$i_o(\infty) = \frac{-12}{R_x + R_3} = -2 mA = K_1$$



$$\tau = R_{eq} C = 1.07 \text{ s}$$

$$i_o(t) = -2 + 0.125 e^{-0.9375 t} \text{ mA}$$

7.33 Find $v_o(t)$ for $t > 0$ in the network in Fig. P7.33 using the step-by-step method. **CS**



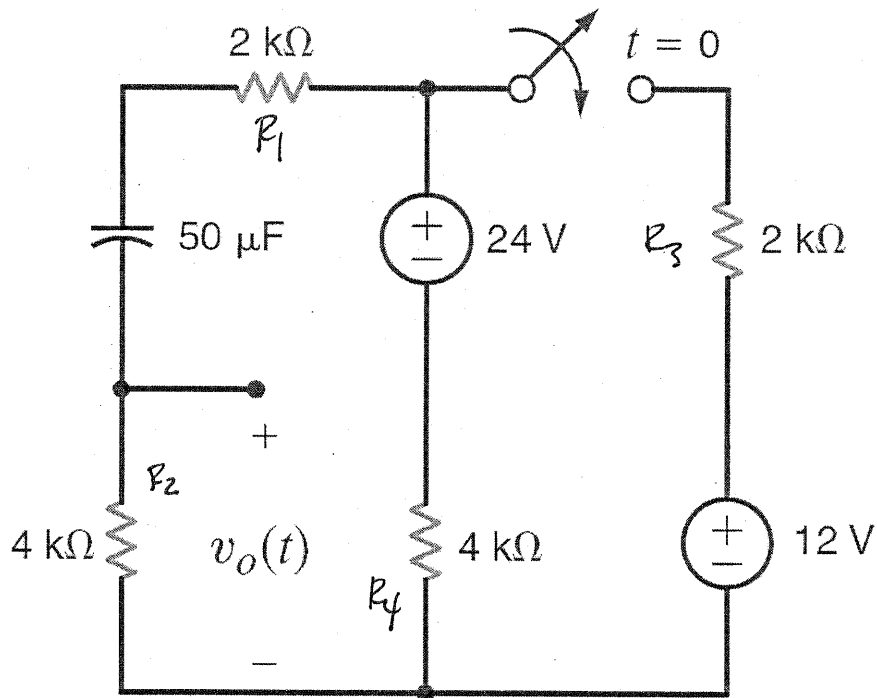


Figure P7.33

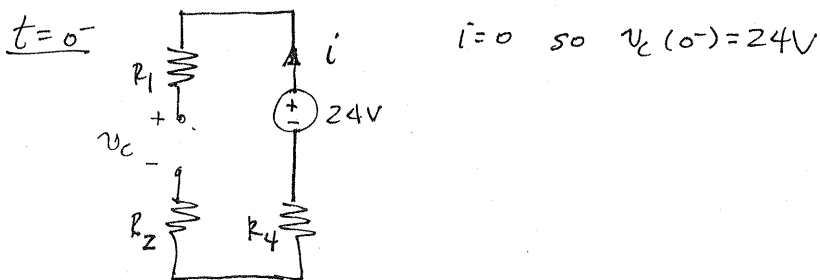SOLUTION: $v_o(t) = K_1 + K_2 e^{-t/\tau}$



$t=0^+$

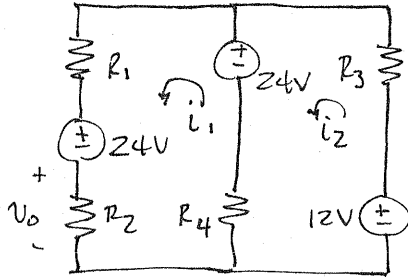

$$24 = i_1 (R_1 + R_2 + R_4) - i_2 R_4 + 24$$

$$\text{or, } i_1 (R_1 + R_2 + R_4) = i_2 R_4$$


$$12 = i_2 (R_3 + R_4) + 24 - i_1 R_4$$

$$\text{or } i_1 R_4 - i_2 (R_3 + R_4) = 12$$

$$i_1 = \frac{-12}{11} \text{ mA} \quad v_o(0^+) = i_1 R_2$$


$$v_o(0^+) = \frac{48}{11} \text{ V} = k_1 + k_2$$

$t=\infty$

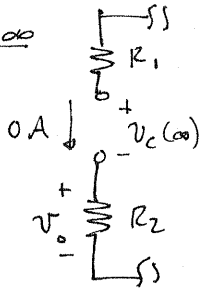

$$v_o(\infty) = 0 = k_1$$

$\tau = ?$

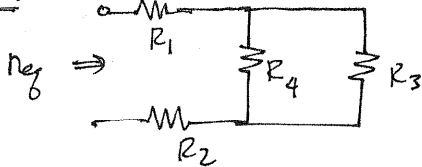

$$R_{eq} = R_1 + R_2 + \frac{R_3 R_4}{R_3 + R_4} = 7.33 \text{ k}\Omega$$

$$\tau = 367 \text{ ms}$$

$$v_o(t) = -4.36 e^{-2.73 t} \text{ V}$$

7.34 Find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.34 using the step-by-step method. **PSV**



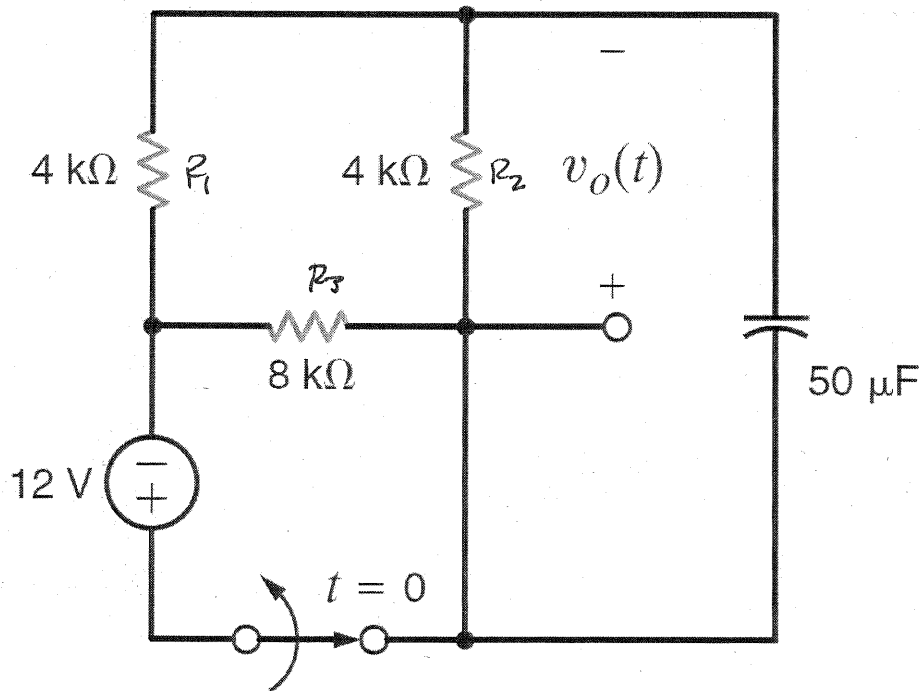


Figure P7.34

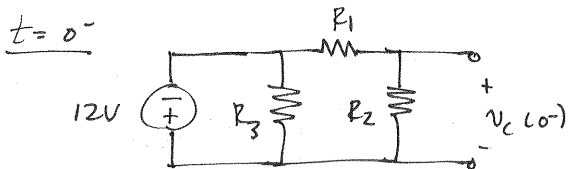SOLUTION: $v_o(t) = k_1 + k_2 e^{-t/\tau}$



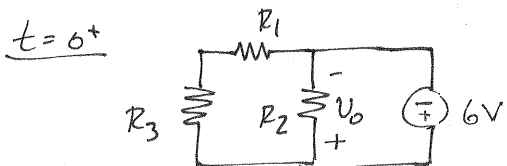
$$v_o(0^-) = -12 \left(\frac{R_2}{R_1 + R_2} \right) = -6 \text{ V}$$



$$v_o(0^+) = 6 \text{ V} = k_1 + k_2$$

$t = \infty$
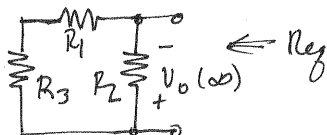
$$v_o(\infty) = 0 = k_1 \quad R_{eq} = R_2 (R_1 + R_3) / (R_1 + R_2 + R_3) = 3 \text{ k}\Omega$$



$$\tau = R_{eq} C = 150 \text{ ms}$$

$$v_o(t) = 6 e^{-6.67t} \text{ V}$$

7.35 Use the step-by-step method to find $i_o(t)$ for $t > 0$ in the network in Fig. P7.35. **CS**



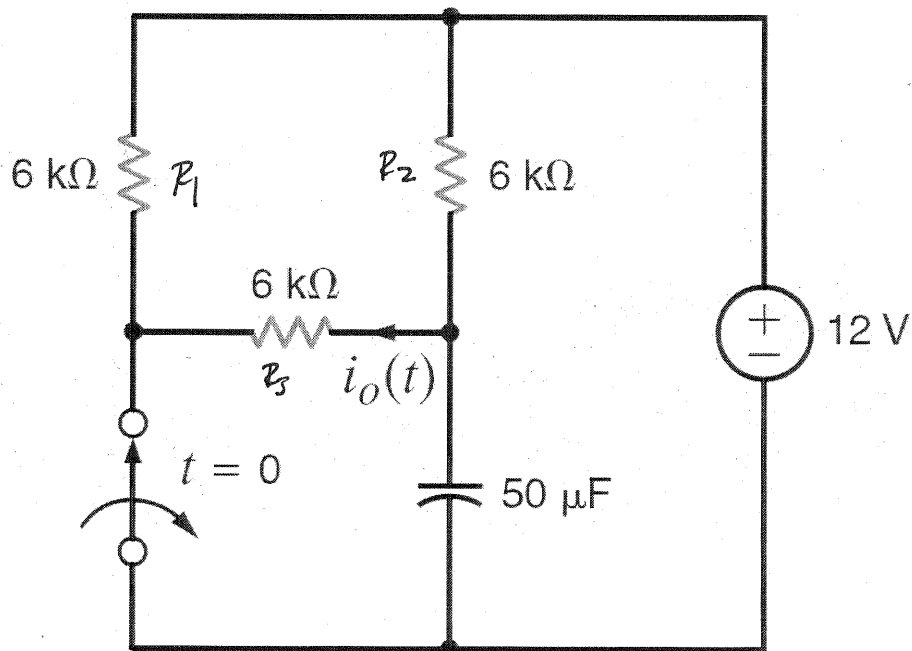


Figure P7.35

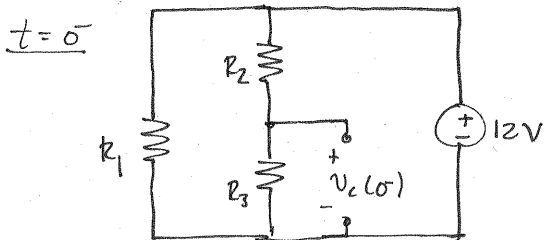SOLUTION: $i_o(t) = k_1 + k_2 e^{-t/\tau}$



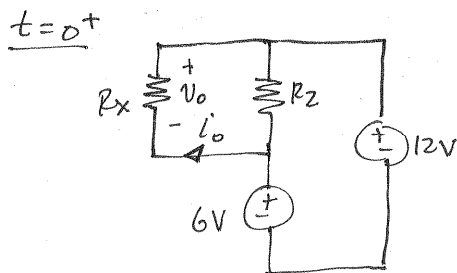
$$v_c(0^-) = \frac{12 R_3}{R_3 + R_2} = 6V$$



$$R_x = R_1 + R_3 = 12k\Omega \quad v_o = 12 - 6 = 6V$$

$$i_o = -\frac{v_o}{R_x} = -0.5mA = k_1 + k_2$$

$t = \infty$

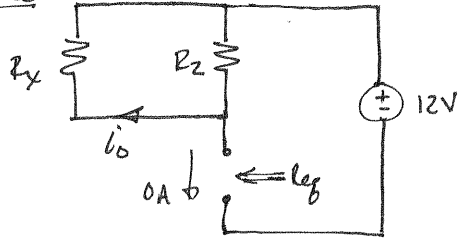

$$i_0 = 0 = K_1$$

$\tau = ?$

$$R_{eq} = \frac{R_x R_2}{R_x + R_2} = 4k\Omega$$

$$\tau = R_{eq} C = 0.25$$

$$i_0(t) = -0.5 e^{-st} \text{ mA}$$

7.36 Use the step-by-step technique to find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.36.


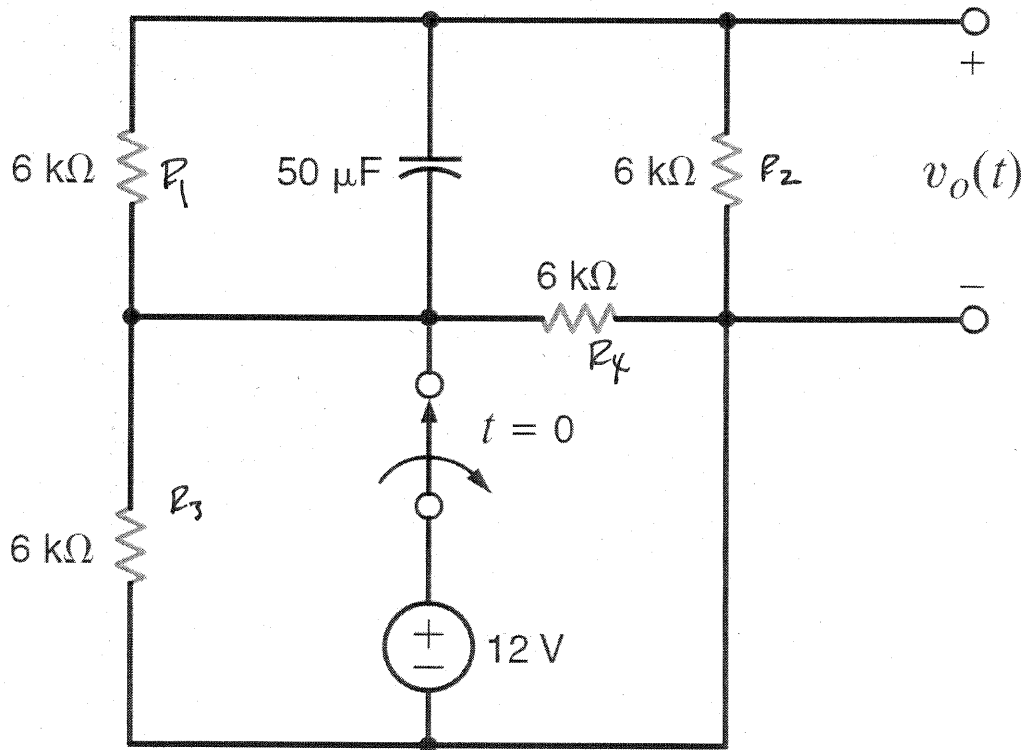



Figure P7.36

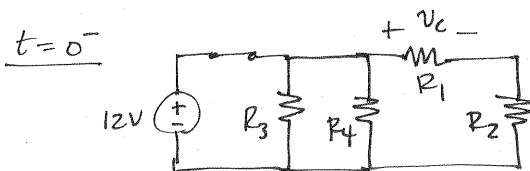SOLUTION: $v_o(t) = k_1 + k_2 e^{-t/\tau}$




$$v_c(0^-) = \frac{12 R_1}{R_1 + R_2} = 6V$$

$$R_x = R_3 // R_4 = 3k\Omega$$

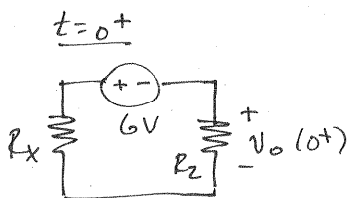

$t = \infty$: $v_o(\infty) = 0 = k_1$

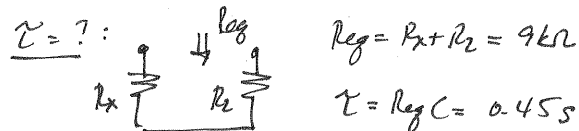

$$R_{eq} = R_x + R_2 = 9k\Omega$$

$$\tau = R_{eq} C = 0.45s$$

$$v_o(0^+) = \frac{-6 R_2}{R_x + R_2} = -4V = k_1 + k_2$$

$$v_o(t) = -4e^{-2.22t} \text{ V}$$

7.37 Find $i_o(t)$ for $t > 0$ in the network in Fig. P7.37 using the step-by-step method. CS


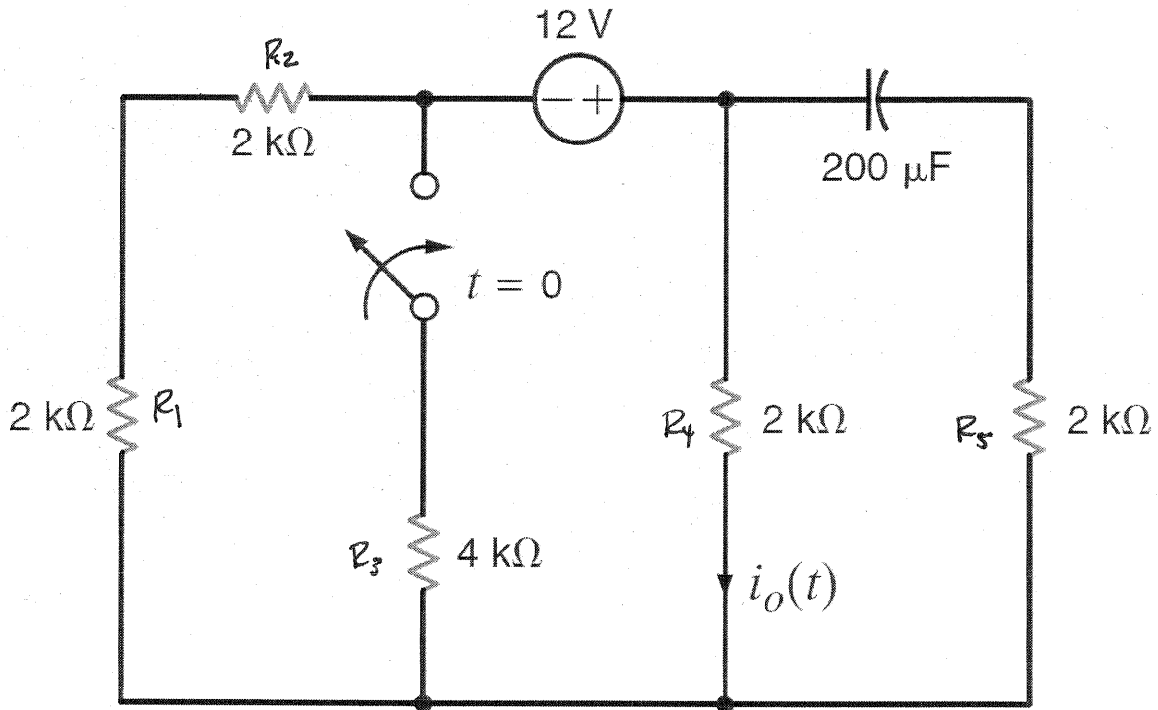



Figure P7.37

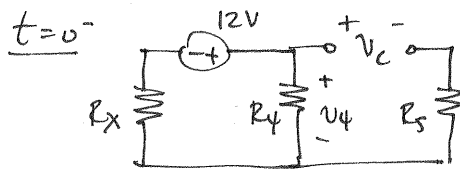SOLUTION: $i_o(t) = k_1 + k_2 e^{-t/\tau}$





$$v_C(0^-) = v_4 = \frac{12 R_4}{R_4 + R_x} \quad R_x = R_1 + R_2 = 4 \text{ k}\Omega$$

$$v_C(0^-) = 8 \text{ V}$$

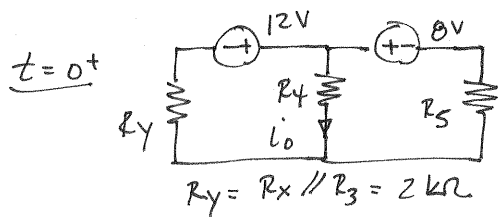


$$R_y = R_x // R_3 = 2 \text{ k}\Omega$$

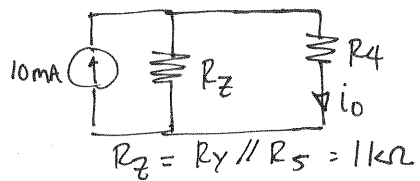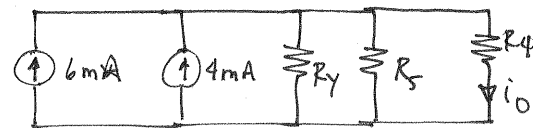


$$R_z = R_y // R_5 = 1 \text{ k}\Omega$$
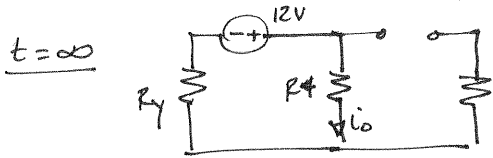
$$i_o(0^+) = \frac{10^{-2} R_z}{R_z + R_4} = 3.33 \text{ mA} = k_1 + k_2$$



$$i_o(\infty) = \frac{+12}{R_Y + R_4} = +3\text{mA} = K_1$$

$\tau = ?$

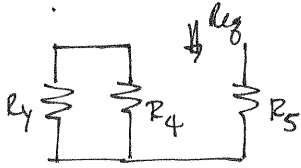

$$R_{eq} = R_5 + (R_4 // R_Y) = 3\text{k}\Omega$$

$$\tau = R_{eq} C = 0.65$$

$$i_o(t) = 3 + 0.33 e^{-1.67t} \text{ mA}$$

7.38 Use the step-by-step technique to find $i_o(t)$ for $t > 0$ in the network in Fig. P7.38.


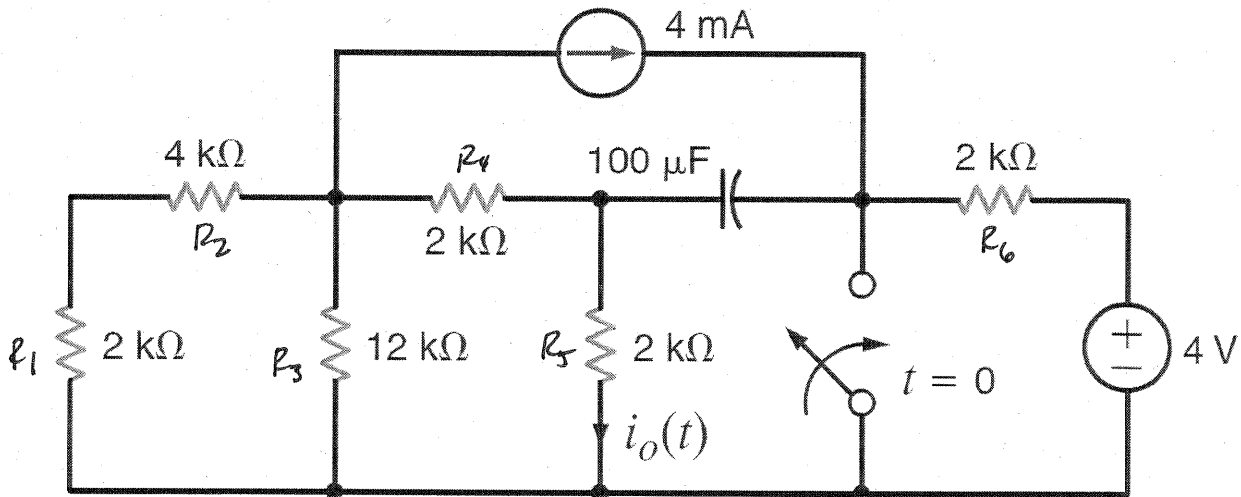


Figure P7.38

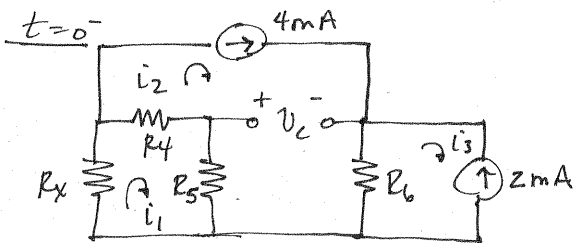SOLUTION: $i_o(t) = K_1 + K_2 e^{-t/\tau}$




$$R_x = R_3 \parallel (R_1 + R_2) = 4 \text{ k}\Omega$$

$$i_2 = 4 \text{ mA} \quad i_3 = -2 \text{ mA}$$

$$i_1 (R_x + R_4 + R_5) - i_2 (R_4 + R_5) = 0$$


$$i_1 = 2 \text{ mA}$$
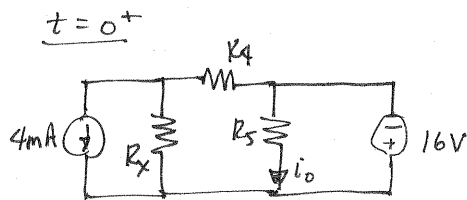
$$v_C(0^-) = (i_1 - i_2) R_5 + (i_3 - i_2) R_6 = -16 \text{ V}$$



$$i_o(0^+) = \frac{-16}{R_5} = -8 \text{ mA}$$

$$K_1 + K_2 = -8 \text{ mA}$$

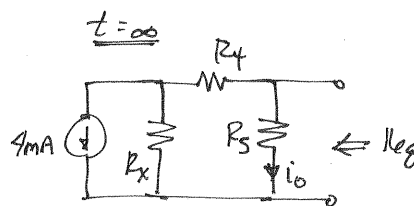

$$i_o(\infty) = \frac{-4 \times 10^{-3} R_x}{R_x + R_4 + R_5}$$

$$i_o(\infty) = -2 \text{ mA} = K_1$$

$\tau = ?$

$$R_{eq} = R_5 \parallel (R_4 + R_x) = 1.5 \text{ k}\Omega$$

$$\tau = R_{eq} C = 0.15 \text{ s}$$

$$i_o(t) = -2 - 6e^{-6.67t} \text{ mA}$$

7.39 Use the step-by-step method to find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.39.



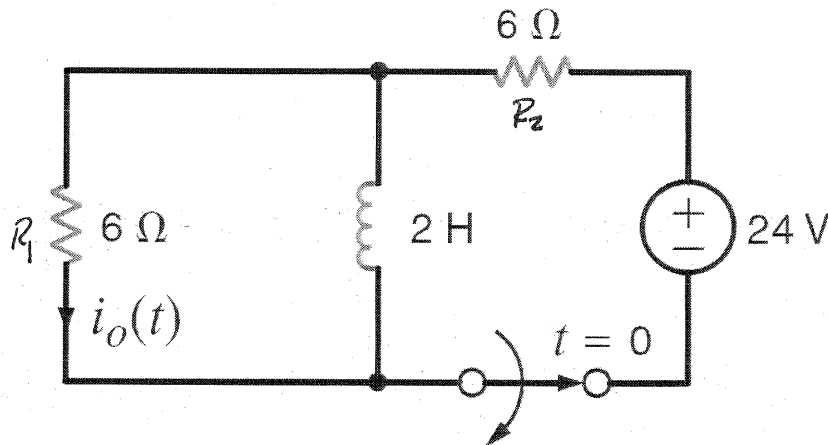


Figure P7.39

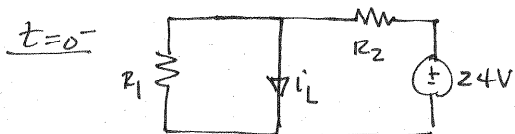SOLUTION: $i_o(t) = K_1 + K_2 e^{-t/\tau}$




$$i_L(0^-) = 24/R_2 = 4A$$

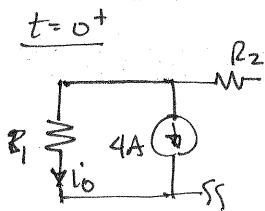


$$i_o(0^+) = -4A$$

$$K_1 + K_2 = -4A$$

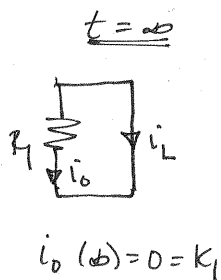

$$i_o(\infty) = 0 = K_1$$

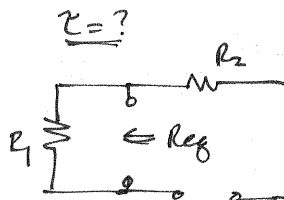

$$R_{eq} = R_1 = 6\Omega$$

$$\tau = L/R_{eq} = \frac{1}{3} s$$

$$i_o(t) = -4e^{-3t} A$$

7.40 Find $i_o(t)$ for $t > 0$ in the network in Fig. P7.40 using the step-by-step method.


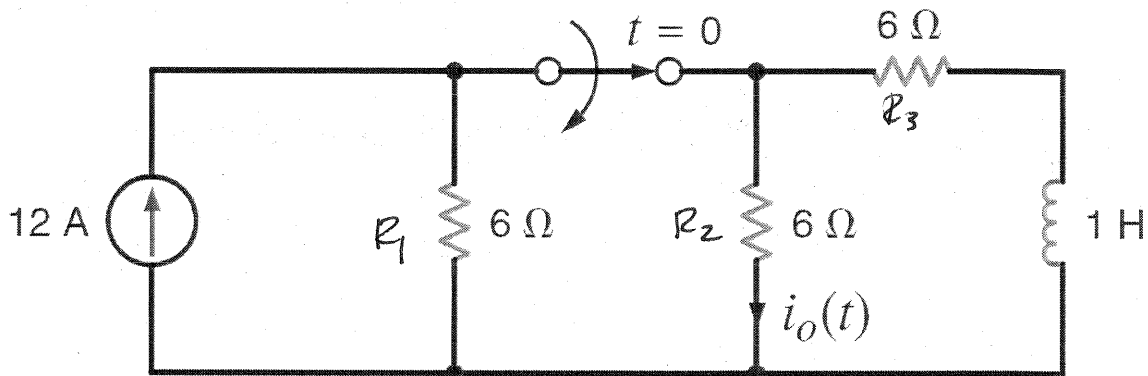





Figure P7.40

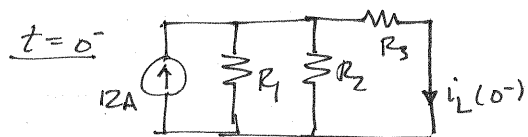SOLUTION: $i_o(t) = K_1 + K_2 e^{-t/\tau}$



$$R_x = R_1 // R_2 = 3 \Omega$$
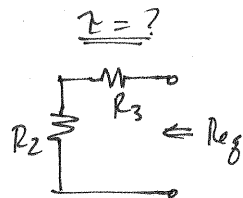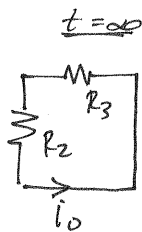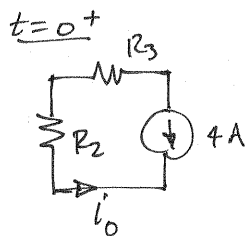
$$i_L(0^-) = \frac{12 R_x}{R_x + R_3} = 4 \text{ A}$$



$$R_{eq} = R_2 + R_3 = 12 \Omega$$

$$\tau = L / R_{eq} = \frac{1}{12} \text{ s}$$

$$i_o = -4 \text{ A} = K_1 + K_2$$

$$i_o(\infty) = 0 = K_1$$

$$i_o(t) = -4 e^{-12t} \text{ A}$$

7.41 Find $i_o(t)$ for $t > 0$ in the network in Fig. P7.41 using the step-by-step method. **CS**


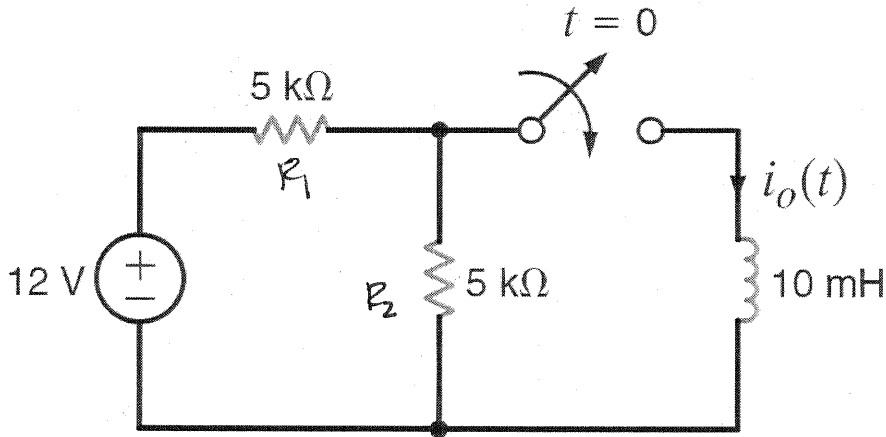



Figure P7.41

SOLUTION: $i_o(t) = K_1 + K_2 e^{-t/\tau}$


$t=0^-$

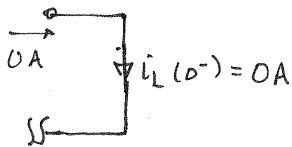


$t=0^+$

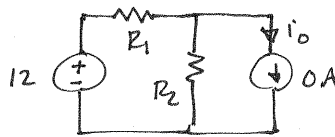

$t=\infty$

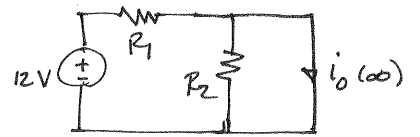

$\tau = ?$

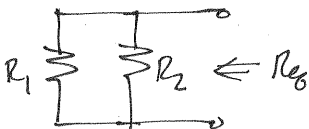

$$R_{eq} = R_1 // R_2 = 2.5k\Omega$$

$$\tau = \frac{L}{R_{eq}} = 4\mu s$$

$$i_o(t) = 2.4 - 2.4e^{-2.5 \times 10^5 t} \text{ mA}$$

7.42 Find $v_o(t)$ for $t > 0$ in the network in Fig. P7.42 using the step-by-step method.


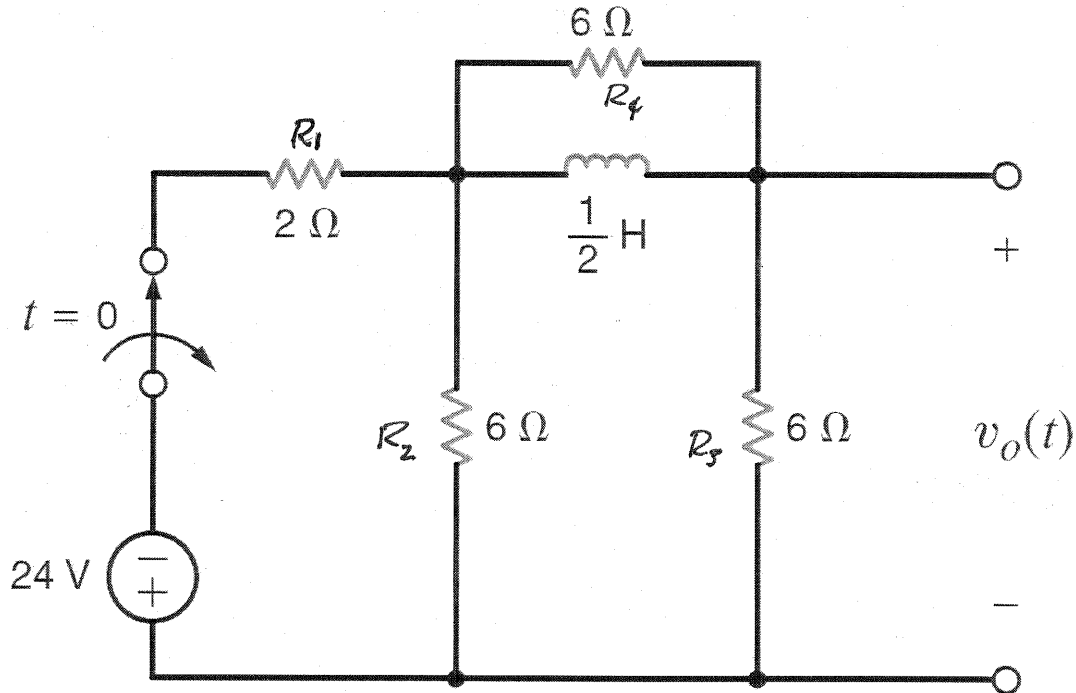
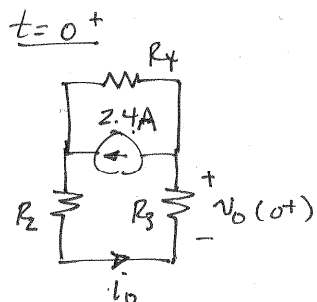


Figure P7.42

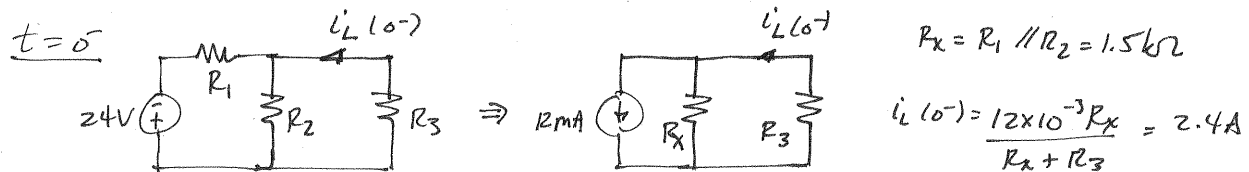
SOLUTION: $v_o(t) = k_1 + k_2 e^{-t/\tau}$




$$i_o = \frac{2.4 R_4}{R_4 + R_3 + R_2} = 0.8 \text{ mA}$$

$$v_o(0^+) = -R_3 i_o(0^+) = -4.8 \text{ V} = k_1 + k_2$$

$t = \infty$

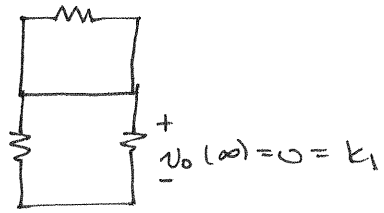

$\tau = ?$

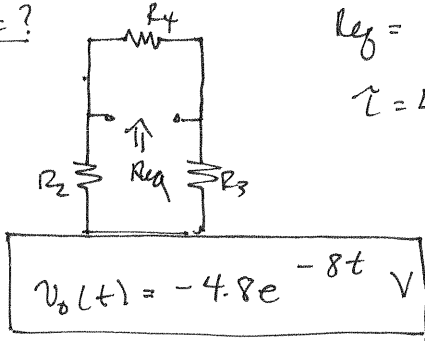

$$R_{eq} = R_4 // (R_2 + R_3) = 4 \Omega$$

$$\tau = L / R_{eq} = \frac{1}{8} \text{ s}$$

$$v_o(t) = -4.8 e^{-8t} \text{ V}$$

7.43 Use the step-by-step method to find $v_o(t)$ for $t > 0$ in the network in Fig. P7.43. **PSV**



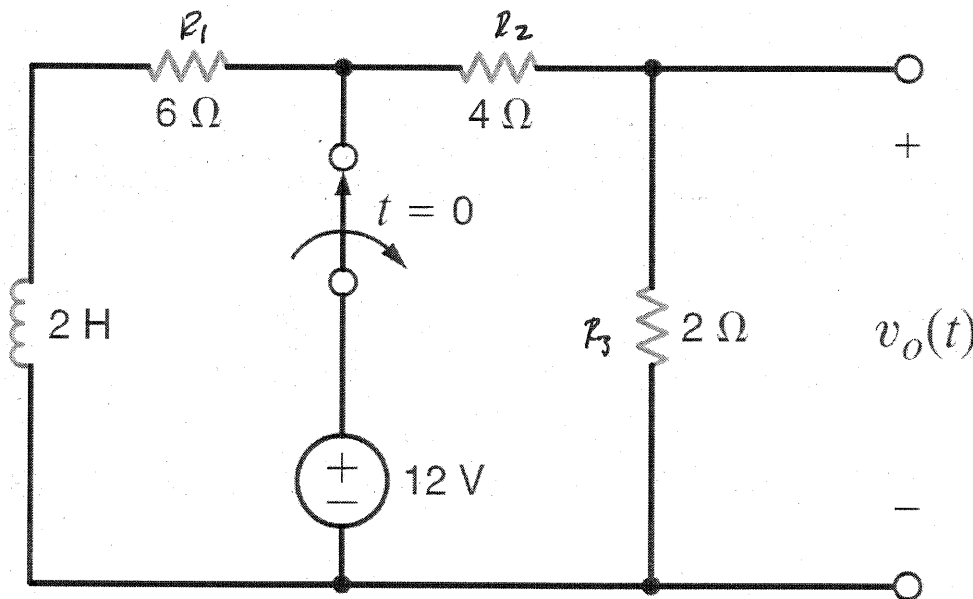


Figure P7.43

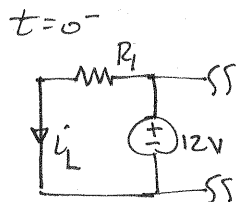
SOLUTION: $v_o(t) = k_1 + k_2 e^{-t/\tau}$



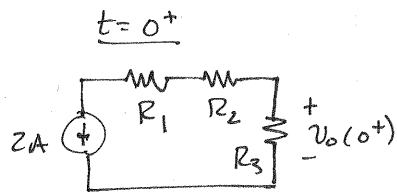
$$i_L(0^-) = \frac{12}{R_1} = 2\text{A}$$


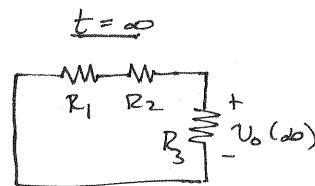
$$v_o(0^+) = -2R_3 = -4\text{V} = k_1 + k_2$$



$$v_o(\infty) = 0 = k_1$$

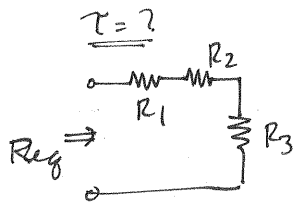

$$\tau = L / R_{eq} = \frac{1}{6}\text{ s}$$

$$v_o = -4e^{-6t}\text{ V}$$

$$R_{eq} = R_1 + R_2 + R_3 = 12\ \Omega$$

7.44 Find $i_o(t)$ for $t > 0$ in the network in Fig. P7.44 using the step-by-step method.


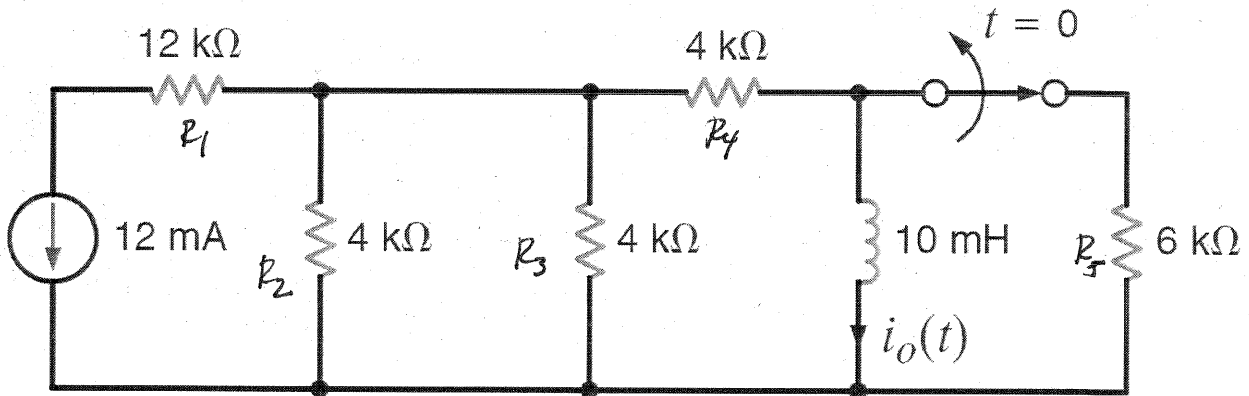



Figure P7.44

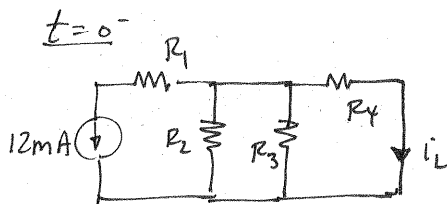SOLUTION: $i_o(t) = K_1 + K_2 e^{-t/\tau}$



$$R_2 = R_3 = R_4 = 4 \text{ k}\Omega$$
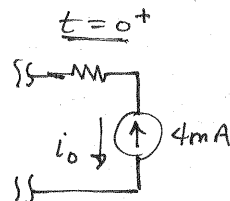
$$i_L(0^-) = \frac{-12 \times 10^{-3}}{3} = -4 \text{ mA}$$



$$i_o(0^+) = -4 \text{ mA} = K_1 + K_2$$

$t = \infty$ Same as $t = 0^-$!

$$i_o(\infty) = -4 \text{ mA} = K_1$$

$$\text{So, } K_2 = 0$$

$$i_o = -4 \text{ mA}$$

7.45 Use the step-by-step technique to find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.45.


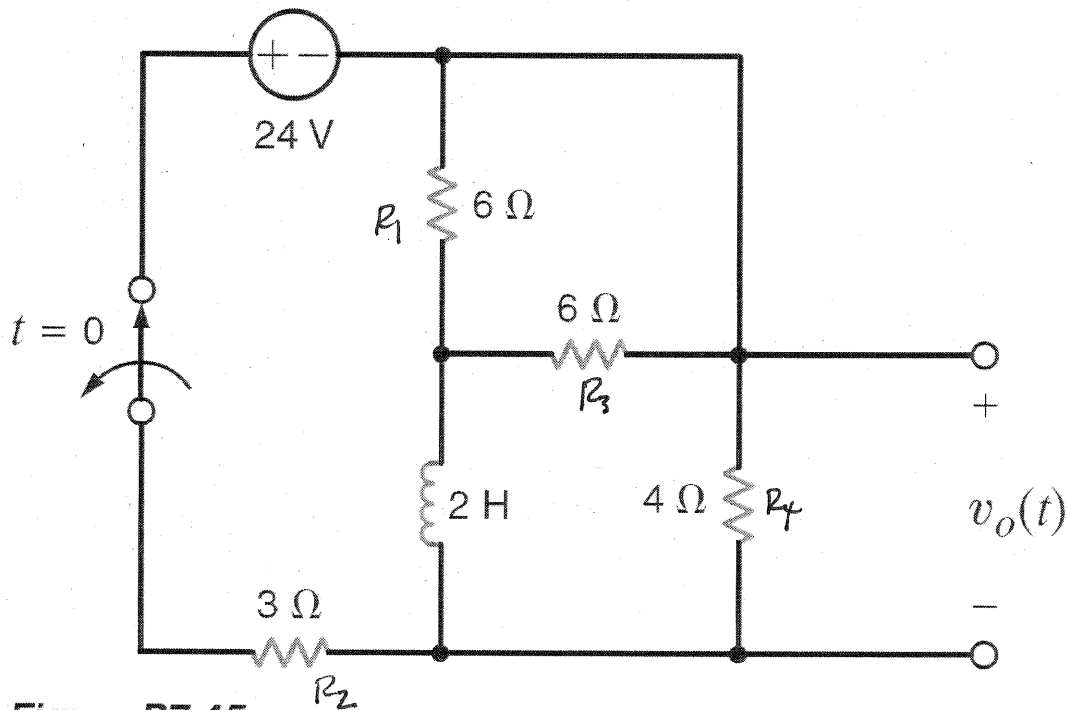



Figure P7.45

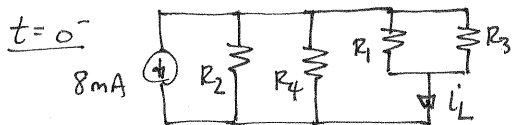SOLUTION: $v_o(t) = k_1 + k_2 e^{-t/\tau}$




$$R_x = R_2 \parallel R_4 = \frac{12}{7} \Omega \quad R_y = R_1 \parallel R_3 = 3 \Omega$$
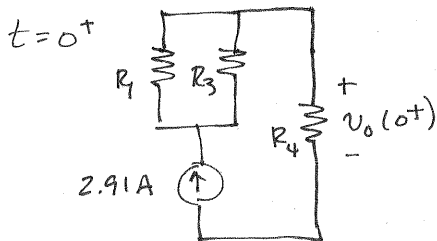
$$i_L = \frac{-8 \times 10^{-3} R_x}{R_x + R_y} = -2.91 \text{ A}$$



$t = \infty \quad v_o = 0 = k_1$

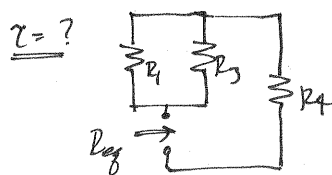

$$R_{eq} = R_4 + (R_1 \parallel R_3) = 7 \Omega$$

$$\tau = L / R_{eq} = \frac{2}{7} \text{ s}$$

$$v_o(0^+) = 2.91 R_4 = 11.64 \text{ V} = k_1 + k_2$$

$$v_o(t) = 11.64 e^{-3.5t} \text{ V}$$

7.46 Use the step-by-step method to find $v_o(t)$ for $t > 0$ in the network in Fig. P7.46.



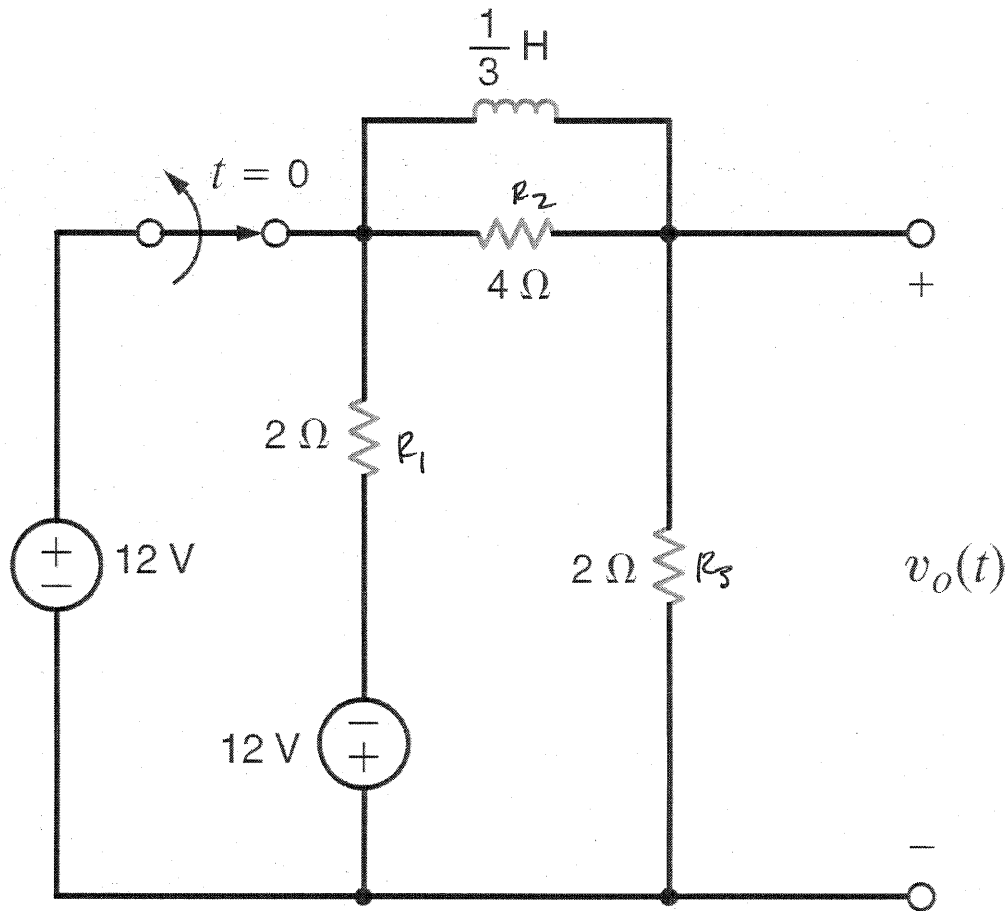
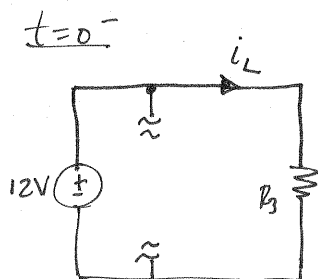


Figure P7.46

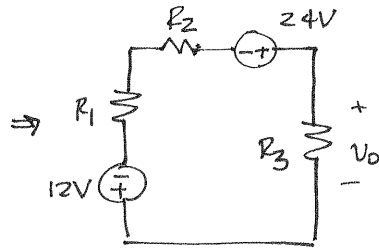SOLUTION: $v_o(t) = k_1 + k_2 e^{-t/\tau}$



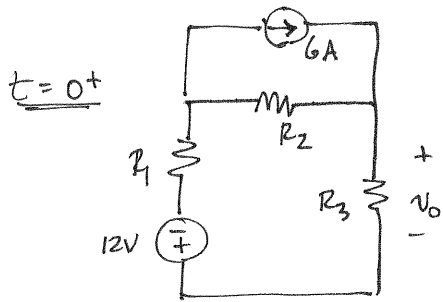
$$i_L(0^-) = \frac{12}{R_3} = 6 \text{ A}$$



$$V_0 = \frac{(24+12) R_3}{R_1 + R_2 + R_3}$$

$$V_0(0^+) = 3V = K_1 + K_2$$


$t = \infty$

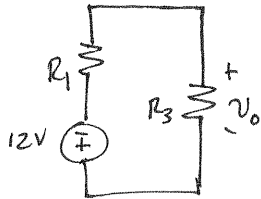

$$V_0(\infty) = \frac{-12 R_3}{R_1 + R_3}$$

$$V_0(\infty) = -6V = K_1$$

$\tau = ?$

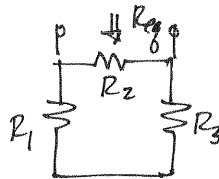

$$R_{eq} = R_2 \parallel (R_1 + R_3)$$

$$R_{eq} = 2\Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{1}{6} \text{ s}$$

$$V_0(t) = -6 + 9e^{-6t} \text{ V}$$

7.47 Find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.47 using the step-by-step method.


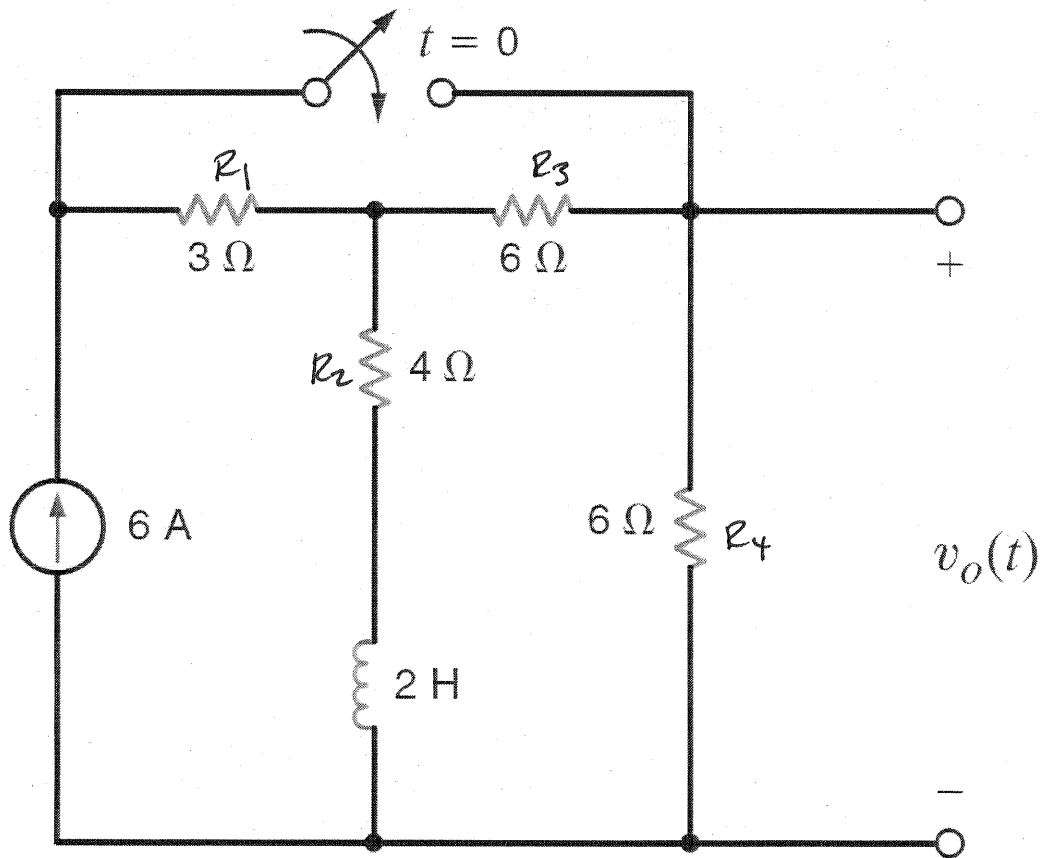


Figure P7.47


SOLUTION: $v_o(t) = K_1 + K_2 e^{-t/\tau}$

$t = 0^-$

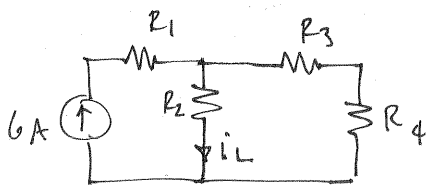


$$R_x = R_3 + R_4 = 12 \Omega$$
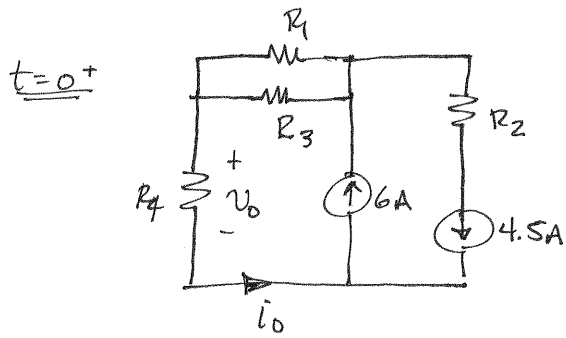
$$i_L = \frac{6 R_x}{R_x + R_2} = 4.5 \text{ A}$$



$$i_0 = 6 - 4.5 = 1.5 \text{ A}$$

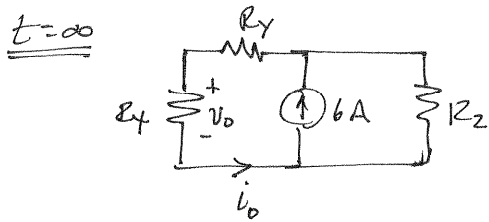
$$v_0 = i_0 R_4 = 9 \text{ V} = K_1 + K_2$$



$$R_Y = R_1 // R_3 = 2 \Omega$$

$$i_0 = \frac{6 R_2}{R_2 + R_Y + R_4} \quad i_0 = 2 \text{ A}$$
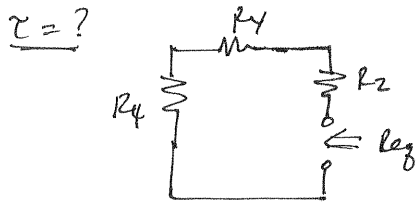
$$v_0(\infty) = i_0 R_4 = 12 \text{ V} = K_1$$



$$R_{eq} = R_2 + R_Y + R_4 = 12 \Omega$$

$$\tau = L / R_{eq} = 1/6 \text{ s}$$

$$v_0(t) = 12 - 3e^{-6t} \text{ V}$$

7.48 Find $v_o(t)$ for $t > 0$ in the network in Fig. P7.48 using the step-by-step technique.


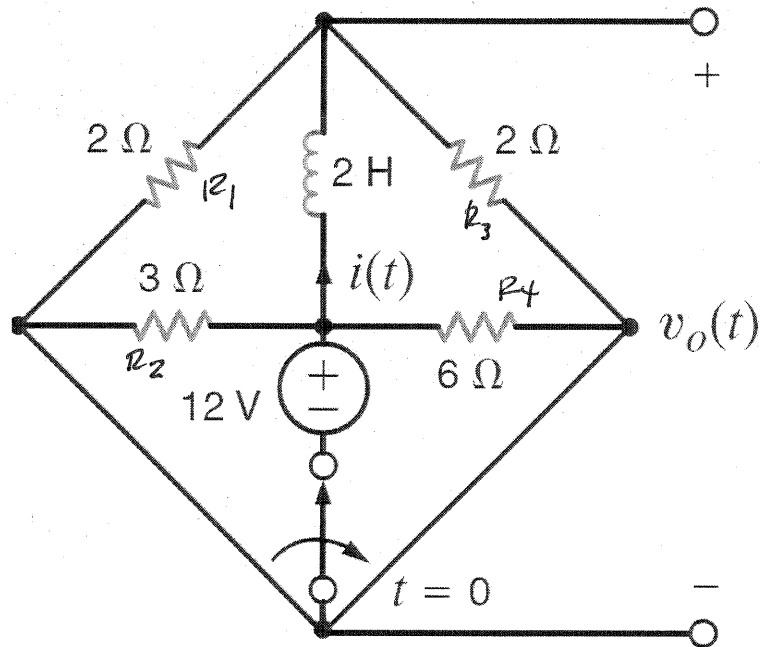
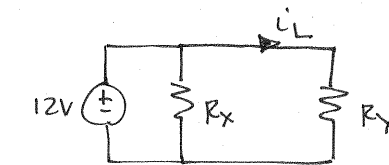


Figure P7.48

SOLUTION: $v_o(t) = k_1 + k_2 e^{-t/\tau}$


$t = 0^-$

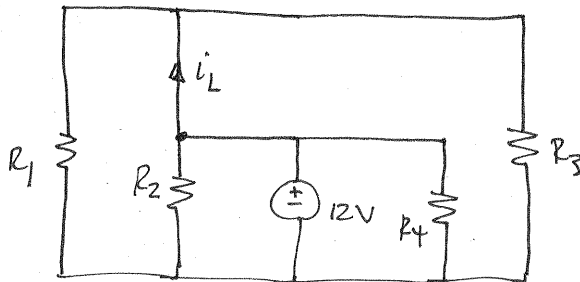


$$R_X = R_2 // R_4 = 2 \Omega$$

$$R_Y = R_1 // R_3 = 1 \Omega$$


$$i_L = \frac{12}{R_Y} = 12 \text{ A}$$

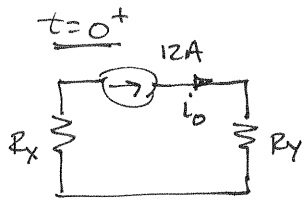

$$i_0 = 12A = k_1 + k_2$$

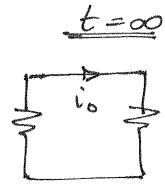

$$i_0 = 0 = k_1$$

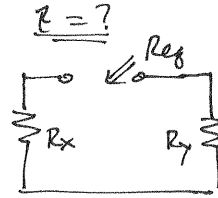

$$R_{eq} = R_x + R_y$$

$$R_{eq} = 3\Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{2}{3} s$$

$$i_0 = 12e^{-1.5t} A$$

7.49 Use the step-by-step method to find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.49.


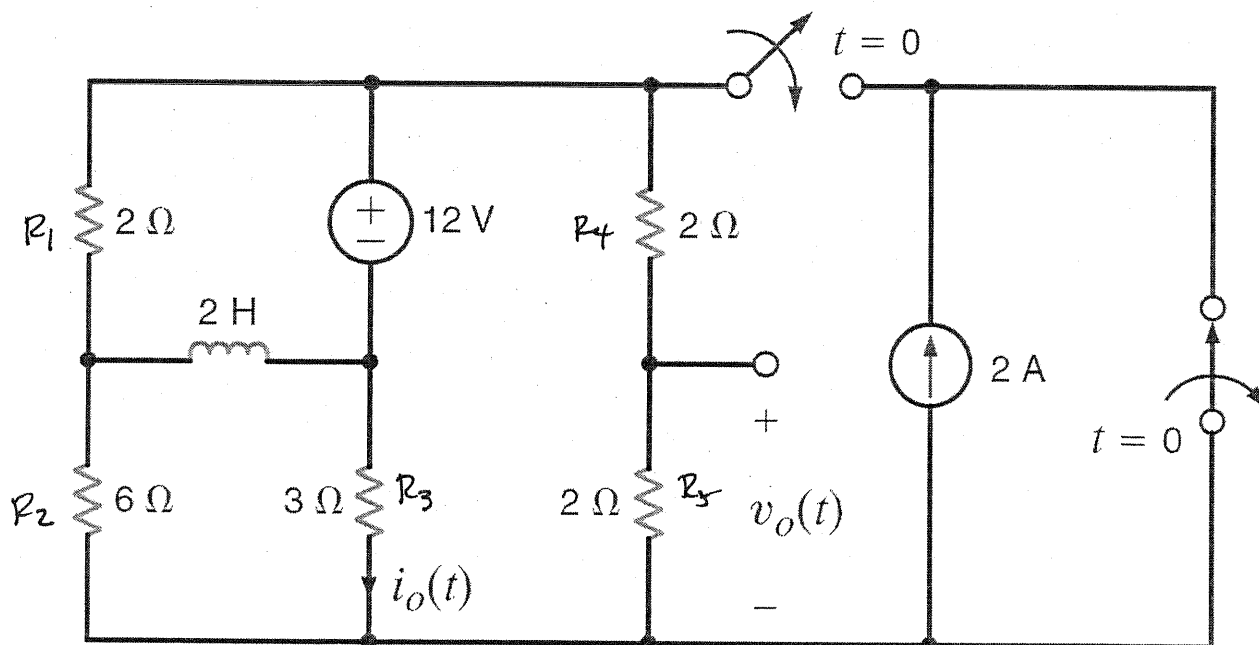


Figure P7.49

SOLUTION: $v_o(t) = k_1 + k_2 e^{-t/\tau}$

$t=0^-$

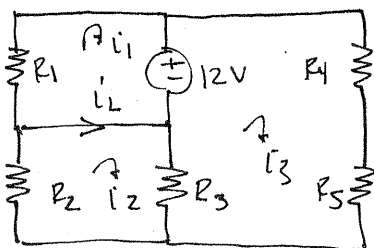

$$i_L(0^-) = i_2 - i_1 = \frac{20}{3} \text{ A}$$

mesh analysis:


$$i_1 R_1 + 12 = 0 \Rightarrow i_1 = -6 \text{ A}$$

$$i_2 (R_2 + R_3) - i_3 R_3 = 0 \Rightarrow i_3 = 3 i_2$$

$$12 = i_3 (R_3 + R_4 + R_5) - i_2 R_3 \Rightarrow 7 i_3 - 3 i_2 = 12$$

yields $i_3 = 2 \text{ A}$ & $i_2 = \frac{2}{3} \text{ A}$

$t=0^+$

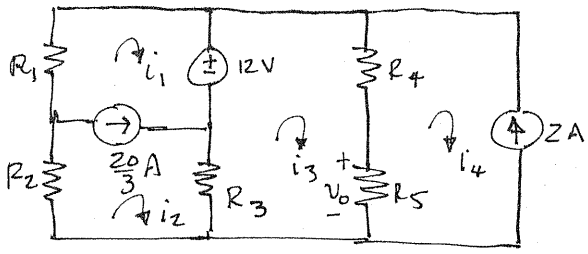

$$v_0 = R_5 (i_3 - i_4) = 5.41 \text{ V}$$

$$5.41 = K_1 + K_2$$

$$i_2 - i_1 = 20/3$$



$$i_4 = -2$$

$$12 = i_3 (R_3 + R_4 + R_5) - i_2 R_3 - i_4 (R_4 + R_5)$$

$$0 = i_1 R_1 + i_2 R_2 + i_3 (R_4 + R_5) - i_4 (R_4 + R_5)$$

$$i_3 = 0.706 \text{ A}$$

$t=\infty$

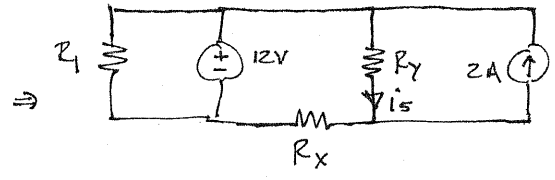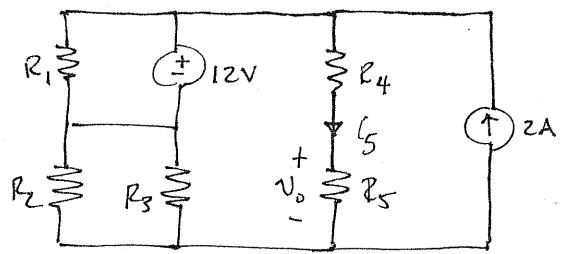


$$R_x = R_2 // R_3 = 2 \Omega \quad R_y = R_4 + R_5 = 4 \Omega$$

$$v_0(\infty) = i_5 R_5 = 2 i_5$$

Find i_5 by superposition:
$$i_5 = \frac{12}{R_x + R_y} + \frac{2 R_x}{R_x + R_y} = \frac{8}{3} \text{ A}$$

$$v_0 = \frac{16}{3} = 5.33 \text{ V} = K_1$$

$\tau = ?$

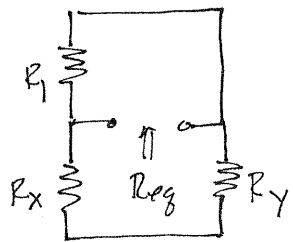

$$R_{eq} = R_1 // (R_x + R_y) = 1.5 \Omega$$

$$\tau = L / R_{eq} = \frac{4}{3} \text{ s}$$

$$v_0 = 5.33 + 0.08 e^{-0.75 t} \text{ V}$$

7.50 Find $i(t)$ for $t > 0$ in the circuit of Fig. P7.50 using the step-by-step method.


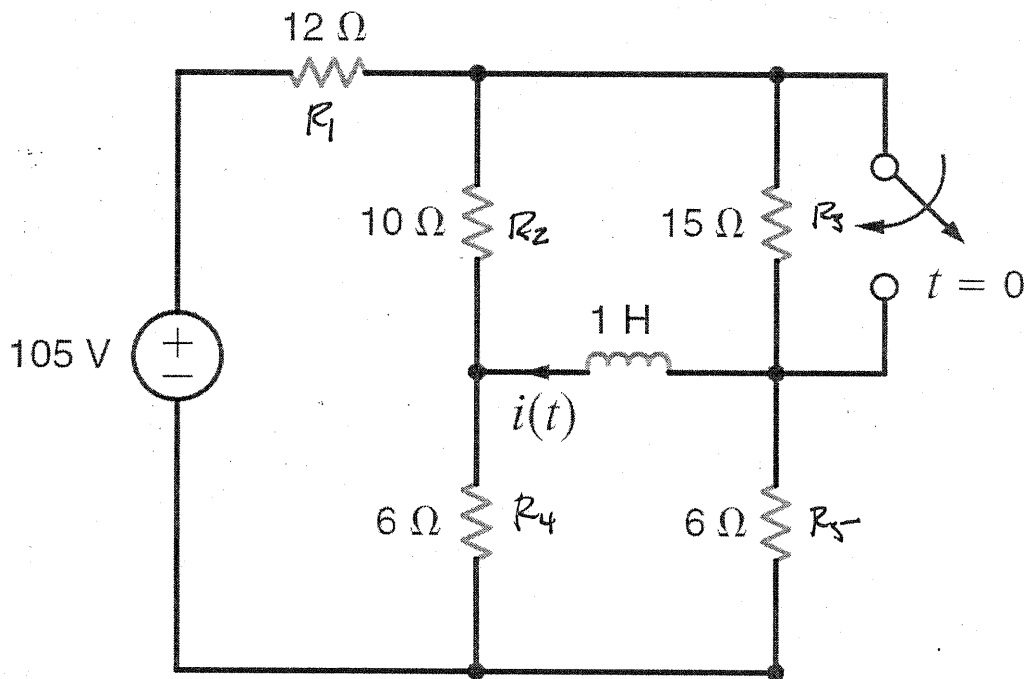


Figure P7.50

SOLUTION: $i(t) = k_1 + k_2 e^{-t/\tau}$


$t = 0^-$

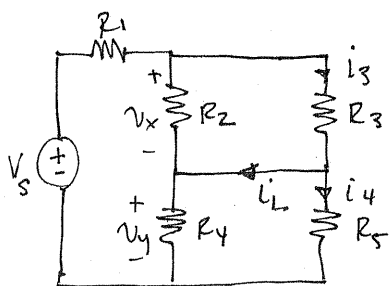

$$i_3 = \frac{V_x}{R_3} = 2 \text{ A}$$

$$i_4 = \frac{V_y}{R_5} = 2.5 \text{ A}$$

$$i_L = i_3 - i_4 = -0.5 \text{ A}$$

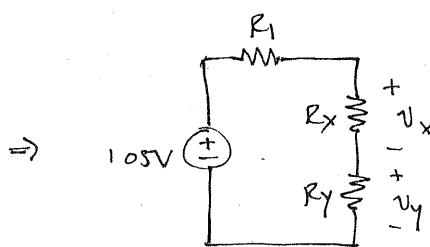


$$R_x = R_2 \parallel R_3 = 6 \Omega$$

$$R_y = R_4 \parallel R_5 = 3 \Omega$$

$$V_x = \frac{105 R_x}{R_x + R_y + R_1} = 30 \text{ V}$$


$$V_y = \frac{105 R_y}{R_1 + R_x + R_y} = 15 \text{ V}$$

$t = 0^+$

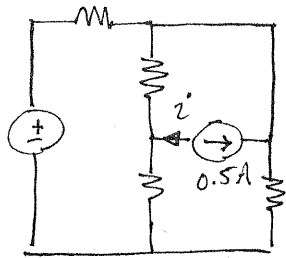

$$i = -0.5A = K_1 + K_2$$

$t = \infty$


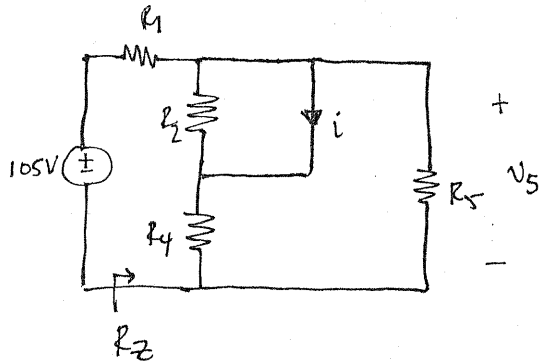


$$R_2 = R_4 // R_5 = 3\Omega$$

$$V_5 = \frac{105 R_2}{R_2 + R_1} = 21V$$

$$i(\infty) = \frac{V_5}{R_4} = 3.5A = K_1$$

$\tau = ?$

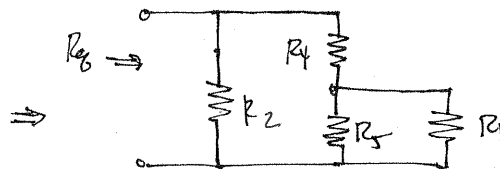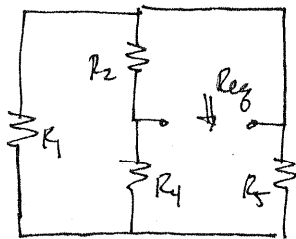

$$R_{eq} = R_2 // \{ R_4 + (R_1 // R_5) \} = 5\Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{1}{5} s$$

$$i(t) = 3.5 - 4e^{-5t} \text{ A}$$

7.51 Find $v_C(t)$ for $t > 0$ in the circuit of Fig. P7.51 using the step-by-step method.

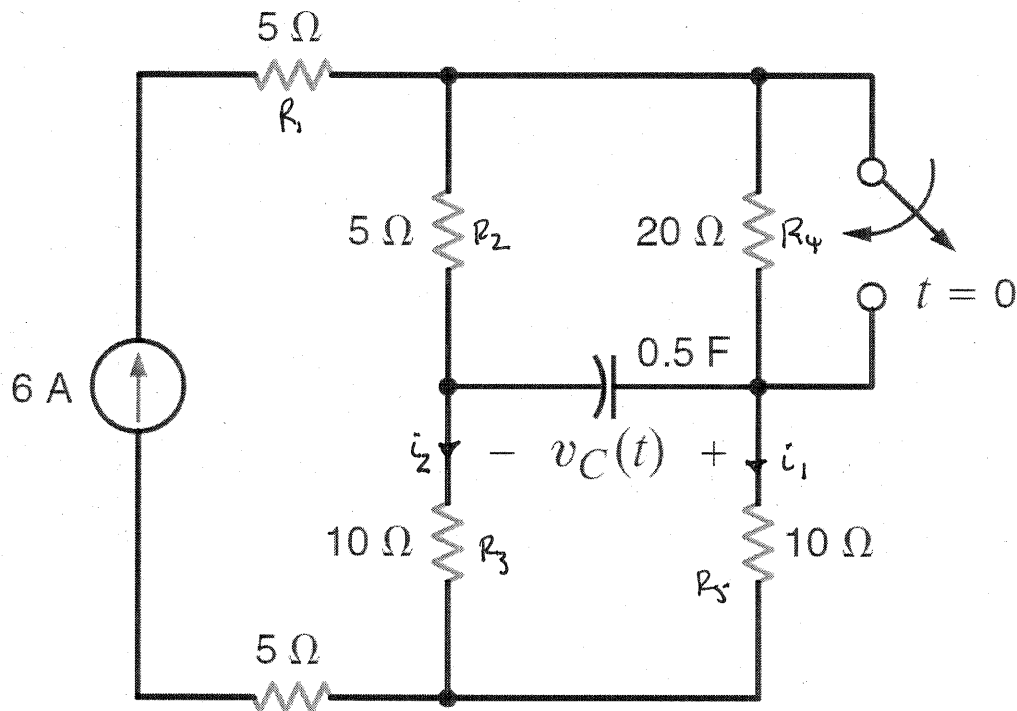


Figure P7.51

SOLUTION: $v_C(t) = K_1 + K_2 e^{-t/\tau}$


$t=0^-$: $R_A = R_4 + R_5 = 30\Omega$ $R_B = R_2 + R_3 = 15\Omega$

$i_1 = \frac{6 R_B}{R_B + R_A} = 2\text{A}$ $i_2 = \frac{6 R_A}{R_A + R_B} = 4\text{A}$ $v_C(0^-) = i_1 R_5 - i_2 R_3$
 $v_C(0^-) = -20\text{V}$

$t=0^+$: $v_C(0^+) = v_C(0^-) = -20 = K_1 + K_2$

$t \rightarrow \infty$: $i_3 = \frac{6 R_5}{R_2 + R_3 + R_5} = 2.4\text{A}$ $v_C(\infty) = R_2 i_3 = 12\text{V} = K_1$

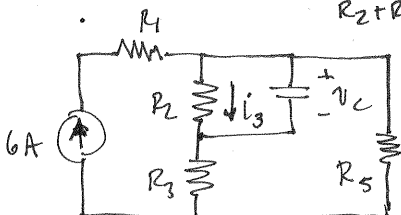$\tau = C [R_2 \parallel (R_3 + R_5)] = 2\text{s}$



$$v_C(t) = 12 - 32 e^{-t/2} \text{ V}$$

7.52 Find $i(t)$ for $t > 0$ in the circuit of Fig. P7.52 using the step-by-step method.


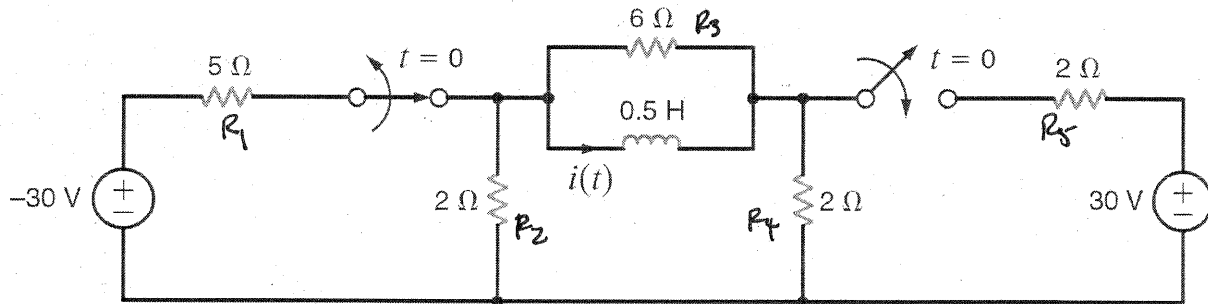


Figure P7.52

SOLUTION:

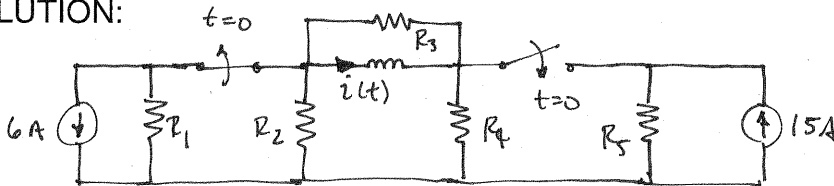


$$t=0^-: i(0^-) = \frac{-6 (1/R_4)}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4}} = -2.5 \text{ A}$$

$$t=0^+: i(0^+) = i(0^-) = -2.5 \text{ A} = K_1 + K_2$$

$$K_2 = 2.5 \text{ A}$$
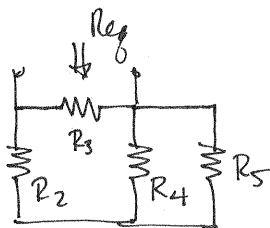
$$t \rightarrow \infty: i(\infty) = \frac{-15 (1/R_2)}{\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_5}} = -5 \text{ A} = K_1$$



$$\tau = \frac{L}{R_{eq}}$$

$$\tau = \frac{1}{4} \text{ s}$$

$$R_{eq} = R_3 \parallel [R_2 + R_A]$$

$$R_{eq} = 2 \Omega$$

$$R_A = R_4 \parallel R_5$$

$$R_A = 1 \Omega$$

$$i(t) = -5 + 2.5e^{-4t} \text{ A}$$

7.53 Find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.53 using the step-by-step method.


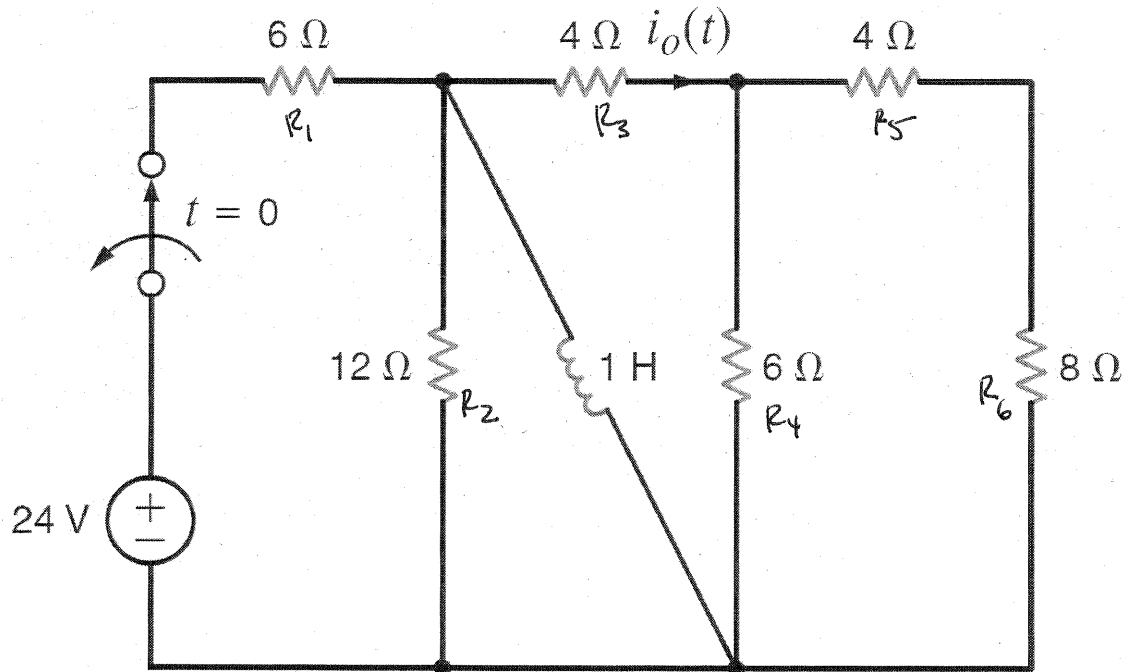


Figure P7.53

SOLUTION:

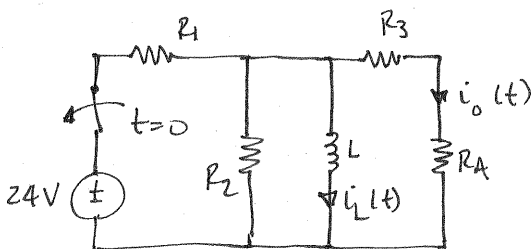

$$R_A = R_4 \parallel (R_5 + R_6) = 4 \Omega$$

$$t = 0^- : i_L(0^-) = \frac{24}{R_1} = 4 \text{ A}$$

$$t = 0^+ : i_o = -\frac{i_L(0^-) R_2}{R_2 + R_3 + R_A} = -2.4 \text{ A} = K_1 + K_2$$

$$t \rightarrow \infty : i_o = 0 = K_1$$

$$\tau = L / R_{eq} \quad R_{eq} = R_2 \parallel (R_3 + R_A) = 4.8 \Omega \quad \tau = 0.208 \text{ s}$$

$$i_o(t) = -2.4 e^{-4.8t} \text{ A}$$

7.54 Find $v_o(t)$ for $t > 0$ in the network in Fig. P7.54 using the step-by-step method.


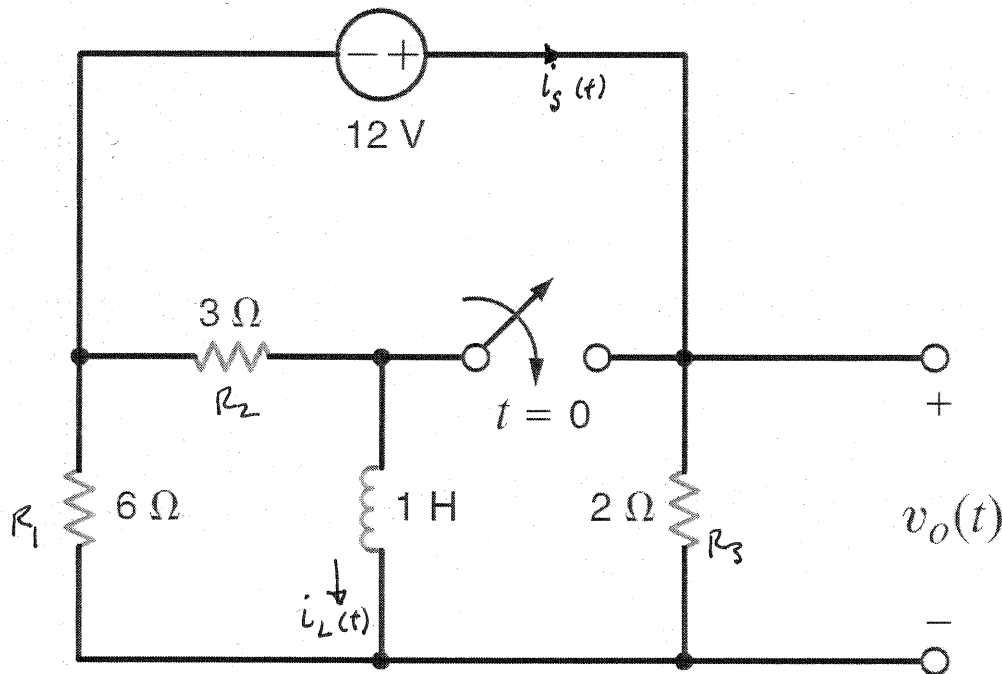


Figure P7.54

SOLUTION:

$$t=0^-: \quad i_s = \frac{12}{R_3 + (R_1 \parallel R_2)} = 3 \text{ A} \quad i_L = -\frac{i_s R_1}{R_1 + R_2} = -2 \text{ A}$$
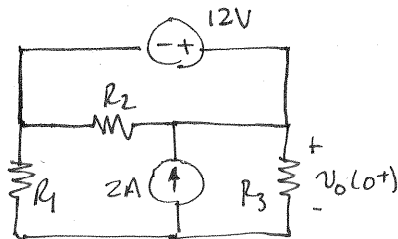
$$t=0^+: \quad \text{By superposition: } v_o(0^+) = \frac{12R_3}{R_1 + R_3} + \frac{2R_1R_3}{R_1 + R_3} = 6 \text{ V} = k_1 + k_2$$



$$t \rightarrow \infty: \quad v_o(\infty) = 0 = k_1$$

$$R_{eq} = R_1 \parallel R_3 = 1.5 \Omega \quad \tau = \frac{L}{R} = \frac{2}{3} \text{ s}$$

$$v_o(t) = 6e^{-1.5t} \text{ V}$$

7.55 Find $i_o(t)$ for $t > 0$ in the network in Fig. P7.55 using the step-by-step method. **PSV**



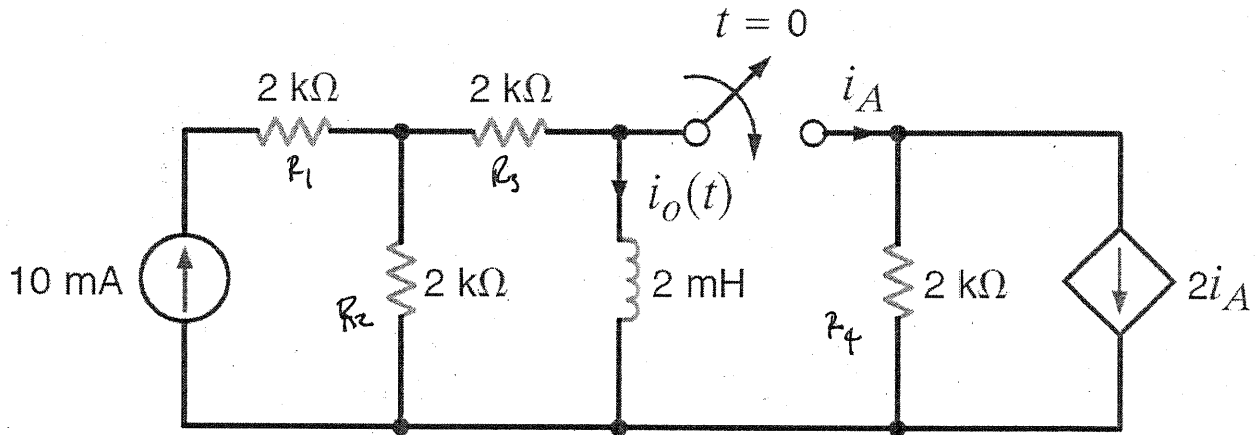
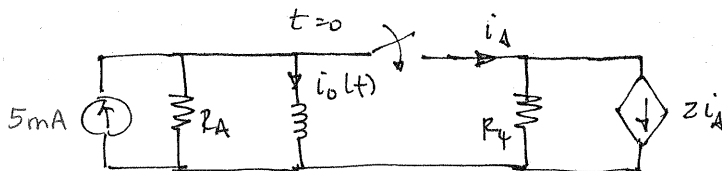


Figure P7.55


SOLUTION:

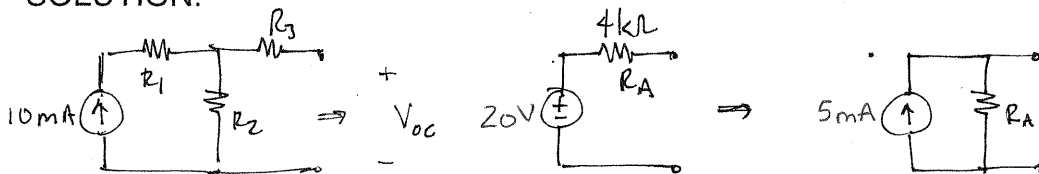

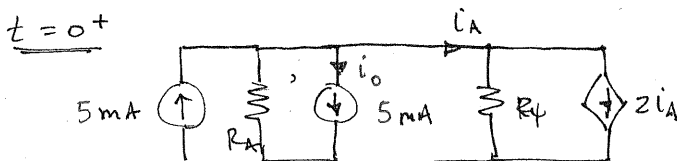$t = 0^- \quad i_A = 0$
 $i_o = 5 \times 10^{-3} = 5 \text{ mA}$



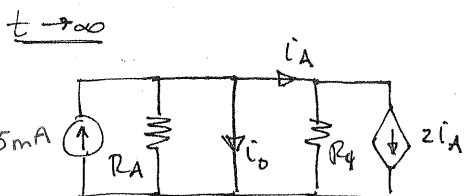$i_o(0^+) = i_o(0^-) = 5 \text{ mA} = K_1 + K_2$



$i_A = 0 \quad i_o = 0.5 \text{ mA} = K_1 \Rightarrow K_2 = 0$

$i_o(t) = 5 \text{ mA}$

7.56 Find $i_L(t)$ for $t > 0$ in the circuit of Fig. P7.56 using the step-by-step method.

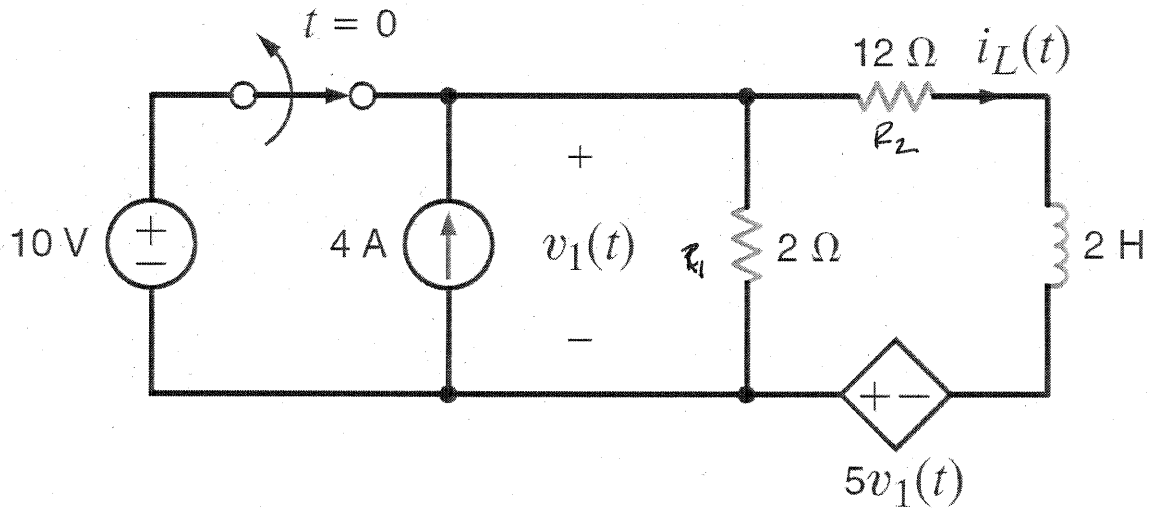



Figure P7.56

SOLUTION:

$$t=0^-: v_1 = 10V \quad v_1 = R_2 i_L - 5v_1 \Rightarrow i_L = \frac{6v_1}{R_2} = 5A$$


$$t=0^+ \quad i_L(0^+) = i_L(0^-) = 5A = k_1 + k_2$$

$t \rightarrow \infty$:

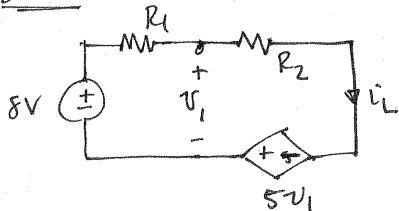

$$i_L = 6v_1/R_2 \Rightarrow v_1 = R_2 i_L / 6$$
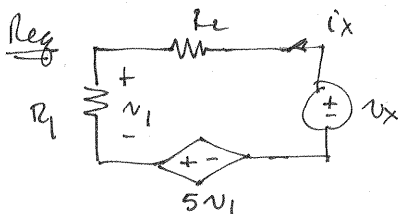
$$8 = i_L (R_1 + R_2) - 5v_1 \Rightarrow i_L(\infty) = 2A = k_1$$



$$R_{eq} = v_x / i_x \quad v_1 = i_x R_1$$

$$v_x = i_x (R_1 + R_2) + 5v_1 = i_x (6R_1 + R_2)$$

$$R_{eq} = 24\Omega \quad \tau = L/R_{eq} = \frac{1}{2} s$$

$$i_L(t) = 2 + 3e^{-12t} A$$

7.57 Use the step-by-step technique to find $v_o(t)$ for $t > 0$ in the network in Fig. P7.57.

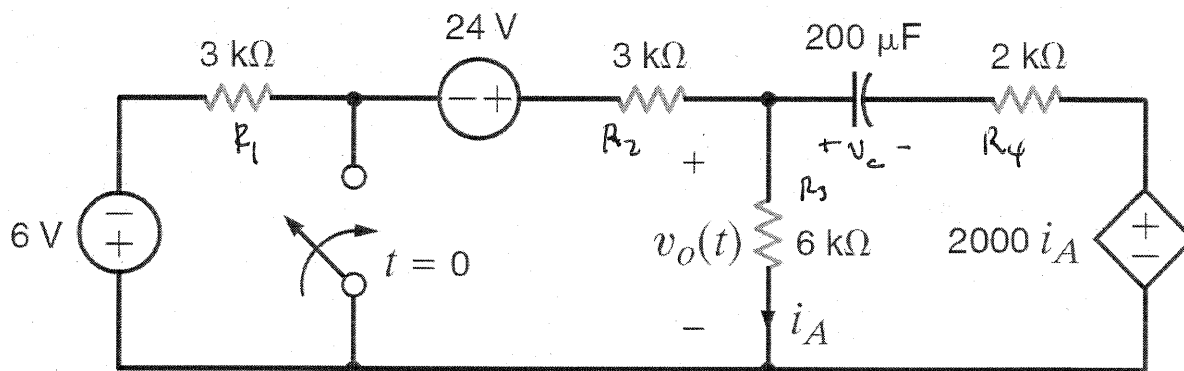



Figure P7.57

SOLUTION:

$$t = 0^-: \quad 6 - 24 + i_A R_1 + i_A R_2 + i_A R_3 = 0 \quad i_A = 1.5 \text{ mA}$$

$$v_C(0^-) = v_o(0^-) - 2000 i_A(0^-) \quad v_o(0^-) = R_3 i_A(0^-) = 9 \text{ V}$$

$$v_C(0^-) = 6 \text{ V}$$

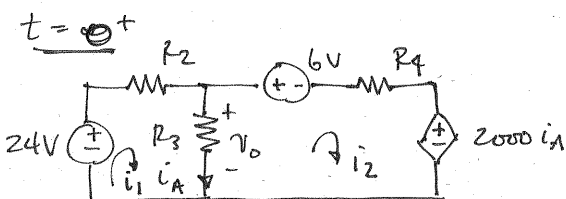

$$24 = i_1(R_2 + R_3) - R_3 i_2$$


$$-6 = i_2(R_3 + R_4) - R_3 i_1 + 2000 i_A$$

$$i_A = i_1 - i_2$$

$$v_o(0^+) = i_A R_3 = 13.2 \text{ V} = K_1 + K_2$$

$$v_o = i_A R_3 = 16 \text{ V} = K_1$$
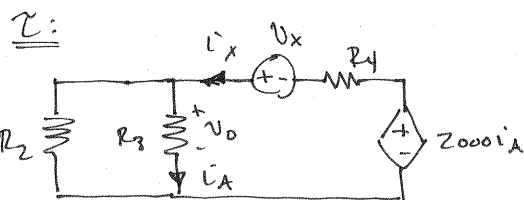
$$t = \infty: \quad i_A = \frac{24}{R_2 + R_3} = 2.67 \text{ A}$$



$$R_{eq} = v_x / i_x$$

$$v_x + 2000 i_A = i_x (R_4 + R_3); \quad R_4 = R_2 // R_3 = 2 \text{ k}\Omega$$

$$i_A = \frac{i_x R_2}{R_2 + R_3} = i_x / 3 \Rightarrow R_{eq} = 3.33 \text{ k}\Omega$$

$$\tau = C R_{eq} = 0.667 \text{ s}$$

$$v_o(t) = 16 - 2.8 e^{-1.5t} \text{ V}$$

7.58 Use the step-by-step method to find $v_o(t)$ for $t > 0$ in the network in Fig. P7.58. CS


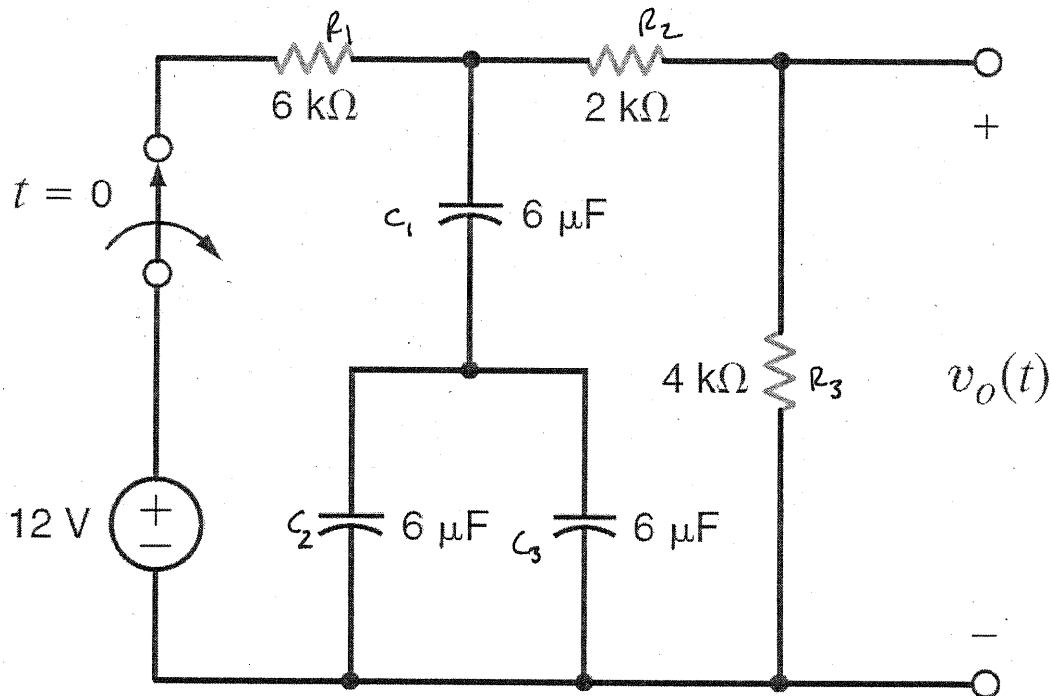


Figure P7.58

SOLUTION:

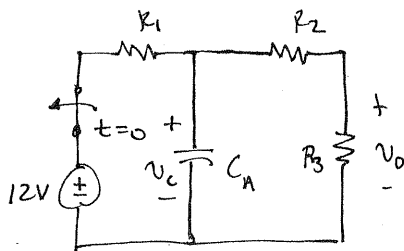

$$C_A = \frac{C_1(C_2 + C_3)}{C_1 + C_2 + C_3} = 4 \mu\text{F}$$

$$t = 0^- : v_c = \frac{12(R_2 + R_3)}{R_1 + R_2 + R_3} = 6 \text{ V}$$

$$t = 0^+ : v_c = 6 \text{ V} \quad v_o = \frac{v_c R_3}{R_2 + R_3} = 4 \text{ V} = K_1 + K_2$$

$$t = \infty : v_o = 0 = K_1$$

$$\underline{\tau} : R_{eq} = R_2 + R_3 = 6 \text{ k}\Omega \quad \tau = C_A R_{eq} = 24 \text{ ms}$$

$$v_o(t) = 4 e^{-41.67t} \text{ V}$$

7.59 Find $i_o(t)$ for $t > 0$ in the circuit in Fig. P7.59 using the step-by-step method. **CS**


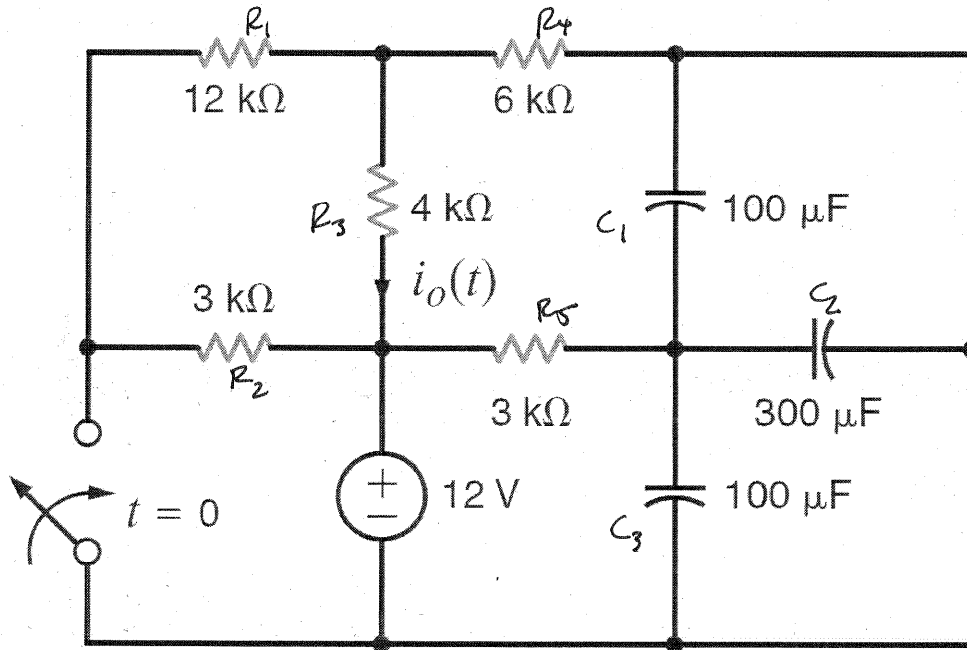


Figure P7.59


SOLUTION:

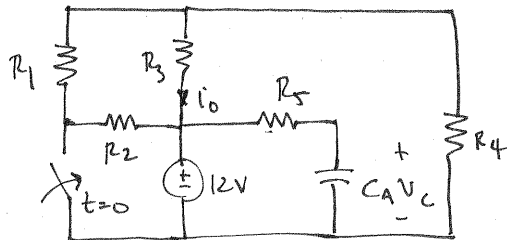


$$C_A = C_1 + C_2 + C_3 = 500 \mu\text{F}$$

$$t = 0^- : v_C = 12\text{V}$$

$$t = 0^+ : v_C = 12\text{V}$$

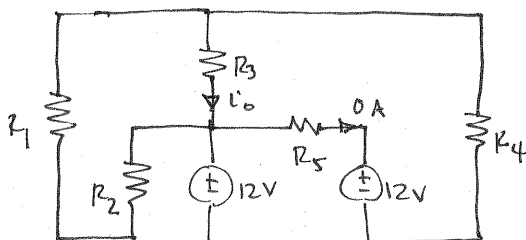

⇒

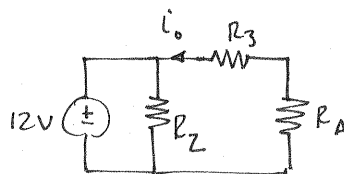

$$R_A = R_1 / R_4 = 4\text{k}\Omega$$

$$i_o = \frac{-12}{R_3 + R_A} = -1.5\text{mA} = K_1 + K_2$$

$t = \infty$ Same situation as $t = 0^+$, $i_o = -1.5 \text{ mA} = K_1 \Rightarrow K_2 = 0$

$$i_o(t) = -1.5 \text{ mA}$$

7.60 Find $v_o(t)$ for $t > 0$ in the network in Fig. P7.60 using the step-by-step method.


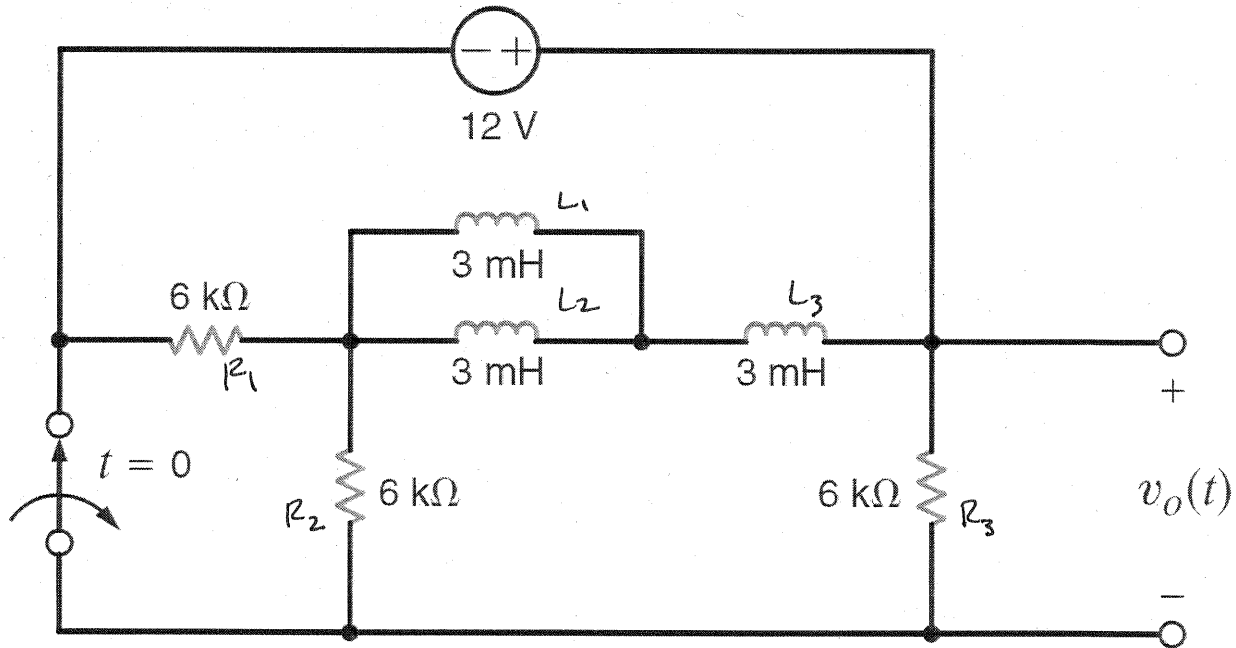



Figure P7.60

SOLUTION:

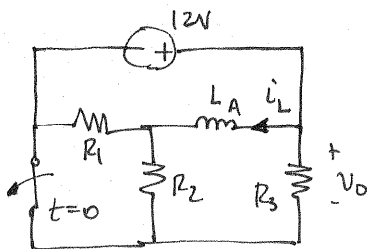

$$L_A = L_3 + \frac{L_1 L_2}{L_1 + L_2} = 4.5 \text{ mH}$$

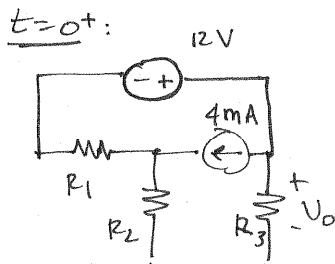
$$t=0^- \quad i_L = \frac{12}{R_1} + \frac{12}{R_2} = 4 \text{ mA}$$



$$\text{Superposition: } v_o = \frac{12 R_3}{R_1 + R_2 + R_3} - \frac{4 \times 10^{-3} R_1 R_3}{R_1 + R_2 + R_3}$$


$$v_o(0^+) = -4 \text{ V} = k_1 + k_2$$

$t = \infty$:

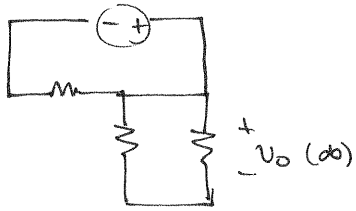

$$v_o(\infty) = 0 \text{ V} = k_1$$

$\tau = ?$

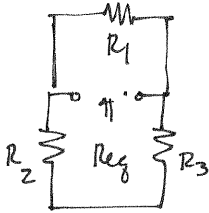

$$R_{eq} = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3} = 4 \text{ k}\Omega$$

$$\tau = \frac{L}{R_{eq}} = 1.125 \mu\text{s}$$

$$v_o(t) = -4 e^{-8.88 \times 10^5 t} \text{ V}$$

7.61 Use the step-by-step method to find $i_o(t)$ for $t > 0$ in the network in Fig. P7.61.


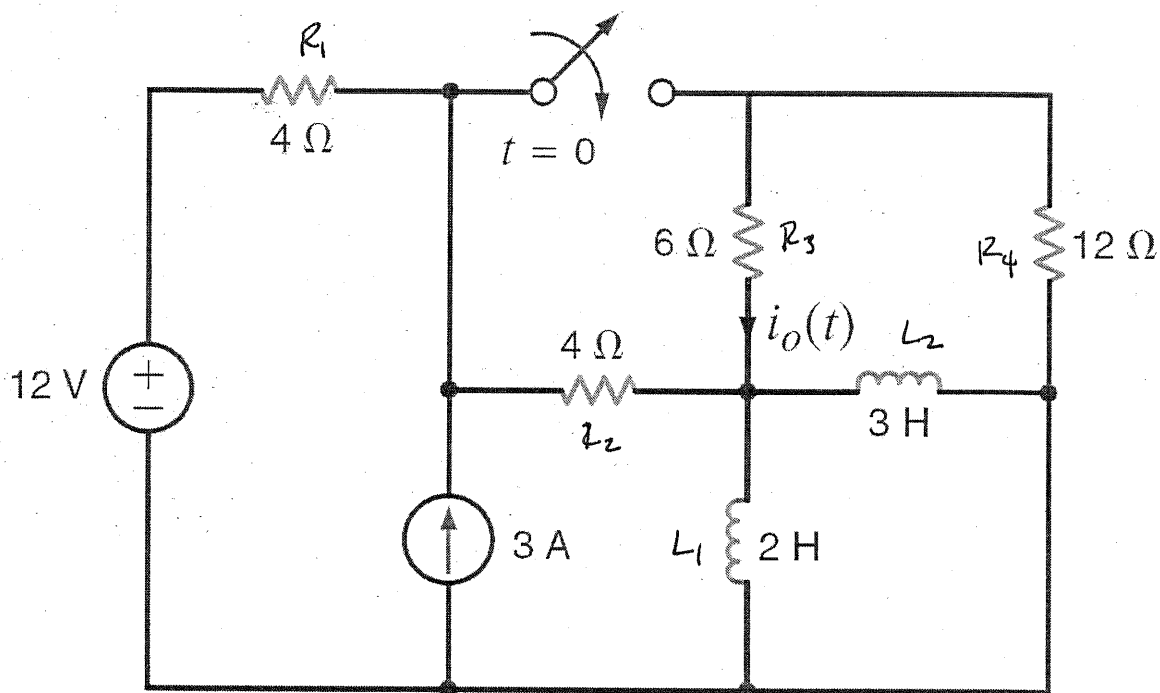


Figure P7.61

SOLUTION: Source transformation

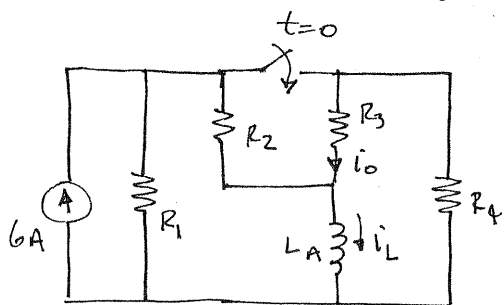


$$t=0^- \quad i_L = 6 \left(\frac{1/R_2}{\frac{1}{R_1} + \frac{1}{R_2}} \right)$$

$$R_A = R_2 // R_3 = 2.4 \Omega$$

$$i_L = 3 \text{ A}$$

$$L_A = \frac{L_1 L_2}{L_1 + L_2} = 1.2 \text{ H}$$


$t=0^+$:

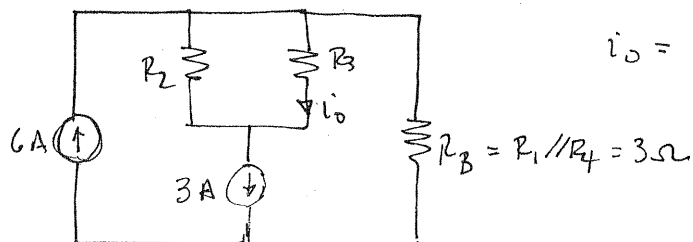

Superposition:


$$i_o = \frac{3 R_2}{R_2 + R_3} = 1.2 \text{ A} = k_1 + k_2$$

$t = \infty$

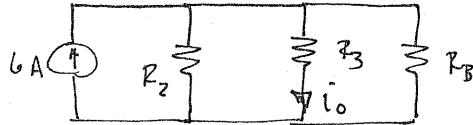

$$i_0 = 6 \left(\frac{1}{R_3} \right) = \frac{4}{3} \text{ A} = K_1$$
$$\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_B}$$

τ

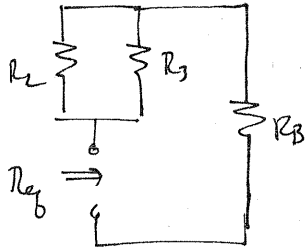


$$R_{eq} = (R_2 // R_3) + R_B = 5.4 \Omega$$


$$\tau = \frac{L A}{R_{eq}} = 222 \text{ ms}$$

$$i_0(t) = 1.33 - 0.133 e^{-4.5t} \text{ A}$$

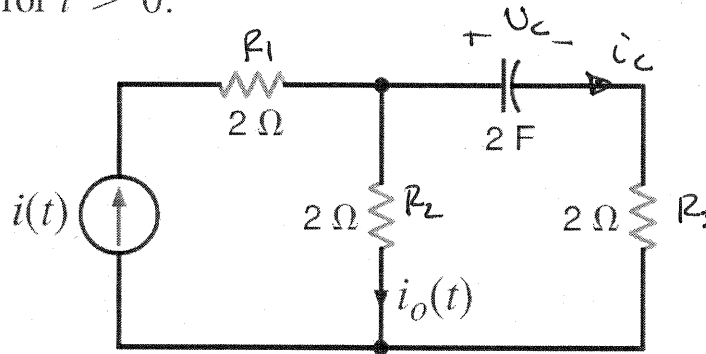7.62 The current source in the network in Fig. P7.62a is defined in Fig. P7.62b. The initial voltage across the capacitor must be zero. (Why?) Determine the current $i_o(t)$ for $t > 0$.



(a)

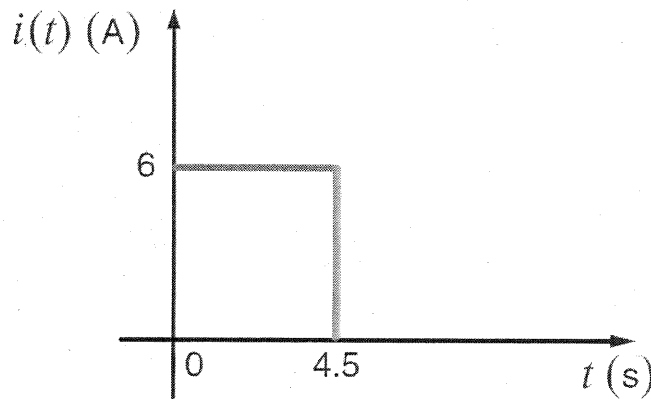

(b)

Figure P7.62

SOLUTION:

Since $i(t)$ is 0 for $t < 0$, no charge has accumulated on the capacitor and v_c must be 0.

$$t = 0^- : v_c = 0$$

$$t = 0^+ \quad v_c = 0, \quad i_o = \frac{i R_3}{R_2 + R_3} = 3 \text{ A} = k_1 + k_2$$

$$v_c(t) = k_3 + k_4 e^{-t/\tau}$$

$$i_o(t) = k_1 + k_2 e^{-t/\tau}$$

$$t = -\infty \quad i_c = 0 \text{ A} \quad i_0 = 6 = k_1 \quad v_c = 6 R_2 = 12 \text{ V} = k_3$$

$$k_2 = -3 \text{ A} \quad k_4 = -12 \text{ V}$$

$$\tau = C R_{eq} = C (R_2 + R_3) = 8 \text{ s}$$

$$i_0(t) = 6 - 3e^{-t/8} \text{ A}$$

$$v_c(t) = 12 - 12e^{-t/8} \text{ V}$$

$$0 \leq t \leq 4.5 \text{ s}$$


$$t = 4.5 \text{ s} \quad v_c(4.5) = 5.16 \text{ V}$$

$$i_0 = k_5 + k_6 e^{-t'/8}$$

$$t > 4.5 \text{ s}$$

$$t' = t - 4.5$$

$$t = 4.5 \text{ s}^+$$

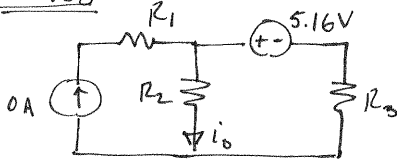

$$i_0 = \frac{5.16}{R_2 + R_3} = 1.29 = k_5 + k_6$$

$$t \rightarrow \infty \quad i_0 = 0 = k_5 \Rightarrow k_6 = 1.29 \text{ A}$$


$$\tau_2 = C R_{eq2} = C [R_2 + R_3] = 8 \text{ s}$$

$$i_0(t) = 1.29 e^{-(t-4.5)/8} \text{ A} \quad t > 4.5 \text{ s}$$


Final answer

$$i_0(t) = \begin{cases} 6 - 3e^{-t/8} \text{ A} & 0 \leq t \leq 4.5 \text{ s} \\ 1.29 e^{-(t-4.5)/8} \text{ A} & t > 4.5 \text{ s} \end{cases}$$

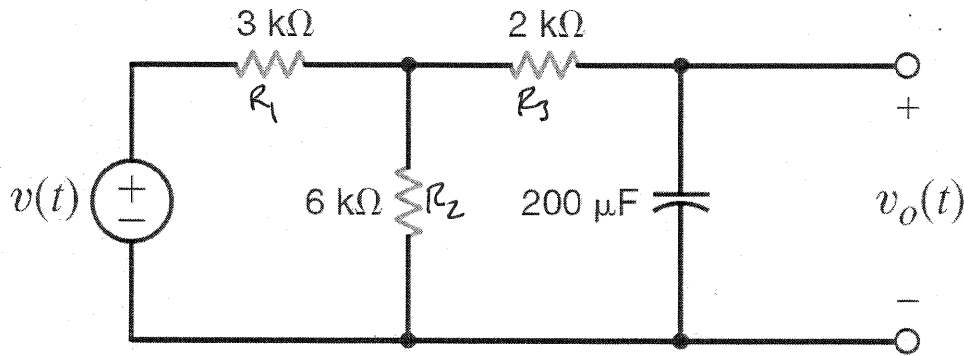7.63 Determine the equation for the voltage $v_o(t)$ for $t > 0$, in Fig. P7.63a when subjected to the input pulse shown in Fig. P7.63b.



(a)

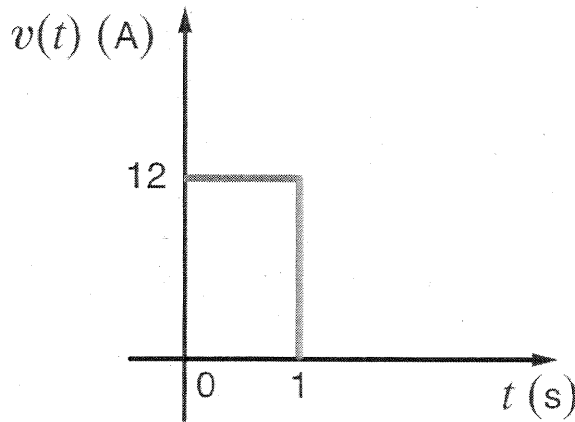


(b)

Figure P7.63


SOLUTION: $v_o = K_1 + K_2 e^{-t/\tau}$

$t = 0^- \quad v_o = 0$

$t = 0^+$

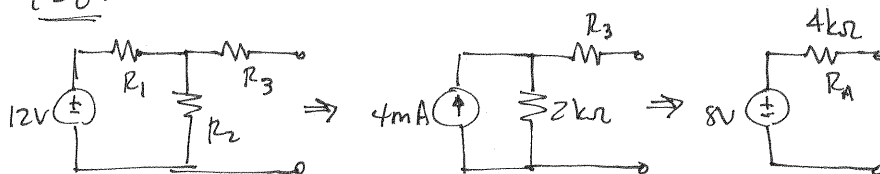

$$\underline{t=0^+}$$

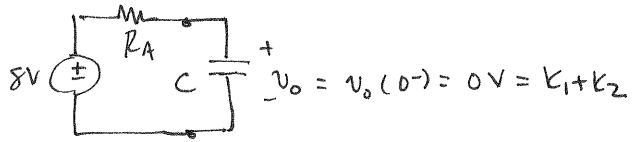

$$\underline{t=\infty}: v_o = 8V = K_1$$

$$\underline{\tau} \quad \tau = CR_A = 0.8s$$

$$v_o(t) = 8 - 8e^{-1.25t} \quad v \quad 0 < t \leq 1$$

$$\text{for } t > 1s, \quad v_o = K_3 + K_4 e^{-t'/\tau} \quad t' = t - 1$$

$$\underline{\text{at } t=1^-}, \quad v_o = 5.71V$$

$$\underline{\text{at } t=1^+}, \quad v_o = 5.71V = K_3 + K_4$$

$$\underline{\text{at } t=\infty} \quad v_o = 0 = K_3 \Rightarrow K_4 = 5.71V$$

$$v_o = \begin{cases} 8 - 8e^{-1.25t} \quad v & 0 \leq t \leq 1 \\ 5.71 e^{-1.25(t-1)} \quad v & t > 1 \end{cases}$$

7.64 Find the output voltage $v_o(t)$ in the network in Fig. P7.64 if the input voltage is $v_i(t) = 5(u(t) - u(t - 0.05))$ V.


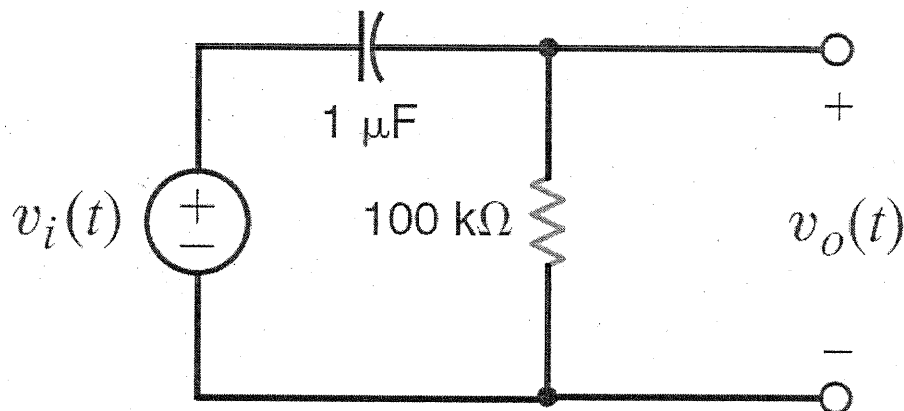


Figure P7.64

SOLUTION:

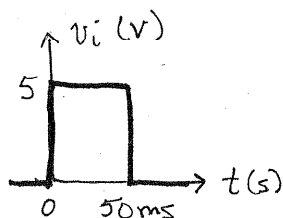

$$\text{For } 0 \leq t \leq 50 \text{ ms} \quad v_o = k_1 + k_2 e^{-t/\tau}$$

$$\text{For } t > 50 \text{ ms} \quad v_o = k_3 + k_4 e^{-t/\tau}$$

$$\underline{t=0^-} \quad v_o = 0 \quad \& \quad v_c = 0 \text{ V}$$

$$\underline{t=0^+} \quad v_c = 0 \quad \& \quad v_o = v_i = 5 = k_1 + k_2$$

$$\underline{t \rightarrow \infty} \quad v_o = 0 = k_1 \Rightarrow k_2 = 5 \text{ V}$$

$$\tau = CR = 0.15 \Rightarrow v_o(t) = 5e^{-10t} \quad 0 \leq t \leq 50 \text{ ms}$$

$$\underline{\text{at } t = 50 \text{ ms}^-} \quad v_o = 3.03 \text{ V} \quad \& \quad v_c = 1.97 \text{ V}$$

$$\underline{t = 50 \text{ ms}^+} \quad v_c = 1.97 \text{ V} \quad \& \quad v_o = v_i - v_c = -1.97 \text{ V} = k_3 + k_4$$

$$\underline{t \rightarrow \infty} \quad v_o = 0 = k_4 \Rightarrow v_o(t) = -1.97 e^{-10(t-0.05)} \text{ V} \quad t > 50 \text{ ms}$$

$$v_o = \begin{cases} 5e^{-10t} \text{ V} & 0 \leq t \leq 50 \text{ ms} \\ -1.97e^{-10(t-0.05)} \text{ V} & t > 50 \text{ ms} \end{cases}$$

7.65 The voltage $v(t)$ shown in Fig. P7.65a is given by the graph shown in Fig. P7.65b. If $i_L(0) = 0$, answer the following questions: (a) how much energy is stored in the inductor at $t = 3$ s?, (b) how much power is supplied by the source at $t = 4$ s?, (c) what is $i(t = 6$ s)?, and (d) how much power is absorbed by the inductor at $t = 3$ s?

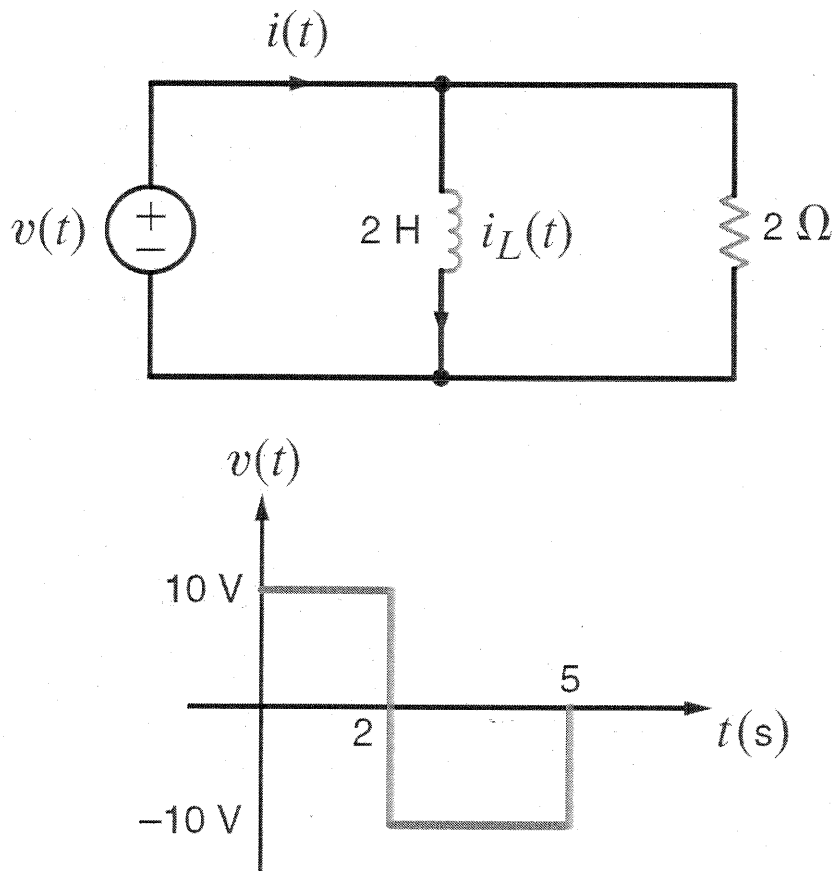


Figure P7.65

SOLUTION:

$$a) \quad w_L = \frac{1}{2} L i_L^2 \quad i_L(t) = \frac{1}{L} \int v_L dt = \frac{1}{L} \int v dt$$

$$i_L(3) = \frac{10}{2} t \Big|_0^2 - \frac{10}{2} t \Big|_2^3 = 5\text{ A}$$

$$w_L(3) = 25\text{ J}$$

$$b) \quad p_s(t) = v(t) i(t) = v(t) [i_L(t) + v(t)/R]$$

$$i_L(4) = \frac{1}{L} \int_0^4 v(t) dt = 5t \Big|_0^2 - 5t \Big|_2^4 = 0A$$

$$P_s(4) = v^2(4)/R = 100/2$$

$$P_s(4) = 50W$$

$$c) \quad i(6) = i_L(6) + \frac{v(6)}{R} \quad v(6) = 0$$

$$i_L(6) = \frac{1}{L} \int_0^6 v(t) dt = 5t \Big|_0^2 - 5t \Big|_2^6 = -5A$$

$$i(6) = -5A$$

$$d) \quad P_L = v(t) i_L(t) \quad i_L(3) = 5A \quad v(3) = -10V$$

$$P_L(3) = -50W \text{ absorbed}$$

7.66 In the circuit in Fig. P7.66, $v_R(t) = 100e^{-400t}$ V for $t < 0$. Find $v_R(t)$ for $t > 0$.

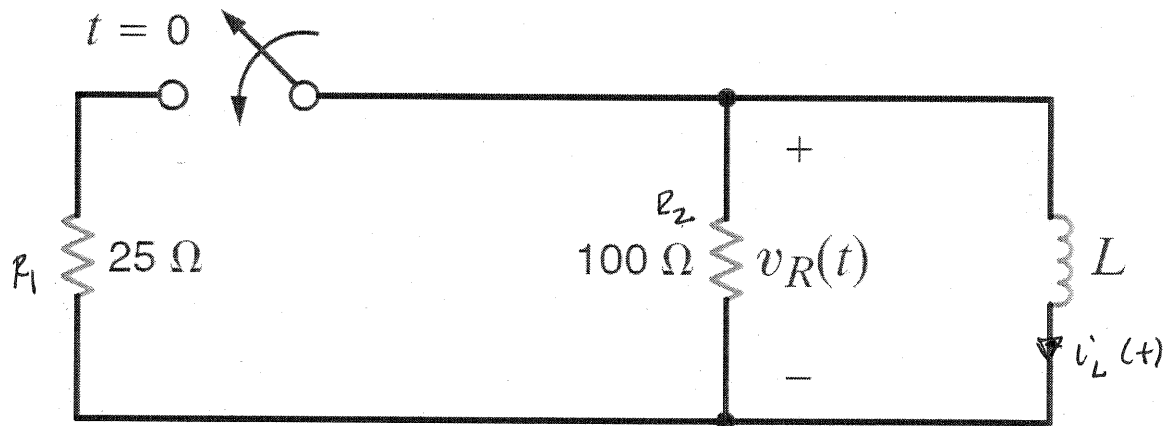


Figure P7.66

SOLUTION:

$$\underline{t=0^-} \quad v_R(0^-) = 100\text{V} \quad i_L(0^-) = -\frac{v_R(0^-)}{R_2} = -1\text{A}$$

$$\tau_1 = \frac{L}{R_2} = \frac{1}{400} \Rightarrow L = \frac{1}{4}\text{H}$$

$$\underline{t=0^+} \quad i_L(0^+) = -1\text{A} \quad v_R(0^+) = -\frac{i_L(0^+) R_2 R_1}{R_1 + R_2} = 20\text{V} = K_1 + K_2$$

$$\underline{t=\infty} \quad v_R = 0 = K_1 \Rightarrow K_2 = 20\text{V}$$

$$\underline{\tau} \quad \tau_2 = \frac{L(R_1 + R_2)}{R_1 R_2} = \frac{1}{80}\text{s}$$

$$\boxed{v_R(t) = 20e^{-80t}\text{V}}$$

7.67 Given that $v_{C1}(0^-) = -10$ V and $v_{C2}(0^-) = 20$ V in the circuit in Fig. P7.67, find $i(0^+)$.


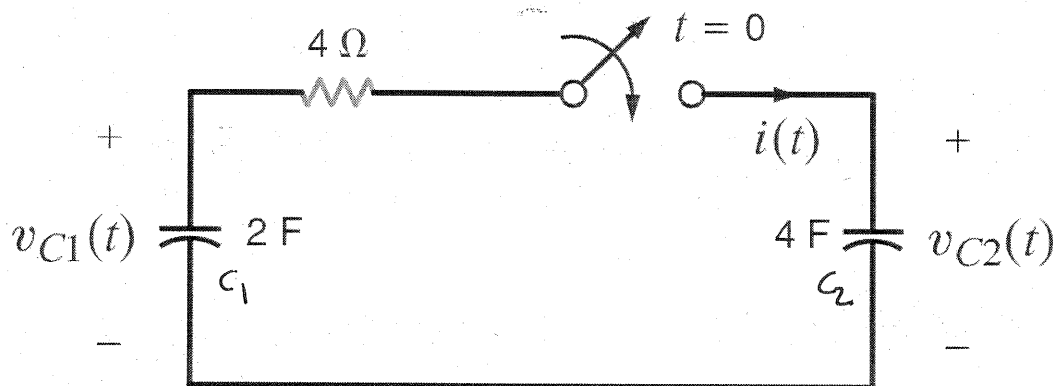


Figure P7.67

SOLUTION:

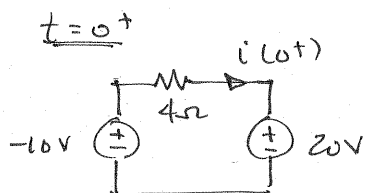v_{C1} & v_{C2} cannot change instantaneously.



$$i(0^+) = \frac{-10 - 20}{4} = -7.5 \text{ A}$$

$$i(0^+) = -7.5 \text{ A}$$

- 7.68 The switch in the circuit in Fig. P7.68 is closed at $t = 0$. If $i_1(0^-) = 2$ A, determine $i_2(0^+)$, $v_R(0^+)$, and $i_1(t = \infty)$.

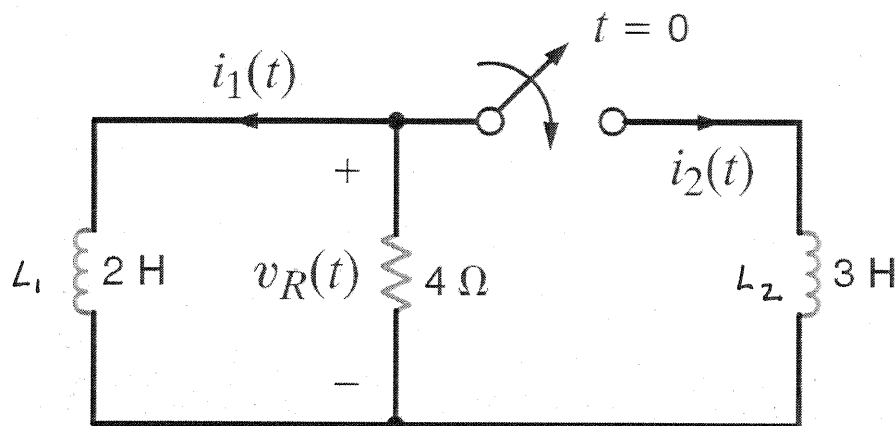


Figure P7.68

SOLUTION:

$$\underline{t=0^-} \quad i_1(0^-) = 2 \text{ A} \quad i_2(0^-) = 0 \text{ A}$$

$$\underline{t=0^+} \quad i_1(0^+) = i_1(0^-) = 2 \text{ A} \quad i_2(0^+) = i_2(0^-) = 0 \text{ A}$$

$$v_R(0^+) = -i_1(0^+) (4) = -8 \text{ V}$$

$v_R(0^+) = -8 \text{ V}$ $i_2(0^+) = 0 \text{ A}$ $i_1(\infty) = 0 \text{ A}$
--

$$\underline{t=\infty} \quad \text{all } v(t) \text{ \& } i(t) \rightarrow 0$$

$$i_1(\infty) = 0$$

7.69 In the network in Fig. P7.69 find $i(t)$ for $t > 0$. If $v_{C1}(0^-) = -10$ V, calculate $v_{C2}(0^-)$.



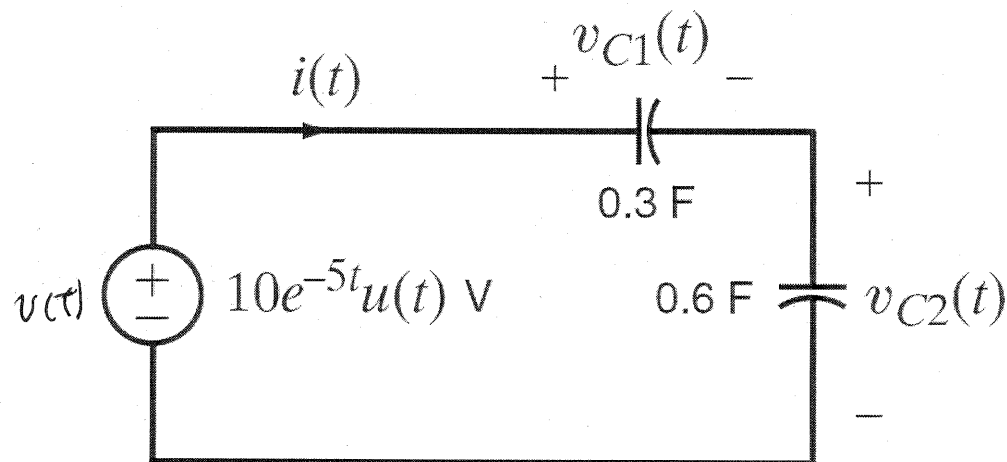
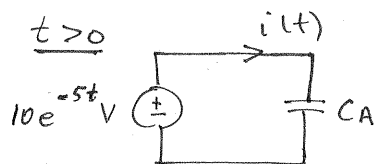


Figure P7.69

SOLUTION:

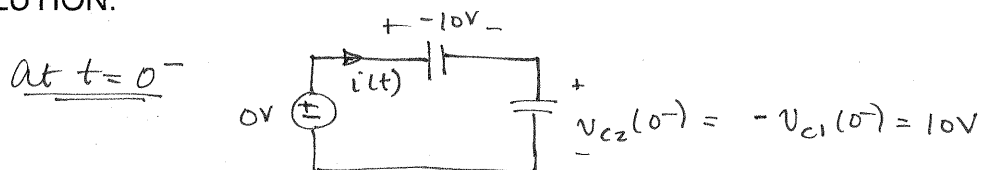
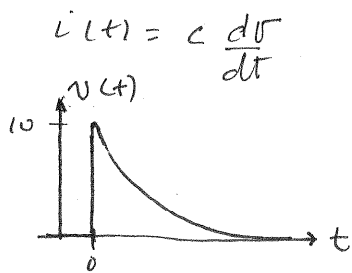
$$C_A = \frac{C_1 C_2}{C_1 + C_2} = 0.2 \text{ F}$$



$$\frac{dv}{dt} = 10 \delta(t) - 50 e^{-5t} \quad t \geq 0$$

$$i(t) = 2 \delta(t) - 10 e^{-5t} \text{ A} \quad t \geq 0$$

$$v_{C2}(0^-) = 10 \text{ V}$$

7.70 The switch in the circuit in Fig. P7.70 has been closed for a long time and is opened at $t = 0$. If $v_C(t) = 20 - 8e^{-0.05t}$ V, find R_1 , R_2 , and C .

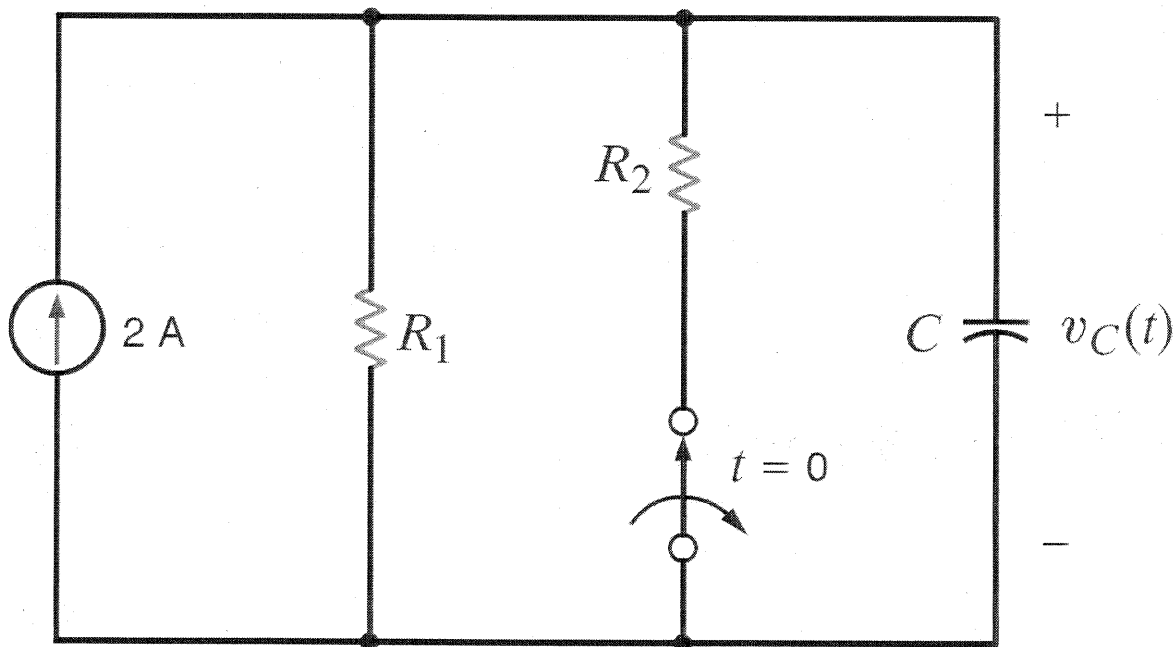


Figure P7.70

SOLUTION:

$$v_C(t) = 20 - 8e^{-t/20} \text{ V} = k_1 + k_2 e^{-t/\tau}$$

$$k_1 = v_C(\infty) = 2R_1 = 20 \quad R_1 = 10 \Omega$$

$$k_1 + k_2 = v_C(0^+) = v_C(0^-) = \frac{2(R_1 R_2)}{R_1 + R_2} = 12 \Rightarrow R_2 = 15 \Omega$$

$$\tau = CR_1 = 20 \text{ s} \quad C = 2 \text{ F}$$

$$\begin{aligned} C &= 2 \text{ F} \\ R_1 &= 10 \Omega \\ R_2 &= 15 \Omega \end{aligned}$$

- 7.71 Given that $i(t) = 13.33e^{-t} - 8.33e^{-0.5t}$ A for $t > 0$ in the network in Fig. P7.71, find the following: (a) $v_C(0)$, (b) $v_C(t = 1 \text{ s})$, and (c) the capacitance C .

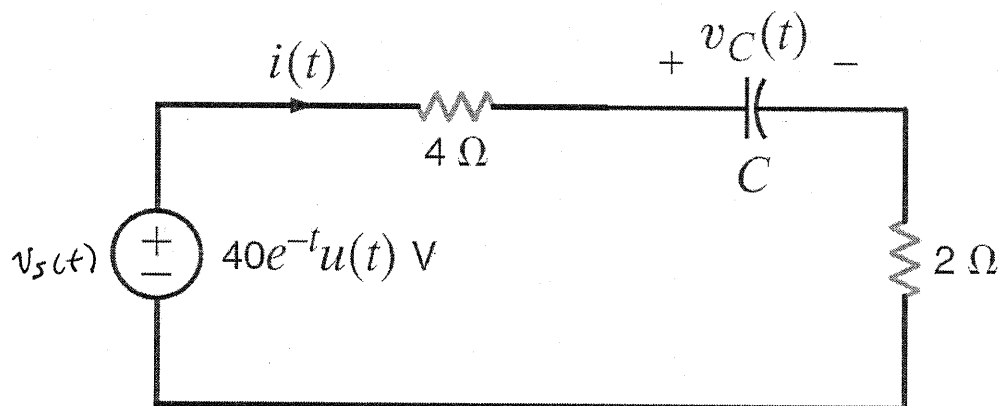


Figure P7.71

SOLUTION:

$$a) v_C(0^-) = v_s(0^-) = 0 \text{ V} = v_C(0^+) \quad \boxed{v_C(0) = 0 \text{ V}}$$

$$b) v_C(t) = \frac{1}{C} \int i \, dt + K$$

$$= \frac{1}{C} \left[16.46 e^{-t/2} - 13.33 e^{-t} \right] + K$$

$$v_C(0) = 0 = \frac{1}{C} [3.33] + K \Rightarrow K = -3.33/C$$

Need C .

$$c) \tau = 2 = C[4+2] = 6C \Rightarrow \boxed{C = 1/3 \text{ F}}$$

Back to b)

$$K = -10 \quad v_C(t) = 50e^{-t/2} - 40e^{-t} - 10$$

$$\boxed{v_C(1) = 5.61 \text{ V}}$$

7.72 Given that $i(t) = 2.5 + 1.5e^{-4t}$ A for $t > 0$ in the circuit in Fig. P7.72, find R_1 , R_2 , and L .

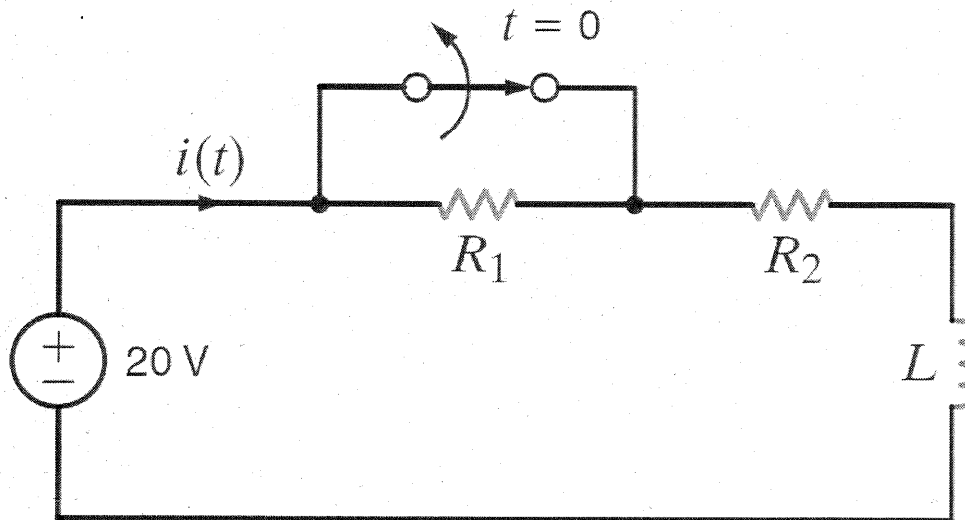


Figure P7.72

SOLUTION:

$$i(t) = 2.5 + 1.5e^{-4t} = k_1 + k_2 e^{-t/\tau}$$

$$k_1 = 2.5 = i(\infty) = \frac{20}{R_1 + R_2} \Rightarrow R_1 + R_2 = 8 \Omega$$

$$k_1 + k_2 = 4 = i(0^+) = i_L(0^+) = i_L(0^-) = \frac{20}{R_2} \Rightarrow R_2 = 5 \Omega$$

$$R_1 = 3 \Omega$$

$$\tau = \frac{1}{4} = \frac{L}{R_1 + R_2} \quad L = 2 \text{ H}$$

$$L = 2 \text{ H}$$

$$R_1 = 3 \Omega$$

$$R_2 = 5 \Omega$$

7.73 The differential equation that describes the current $i_o(t)$ in a network is

$$\frac{d^2 i_o(t)}{dt^2} + 6 \left[\frac{di_o(t)}{dt} \right] + 4i_o(t) = 0$$

Find (a) the characteristic equation of the network, (b) the network's natural frequencies, and (c) the expression for $i_o(t)$.

SOLUTION:

a) $s^2 + 6s + 4 = 0$

b) $s_{1,2} = \frac{-6 \pm \sqrt{36 - 16}}{2} = \left\{ \begin{array}{l} -0.764 \\ -5.24 \end{array} \right\} = s_{1,2}$

c) $2\zeta\omega_0 = 6 \quad \omega_0^2 = 4 \quad \Rightarrow \quad \zeta = 1.5 \quad \text{over damped.}$

$$i_o(t) = k_1 e^{-0.764t} + k_2 e^{-5.24t}$$

7.74 The terminal current in a network is described by the equation

$$\frac{d^2 i_o(t)}{dt^2} + 8 \left[\frac{di_o(t)}{dt} \right] + 16 i_o(t) = 0$$

Find (a) the characteristic equation of the network, (b) the network's natural frequencies, and (c) the equation for $i_o(t)$.

SOLUTION:

a) $s^2 + 8s + 16 = 0$

b) $s_{1,2} = \frac{-8 \pm \sqrt{64 - 64}}{2} = -4 \text{ r/s}$

c) $2\zeta\omega_0 = 8 \quad \omega_0^2 = 16 \Rightarrow \zeta = 1 \Rightarrow \text{critically damped.}$

$$i_o(t) = B_1 e^{-4t} + B_2 t e^{-4t}$$

7.75 The voltage $v_1(t)$ in a network is defined by the equation

$$\frac{d^2v_1(t)}{dt^2} + 2\left[\frac{dv_1(t)}{dt}\right] + 5v_1(t) = 0$$

Find

- (a) the characteristic equation of the network.
- (b) the circuit's natural frequencies.
- (c) the expression for $v_1(t)$. **CS**

SOLUTION:

a) $s^2 + 2s + 5 = 0$

b) $s_{1,2} = \frac{-2 \pm \sqrt{4 - 20}}{2} = -1 \pm j2 \text{ r/s}$

c) underdamped!

$$v_1(t) = e^{-t} [A_1 \cos 2t + A_2 \sin 2t]$$

7.76 The output voltage of a circuit is described by the differential equation

$$\frac{d^2v_o(t)}{dt^2} + 8\left[\frac{dv_o(t)}{dt}\right] + 10v_o(t) = 0$$

Find (a) the characteristic equation of the circuit, (b) the network's natural frequencies, and (c) the equation for $v_o(t)$.

SOLUTION:

a) $s^2 + 8s + 10 = 0$


b) $s_{1,2} = \frac{-8 \pm \sqrt{64 - 40}}{2} = \begin{cases} -1.55 \text{ r/s} \\ -6.45 \text{ r/s} \end{cases}$

c) overdamped!

$$v_o(t) = k_1 e^{-1.55t} + k_2 e^{-6.45t}$$

7.77 The parameters for a parallel RLC circuit are $R = 1 \Omega$, $L = 1/2 \text{ H}$, and $C = 1/2 \text{ F}$. Determine the type of damping exhibited by the circuit.

SOLUTION:

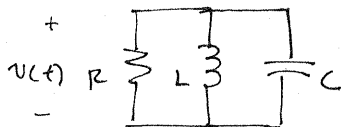

$$\frac{v(t)}{R} + \frac{1}{L} \int v dt + C \frac{dv}{dt} = 0$$

$$C \frac{d^2 v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v(t) = 0$$

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v(t) = 0$$


$$\omega_0^2 = \frac{1}{LC} = 4 \Rightarrow \omega_0 = 2 \text{ rad/s}$$

$$2\zeta\omega_0 = 2 \Rightarrow \zeta = 1/2$$

Underdamped

7.78 A series RLC circuit contains a resistor $R = 2 \Omega$ and a capacitor $C = 1/2 \text{ F}$. Select the value of the inductor so that the circuit is critically damped.

SOLUTION:

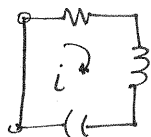

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0$$

$$\frac{di^2}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i(t) = 0$$

$$\frac{1}{LC} = \omega_0^2$$

$$2 \zeta \omega_0 = \frac{R}{L}$$

for $\zeta = 1$,


$$2\omega_0 = \frac{R}{L} \Rightarrow \frac{2}{\sqrt{LC}} = \frac{R}{L} \Rightarrow \sqrt{L} = \frac{R\sqrt{C}}{2}$$

$$L = \frac{R^2 C}{4}$$

$$\boxed{L = \frac{1}{2} \text{ H}}$$

7.79 A parallel RLC circuit contains a resistor $R = 1 \Omega$ and an inductor $L = 2 \text{ H}$. Select the value of the capacitor so that the circuit is critically damped.

SOLUTION:

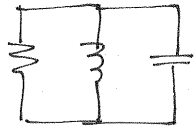

$$s^2 + \frac{s}{RC} + \frac{1}{LC} = 0$$

$$\omega_0^2 = \frac{1}{LC}$$

$$2\zeta\omega_0 = \frac{1}{RC}$$

$$\zeta = 1$$

$$2\omega_0 = \frac{1}{RC} = \frac{2}{\sqrt{LC}} \Rightarrow \sqrt{C} = \frac{\sqrt{L}}{2R} \Rightarrow C = \frac{L}{4R^2} = \frac{1}{2} \text{ F}$$

$$\boxed{C = \frac{1}{2} \text{ F}}$$

- 7.80 For the underdamped circuit shown in Fig. P7.80, determine the voltage $v(t)$ if the initial conditions on the storage elements are $i_L(0) = 1$ A and $v_C(0) = 10$ V. **CS**

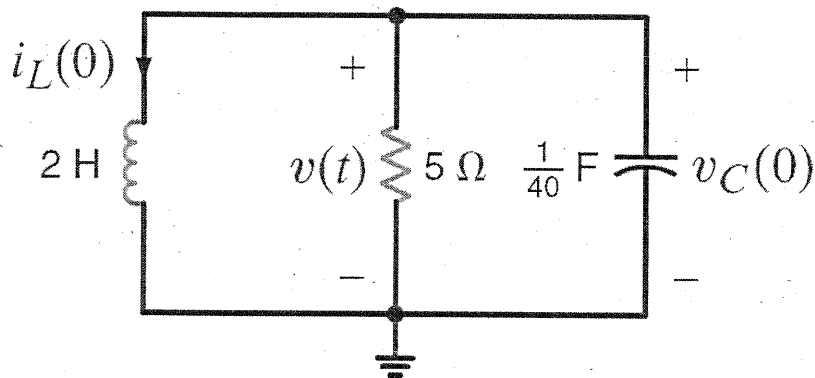


Figure P7.80

SOLUTION:

characteristic eq: $s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0 \Rightarrow s^2 + 8s + 20 = 0$

natural freq: $s_{1,2} = \frac{-8 \pm \sqrt{64 - 80}}{2}$ $s_{1,2} = -4 \pm j2$ r/s

$$v(t) = e^{-4t} [A_1 \cos 2t + A_2 \sin 2t]$$

$$v_C(0) = v(0) = A_1 = 10$$

$$i_L(0) = 1 = -\frac{v(0)}{5} - C \frac{dv}{dt} \Big|_{t=0} \quad v(0) = 10 \text{ V}$$

$$\frac{dv}{dt} = -4e^{-4t} [A_1 \cos 2t + A_2 \sin 2t] + e^{-4t} [-2A_1 \sin 2t + 2A_2 \cos 2t]$$

$$\frac{dv}{dt} \Big|_{t=0} = -40 + 2A_2 \quad \rightarrow \quad 1 = -2 + \frac{40}{40} - \frac{2A_2}{40} \Rightarrow A_2 = -40 \text{ V}$$

$$v(t) = e^{-4t} [10 \cos 2t - 40 \sin 2t] \text{ V}$$

7.81 In the critically damped circuit shown in Fig. P7.81, the initial conditions on the storage elements are $i_L(0) = 2$ A and $v_C(0) = 5$ V. Determine the voltage $v(t)$.

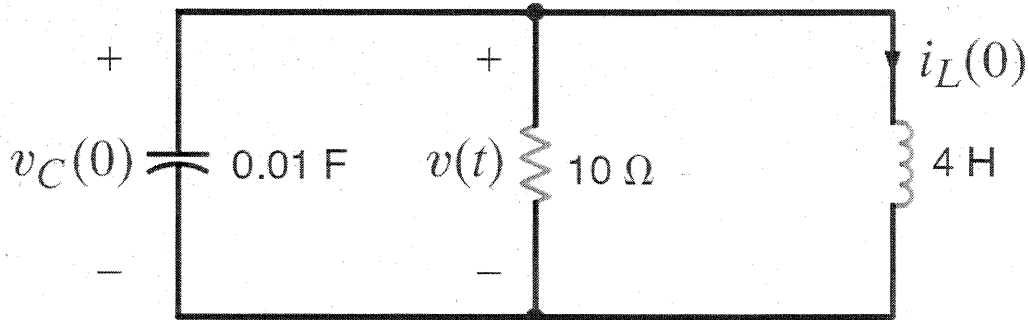


Figure P7.81

SOLUTION:

characteristic eq: $s^2 + \frac{s}{RC} + \frac{1}{LC} = 0 = s^2 + 10s + 25 = 0$

natural freq: $s_{1,2} = \frac{-10 \pm \sqrt{100 - 100}}{2} = -5$ critically damped!

$$v(t) = B_1 e^{-5t} + B_2 t e^{-5t} \text{ V}$$

$$v_C(0) = v(0) = B_1 = 5$$

$$i_L(0) = 2 = -\frac{v(0)}{R} - C \left. \frac{dv}{dt} \right|_{t=0} = -\frac{1}{2} - C \left. \frac{dv}{dt} \right|_{t=0}$$


$$\left. \frac{dv}{dt} \right|_{t=0} = \left[-5B_1 e^{-5t} + B_2 e^{-5t} - 5B_2 t e^{-5t} \right]_{t=0} = -5B_1 + B_2$$

$$2 = -\frac{1}{2} + \frac{25 - B_2}{100} \Rightarrow B_2 = -225$$

$$v(t) = 5e^{-5t} - 225te^{-5t} \text{ V}$$

7.82 Given the circuit and the initial conditions from Problem 7.81, determine the current $i_L(t)$ that is flowing through the inductor.

SOLUTION:

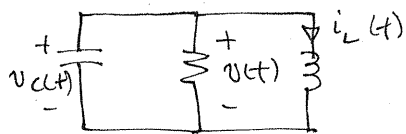

$$R = 10\Omega \quad L = 4\text{H} \quad C = 0.01\text{F}$$

$$v_L(0^-) = 5\text{V} \quad i_L(0^-) = 2\text{A}$$

from 7.81, $v(t) = 5e^{-5t} - 225te^{-5t} \text{ V}$

$$i_L = \frac{1}{L} \int v dt$$

from integration tables: $\int te^{-st} dt = -\frac{te^{-st}}{s} - \frac{1}{s^2} e^{-st}$

$$i_L = \frac{1}{L} \int 5e^{-5t} - 225te^{-5t} dt = 2e^{-5t} + 11.25te^{-5t} \text{ A}$$

$$i_L(t) = 2e^{-5t} + 11.25te^{-5t} \text{ A}$$

7.83 Find $v_C(t)$ for $t > 0$ in the circuit in Fig. P7.83. CS

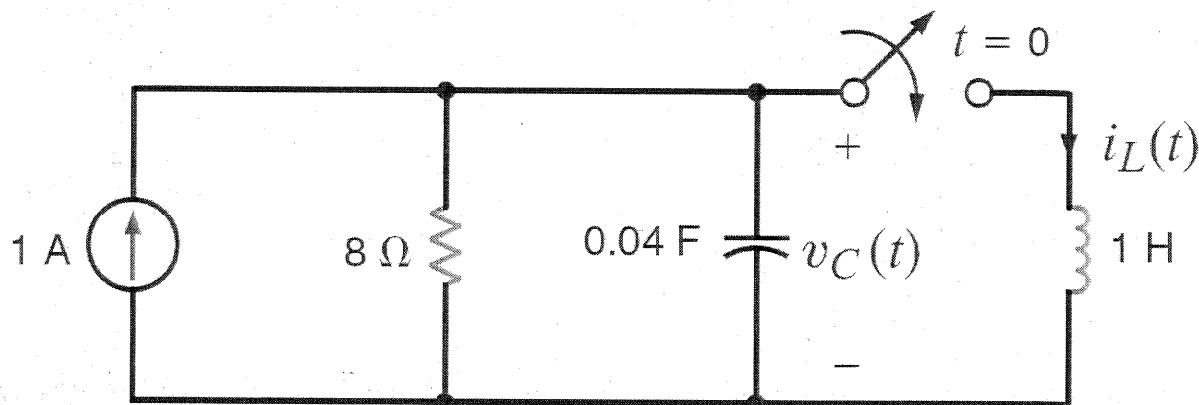


Figure P7.83

SOLUTION:

$$t=0^-: \quad v_C(0^-) = 8V \quad i_L(0^-) = 0$$

$$t>0: \quad \frac{d^2 v_C}{dt^2} + \frac{1}{RC} \frac{dv_C}{dt} + \frac{1}{LC} v_C = 0 \Rightarrow s^2 + 3.125s + 25 = 0$$

natural frequencies: $s_{1,2} = -1.5625 \pm j4.75 \text{ r/s} = \sigma \pm j\omega$

$$v_C(t) = e^{-\sigma t} [A_1 \cos \omega t + A_2 \sin \omega t]$$

$$v_C(0^-) = A_1 = 8$$

$$-i_L(0^-) = 0 = \left. \frac{v_C}{R} \right|_{t=0} + C \left. \frac{dv_C}{dt} \right|_{t=0} = \frac{A_1}{R} + C [A_2 \omega - \sigma A_1]$$

yields $A_2 = -2.63 \text{ V}$

$$v_C(t) = e^{-\sigma t} [8 \cos \omega t - 2.63 \sin \omega t]$$

$$\sigma = 1.5625 \quad \omega = 4.75 \text{ r/s}$$

7.84 Find $v_C(t)$ for $t > 0$ in the circuit in Fig. P7.84 if $v_C(0) = 0$.

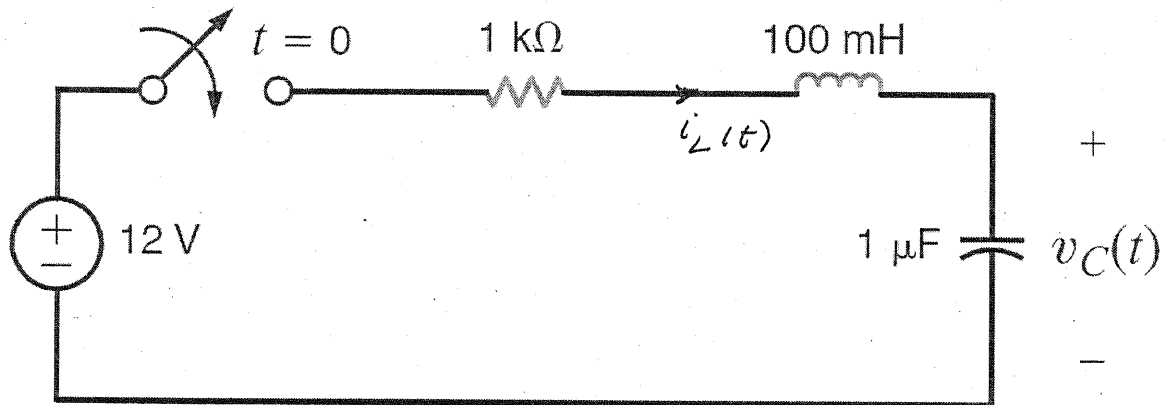


Figure P7.84

SOLUTION: $t=0^-: v_C = 0 \quad i_L = 0$

$$\frac{di_L}{dt^2} + \frac{R}{L} \frac{di_L}{dt} + \frac{i_L}{LC} = 0 \Rightarrow s^2 + 10^4 s + 10^7 = 0$$

$$\text{Natural frequencies: } s_{1,2} = \begin{cases} -1127 = -\sigma_1 \\ -8873 = -\sigma_2 \end{cases}$$

$$i_L(t) = k_1 e^{-1127t} + k_2 e^{-8873t} = k_1 e^{-\sigma_1 t} + k_2 e^{-\sigma_2 t}$$

$$i_L(0) = 0 = k_1 + k_2$$

$$12 = R i_L(0^+) + L \left. \frac{di_L}{dt} \right|_{t=0^+} + v_C(0^+) = R k_1 + R k_2 - L \sigma_1 k_1 - L \sigma_2 k_2 + v_C(0^+)$$

$$v_C(0^+) = v_C(0^-) = 0V \Rightarrow k_1 = 15.5 \text{ mA} \quad k_2 = -15.5 \text{ mA}$$

$$v_C(t) = \frac{1}{C} \int i_L(t) dt + k_3 \Rightarrow v_C(0^+) = 0 = -\frac{k_1}{C\sigma_1} - \frac{k_2}{C\sigma_2} + k_3$$

$$k_3 = 12V$$

$$v_C(t) = 17.5 e^{-\sigma_2 t} - 13.75 e^{-\sigma_1 t} + 12 \text{ V} \quad \begin{matrix} \sigma_1 = 1127 \\ \sigma_2 = 8873 \end{matrix}$$

7.85 Find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.85 and plot the response including the time interval just prior to closing the switch. **PSV**

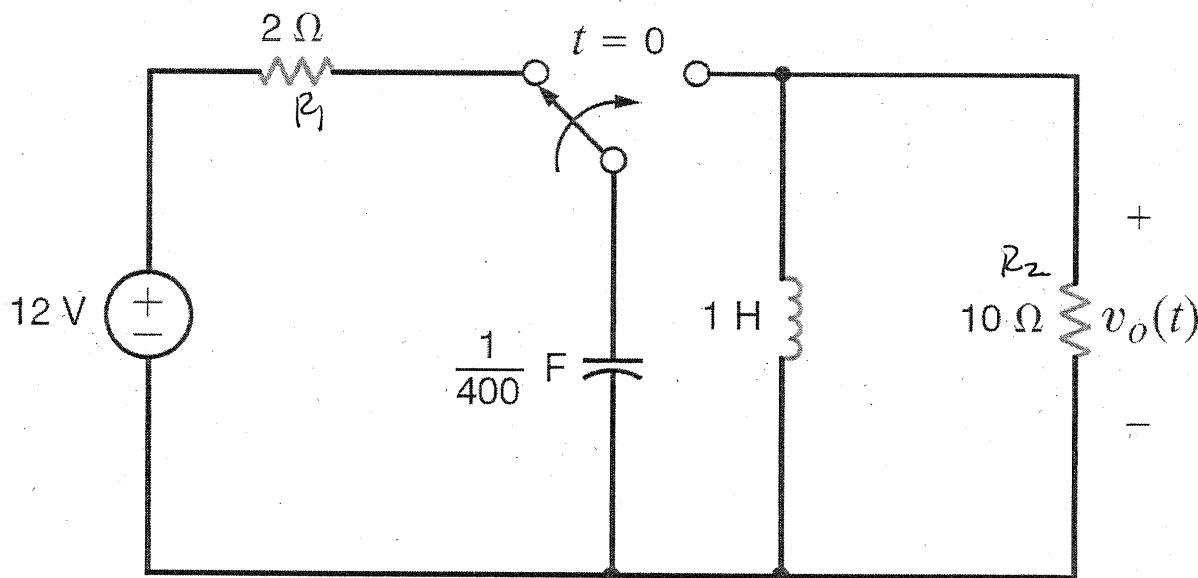


Figure P7.85

SOLUTION: $t=0^-$ $v_C(0^-) = 12\text{V}$ $i_L(0^+) = 0 = i_L(0^-)$

$$t > 0 \quad \frac{d^2 v_o}{dt^2} + \frac{dv_o}{dt} \left(\frac{1}{RC} \right) + \frac{v_o}{LC} = 0 \Rightarrow s^2 + 40s + 400 = 0$$

natural frequencies: $s_{1,2} = -20 \pm 15j$

$$v_o(t) = B_1 e^{-20t} + B_2 t e^{-20t}$$


$$v_o(0^+) = v_C(0^+) = 12\text{V} = B_1$$

$$-i_L(0^+) = 0 = \frac{v_o(0^+)}{R_2} + C \left. \frac{dv_o}{dt} \right|_{t=0^+} = \frac{12}{10} + C [-20B_1 + B_2]$$

$$B_2 = -240\text{V}$$

$$v_o(t) = 12e^{-20t} - 240te^{-20t} \text{ V}$$

PROBLEM 7.85

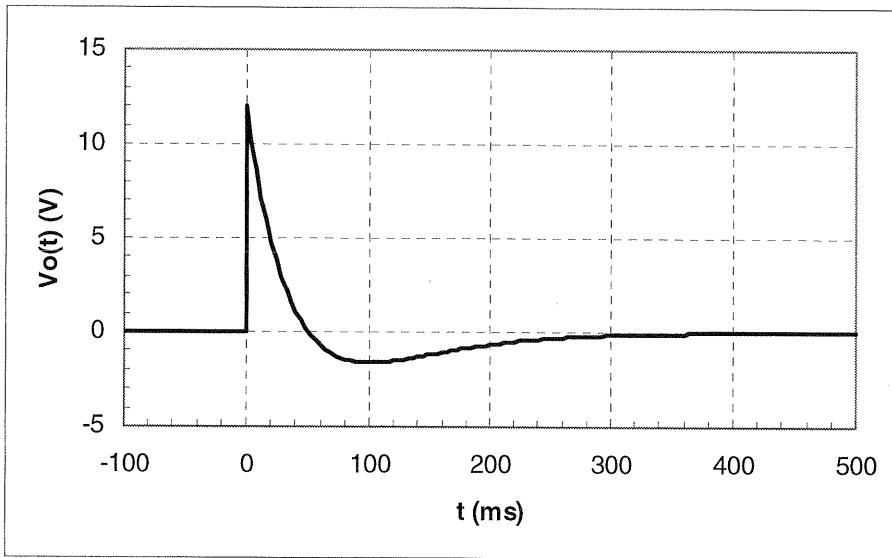

7.86 Find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.86 and plot the response including the time interval just prior to closing the switch.


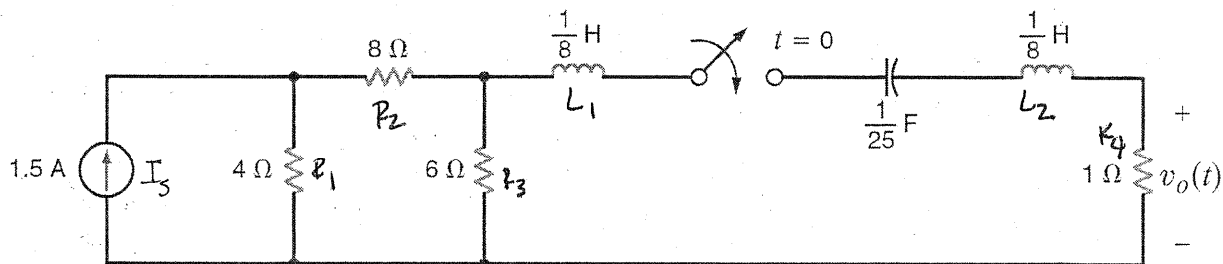



Figure P7.86

SOLUTION:

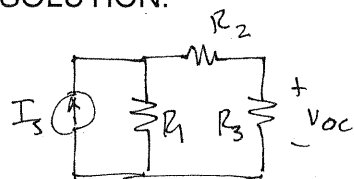

$$V_{oc} = \frac{I_s R_1}{R_1 + R_2 + R_3} R_3 = 2V$$
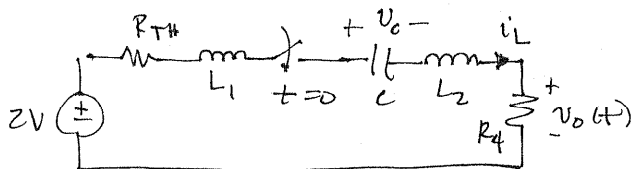
$$R_{TH} = R_3 // (R_1 + R_2) = 4\Omega$$



$$t=0^- : i_{L1} = i_{L2} = i_L = 0A \\ v_c(0^-) = 0V$$

$$t > 0 : \frac{di_L}{dt} + \frac{R}{L} i_L + \frac{1}{LC} i_L = 0 \Rightarrow s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

$$R = R_{TH} + R_4$$

$$L = L_1 + L_2$$

$$s_{1,2} = -10 \pm 15 \quad i_L(t) = B_1 e^{-10t} + B_2 t e^{-10t}$$

$$i_L(0^+) = i_L(0^-) = 0 = B_1 \Rightarrow i_L(t) = B_2 t e^{-10t}$$

$$v_c(0^+) = 0 = 2 - R i_L(0^+) - L \left. \frac{di_L}{dt} \right|_{t=0} = 2 - 0 - L B_2$$


$$B_2 = \frac{2}{L} = 8$$

$$i_L(t) = 8t e^{-10t} A$$

$$v_o = R_4 i_L(t)$$

$$v_o(t) = 8t e^{-10t} V$$

PROBLEM 7.86

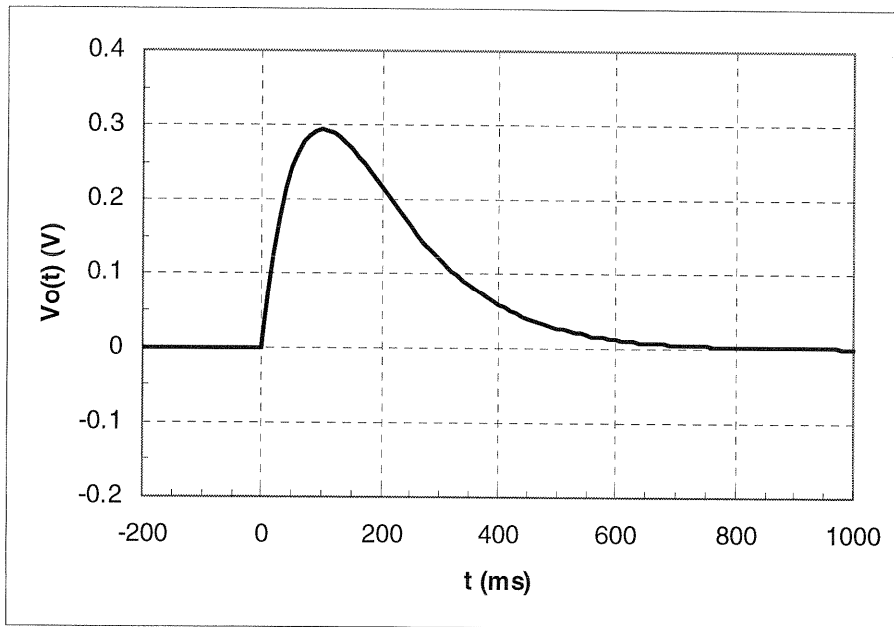

7.87 In the circuit shown in Fig. P7.87, switch action occurs at $t = 0$. Determine the voltage $v_o(t)$, $t > 0$.

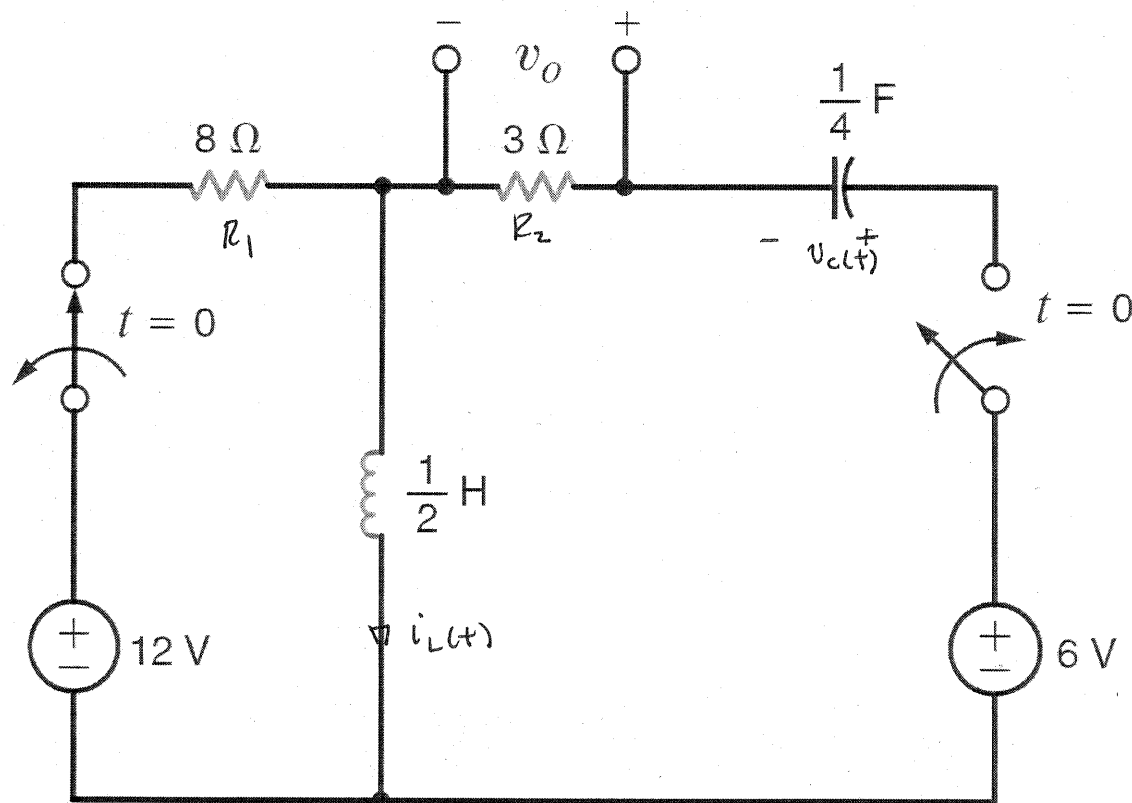


Figure P7.87

SOLUTION: $t = 0^-$: $i_L(0^-) = 12/R_1 = 1.5\text{A}$ $v_c(0^-) = 0\text{V}$

$$t > 0: \quad 6 = \frac{1}{C} \int i_L dt + R_2 i_L(t) + L \frac{di_L}{dt} \Rightarrow \frac{di_L^2}{dt^2} + \frac{R_2}{L} \frac{di_L}{dt} + \frac{i_L(t)}{LC} = 0$$

$$s^2 + 6s + 8 = 0 \Rightarrow s_{1,2} = \left\{ \begin{array}{l} -2 = -\sigma_1 \\ -4 = -\sigma_2 \end{array} \right\}$$

$$i_L(t) = K_1 e^{-\sigma_1 t} + K_2 e^{-\sigma_2 t} \quad i_L(0^+) = 1.5 = K_1 + K_2$$

$$6 = v_c(0^+) + R_2 i_L(0^+) + L \left. \frac{di_L}{dt} \right|_{t=0} = 0 + R_2(1.5) - LK_1\sigma_1 - LK_2\sigma_2$$

yields,

$$K_1 = 4.5\text{V} \quad K_2 = -3\text{V}$$

$$v_o = R_2 i_L$$

$$v_o = 4.5e^{-2t} - 3e^{-4t} \text{ V}$$

7.88 Find $v_o(t)$ for $t > 0$ in the circuit in Fig. P7.88 and plot the response including the time interval just prior to moving the switch.


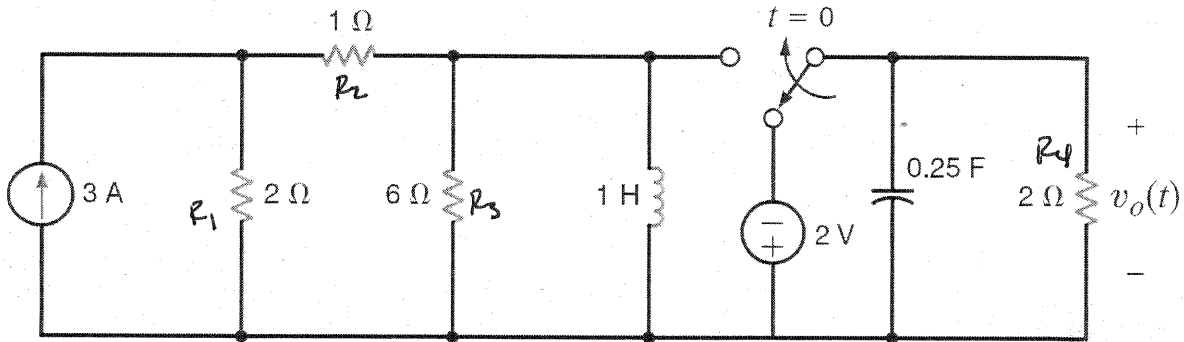



Figure P7.88

SOLUTION:

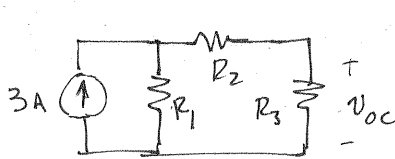

$$V_{oc} = 3 \left[\frac{R_1 R_3}{R_1 + R_2 + R_3} \right] = 4V$$

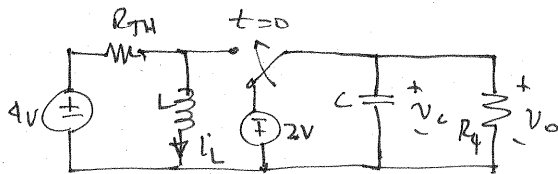
$$R_{TH} = R_3 \parallel [R_1 + R_2] = 2\Omega$$



$$t < 0: i_L = \frac{4}{R_{TH}} = 2A$$

$$v_C = -2V$$

$t > 0:$

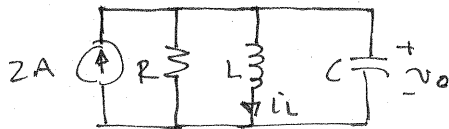

$$R = R_4 \parallel R_{TH} = 1\Omega$$

$$\frac{d^2 v_o}{dt^2} + \frac{dv_o}{dt} \left(\frac{1}{RC} \right) + \frac{v_o}{LC} = 0$$


$$s^2 + 4s + 4 = 0 \Rightarrow s_{1,2} = -2 \text{ r/s} \quad v_o(t) = B_1 e^{-2t} + B_2 t e^{-2t}$$

$$v_o(0^+) = v_o(0^-) = -2V = B_1$$

$$2 - i_L(0^+) = 0 = \frac{v_o(0^+)}{R} + C \left. \frac{dv_o}{dt} \right|_{t=0^+} = \frac{B_1}{R} - 2B_1 C + C B_2 \Rightarrow B_2 = 4V$$

$$v_o(t) = -2e^{-2t} + 4te^{-2t} \text{ V}$$

PROBLEM 7.88

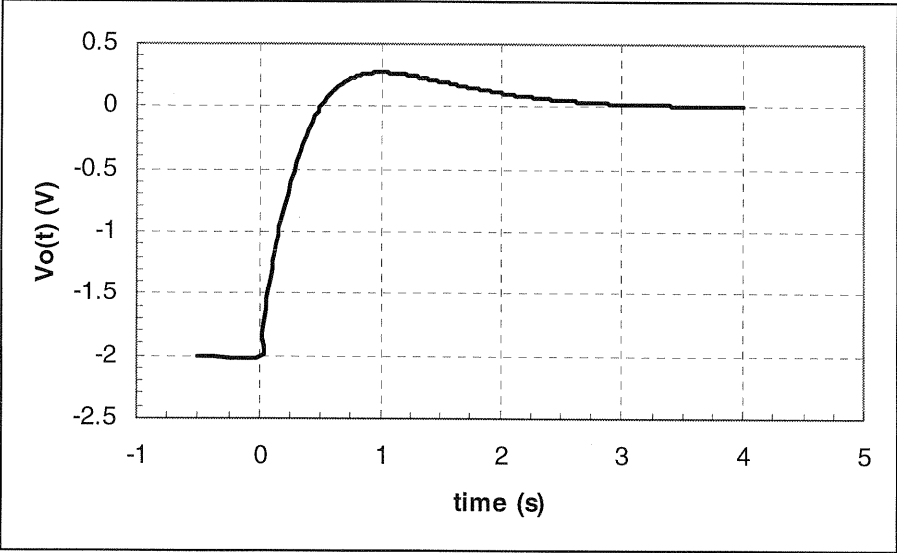

7.89 The switch in the circuit in Fig. P7.89 has been closed for a long time and is opened at $t = 0$. Find $i(t)$ for $t > 0$. **PSV**

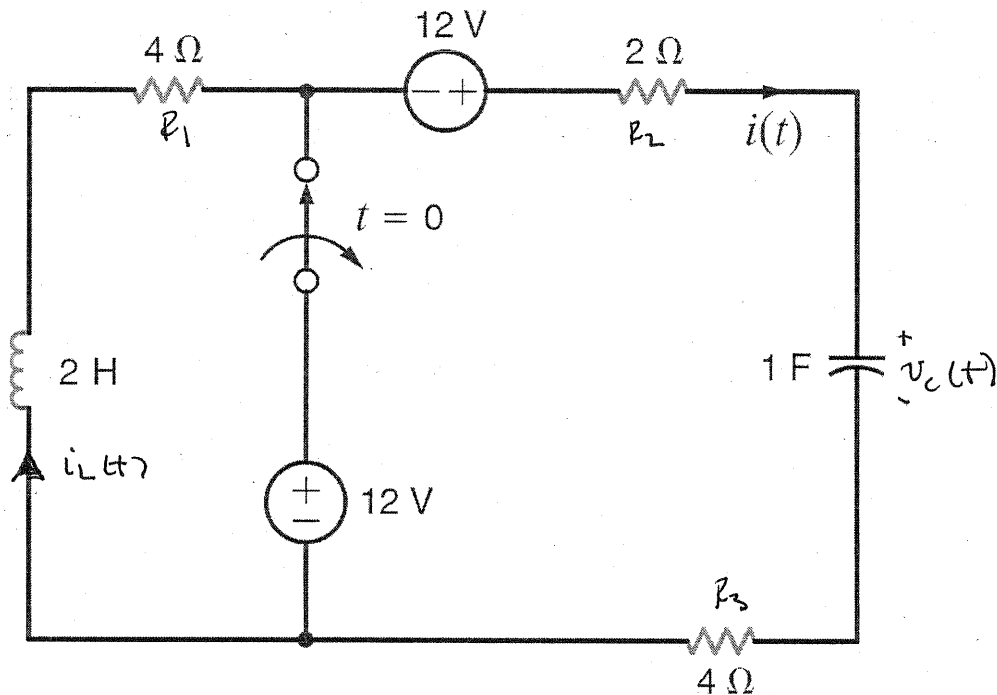


Figure P7.89

SOLUTION: $t < 0^-$: $i_L(0^-) = -\frac{12}{R_1} = -3 \text{ A}$ $v_C(0^-) = 24 \text{ V}$

$t > 0$: $12 = (R_1 + R_2 + R_3)i(t) + \frac{1}{C} \int i(t) dt + L \frac{di(t)}{dt} = R i(t) + \frac{1}{C} \int i(t) dt + L \frac{di}{dt}$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \Rightarrow s^2 + 5s + 0.5 = 0 \quad s_{1,2} = \begin{cases} -0.10 = -\sigma_1 \\ -4.89 = -\sigma_2 \end{cases}$$

$$i(t) = K_1 e^{-\sigma_1 t} + K_2 e^{-\sigma_2 t} \quad i(0^+) = i_L(0^+) = -3 = K_1 + K_2$$

$$v_C(0^+) = 12 - R i(0^+) - L \left. \frac{di}{dt} \right|_{t=0^+} = 12 + 3R + L K_1 \sigma_1 + L K_2 \sigma_2 = 24$$

yields

$$K_1 = -1.19 \text{ A}$$

$$K_2 = -1.81 \text{ A}$$

$$i(t) = -1.19 e^{-0.10t} - 1.81 e^{-4.89t} \text{ A}$$

7.90 The switch in the circuit in Fig. P7.90 has been closed for a long time and is opened at $t = 0$. Solve for $i(t)$ for $t > 0$.

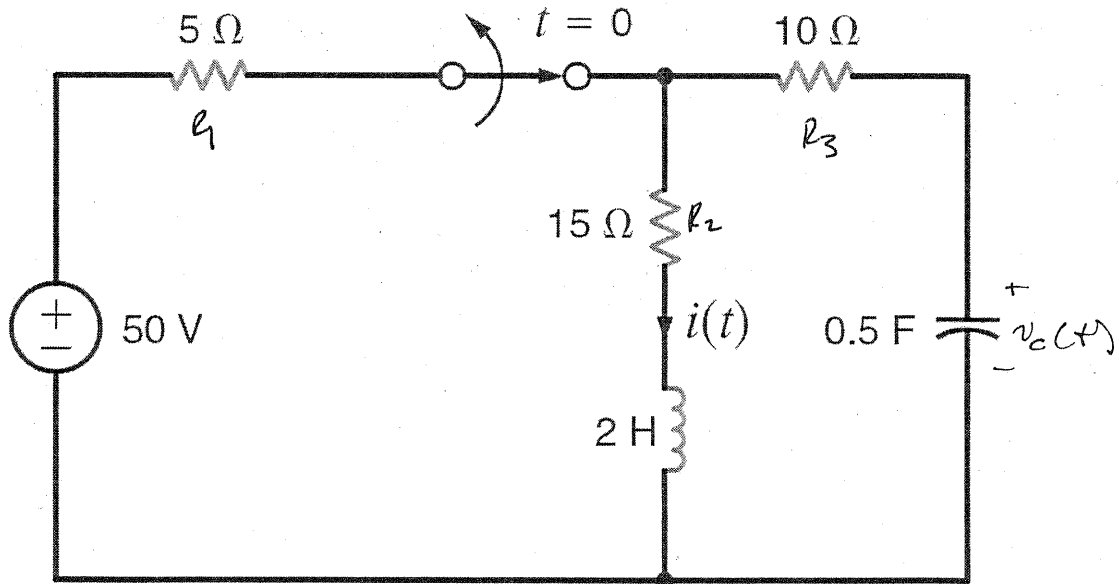


Figure P7.90

SOLUTION: $t = 0^-$: $i(0^-) = \frac{50}{R_1 + R_2} = 2.5 \text{ A}$ $v_c(0^-) = i(0^-) R_3 = 37.5 \text{ V}$

$t > 0$: $L \frac{di}{dt} + R i(t) + \frac{1}{C} \int i dt = 0$ $R = R_2 + R_3 = 25$
 $v_c(t) = -\frac{1}{C} \int i dt$

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0 = s^2 + 12.5s + 1$$

$$s_{1,2} = \left\{ \begin{array}{l} -0.08 = -\sigma_1 \\ -12.42 = -\sigma_2 \end{array} \right\} \quad i(t) = K_1 e^{-\sigma_1 t} + K_2 e^{-\sigma_2 t}$$

$$i(0^+) = K_1 + K_2 = 2.5 \quad v_c(0^+) = 37.5 = R i(0^+) + L \left. \frac{di}{dt} \right|_{t=0}$$

yield

$$= R(2.5) - L\sigma_1 K_1 - L\sigma_2 K_2$$

$$K_1 = 1.5 \quad K_2 = 1$$

$$i(t) = e^{-12.42t} + 1.5 e^{0.08t} \text{ A} \quad \begin{array}{l} \sigma_1 = 0.08 \\ \sigma_2 = 12.42 \end{array}$$

7.91 The switch in the circuit in Fig. P7.91 has been closed for a long time and is opened at $t = 0$. Solve for $i(t)$ for $t > 0$.

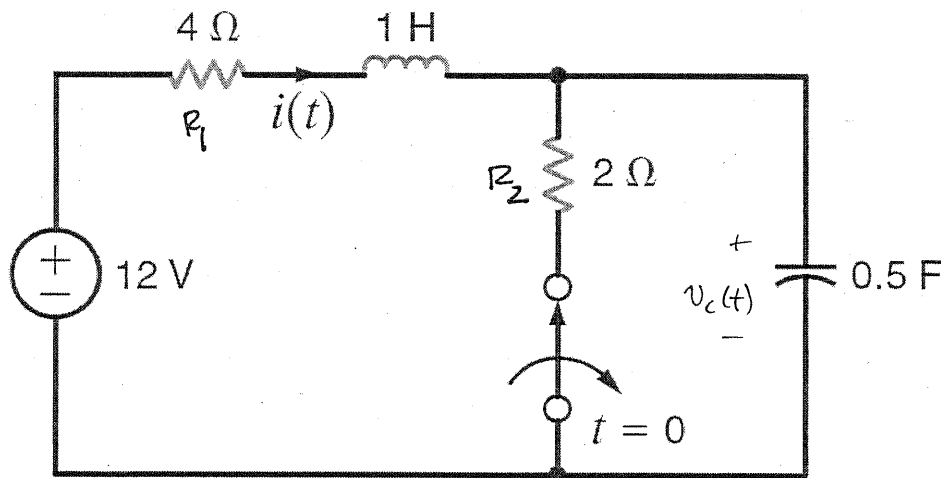


Figure P7.91

SOLUTION: $t = 0^-$: $i(0^+) = \frac{12}{R_1 + R_2} = 2 \text{ A}$ $v_c(0^+) = i(0^+) R_2 = 4 \text{ V}$

$$t = 0^+ \quad 12 = L \frac{di}{dt} + R_1 i + \frac{1}{C} \int i(t) dt \Rightarrow \frac{d^2 i}{dt^2} + 4 \frac{di}{dt} + 2 = 0$$

$$s^2 + 4s + 1/2 = 0 \quad s_{1,2} = \begin{cases} -0.586 = -\sigma_1 \\ -3.41 = -\sigma_2 \end{cases}$$

$$i(t) = k_1 e^{-\sigma_1 t} + k_2 e^{-\sigma_2 t} \quad i(0) = 2 = k_1 + k_2$$

$$v_c(0^+) = 12 - R_1 i(0^+) - L \left. \frac{di}{dt} \right|_{t=0} = 12 - 8 + \sigma_1 k_1 + \sigma_2 k_2 = 4$$

$$k_1 + k_2 = 2 \quad \& \quad \sigma_1 k_1 + \sigma_2 k_2 = 0 \Rightarrow k_1 = 2.414 \quad \& \quad k_2 = -0.414$$

$$i(t) = 2.414 e^{-0.586 t} - 0.414 e^{-3.41 t} \quad \text{A} \quad \begin{cases} \sigma_1 = 0.586 \\ \sigma_2 = 3.41 \end{cases}$$

7.92 The switch in the circuit in Fig. P7.92 has been closed for a long time and is opened at $t = 0$. Find $i(t)$ for $t > 0$.

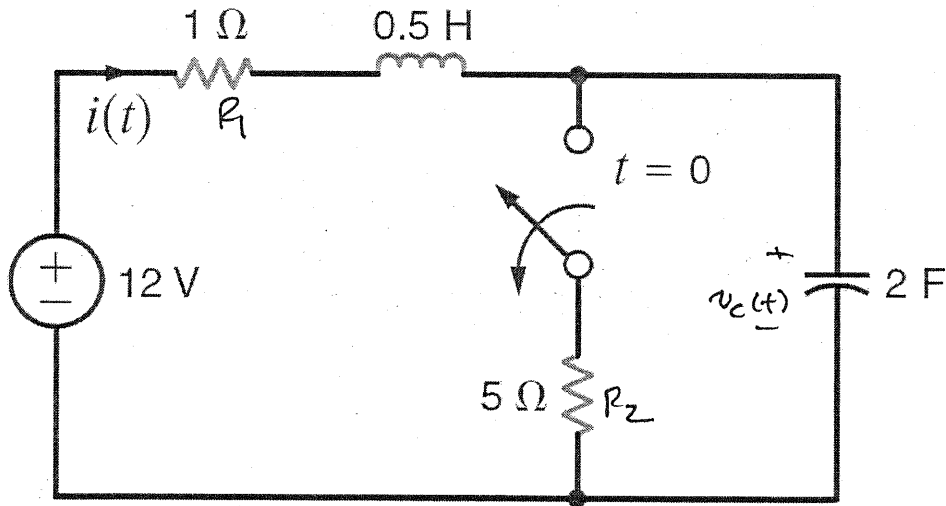


Figure P7.92

SOLUTION: $t=0^-$: $i(0^-) = \frac{12}{R_1 + R_2} = 2\text{A}$ $v_C(0^-) = \frac{12 R_2}{R_1 + R_2} = 10\text{V}$

$t=0^+$: $12 = L \frac{di}{dt} + R_1 i + \frac{1}{C} \int i dt \Rightarrow s^2 + \frac{R_1}{L} s + \frac{1}{LC} = 0$

$s_{1,2} = -1 \pm j$ $i(t) = B_1 e^{-t} + B_2 t e^{-t}$

$i(0^+) = 2\text{A} = B_1$ $12 = L \left. \frac{di}{dt} \right|_{t=0} + R_1 i(0^+) + v_C(0^+)$

$12 = -L B_1 + L B_2 + R_1 B_1 + 10 \Rightarrow B_2 = 2$

$$i(t) = 2e^{-t} + 2te^{-t}$$

7.93 The switch in the circuit in Fig. P7.93 has been closed for a long time and is opened at $t = 0$. Find $i(t)$ for $t > 0$.

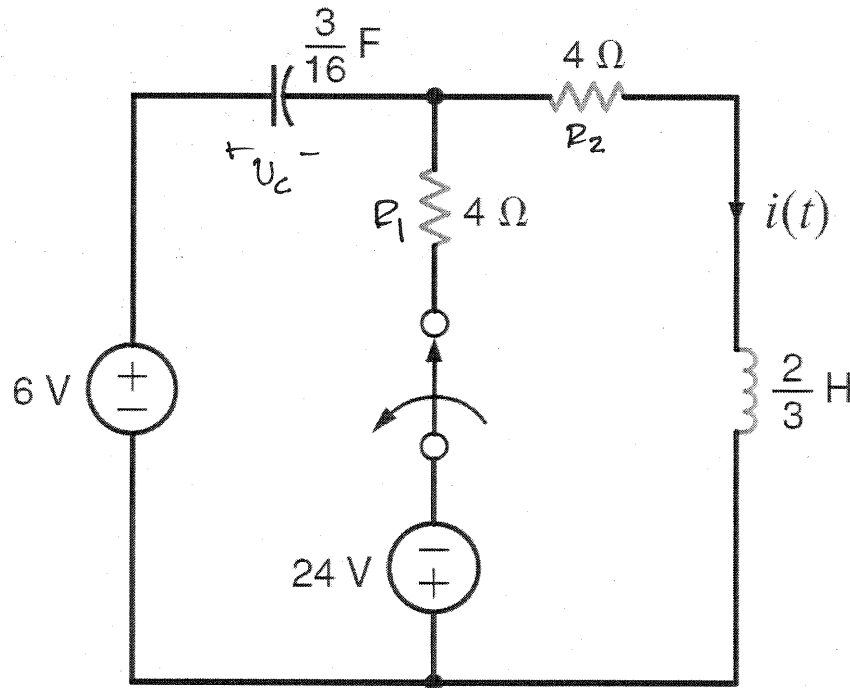


Figure P7.93

SOLUTION: $t=0^-$: $i(0^-) = \frac{-24}{R_1 + R_2} = -3\text{A}$ $v_C(0^-) = 6 - i(0^-)R_2 = 18\text{V}$

$t=0^+$ $s^2 + \frac{R_2}{L}s + \frac{1}{LC} = 0 = s^2 + 6s + 8$ $s_{1,2} = \begin{cases} -2 \\ -4 \end{cases}$

$i(t) = K_1 e^{-2t} + K_2 e^{-4t}$ $i(0^+) = -3 = K_1 + K_2$

$v_L(0^+) = 6 - R_2 i(0^+) - L \frac{di}{dt} \Big|_{t=0^+} = 6 + 12 + 2LK_1 + 4LK_2 = 18$

yields, $K_1 = -6$ & $K_2 = 3 \Rightarrow$ $i(t) = -6e^{-2t} + 3e^{-4t} \text{ A}$

7.94 The switch in the circuit in Fig. P7.94 has been closed for a long time and is opened at $t = 0$. Find $i(t)$ for $t > 0$.

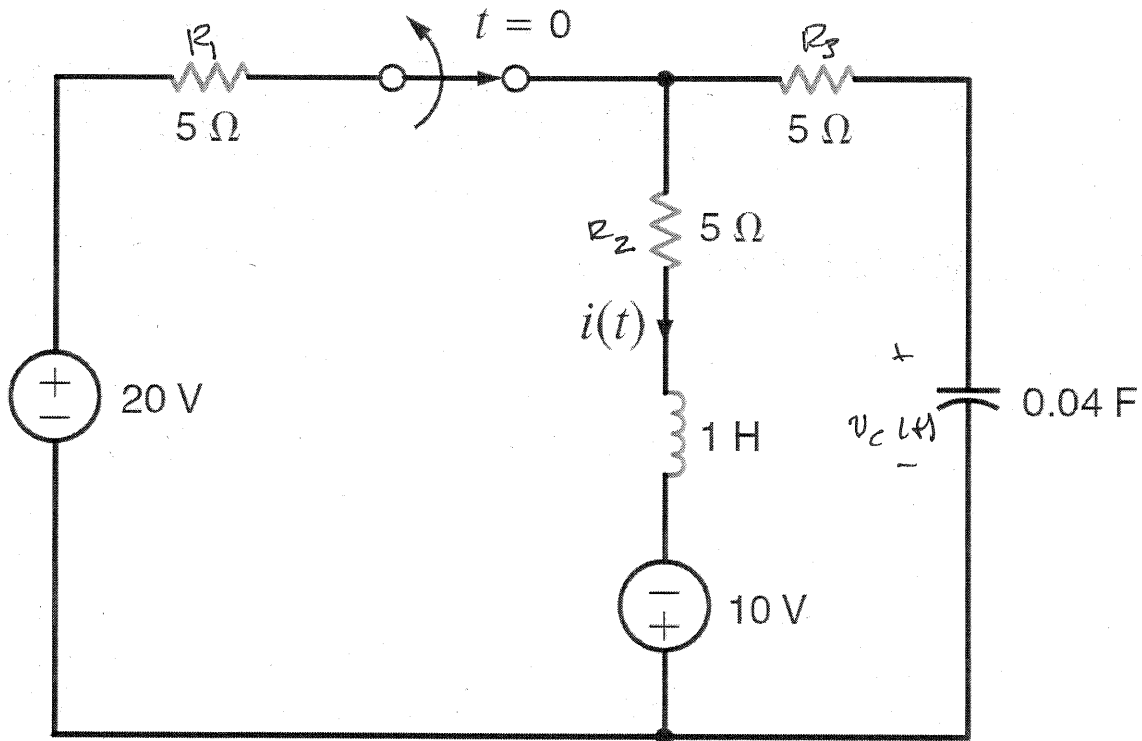


Figure P7.94

SOLUTION: $t=0^-$: $i(0^-) = \frac{20}{R_1 + R_2} = 3\text{ A}$ $v_c(0^-) = 20 - R_1 i(0^-) = 5\text{ V}$

$t > 0$: $10 = L \frac{di}{dt} + R i(t) + \frac{1}{C} \int i dt$ $R = R_2 + R_3 = 10\ \Omega$ $v_c = -\frac{1}{C} \int i dt$

$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0 = s^2 + 10s + 25 \Rightarrow s_{1,2} = -5 \pm 5j$

$i(t) = B_1 e^{-5t} + B_2 t e^{-5t}$ $i(0^+) = 3 = B_1$

$-v_c(0^+) = -5 = 10 - R i(0^+) - L \frac{di}{dt} \Big|_{t=0^+} = 10 - 30 + L(5)B_1 - L B_2 \Rightarrow B_2 = 0$

$i(t) = 3e^{-5t}\text{ A}$

7.95 The switch in the circuit in Fig. P7.95 has been closed for a long time and is opened at $t = 0$. Find $i(t)$ for $t > 0$.

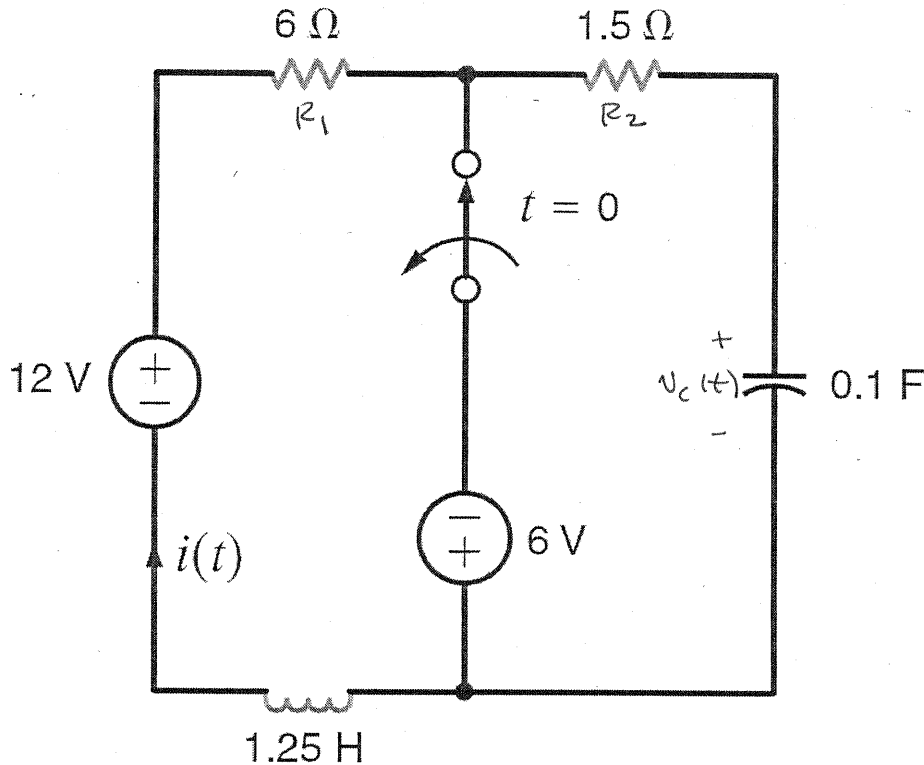


Figure P7.95

SOLUTION: $t = 0^-$: $i(0^-) = 18/R_1 = 3\text{A}$ $v_c(0^-) = -6\text{V} = v_c(0^+)$

$t > 0$: $12 = Ri + \frac{1}{C} \int i dt + L \frac{di}{dt}$ $R = R_1 + R_2 = 7.5\Omega$

$$s^2 + \left(\frac{R}{L}\right)s + \frac{1}{LC} = s^2 + 6s + 8 \Rightarrow \sigma_1 = -2 \quad \sigma_2 = -4$$

$$i(t) = K_1 e^{-2t} + K_2 e^{-4t} \quad \& \quad i(0^+) = 3 = K_1 + K_2$$

$$\text{at } t = 0^+ : 12 = R(K_1 + K_2) + \frac{1}{C} \left[-\frac{K_1}{2} - \frac{K_2}{4} \right] + K + L[-2K_1 - 4K_2] \Rightarrow K = 12$$

$$\text{and } v_c(0^+) = \frac{1}{C} \left[-\frac{K_1}{2} - \frac{K_2}{4} \right] + K = -6 \Rightarrow +5K_1 + 2.5K_2 = 18$$

yields $K_1 = 4.2$ & $K_2 = -1.2$

$$i(t) = 4.2 e^{-2t} - 1.2 e^{-4t} \text{ A}$$

- 7.96 Using the PSpice *Schematics* editor, draw the circuit in Fig. P7.96, and use the PROBE utility to plot $v_C(t)$ and determine the time constants for $0 < t < 1$ ms and 1 ms $< t < \infty$. Also, find the maximum voltage on the capacitor.


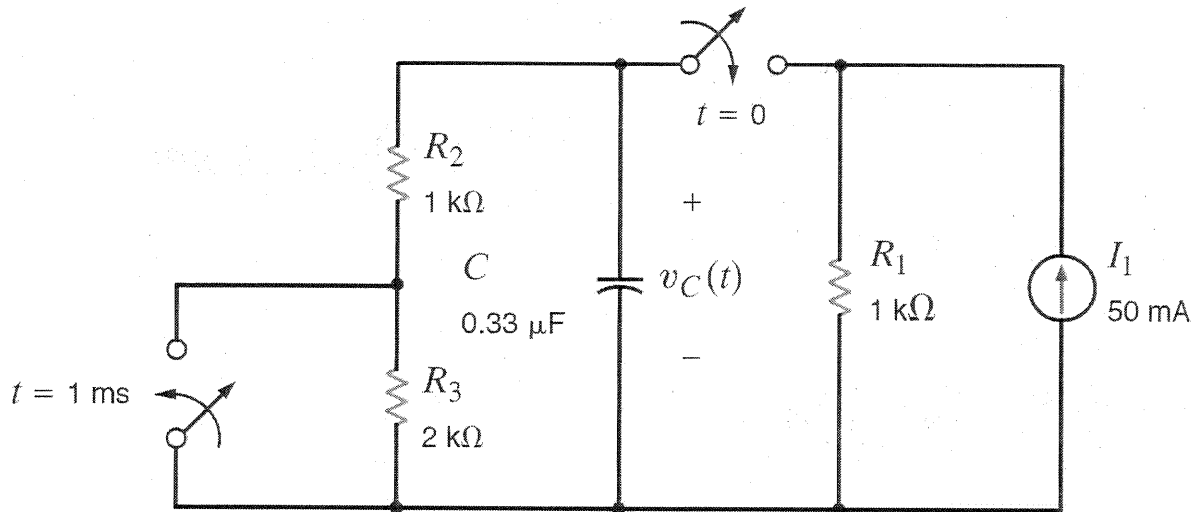


Figure P7.96

SOLUTION:

PROBLEM 7.96 PSPICE RESULTS

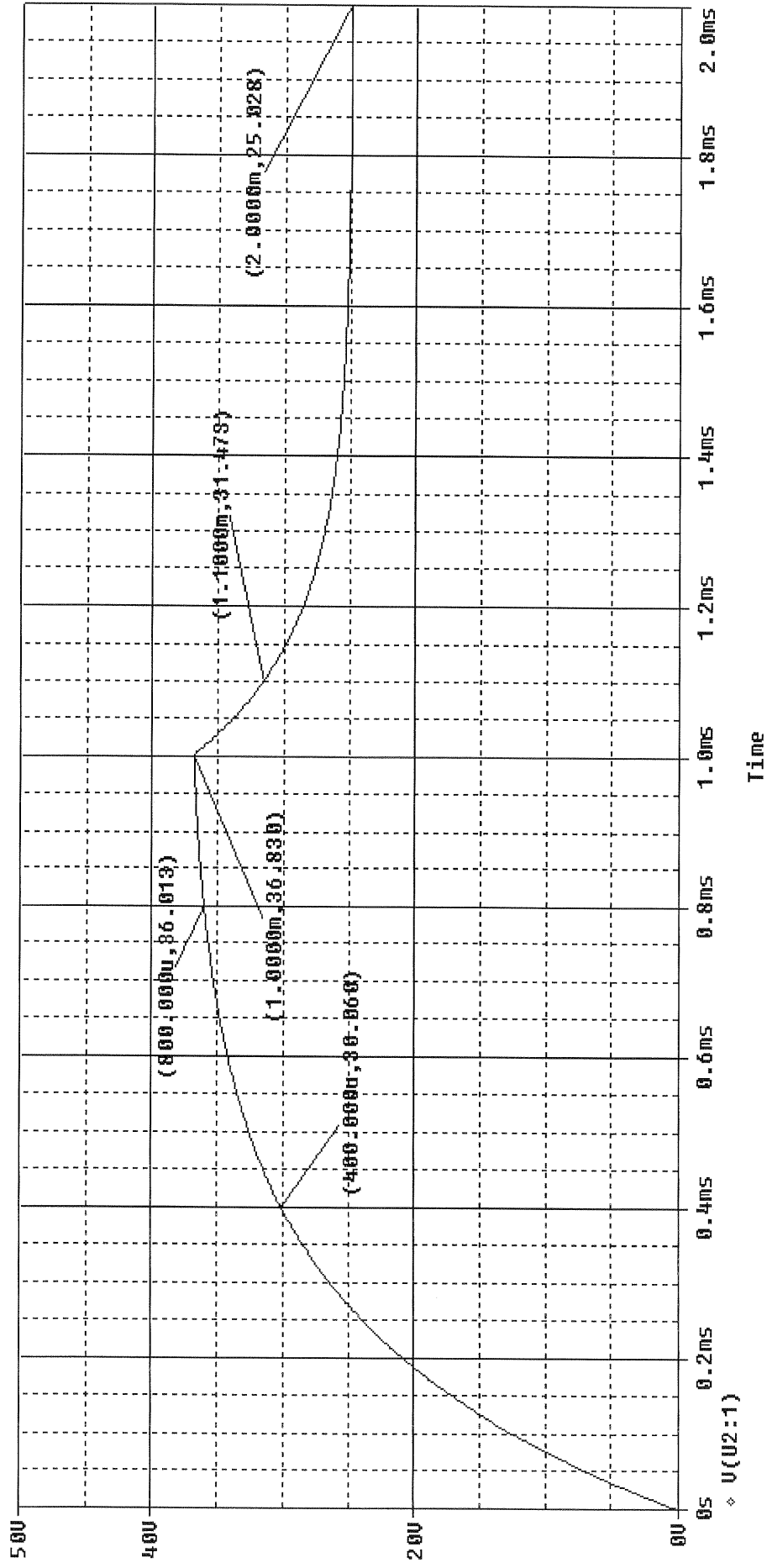

7.96 for $0 \leq t \leq 1 \text{ms}$ $v_c(t) = K_1 + K_2 e^{-t/\tau_1}$

$v_c(0) = 0 = K_1 + K_2 \Rightarrow K_2 = -K_1$

$v_c(t_1) = 30.6 = K_1 + K_2 e^{-t_1/\tau_1}$ ($t_1 = 0.4 \text{ms}$)

$v_c(t_2) = 36.03 = K_1 + K_2 e^{-t_2/\tau_1}$ ($t_2 = 0.8 \text{ms}$)

$$\frac{36.03}{30.60} = \frac{1 - e^{-t_2/\tau_1}}{1 - e^{-t_1/\tau_1}} = 1.177$$

$$1.177 e^{-t_1/\tau_1} - e^{-t_2/\tau_1} = 0.177 = K$$

iterate!

$\tau_1 (\text{ms})$	K
0.1	0.141
0.3	0.982
0.25	0.177 ✓

$$\tau_1 = 0.25 \text{ms}$$

for $t > 1 \text{ms}$, $v_c(t) = K_3 + K_4 e^{-(t-10^{-3})/\tau_2}$

$v_c(10^{-3}) = K_3 + K_4 = 36.83$ $v_c(\infty) = 25 = K_3 \Rightarrow K_4 = 11.83$

$v_c(t_3) = K_3 + K_4 e^{-(t_3-10^{-3})/\tau_2} = 31.48$ ($t_3 = 1.1 \text{ms}$)

yields $\tau_3 = 0.166 \text{ms}$

$v_c \text{ max occurs at } t = 1 \text{ms}$

$$v_{c \text{ max}} = 36.83 \text{V}$$

7.97 Using the PSPICE *Schematics* editor, draw the circuit in Fig. P7.97, and use the PROBE utility to find the maximum values of $v_L(t)$, $i_C(t)$, and $i(t)$.

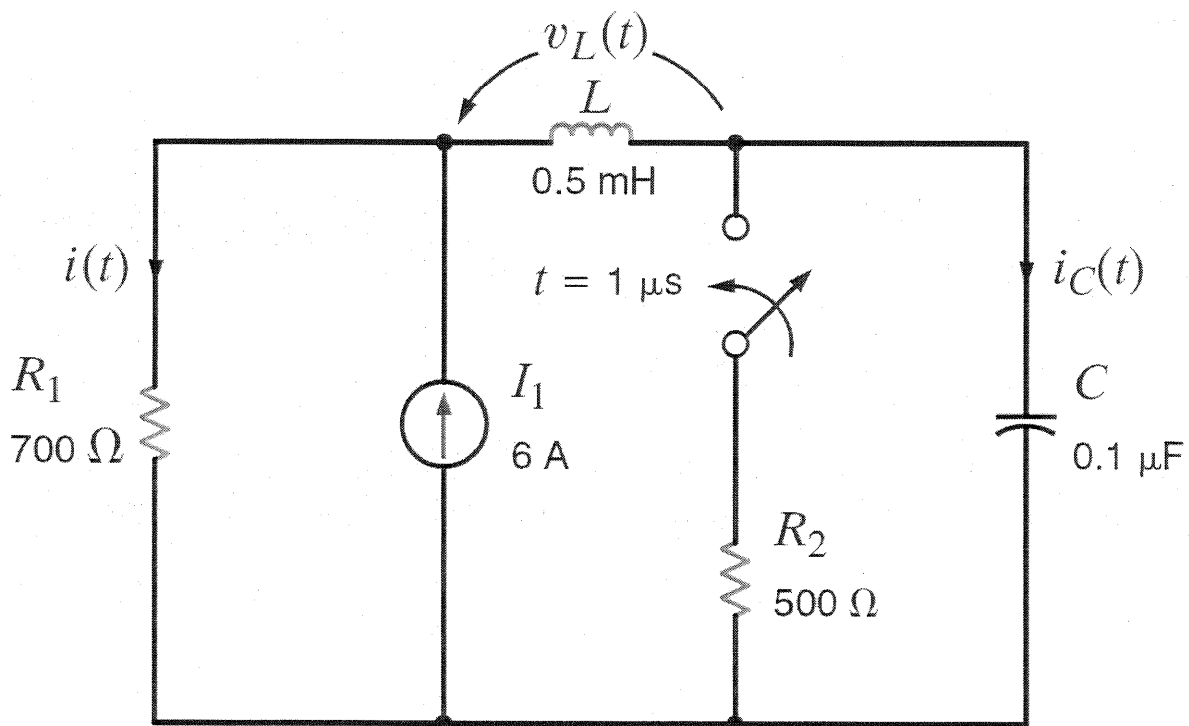



Figure P7.97

SOLUTION:

From the PSPICE simulation results,

$$v_{L \max} = 55.1 \text{ V} \quad i_{C \max} = -8.31 \text{ A} \quad (\text{actually the greatest deviation from } 0!) \\ i_{\max} = 6.00 \text{ A}$$


PROBLEM 7.97 PSPICE RESULTS

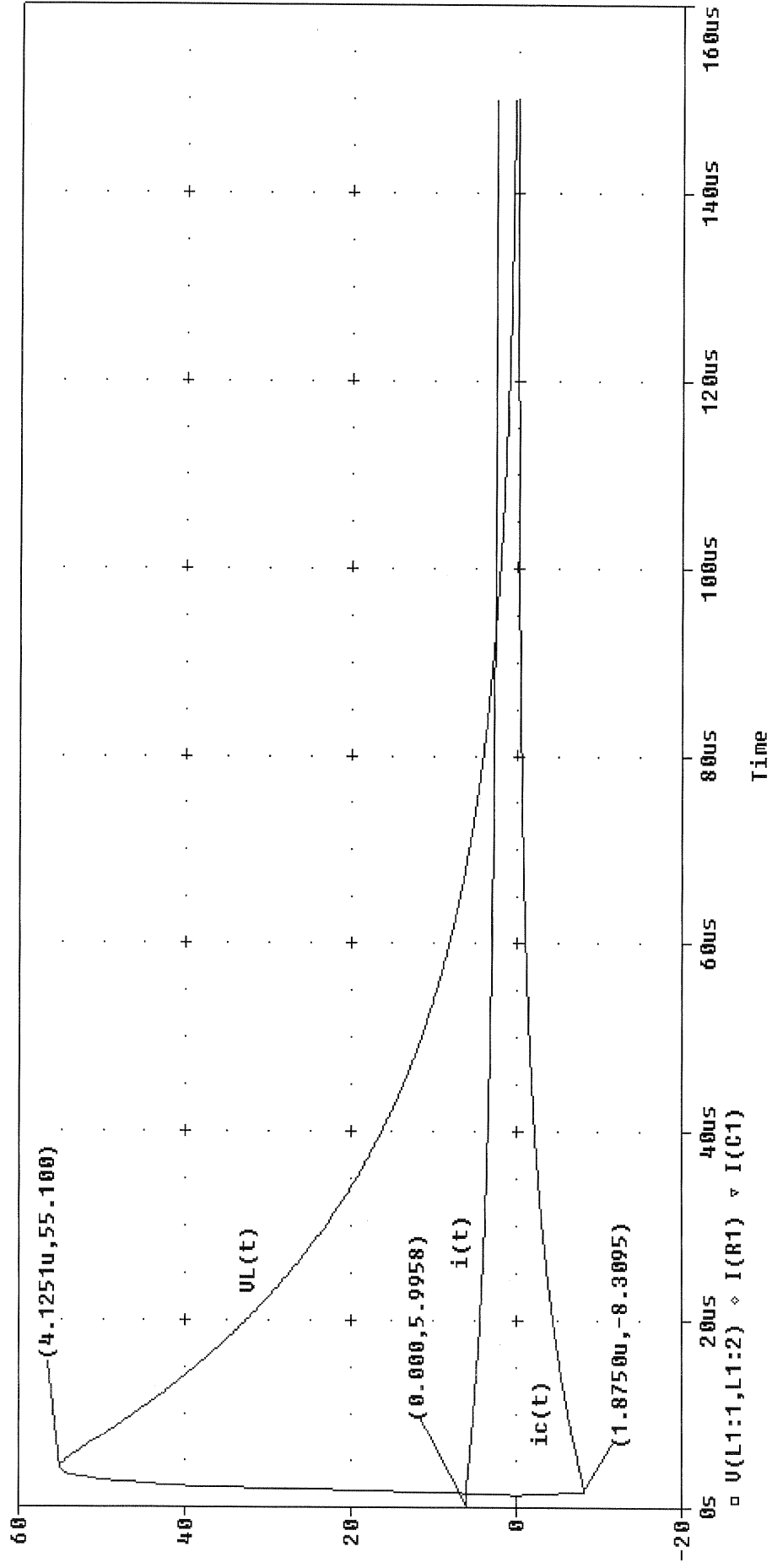

7.98 Design a parallel RLC circuit with $R \geq 1 \text{ k}\Omega$ that has the characteristic equation

$$s^2 + 4 \times 10^7 s + 4 \times 10^{14} = 0$$

SOLUTION:

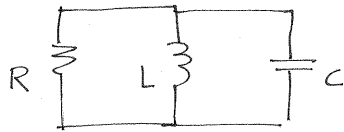

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

$$RC = 2.5 \times 10^{-8} \quad LC = 2.5 \times 10^{-15}$$

$$\frac{L}{R} = \frac{LC}{RC} = 10^{-7}$$


Arbitrarily select

$$L = 1 \mu\text{H} \rightarrow R = 10 \Omega, C = 2.5 \text{ nF}$$

7.99 Design a parallel RLC circuit with $R \geq 1 \text{ k}\Omega$ that has the characteristic equation

$$s^2 + 4 \times 10^7 s + 3 \times 10^{14} = 0$$

SOLUTION:

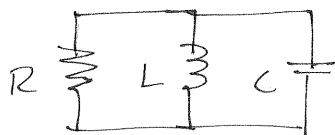

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

$$RC = 0.25 \times 10^{-7} \quad LC = 0.33 \times 10^{-14}$$

Arbitrarily choose

$$L = 10 \mu\text{H} \rightarrow R = 75 \Omega \text{ \& } C = 0.33 \text{ nF}$$

7.100 The curve shown in Fig. P7.100 is used to model the pressure in a vessel located in a chemical plant. We wish to design a circuit to realize this function so that we can study various parameters in the vessel, such as volume.


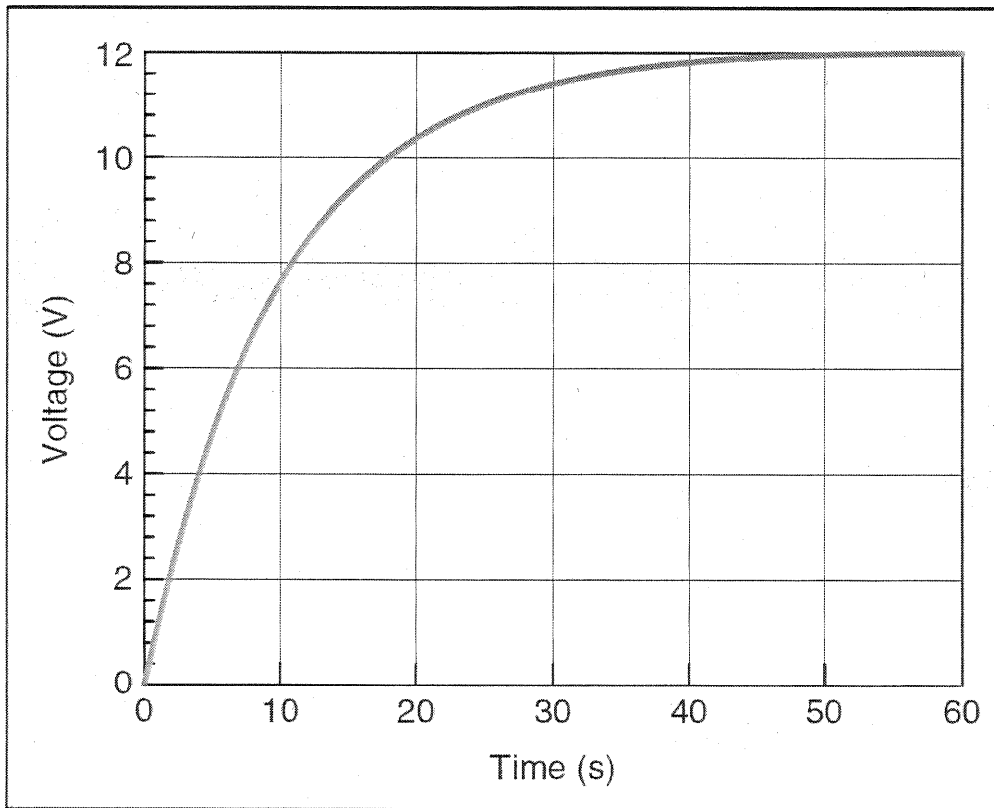


Figure P7.100

SOLUTION:

$$v(t) = k_1 + k_2 e^{-t/\tau} \quad v(0) = k_1 + k_2 = 0 \quad v(\infty) = 12 = k_1$$
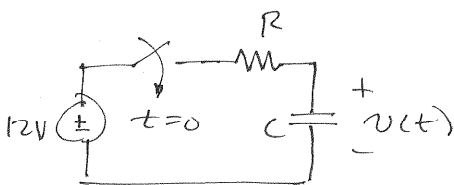
$$t_1 = 10 \text{ s} \quad v(t_1) = 7.6 \text{ V} = 12 (1 - e^{-t_1/\tau}) \Rightarrow \tau = 10 \text{ s}$$




$$RC = \tau = 10$$

select $C = 100 \mu\text{F} \rightarrow R = 100 \text{ k}\Omega$

7.101 Let us redesign the pulse generator in Example 7.14 such that a voltage with the following characteristics is created across a $10\text{-k}\Omega$ resistor: a peak value of 250 V , a cycle time of $10,000$ pulses/second, and a T_1 value of one-half the cycle time.

SOLUTION:

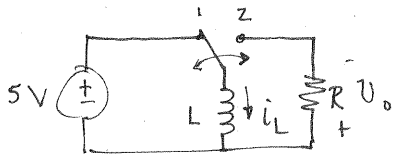

$$\text{frequency} = 10\text{ kHz}$$

$$\text{period} = \frac{1}{f} = 0.1\text{ ms}$$

$$T_1 = \frac{\text{period}}{2} = 50\mu\text{s}$$

$$i_{L\text{max}} = \frac{5}{L} T_1$$

$$v_{o\text{max}} = i_{L\text{max}} R = \frac{5}{L} (50 \times 10^{-6}) (10^4) = 250$$

$$\boxed{L = 10\text{ mH}}$$

Check repeatability: $\tau = \frac{L}{R} = 1\mu\text{s}$

$5\tau < T_1$? yes!!

7FE-1 In the circuit in Fig. 7PFE-1, the switch, which has been closed for a long time, opens at $t = 0$. Find the value of the capacitor voltage $v_C(t)$ at $t = 2$ s. **CS**


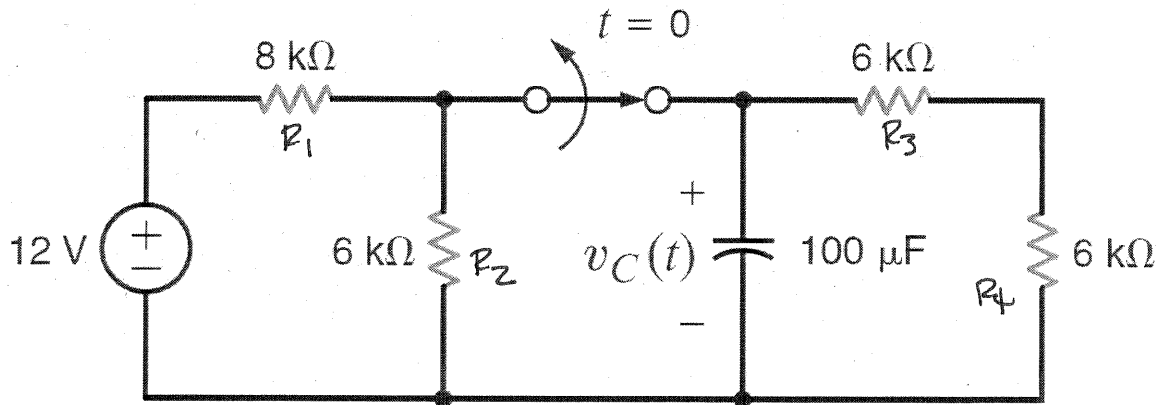


Figure 7PFE-1

SOLUTION:

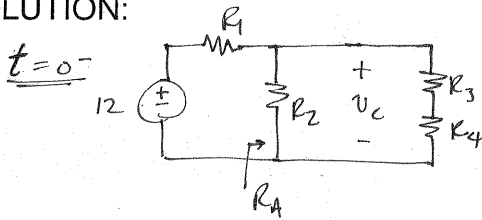

$$R_A = R_2 \parallel (R_3 + R_4) = 4 \text{ k}\Omega$$

$$v_C(0^-) = \frac{12 R_A}{R_A + R_1} = 4 \text{ V}$$

$$t = 0^+ : K_1 + K_2 = v_C(0^-) = 4$$

$$t = \infty \quad K_1 = 0$$

$$\tau = C R_{eq} \quad R_{eq} = R_3 + R_4 = 12 \text{ k}\Omega \quad \tau = 1.2 \text{ s}$$

$$v_C(t) = 4 e^{-t/1.2} \text{ V}$$

$$v_C(2) = 0.756 \text{ V}$$

7FE-2 In the network in Fig. 7PFE-2, the switch closes at $t = 0$. Find $v_o(t)$ at $t = 1$ s.

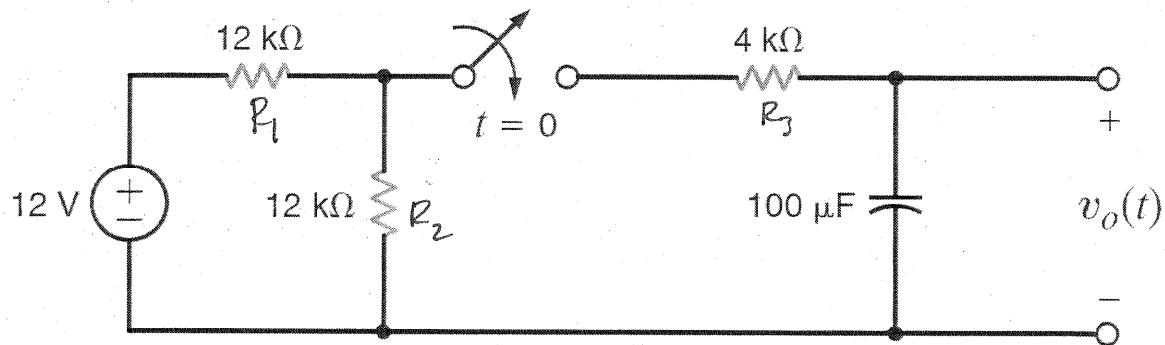


Figure 7PFE-2

SOLUTION: $v_o(t) = K_1 + K_2 e^{-t/\tau}$

$$\underline{t=0^-}: v_c(0^-) = 0 = v_o(0^-) \quad \underline{t=0^+}: v_c(0^+) = 0 = v_o(0^+) = K_1 + K_2$$

$$\underline{t \rightarrow \infty}: v_o(\infty) = \frac{12 R_2}{R_1 + R_2} = 6V = K_1$$

$$\tau = C R_{eq} \quad R_{eq} = R_3 + (R_1 // R_2) = 10k\Omega \quad \tau = 1s$$

$$v_o(t) = 6(1 - e^{-t})$$

$$v_o(1) = 3.79V$$

7FE-3 Assume that the switch in the network in Fig. 7PFE-3 has been closed for some time. At $t = 0$ the switch opens. Determine the time required for the capacitor voltage to decay to one-half of its initially charged value. **CS**

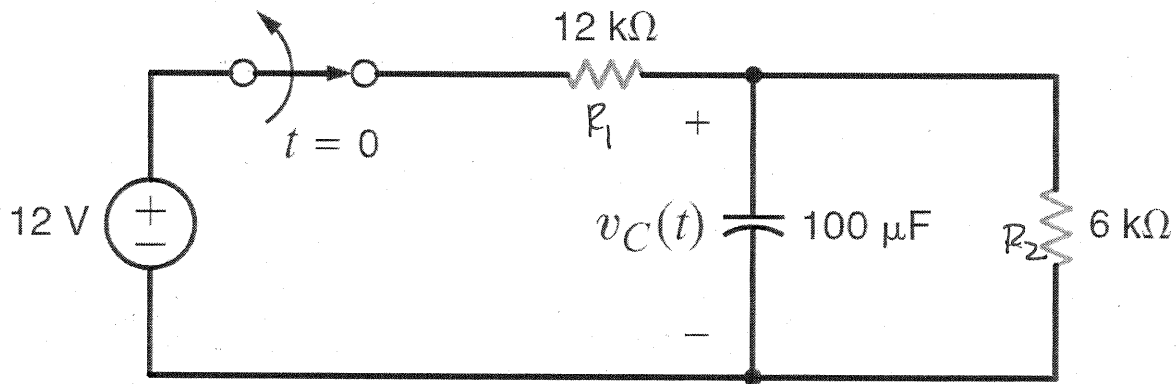


Figure 7PFE-3

SOLUTION: $v_C(t) = k_1 + k_2 e^{-t/\tau}$

$$\underline{t=0^-}: v_C(0^-) = \frac{12 R_2}{R_1 + R_2} = 4V = v_C(0^+)$$

$$\underline{t=0^+}: v_C(0^+) = 4 = k_1 + k_2 \quad \underline{t \rightarrow \infty}: v_C(\infty) = 0 = k_1$$

$$\tau = C R_{eq} \Rightarrow R_{eq} = R_2 \quad \tau = 0.6s$$

$$v_C(t) = 4 e^{-t/0.6} \text{ V} \quad v_C(t_1) = 2 = 4 e^{-t_1/0.6}$$

$$t_1 = 0.416 \text{ s}$$