

14.39 Determine the initial and final values of the voltage $v_o(t)$ in the network in Fig. P14.39.


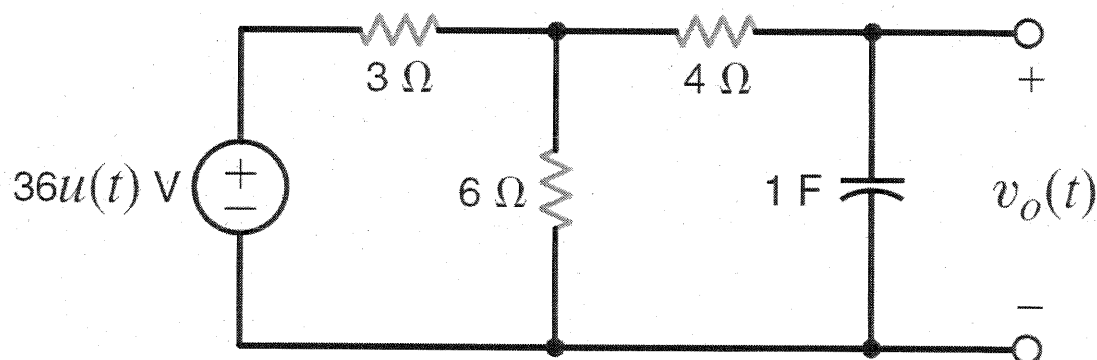



Figure P14.39

SOLUTION: Use Thevenin's

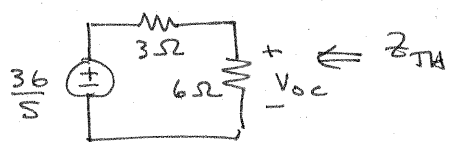

$$V_{OC} = \frac{6}{9} \left(\frac{36}{s} \right) = \frac{24}{s} \text{ V}$$

$$Z_{TH} = 3(6)/9 = 2\Omega$$

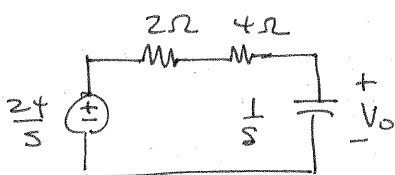

$$V_O = \frac{24}{s} \left[\frac{1/s}{6 + 1/s} \right] = \frac{24}{s(6s + 1)}$$

$$\lim_{t \rightarrow 0} v_o(t) = \lim_{s \rightarrow \infty} s V_O(s) = \frac{24}{6(\infty)} = 0$$

$$v_o(0) \rightarrow 0 \text{ V}$$

$$\lim_{t \rightarrow \infty} v_o(t) = \lim_{s \rightarrow 0} s V_O(s) = \frac{24}{1} = 24 \text{ V}$$

$$v_o(\infty) \rightarrow 24 \text{ V}$$