

14.9 Find $v_o(t)$, $t > 0$, in the network shown in Fig. P14.9 using nodal analysis. **CS**


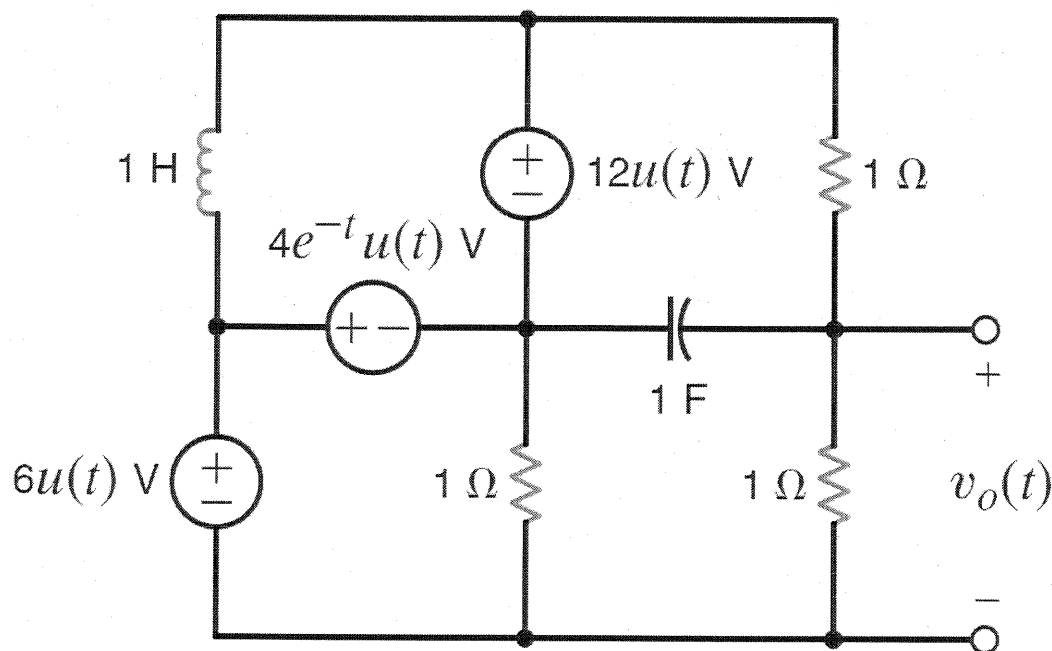


Figure P14.9

SOLUTION:

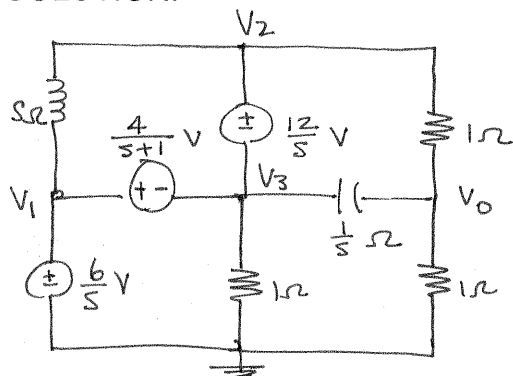

$$V_1 = \frac{6}{s} \quad V_1 - V_3 = \frac{4}{s+1} \Rightarrow V_3 = \frac{6}{s} - \frac{4}{s+1}$$

$$V_2 - V_3 = \frac{12}{s} \Rightarrow V_2 = \frac{12}{s} + V_3 = \frac{18}{s} - \frac{4}{s+1}$$

$$\frac{V_0 - V_2}{1} + s(V_0 - V_3) + \frac{V_0}{1} = 0$$

$$V_0(s+2) = V_2 + sV_3$$

$$V_0(s+2) = \frac{2(s+9)}{s} \Rightarrow V_0(s) = \frac{2(s+9)}{s(s+2)} = \frac{k_1}{s} + \frac{k_2}{s+2}$$

$$k_1 = 9 \quad k_2 = -7$$

$$v_o(t) = [9 - 7e^{-2t}]u(t)$$