
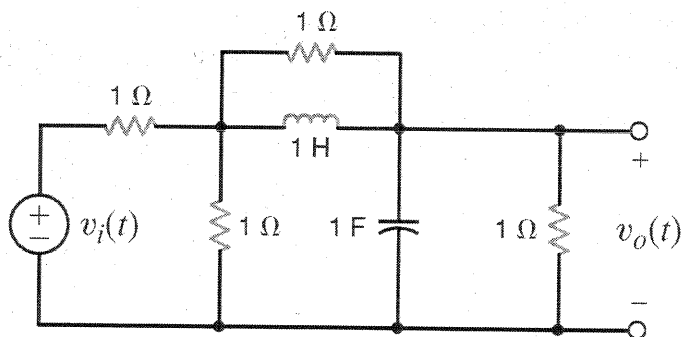


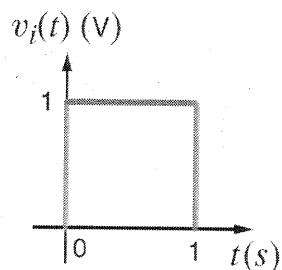- 14.43** Determine the output voltage, $v_o(t)$, in the circuit in Fig. P14.43a if the input is given by the source described in Fig. P14.43b.



(a)




(b)

Figure P14.43

SOLUTION: $v_i(t) = u(t) - u(t-1) \Rightarrow V_I(s) = \frac{1}{s}(1 - e^{-s})$ V


Use Thevenins twice!

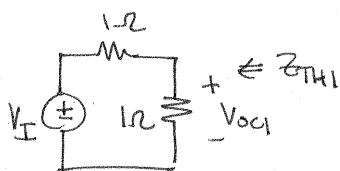

$$V_{OC1} = \frac{V_I}{2}$$


$$Z_{TH1} = \frac{1}{2} \Omega$$

\Rightarrow

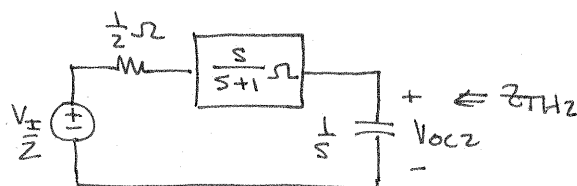

$$V_{OC2} = \frac{V_I}{2} \left[\frac{1/s}{\frac{1}{2} + \frac{s}{s+1} + \frac{1}{s}} \right] = \frac{V_I(s+1)}{3s^2 + 3s + 2}$$
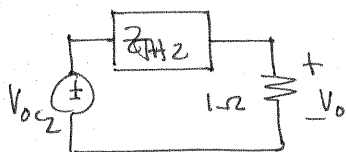
$$Z_{TH2} = \frac{\frac{1}{s} \left(\frac{1}{2} + \frac{s}{s+1} \right)}{\frac{1}{2} + \frac{1}{s} + \frac{s}{s+1}}$$



$$V_O = V_{OC2} \left(\frac{1}{1 + Z_{TH2}} \right)$$

$$Z_{TH2} = \frac{3s+1}{3s^2+3s+2}$$

$$V_0 = \frac{(\frac{1}{3})}{s(s+1)} (1-e^{-s}) = \left(\frac{1}{3} - \frac{1/3}{s+1}\right) (1-e^{-s})$$

$$v_0(t) = \frac{1}{3} [1-e^{-t}] u(t) - \frac{1}{3} [1-e^{-(t-1)}] u(t-1) \quad \checkmark$$