

14.34 Find $v_o(t)$, for $t > 0$, in the network in Fig. P14.34.


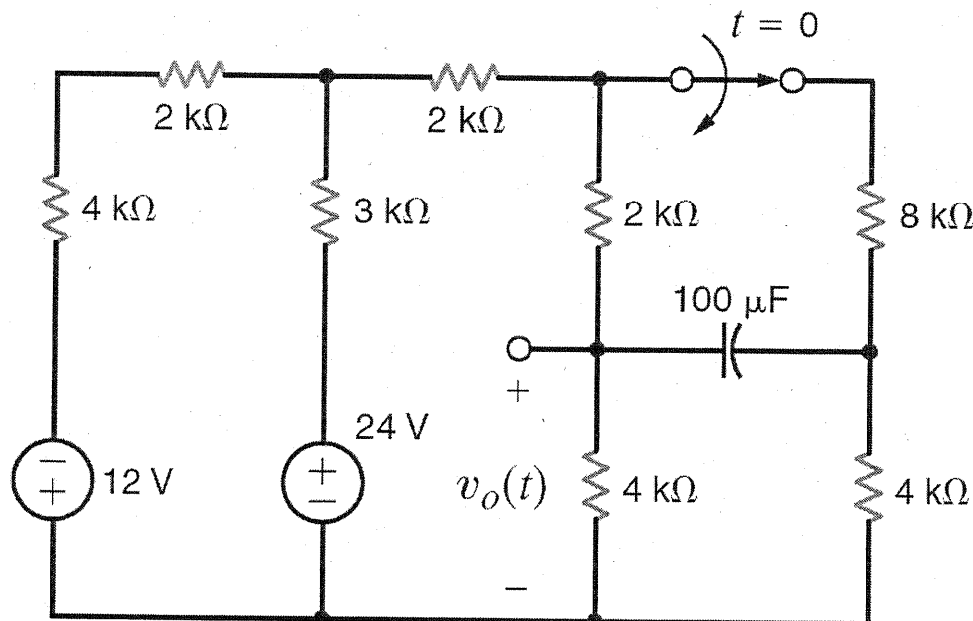
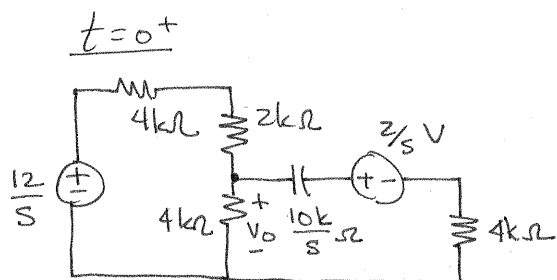


Figure P14.34

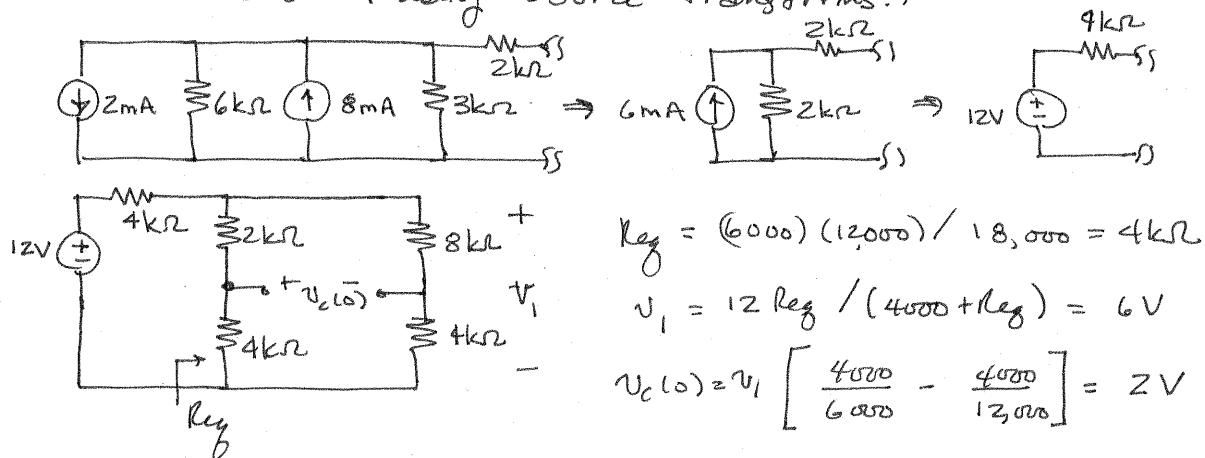SOLUTION: $t=0^-$ (using source transforms!)



$$\frac{V_o - 12/s}{6000} + \frac{V_o}{4000} + \frac{V_o - 2/s}{4000 + \frac{10,000}{s}} = 0$$

$$\frac{V_o}{6} + \frac{V_o}{4} + \frac{V_o s}{4s + 10} = \frac{2}{s} + \frac{2}{4s + 10}$$

$$V_o \left[\frac{5}{12} + \frac{5}{4s+10} \right] = \frac{10s+20}{s(4s+10)} = V_o \left[\frac{32s+50}{12(4s+10)} \right]$$

$$V_o = \frac{\frac{15}{4}(s+2)}{s(s+\frac{25}{16})} = \frac{24/5}{s} - \frac{21/20}{s+\frac{25}{16}}$$

$$V_o(t) = \left[\frac{24}{5} - \frac{21}{20} e^{-(25/16)t} \right] u(t) \text{ V}$$