

14.12 For the network shown in Fig. P14.12, find $v_o(t)$, $t > 0$, using mesh equations.


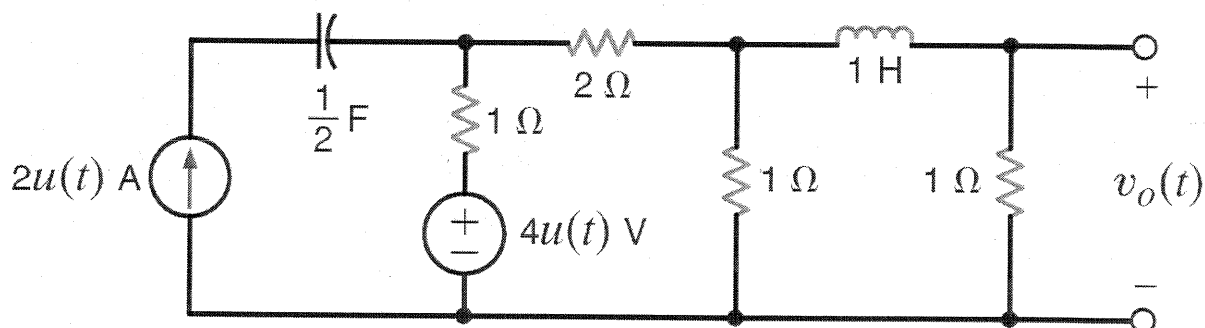


Figure P14.12

SOLUTION:

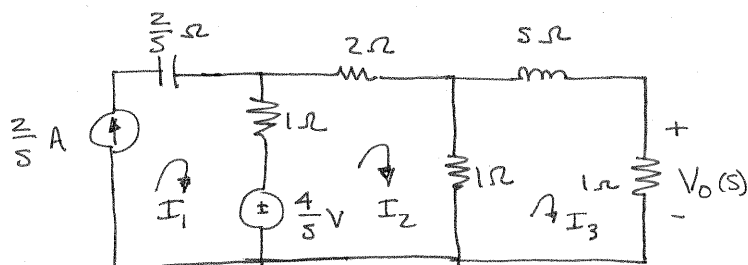

$$I_1 = \frac{2}{s} \text{ A}$$

$$\frac{4}{s} = -I_1 + I_2(4) - I_3$$

$$0 = -I_2 + I_3(s+2)$$

$$\frac{4}{s} = -\frac{2}{s} + 4I_2 - I_3 \Rightarrow \frac{6}{s} = 4I_2 - I_3$$

and

$$0 = -I_2 + I_3(s+2)$$

$$\left. \begin{array}{l} \frac{6}{s} = 4I_2 - I_3 \\ 0 = -I_2 + I_3(s+2) \end{array} \right\} I_3(s) [4(s+2) - 1] = 6/s$$

$$I_3(s) = \frac{6}{s(4s+7)}$$

$$V_o = (1) I_3 = \frac{3/2}{s(s+7/4)}$$

$$V_o(s) = \frac{k_1}{s} + \frac{k_2}{s+7/4}$$

$$k_1 = \left(\frac{3}{2}\right)\left(\frac{4}{7}\right) = \frac{6}{7} \quad k_2 = \frac{3}{2}\left(-\frac{4}{7}\right) = -\frac{6}{7}$$

$$V_o(s) = \frac{6}{7} \left[\frac{1}{s} - \frac{1}{s+7/4} \right]$$

$$v_o(t) = \left[\frac{6}{7} (1 - e^{-1.75t}) \right] u(t)$$