

14.8 Find $v_o(t)$, $t > 0$, in the network in Fig. P14.8 using node equations.


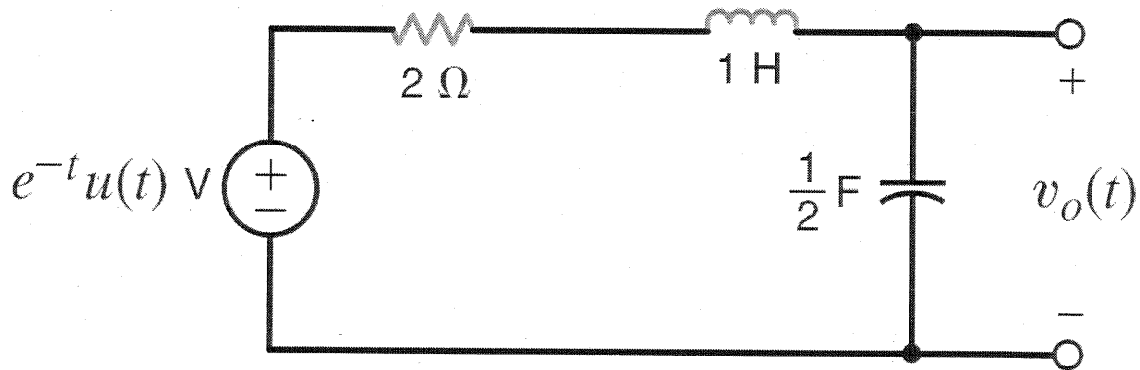


Figure P14.8

SOLUTION: $v_o(0^-) = 0$ V

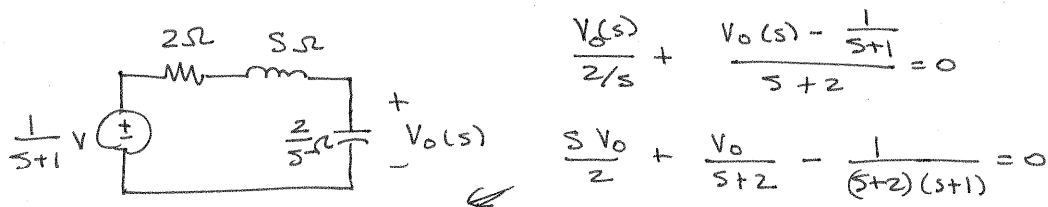

$$s(s+2)V_o + 2V_o = \frac{2}{s+1} = V_o [s^2 + 2s + 2]$$

$$V_o = \frac{2}{(s+1)(s^2+2s+2)} = \frac{K_1}{s+1} + \frac{K_2}{s+1-j1} + \frac{K_2^*}{s+1+j1}$$

$$K_1 = 2 \quad K_2 = \frac{2}{(j1)(j2)} = -1 \quad K_2^* = -1$$

$$V_o = \frac{2}{s+1} - \frac{1}{s+1-j1} - \frac{1}{s+1+j1}$$

$$v_o(t) = [2e^{-t} - 2e^{-t} \cos(t)] u(t)$$