

Microelectronic Circuit Design

Third Edition - Part I

Solutions to Exercises

CHAPTER 1

Page 11

$$V_{LSB} = \frac{5.12V}{2^{10} \text{ bits}} = \frac{5.12V}{1024 \text{ bits}} = 5.00 \text{ mV} \quad V_{MSB} = \frac{5.12V}{2} = 2.560V$$
$$1100010001_2 = 2^9 + 2^8 + 2^4 + 2^0 = 785_{10} \quad V_o = 786(5.00 \text{ mV}) = 3.925 \text{ V}$$

or $V_o = (2^{-1} + 2^{-2} + 2^{-6} + 2^{-10}) 5.12V = 3.912 \text{ V}$

Page 12

The dc component is $V_A = 4V$.

The signal consists of the remaining portion of v_A : $v_a = (5 \sin 2000\pi t + 3 \cos 1000 \pi t)$ Volts.

Page 19

$$i_{SC} = i_1 + \beta i_1 = \frac{v_s}{R_1} + \beta \frac{v_s}{R_1} = (\beta + 1) \frac{v_s}{R_1} \quad v_{OC} = \frac{(\beta + 1)R_S}{(\beta + 1)R_S + R_1} v_s$$
$$R_{th} = \frac{v_{OC}}{i_{SC}} = \frac{(\beta + 1)R_S}{(\beta + 1)R_S + R_1} \frac{R_1}{(\beta + 1)} = \frac{1}{\frac{(\beta + 1)}{R_1} + \frac{1}{R_S}} \rightarrow R_{th} = R_S \parallel \frac{R_1}{(\beta + 1)}$$

Page 23

$$v_o = -5 \cos(2000\pi t + 25^\circ) = -[-5 \sin(2000\pi t + 25^\circ - 90^\circ)] = 5 \sin(2000\pi t - 65^\circ)$$

$$V_o = 5 \angle -65^\circ \quad V_s = 0.001 \angle 0^\circ \quad A_v = \frac{5 \angle -65^\circ}{0.001 \angle 0^\circ} = 5000 \angle -65^\circ$$

Page 26

$$v_s = \left[0.5 \sin(2000\pi t) + \sin(4000\pi t) + 1.5 \sin(6000\pi t) \right]$$

The three spectral components are $f_1 = 1000 \text{ Hz}$ $f_2 = 2000 \text{ Hz}$ $f_3 = 3000 \text{ Hz}$

(a) The gain of the band - pass filter is zero at both f_1 and f_3 . At f_2 , $V_o = 10(1V) = 10V$, and $v_o = 10.0 \sin(4000\pi t)$ volts.

(b) The gain of the low - pass filter is zero at both f_2 and f_3 . At f_1 , $V_o = 6(0.5V) = 3V$, and $v_o = 3.00 \sin(2000\pi t)$ volts.

Page 27

$$39k\Omega(1 - 0.1) \leq R \leq 39k\Omega(1 + 0.1) \quad \text{or} \quad 35.1 \text{ k}\Omega \leq R \leq 42.9 \text{ k}\Omega$$

$$3.6k\Omega(1 - 0.01) \leq R \leq 3.6k\Omega(1 + 0.01) \quad \text{or} \quad 3.56 \text{ k}\Omega \leq R \leq 3.64 \text{ k}\Omega$$

Page 29

$$P = \frac{V_s^2}{R_1 + R_2} \quad P^{nom} = \frac{15^2}{54k\Omega} = 4.17 \text{ mW}$$

$$P^{max} = \frac{(1.1 \times 15)^2}{0.95 \times 54k\Omega} = 5.31 \text{ mW} \quad P^{min} = \frac{(0.9 \times 15)^2}{1.05 \times 54k\Omega} = 3.21 \text{ mW}$$

Page 33

$$R = 10k\Omega \left[1 + \frac{10^{-3}}{^{\circ}C} (-55 - 25)^{\circ}C \right] = 9.20 \text{ k}\Omega \quad R = 10k\Omega \left[1 + \frac{10^{-3}}{^{\circ}C} (85 - 25)^{\circ}C \right] = 10.6 \text{ k}\Omega$$

CHAPTER 2

Page 47

$$n_i = \sqrt{(2.31 \times 10^{30} \text{ K}^{-3} \text{ cm}^{-6})(300 \text{ K})^3 \exp\left[\frac{-0.66 \text{ eV}}{(8.62 \times 10^{-5} \text{ eV/K})(300 \text{ K})}\right]} = 2.27 \times 10^{13} / \text{cm}^3$$

$$n_i = \sqrt{(1.08 \times 10^{31} \text{ K}^{-3} \text{ cm}^{-6})(50 \text{ K})^3 \exp\left[\frac{-1.12 \text{ eV}}{(8.62 \times 10^{-5} \text{ eV/K})(50 \text{ K})}\right]} = 4.34 \times 10^{-39} / \text{cm}^3$$

$$n_i = \sqrt{(1.08 \times 10^{31} \text{ K}^{-3} \text{ cm}^{-6})(325 \text{ K})^3 \exp\left[\frac{-1.12 \text{ eV}}{(8.62 \times 10^{-5} \text{ eV/K})(325 \text{ K})}\right]} = 4.01 \times 10^{10} / \text{cm}^3$$

$$L^3 = \frac{\text{cm}^3}{4.34 \times 10^{-39}} \left(10^{-2} \frac{\text{m}}{\text{cm}}\right)^3 \rightarrow L = 6.13 \times 10^{10} \text{ m}$$

Page 48

$$v_p = \mu_p E = 500 \frac{\text{cm}^2}{\text{V-s}} \left(10 \frac{\text{V}}{\text{cm}}\right) = 5.00 \times 10^3 \frac{\text{cm}}{\text{s}} \quad v_n = -\mu_n E = 1350 \frac{\text{cm}^2}{\text{V-s}} \left(1000 \frac{\text{V}}{\text{cm}}\right) = 1.35 \times 10^6 \frac{\text{cm}}{\text{s}}$$

$$E = \frac{V}{L} = \frac{1}{2 \times 10^{-4} \text{ cm}} \frac{\text{V}}{\text{cm}} = 5.00 \times 10^3 \frac{\text{V}}{\text{cm}}$$

Page 48

$$\mu_n = \frac{v_n}{E} = \frac{4.3 \times 10^5 \text{ cm/s}}{100 \text{ V/cm}} = 4300 \frac{\text{cm}^2}{\text{s}} \quad \mu_p = \frac{v_p}{E} = \frac{2.1 \times 10^5 \text{ cm/s}}{100 \text{ V/cm}} = 2100 \frac{\text{cm}^2}{\text{s}}$$

$$\mu_n = \frac{v_n}{E} = \frac{8.5 \times 10^5 \text{ cm/s}}{100 \text{ V/cm}} = 8500 \frac{\text{cm}^2}{\text{s}}$$

Page 50

$$n_i^2 = 1.08 \times 10^{31} (400)^3 \exp\left[\frac{-1.12}{8.62 \times 10^{-5} (400)}\right] = 5.40 \times 10^{24} / \text{cm}^6$$

$$\rho = \frac{1}{\sigma} = \frac{1}{1.60 \times 10^{-19} \left[(2.32 \times 10^{12})(1350) + (2.32 \times 10^{12})(500) \right]} = 1450 \, \Omega - \text{cm}$$

$$n_i^2 = 1.08 \times 10^{31} (50)^3 \exp\left[\frac{-1.12}{8.62 \times 10^{-5} (50)}\right] = 1.88 \times 10^{-77} / \text{cm}^6$$

$$\rho = \frac{1}{\sigma} = \frac{1}{1.60 \times 10^{-19} \left[(4.34 \times 10^{-39})(6500) + (4.34 \times 10^{-39})(2000) \right]} = 1.69 \times 10^{53} \, \Omega - \text{cm}$$

Page 54

$$n_i^2 = 1.08 \times 10^{31} (400)^3 \exp\left[\frac{-1.12}{8.62 \times 10^{-5} (400)}\right] = 5.40 \times 10^{24} / \text{cm}^6$$

$$p = N_A - N_D = 10^{16} - 2 \times 10^{15} = 8 \times 10^{15} \frac{\text{holes}}{\text{cm}^3} \quad n = \frac{n_i^2}{p} = \frac{5.40 \times 10^{24}}{8 \times 10^{15}} = 6.75 \times 10^8 \frac{\text{electrons}}{\text{cm}^3}$$

$$n = N_D = 2 \times 10^{16} \frac{\text{electrons}}{\text{cm}^3} \quad n = \frac{n_i^2}{p} = \frac{10^{20}}{2 \times 10^{16}} = 5.00 \times 10^3 \frac{\text{holes}}{\text{cm}^3} \quad n > p \rightarrow n\text{-type silicon}$$

Page 55

Reading from the graph for $N_T = 10^{16} / \text{cm}^3$, $1250 \text{ cm}^2 / \text{V-s}$ and $400 \text{ cm}^2 / \text{V-s}$.

Reading from the graph for $N_T = 10^{17} / \text{cm}^3$, $800 \text{ cm}^2 / \text{V-s}$ and $230 \text{ cm}^2 / \text{V-s}$.

Page 57

$$\sigma = 1000 = 1.60 \times 10^{-19} \mu_n n \rightarrow u_n n = 6.25 \times 10^{21} / \text{cm}^3 = (6.25 \times 10^{19})(100)$$

$$(a) N_T = 2 \times 10^{16} / \text{cm}^3 \quad (b) N_T = 5 \times 10^{16} / \text{cm}^3$$

Page 58

$$p = N_A - N_D = 4 \times 10^{18} \frac{\text{holes}}{\text{cm}^3} \quad n = \frac{n_i^2}{p} = \frac{10^{20}}{4 \times 10^{18}} = 25 \frac{\text{electrons}}{\text{cm}^3}$$

$$N_T = \frac{4 \times 10^{18}}{\text{cm}^3} \text{ and mobilities from Fig. 2.8}$$

$$p = N_A - N_D = 7 \times 10^{19} \frac{\text{holes}}{\text{cm}^3} \quad n = \frac{n_i^2}{p} = \frac{10^{20}}{7 \times 10^{19}} = 1.4 \frac{\text{electrons}}{\text{cm}^3}$$

$$N_T = \frac{7 \times 10^{19}}{\text{cm}^3} \text{ and mobilities from Fig. 2.8}$$

$$\rho = \frac{1}{\sigma} = \frac{1}{1.60 \times 10^{-19} [(1.4)(100) + (7 \times 10^{19})(50)]} = 1.79 \text{ m}\Omega - \text{cm}$$

Page 59

$$V_T = \frac{kT}{q} = \frac{1.38 \times 10^{-23}(50)}{1.602 \times 10^{-19}} = 4.31 \text{ mV}$$

$$V_T = \frac{1.38 \times 10^{-23}(300)}{1.602 \times 10^{-19}} = 25.8 \text{ mV}$$

$$V_T = \frac{1.38 \times 10^{-23}(400)}{1.602 \times 10^{-19}} = 34.5 \text{ mV}$$

Page 59

$$D_n = \frac{kT}{q} \mu_n = 25.8 \text{ mV} \left(1362 \frac{\text{cm}^2}{\text{V-s}} \right) = 35.1 \frac{\text{cm}^2}{\text{s}} \quad D_p = \frac{kT}{q} \mu_p = 25.8 \text{ mV} \left(492 \frac{\text{cm}^2}{\text{V-s}} \right) = 12.7 \frac{\text{cm}^2}{\text{s}}$$

$$j_n = qD_n \frac{dn}{dx} = 1.60 \times 10^{-19} \text{ C} \left(20 \frac{\text{cm}^2}{\text{s}} \right) \left(\frac{10^{16}}{\text{cm}^3 - \mu\text{m}} \right) \left(\frac{10^4 \mu\text{m}}{\text{cm}} \right) = 320 \frac{\text{A}}{\text{cm}^2}$$

$$j_p = -qD_p \frac{dp}{dx} = -1.60 \times 10^{-19} \text{ C} \left(4 \frac{\text{cm}^2}{\text{s}} \right) \left(\frac{10^{16}}{\text{cm}^3 - \mu\text{m}} \right) \left(\frac{10^4 \mu\text{m}}{\text{cm}} \right) = -64 \frac{\text{A}}{\text{cm}^2}$$

CHAPTER 3

Page 79

$$E_{\max} = \frac{1}{\epsilon_s} \int_{-x_p}^0 -qN_A dx = \frac{qN_A x_p}{\epsilon_s} \quad E_{\max} = -\frac{1}{\epsilon_s} \int_0^{x_n} qN_D dx = \frac{qN_D x_n}{\epsilon_s} \quad \text{For the values in Ex.3.2:}$$

$$E_{\max} = \frac{1.6x10^{-19} C(10^{17} / cm^3)(1.13x10^{-5} cm)}{11.7(8.854x10^{-14} F / cm)} = 175 \frac{kV}{cm}$$

$$E_{\max} = \frac{1.6x10^{-19} C(10^{20} / cm^3)(1.13x10^{-8} cm)}{11.7(8.854x10^{-14} F / cm)} = 175 \frac{kV}{cm}$$

$$E_{\max} = \frac{2(1.05V)}{2.63x10^{-6} cm} = 799 \frac{kV}{cm}$$

$$x_p = 0.0258 \mu m \left(1 + \frac{2x10^{18}}{10^{20}}\right)^{-1} = 0.0253 \mu m \quad x_n = 0.0258 \mu m \left(1 + \frac{10^{20}}{2x10^{18}}\right)^{-1} = 5.06x10^{-4} \mu m$$

Page 82

$$T = \frac{1.602x10^{-19}(25.8mV)}{1.03(1.38x10^{-23})} = 291K$$

Page 84

$$i_D = 5x10^{-15} A \left[\exp\left(\frac{-0.04}{0.025}\right) - 1 \right] = -3.99 fA \quad i_D = 5x10^{-15} A \left[\exp\left(\frac{-2.0}{0.025}\right) - 1 \right] = -5.00 fA$$

Page 86

$$V_{BE} = V_T \ln\left(1 + \frac{I_D}{I_S}\right) = 0.025V \ln\left(1 + \frac{40x10^{-6} A}{2x10^{-15} A}\right) = 0.593 V$$

$$V_{BE} = V_T \ln\left(1 + \frac{I_D}{I_S}\right) = 0.025V \ln\left(1 + \frac{400x10^{-6} A}{2x10^{-15} A}\right) = 0.651 V \quad \Delta V_{BE} = 57.6 mV$$

$$V_{BE} = V_T \ln\left(1 + \frac{I_D}{I_S}\right) = 0.0258V \ln\left(1 + \frac{40x10^{-6} A}{2x10^{-15} A}\right) = 0.612 V$$

$$V_{BE} = V_T \ln\left(1 + \frac{I_D}{I_S}\right) = 0.0258V \ln\left(1 + \frac{400x10^{-6} A}{2x10^{-15} A}\right) = 0.671 V \quad \Delta V_{BE} = 59.4 mV$$

Page 89

$$w_d = 0.113 \mu m \sqrt{1 + \frac{10V}{0.979V}} = 0.378 \mu m \quad E_{\max} = \frac{2(10.979V)}{0.378x10^{-4} cm} = 581 \frac{kV}{cm}$$

Page 89

$$I_S = 10 \text{ fA} \sqrt{1 + \frac{10V}{0.8V}} = 36.7 \text{ fA}$$

Page 92

$$C_{j0} = \frac{11.7(8.854 \times 10^{-14} \text{ F/cm})}{0.113 \times 10^{-4} \text{ cm}} = 91.7 \frac{\text{nF}}{\text{cm}^2} \quad C_j(0V) = 91.7 \frac{\text{nF}}{\text{cm}^2} (10^{-2} \text{ cm})(1.25 \times 10^{-2} \text{ cm}) = 11.5 \text{ pF}$$

$$C_j(5V) = \frac{11.5 \text{ pF}}{\sqrt{1 + \frac{5V}{0.979V}}} = 4.64 \text{ pF}$$

Page 92

$$C_D = \frac{10^{-5} \text{ A}}{0.025V} 10^{-8} \text{ s} = 4.00 \text{ pF} \quad C_D = \frac{8 \times 10^{-4} \text{ A}}{0.025V} 10^{-8} \text{ s} = 320 \text{ pF} \quad C_D = \frac{5 \times 10^{-2} \text{ A}}{0.025V} 10^{-8} \text{ s} = 0.02 \text{ } \mu\text{F}$$

Page 97

Two points on the load line: $V_D = 0, I_D = \frac{5V}{5k\Omega} = 1 \text{ mA}; I_D = 0, V_D = 5V$

Page 108

From the answer, the diodes are on, on, off.

$$I_1 = I_{D1} + I_{D2} \quad \frac{10V - V_B}{2.5k\Omega} = \frac{V_B - 0.6V - (-20V)}{10k\Omega} + \frac{V_B - 0.6V - (-10V)}{10k\Omega} = 0 \rightarrow V_B = 1.87 \text{ V}$$

$$I_{D1} = \frac{1.87 - 0.6 - (-20V)}{10k\Omega} = 2.13 \text{ mA} \quad I_{D2} = \frac{1.87 - 0.6 - (-10V)}{10k\Omega} = 1.13 \text{ mA}$$

$$V_{D3} = -(1.87 - 0.6) = -1.27 \text{ V}$$

Page 110

$$R_{\min} = \frac{5k\Omega}{\frac{20}{5} - 1} = 1.67 \text{ k}\Omega \quad V_O = 20V \frac{1k\Omega}{5k\Omega + 1k\Omega} = 3.33 \text{ V} \text{ (} V_Z \text{ is off)} \quad V_O = 5 \text{ V} \text{ (} V_Z \text{ is conducting)}$$

Page 111

$$\frac{V_L - 20V}{1k\Omega} + \frac{V_L - 5V}{0.1k\Omega} + \frac{V_L}{5k\Omega} = 0 \rightarrow V_L = 6.25 \text{ V} \quad I_Z = \frac{6.25V - 5V}{0.1k\Omega} = 12.5 \text{ mA}$$

$$P_Z = 5V(12.5 \text{ mA}) + 100\Omega(12.5 \text{ mA})^2 = 78.1 \text{ mW}$$

Page 112

$$\text{Line Regulation} = \frac{0.1k\Omega}{0.1k\Omega + 5k\Omega} = 19.6 \frac{\text{mV}}{\text{V}} \quad \text{Load Regulation} = 0.1k\Omega \parallel 5k\Omega = 98.0 \text{ } \Omega$$

Page 117

$$V_{dc} = V_P - V_{on} = 6.3\sqrt{2} - 1 = 7.91 \text{ V} \quad I_{dc} = \frac{7.91V}{0.5\Omega} = 15.8 \text{ A} \quad V_r = \frac{I_{dc}}{C} T = \frac{15.8 \text{ A}}{0.5F} \frac{1}{60} \text{ s} = 0.527 \text{ V}$$

$$\Delta T = \frac{1}{\omega} \sqrt{2 \frac{V_r}{V_P}} = \frac{1}{2\pi(60)} \sqrt{2 \left(\frac{0.527V}{8.91V} \right)} = 0.912 \text{ ms} \quad \theta_c = 120\pi(0.912 \text{ ms}) \frac{180^\circ}{\pi} = 19.7^\circ$$

Page 118

$$V_{dc} = V_P - V_{on} = 10\sqrt{2} - 1 = 13.1 \text{ V} \quad I_{dc} = \frac{13.1V}{2\Omega} = 6.57 \text{ A} \quad C = \frac{I_{dc}}{V_r} T = \frac{6.57 \text{ A}}{0.1F} \frac{1}{60} \text{ s} = 1.10 \text{ F}$$

$$\Delta T = \frac{1}{\omega} \sqrt{2 \frac{V_r}{V_P}} = \frac{1}{2\pi(60)} \sqrt{2 \left(\frac{0.1V}{14.1V} \right)} = 0.316 \text{ ms} \quad \theta_c = 120\pi(0.316 \text{ ms}) \frac{180^\circ}{\pi} = 6.82^\circ$$

Page 118

$$\text{For } V_T = 0.025V, \quad V_D = \frac{kT}{q} \ln \left(1 + \frac{I_D}{I_S} \right) = 0.025V \ln \left(1 + \frac{48.6A}{10^{-15}A} \right) = 0.961 \text{ V}$$

$$V_D = \frac{kT}{q} \ln \left(1 + \frac{I_D}{I_S} \right) = \frac{1.38 \times 10^{-23} \text{ J/K} (300 \text{ K})}{1.60 \times 10^{-19} \text{ C}} \ln \left(1 + \frac{48.6A}{10^{-15}A} \right) = 0.994 \text{ V}$$

$$V_D = \frac{kT}{q} \ln \left(1 + \frac{I_D}{I_S} \right) = \frac{1.38 \times 10^{-23} \text{ J/K} (273 \text{ K} + 50 \text{ K})}{1.60 \times 10^{-19} \text{ C}} \ln \left(1 + \frac{48.6A}{10^{-15}A} \right) = 1.07 \text{ V}$$

CHAPTER 4

Page 151

$$(i) K'_n = \mu_n \frac{\epsilon_{ox}}{T_{ox}} = 500 \frac{cm^2}{V-s} \frac{3.9(8.854 \times 10^{-14} F/cm)}{25 \times 10^{-7} cm} = 69.1 \times 10^{-6} \frac{C}{V^2-s} = 69.1 \frac{\mu A}{V^2}$$

$$(ii) K_n = K'_n \frac{W}{L} = 50 \frac{\mu A}{V^2} \left(\frac{20 \mu m}{1 \mu m} \right) = 1000 \frac{\mu A}{V^2} \quad K_n = 50 \frac{\mu A}{V^2} \left(\frac{60 \mu m}{3 \mu m} \right) = 1000 \frac{\mu A}{V^2}$$

$$K_n = 50 \frac{\mu A}{V^2} \left(\frac{10 \mu m}{0.25 \mu m} \right) = 2000 \frac{\mu A}{V^2}$$

(iii) For $V_{GS} = 0V$ and $1V$, $V_{GS} < V_{TN}$ and the transistor is off. Therefore $I_D = 0$.

$V_{GS} - V_{TN} = 2 - 1.5 = 0.5V$ and $V_{DS} = 0.1V \rightarrow$ Triode region operation

$$I_D = K'_n \frac{W}{L} \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} = 25 \frac{\mu A}{V^2} \left(\frac{10 \mu m}{1 \mu m} \right) \left(2 - 1.5 - \frac{0.1}{2} \right) 0.1V^2 = 11.3 \mu A$$

$V_{GS} - V_{TN} = 3 - 1.5 = 1.5V$ and $V_{DS} = 0.1V \rightarrow$ Triode region operation

$$I_D = K'_n \frac{W}{L} \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} = 25 \frac{\mu A}{V^2} \left(\frac{10 \mu m}{1 \mu m} \right) \left(3 - 1.5 - \frac{0.1}{2} \right) 0.1V^2 = 36.3 \mu A$$

$$K'_n = 25 \frac{\mu A}{V^2} \left(\frac{100 \mu m}{1 \mu m} \right) = 250 \frac{\mu A}{V^2}$$

Page 152

$$R_{on} = \frac{1}{K'_n \frac{W}{L} (V_{GS} - V_{TN})} = \frac{1}{250 \frac{\mu A}{V^2} (2 - 1)} = 4.00 k\Omega \quad R_{on} = \frac{1}{250 \frac{\mu A}{V^2} (4 - 1)} = 1.00 k\Omega$$

$$V_{GS} = V_{TN} + \frac{1}{K_n R_{on}} = 1V + \frac{1}{250 \frac{\mu A}{V^2} (2000\Omega)} = 3.00 V$$

Page 155

$V_{GS} - V_{TN} = 5 - 1 = 4 \text{ V}$ and $V_{DS} = 10 \text{ V} \rightarrow$ Saturation region operation

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 = \frac{1 \text{ mA}}{2 V^2} (5 - 1)^2 V^2 = 8.00 \text{ mA}$$

$$K_n = K'_n \frac{W}{L} \rightarrow \frac{W}{L} = \frac{1 \text{ mA}}{40 \mu\text{A}} = \frac{25}{1} \quad W = 25L = 8.75 \mu\text{m}$$

Assuming saturation region operation,

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 = \frac{1 \text{ mA}}{2 V^2} (2.5 - 1)^2 V^2 = 1.13 \text{ mA}$$

$$g_m = K_n (V_{GS} - V_{TN}) = 1 \frac{\text{mA}}{V^2} (2.5 - 1) V = 1.50 \text{ mS}$$

$$\text{Checking: } g_m = \frac{2(1.125 \text{ mA})}{(2.5 - 1) V} = 1.50 \text{ mS}$$

Page 156

(i) $V_{GS} - V_{TN} = 5 - 1 = 4 \text{ V}$ and $V_{DS} = 10 \text{ V} \rightarrow$ Saturation region operation

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) = \frac{1 \text{ mA}}{2 V^2} (5 - 1)^2 V^2 [1 + 0.02(10)] = 9.60 \text{ mA}$$

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) = \frac{1 \text{ mA}}{2 V^2} (5 - 1)^2 V^2 [1 + 0(10)] = 8.00 \text{ mA}$$

(ii) $V_{GS} - V_{TN} = 4 - 1 = 3 \text{ V}$ and $V_{DS} = 5 \text{ V} \rightarrow$ Saturation region operation

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) = \frac{25 \mu\text{A}}{2 V^2} (4 - 1)^2 V^2 [1 + 0.01(5)] = 118 \mu\text{A}$$

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) = \frac{25 \mu\text{A}}{2 V^2} (5 - 1)^2 V^2 [1 + 0.01(10)] = 220 \mu\text{A}$$

Page 157

(i) Assuming pinchoff region operation, $I_D = \frac{K_n}{2} (0 - V_{TN})^2 = \frac{50 \mu\text{A}}{2 V^2} (+2V)^2 = 100 \mu\text{A}$

$$V_{GS} = V_{TN} + \sqrt{\frac{2I_D}{K_n}} = 2V + \sqrt{\frac{2(100 \mu\text{A})}{50 \mu\text{A}/V^2}} = 4.00 \text{ V}$$

(ii) Assuming pinchoff region operation, $I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 = \frac{50 \mu\text{A}}{2 V^2} [1 - (-2V)]^2 = 225 \mu\text{A}$

Page 159

$$(i) V_{TN} = V_{TO} + \gamma(\sqrt{V_{SB} + 0.6V} - \sqrt{0.6V}) = 1 + 0.75(\sqrt{0 + 0.6} - \sqrt{0.6}) = 1 V$$

$$V_{TN} = 1 + 0.75(\sqrt{1.5 + 0.6} - \sqrt{0.6}) = 1.51 V \quad V_{TN} = 1 + 0.75(\sqrt{3 + 0.6} - \sqrt{0.6}) = 1.84 V$$

(ii - a) V_{GS} is less than the threshold voltage, so the transistor is cut off and $I_D = 0$.

(b) $V_{GS} - V_{TN} = 2 - 1 = 1 V$ and $V_{DS} = 0.5 V \rightarrow$ Triode region operation

$$I_D = K_n \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} = 1 \frac{mA}{V^2} \left(2 - 1 - \frac{0.5}{2} \right) 0.5 V^2 = 375 \mu A$$

(c) $V_{GS} - V_{TN} = 2 - 1 = 1 V$ and $V_{DS} = 2 V \rightarrow$ Saturation region operation

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) = 0.5 \frac{mA}{V^2} (2 - 1)^2 V^2 [1 + 0.02(2)] = 520 \mu A$$

Page 160

(a) V_{GS} is greater than the threshold voltage, so the transistor is cut off and $I_D = 0$.

(b) $|V_{GS} - V_{TN}| = |-2 + 1| = 1 V$ and $|V_{DS}| = 0.5 V \rightarrow$ Triode region operation

$$I_D = K_n \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} = 0.4 \frac{mA}{V^2} \left(-2 + 1 - \frac{-0.5}{2} \right) (-0.5) V^2 = 150 \mu A$$

(c) $|V_{GS} - V_{TN}| = |-2 + 1| = 1 V$ and $|V_{DS}| = 2 V \rightarrow$ Saturation region operation

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) = \frac{0.4}{2} \frac{mA}{V^2} (-2 + 1)^2 V^2 [1 + 0.02(2)] = 208 \mu A$$

Page 165

$$\text{Active area} = 120 \Lambda^2 = 120(0.5 \mu m)^2 = 30 \mu m^2 \quad L = 2 \Lambda = 1 \mu m \quad W = 10 \Lambda = 5 \mu m$$

$$\text{Gate area} = 20 \Lambda^2 = 20(0.5 \mu m)^2 = 5 \mu m^2 \quad N = \frac{(10^4 \mu m)^2}{(14 \Lambda)(16 \Lambda)(0.5 \mu m)^2} = 1.79 \times 10^6 \text{ transistors}$$

Page 167

$$C_{GC} = \left(200 \frac{\mu F}{m^2}\right) (5 \times 10^{-6} m) (0.5 \times 10^{-6} m) = 0.500 fF$$

$$\text{Triode region : } C_{GD} = C_{GS} = \frac{C_{GC}}{2} + C_{GSO}W = 0.25 fF + \left(300 \frac{pF}{m}\right) (5 \times 10^{-6} m) = 1.75 fF$$

$$\text{Saturation region : } C_{GS} = \frac{2}{3}C_{GC} + C_{GSO}W = 0.333 fF + \left(300 \frac{pF}{m}\right) (5 \times 10^{-6} m) = 1.83 fF$$

$$C_{GD} = C_{GSO}W = \left(300 \frac{pF}{m}\right) (5 \times 10^{-6} m) = 1.50 fF$$

Page 169

$$KP = K_n = 150U \quad LAMBDA = \lambda = 0.0133 \quad VTO = V_{TN} = 1 \quad PHI = 2\phi_F = 0.6$$

$$W = W = 1.5U \quad L = L = 0.25U$$

Page 173

(i) Assume saturation region operation and $\lambda = 0$. Then I_D is independent of V_{DS} , and $I_D = 50 \mu A$.

$$V_{DS} = V_{DD} - I_D R_D = 10 - 50 k\Omega (50 \mu A) = 7.50 V. \quad V_{DS} \geq V_{GS} - V_{TN}, \text{ so our assumption was correct.}$$

$$\text{Q-Point} = (50.0 \mu A, 7.50 V)$$

$$(ii) V_{EQ} = \frac{270 k\Omega}{270 k\Omega + 750 k\Omega} 10V = 2.647 V \quad R_{EQ} = 270 k\Omega \parallel 750 k\Omega \quad \text{Assume saturation region.}$$

$$I_D = \frac{25 \times 10^{-6} A}{2} \frac{1}{V^2} (2.647 - 1)^2 V^2 = 33.9 \mu A \quad V_{DS} = V_{DD} - I_D R_D = 10 - 100 k\Omega (33.9 \mu A) = 6.61 V.$$

$$V_{DS} \geq V_{GS} - V_{TN}, \text{ so our assumption was correct.} \quad \text{Q-Point} = (33.9 \mu A, 6.61 V)$$

$$(iii) V_{GS} \text{ does not change : } V_{GS} = 3.00 V. \quad I_D = \frac{30 \times 10^{-6} A}{2} \frac{1}{V^2} (3 - 1)^2 V^2 = 60.0 \mu A$$

$$V_{DS} = V_{DD} - I_D R_D = 10 - 100 k\Omega (60.0 \mu A) = 4.00 V. \quad V_{DS} \geq V_{GS} - V_{TN}, \text{ so our assumption was correct.}$$

$$\text{Q-Point} = (60.0 \mu A, 4.00 V)$$

$$(iv) V_{GS} \text{ does not change : } V_{GS} = 3.00 V. \quad I_D = \frac{25 \times 10^{-6} A}{2} \frac{1}{V^2} (3 - 1.5)^2 V^2 = 28.1 \mu A$$

$$V_{DS} = V_{DD} - I_D R_D = 10 - 100 k\Omega (28.1 \mu A) = 7.19 V. \quad V_{DS} \geq V_{GS} - V_{TN}, \text{ so our assumption was correct.}$$

$$\text{Q-Point} = (28.1 \mu A, 7.19 V)$$

Page 174

$$V_{DS} = 10 - \frac{25 \times 10^{-6} (10^5)}{2} (3-1)^2 (1 + 0.01 V_{DS}) \rightarrow V_{DS} = 10 - 5(1 + 0.01 V_{DS})$$

$$V_{DS} = \frac{10-5}{1.05} V = 4.76 V \quad I_D = \frac{25 \times 10^{-6}}{2} (3-1)^2 [1 + 0.01(4.76)] = 52.4 \mu A$$

Page 176

For $I_D = 0$, $V_{DS} = 10 V$. For $V_{DS} = 0$, $I_D = \frac{10V}{66.7k\Omega} = 150\mu A$.

The load line intersects the $V_{GS} = 3 - V$ curve at $I_D = 50 \mu A$, $V_{DS} = 6.7 V$.

Page 178

$$(i) 4 = V_{GS} + \frac{30 \times 10^{-6} (3.9 \times 10^4)}{2} (V_{GS} - 1)^2 \rightarrow V_{GS}^2 - 0.291 V_{GS} - 5.838 = 0 \rightarrow V_{GS} = 2.566V, -2.275V$$

$$I_D = \frac{30 \times 10^{-6}}{2} (2.566 - 1)^2 = 36.8 \mu A \quad V_{DS} = 10 - 114k\Omega(36.8\mu A) = 5.81 V$$

Q-Point : (36.8 μA , 5.81 V)

$$(ii) 4 = V_{GS} + \frac{25 \times 10^{-6} (3.9 \times 10^4)}{2} (V_{GS} - 1.5)^2 \rightarrow V_{GS}^2 - 0.949 V_{GS} - 5.955 = 0 \rightarrow V_{GS} = 2.960V, -2.012V$$

$$I_D = \frac{25 \times 10^{-6}}{2} (2.960 - 1.5)^2 = 26.7 \mu A \quad V_{DS} = 10 - 114k\Omega(26.7\mu A) = 6.96 V$$

Q-Point : (26.7 μA , 6.96 V)

$$(ii) 4 = V_{GS} + \frac{25 \times 10^{-6} (6.2 \times 10^4)}{2} (V_{GS} - 1)^2 \rightarrow V_{GS}^2 - 0.710 V_{GS} - 4.161 = 0 \rightarrow V_{GS} = 2.426V, -1.716V$$

$$I_D = \frac{25 \times 10^{-6}}{2} (2.426 - 1)^2 = 25.4 \mu A \quad V_{DS} = 10 - 137k\Omega(25.4\mu A) = 6.52 V$$

Q-Point : (25.4 μA , 6.52 V)

Page 180

(i) Assume saturation. For $I_D = 99.5\mu A$, $V_{GS} = 4V - 99.5\mu A(1.8k\Omega) = 3.821V$

$$I_D = \frac{25\mu A}{2}(3.821-1)^2 = 99.5\mu A \text{ which agrees. } V_{DS} = 10V - 99.5\mu A(40.8k\Omega) = 5.94V$$

Saturation region operation is correct.

(ii) $V_{EQ} = \frac{1.5M\Omega}{1.5M\Omega + 1M\Omega}10V = 6.00V$ $R_{EQ} = 1.5M\Omega \parallel 1M\Omega = 600k\Omega$ Assume saturation region.

$$6 = V_{GS} + \frac{25 \times 10^{-6} (22 \times 10^3)}{2} (V_{GS} - 1)^2 \rightarrow V_{GS}^2 + 1.636V_{GS} - 20.82 = 0 \rightarrow V_{GS} = 3.818V$$

$$I_D = \frac{25 \times 10^{-6}}{2} (3.818 - 1)^2 = 99.3 \mu A \quad V_{DS} = 10 - 40k\Omega(99.3\mu A) = 6.03V$$

Saturation region operation is correct. Q-Point : (99.3 μA , 6.03 V)

(iii) $R_1 + R_2 = \frac{10V}{2\mu A} = 5M\Omega$ $\frac{R_1}{R_1 + R_2}10V = 6V \rightarrow R_1 = 5M\Omega \frac{6V}{10V} = 3M\Omega \rightarrow R_2 = 2M\Omega$

$$R_{EQ} = 3M\Omega \parallel 2M\Omega = 1.2M\Omega$$

Page 182

$$V_{GS} = 6 - 22000I_D \quad V_{SB} = 22000I_D \quad V_{TN} = 1 + 0.75(\sqrt{V_{SB} + 0.6} - \sqrt{0.6}) \quad I_D = \frac{25\mu A}{2}(V_{GS} - V_{TN})^2$$

Spreadsheet iteration yields $I_D = 83.2 \mu A$.

Page 183

Equation 4.55 becomes $6 - [1 + 0.75(\sqrt{V_{SB} + 0.6} - \sqrt{0.6}) + 2.83] - V_{SB} = 0$.

$$V_{SB}^2 - 6.065V_{SB} + 7.231 = 0 \rightarrow V_{SB} = 1.63V.$$

$$R_S = \frac{1.63V}{10^{-4}A} = 16.3k\Omega \rightarrow 16k\Omega \quad R_D = \frac{(10 - 6 - 1.63)V}{10^{-4}A} = 23.7k\Omega \rightarrow 24k\Omega$$

Page 185

(i) Using Eq. (4.58) $V_{GS} = 3.3 - \frac{2 \times 10^{-4}(10k\Omega)}{2}(V_{GS} - 1)^2 \rightarrow V_{GS}^2 - V_{GS} - 2.3 = 0 \rightarrow V_{GS} = 2.097V$

$$V_{GS} = \frac{2 \times 10^{-4}}{2}(2.097 - 1)^2 = 120.3\mu A \quad V_{DS} = V_{GS} \quad Q\text{-Point : } (120 \mu A, 2.10V)$$

(ii) Since there was no voltage drop across R_G in (i), the equations and answers are identical to the first part.

Page 186

$$\frac{4 - V_{DS}}{1.8 \times 10^6} = 2.5 \times 10^{-4} \left(4 - 1 - \frac{V_{DS}}{2} \right) V_{DS} \rightarrow V_{DS} = 2.96 \text{ mV} \quad I_D = \frac{4 - V_{DS}}{1.8 \times 10^6} = 2.22 \text{ } \mu\text{A}$$

$$Q - \text{Point} : (2.22 \text{ } \mu\text{A}, 2.96 \text{ mV}) \quad \text{Checking; } I_D R_{on} = \frac{2.22 \mu\text{A}}{2.5 \times 10^{-4} (4 - 1)} = 2.96 \text{ mV}$$

Page 189

$$(i) 10 - 6 = \frac{25 \times 10^{-6} (62 \times 10^4)}{2} (V_{GS} + 1)^2 - V_{GS} \rightarrow V_{GS}^2 + 0.710 V_{GS} - 4.161 = 0 \rightarrow V_{GS} = -2.426 \text{ V}, +1.716 \text{ V}$$

$$I_D = \frac{25 \times 10^{-6}}{2} (-2.426 + 1)^2 = 25.4 \text{ } \mu\text{A} \quad V_{DS} = -[10 - 137 \text{ k}\Omega (25.4 \mu\text{A})] = -6.52 \text{ V}$$

$$Q - \text{Point} : (25.4 \text{ } \mu\text{A}, -6.52 \text{ V})$$

Page 192

$$(i) \text{ Circuits/cm}^2 \propto \alpha^2 = \left(\frac{1 \mu\text{m}}{0.25 \mu\text{m}} \right)^2 = 16$$

$$\text{Power - Delay Product} \propto \frac{1}{\alpha^3} = \frac{1}{4^3} = \frac{1}{64} \rightarrow 64 \text{ times improvement}$$

$$(ii) i_D^* = \mu_n \frac{\epsilon_{ox}}{T_{ox}} \frac{W}{\alpha} \frac{V_{GS} - V_{TN} - \frac{V_{DS}}{2}}{L/\alpha} V_{DS} = \alpha i_D \quad P^* = V_{DD} i_D^* = V_{DD} (\alpha i_D) = \alpha P$$

$$\frac{P^*}{A^*} = \frac{\alpha P}{(W/\alpha)(L/\alpha)} = \alpha^3 \frac{P}{A}$$

$$(iii) f_T = \frac{1}{2\pi} \frac{500 \text{ cm}^2 / \text{V} \cdot \text{s}}{(10^{-4} \text{ cm})^2} (1 \text{ V}) = 7.96 \text{ GHz} \quad f_T = \frac{1}{2\pi} \frac{500 \text{ cm}^2 / \text{V} \cdot \text{s}}{(0.25 \times 10^{-4} \text{ cm})^2} (1 \text{ V}) = 127 \text{ GHz}$$

Page 193

The field in the first sentence at the top of the page should be 10^5 V/cm .

$$\frac{V}{L} = 10^4 \frac{\text{V}}{\text{cm}} \rightarrow L = \left(10^5 \frac{\text{V}}{\text{cm}} \right) (10^{-4} \text{ cm}) = 10 \text{ V} \quad L = \left(10^5 \frac{\text{V}}{\text{cm}} \right) (10^{-5} \text{ cm}) = 1 \text{ V}$$

CHAPTER 5

Page 213

$$\beta_F = \frac{\alpha_F}{1 - \alpha_F} = \frac{0.970}{1 - 0.970} = 32.3 \quad \beta_F = \frac{0.993}{1 - 0.993} = 142 \quad \beta_F = \frac{0.250}{1 - .250} = 0.333$$
$$\alpha_F = \frac{\beta_F}{\beta_F + 1} = \frac{40}{41} = 0.976 \quad \alpha_F = \frac{200}{201} = 0.995 \quad \alpha_F = \frac{3}{4} = 0.750$$

Page 215

$$i_C = 10^{-15} A \left[\exp\left(\frac{0.700}{0.025}\right) - \exp\left(\frac{-9.30}{0.025}\right) \right] - \frac{10^{-15} A}{0.5} \left[\exp\left(\frac{-9.30}{0.025}\right) - 1 \right] = 1.45 \text{ mA}$$

$$i_E = 10^{-15} A \left[\exp\left(\frac{0.700}{0.025}\right) - \exp\left(\frac{-9.30}{0.025}\right) \right] + \frac{10^{-15} A}{100} \left[\exp\left(\frac{0.700}{0.025}\right) - 1 \right] = 1.46 \text{ mA}$$

$$i_B = \frac{10^{-15} A}{100} \left[\exp\left(\frac{0.700}{0.025}\right) - 1 \right] + \frac{10^{-15} A}{0.5} \left[\exp\left(\frac{-9.30}{0.025}\right) - 1 \right] = 14.5 \text{ }\mu\text{A}$$

Page 217

$$i_C = 10^{-16} A \left[\exp\left(\frac{0.750}{0.025}\right) - \exp\left(\frac{0.700}{0.025}\right) \right] - \frac{10^{-16} A}{0.4} \left[\exp\left(\frac{0.700}{0.025}\right) - 1 \right] = 563 \text{ }\mu\text{A}$$

$$i_E = 10^{-16} A \left[\exp\left(\frac{0.750}{0.025}\right) - \exp\left(\frac{0.700}{0.025}\right) \right] + \frac{10^{-16} A}{75} \left[\exp\left(\frac{0.750}{0.025}\right) - 1 \right] = 938 \text{ }\mu\text{A}$$

$$i_B = \frac{10^{-16} A}{75} \left[\exp\left(\frac{0.750}{0.025}\right) - 1 \right] + \frac{10^{-16} A}{0.4} \left[\exp\left(\frac{0.700}{0.025}\right) - 1 \right] = 376 \text{ }\mu\text{A}$$

Page 217

$$i_T = 10^{-15} A \left[\exp\left(\frac{0.750}{0.025}\right) - \exp\left(\frac{-2}{0.025}\right) \right] = 10.7 \text{ mA}$$

$$i_T = 10^{-16} A \left[\exp\left(\frac{0.750}{0.025}\right) - \exp\left(\frac{-5}{0.025}\right) \right] = 1.07 \text{ mA}$$

Page 220

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S} + 1\right) = 0.025V \ln\left(\frac{10^{-4} A}{10^{-16} A} + 1\right) = 0.691 V$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S} + 1\right) = 0.025V \ln\left(\frac{10^{-3} A}{10^{-16} A} + 1\right) = 0.748 V$$

Page 221

$nnp : V_{BE} > 0, V_{BC} < 0 \rightarrow$ Forward – Active Region $pnp : V_{EB} > 0, V_{CB} > 0 \rightarrow$ Saturation Region

Page 223

$$\beta_F = \frac{\alpha_F}{1 - \alpha_F} = \frac{0.95}{0.05} = 19 \quad \beta_R = \frac{\alpha_R}{1 - \alpha_R} = \frac{0.25}{0.75} = \frac{1}{3}$$

$$V_{BE} = 0, V_{BC} \ll 0 \quad I_C = I_S \left(1 + \frac{1}{\beta_R}\right) = 10^{-16} A \left(1 + \frac{1}{0.333}\right) = 0.400 fA$$

$$I_E = I_S = 0.100 fA \quad I_B = -\frac{I_S}{\beta_R} = -\frac{10^{-16} A}{0.333} = -0.300 fA$$

$$V_{BE} \ll 0, V_{BC} \ll 0 \quad I_C = \frac{I_S}{\beta_R} = 3 \times 10^{-16} A = 0.300 fA$$

$$I_E = \frac{I_S}{\beta_F} = \frac{10^{-16} A}{19.0} = 5.26 aA \quad I_B = -\frac{I_S}{\beta_F} - \frac{I_S}{\beta_R} = -\frac{10^{-16} A}{19.0} - \frac{10^{-16} A}{1/3} = -0.305 fA$$

Page 225

(a) The currents do not depend upon V_{CC} as long as the collector - base junction is reverse biased. (Later when Early voltage V_A is discussed, one should revisit this problem.)

$$(b) I_E = 100 \mu A, I_B = \frac{I_E}{\beta_F + 1} = \frac{100 \mu A}{51} = 1.96 \mu A, I_C = \beta_F I_B = 50 I_B = 98.0 \mu A$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S} + 1\right) = 0.025V \ln\left(\frac{98.0 \mu A}{10^{-16} A} + 1\right) = 0.690 V$$

Page 226

(a) The currents do not depend upon V_{CC} as long as the collector - base junction is reverse biased. (Later when Early voltage V_A is discussed, one should revisit this problem.)

(b) Forward - active region : $I_B = 100 \mu A$, $I_E = (\beta_F + 1)I_B = 5.10 \text{ mA}$, $I_C = \beta_F I_B = 5.00 \text{ mA}$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S} + 1\right) = 0.025V \ln\left(\frac{5.00 \text{ mA}}{10^{-16} \text{ A}} + 1\right) = 0.789 \text{ V} \quad \text{Checking: } V_{BC} = -5 + 0.789 = -4.21 \text{ V}$$

(c) Forward - active region with $V_{CB} \geq 0$ requires $V_{CC} \geq V_{BE}$ or $V_{CC} \geq 0.764 \text{ V}$

Page 228

$$I_E = \frac{-0.7V - (-9V)}{5.6k\Omega} = 1.48 \text{ mA} \quad I_B = \frac{I_E}{\beta_F + 1} = 29.1 \mu A, \quad I_C = \beta_F I_B = 1.45 \text{ mA}$$

$$V_{CE} = V_C - V_E = (9 - 4300I_C) - (-0.7) = 3.47 \text{ V} \quad \text{Q-Point: } (1.45 \text{ mA}, 3.47 \text{ V})$$

$$I_E = \frac{\beta_F + 1}{\beta_F} I_C = \frac{51}{50} 100 \mu A = 102 \mu A \quad R = \frac{-0.7V - (-9V)}{102 \mu A} = \frac{8.3V}{102 \mu A} = 81.4 \text{ k}\Omega$$

Nearest 5% value is 82 k Ω .

Page 229

$$(i) \quad I_E = \frac{-0.7V - (-9V)}{5.6k\Omega} = 1.48 \text{ mA} \quad I_B = \frac{I_E}{\beta_F + 1} = 29.1 \mu A, \quad I_C = \beta_F I_B = 1.45 \text{ mA}$$

$$(ii) \quad I_E = \frac{\beta_F + 1}{\beta_F} I_C = \frac{51}{50} I_C = 1.02 I_C \quad V_{BE} = V_T \ln\left(\frac{I_C}{I_S} + 1\right) = 0.025 \ln(2 \times 10^{15} I_C + 1)$$

$$V_{BE} + 8200 \left[5.10 \times 10^{-16} \exp\left(\frac{V_{BE}}{0.025}\right) - 1 \right] = 9 \rightarrow V_{BE} = 0.7079 \text{ V} \text{ using a calculator solver or spreadsheet.}$$

$$I_C = 5 \times 10^{-16} \exp\left(\frac{0.7079}{0.025}\right) = 992 \mu A \quad V_{CE} = 9 - 4300 I_C - (-0.708) = 5.44 \text{ V}$$

Page 229

$$I_{SD} = \frac{I_{SBJT}}{\alpha_F} = \frac{2 \times 10^{-14} \text{ A}}{0.95} = 21.0 \text{ fA}$$

Page 232

$$-I_C = \frac{-0.7V - (-9V)}{5.6k\Omega} = 1.48 \text{ mA} \quad I_B = \frac{-I_C}{\beta_R + 1} = 0.741 \text{ mA}, \quad -I_E = \beta_R I_B = 0.741 \text{ mA}$$

Page 234

$$(i) V_{CESAT} = (0.025V) \ln \left[\frac{\left(\frac{1}{0.5}\right) \frac{1 + \frac{1mA}{2(40\mu A)}}{1 - \frac{1mA}{50(40\mu A)}}}{1} \right] = 99.7 mV$$

$$(ii) V_{BE} = (0.025V) \ln \left[\frac{0.1mA + (1 - 0.5)1mA}{10^{-15} A \left(\frac{1}{50} + 1 - 0.5\right)} \right] = 0.694 mV$$

$$V_{BC} = (0.025V) \ln \left[\frac{0.1mA - \frac{1mA}{50}}{10^{-15} A \left(\frac{1}{0.5}\right) \left(\frac{1}{50} + 1 - 0.5\right)} \right] = 0.627 mV \quad V_{BE} - V_{BC} = 67.7 mV$$

Page 237

$$D_n = \frac{kT}{q} \mu_n = 0.025V (500 cm^2 / V - s) = 12.5 cm^2 / s$$

$$I_S = \frac{qAD_n n_i^2}{N_{AB} W} = \frac{1.6 \times 10^{-19} C (50 \mu m^2) (10^{-4} cm / \mu m) (12.5 cm^2 / s) (10^{20} / cm^6)}{(10^{18} / cm^3) (1 \mu m)} = 10^{-18} A$$

Page 240

$$(i) V_T = \frac{(1.38 \times 10^{-23} J / K) (373 K)}{1.60 \times 10^{-19} C} = 32.2 mV \quad C_D = \frac{I_C}{V_T} \tau_F = \frac{10 A}{0.0322 V} (4 \times 10^{-9} s) = 1.24 \mu F$$

$$(ii) f_\beta = \frac{f_T}{\beta_F} = \frac{300 MHz}{125} = 2.40 MHz$$

Page 241

$$(a) I_C = 10^{-15} A \exp\left(\frac{0.7}{0.025}\right) \left(1 + \frac{10}{50}\right) = 1.74 mA \quad \beta_F = 75 \left(1 + \frac{10}{50}\right) = 90.0 \quad I_B = \frac{1.74 mA}{90.0} = 19.3 \mu A$$

$$(b) I_C = 10^{-15} A \exp\left(\frac{0.7}{0.025}\right) = 1.45 mA \quad \beta_F = 75 \quad I_B = \frac{1.45 mA}{75} = 19.3 \mu A$$

Page 243

$$g_m = 40(10^{-4}) = 4.00 mS \quad g_m = 40(10^{-3}) = 40.0 mS$$

$$C_D = 4.00 mS (25 ps) = 0.100 pF \quad C_D = 40.0 mS (25 ps) = 1.00 pF$$

Page 249

$$V_{EQ} = \frac{180k\Omega}{180k\Omega + 360k\Omega} 12V = 4.00V \quad | \quad R_{EQ} = 180k\Omega \parallel 360k\Omega = 120k\Omega$$

$$I_B = \frac{4.00 - 0.7}{120 + (75 + 1)16} \frac{V}{k\Omega} = 2.470\mu A \quad | \quad I_C = 75I_B = 185.3\mu A \quad | \quad I_E = 76I_B = 187.7\mu A$$

$$V_{CE} = 12 - 22000I_C - 16000I_E = 4.92V \quad | \quad Q\text{-point} : (185 \mu A, 4.92 V)$$

Page 250

$$(i) \quad I_2 = \frac{I_C}{5} = \frac{50I_B}{5} = 10I_B$$

$$(ii) \quad V_{EQ} = \frac{18k\Omega}{18k\Omega + 36k\Omega} 12V = 4.00V \quad | \quad R_{EQ} = 18k\Omega \parallel 36k\Omega = 12k\Omega$$

$$I_B = \frac{4.00 - 0.7}{12 + (500 + 1)16} \frac{V}{k\Omega} = 0.4111\mu A \quad | \quad I_C = 500I_B = 205.5\mu A \quad | \quad I_E = 76I_B = 206.0\mu A$$

$$V_{CE} = 12 - 22000I_C - 16000I_E = 4.18V \quad | \quad Q\text{-point} : (206 \mu A, 4.18 V)$$

Page 251

The voltages all remain the same, and the currents are reduced by a factor of 10. Hence all the resistors are just scaled up by a factor of 10.

$$120 \text{ k}\Omega \rightarrow 1.2 \text{ M}\Omega \quad 82 \text{ k}\Omega \rightarrow 820 \text{ k}\Omega \quad 6.8 \text{ k}\Omega \rightarrow 68 \text{ k}\Omega$$

Page 253

$$(i) \quad V_{CE} = 0.7 \text{ V at the edge of saturation.} \quad 0.7V = 12V - \left(R_C + \frac{76}{75} 16k\Omega \right) (205\mu A) \rightarrow R_C = 38.9 \text{ k}\Omega$$

$$(ii) \quad V_{BESAT} = 4 - 12k\Omega(24\mu A) - 16k\Omega(184\mu A) = 0.768 \text{ V}$$

$$V_{CESAT} = 12 - 56k\Omega(160\mu A) - 16k\Omega(184\mu A) = 0.096 \text{ V}$$

Page 254

$$I_B = \frac{9 - 0.7}{36 + (50 + 1)1} \frac{V}{k\Omega} = 95.4\mu A \quad | \quad I_C = 50I_B = 4.77 \text{ mA} \quad | \quad I_E = 76I_B = 187.7\mu A$$

$$V_{CE} = 9 - 1000(I_C + I_B) = 4.13V \quad | \quad Q\text{-point} : (4.77 \text{ mA}, 4.13 \text{ V})$$
