

Microelectronic Circuit Design

Third Edition - Part II

Solutions to Exercises

CHAPTER 6

Page 280

$$NM_L = 0.8V - 0.4V = 0.4V \quad NM_H = 3.6V - 2.0V = 1.6V$$

Page 282

$$V_{10\%} = V_L + 0.1(\Delta V) = -2.6V + 0.1[-0.6 - (-2.6)] = -2.4V \quad \text{or}$$

$$V_{10\%} = V_H - 0.9(\Delta V) = -0.6V - 0.9[-0.6 - (-2.6)] = -2.4V$$

$$V_{90\%} = V_L + 0.9(\Delta V) = -2.6V + 0.9[-0.6 - (-2.6)] = -0.8V \quad \text{or}$$

$$V_{90\%} = V_H - 0.1(\Delta V) = -0.6V - 0.1[-0.6 - (-2.6)] = -0.8V$$

$$V_{50\%} = \frac{V_H + V_L}{2} = \frac{-0.6 - 2.6}{2} = -1.6V \quad t_r = t_4 - t_3 = 3ns \quad t_f = t_2 - t_1 = 5ns$$

Page 283

$$\text{At } P = 1 \text{ mW} : \text{PDP} = 1mW(1ns) = 1pJ$$

$$\text{At } P = 3 \text{ mW} : \text{PDP} = 3mW(1ns) = 3pJ$$

$$\text{At } P = 20 \text{ mW} : \text{PDP} = 20mW(2ns) = 40pJ$$

Page 285

$$Z = (A + B)(B + C) = AB + AC + BB + BC = AB + BB + AC + BB + BC$$

$$Z = AB + B + AC + B + BC = B(A + 1) + AC + B(C + 1) = B + AC + B$$

$$Z = B + B + AC = B + AC$$

Page 288

$$I_{DD} = \frac{P}{V_{DD}} = \frac{0.4mW}{2.5V} = 160 \mu A \quad R = \frac{V_{DD} - V_L}{I_{DD}} = \frac{2.5V - 0.2V}{160\mu A} = 14.4 k\Omega$$

$$1.6 \times 10^{-4} A = 10^{-4} \frac{A}{V^2} \left(\frac{W}{L} \right)_s \left(2.5 - 0.6 - \frac{0.2}{2} \right) 0.2 V^2 \rightarrow \left(\frac{W}{L} \right)_s = \frac{4.44}{1}$$

Page 289

$$I_{DD} = \frac{V_{DD} - V_L}{R} = \frac{3.3V - 0.1V}{102k\Omega} = 31.4\mu A$$

$$31.4 \times 10^{-6} A = 6 \times 10^{-5} \frac{A}{V^2} \left(\frac{W}{L} \right)_s \left(3.3 - 0.75 - \frac{0.1}{2} \right) 0.1 V^2 \rightarrow \left(\frac{W}{L} \right)_s = \frac{2.09}{1}$$

Page 290

$$0.15V = \frac{R_{on}}{R_{on} + 28.8k\Omega} 2.5V \rightarrow R_{on} = 1.84 k\Omega$$

$$\left(\frac{W}{L} \right)_s = \frac{1}{10^{-4} \left(2.5 - 0.60 - \frac{0.15}{2} \right) (1.84k\Omega)} \rightarrow \left(\frac{W}{L} \right)_s = \frac{2.98}{1}$$

Page 291

$$(i) R_{on} = \frac{1}{6 \times 10^{-5} \left(\frac{1.03}{1} \right) \left(3.3 - 0.75 - \frac{0.2}{2} \right)} = 6.61 k\Omega \quad V_L = \frac{6.61k\Omega}{6.61k\Omega + 102k\Omega} 3.3V = 0.201 V$$

$$(ii) \left[\frac{1}{K_n R} \right] = \frac{V^2}{A} \frac{1}{\Omega} = V$$

Page 293

$$K_n R = \left(6 \times 10^{-5} \right) \left(\frac{1.03}{1} \right) (1.02 \times 10^5) = \frac{6.30}{V}$$

$$NM_H = 3.3 - 0.75 + \frac{1}{2(6.30)} - 1.63 \sqrt{\frac{3.3}{6.30}} = 1.45 V \quad NM_L = 0.75 + \frac{1}{6.30} - \sqrt{\frac{2(3.3)}{3(6.30)}} = 0.318 V$$

Page 297

$$(i) V_H = 2.5 - \left[0.6 + 0.75 \left(\sqrt{V_H + 0.6} - \sqrt{0.6} \right) \right] \rightarrow V_H = 1.416 V$$

$$(ii) 80 \times 10^{-6} A = 100 \times 10^{-6} \frac{A}{V^2} \left(\frac{W}{L} \right)_s \left(1.55 - 0.60 - \frac{0.15}{2} \right) 0.15 V^2 \rightarrow \left(\frac{W}{L} \right)_s = \frac{6.10}{1}$$

$$V_{TNL} = 0.6 + 0.5 \left(\sqrt{0.15 + 0.6} - \sqrt{0.6} \right) = 0.646 V$$

$$80 \times 10^{-6} A = \frac{100 \times 10^{-6}}{2} \frac{A}{V^2} \left(\frac{W}{L} \right)_L \left(2.5 - 0.15 - 0.646 \right)^2 V^2 \rightarrow \left(\frac{W}{L} \right)_L = \frac{0.551}{1} = \frac{1}{1.82}$$

$$(iii) 80 \times 10^{-6} A = 100 \times 10^{-6} \frac{A}{V^2} \left(\frac{W}{L} \right)_s \left(1.55 - 0.60 - \frac{0.1}{2} \right) 0.1 V^2 \rightarrow \left(\frac{W}{L} \right)_s = \frac{8.89}{1}$$

$$V_{TNL} = 0.6 + 0.5 \left(\sqrt{0.1 + 0.6} - \sqrt{0.6} \right) = 0.631 V$$

$$80 \times 10^{-6} A = \frac{100 \times 10^{-6}}{2} \frac{A}{V^2} \left(\frac{W}{L} \right)_L \left(2.5 - 0.1 - 0.631 \right)^2 V^2 \rightarrow \left(\frac{W}{L} \right)_L = \frac{0.511}{1} = \frac{1}{1.96}$$

Page 300

The high logic level is unchanged : $V_H = 2.11$

$$60 \times 10^{-6} A = 50 \times 10^{-6} \frac{A}{V^2} \left(\frac{W}{L} \right)_S \left(2.11 - 0.75 - \frac{0.1}{2} \right) 0.1 V^2 \rightarrow \left(\frac{W}{L} \right)_S = \frac{9.16}{1}$$

$$V_{TNL} = 0.75 + 0.5 \left(\sqrt{1 + 0.6} - \sqrt{0.6} \right) = 0.781 V$$

$$60 \times 10^{-6} A = \frac{50 \times 10^{-6}}{2} \frac{A}{V^2} \left(\frac{W}{L} \right)_L \left(3.3 - 0.1 - 0.781 \right)^2 V^2 \rightarrow \left(\frac{W}{L} \right)_L = \frac{0.410}{1} = \frac{1}{2.44}$$

Page 302

$\gamma = 0 \rightarrow V_{TN} = 0.6V$ and $V_H = 2.5 - 0.6 = 1.9 V$ $I_{DD} = 0$ for $v_o = V_H$

$$100 \times 10^{-6} \left(\frac{10}{1} \right) \left(1.9 - 0.6 - \frac{V_L}{2} \right) V_L = \frac{100 \times 10^{-6}}{2} \left(\frac{2}{1} \right) \left(2.5 - V_L - 0.6 \right)^2$$

$$6V_L^2 - 116.8V_L + 3.61 = 0 \rightarrow V_L = 0.235V \quad I_{DD} = 100 \times 10^{-6} \left(\frac{10}{1} \right) \left(1.9 - 0.6 - \frac{0.235}{2} \right) 0.235 = 278 \mu A$$

$$\text{Checking: } I_{DD} = \frac{100 \times 10^{-6}}{2} \left(\frac{2}{1} \right) \left(2.5 - 0.235 - 0.6 \right)^2 = 277 \mu A$$

Page 307

$$V_{TNL} = -1.5 + 0.5 \left(\sqrt{0.2 + 0.6} - \sqrt{0.6} \right) = -1.44V$$

$$60.6 \times 10^{-6} = \frac{100 \times 10^{-6}}{2} \left(\frac{W}{L} \right)_L \left(0 - 1.44 \right)^2 \rightarrow \left(\frac{W}{L} \right)_L = \frac{0.585}{1} = \frac{1}{1.71}$$

$$60.6 \times 10^{-6} = 100 \times 10^{-6} \left(\frac{W}{L} \right)_S \left(3.3 - 0.6 - \frac{0.2}{2} \right) 0.2 \rightarrow \left(\frac{W}{L} \right)_S = \frac{1.17}{1}$$

Page 308

$$I_{DS} = 100 \times 10^{-6} \left(\frac{2.22}{1} \right) \left(2.5 - 0.6 - \frac{0.2}{2} \right) 0.2 = 79.9 \mu A \text{ which checks.}$$

Page 309

The PMOS transistor is still saturated so $I_{DL} = 144 \mu A$, and $V_H = 2.5 V$.

$$144 \times 10^{-6} = 100 \times 10^{-6} \left(\frac{5}{1} \right) \left(2.5 - 0.6 - \frac{V_L}{2} \right) V_L \rightarrow V_L = 0.158 V$$

Page 314

Place a third transistor with $\frac{W}{L} = \frac{2.22}{1}$ in parallel with transistors A and B.

Page 315

Place a third transistor in series with transistors A and B.

The new W/L ratios of transistors A, B and C are $\frac{W}{L} = 3 \frac{2.22}{1} = \frac{6.66}{1}$.

Page 321

M_{L1} is saturated for all three voltages. $I_{DD} = \frac{40 \times 10^{-6}}{2} \left(\frac{1.11}{1} \right)_L [-2.5 - (-0.6)]^2 = 80.1 \mu A$

Note that the voltages in two rows are in error in the table.

11000 132 64.4 0 11111 64.6 31.9 31.9

The voltages can be estimated using the on - resistance method.

For the 11000 case, $R_{onA} = \frac{132mV - 64.4mV}{80.1\mu A} = 844 \Omega$ $R_{onB} = \frac{64.4mV}{80.1\mu A} = 804 \Omega$

For the 00101 case, $R_{onE} = \frac{64.4mV}{80.1\mu A} = 804 \Omega$.

For the 01110 case, $R_{onC} = \frac{203mV - 132mV}{80.1\mu A} = 886 \Omega$ $R_{onD} = \frac{132mV - 64.4mV}{80.1\mu A} = 844 \Omega$

The voltage across a given conducting device is $I_D R_{on}$. Small variations in R_{on} are ignored.

ABCDE	Y (mV)	2 (mV)	3 (mV)	I _{DD} (uA)	ABCDE	Y (mV)	2 (mV)	3 (mV)	I _{DD} (uA)
00000	2.5 V	0	0	0	10000	2.5 V	2.5 V	0	0
00001	2.5 V	0	0	0	10001	2.5 V	2.5 V	0	0
00010	2.5 V	0	0	0	10010	2.5 V	2.5 V	2.5 V	0
00011	2.5 V	0	0	0	10011	200	130	64	80.1
00100	2.5 V	0	2.5 V	0	10100	2.5 V	2.5 V	2.5 V	0
00101	130	0	64	80.1	10101	130	130	64	80.1
00110	2.5 V	2.5 V	2.5 V	0	10110	2.5 V	2.5 V	2.5 V	0
00111	130	64	64	80.1	10111	100	83	64	80.1
01000	2.5 V	0	0	0	11000	130	64	0	80.1
01001	2.5 V	0	0	0	11001	130	64	0	80.1
01010	2.5 V	0	0	0	11010	130	64	64	80.1
01011	2.5 V	0	0	0	11011	110	43	22	80.1
01100	2.5 V	0	2.5 V	0	11100	130	64	64	80.1
01101	130	0	64	80.1	11101	66	32	32	80.1
01110	200	64	130	80.1	11110	110	64	87	80.1
01111	114	21	43	80.1	11111	65	32	32	80.1

Page 322

$P_{av} = \frac{2.5V(80.1 \mu A)}{2} = 0.100 mW$

Page 323

$$P_D = 10^{-12} F (2.5V)^2 (32 \times 10^6 \text{ Hz}) = 2 \times 10^{-4} W = 200 \mu W \text{ or } 0.200 \text{ mW}$$

Page 324

(i) The inverter in Fig. 6.38(a) was designed for a power dissipation of 0.2 mW.

To reduce the power by a factor of two, we must reduce the W/L ratios by a factor of 2.

$$\left(\frac{W}{L}\right)_L = \frac{1}{2} \left(\frac{1}{1.68}\right) = \frac{1}{3.36} \quad \left(\frac{W}{L}\right)_S = \frac{1}{2} \left(\frac{4.71}{1}\right) = \frac{2.36}{1}$$

(ii) To increase the power by a factor of $\frac{4\text{mW}}{0.2\text{mW}}$, we must increase the W/L ratios by a factor of 20.

$$\left(\frac{W}{L}\right)_L = 20 \left(\frac{1.81}{1}\right) = \frac{36.2}{1} \quad \left(\frac{W}{L}\right)_S = 2 \left(\frac{2.22}{1}\right) = \frac{44.4}{1}$$

(iii) To reduce the power by a factor of three, we must reduce the W/L ratios by a factor of 3.

$$\left(\frac{W}{L}\right)_L = \frac{1}{3} \left(\frac{1.81}{1}\right) = \frac{0.603}{1} = \frac{1}{1.66} \quad \left(\frac{W}{L}\right)_A = \frac{1}{3} \left(\frac{3.33}{1}\right) = \frac{1.11}{1} \quad \left(\frac{W}{L}\right)_{BCD} = \frac{1}{3} \left(\frac{6.66}{1}\right) = \frac{2.22}{1}$$

Page 327

$$t_r = 2.2(28.8 \times 10^3 \Omega)(2 \times 10^{-13} F) = 12.7 \text{ ns} \quad \tau_{PLH} = 0.69(28.8 \times 10^3 \Omega)(2 \times 10^{-13} F) = 3.97 \text{ ns}$$

Page 330

$$t_f = 3.7(2.37 \times 10^3 \Omega)(2.5 \times 10^{-13} F) = 2.19 \text{ ns} \quad \tau_{PHL} = 1.2(2.37 \times 10^3 \Omega)(2.5 \times 10^{-13} F) = 0.711 \text{ ns}$$

$$t_r = 2.2(28.8 \times 10^3 \Omega)(2.5 \times 10^{-13} F) = 15.8 \text{ ns} \quad \tau_{PLH} = 0.69(28.8 \times 10^3 \Omega)(2.5 \times 10^{-13} F) = 4.97 \text{ ns}$$

$$\tau_p = \frac{0.711 \text{ ns} + 4.97 \text{ ns}}{2} = 2.84 \text{ ns}$$

Page 335

(i) The PMOS transistor is saturated for $v_o = V_L$. $I_{DD} = \frac{40 \times 10^{-6}}{2} \left(\frac{23.7}{1}\right)_L [-2.5 - (-0.6)]^2 = 1.71 \text{ mA}$

$$P_{av} = \frac{2.5V(1.71 \text{ mA})}{2} = 2.14 \text{ mW} \quad P_D = 5 \times 10^{-12} F (2.5V - 0.2V)^2 \left(\frac{1}{2 \times 10^{-9} s}\right) = 13.2 \text{ mW}$$

(ii) We must increase the power by a factor of $\frac{20\text{pF}}{5\text{pF}} \left(\frac{2\text{ns}}{1\text{ns}}\right) = 8$,

so the W/L ratios must also be increased by a factor of 8.

$$\left(\frac{W}{L}\right)_L = 8 \left(\frac{23.7}{1}\right) = \frac{190}{1} \quad \left(\frac{W}{L}\right)_S = 8 \left(\frac{47.4}{1}\right) = \frac{379}{1} \quad P_D = 20 \times 10^{-12} F (2.5V - 0.2V)^2 \left(\frac{1}{10^{-9} s}\right) = 106 \text{ mW}$$

CHAPTER 7

Page 355

- (a) $K_p = 40 \times 10^{-6} \left(\frac{20}{1} \right) = 800 \frac{\mu A}{V^2}$ $K_n = 100 \times 10^{-6} \left(\frac{20}{1} \right) = 2000 \frac{\mu A}{V^2} = 2.00 \frac{mA}{V^2}$
- (b) $V_{TN} = 0.6 + 0.5(\sqrt{2.5 + 0.6} - \sqrt{0.6}) = 1.09 V$
- (c) $V_{TP} = -0.6 - 0.75(\sqrt{2.5 + 0.7} - \sqrt{0.7}) = -1.31 V$

Page 357

- (a) For $v_I = 1V$, $V_{GSN} - V_{TN} = 1 - 0.6 = 0.4V$ and $V_{GSP} - V_{TP} = -1.5 + 0.6 = -0.9V$
 M_N is saturated for $v_O \geq 0.4 V$. M_P is in the triode region for $v_O \geq 1.6 V$. $\therefore 1.6 V \leq v_O \leq 2.5 V$
- (b) M_P is saturated for $v_O \leq 1.6 V$. $\therefore 0.4 V \leq v_O \leq 1.6 V$
- (c) M_N is in the triode region for $v_O \leq 0.4 V$. M_P is saturated for $v_O \leq 1.6 V$. $\therefore 0 \leq v_O \leq 0.4 V$

Page 357

$$\left(\frac{W}{L} \right)_P = \frac{K_n}{K_p} \left(\frac{W}{L} \right)_N = 2.5 \left(\frac{10}{1} \right) = \frac{25}{1}$$

Page 358

- (i) Both transistors are saturated since $|V_{GS}| = |V_{DS}|$.
- $$\frac{K_n}{2} (V_{GSN} - V_{TN})^2 = \frac{K_p}{2} (V_{GSP} - V_{TP})^2 \quad K_n = K_p \quad |V_{TN}| = |V_{TP}|$$
- $$V_{GSN} = -V_{GSP} \rightarrow v_I = V_{DD} - v_I \rightarrow v_I = \frac{V_{DD}}{2}$$
- (ii) $\frac{10K_p}{2} (V_{GSN} - V_{TN})^2 = \frac{K_p}{2} (V_{GSP} - V_{TP})^2 \rightarrow \sqrt{10}(V_{GSN} - V_{TN}) = -V_{GSP} + V_{TP}$
- $$\sqrt{10}(v_I - 0.6) = 4 - v_I - 0.6 \rightarrow v_I = 1.273 V$$

Page 360

$$K_R = \frac{K_n \left(\frac{W}{L}\right)_N}{K_p \left(\frac{W}{L}\right)_P} = \frac{K_n}{K_p} = 2.5$$

$$V_{IH} = \frac{2K_R(V_{DD} - V_{TN} + V_{TP})}{(K_R - 1)\sqrt{1 + 3K_R}} - \frac{(V_{DD} - K_R V_{TN} + V_{TP})}{K_R - 1}$$

$$V_{IH} = \frac{2(2.5)(2.5 - 0.6 - 0.6)}{(2.5 - 1)\sqrt{1 + 3(2.5)}} - \frac{(2.5 - 2.5(0.6) - 0.6)}{2.5 - 1} = 1.22V$$

$$V_{OL} = \frac{(K_R + 1)V_{IH} - V_{DD} - K_R V_{TN} - V_{TP}}{2K_R} = \frac{(2.5 + 1)1.22 - 2.5 - 2.5(0.6) + 0.6}{2(2.5)} = 0.174V$$

$$V_{IL} = \frac{2\sqrt{K_R}(V_{DD} - V_{TN} + V_{TP})}{(K_R - 1)\sqrt{K_R + 3}} - \frac{(V_{DD} - K_R V_{TN} + V_{TP})}{K_R - 1}$$

$$V_{IL} = \frac{2\sqrt{2.5}(2.5 - 0.6 - 0.6)}{(2.5 - 1)\sqrt{2.5 + 3}} - \frac{(2.5 - 2.5(0.6) - 0.6)}{2.5 - 1} = 0.902V$$

$$V_{OH} = \frac{(K_R + 1)V_{IL} + V_{DD} - K_R V_{TN} - V_{TP}}{2} = \frac{(2.5 + 1)0.902 + 2.5 - 2.5(0.6) + 0.6}{2} = 2.38V$$

$$NM_H = V_{OH} - V_{IH} = 2.38 - 1.22 = 1.16V \quad NM_L = V_{IL} - V_{OL} = 0.902 - 0.174 = 0.728V$$

Page 362

C should be 0.75 pF, and the delay in the inverter in Fig. 7.13(b) should be 1.6 ns.

$$(i) \text{ Symmetrical Inverter: } \tau_p = 1.2R_{onn}C = 1.2 \frac{0.75 \times 10^{-12} F}{2(10^{-4})(2.5 - 0.6)} \Omega = 2.4 \text{ ns}$$

$$(ii) \text{ Symmetrical Inverter: } R_{onn} = \frac{\tau_p}{1.2C} = \frac{10^{-9} s}{1.2(5 \times 10^{-12} F)} = 167 \Omega$$

$$\left(\frac{W}{L}\right)_N = \frac{1}{R_{onn}K_n(V_{GS} - V_{TN})} = \frac{1}{167(10^{-4})(2.5 - 0.6)} = \frac{31.5}{1} \quad \left(\frac{W}{L}\right)_P = 2.5 \left(\frac{W}{L}\right)_N = 78.8$$

Page 364

The inverters need to be increased in size by a factor of $\frac{280\text{ps}}{250\text{ps}} = 1.12$.

$$\left(\frac{W}{L}\right)_N = 1.12 \left(\frac{3.77}{1}\right) = \frac{4.22}{1} \quad \left(\frac{W}{L}\right)_P = 1.12 \left(\frac{9.43}{1}\right) = \frac{10.6}{1}$$

Page 364

$$\left(\frac{W}{L}\right)_N = \left(\frac{3.77}{1}\right)\left(\frac{3.3-0.75}{3.3-0.5}\right) = \frac{3.43}{1} \quad \left(\frac{W}{L}\right)_P = \left(\frac{9.43}{1}\right)\left(\frac{3.3-0.75}{3.3-0.5}\right) = \frac{8.59}{1}$$

Page 364

$$\tau_{PHL} = 2.4R_{onn}C = \frac{2.4C}{K_n(V_{GS} - V_{TN})} = \frac{2.4C}{K_n(2.5 - 0.6)} = 1.26 \frac{C}{K_n}$$

$$\tau_{PLH} = 2.4R_{onp}C = \frac{2.4C}{K_p(V_{GS} - V_{TN})} = \frac{2.4C}{K_p(2.5 - 0.6)} = 1.26 \frac{C}{K_p}$$

Page 365

$$\tau_{PHL} = 2.4R_{onn}C = \frac{2.4C}{K_n(V_{GS} - V_{TN})} = \frac{2.4C}{K_n(3.3 - 0.75)} = 0.94 \frac{C}{K_n}$$

$$\tau_{PLH} = 2.4R_{onp}C = \frac{2.4C}{K_p(V_{GS} - V_{TN})} = \frac{2.4C}{K_p(3.3 - 0.75)} = 0.94 \frac{C}{K_p}$$

Page 366

The inverter in Fig. 7.12 is a symmetrical design, so the maximum current occurs for $v_o = v_i = \frac{V_{DD}}{2}$.

Both transistors are saturated. $i_{DN} = \frac{10^{-4}}{2}\left(\frac{2}{1}\right)(1.25 - 0.6)^2 = 42.3 \mu A$

Checking: $i_{DP} = \frac{4 \times 10^{-5}}{2}\left(\frac{5}{1}\right)(1.25 - 0.6)^2 = 42.3 \mu A$

Page 367

$$PDP \cong \frac{CV_{DD}^2}{5} = \frac{10^{-13} F (2.5V)^2}{5} = 0.13 pJ \quad PDP \cong \frac{CV_{DD}^2}{5} = \frac{10^{-13} F (3.3V)^2}{5} = 0.22 pJ$$

Page 371


Remove the NMOS and PMOS transistors connected to input E, and ground the source of the NMOS transistor connected to input D. There are now 4 NMOS transistors in series, and

$$\left(\frac{W}{L}\right)_N = 4\left(\frac{2}{1}\right) = \frac{8}{1} \quad \left(\frac{W}{L}\right)_P = \frac{5}{1}$$

Page 376

There are two NMOS transistors in series in the AB and CD NMOS paths, and three PMOS transistors in the ACE and BDE PMOS paths. Therefore:

$$\left(\frac{W}{L}\right)_{N-ABCD} = 2\left(\frac{2}{1}\right) = \frac{4}{1} \quad \left(\frac{W}{L}\right)_{N-E} = \frac{2}{1} \quad \left(\frac{W}{L}\right)_P = 3\left(\frac{5}{1}\right) = \frac{15}{1}$$

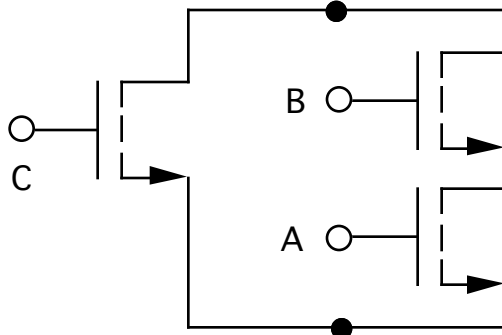Page 380**AB+C**

$$P = CV_{DD}^2 f = (50 \times 10^{-12} F)(5V)^2(10^7 Hz) = 12.5 mW$$

Page 383

$$\beta = \left(\frac{50 pF}{50 fF}\right)^{\frac{1}{2}} = 31.6 \quad \tau_p = 31.6\tau_o + 31.6\tau_o = 63.2\tau_o \quad | \quad z = e^{\ln z} \quad | \quad z^{\frac{1}{\ln z}} = (e^{\ln z})^{\frac{1}{\ln z}} = e$$

$$\beta = \left(\frac{50 pF}{50 fF}\right)^{\frac{1}{7}} = 2.683$$

$$1, 2.68, 2.68^2 = 7.20, 2.68^3 = 19.3, 2.68^4 = 51.8, 2.68^5 = 139, 2.68^6 = 373$$

$$A_6 = (1 + 3.16 + 10 + 31.6 + 100 + 316)A_o = 462A_o$$

$$A_7 = (1 + 2.68 + 7.20 + 19.3 + 51.8 + 139 + 373)A_o = 594A_o$$

CHAPTER 8

Page 401

$$NS = \frac{2^8 \cdot 2^{20}}{2^7 \cdot 2^{10}} = 2^{11} = 2048 \text{ segments} \quad NS = \frac{2^{30}}{2^9 \cdot 2^{10}} = 2^{11} = 2048 \text{ segments}$$

Page 403

(i) $N = 2^8 \cdot 2^{20} = 2^{28} = 268,435,456$ $I_{DD} = \frac{0.05W}{3.3V} = 15.2 \text{ mA}$ $\text{Current/cell} = \frac{15.2\text{mA}}{2^{28} \text{ cells}} = 56.4 \text{ pA}$

(ii) Reverse the direction of the substrate arrows, and connect the substrates of the PMOS transistors to V_{DD} .

Page 406

M_{A1} : At $t = 0^+$, $V_{GS} - V_{TN} = 4V$ and $V_{DS} = 2.5V$, so transistor M_{A1} is operating in the triode region.

$$i_1 = 60 \times 10^{-6} \left(\frac{1}{1} \right) \left(5 - 1 - \frac{2.5}{2} \right) 2.5 = 413 \mu A$$

M_{A2} : At $t = 0^+$, $V_{GS} = V_{DS}$, so transistor M_{A2} is operating in the saturation region.

$$V_{TN2} = 1 + 0.6 \left(\sqrt{2.5 + 0.6} - \sqrt{0.6} \right) = 1.592V \quad i_2 = \frac{60 \times 10^{-6}}{2} \left(\frac{1}{1} \right) \left(5 - 2.5 - 1.592 \right)^2 = 24.8 \mu A$$

Page 408

M_{A1} : At $t = 0^+$, $V_{GS} = V_{DS}$, so transistor M_{A1} is operating in the saturation region.

$$i_1 = \frac{60 \times 10^{-6}}{2} \left(\frac{1}{1} \right) (5 - 1)^2 = 480 \mu A$$

M_{A2} : At $t = 0^+$, $V_{GS} = V_{DS}$, so transistor M_{A2} is operating in the saturation region.

$$i_1 = \frac{60 \times 10^{-6}}{2} \left(\frac{1}{1} \right) (5 - 1)^2 = 480 \mu A$$

Page 411

(i) At $t = 0^+$, $V_{GS} - V_{TN} = 3 - 0.7 = 2.3 \text{ V}$ and $V_{DS} = 1.9 \text{ V}$, so transistor M_A is operating in the triode region.

$$i_1 = 60 \times 10^{-6} \left(\frac{1}{1} \right) \left(3 - 0.7 - \frac{1.9}{2} \right) 1.9 = 154 \mu A \quad t_f = 3.6 R_{on} C = 3.6 \frac{50 \times 10^{-15} F}{60 \times 10^{-6} (3 - 0.7)} = 1.30 \text{ ns}$$

(ii) $V_C = V_{BL} - V_{TN} \quad V_C = 3 - \left[0.7 + 0.5 \left(\sqrt{V_C + 0.6} - \sqrt{0.6} \right) \right] \rightarrow V_C = 1.89 \text{ V} \quad | \quad V_C = 3 - 0.7 = 2.3V$

(iii) $n = \frac{CV}{q} = \frac{25 \times 10^{-15} F (1.89V)}{1.60 \times 10^{-19} C} = 2.95 \times 10^5 \text{ electrons}$

Page 413

$$\Delta V = \frac{V_C - V_{BL}}{\frac{C_{BL}}{C_C} + 1} = \frac{1.9 - 0.95}{\frac{49C_C}{C_C} + 1} V = 0.019 V \quad \Delta V = \frac{V_C - V_{BL}}{\frac{C_{BL}}{C_C} + 1} = \frac{0 - 0.95}{\frac{49C_C}{C_C} + 1} V = -0.019 V$$

$$\tau = R_{on} \frac{C_C}{\frac{C_{BL}}{C_C} + 1} = 5k\Omega \frac{25fF}{\frac{1}{49} + 1} = 0.123 ns \quad \text{or} \quad \tau \cong R_{on} C_C = 5k\Omega(25fF) = 0.125 ns$$

Page 414

At $t = 0^+$, $V_{GS} - V_{TN} = (3 - 0) - 0.7 = 2.3 V$ and $V_{DS} = 1.5 V$, so transistor M_{A2} is operating in

the triode region. $i_D = 60 \times 10^{-6} \left(\frac{2}{1} \right) \left(3 - 0.7 - \frac{1.5}{2} \right) 1.5 = 279 \mu A$

Page 416

(i) In setting the drain currents equal, we see that the change in W/L cancels out, and the voltages remain the same.

$$\therefore i_D = \frac{1}{2} (60 \times 10^{-6}) \left(\frac{5}{1} \right) (1.33 - 0.7)^2 = 59.5 \mu A \quad P_D = 2(59.5 \mu A)(3V) = 0.357 mW$$

As a check, the current should scale with W/L: $i_D = \frac{5}{2} (23.5 \mu A) = 58.8 \mu A$

$$(ii) \frac{1}{2} (25 \times 10^{-6}) \left(\frac{2}{1} \right) (2.5 - V_o - 0.6)^2 = \frac{1}{2} (60 \times 10^{-6}) \left(\frac{2}{1} \right) (V_o - 0.6)^2$$

$$1.4V_o^2 + 0.92V_o - 2.746 = 0 \rightarrow V_o = 1.11V$$

$$i_D = \frac{1}{2} (25 \times 10^{-6}) \left(\frac{2}{1} \right) (2.5 - 1.11 - 0.6)^2 = 15.6 \mu A \quad P_D = 2(15.6 \mu A)(2.5V) = 78.0 \mu W$$

$$\text{Checking: } \frac{1}{2} (60 \times 10^{-6}) \left(\frac{2}{1} \right) (1.11 - 0.6)^2 = 15.6 \mu A$$

Page 418

$$R_{on} = \frac{1}{60 \times 10^{-6} (3 - 1.3 - 1)} = 23.8 k\Omega \quad \tau = 23.8 k\Omega (25 fF) = 0.595 ns$$

Page 420

For all possible input combinations there will be two inverters and 3 output lines in the low state.

$$P_D = 5(0.2mW) = 1.0 mW$$

Page 422

$$\left(\frac{W}{L} \right)_L = \frac{2}{2.22} \left(\frac{1.81}{1} \right) = \frac{1.63}{1}$$

Page 424

(i) For a 0-V input, all transistors will be on and the input nodes will all discharge to 0 V.

For the 3-V input, the nodes will all charge to 3 V as long as $V_{TN} \leq 2V$.

$V_{TN} = 0.7 + 0.5(\sqrt{3 + 0.6} - \sqrt{0.6}) = 1.26 V$. Thus the nodes will all be a 3 V.

$$2 \geq 0.7 + \gamma(\sqrt{3 + 0.6} - \sqrt{0.6}) \rightarrow \gamma \leq 1.158$$

(ii) The output will drop below $V_{DD}/2$. For the PMOS device, $|V_{GS} - V_{TP}| = 3 - 1.9 - 0.7 = 0.4V$.

The PMOS transistor will be saturated. For the NMOS device, $|V_{GS} - V_{TP}| = 1.9 - 0.7 = 1.2V$.

Assume linear region operation.

$$\frac{40 \times 10^{-6}}{2} \left(\frac{5}{1} \right) (-1.1 + 0.7)^2 = 100 \times 10^{-6} \left(\frac{2}{1} \right) \left(1.9 - 0.7 - \frac{V_o}{2} \right) V_o$$

$$V_o^2 - 2.4V_o + 0.16 = 0 \rightarrow V_o = 68.6 mV$$

CHAPTER 9

Page 442

$$\frac{i_{C2}}{i_{C1}} = \exp\left(\frac{0.2V}{0.025V}\right) = 2.98 \times 10^3 \quad \frac{i_{C2}}{i_{C1}} = \exp\left(\frac{0.4V}{0.025V}\right) = 8.89 \times 10^6 \quad (2.98 \times 10^3)^2 = 8.88 \times 10^6$$

Page 444

The current must be reduced by 5 while the voltages remain the same.

$$I_{EE} = \frac{300\mu A}{5} = 60 \mu A \quad R_C = 5(2k\Omega) = 10 k\Omega$$

Page 445

$$I_B = \frac{I_E}{\beta_F + 1} \quad I_{B3} = \frac{92.9\mu A}{21} = 4.42 \mu A \quad I_{B4} = \frac{107\mu A}{21} = 5.10 \mu A$$

$$I_{B3}R_C = 4.42\mu A(2k\Omega) = 8.84 mV \ll 0.7 V \quad I_{B4}R_C = 5.10\mu A(2k\Omega) = 10.2 mV \ll 0.7 V$$

Page 447

$$V_H = 0 - 0.7 = -0.7 V \quad | \quad V_L = 0 - 0.2mA(2k\Omega) - 0.7V = -1.1 V$$

$$\Delta V = -0.7V - (1.1V) - 0.4 V \quad | \quad V_{REF} = \frac{-0.7V + (-1.10V)}{2} = -0.9 V$$

Page 449

$$NM_H = NM_L = \frac{0.4V}{2} - 0.025V \left[1 + \ln\left(\frac{0.4}{0.025} - 1\right) \right] = 0.107 V$$

Page 451

$$(i) P = 3.3V(0.3mA + 0.2mA) = 1.65mW \quad P = 3.3V(0.357mA + 0.2mA) = 1.84mW$$

$$NM_H = NM_L = \frac{0.6V}{2} - 0.025V \left[1 + \ln\left(\frac{0.6}{0.025} - 1\right) \right] = 0.20 V$$

(ii) From the graph, the VTC slope is -1 for $V_{IL} = -1.08 V$, $V_{OH} = -0.71 V$ and

$$V_{IH} = -0.91 V, \quad V_{OL} = -1.28 V. \quad NM_H = -0.71 - (-0.91) = 0.20 V. \quad NM_L = -1.08 - (-1.28) = 0.20 V$$

(iii) The voltages remain the same. Thus the currents must be reduced by a factor of 3,

and the resistor values must be increase by a factor of 3.

$$(v) R_{EE} = \frac{-1.7V - (-5.2V)}{0.20mA} = 17.5 k\Omega \quad I_E = \frac{-1.4V - (-5.2V)}{18 k\Omega} = 0.211 mA \quad R_{C1} = \frac{0.4V}{0.211mA} = 1.90 k\Omega$$

Page 452

(a) For all inputs low : $I_{EE} = \frac{-1 - 0.7 - (-5.2)}{11.7} \frac{V}{k\Omega} = 299\mu A$

$$\frac{\Delta V}{2} = V_H - V_{REF} = -0.7 - (-1) = 0.3 V \quad \Delta V = 0.6 V \quad R_{C2} = \frac{0.6V}{299\mu A} = 2.00 k\Omega$$

For an inputs high : $I_{EE} = \frac{-0.7 - 0.7 - (-5.2)}{11.7} \frac{V}{k\Omega} = 325\mu A \quad R_{C1} = \frac{0.6V}{325\mu A} = 1.85 k\Omega$

(b) Based upon analysis above, $R_C = \frac{0.6V}{325\mu A} = 1.85 k\Omega$

Page 453

For all inputs low : $I_{EE} = \frac{-1 - 0.7 - (-5.2)}{11.7} \frac{V}{k\Omega} = 299\mu A$

$$\frac{\Delta V}{2} = V_H - V_{REF} = -0.7 - (-1) = 0.3 V \quad \Delta V = 0.6 V \quad R_C = \frac{0.6V}{299\mu A} = 2.00 k\Omega$$

Page 454

$$R_E = \frac{V_E - (-V_{EE})}{0.3mA} = \frac{0 - 0.7 - (-5.2V)}{0.3} \frac{V}{mA} = 15.0 k\Omega$$

Page 455

(a) For $I_E = 0$, $v_O = -5.2 V$. (b) For $I_E = 0$, $v_O = -5.2V \frac{10k\Omega}{10k\Omega + 15k\Omega} = -2.08 V$

Page 456

(i) The transistor's power dissipation is $P = V_{CB}I_C + V_{BE}I_E = 5V \left(2.55mA \frac{50}{51} \right) + 0.7V(2.55mA) = 14.3 mW$

The total power dissipation in the circuit is $P = V_{CC}I_C + V_{EE}I_E = 5V \left(2.55mA \frac{50}{51} \right) + 5V(2.55mA) = 25.3 mW$

For $v_O = -3.7V$, $I_E = \frac{-3.7 - (-5)}{1300} - \frac{3.7}{5000} = 260 \mu A$. At the Q-point, $I_E = \frac{-0.7 - (-5)}{1300} - \frac{0.7}{5000} = 3.17 mA$

The transistor's power dissipation is $P = V_{CB}I_C + V_{BE}I_E = 5V \left(3.17mA \frac{50}{51} \right) + 0.7V(3.17mA) = 17.8 mW$

(ii) $-4V = -5.2V \frac{10k\Omega}{10k\Omega + R_E} \rightarrow R_E = 3.00 k\Omega$

$$I_E = \frac{5.2V}{3k\Omega} = 1.73 mA \quad I_E = \frac{-4 - (-5.2)}{3000} - \frac{4}{10000} = 0 \quad I_E = \frac{4 - (-5.2)}{3000} + \frac{4}{10000} = 3.47 mA$$

Page 458

Increase the value of each resistor by a factor of 10.

Page 461

$$R_C = \frac{\Delta V}{I_{EE}} = \frac{0.6V}{0.5mA} = 1.2k\Omega \quad \tau_p = 0.69(1.2k\Omega)(2pF) = 1.66 ns$$

$$P = 5.2V(0.5 + 0.1 + 0.1)mA = 3.64mW \quad PDP = 6.0 pJ$$

Page 464

For $v_O = V_H$, $I_C = 0$, and $P = 0$. $P = V_{DD}I_{DD} = 5V(2.43mA) = 12.1 mW$

Increase R by a factor of 10: $R = 10(2k\Omega) = 20k\Omega$.

Page 466

$$(i) \quad \Gamma = \exp\left(\frac{0.1}{0.0258}\right) = 48.2 \quad I_B \geq \frac{10A}{20} \left[\frac{1 + \frac{20}{0.1(48.2)}}{1 - \frac{11}{48.2}} \right] = 3.34 A \quad \beta_{FOR} = \frac{10A}{3.34A} = 3.00$$

$$(ii) \quad \alpha_R = \frac{0.2}{0.2 + 1} = \frac{1}{6} \quad I_B \geq \frac{10A}{20} \left[\frac{1 + \frac{20}{0.2(54.6)}}{1 - \frac{6}{54.6}} \right] = 1.59 A$$

$$(iii) \quad \Gamma = \exp\left(\frac{0.15}{0.025}\right) = 403 \quad I_B \geq \frac{10A}{20} \left[\frac{1 + \frac{20}{0.1(403)}}{1 - \frac{11}{403}} \right] = 0.769 A$$

$$(iv) \quad V_T = \frac{1.38 \times 10^{-23}(273 + 150)}{1.60 \times 10^{-19}} = 36.5 mV \quad V_{CEMIN} = 36.5mV \ln\left(\frac{0.05 + 1}{0.05}\right) = 111 mV$$

Page 467

$$\Gamma = 54.6 \quad \alpha_R = \frac{0.25}{1 + 0.25} = \frac{1}{5} \quad I_B \geq \frac{10mA}{40} \left[\frac{1 + \frac{40}{0.25(54.6)}}{1 - \frac{5}{54.6}} \right] = 1.08 mA \quad \beta_{FOR} = \frac{10mA}{1.08mA} = 9.24$$

Page 467

$$(i) \quad 1ns = 6.4ns \ln \left(\frac{1mA - I_{BR}}{\frac{2.5mA}{40.7} - I_{BR}} \right) \quad 1.169 = \frac{1mA - I_{BR}}{0.0614mA - I_{BR}} \rightarrow I_{BR} = -5.49 mA$$

$$(ii) \quad i_{C_{MAX}} = \frac{V_{CC} - V_{CE}}{\beta_F} \cong \frac{5-0}{2500} = 2.5mA \quad Q_{XS} = 6.4ns \left(1mA - \frac{2.5mA}{40.7} \right) = 6.01 pC$$

$$Q_F = i_F \tau_F = 2.5mA(0.25ns) = 0.625 pC \quad Q_{XS} \gg Q_F$$

Page 471

$$(i) \quad v_I = V_L = 0.15 V \quad I_{IL} = -\frac{5-0.95}{4000} = -1.01 mA \quad V_{BE2} = V_L + V_{CESAT1}$$

Using the value of V_{CESAT} in Fig.9.32, $V_{BE2} = 0.15 + 0.04 = 0.19 V$

$$\text{A better estimate is } V_{CESAT1} = 25mV \ln \left(\frac{2+1}{2} \right) = 10.1 mV$$

$$V_{BE2} = 0.15 + 0.010 = 0.16 V$$

$$(ii) \quad v_I = V_H = 5 V \quad I_{IH} = 2 \frac{5-1.5}{4000} = 1.75 mA \quad V_{BE2} = 0.8 V$$

$$\text{Using Eq. (5.29), } V_{BESAT} = 0.025V \ln \frac{0.875mA + \left(1 - \frac{2}{3}\right)(2.4mA)}{10^{-15} A \left[\frac{1}{40} + \left(1 - \frac{2}{3}\right) \right]} = 0.729 V$$

Page 477

$$(i) \quad 5V - N(2k\Omega)\beta_R I_B \geq 1.5V \quad I_B = \frac{5-1.5}{4000} = 0.875mA$$

$$\beta_R \leq \frac{3.5V}{5(2k\Omega)(0.875mA)} = 0.4 \quad \beta_R \leq \frac{3.5V}{10(2k\Omega)(0.875mA)} = 0.2$$

$$(ii) \quad I_{B2} = (2+1) \frac{5-1.5}{4000} = 2.63 mA \quad 2.43mA + N(1.01mA) \leq 28.3(2.63mA) \rightarrow N \leq 71$$

Page 479

$$v_I = V_L \text{ and } v_O = 0: I_{B4} = \frac{5 - V_{B4}}{1600} = \frac{5 - (0 + 0.7 + 0.7)}{1600} = 2.25 \text{ mA} \quad I_L = 41 I_{B4} = 92.3 \text{ mA}$$

$$5 - 1600 \frac{I_L}{41} - 0.7 - 0.7 \geq 3 \quad \frac{5 - (3 + 0.7 + 0.7)}{1600} = 0.375 \text{ mA} \quad I_L = 41 I_{B4} = 15.4 \text{ mA}$$

$$V_{CE} = 5 - 130 \Omega I_C - V_O = 5V - 130 \Omega (15.4 \text{ mA}) - 3.7 = -0.702V$$

Oops! - the transistor is not forward active. Assume saturation with $V_{CESAT} = 0.15V$.

$$I_L = I_B + I_C = \frac{5 - (0.8 + 0.7 + 3.0)}{1600} + \frac{5 - (0.15 + 0.7 + 3)}{130} = 9.16 \text{ mA}$$
