

Wrap Up



In this course, you have learned...

- Microelectronic devices that can provide gain (active)
 - Basic semiconductor physics
 - Operation principles, terminal I-V equations and circuit models of
 - PN-junction diode
 - BJT transistor
 - MOS transistor
- Special analysis techniques for microelectronic circuits
 - DC analysis (biasing)
 - Small signal analysis
- Diode circuits
 - Rectifiers
 - Regulators
 - DC-DC converters
 - Clipping & Clamping ckts
- BJT & MOS transistor circuits
 - Single transistor amplifiers
 - Differential amplifiers
 - Multi-vibrators
 - Logic circuits
- Feedback principles
 - Topologies
 - Stability analysis
 - Oscillators



PN Junction Diode

- Physical operation
 - Including the reverse-breakdown phenomenon
- Simplified circuit models
 - E.g., the 0.7V constant voltage drop model
- Zener-Diode and voltage regulator
- Half-wave, full-wave and bridge rectifiers
 - Advantages and disadvantages
- DC-DC converters
- Clipping and clamping circuits



Bipolar Junction Transistor

- Regions of operation: Cutoff, Saturation and Active
- I-V behaviors for the three regions:
 - Cutoff: $I_B=I_E=I_C=0$;
Voltages depend on external circuit
 - Saturation: $V_{BE}=V_{ON}$, $V_{CE}=V_{CESat}$;
Currents depends on external circuit
 - Active: $i_C=\beta i_B$, $i_C=\alpha i_E$,
- Non-ideal effects
 - Early Effect
 - Temperature dependence
 - Breakdown

$$i_C = I_S \exp\left(\frac{v_{BE}}{V_T}\right)$$




MOSFET

- Three regions of operation:
 - Cutoff: $V_{GS} < V_{TN}$ (for nmos, same below)
 - Triode or Linear: $V_{GS} \geq V_{TN}$, $V_{GD} \geq V_{TN}$
 - Saturation: $V_{GS} > V_{TN}$, $V_{GD} < V_{TN}$
- I-V equations in three regions
 - Square-law I-V behavior in saturation mode


$$i_D = \frac{1}{2} (\mu_n C_{ox}) \frac{W}{L} (v_{GS} - V_{TN})^2 \quad K_n = \mu_n C_{ox} \frac{W}{L}$$
$$K'_n = \mu_n C_{ox}$$

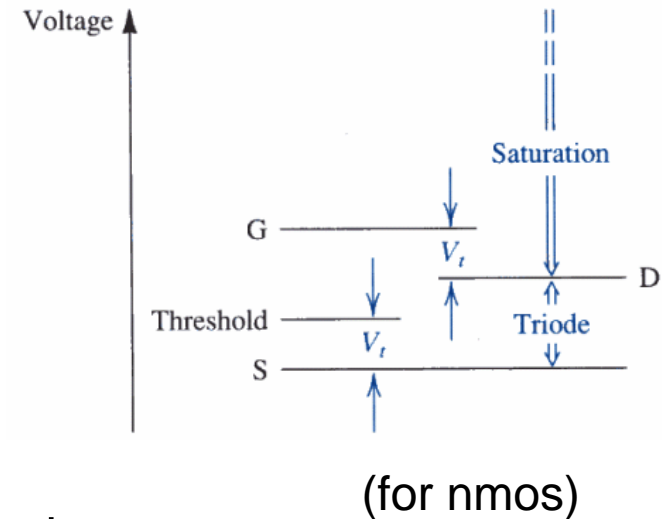- Non-ideal Effects
 - Channel length modulation
 - Body effect
 - Breakdowns and gate-breakdown protection



BJT Small Signal Model

Can also be βi_b

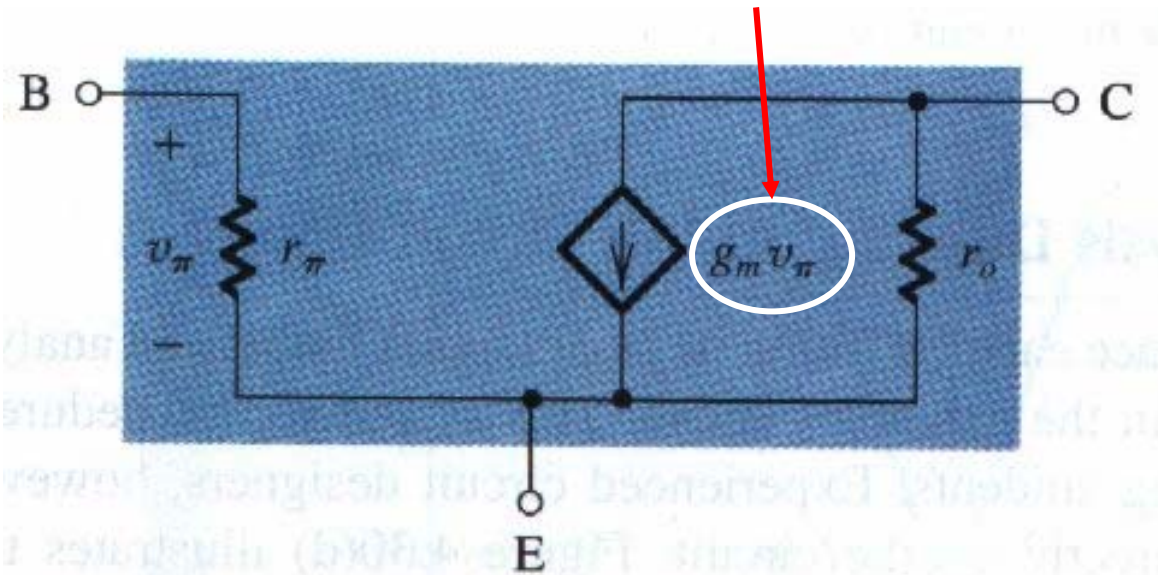


$$r_{\pi} = \frac{V_T}{I_B}$$

$$g_m = \frac{I_C}{V_T}$$

$$r_o = \frac{V_A + V_{CE}}{I_C} \approx \frac{V_A}{I_C}$$



MOSFET Small Signal Model

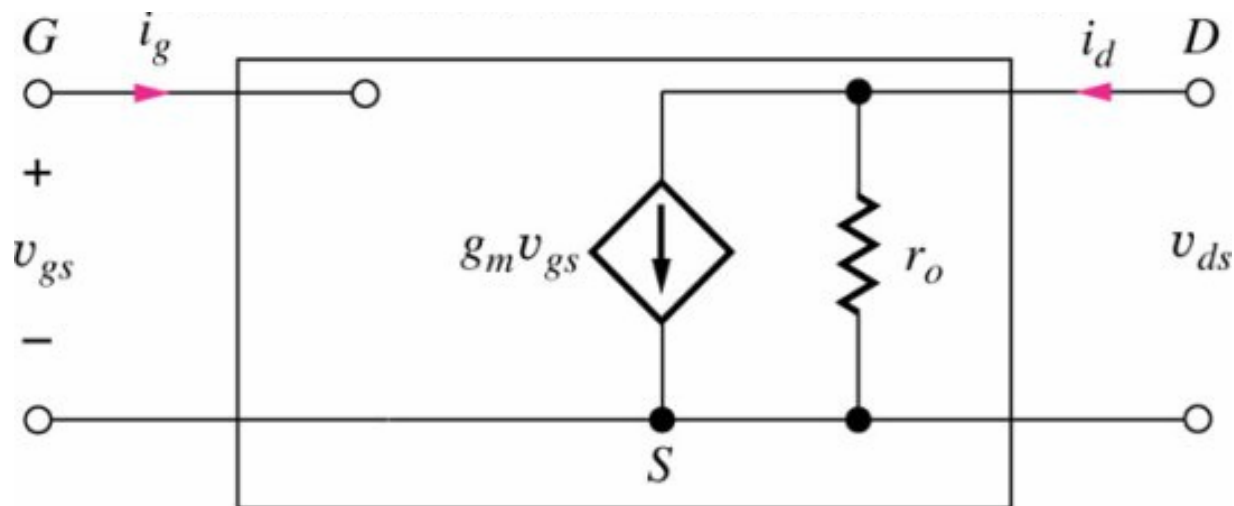

$$g_m = k'_n \frac{W}{L} (V_{GS} - V_t) = \sqrt{2k'_n} \sqrt{\frac{W}{L}} \sqrt{I_D} = \frac{I_D}{(V_{GS} - V_t)/2}$$

$$r_o = \frac{1 + \lambda V_{DS}}{\lambda I_D} \cong \frac{1}{\lambda I_D}$$



Single Stage Amplifiers

- For use as an amplifier
 - BJT operates in active region
 - MOSFET operates in saturation region
- Amplifiers need a stable biasing point
 - Four-resistor bias network
 - Current mirror
- Basic amplifier configurations and their properties
 - Common-emitter/Common-source
 - Effect of emitter/source resistor
 - Common-base/Common-gate
 - Emitter/Source follower



Multivibrators

- A multivibrator is used to implement simple **two-state systems** such as oscillators, timers and flip-flops.
- Three types:
 - **Astable** – neither state is stable.
Applications: oscillator, etc.
 - **Monostable** - one of the states is stable, but the other is not;
Applications: timer, etc.
 - **Bistable** – it remains in either state indefinitely.
Applications: flip-flop, etc.



Differential Amplifier

- Purpose:
 - To amplify the difference between two input voltages
- Properties:
 - Effectively a single-stage CS/CE amplifier
 - No bypass capacitor is needed to produce emitter ac ground for differential mode inputs
 - Common-mode signal is not amplified
 - CMRR measures the ability to reject CM signals
- Half-circuit analysis technique
 - Common-mode and differential-mode equivalent half circuits



Output Stage

- Class A: highest linearity, lowest power efficiency
- Class B: lowest linearity, highest power efficiency
- Class AB: linearity better than that of Class B, power efficiency close to that of Class B, but lower.





Frequency Response of Amplifiers

- Amplifiers' gain depends on frequency
 - b/c the impedance of capacitors depends on frequency
- High-frequency models for BJT and MOSFET
 - Device capacitors added
- Low frequency response
 - Determined by coupling and bypass capacitors
 - Can be estimated by SCTC method
- High frequency response
 - Determined by internal capacitors of transistors
 - Can be estimated by OCTC method
- Mid-band gain
 - Calculated with circuit capacitors short-circuited and device capacitors open-circuited



Bode Plot
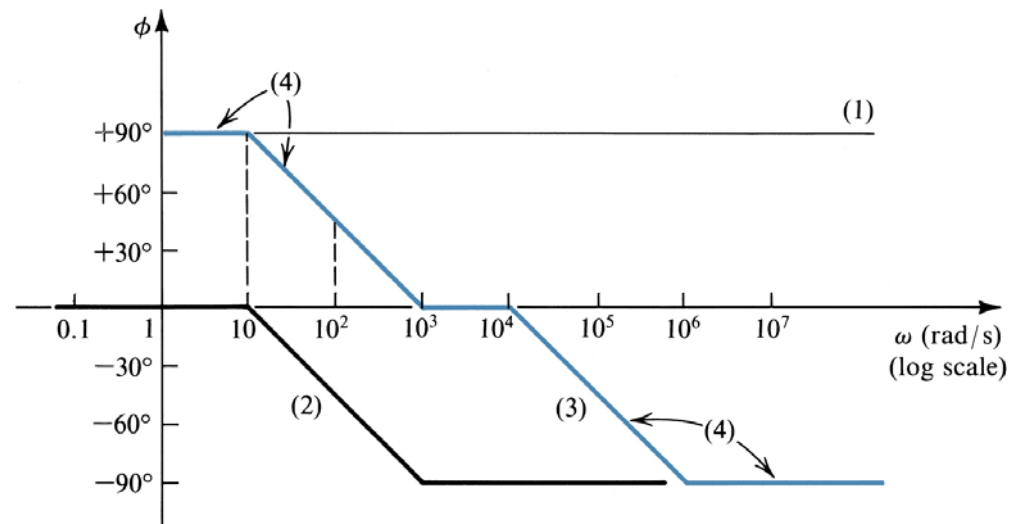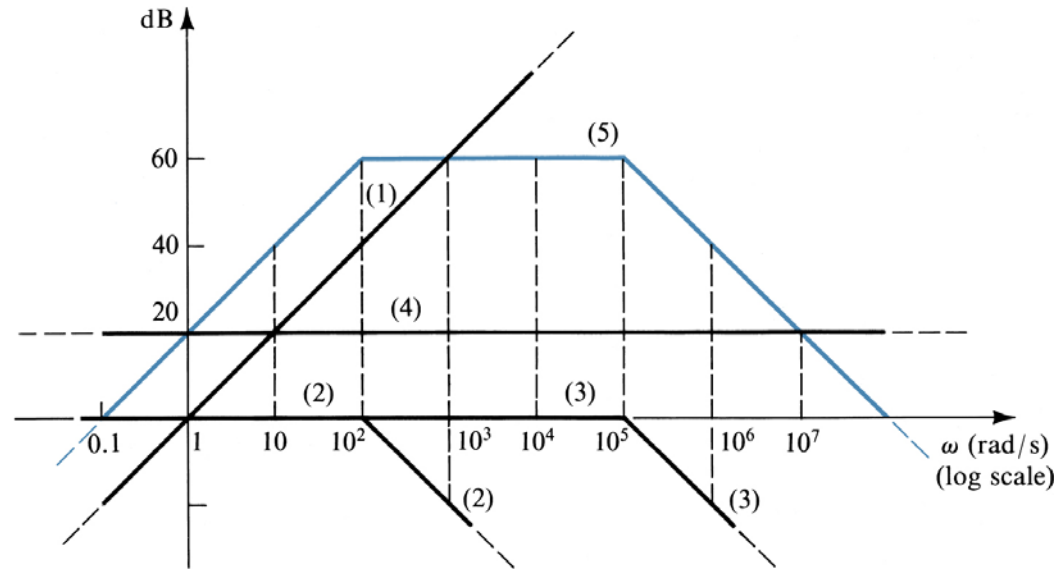
$$T(s) = \frac{10s}{(1 + s/10^2)(1 + s/10^5)}$$



Feedback

- Feedback amplifiers combine the advantages of both active and passive circuits:
 - It can provide gain (advantage of active circuits)
 - The gain can be accurate (advantage of passive circuits)
- Properties of negative feedback amplifier
 - Gain variation is reduced
 - Bandwidth is extended
 - Non-linearity is reduced
- Four topologies
- Stability can be determined by
 - Nyquist plot
 - Root locus diagram
 - Bode plot (phase and gain margins)
- Positive feedback is used in oscillator circuits



Digital Circuits

- CMOS logic circuits (Inverter, NAND, NOR)
 - Transistor operates as a switch
 - Either in cutoff mode or triode mode
 - Performance parameters
 - Dynamic power consumption

$$P = fCV_{DD}^2$$

- Propagation delay (speed)

$$t_p \propto \frac{1}{\left(\frac{W}{L}\right)}$$

$$t_p \propto C_{load}$$



Final Examination:

25 April 2008, Friday
9:30am – 11:30am
Sir Run Run Shaw Hall

Closed-book, closed-notes.

Unlike last year, no equations sheet will be provided!

But you can expect the questions to be less complex.

