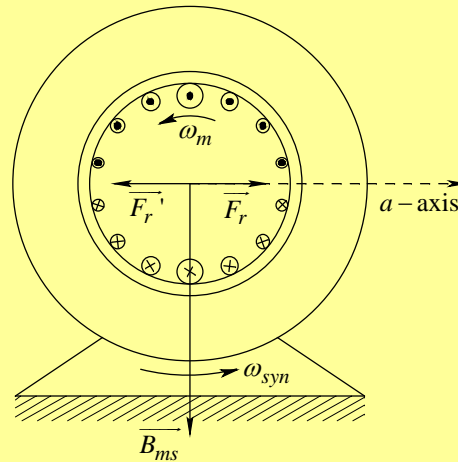


Induction Motors: Balanced, Sinusoidal Steady State Operation

- ◆ Generator Operation
- ◆ Including Rotor Leakage Inductance
- ◆ Per-Phase Equivalent Circuit
- ◆ Determining Equivalent Circuit parameters

Generator (Regenerative Braking) Mode




- ❑ For generation or for braking – in either case rotor speed exceeds synchronous speed,
 $\omega_m > \omega_{syn}$
- ❑ $\omega_{slip} < 0$
 - Bar voltage polarities reversed
 - Rotor currents and mmf reversed
 - Reflected rotor currents and mmf reversed
 - Torque reversed


Rotor Leakage Inductance (cont...)

- ❑ Effect of rotor leakage inductance is to reduce T_{em} at high slip
- ❑ Rotor leakage inductance is often neglected when motor is operating near synchronous speed (below the rated torque)


Per-Phase Equivalent Circuit

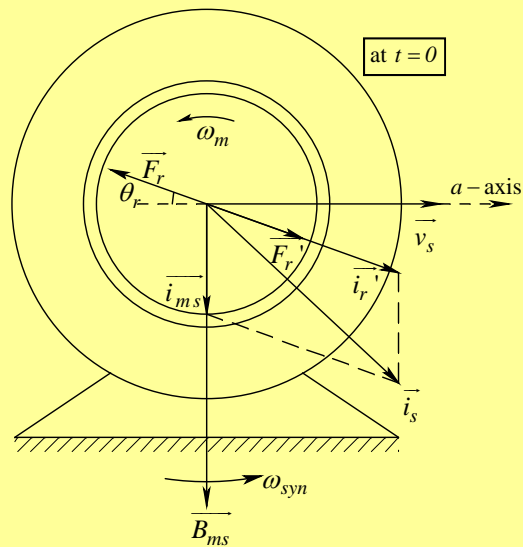

Space Vectors

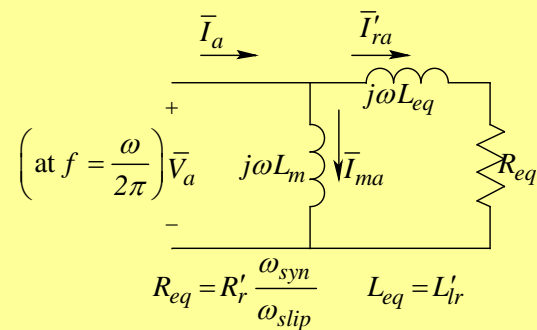


Equivalent Circuit

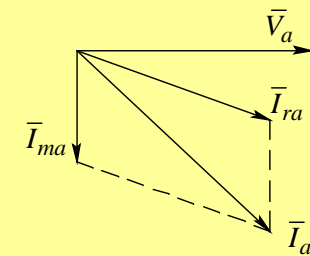


Phasor Diagram

- Includes rotor leakage inductance
- Does not include stator leakage inductance or resistance
- R_{eq} depends on slip

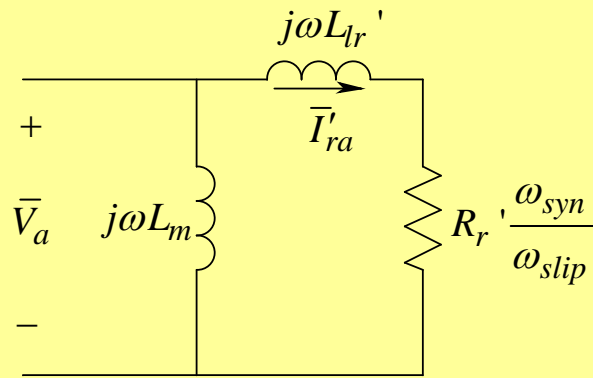Power Into Rotor – Power Lost In Rotor – Power Out Of Rotor



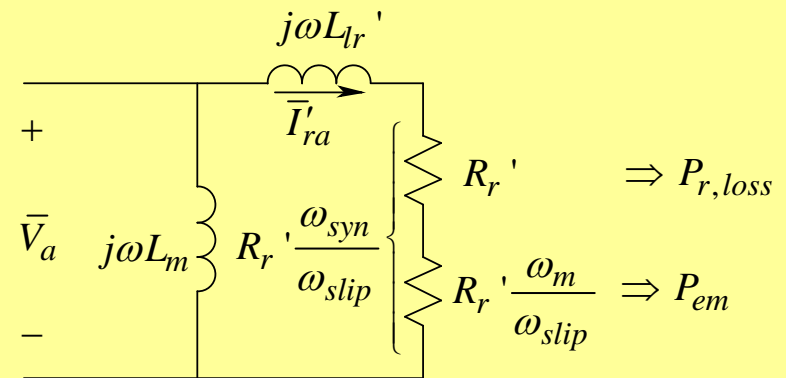
Power in resistor is power into the rotor circuit




Resistor split to indicate rotor loss and mechanical power

- ❑ Power in equivalent resistance represents power entering rotor across air gap
- ❑ Depending on slip, some or all of this power becomes losses in the rotor

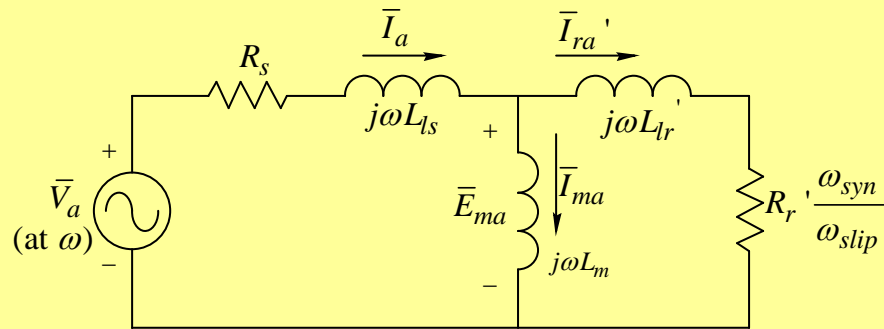Stator Winding Resistance and Leakage Inductance



Equivalent Circuit

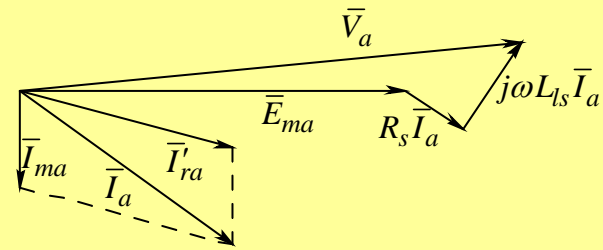


Phasor Diagram


Motor Tests

- ❑ DC – Resistance Test (R_s)
- ❑ No Load Test (L_m)
- ❑ Blocked Rotor Test (R'_r, L_{ls}, L'_{lr})


No Load Test (L_m)

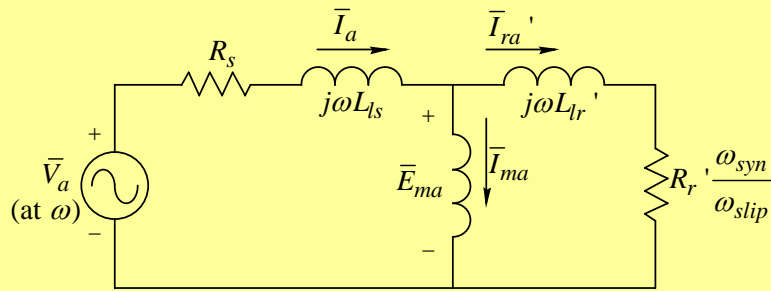

Equivalent Circuit

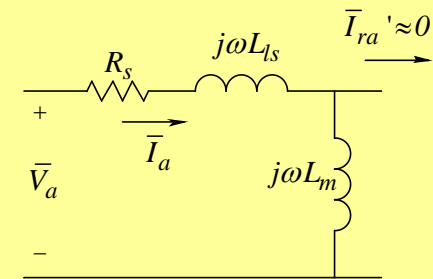

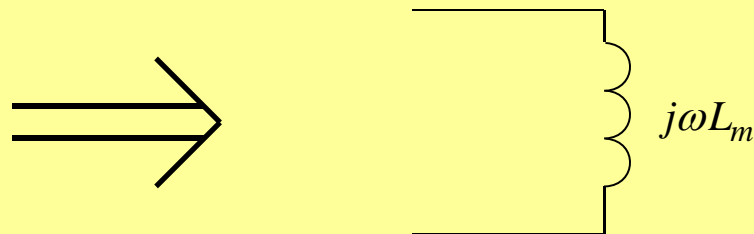
Equivalent Circuit under no load conditions
 $(\omega_{slip} = 0 \therefore R_{eq} = \infty)$




Approximate Circuit
 $(L_m \gg L_l) \quad (R_s \text{ negligible})$

- Under no load conditions the equivalent circuit is dominated by the magnetizing inductance

Blocked Rotor Test (L_l)

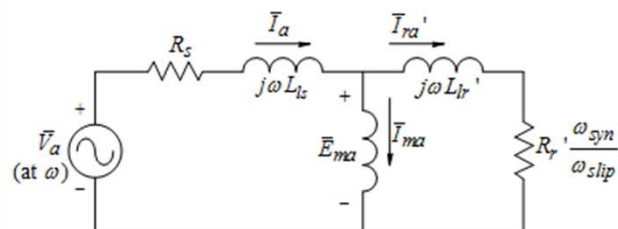

Equivalent Circuit

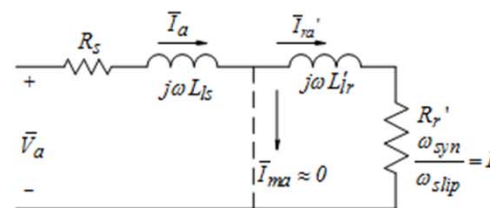

Approximate Circuit With Rotor Blocked

($R_{eq} \ll \omega L_m$) and ($\omega L_{lr}' \ll \omega L_m$)

- With the rotor blocked, the magnetizing inductance is nearly shorted out and can be neglected
- Measurements give real power (into R_s and R_r') and reactive power (into L_{ls} and L_{lr}')
- R_r' can be found since R_s was previously determined through the DC test
- To find L_{ls} and L_{lr}' we can often assume that $L_{ls} = \frac{2}{3} L_{lr}'$

Summary

- ◆ Generator Operation
- ◆ Including Rotor Leakage Inductance
- ◆ Per-Phase Equivalent Circuit
- ◆ Determining Equivalent Circuit parameters