
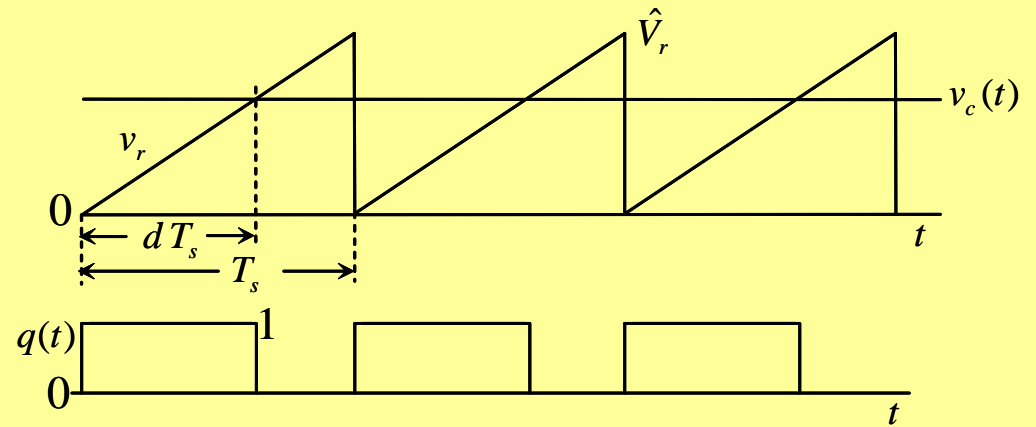


Average Representation of a Switching Power-Pole

Switching information is removed:


- Design the feedback controller
- Studying the dynamic behavior
 - Much faster simulation

Average Representation of PWM Block:

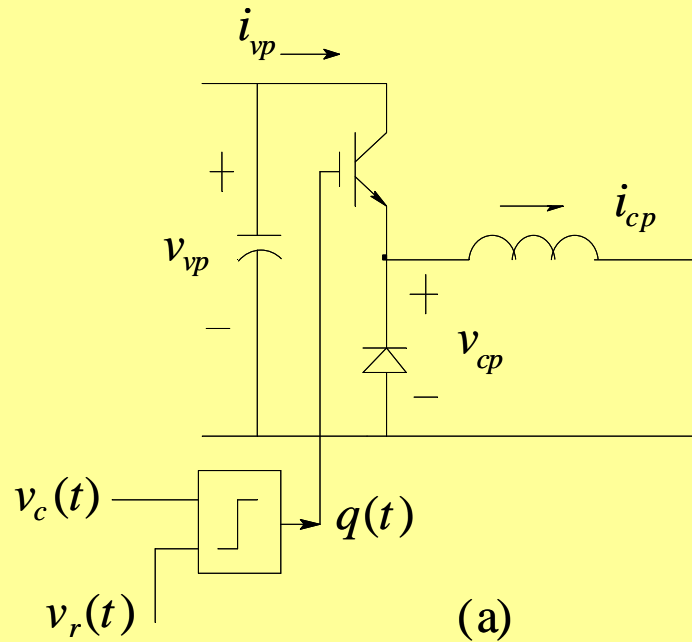

$$v_c(t) \longrightarrow \left[\frac{1}{\hat{V}_r} \right] \longrightarrow d(t) = \frac{v_c(t)}{\hat{V}_r}$$

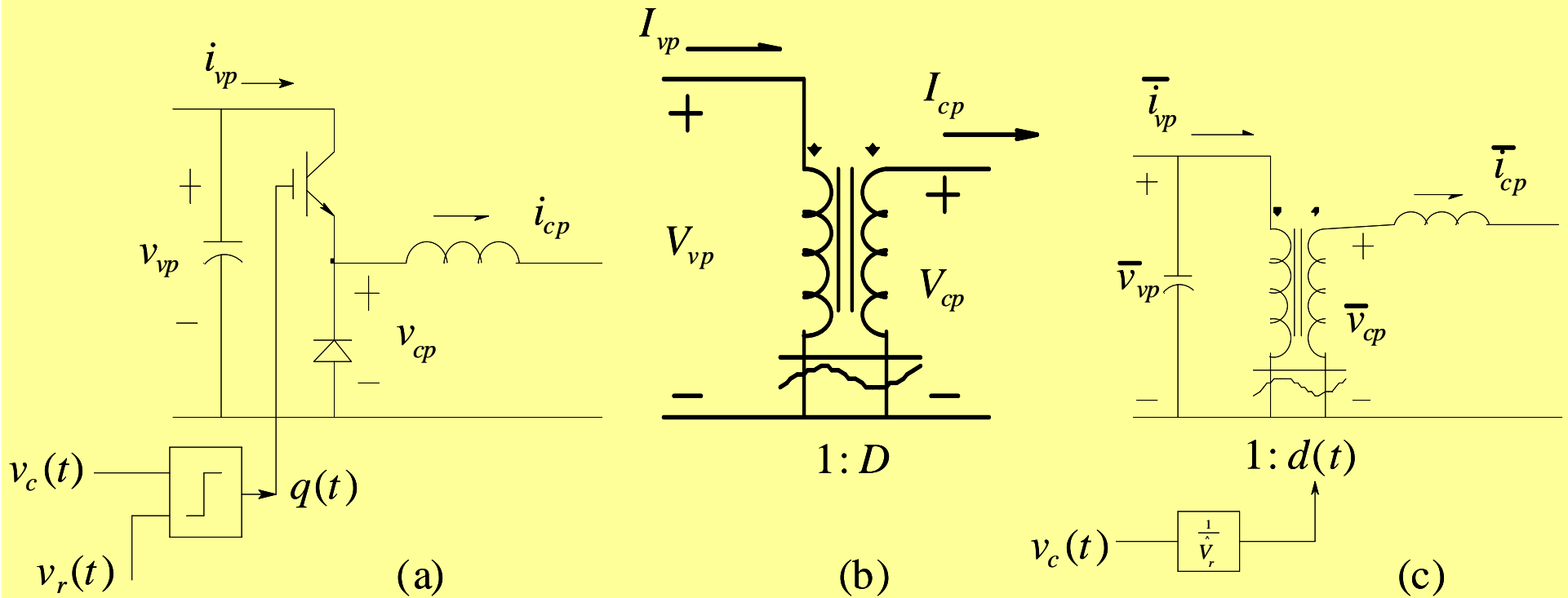Average Representation of Switching Power-Pole in CCM:




$$V_{cp} = DV_{vp}$$

$$I_{vp} = DI_o$$


$$\bar{v}_{cp}(t) = d(t)\bar{v}_{vp}(t)$$

$$\bar{i}_{vp}(t) = d(t)\bar{i}_{cp}(t)$$

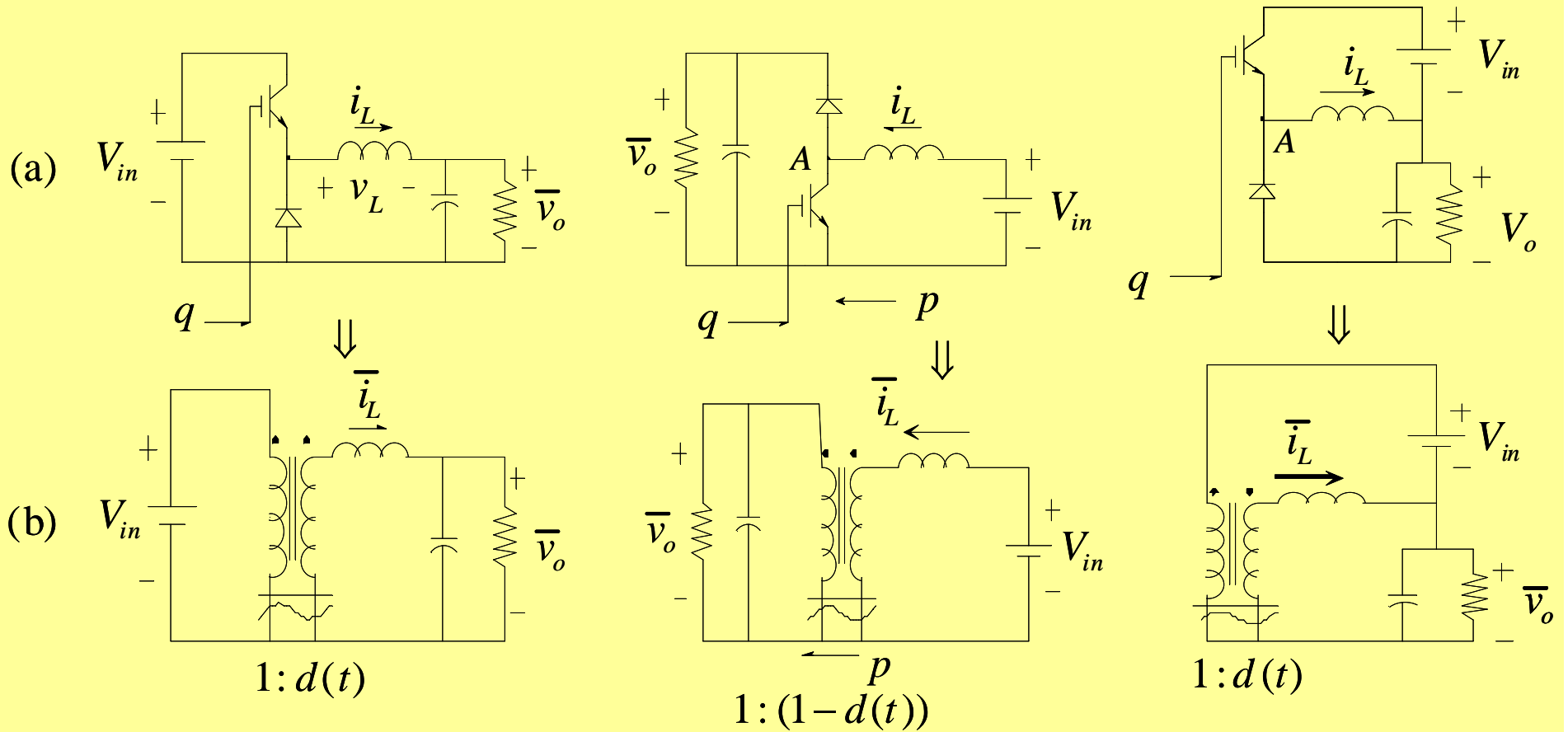
Average dynamic representations of three dc-dc converters in CCM:



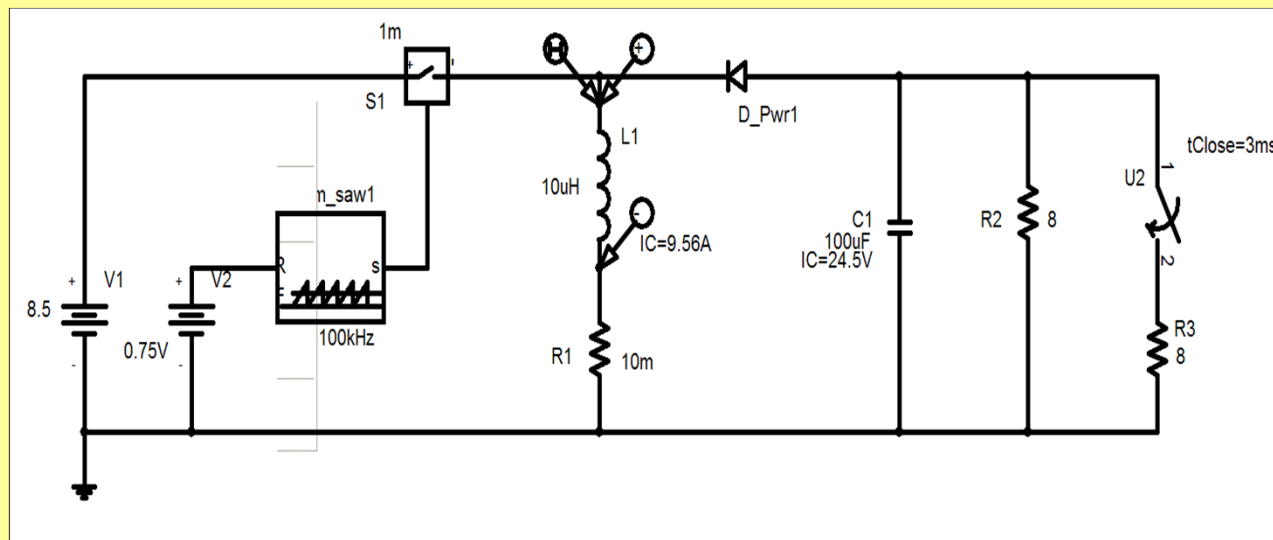
PSpice Modeling (Switching Representation):




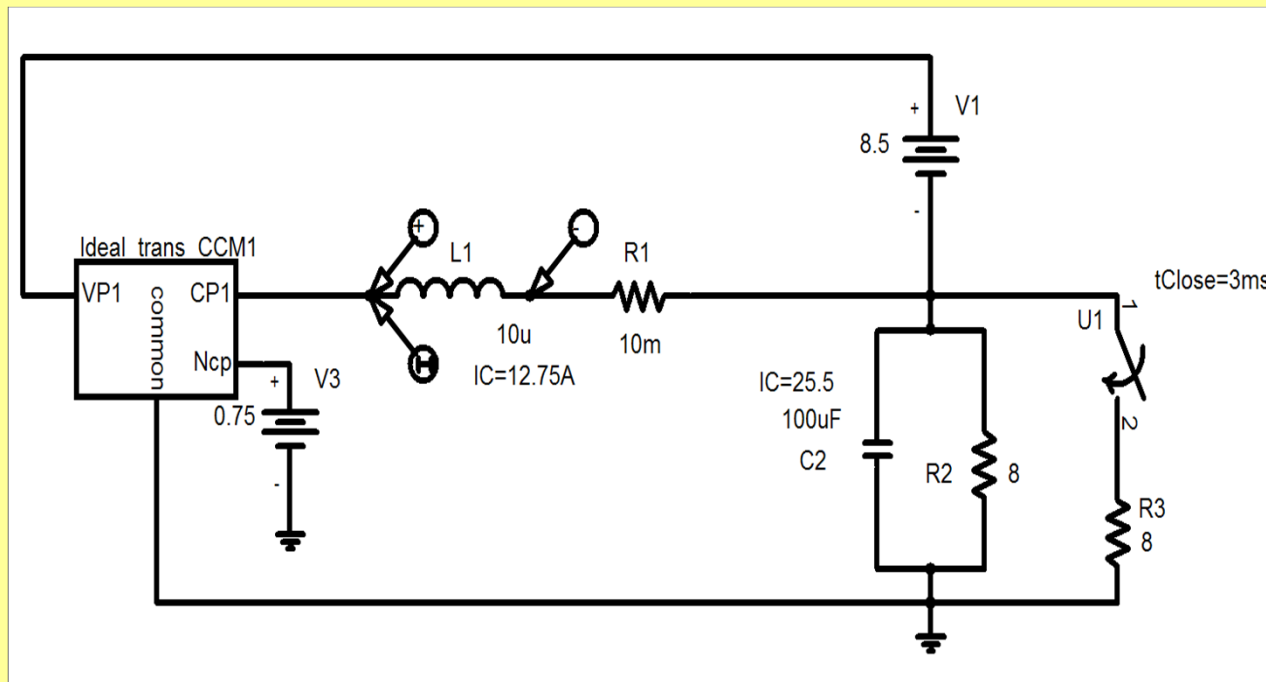
PSpice Modeling (Average Representation):



Simulation Results

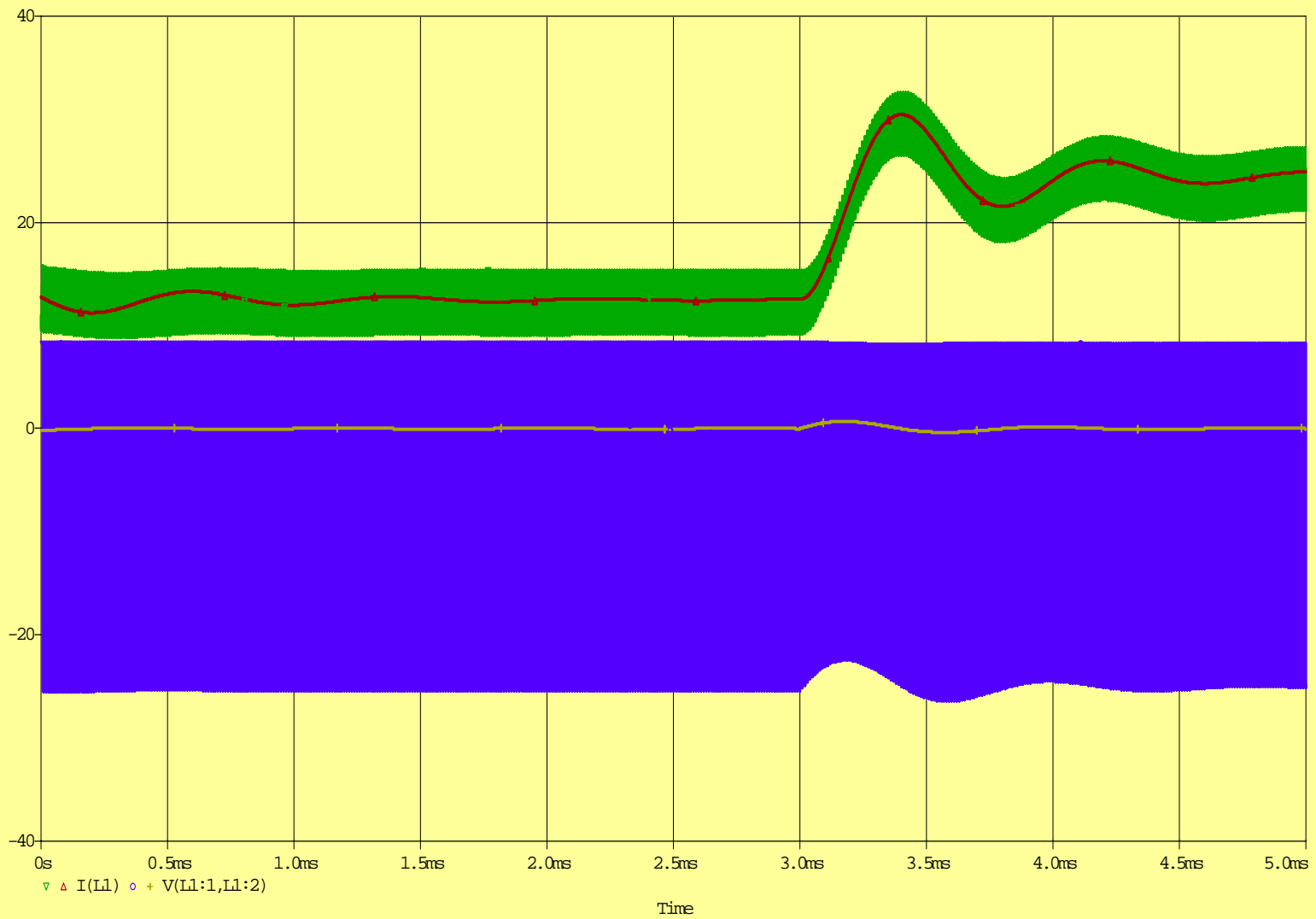

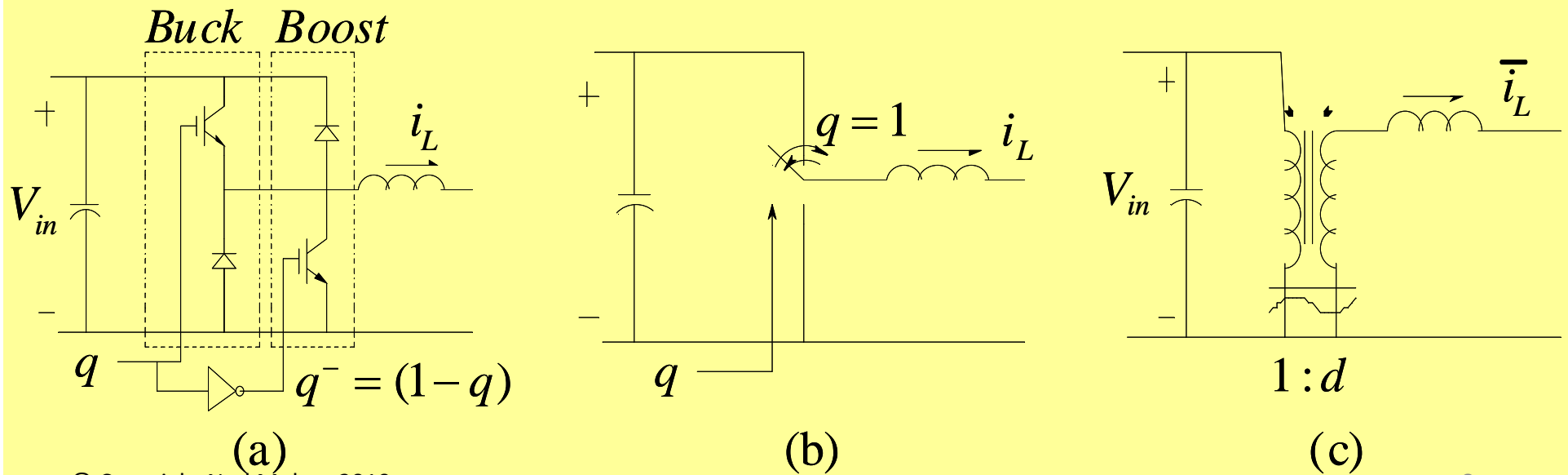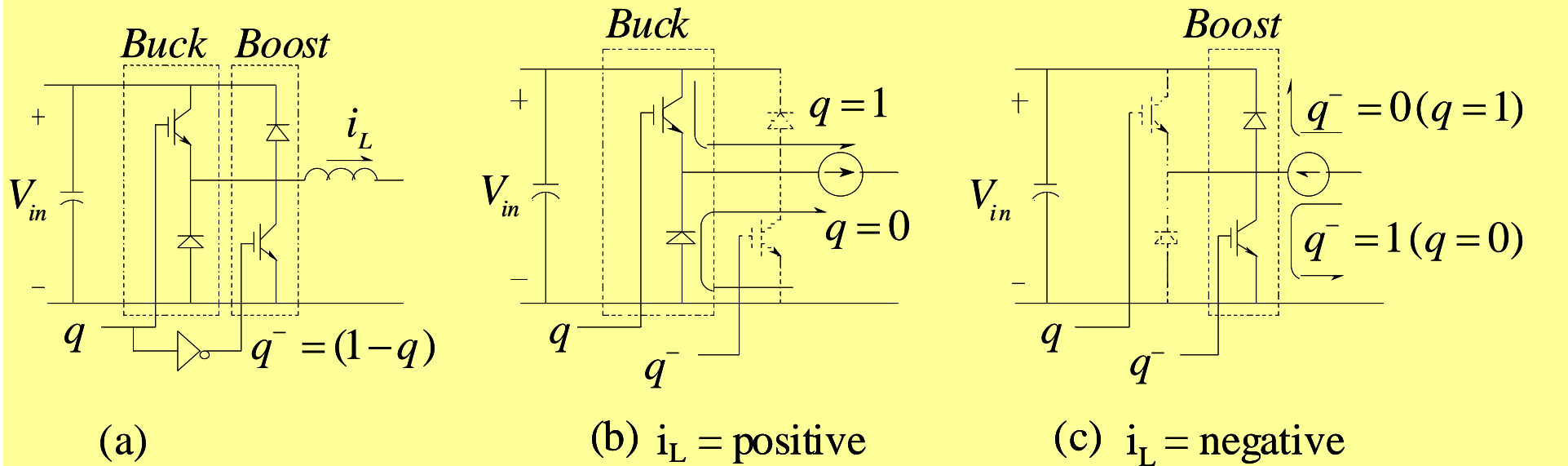Average representation of a bi-directional switching power-pole:



Summary

- Average representation of a switching power-pole
 - Developing the feedback controller
 - Studying the dynamic behavior
 - Much faster simulation