
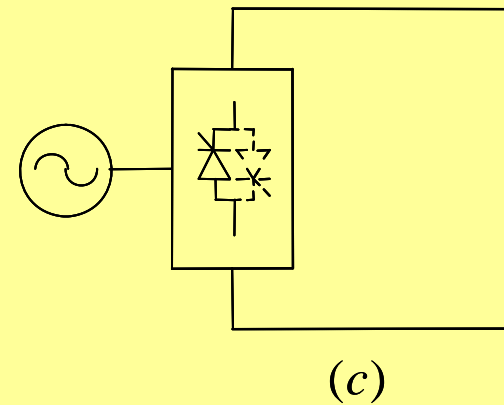
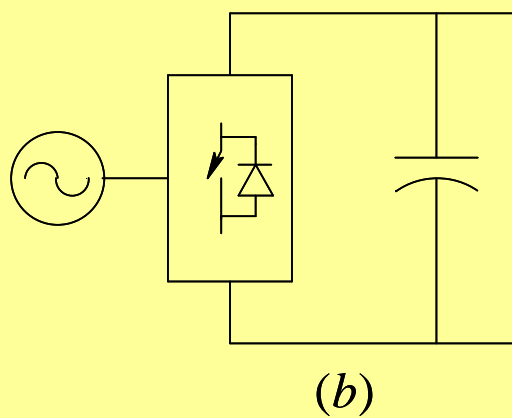


Diode Rectification of Utility Input


- Single-Phase Rectifiers
- Three-Phase Rectifiers

Types of Rectifier Front-Ends

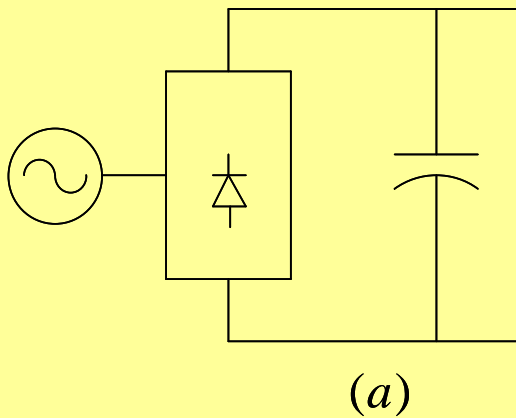


- Diode-bridge rectifiers
- Switch-mode converters
- Thyristor converter

Single-Phase, Diode-Bridge Rectifier

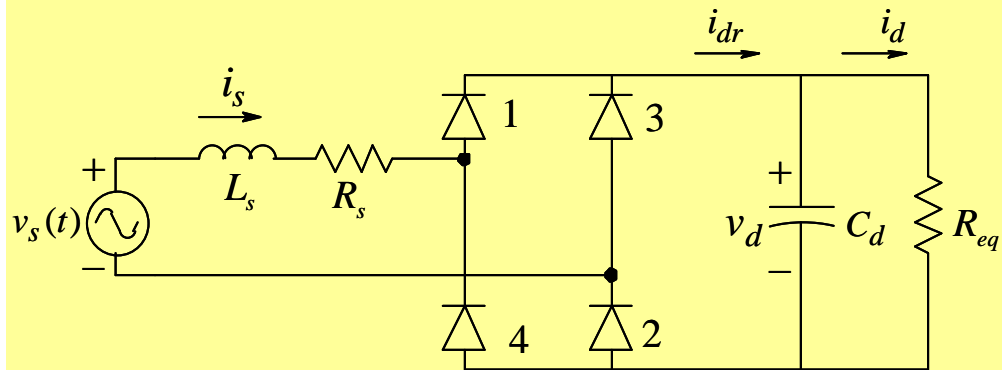



(a)

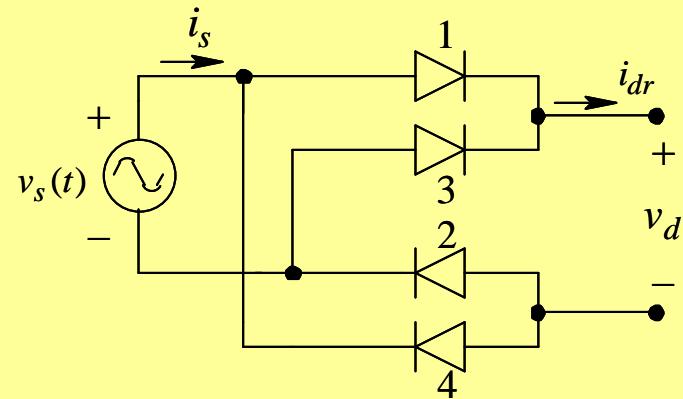



(b)

- ❑ Power levels up to 1-2 kW
- ❑ Current drawn from utility in short pulses

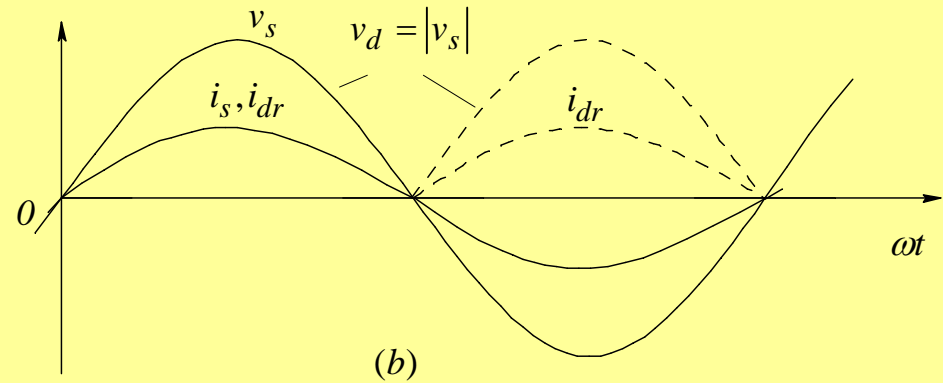
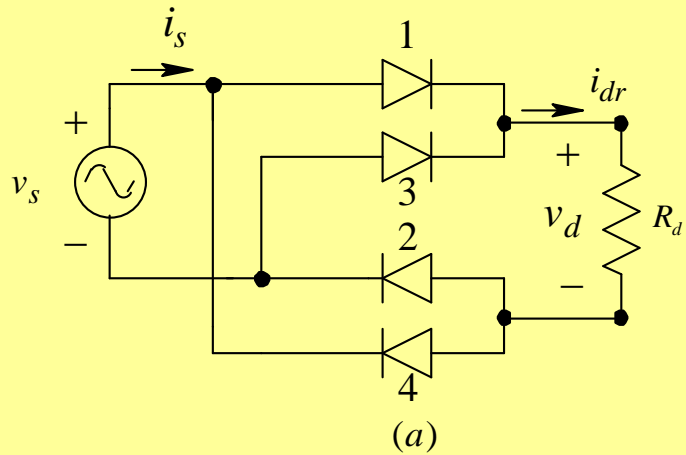
Full-bridge diode rectifier with resistive load



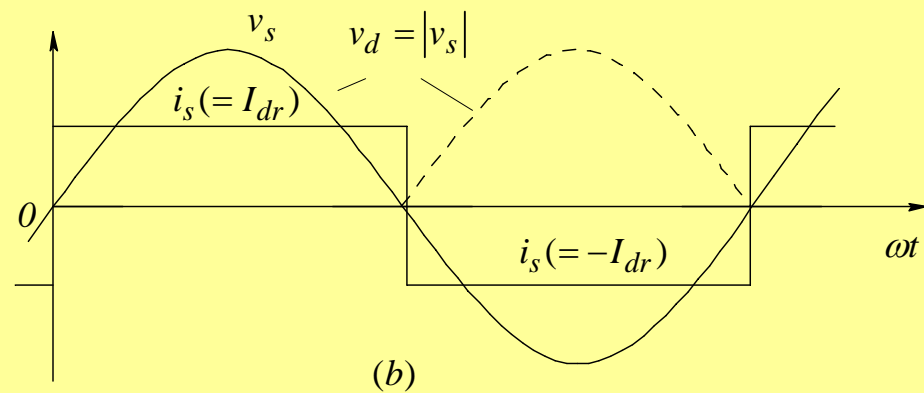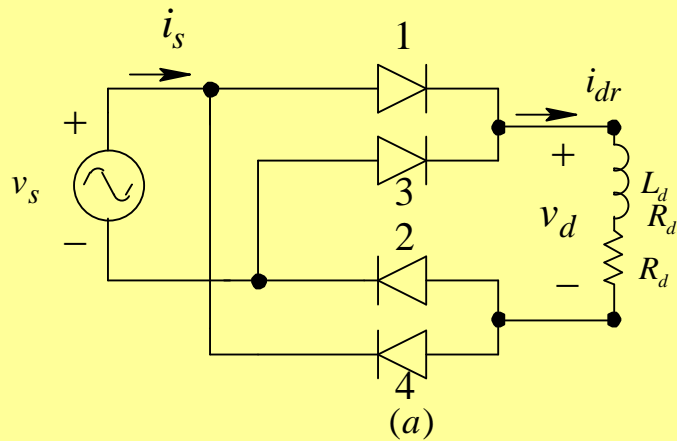
Full-bridge diode rectifier with a highly inductive load




Peak-Charging Circuit

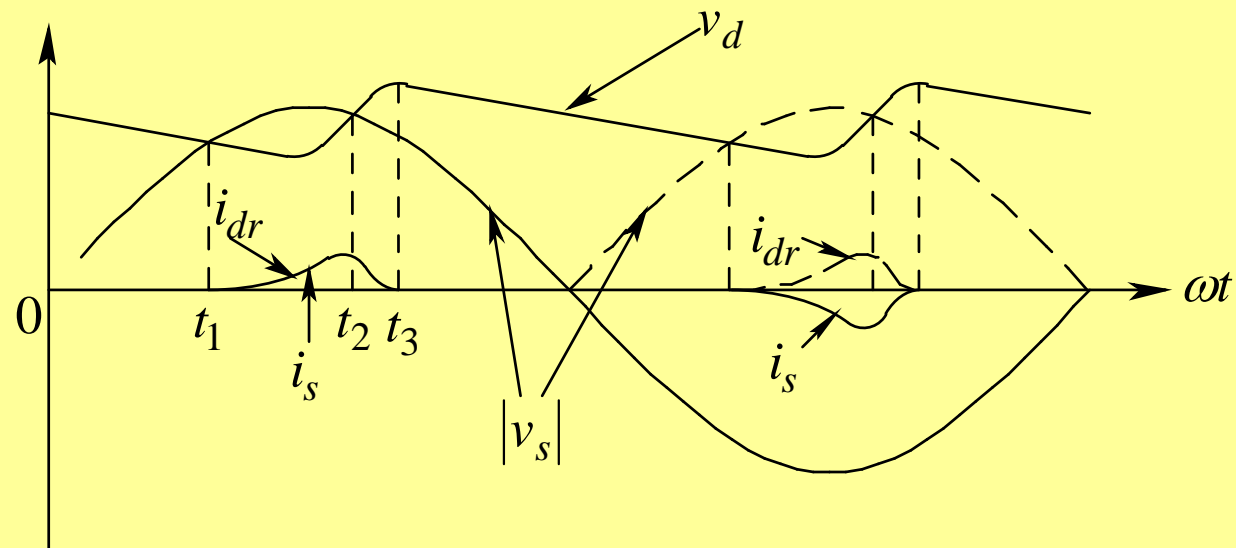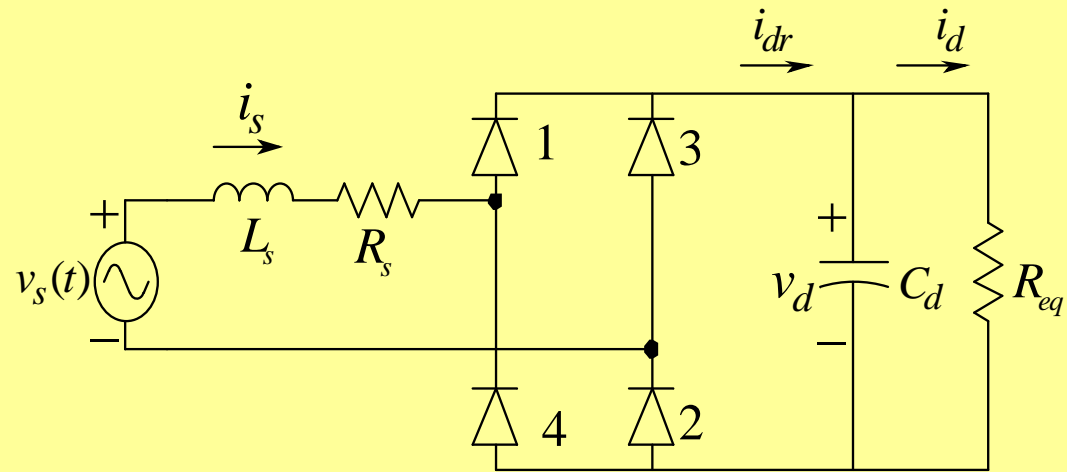



PSpice Modeling:

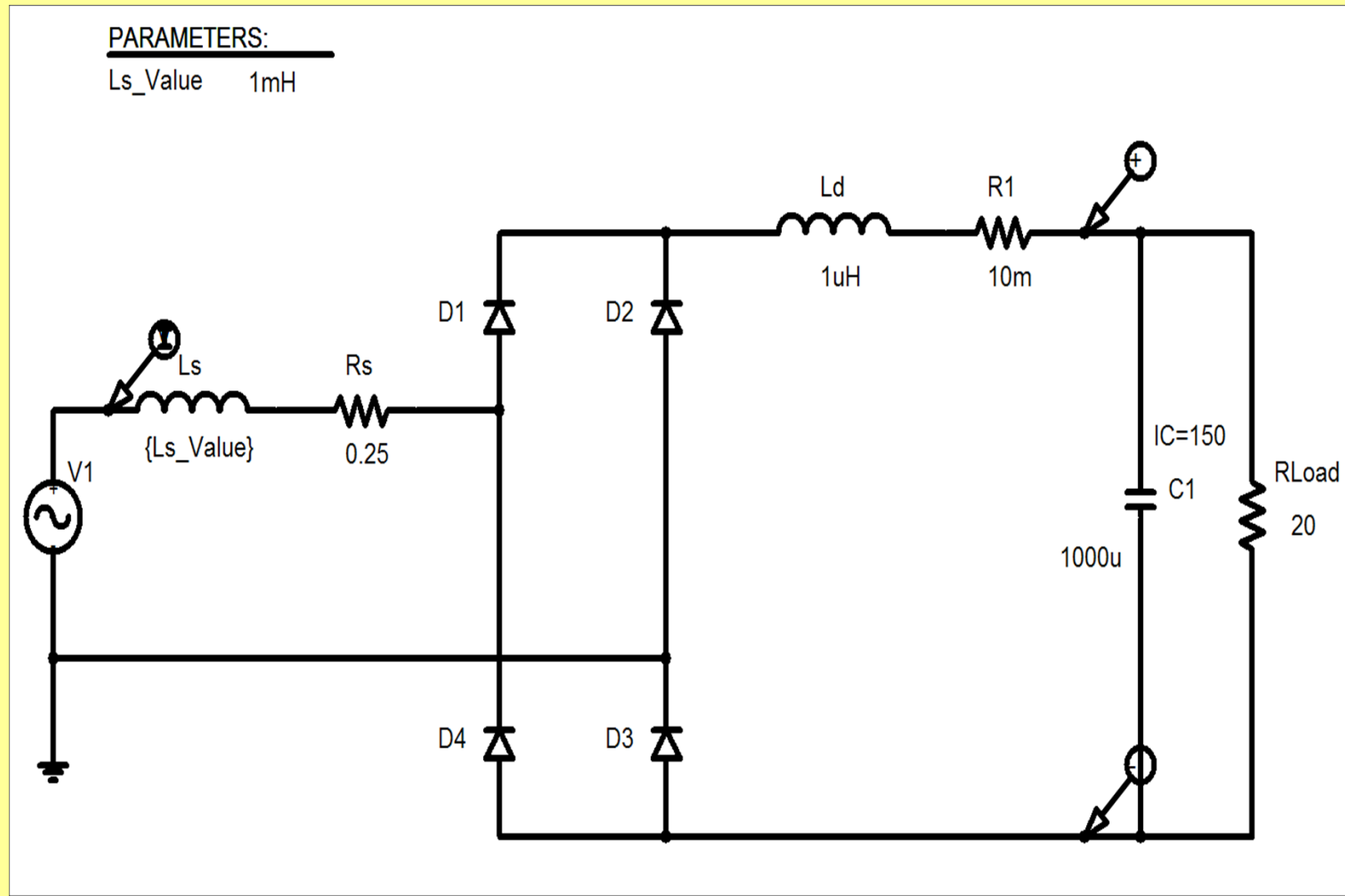


Simulation Results

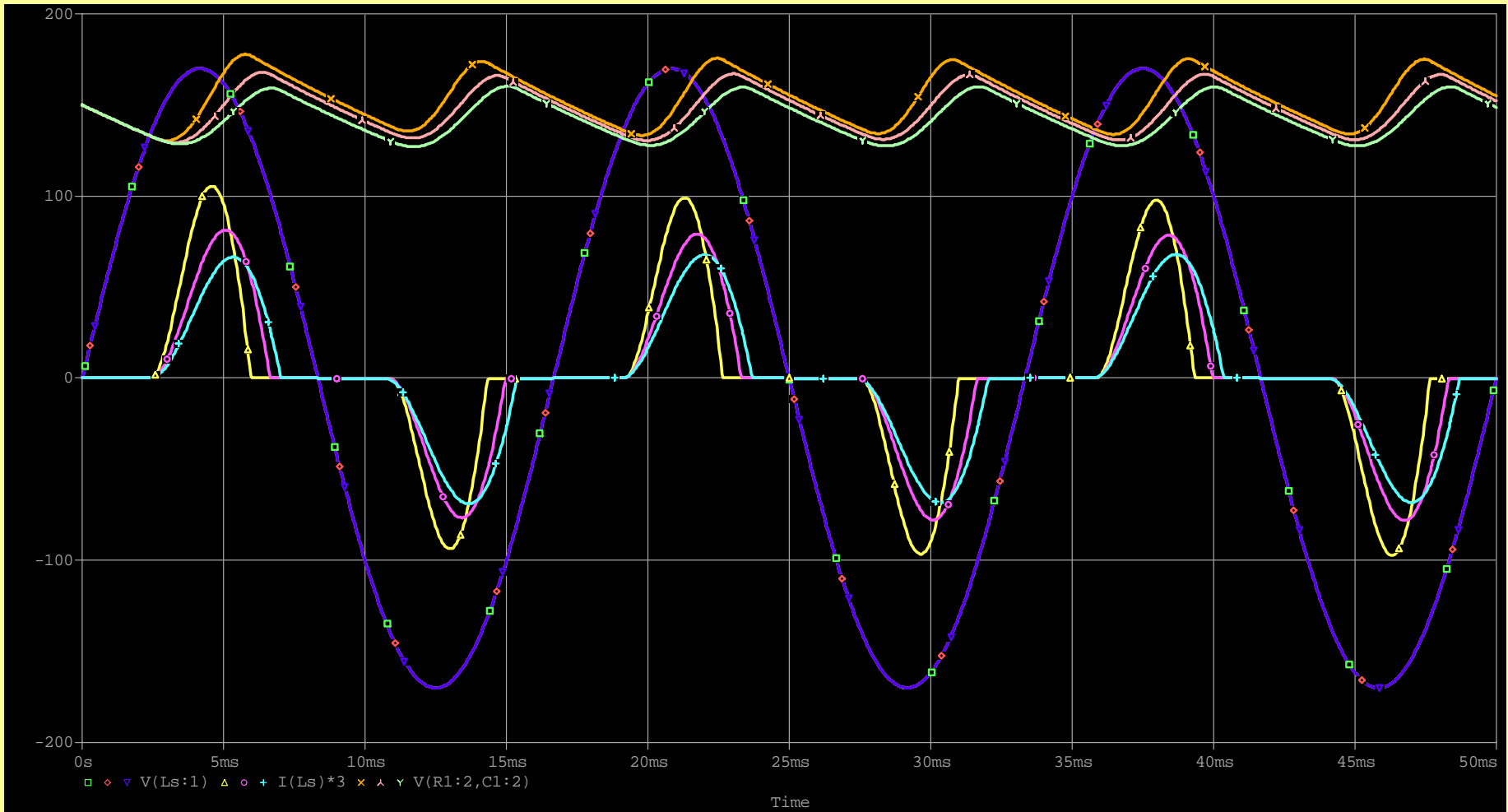




Three-Phase, Diode- Bridge Rectifier

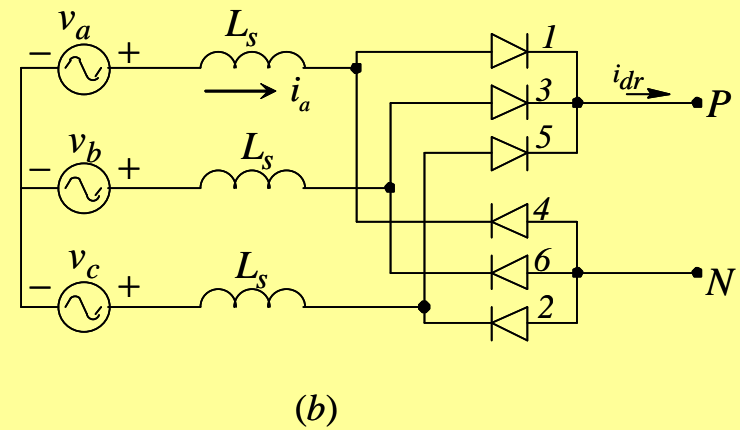
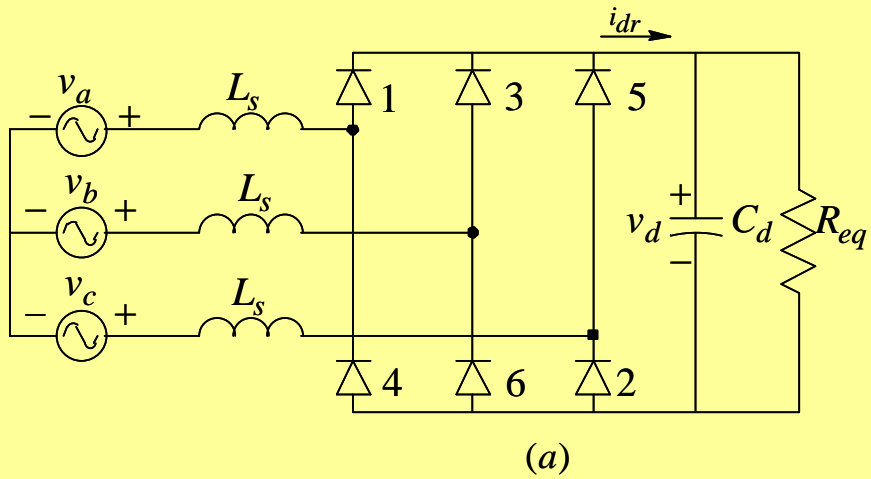


Voltage and Current Without C_d

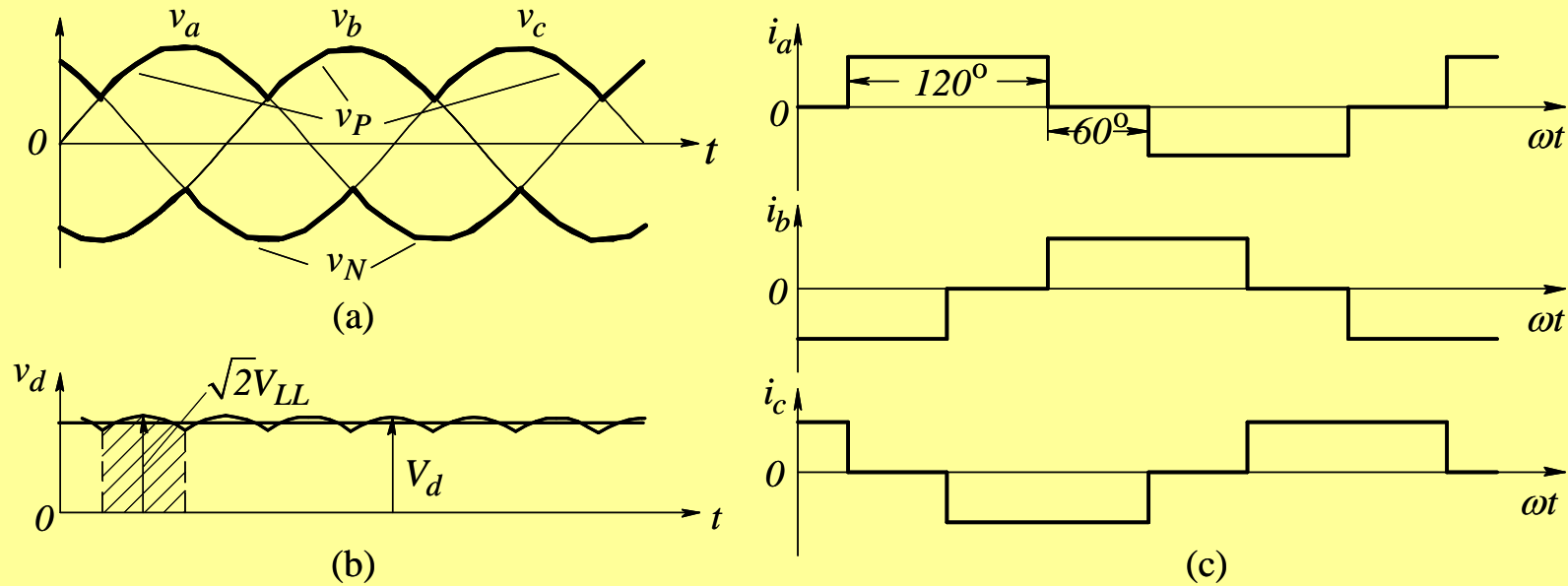


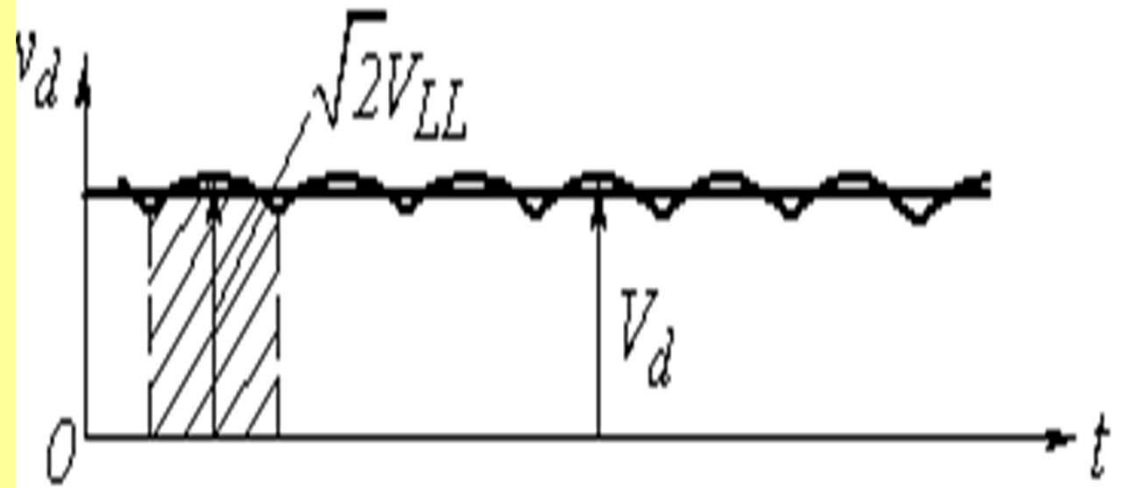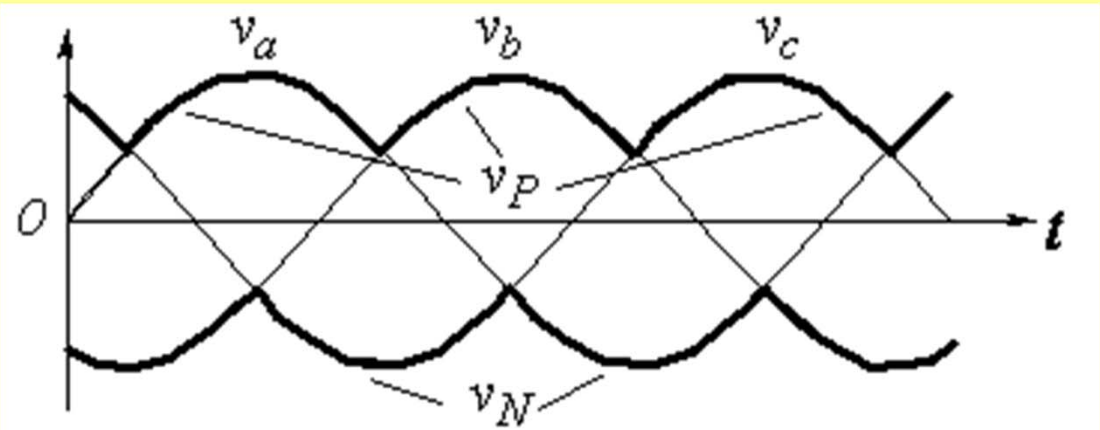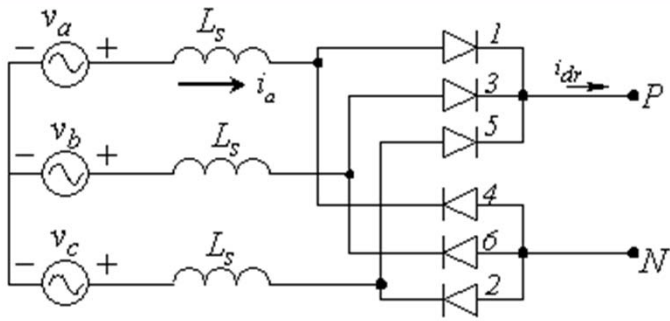- ❑ v_P follows whichever phase voltage is most positive at any moment
- ❑ v_N follows whichever phase voltage is most negative at any moment
- ❑ Without C_d , phase currents flow for a full 120° duration




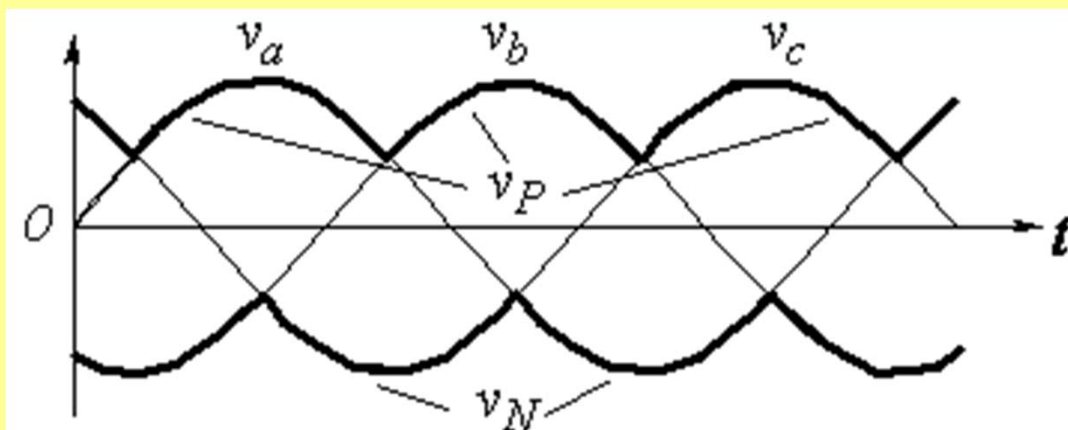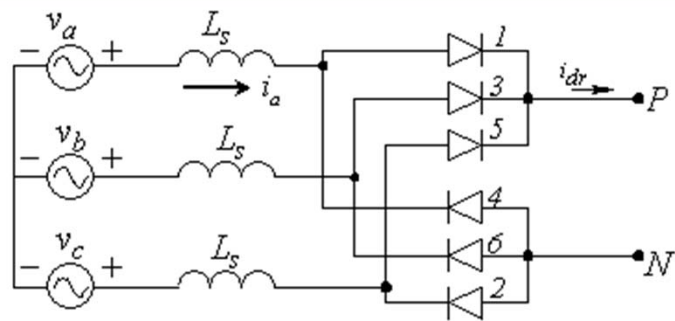


(a)


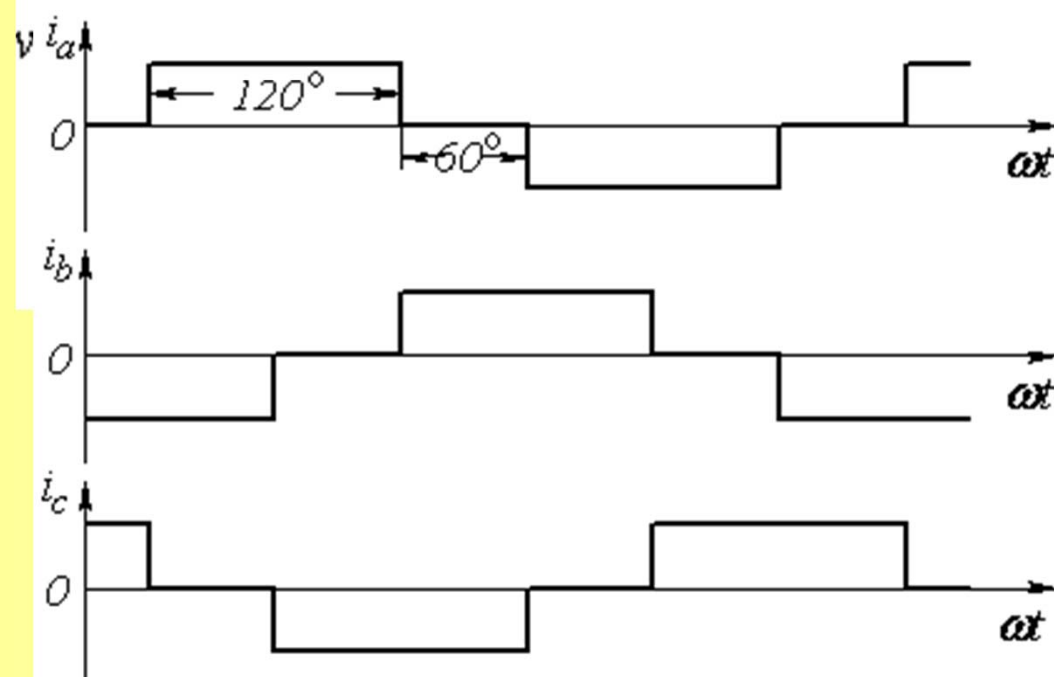


PSpice Modeling:

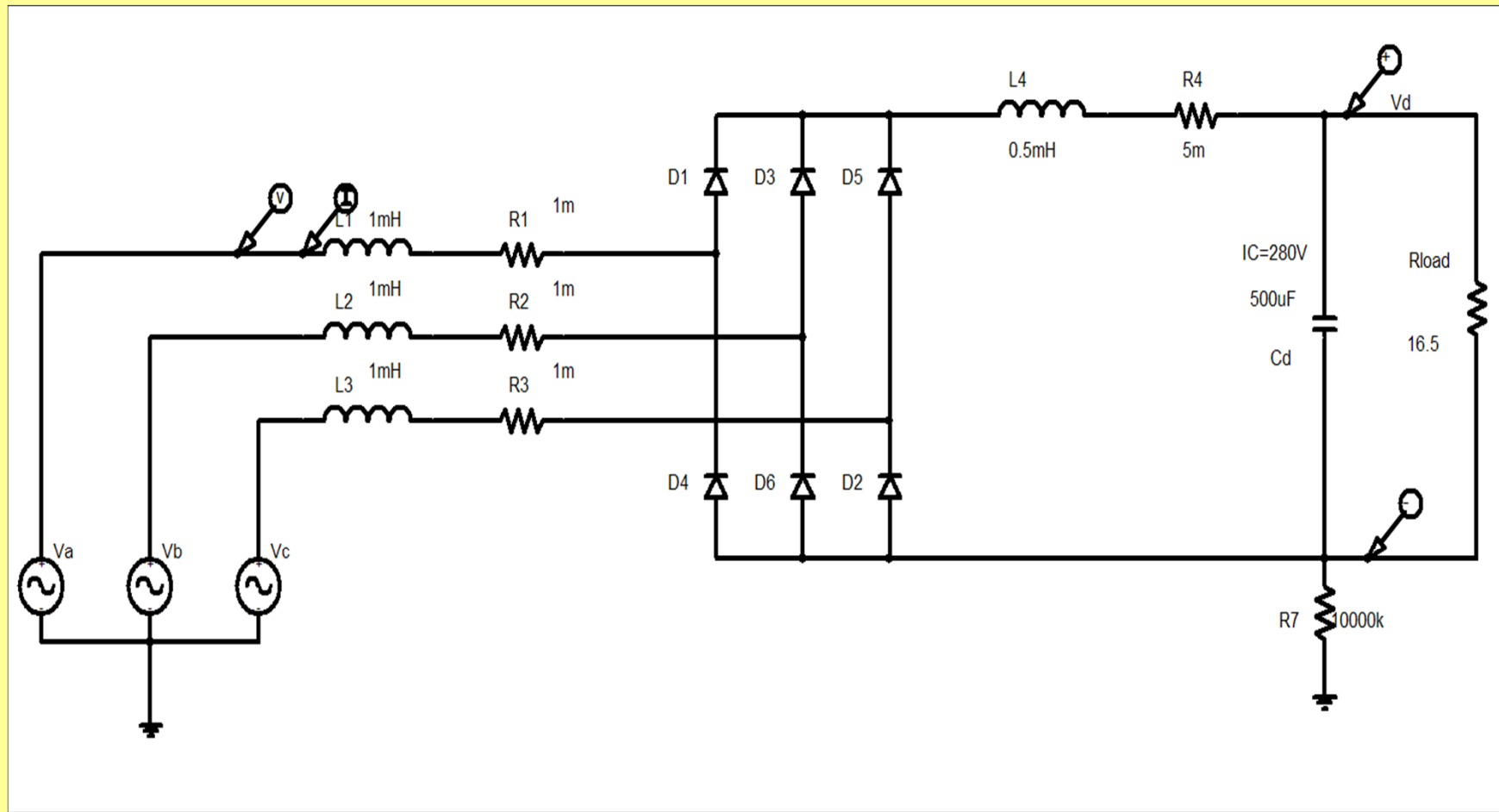

Simulation Results

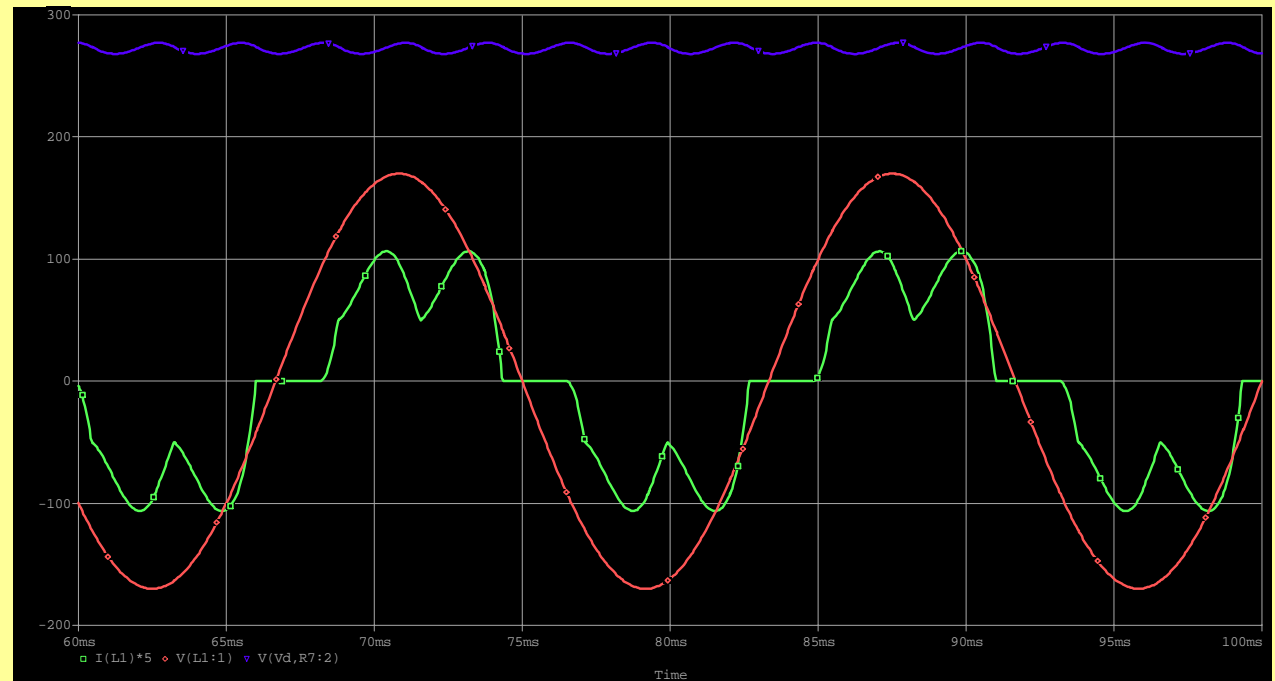

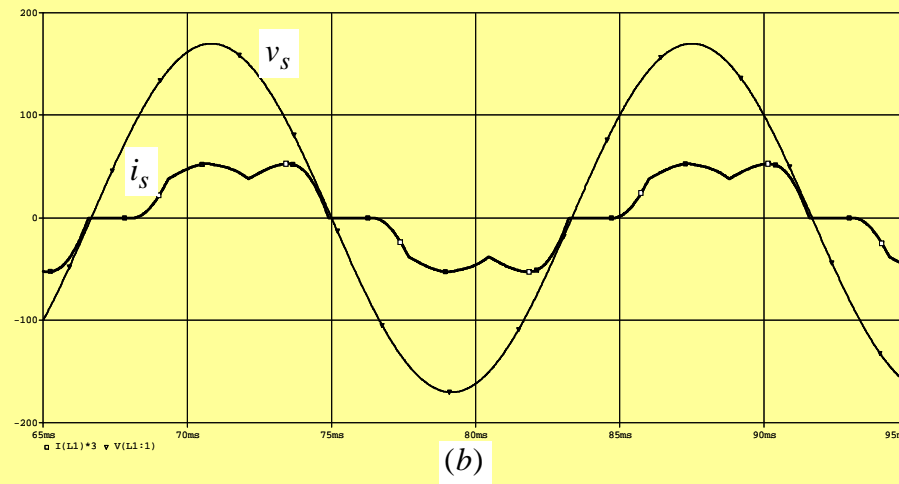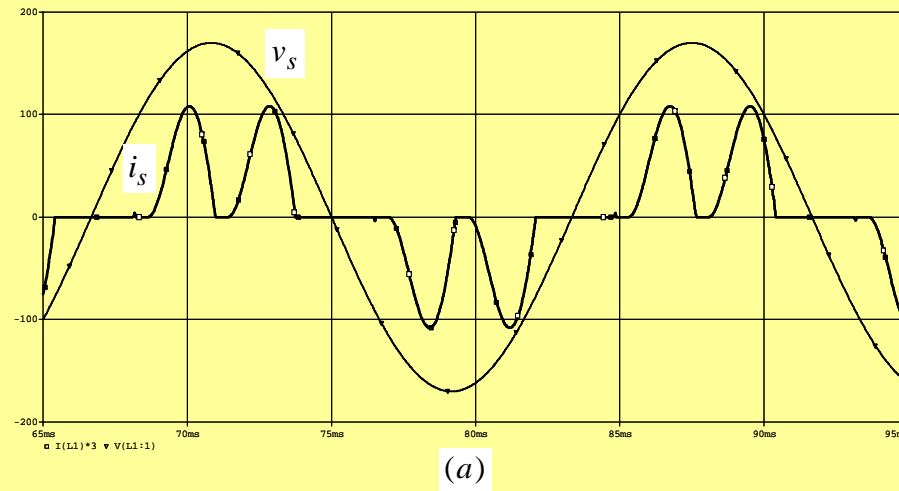

Effect of L_s variation (a) $L_s = 0.1mH$; (b) $L_s = 3mH$.

Summary

Diode Rectification of Utility Input

- Single-Phase Rectifiers
- Three-Phase Rectifiers