
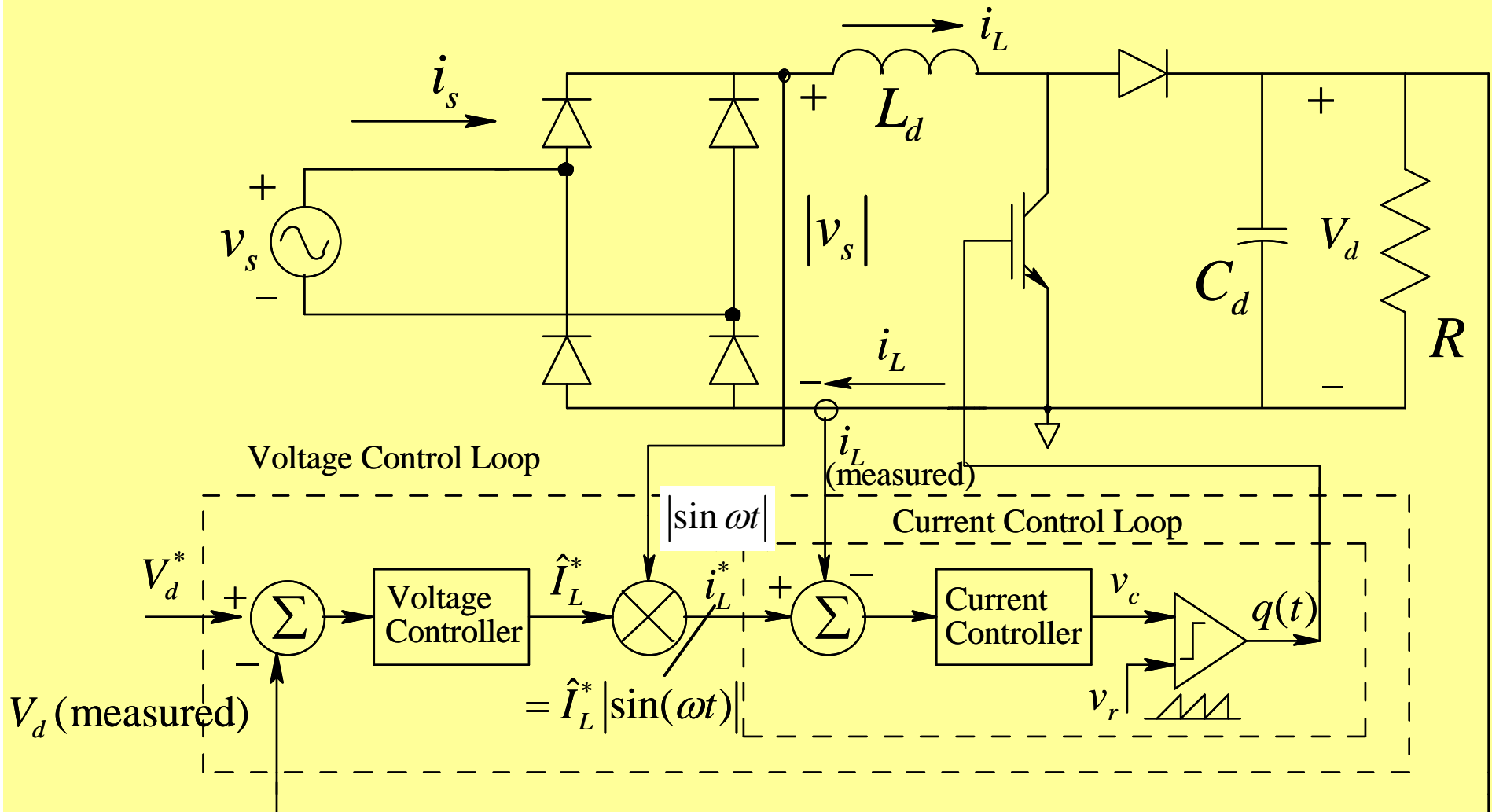



PFC Controller Design

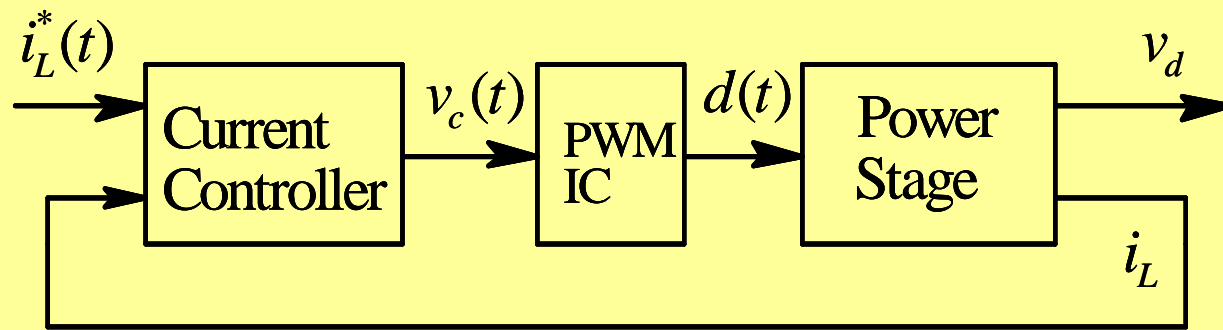


DESIGNING INNER AVERAGE-CURRENT-CONTROL LOOP




(a)

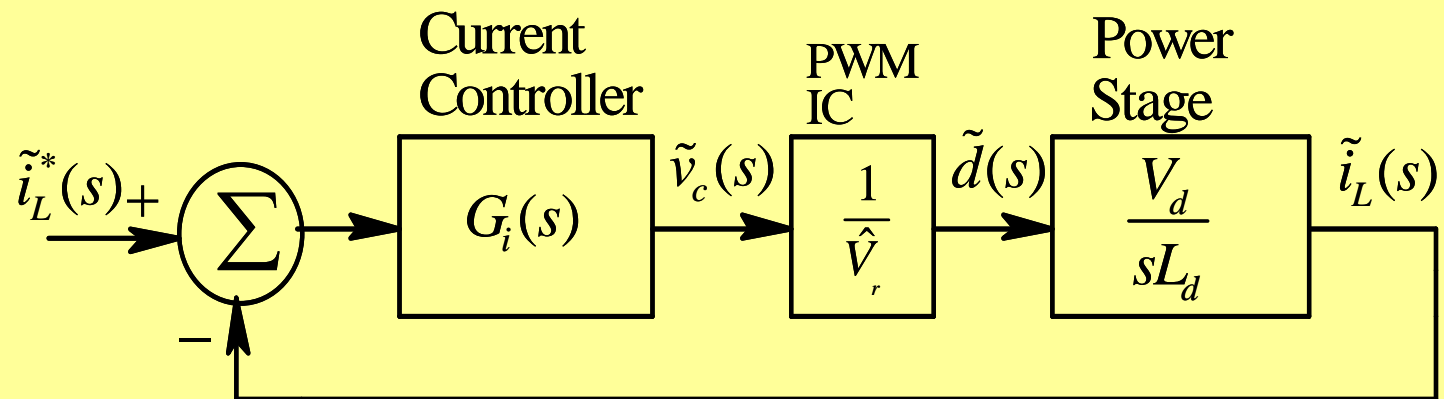


(b)

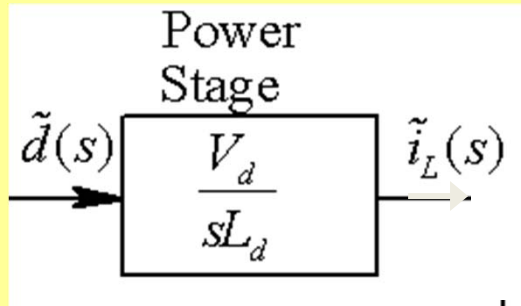


Why?

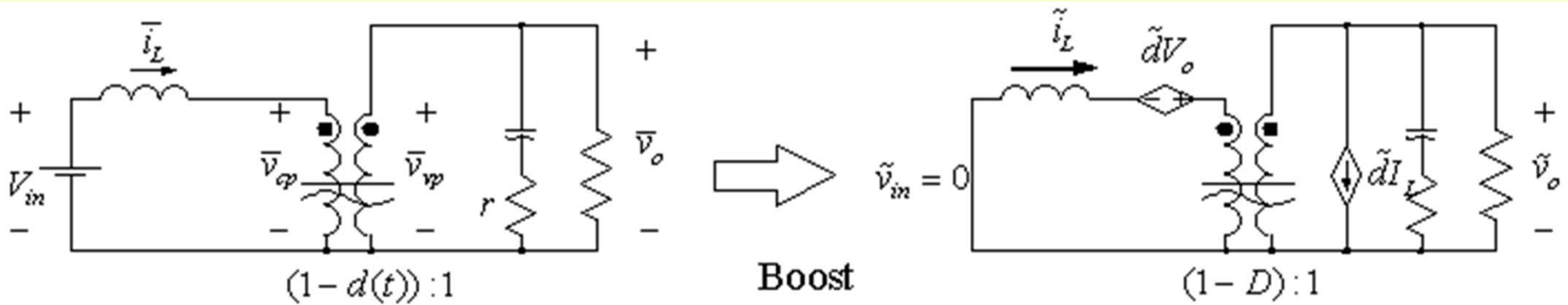

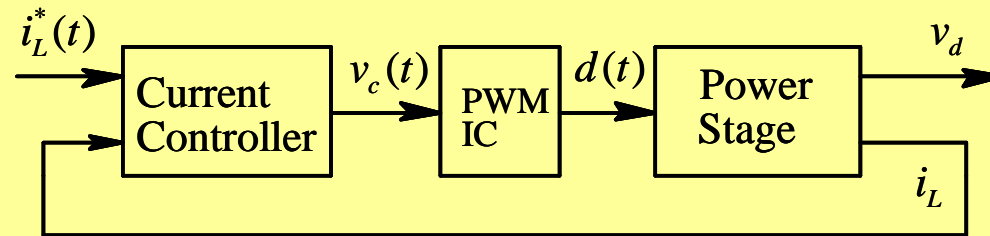DESIGNING INNER AVERAGE-CURRENT-CONTROL LOOP



(a)

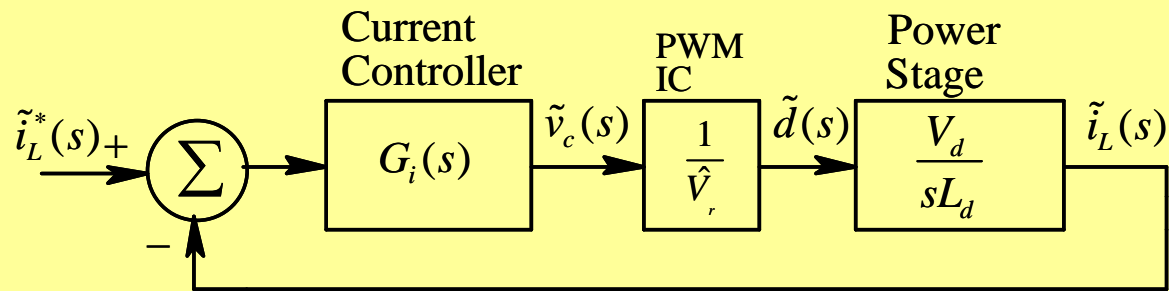

(b)

PWM-IC: $\frac{\tilde{d}(s)}{\tilde{v}_c(s)} = \frac{1}{\hat{V}_r}$


Controller: $G_i(s) = \frac{k_c}{s} \frac{1 + s/\omega_z}{1 + s/\omega_p}$

Power-Stage: $\frac{\tilde{i}_L(s)}{\tilde{d}(s)} = \frac{V_d}{sL_d}$


$K_{boost} = \tan(45^\circ + \frac{\phi_{boost}}{2})$ phase boost

$f_z = \frac{f_{ci}}{K_{boost}}$ $f_p = K_{boost} f_{ci}$ $k_c = \omega_z |G_C(s)|_{f_c}$

DESIGNING THE OUTER VOLTAGE LOOP

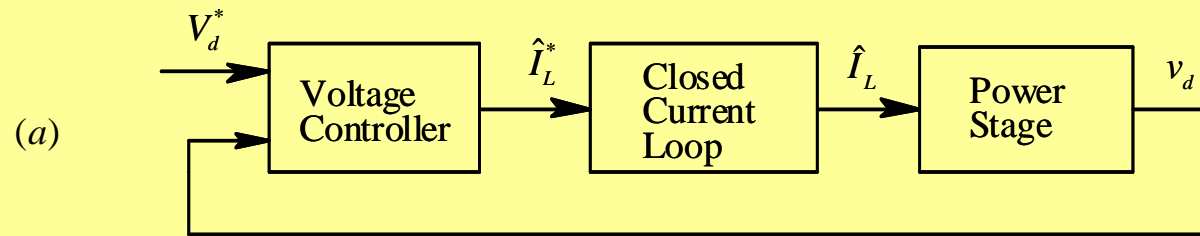

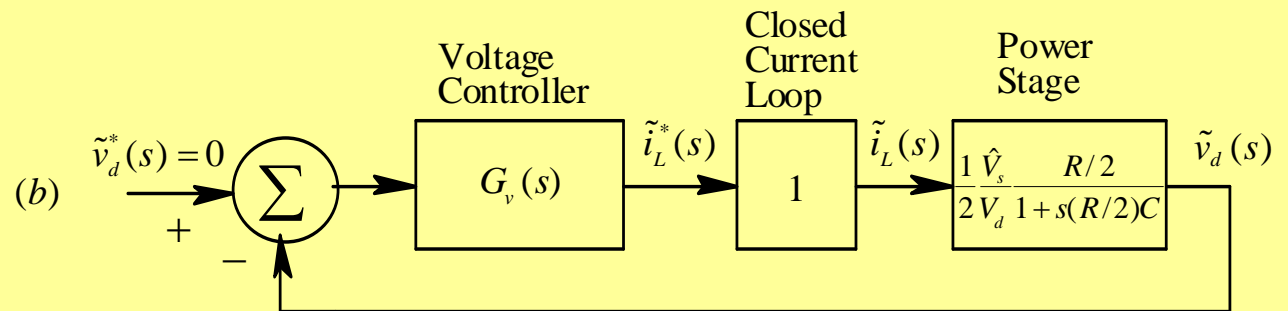
$$G_v(s) = \frac{k_v}{1 + s/\omega_{cv}}$$




$$\left| \frac{k_v}{1 + s/\omega_{cv}} \frac{1}{2} \frac{\hat{V}_s}{V_d} \frac{R/2}{1 + s(R/2)C} \right|_{s=j(2\pi \times f_{cv})} = 1$$

$$\left| \frac{k_v}{1 + s/\omega_{cv}} \right|_{s=j(2\pi \times 120)} = \frac{\hat{I}_{L2}}{\hat{V}_{d2}} \quad \frac{\hat{I}_{L2}}{\hat{I}_L} = 1.5\%$$

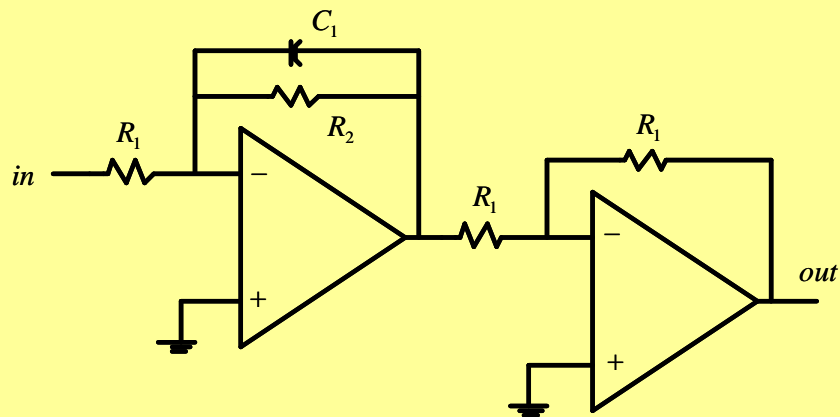
$$G_v(s) = \frac{k_v}{1 + s/\omega_{cv}}$$




PSpice Modeling:

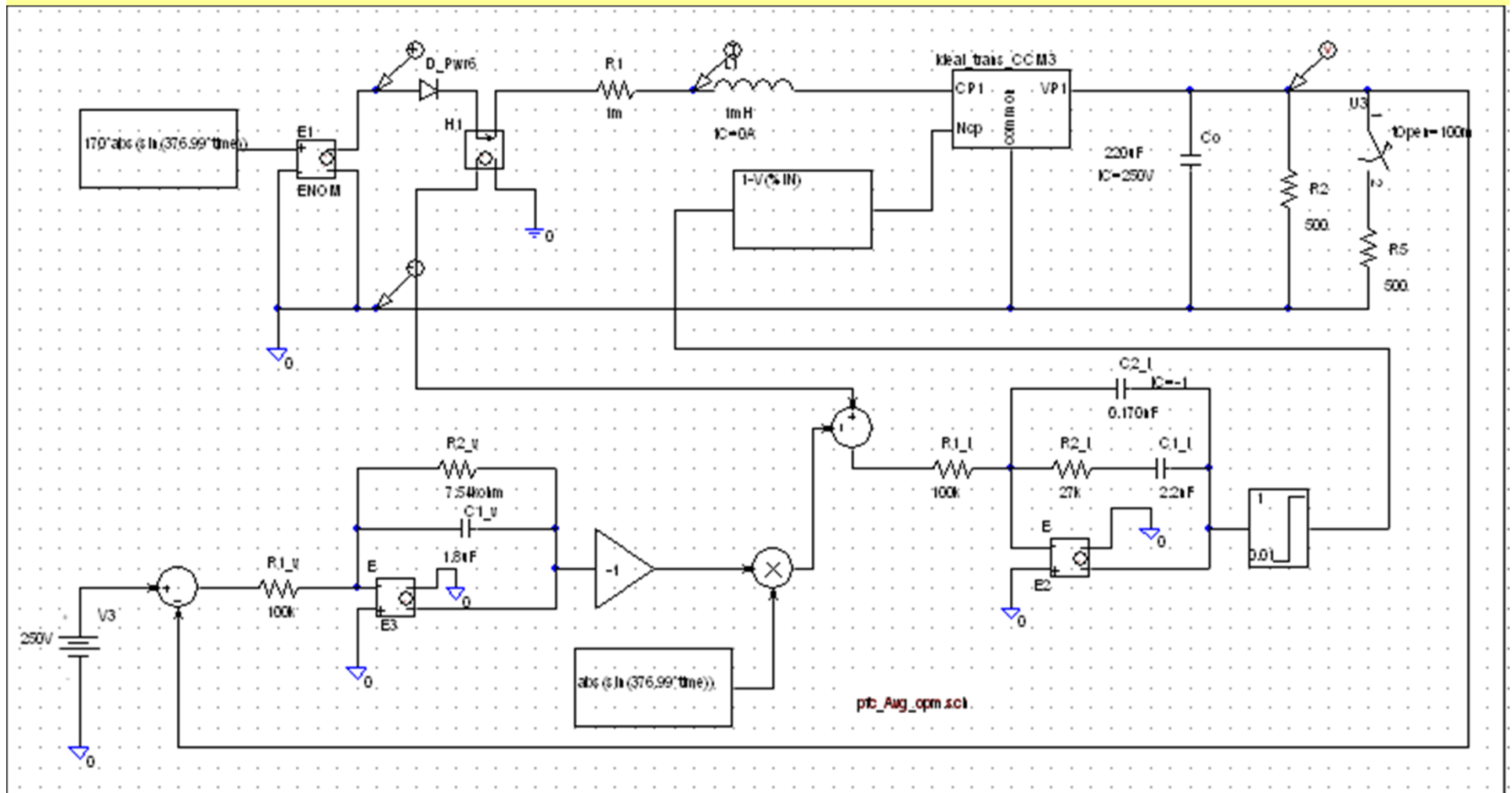


Simulation Results

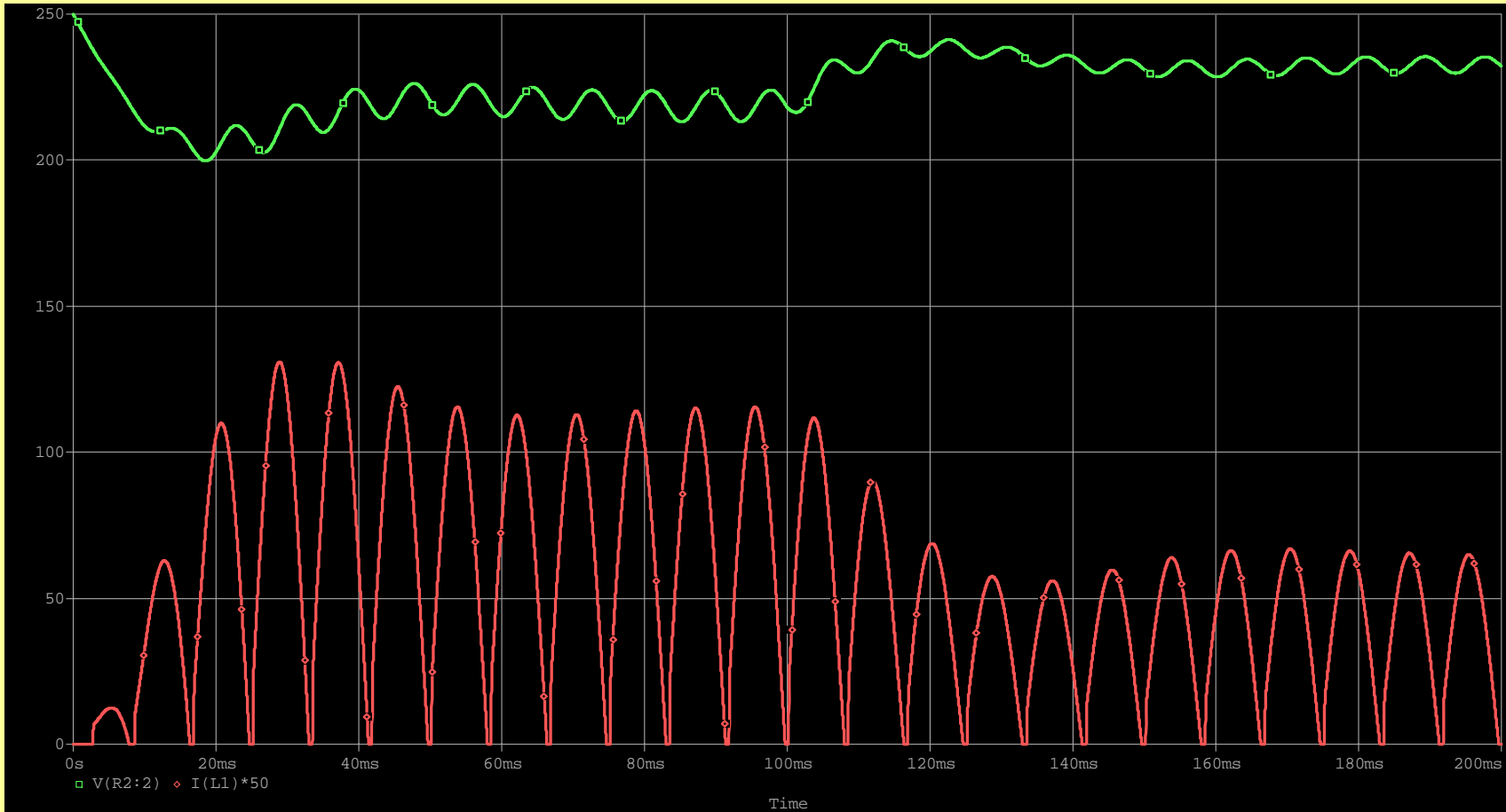


PSpice Switching Circuit Modeling:

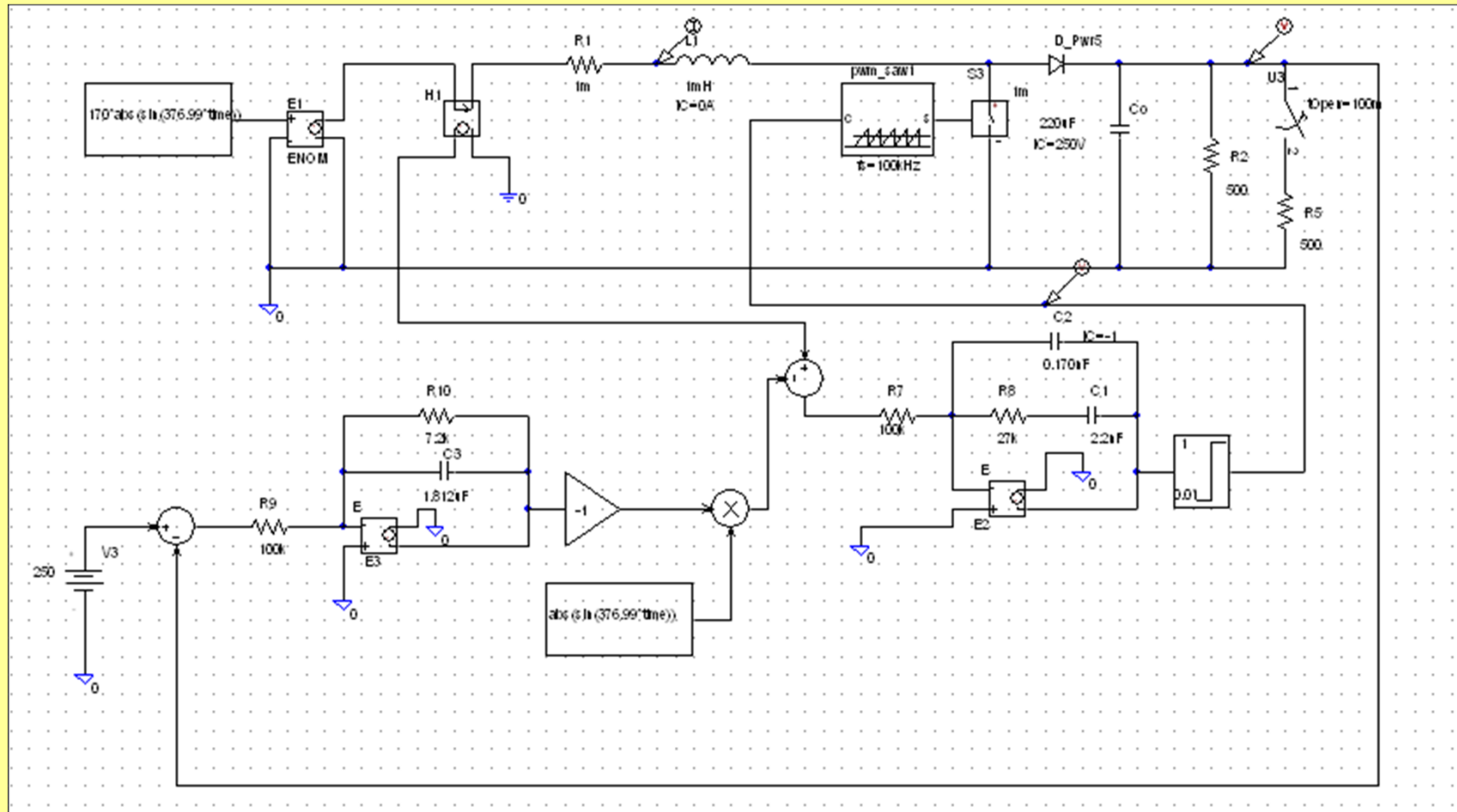

Simulation Results

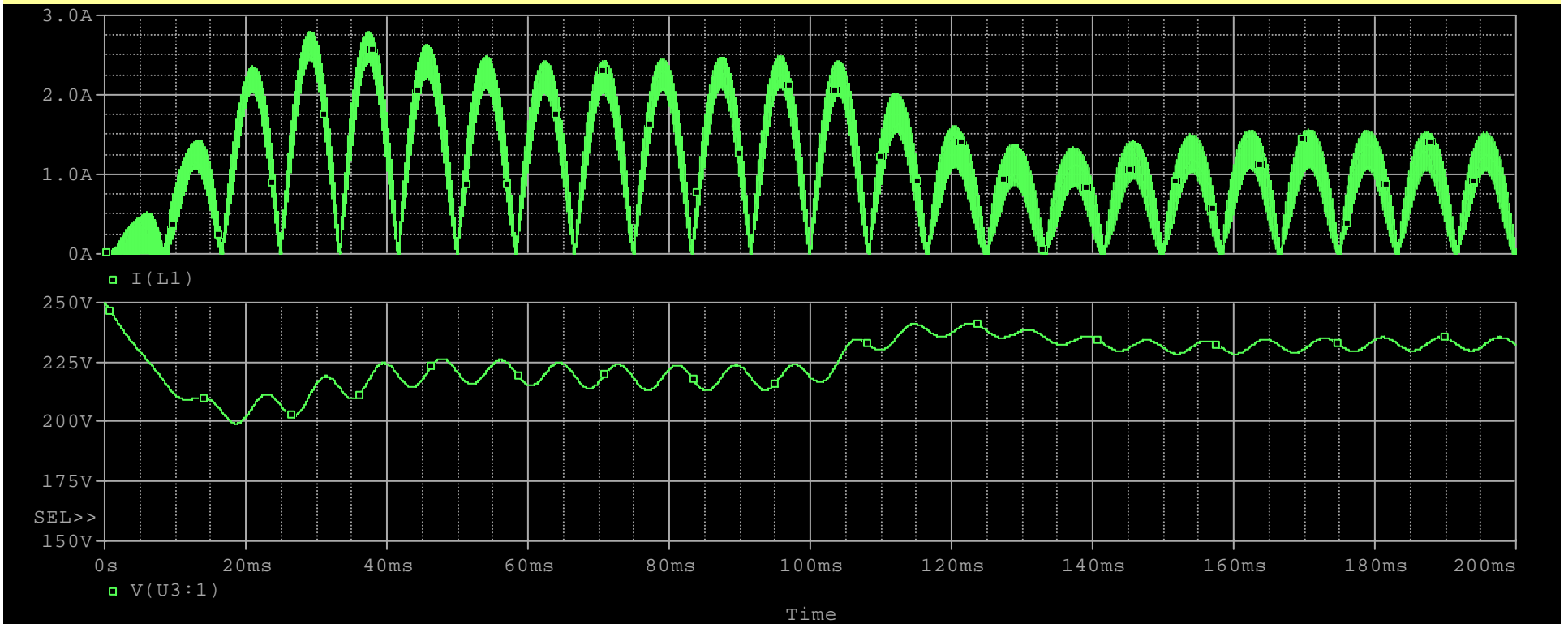

FEEDFORWARD OF THE INPUT VOLTAGE

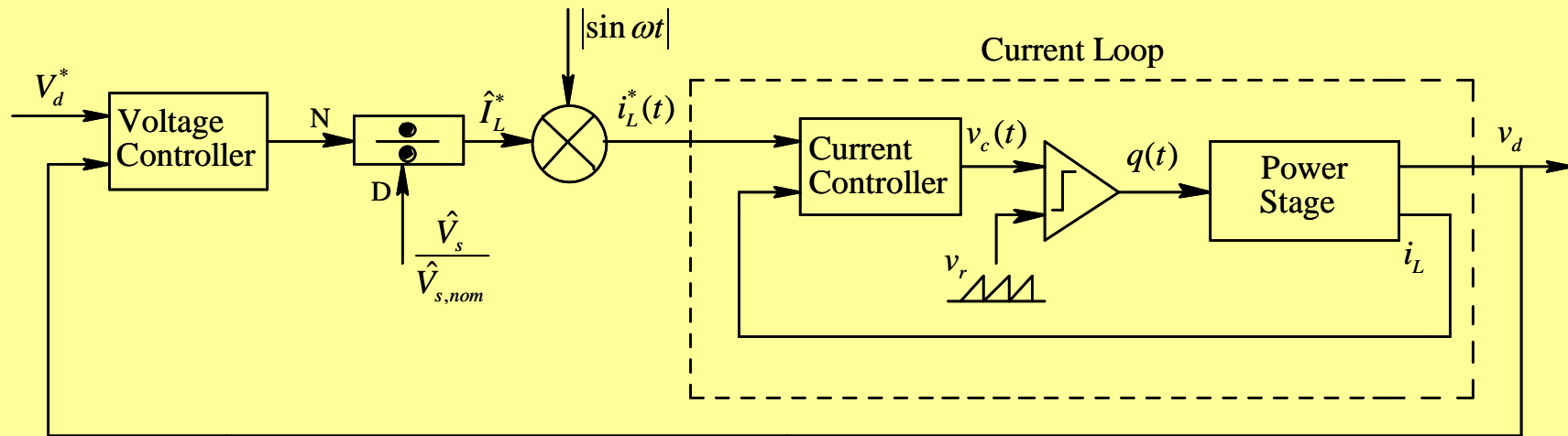

Summary

- PFC Controller Design