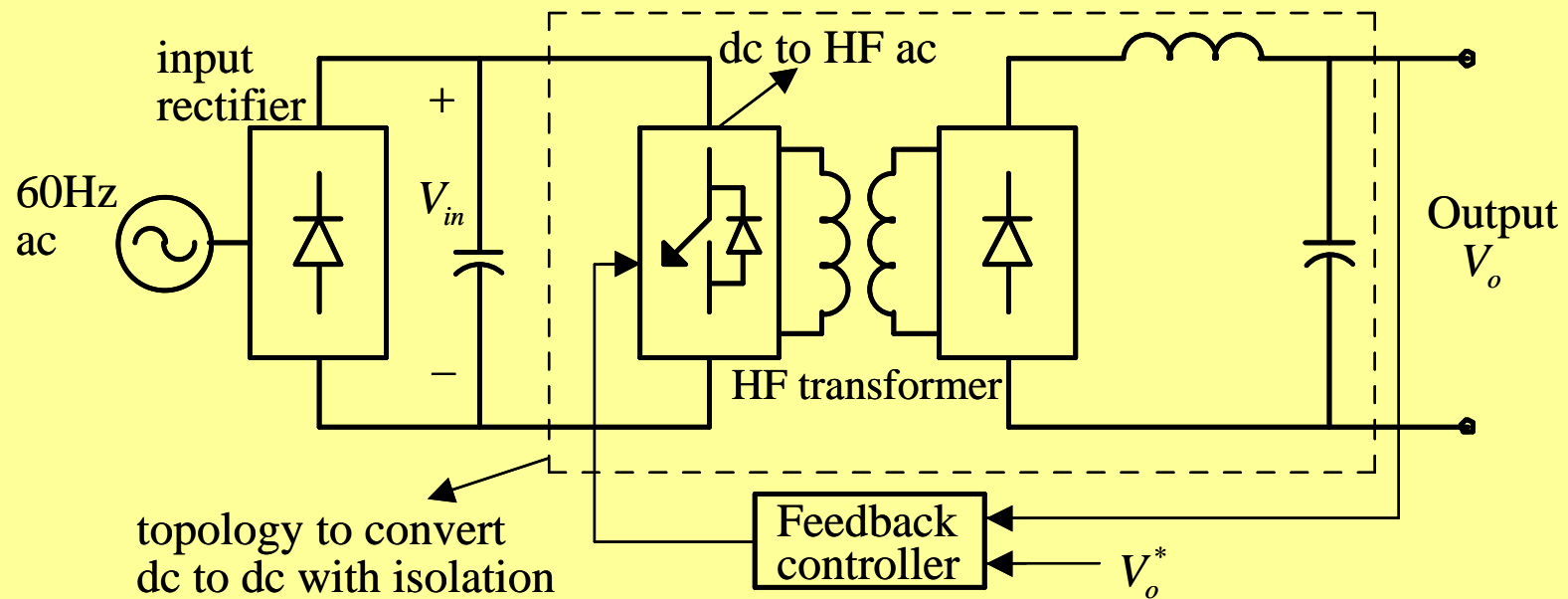


Isolated Switch-Mode DC Power Supplies

- Flyback Converters
- Forward Converters

SWITCH-MODE DC POWER SUPPLIES






NEED FOR ELECTRICAL ISOLATION

CLASSIFICATION

- Flyback converters derived from Buck-Boost dc-dc converters
- Forward converter derived from Buck dc-dc converters
- Full-Bridge and Half-Bridge converters derived from Buck dc-dc converters

FLYBACK CONVERTERS

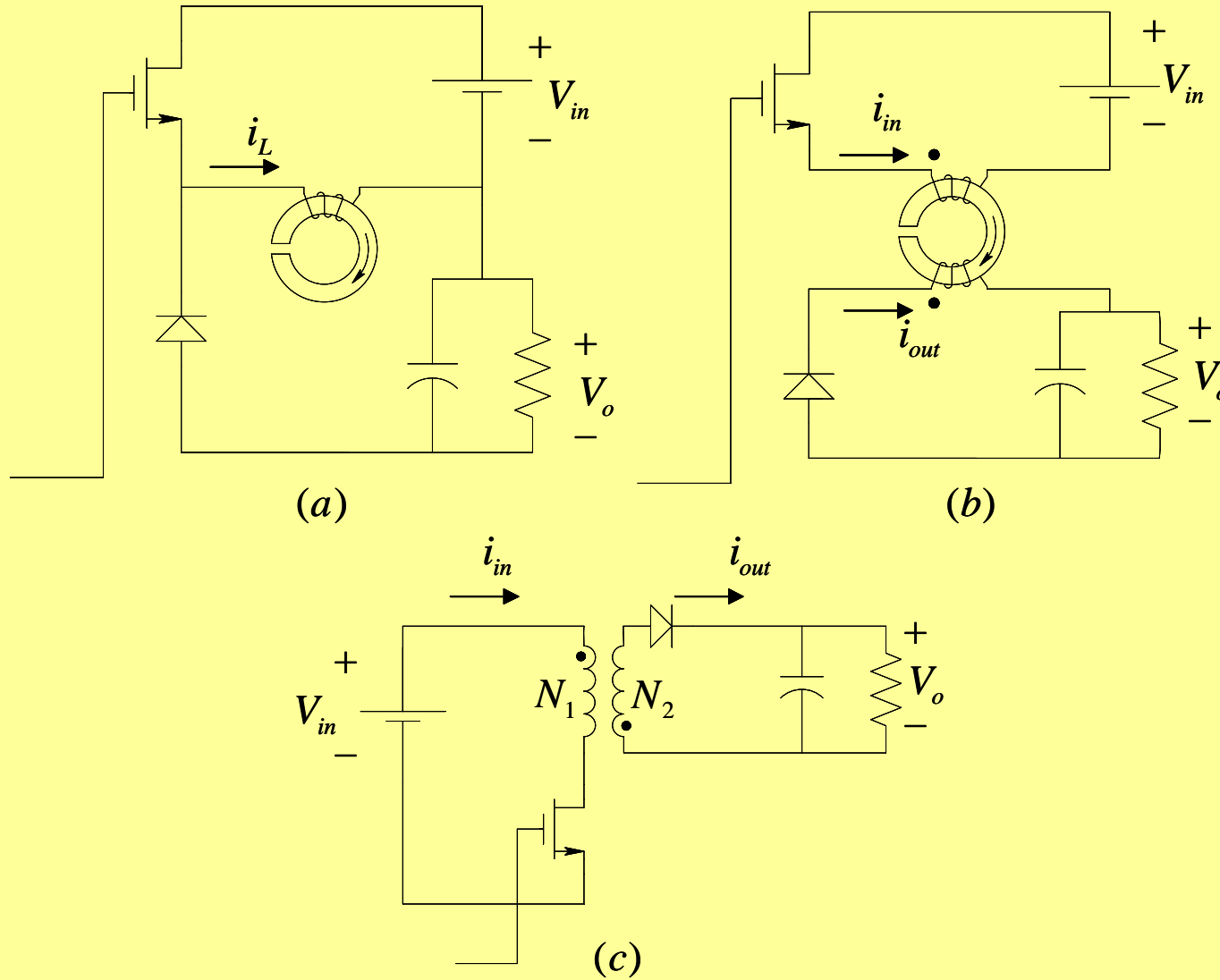


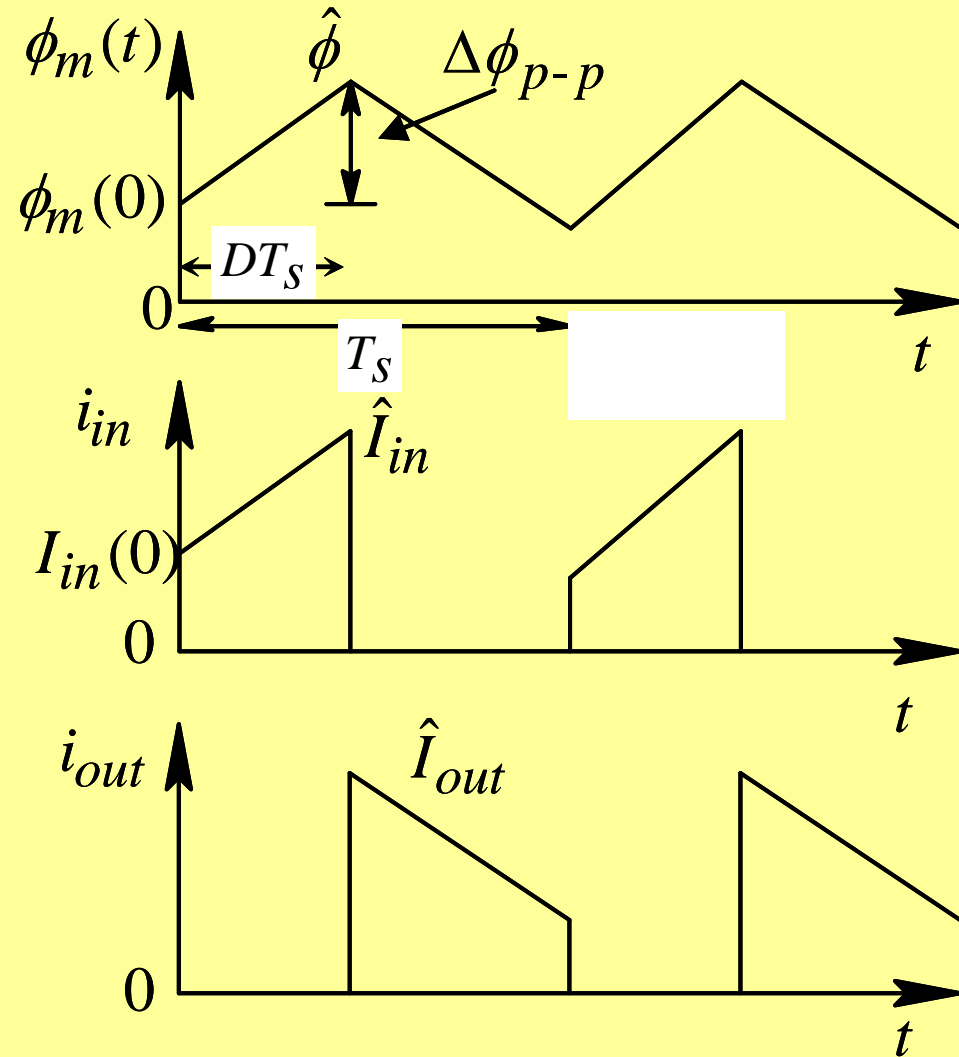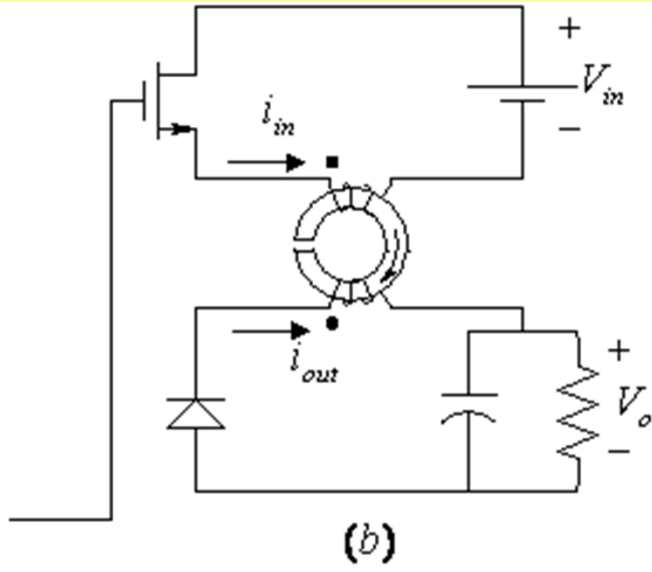


$$\Delta\phi_{p-p} = \frac{V_{in}}{N_1} DT_s = \frac{V_o}{N_2} (1-D)T_s$$


$$\frac{V_o}{V_{in}} \Rightarrow \left(\frac{N_2}{N_1} \right) \frac{D}{1-D}$$

PSpice Modeling:

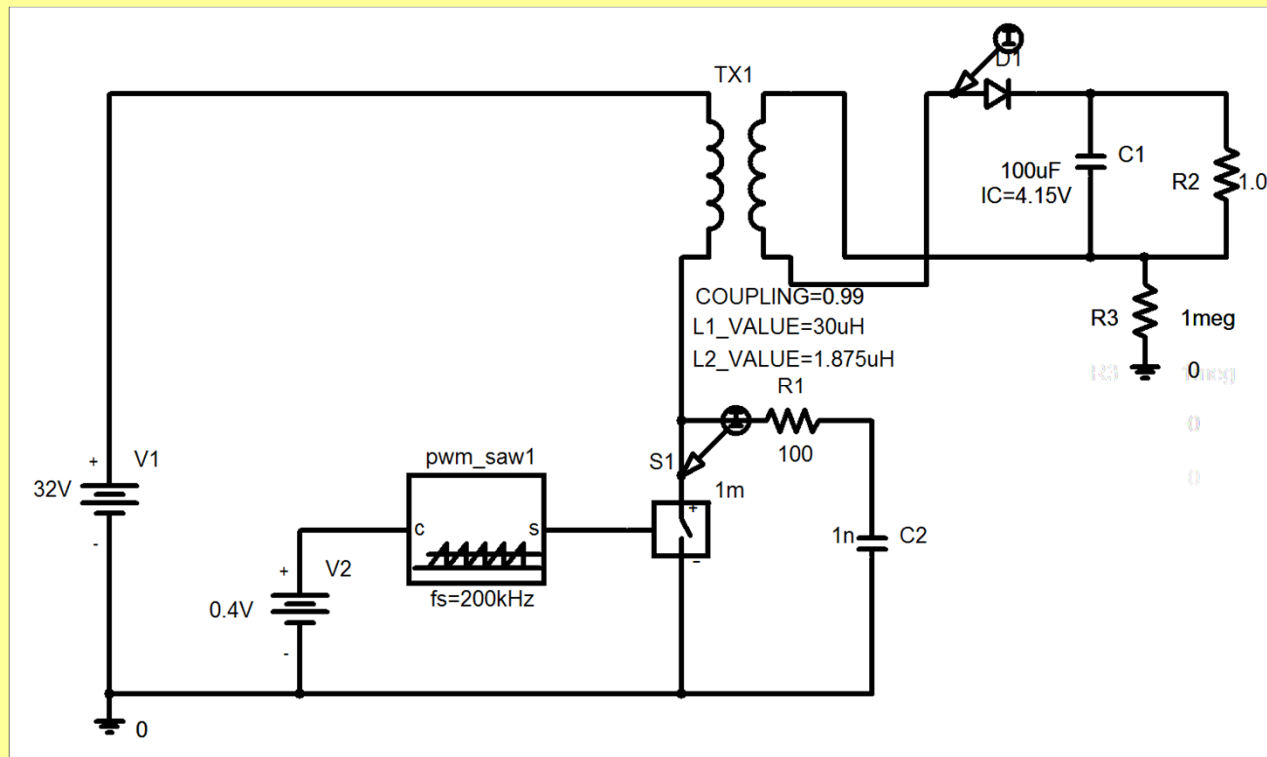


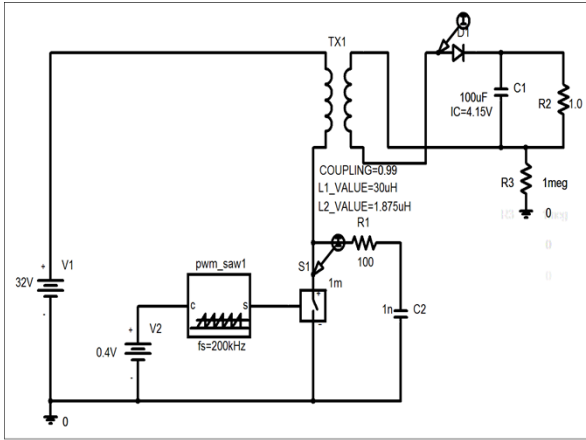


Simulation Results

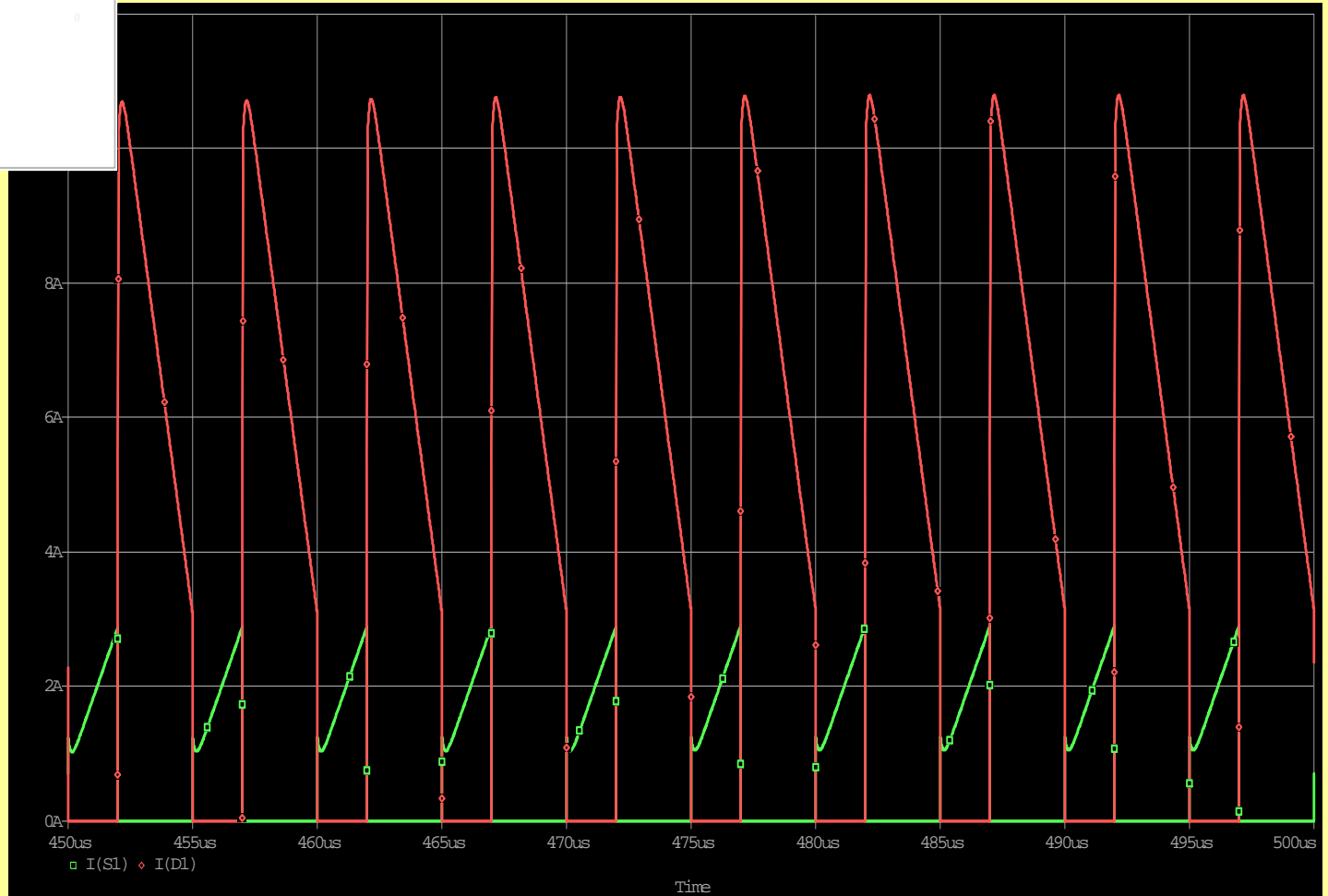


FORWARD CONVERTERS

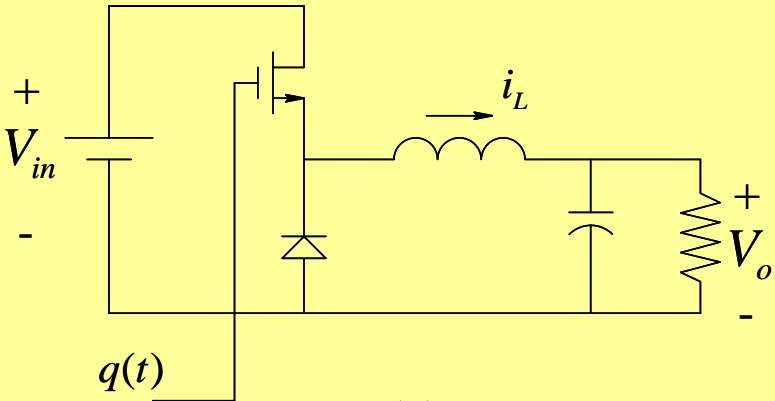


(a)

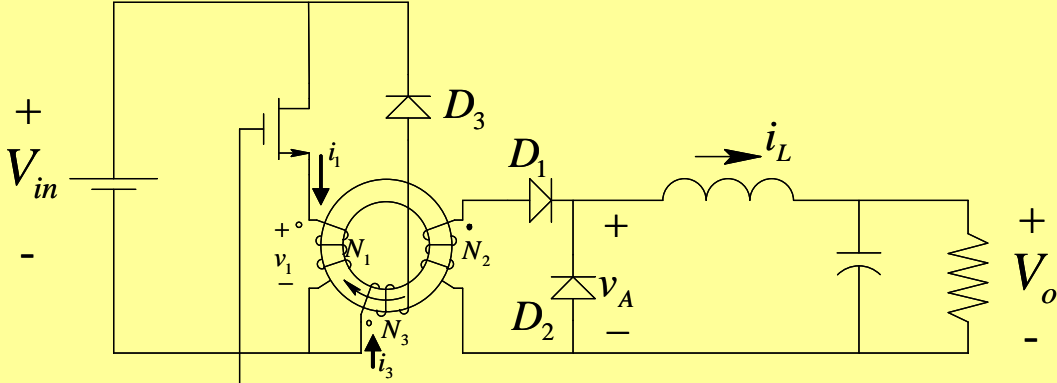


(b)

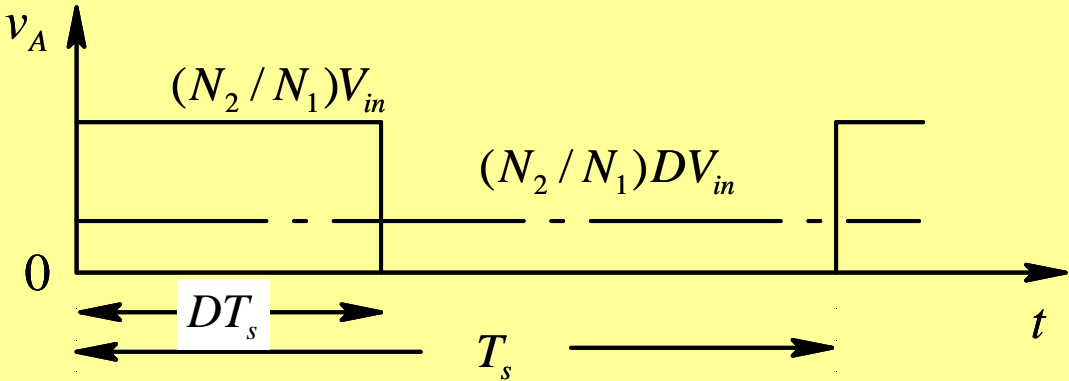

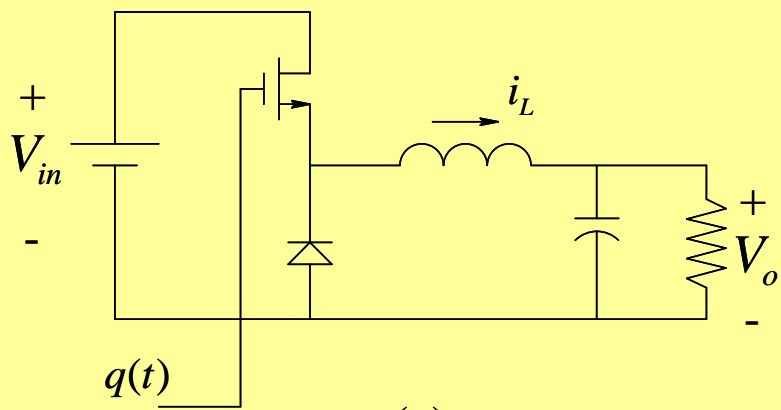
$$V_o = \left(\frac{N_2}{N_1} \right) DV_{in}$$





(a)

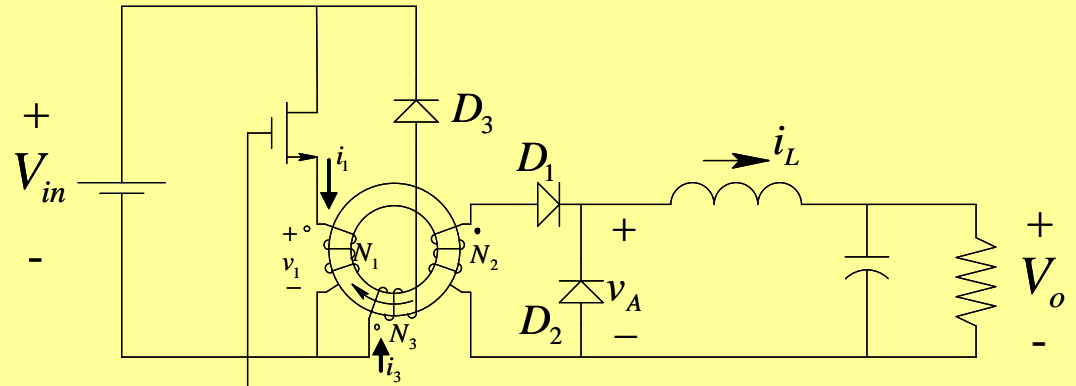



(b)

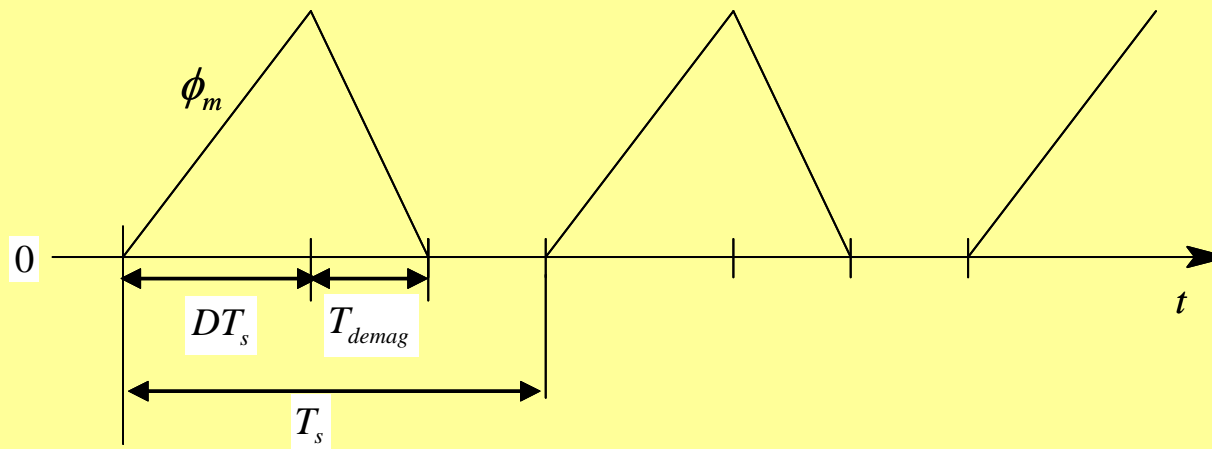

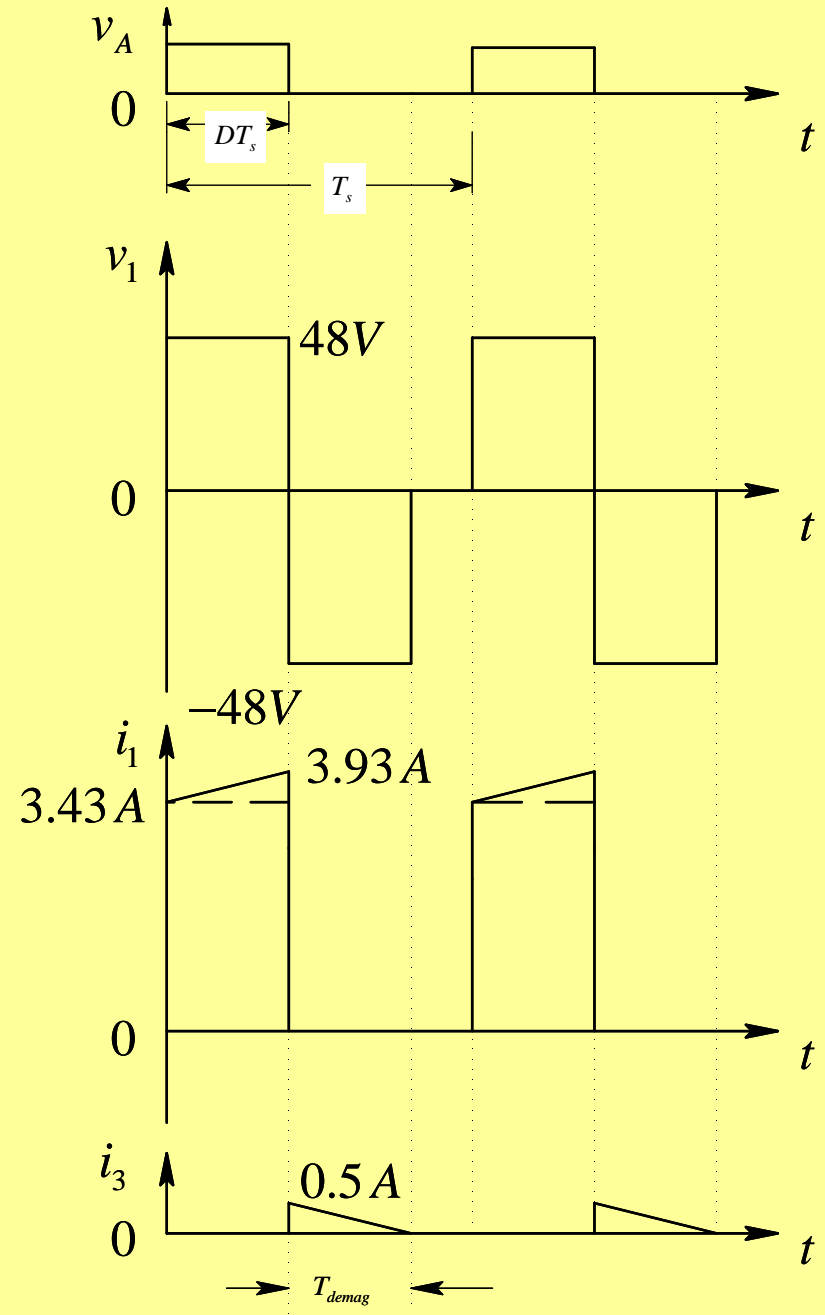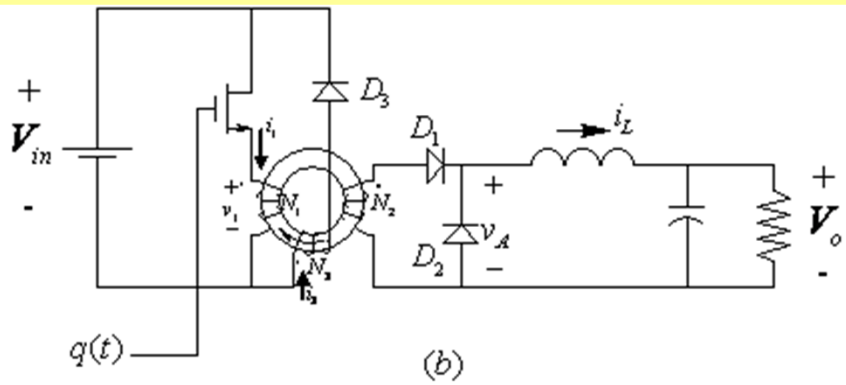


PSpice Modeling:

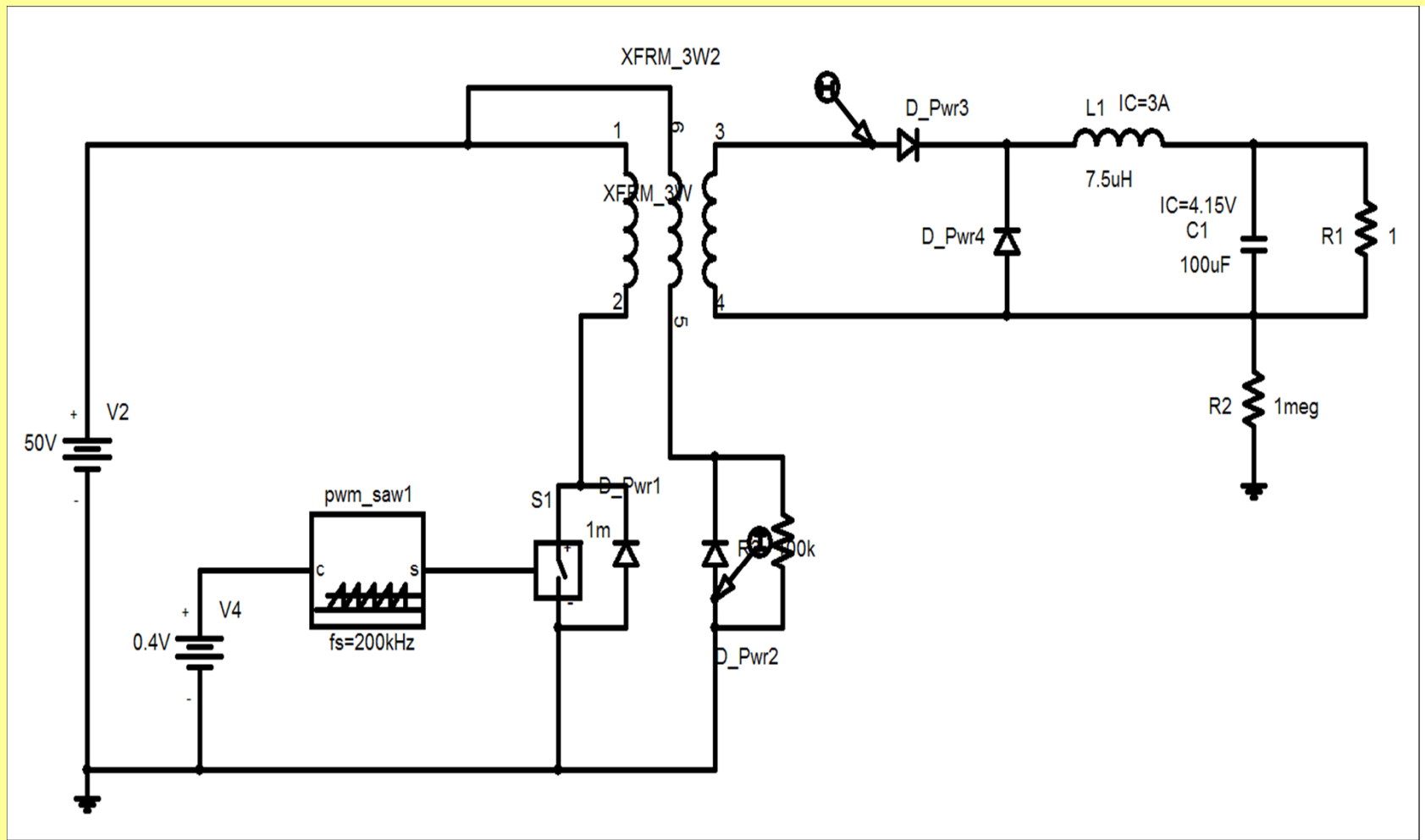


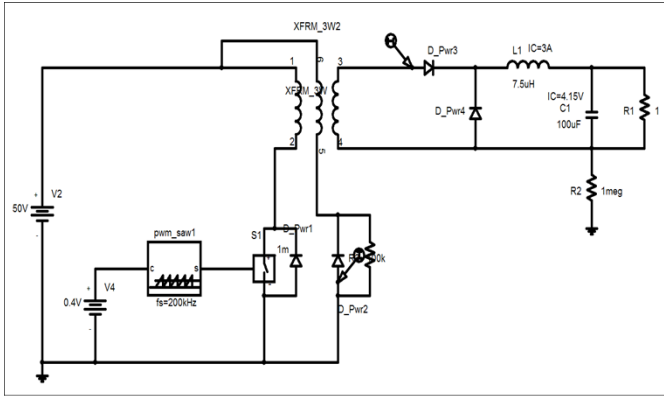

Simulation Results

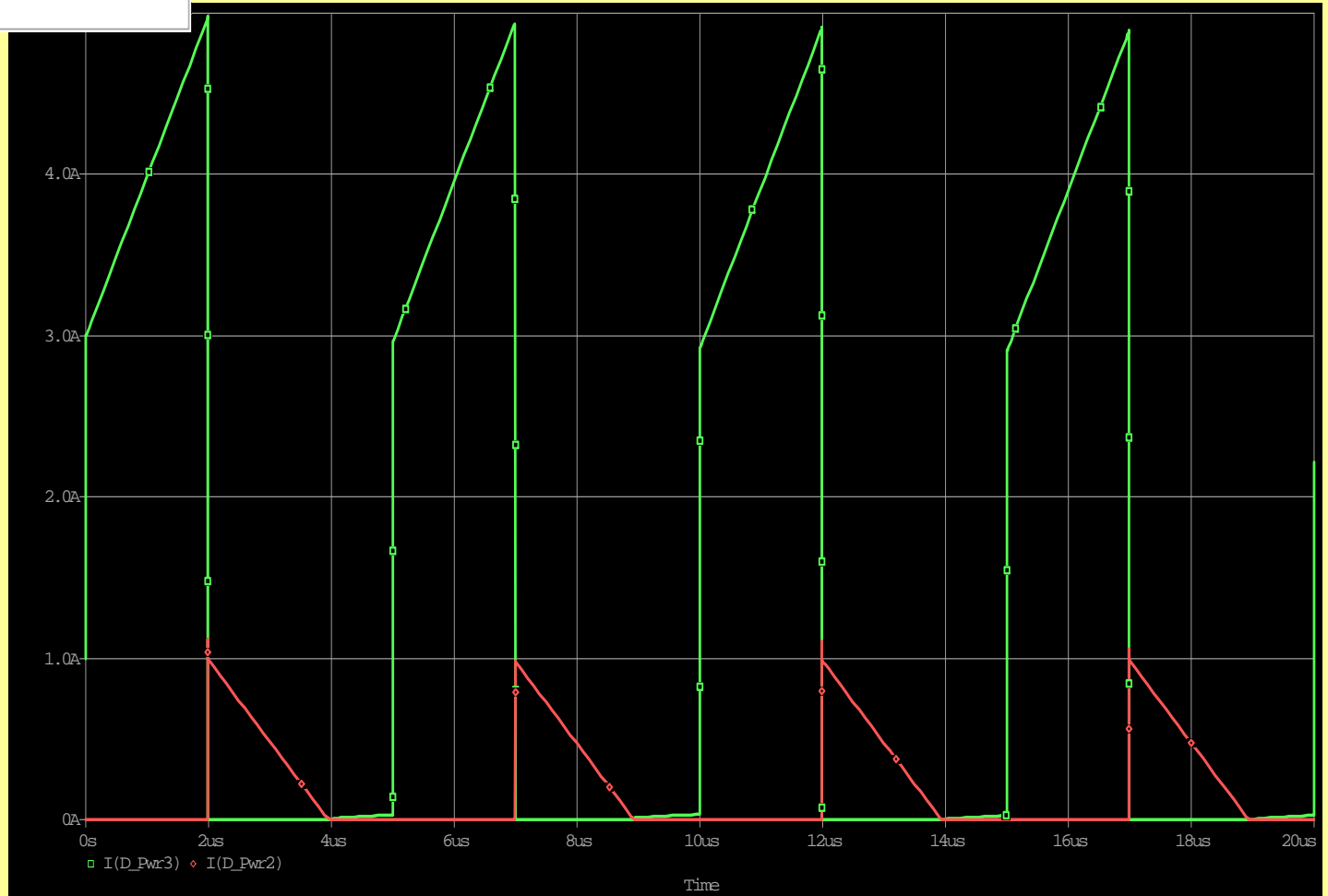

Two-Switch Forward Converters

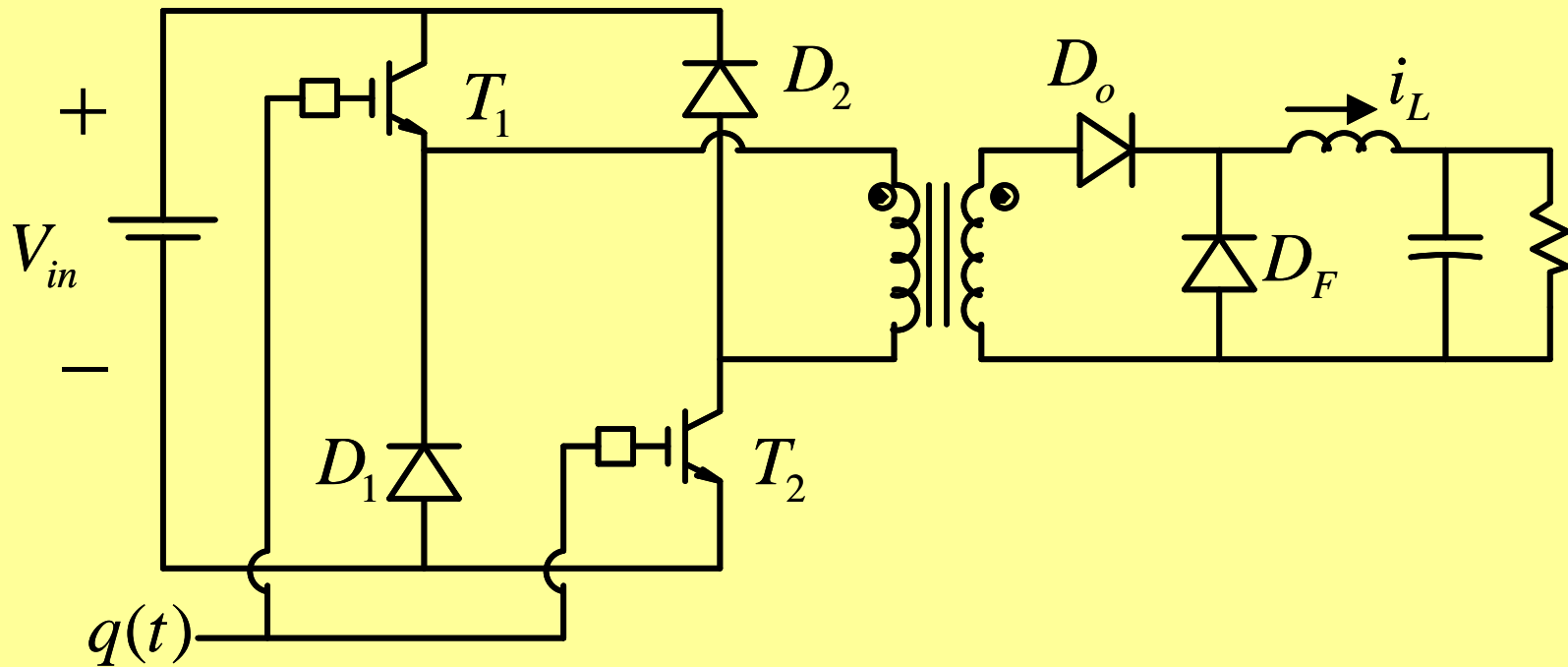

Summary

Switch-Mode DC Power Supplies

- Flyback Converters
- Forward Converters