
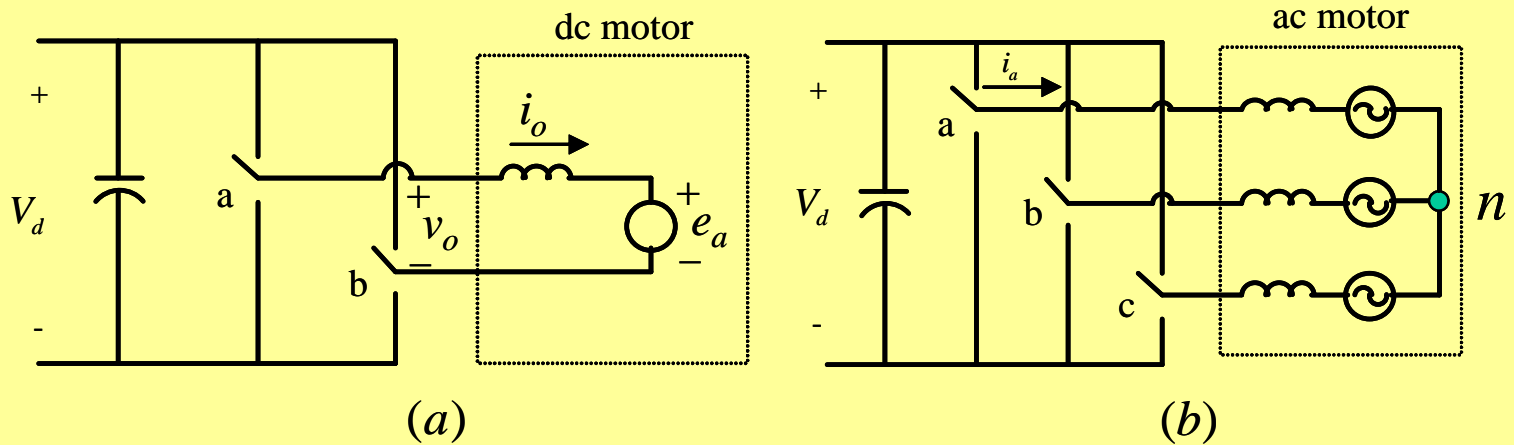



Synthesis of DC and Sinusoidal AC Voltages

Applications in


- Electric Drives
- UPS
- Power Systems

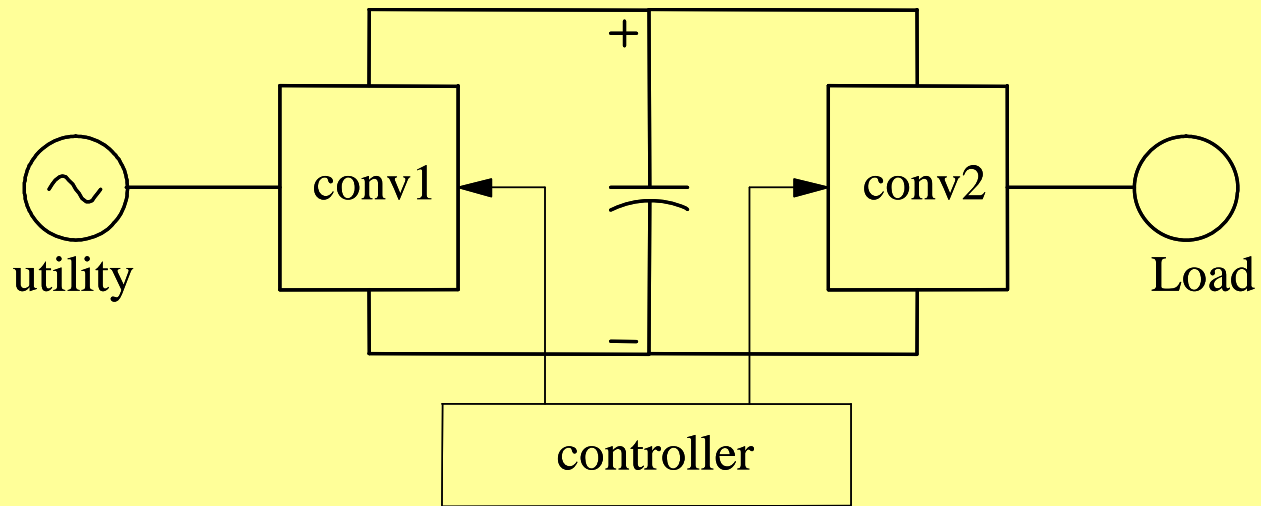

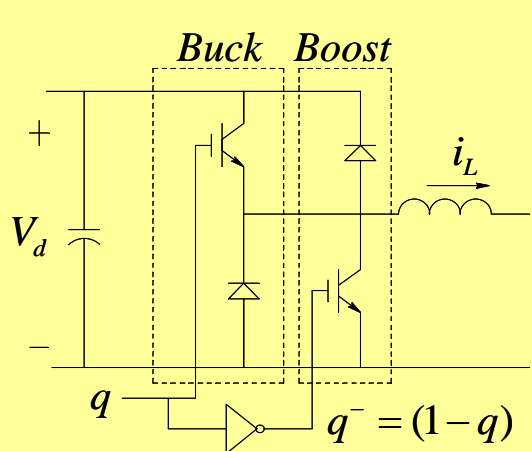
SWITCHING POWER-POLE AS THE BUILDING BLOCK




(a)

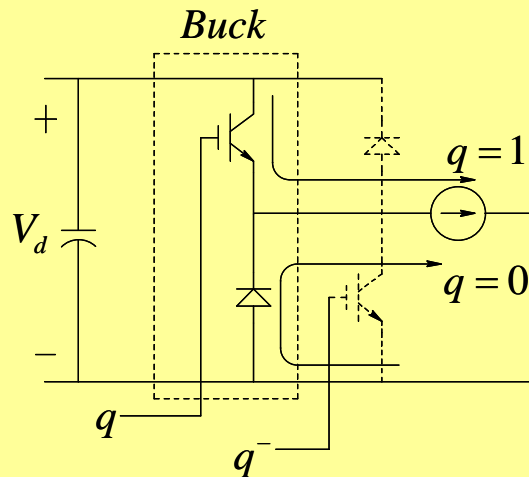


(b) $i_L = \text{positive}$

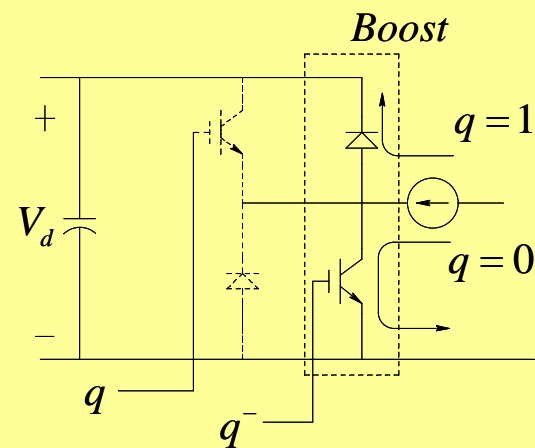


(c) $i_L = \text{negative}$

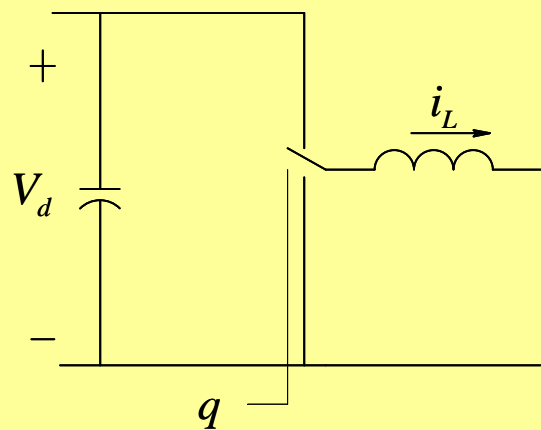

(a)

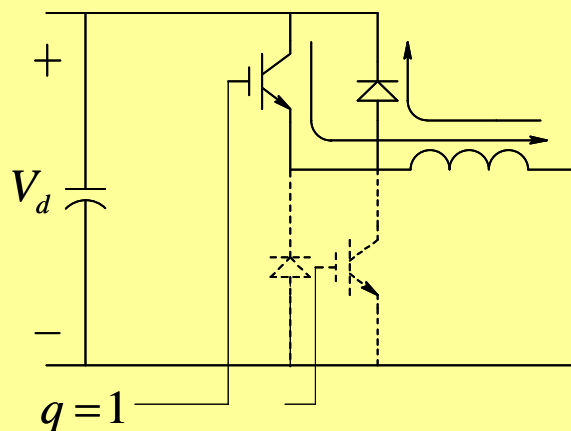

(b) $q = 1$

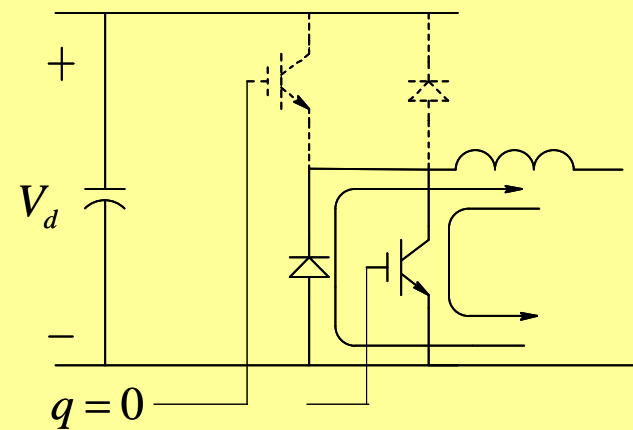


(c) $q = 0$


Average Representation of a Switching Power-Pole

$$\bar{v}_{aN} = d_a V_d$$

$$\bar{i}_{da} = d_a \bar{i}_a$$

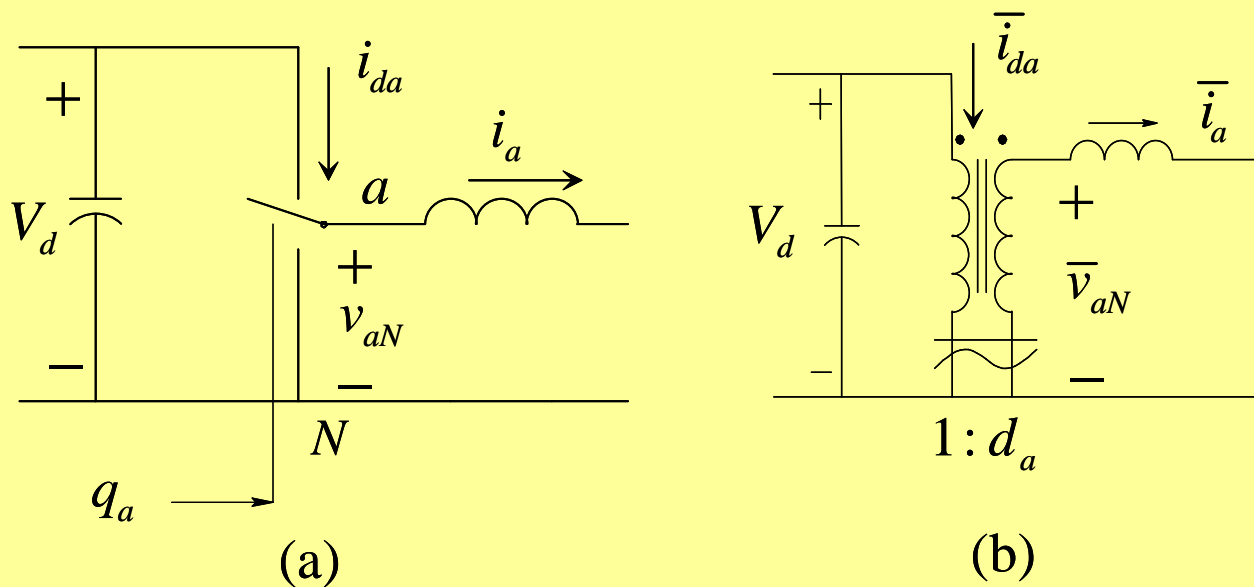


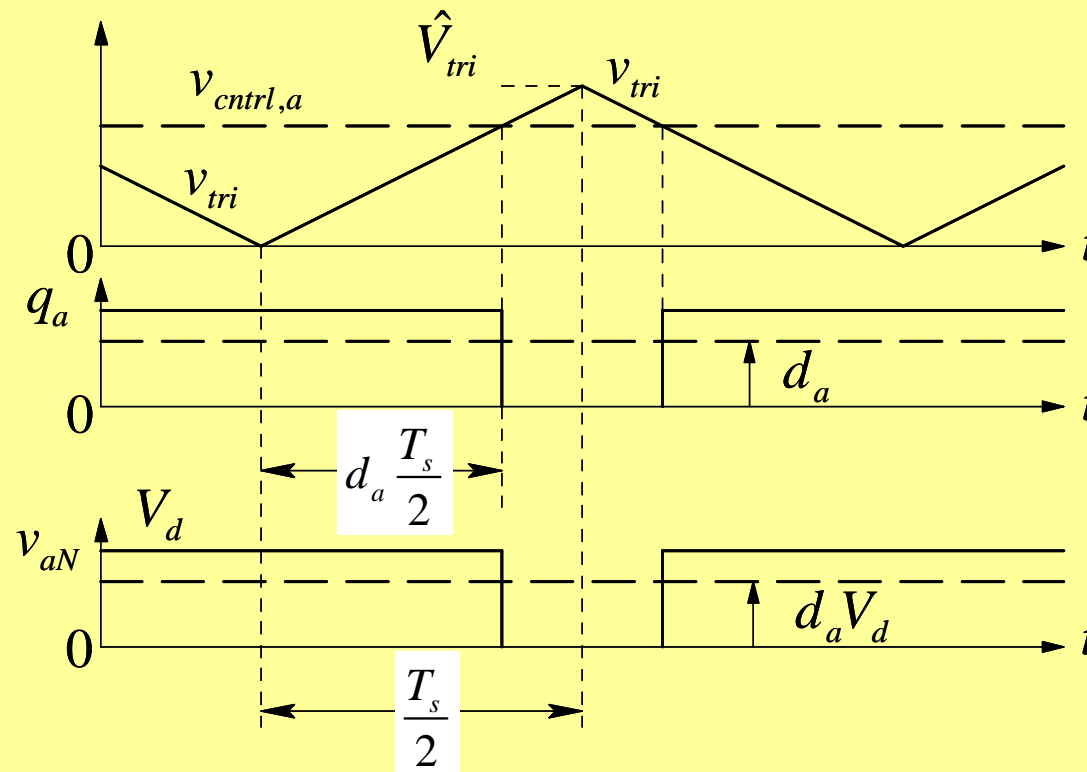Pulse-Width-Modulation (PWM) of the Bi-Directional Switching Power-Pole



$$d_a = \frac{v_{ctrl,a}}{\hat{V}_{tri}}$$

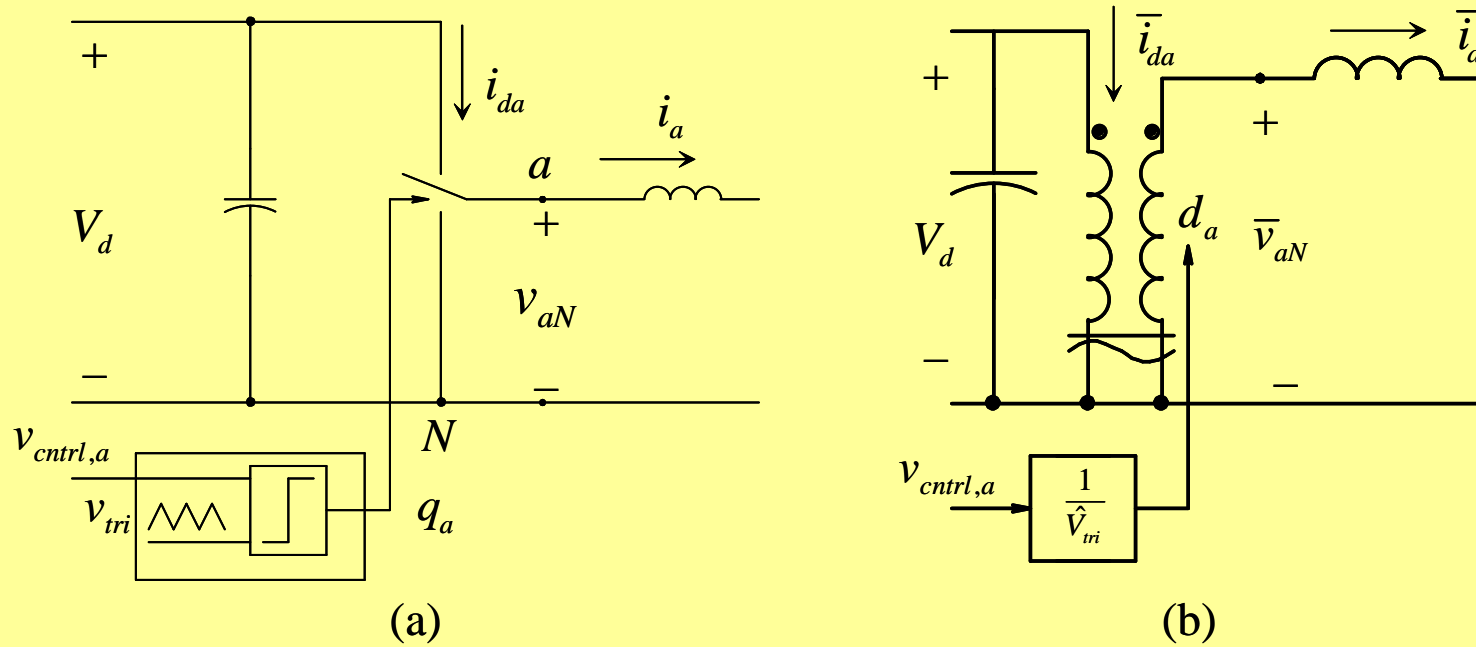
Obtaining Pulse-Width-Modulation (PWM) Signal:



$$d_a = \frac{v_{cntrl,a}}{\hat{V}_{tri}}$$


$$\bar{v}_{aN} = d_a V_d$$

Harmonics in the Output Voltage:

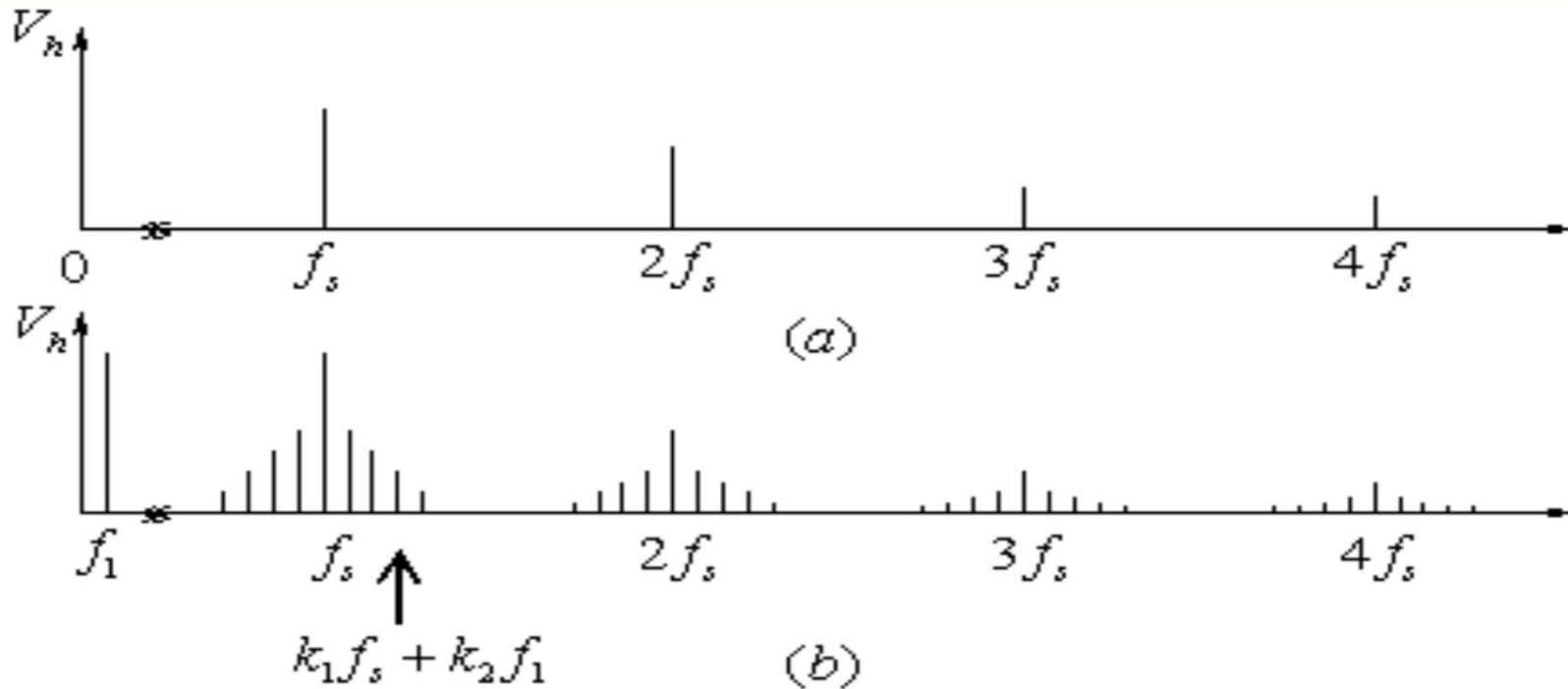


$$f_h = k_1 f_s \pm \underbrace{k_2 f_1}_{\text{sidebands}}$$

DC-MOTOR DRIVES

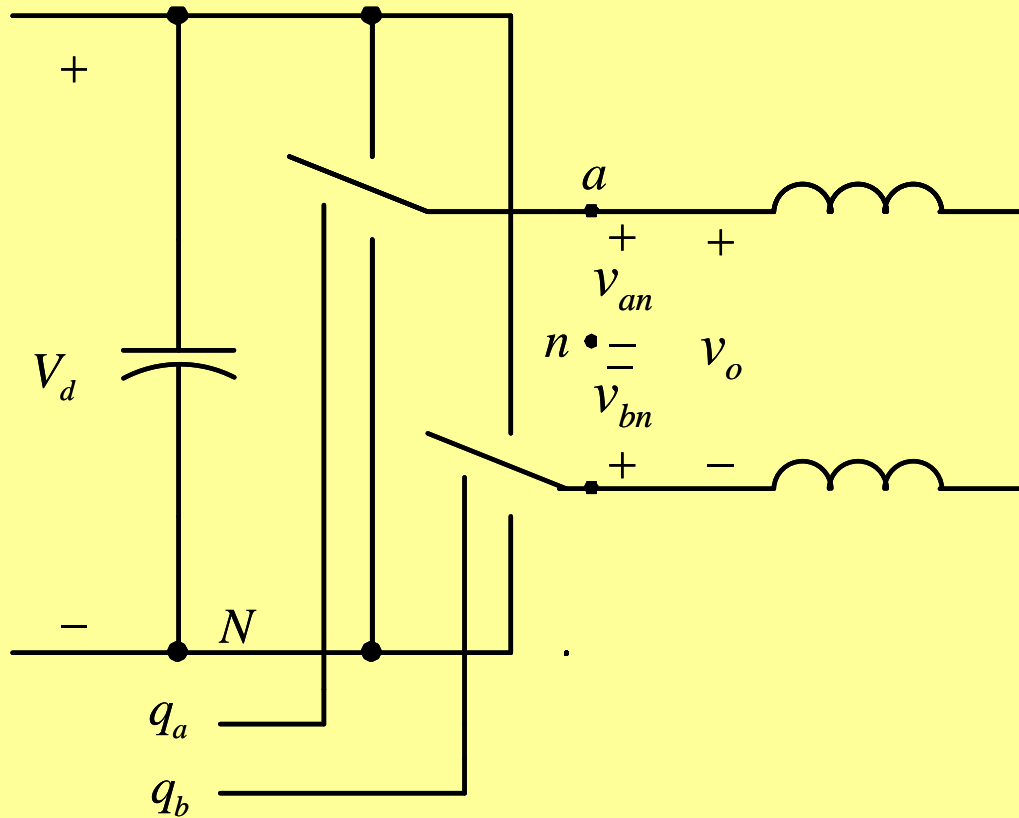

(a)

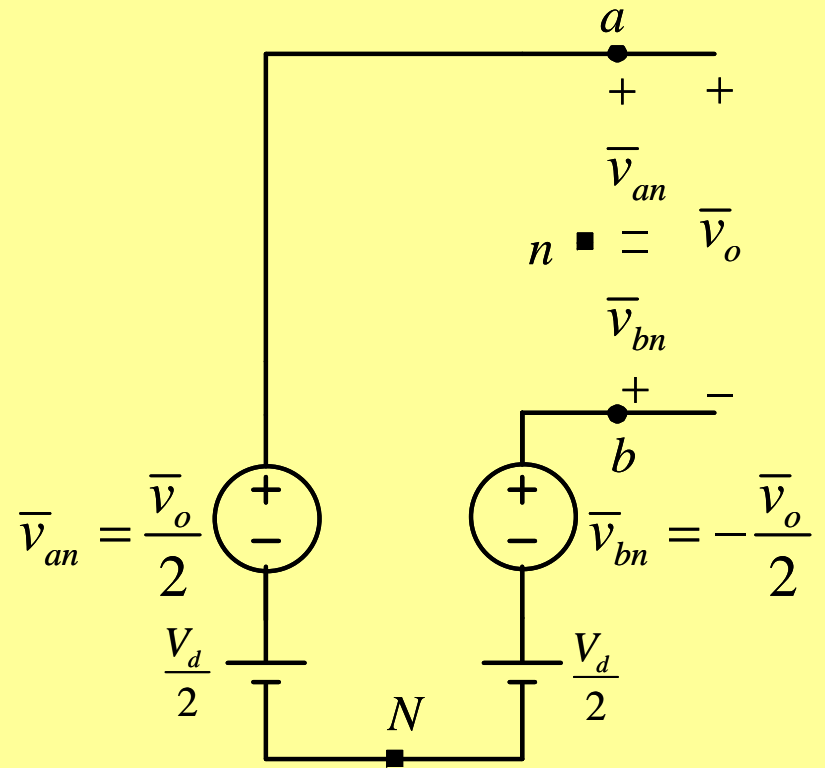

(b)

$$\bar{v}_{an} = \frac{\bar{v}_o}{2}$$


$$\bar{v}_{bn} = -\frac{\bar{v}_o}{2}$$

$$\bar{v}_{com} = \frac{V_d}{2}$$

$$\bar{v}_{aN} = \bar{v}_{com} + \bar{v}_{an}$$

$$\bar{v}_{bN} = \bar{v}_{com} + \bar{v}_{bn}$$

DC-MOTOR DRIVE: Average Representation:

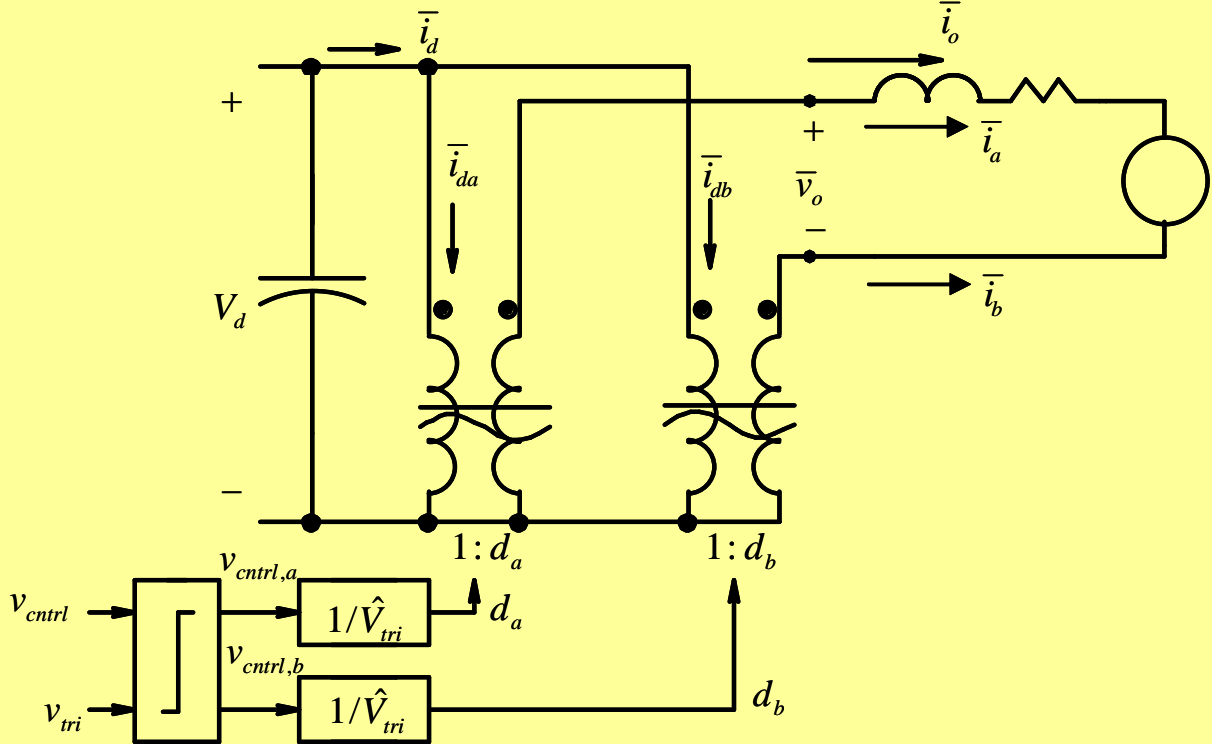


$$\bar{v}_{aN} = \frac{V_d}{2} + \frac{\bar{v}_o}{2}$$

$$d_a = \frac{1}{2} + \frac{1}{2} \frac{\bar{v}_o}{V_d}$$


$$\bar{v}_{bN} = \frac{V_d}{2} - \frac{\bar{v}_o}{2}$$

$$d_b = \frac{1}{2} - \frac{1}{2} \frac{\bar{v}_o}{V_d}$$


Gain of the DC-Drive Converter:

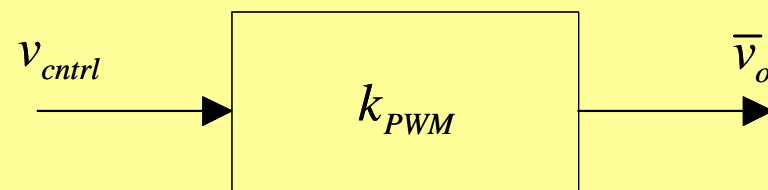


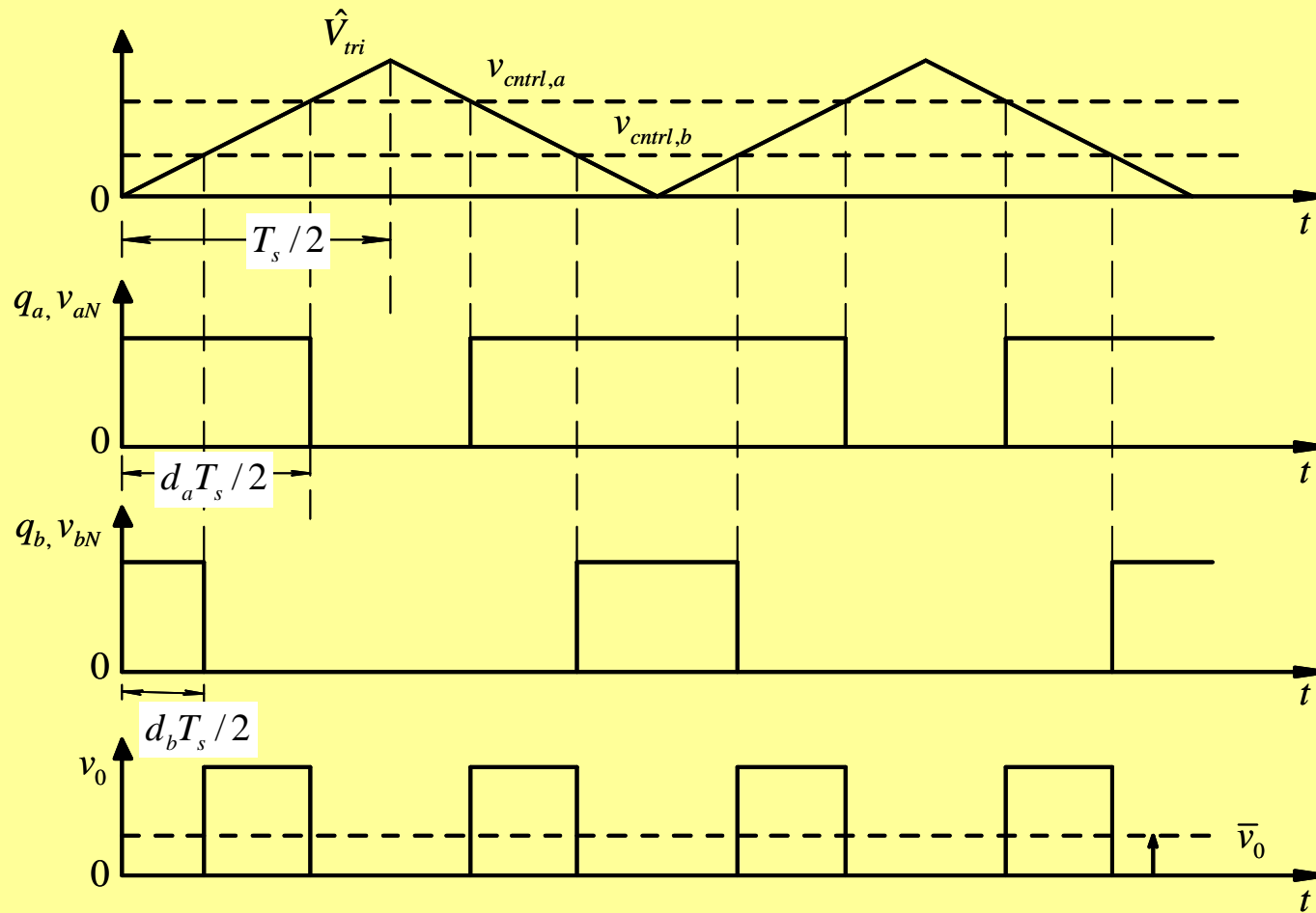Switching Waveforms in a DC-Drive Converter:



Currents in a DC-Drive Converter:

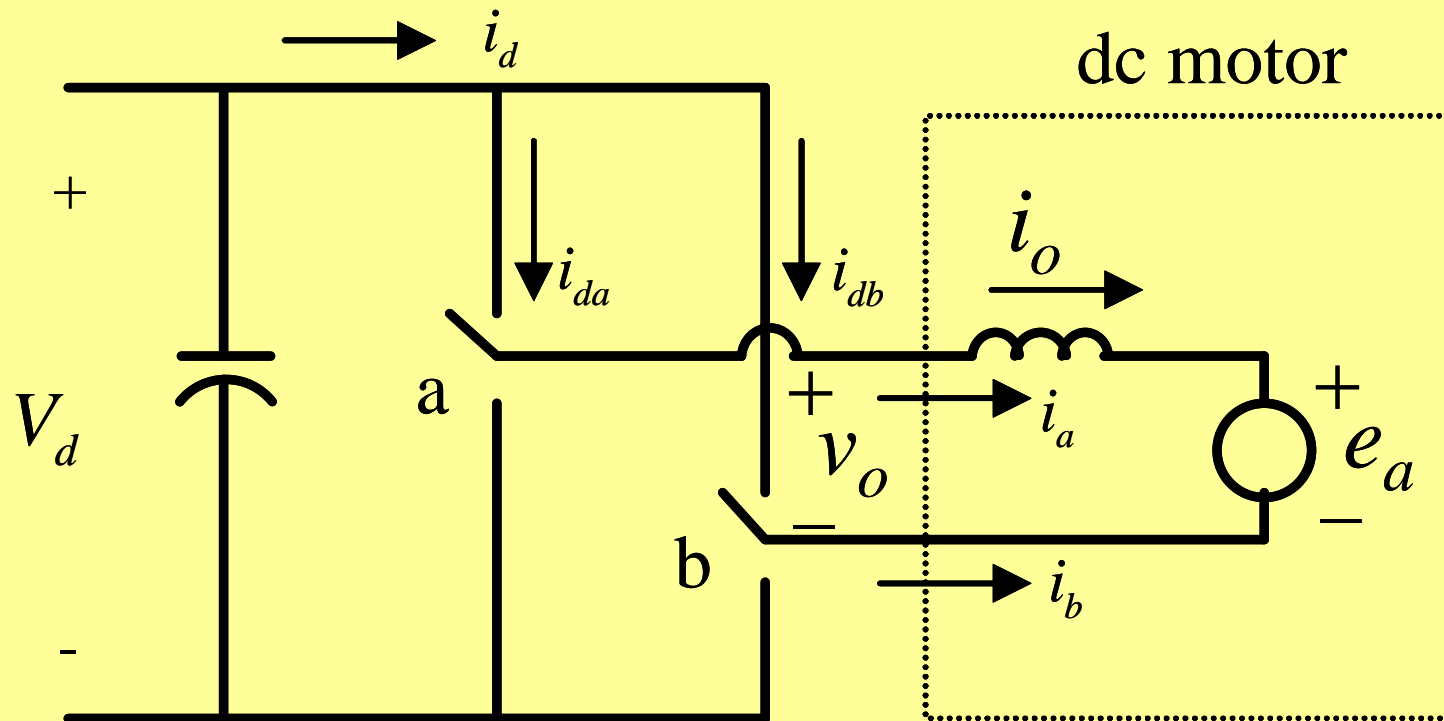

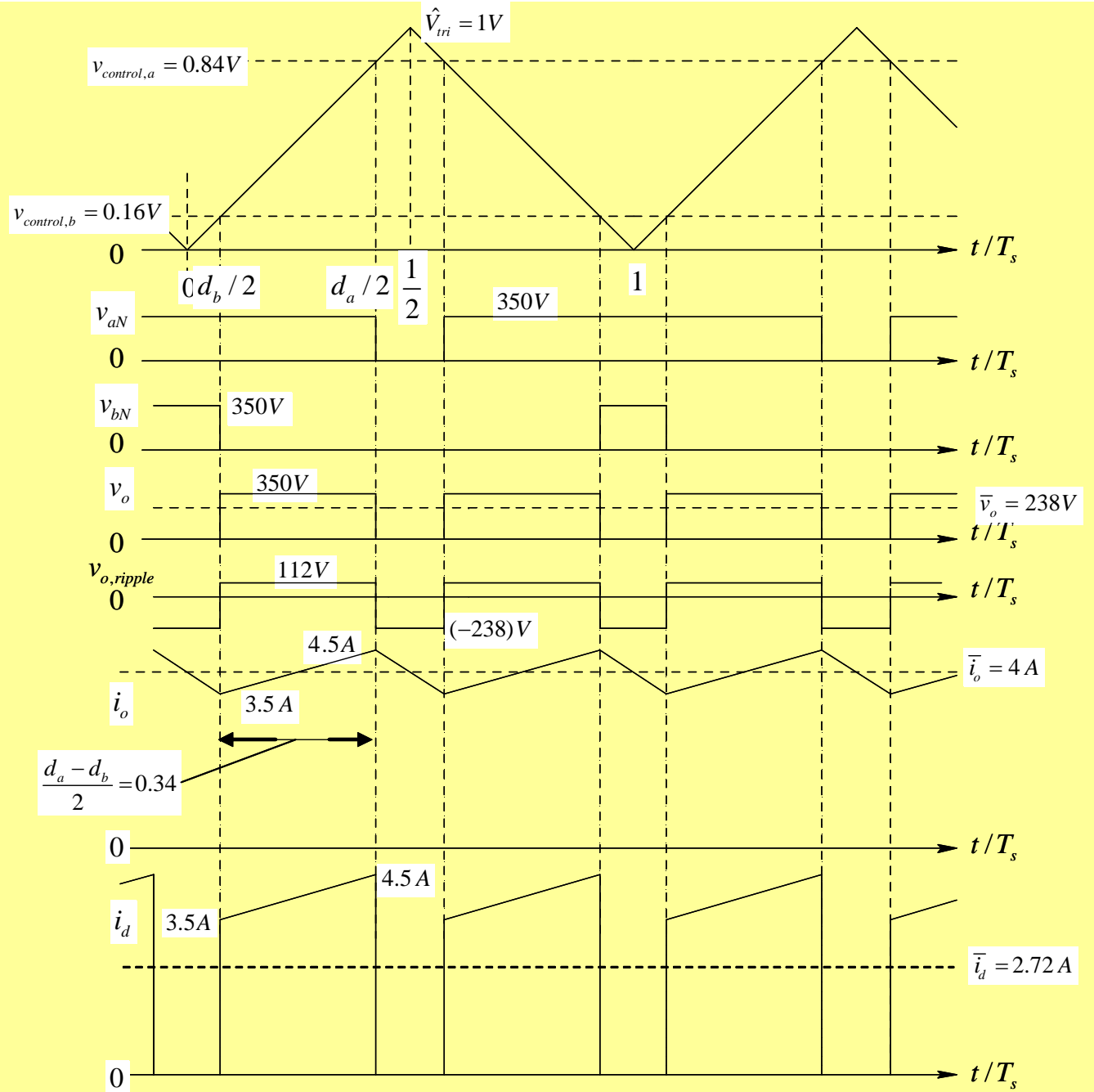

Summary

Synthesis of DC and Sinusoidal AC Voltages

- Applications in
 - Electric Drives
 - UPS
 - Power Systems