
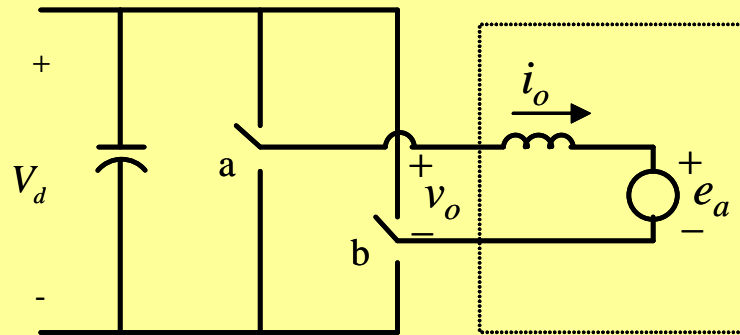


Synthesis of Single-Phase AC

Applications:


- UPS
- PV Systems

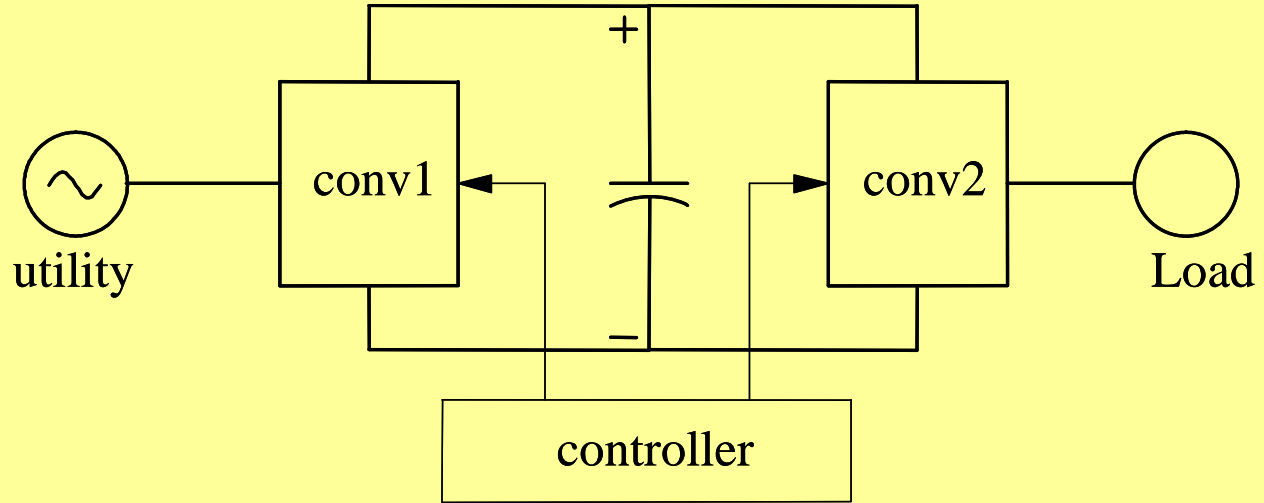


Average Representation of the Switching Power-Pole

$$\bar{v}_{aN} = d_a V_d$$


$$\bar{i}_{da} = d_a \bar{i}_a$$

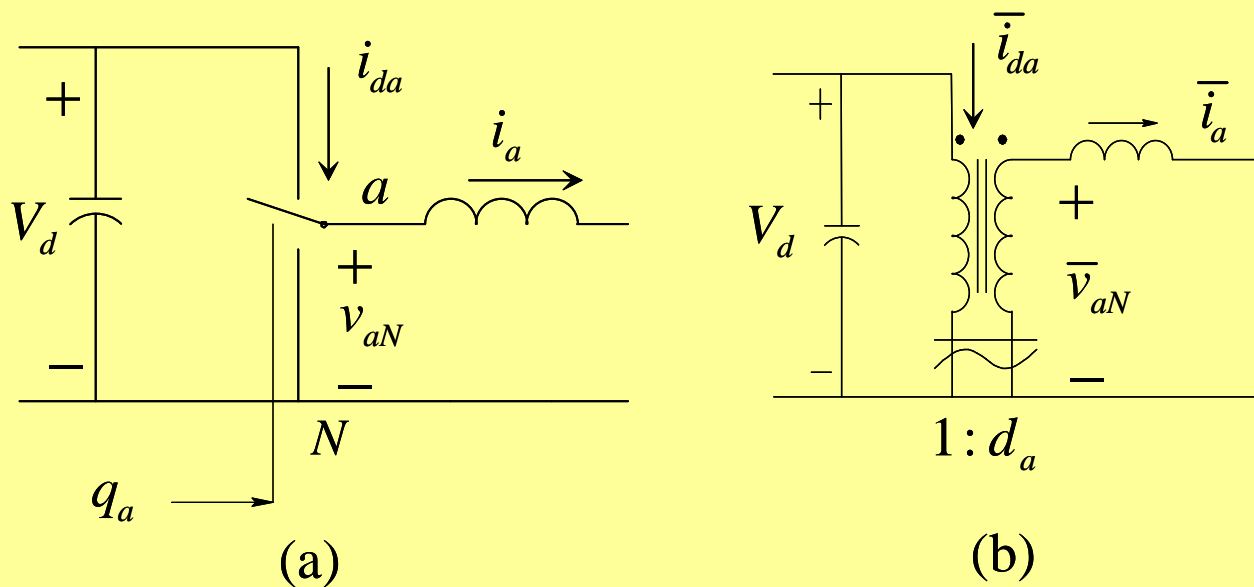


Synthesis of Low-Frequency AC:

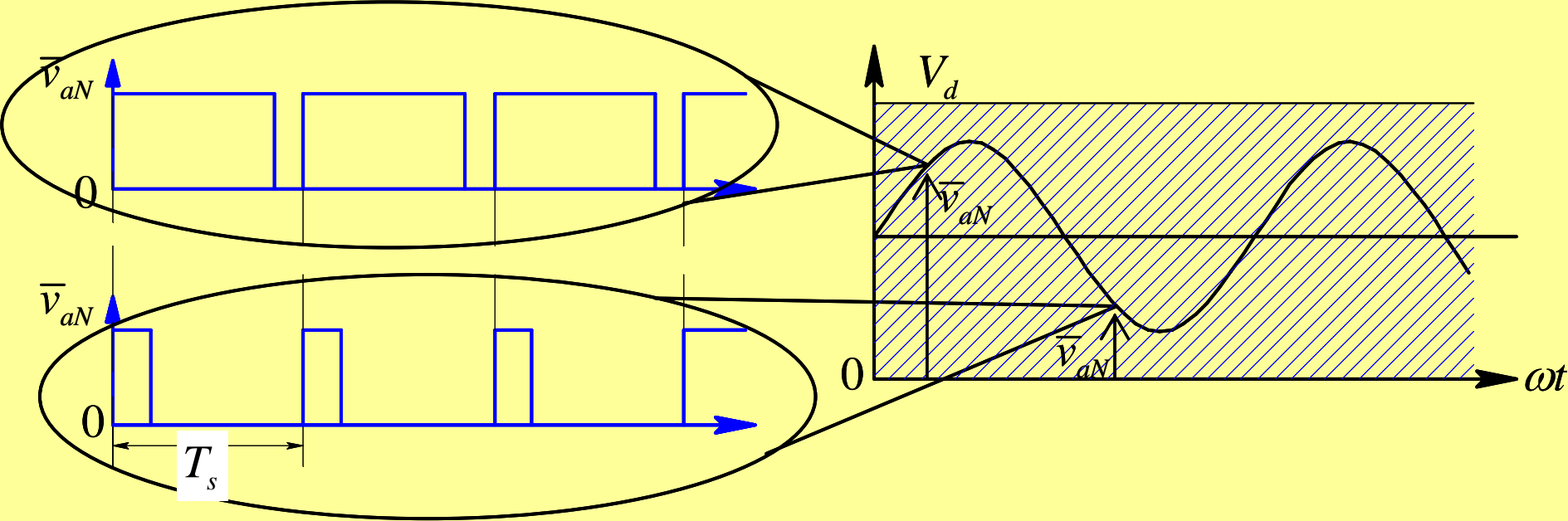

DC-MOTOR DRIVES

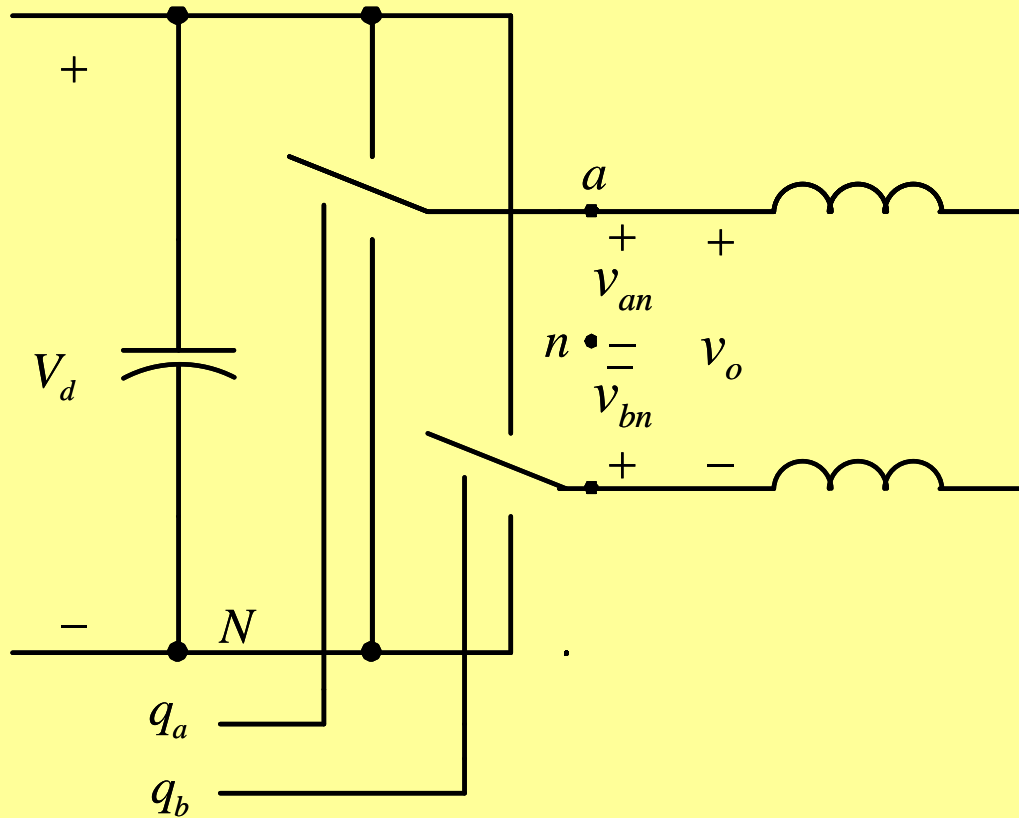

(a)

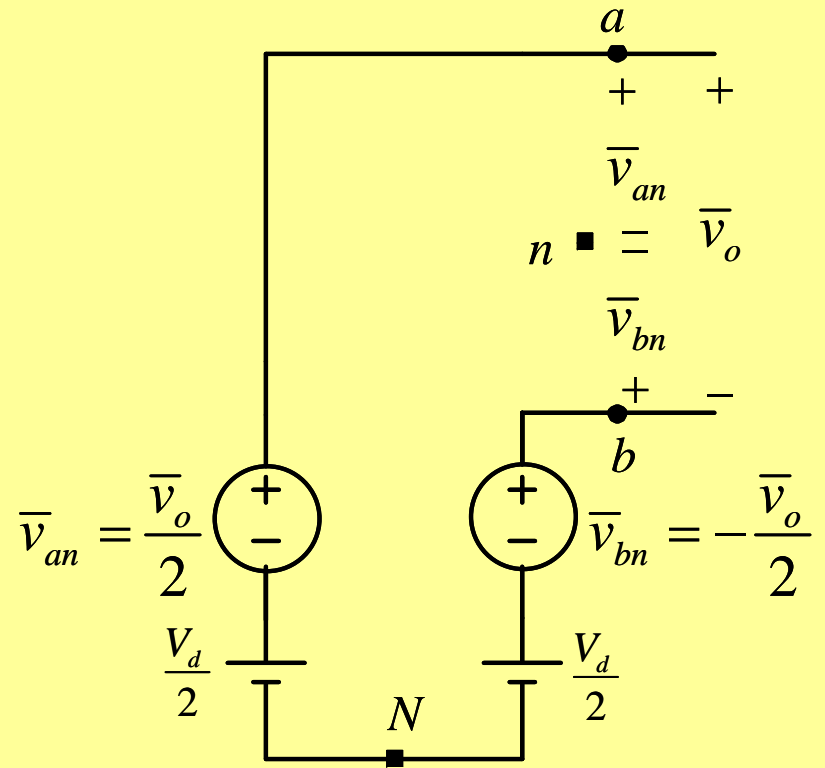

(b)

$$\bar{v}_{an} = \frac{\bar{v}_o}{2}$$

$$\bar{v}_{bn} = -\frac{\bar{v}_o}{2}$$


$$\bar{v}_{com} = \frac{V_d}{2}$$

$$\bar{v}_{aN} = \bar{v}_{com} + \bar{v}_{an}$$


$$\bar{v}_{bN} = \bar{v}_{com} + \bar{v}_{bn}$$

Single-Phase Inverters:
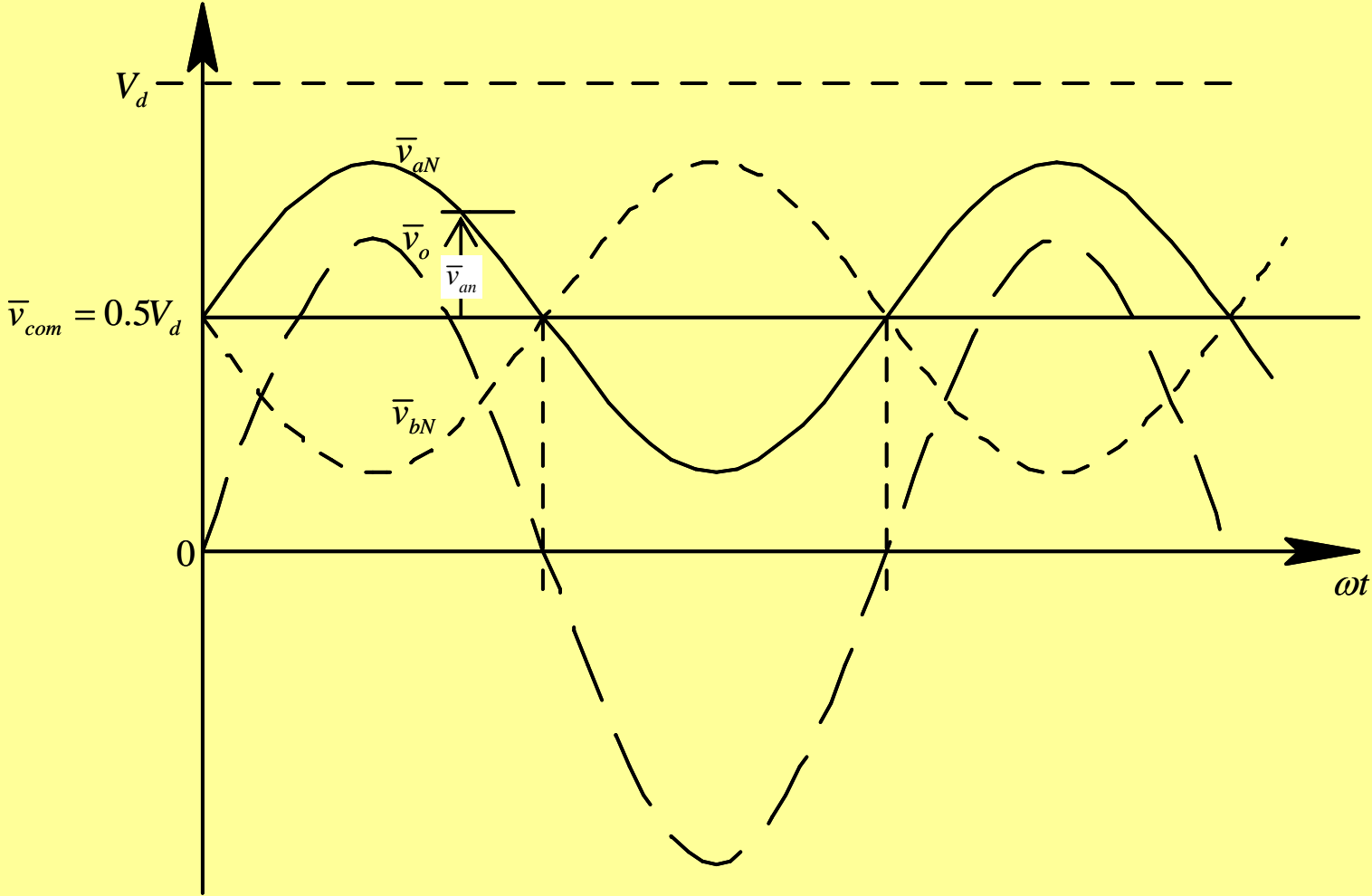
$$\bar{v}_{aN} = \frac{V_d}{2} + \frac{\bar{v}_o}{2} \qquad \bar{v}_{bN} = \frac{V_d}{2} - \frac{\bar{v}_o}{2}$$



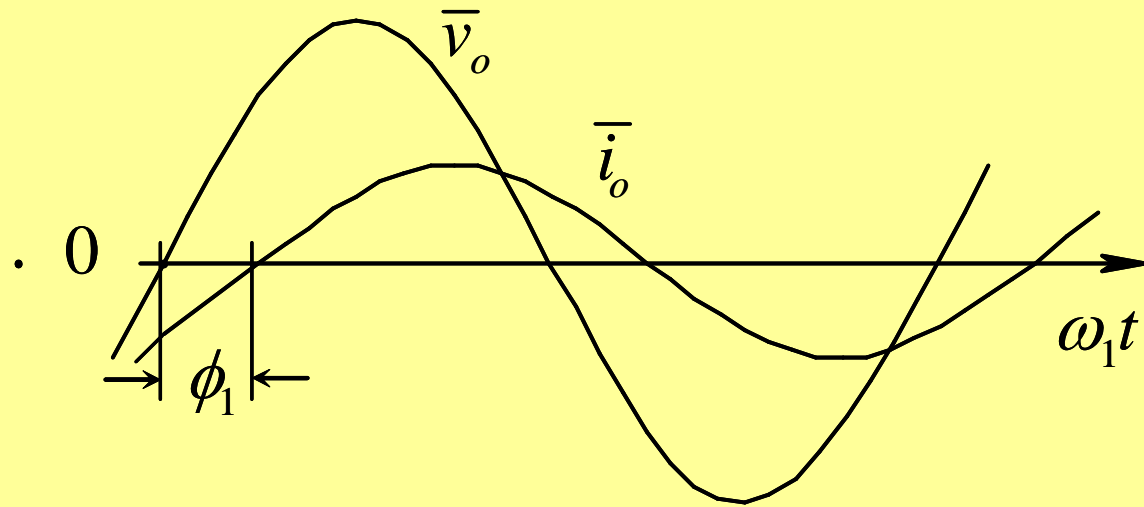Single-Phase Inverters - Output Voltage and Current:



$$\bar{i}_d = \frac{\bar{v}_o \bar{i}_o}{V_d} = \frac{\hat{V}_o \hat{I}_o}{V_d} \sin \omega_1 t \times \sin(\omega_1 t - \phi_1) = \underbrace{0.5 \frac{\hat{V}_o}{V_d} \hat{I}_o \cos \phi_1}_{I_d} - \underbrace{0.5 \frac{\hat{V}_o}{V_d} \hat{I}_o \cos(2\omega_1 t - \phi_1)}_{i_{d2}(t)}$$

Summary

Synthesis of Single-Phase AC:

- UPS
- PV Systems