
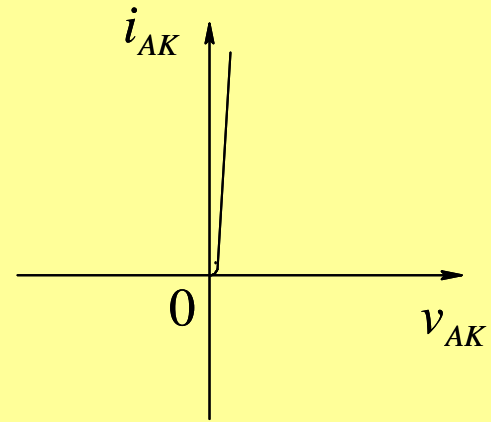


Design of Switching Power-Poles


- Power Semiconductor Devices
 - Diodes
 - Transistors
- Losses in Switching Power-Poles
 - Switching Losses
 - Conduction Losses

Choice of Diodes

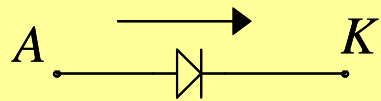


- Line-Frequency Diodes
- Fast Recovery Diodes
- Schottky Diodes

Choice of Power Transistors

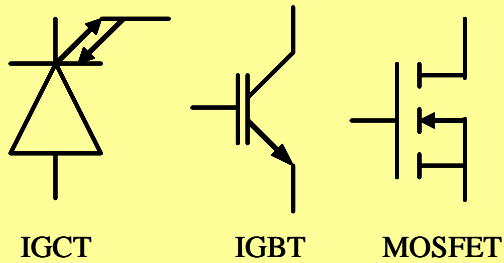

(a)

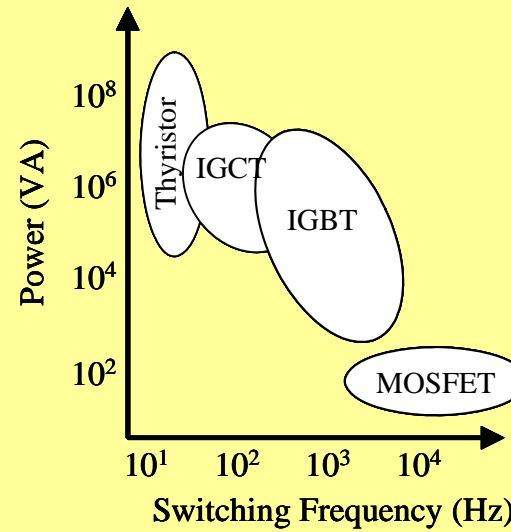


- MOSFET
- IGBT
- IGCT
- GTO
- Others


SELECTION OF POWER TRANSISTORS AND POWER DIODES

- Voltage Ratings
- Current Ratings
- Switching Speeds
- On-State Voltage Drop


MOSFET Characteristics

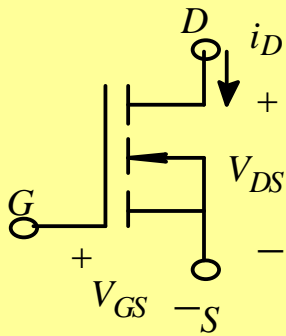

(a)

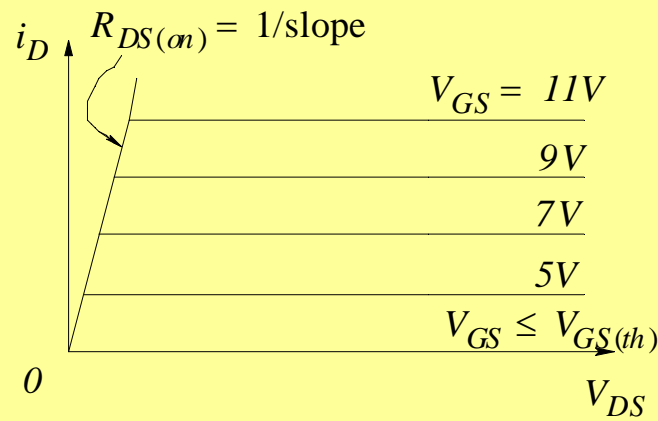


(b)

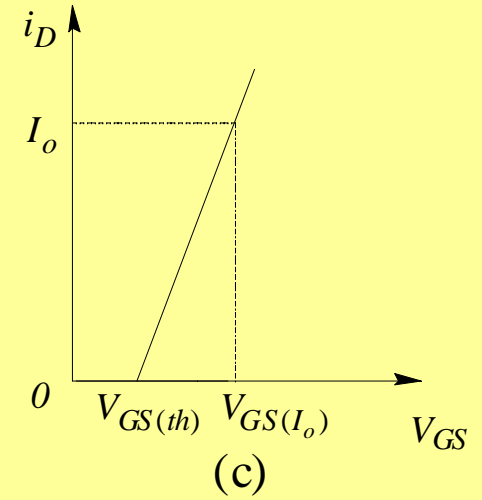


(c)

$$R_{DS(on)} \propto V_{DSS}^{2.5 \text{ to } 2.7}$$

IGBT Characteristics



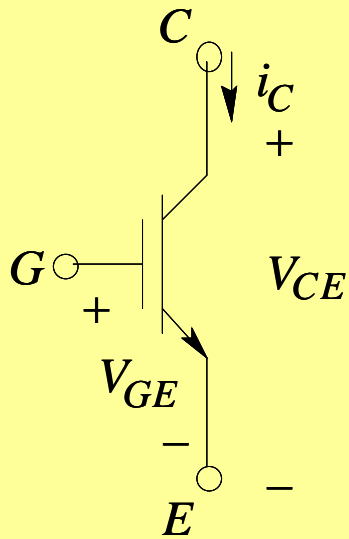


(a)



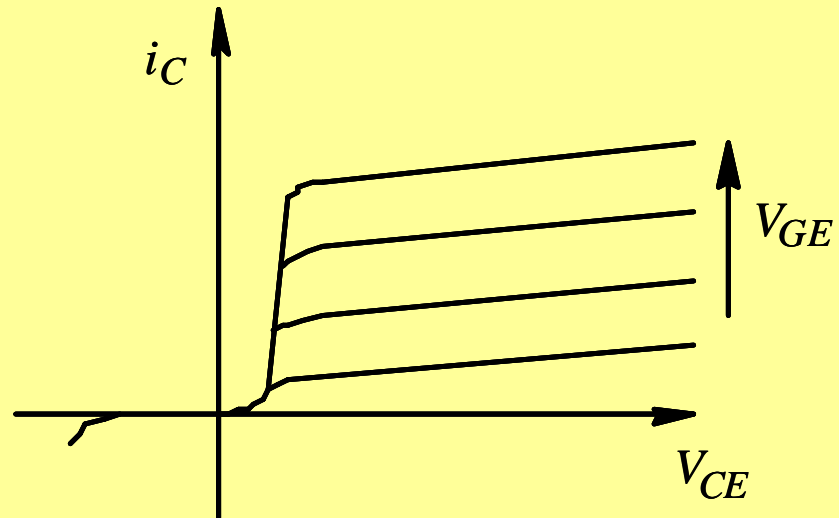


(b)


Switching in a Power-Pole

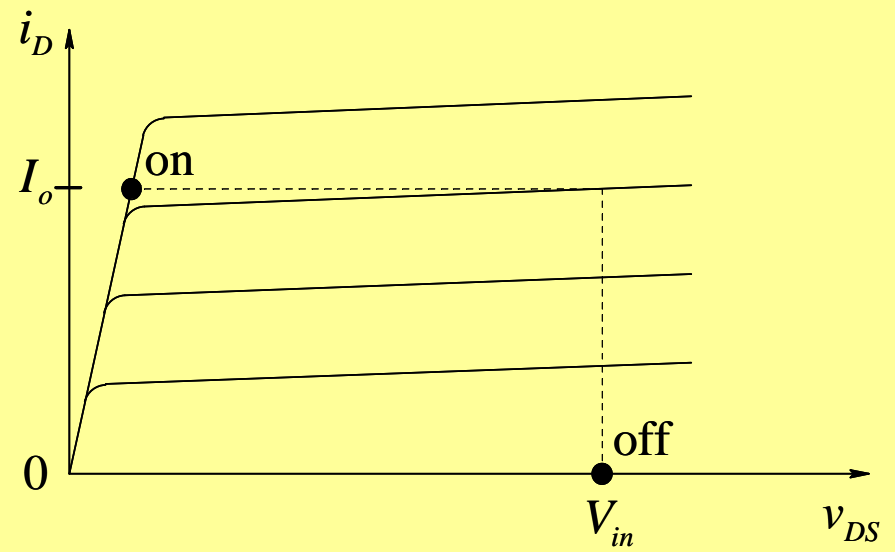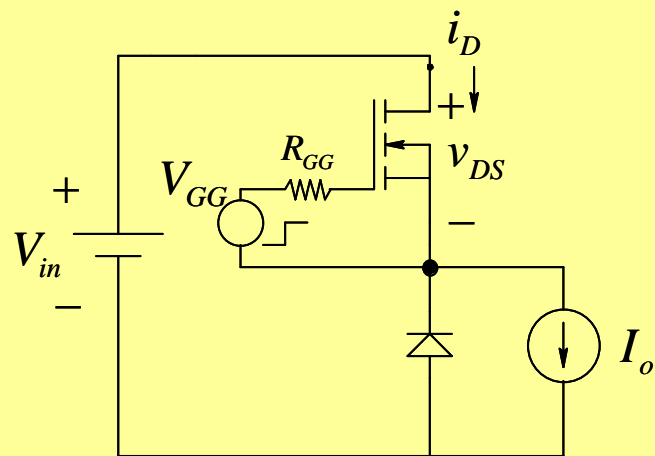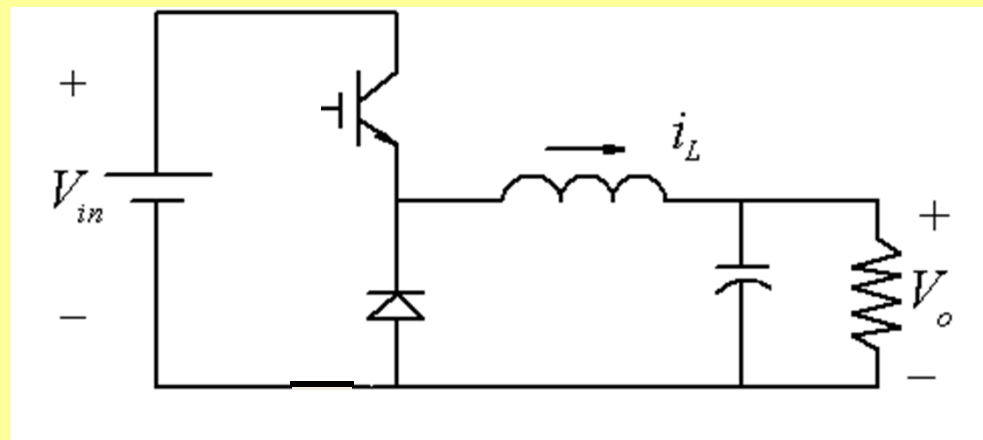





Turn-on Characteristics

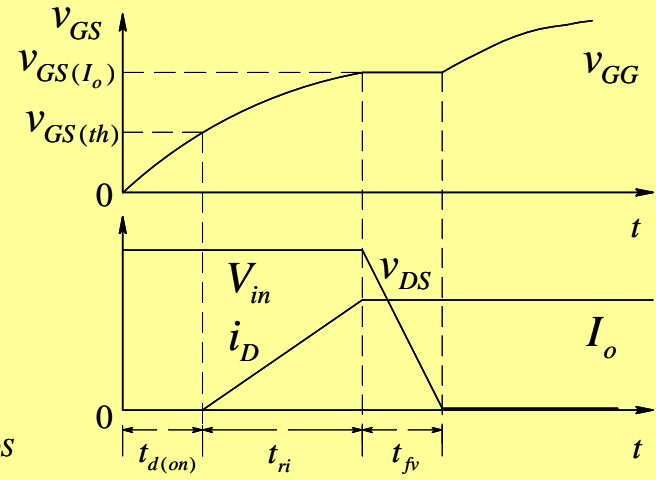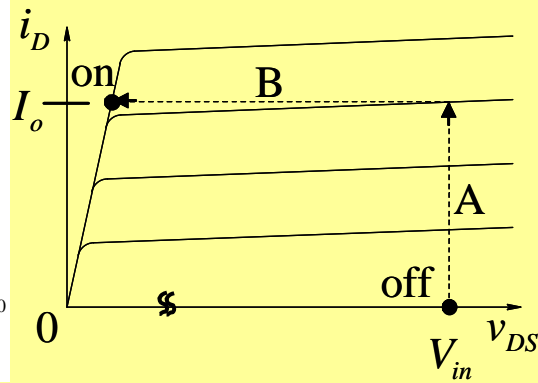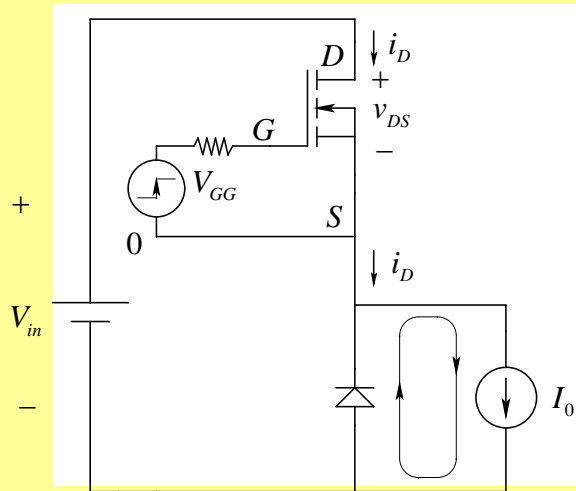

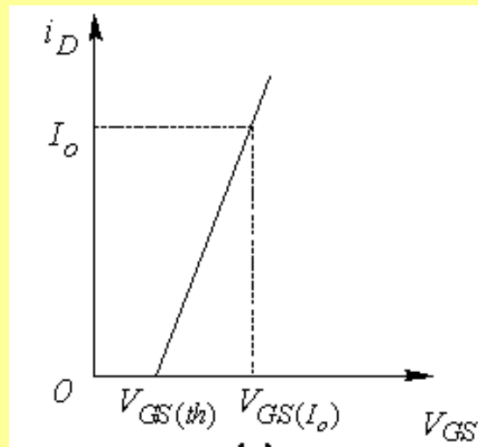
$$i_{diode} = I_o - i_D \quad i_D \leq I_o$$



Turn-off Characteristic

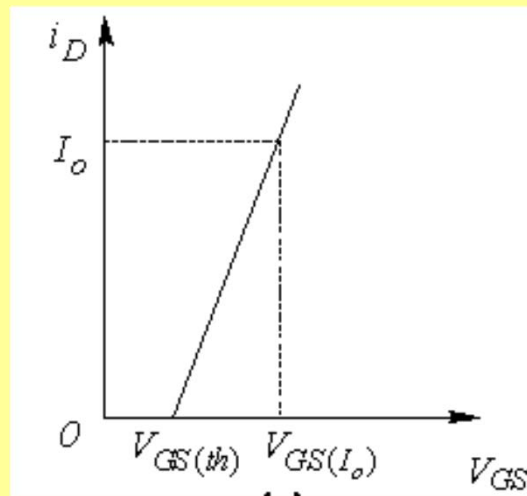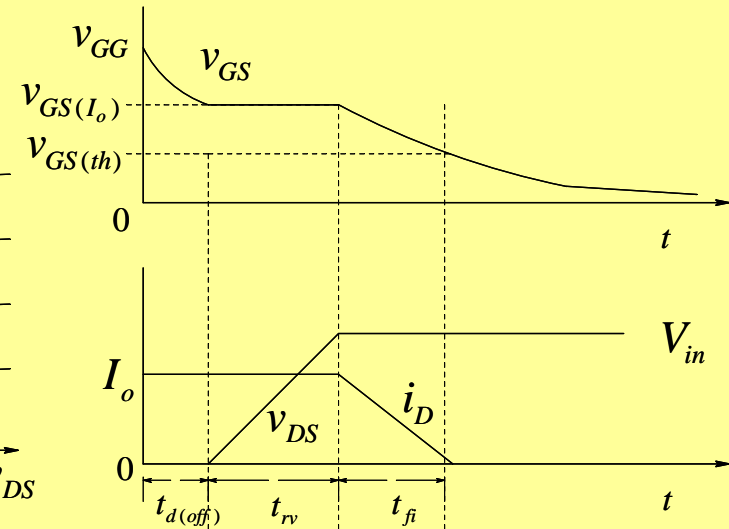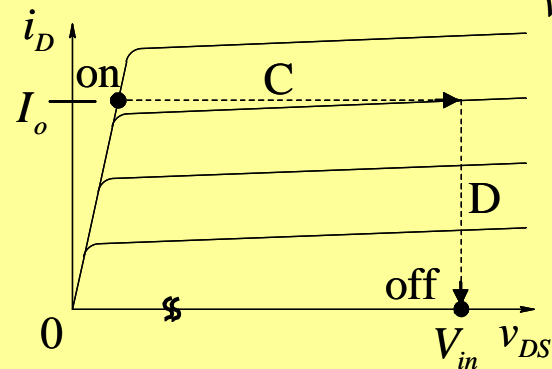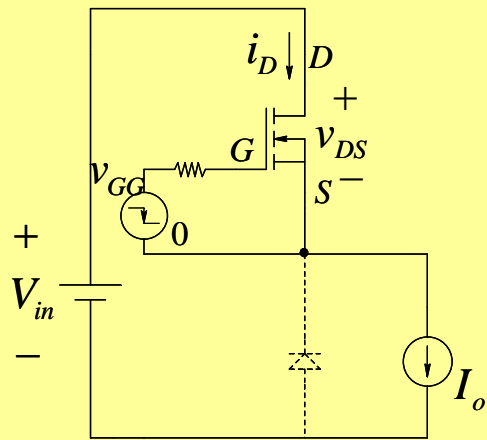

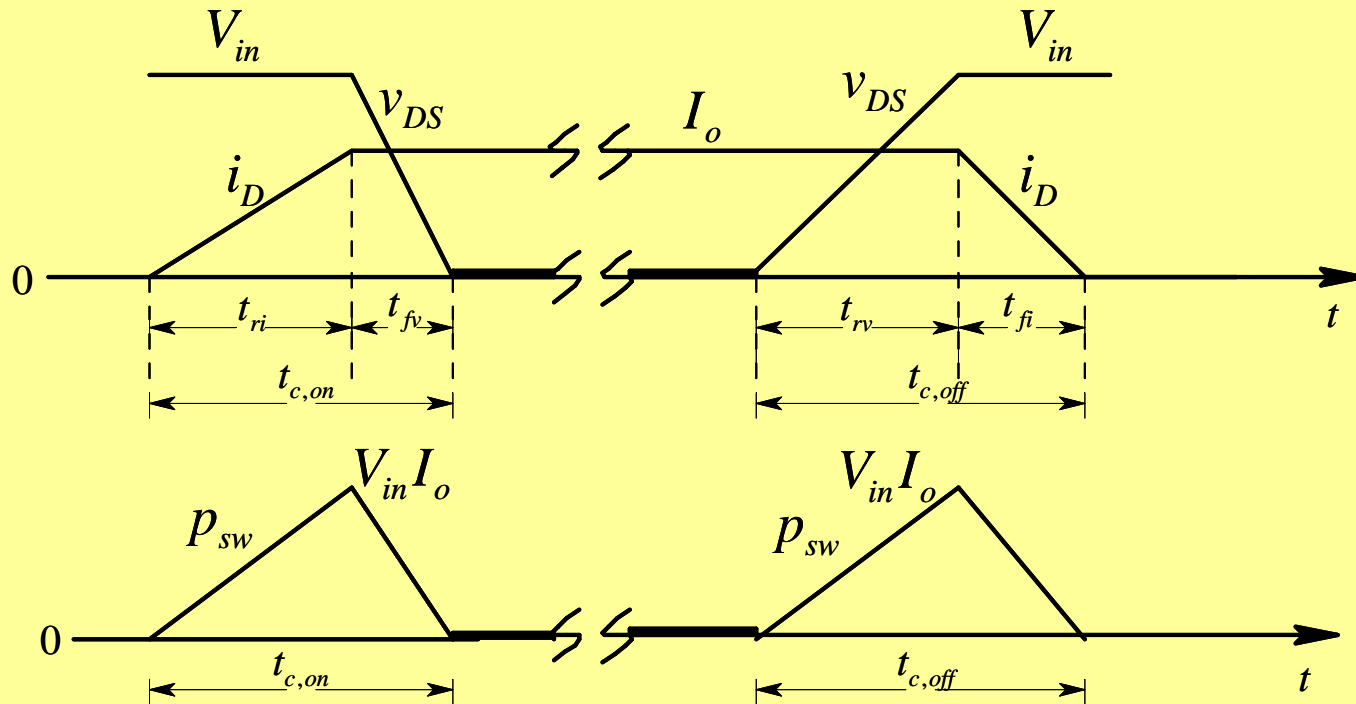Calculating Power Losses Within the MOSFET (assuming an ideal diode)




Switching Losses:

$$P_{sw} = \frac{1}{2} V_{in} I_o (t_{c,on} + t_{c,off}) f_s$$

$$t_{c,on} = t_{ri} + t_{fv}$$

$$t_{c,off} = t_{rv} + t_{fi}$$

Conduction Loss:

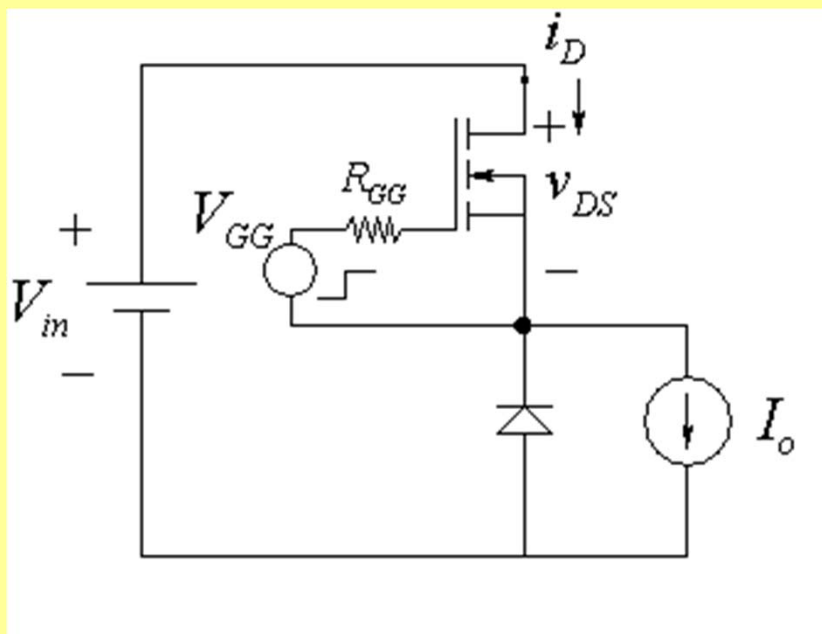

$$P_{cond} = d \left(R_{DS(on)} I_o^2 \right)$$

Summary

- Design of a Switching Power-Pole
 - Power Semiconductor Devices
 - Diodes
 - Transistors
 - Losses in Switching Power-Poles
 - Switching Losses
 - Conduction Losses