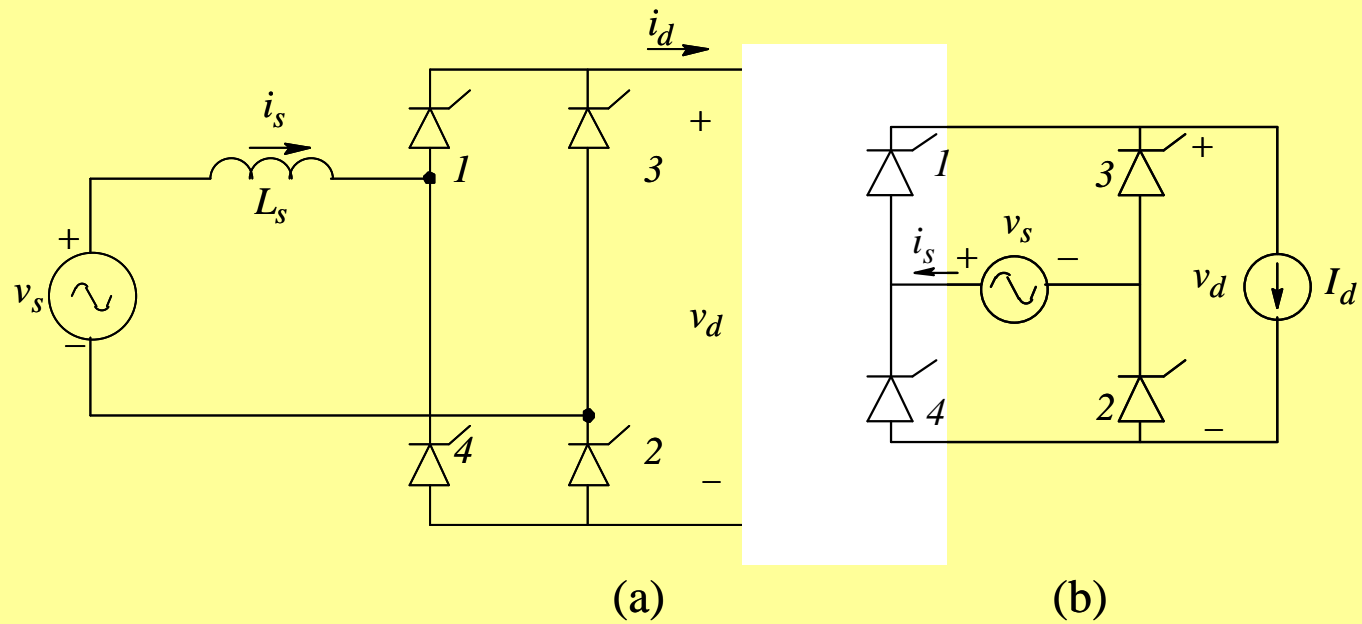




Thyristor Converters



- Single-Phase Thyristor Inverter Operation


Single-Phase, Phase-Controlled Thyristor Converters



Review: Diode Rectifiers

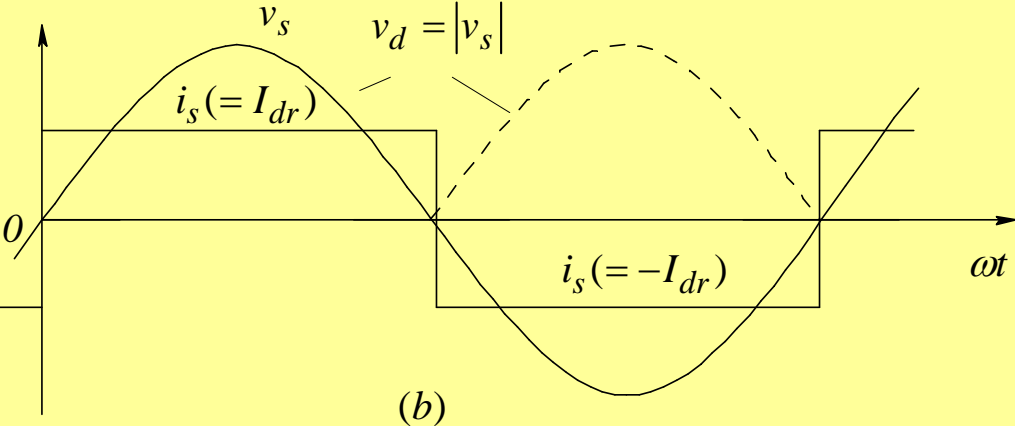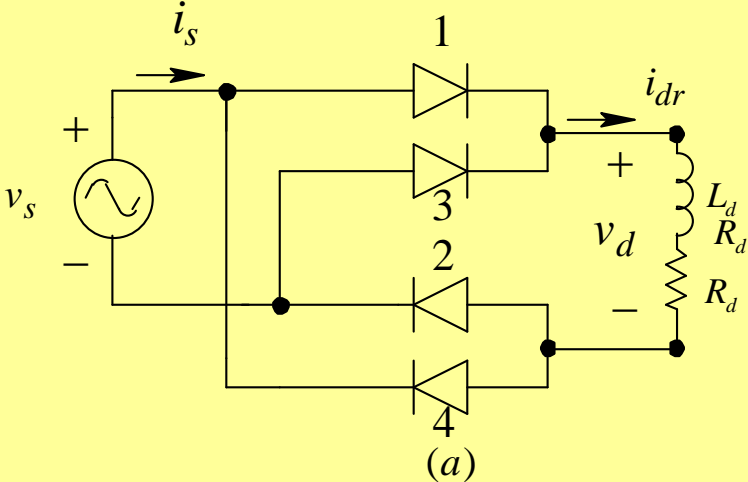

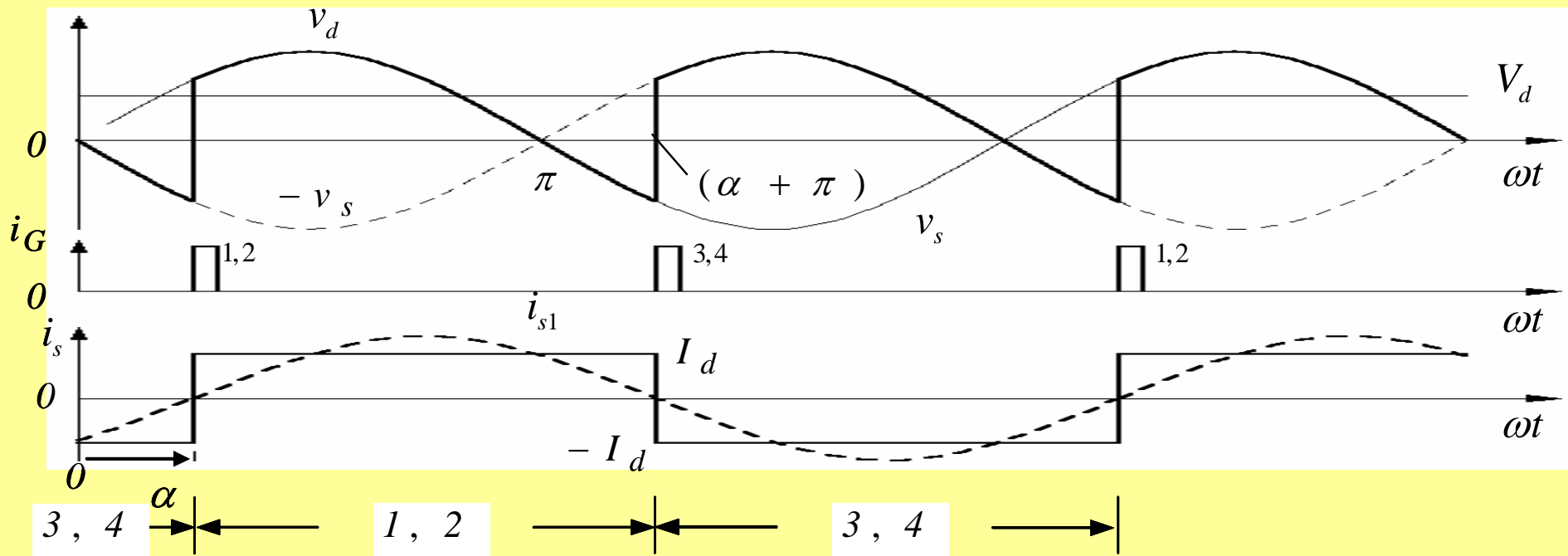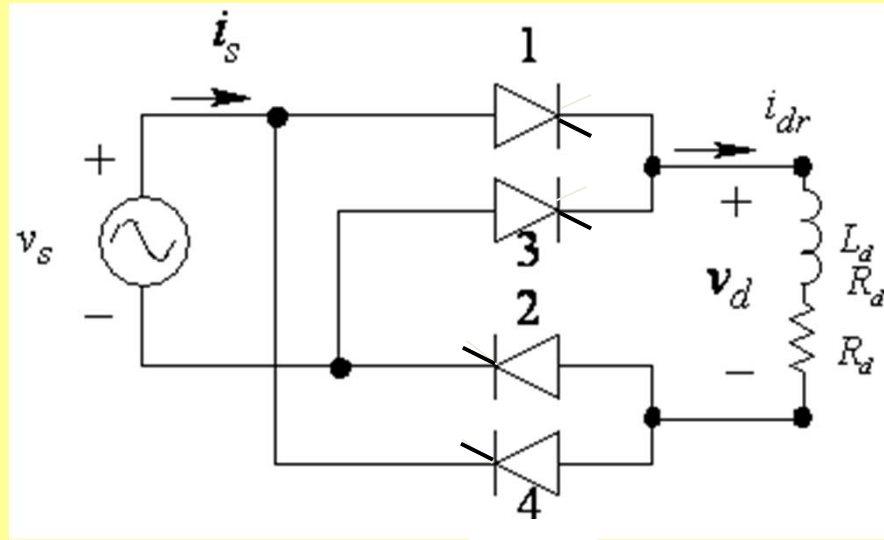

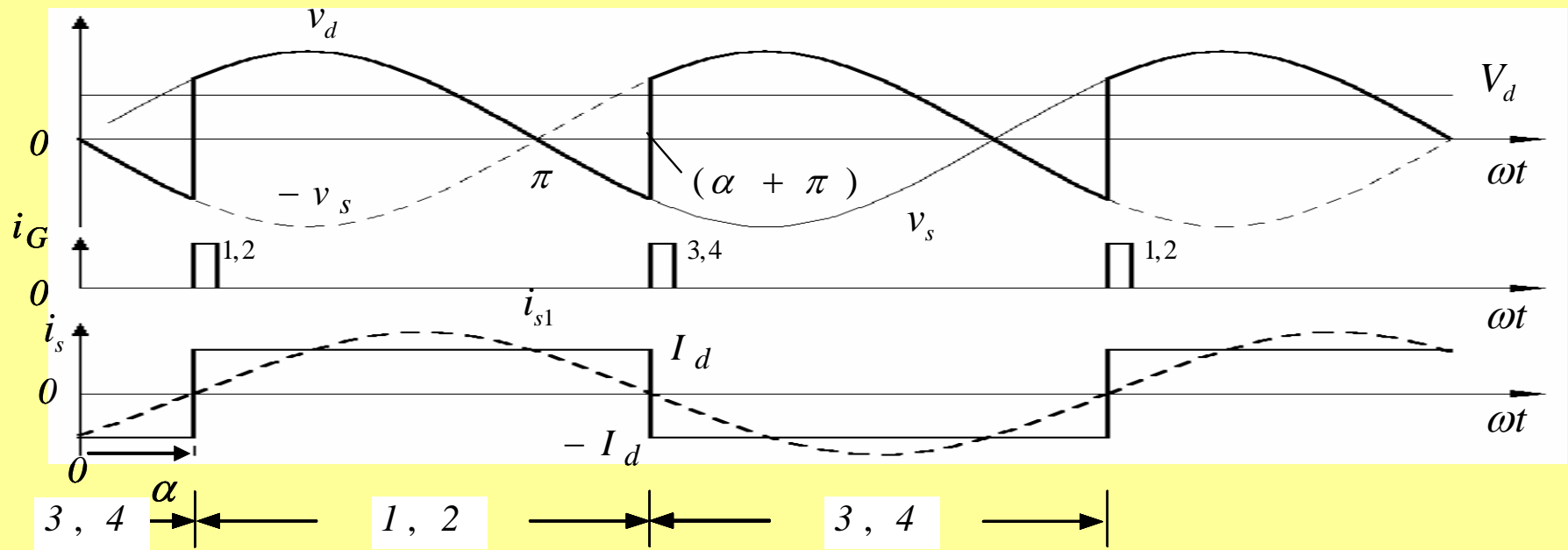

$$v_d(t) = v_s(t) \quad \text{and} \quad i_s(t) = I_d \quad \alpha < \omega t \leq \alpha + \pi$$

$$v_d(t) = -v_s(t) \quad \text{and} \quad i_s(t) = -I_d \quad \alpha + \pi < \omega t \leq \alpha + 2\pi$$



$$V_d = \frac{1}{\pi} \int_{\alpha}^{\alpha+\pi} \hat{V}_s \sin \omega t \cdot d(\omega t) = \frac{2}{\pi} \hat{V}_s \cos \alpha$$

$$\hat{I}_{s1} = \frac{4}{\pi} I_d$$


$$P = \frac{1}{2} \hat{V}_s \hat{I}_{s1} \cos \alpha$$

$$= V_d I_d$$

Effect of Delay Angle:

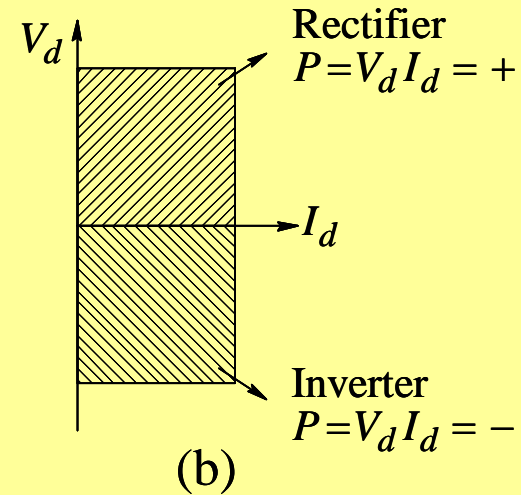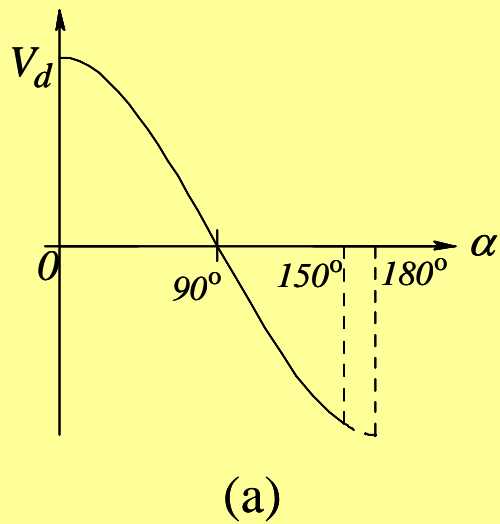
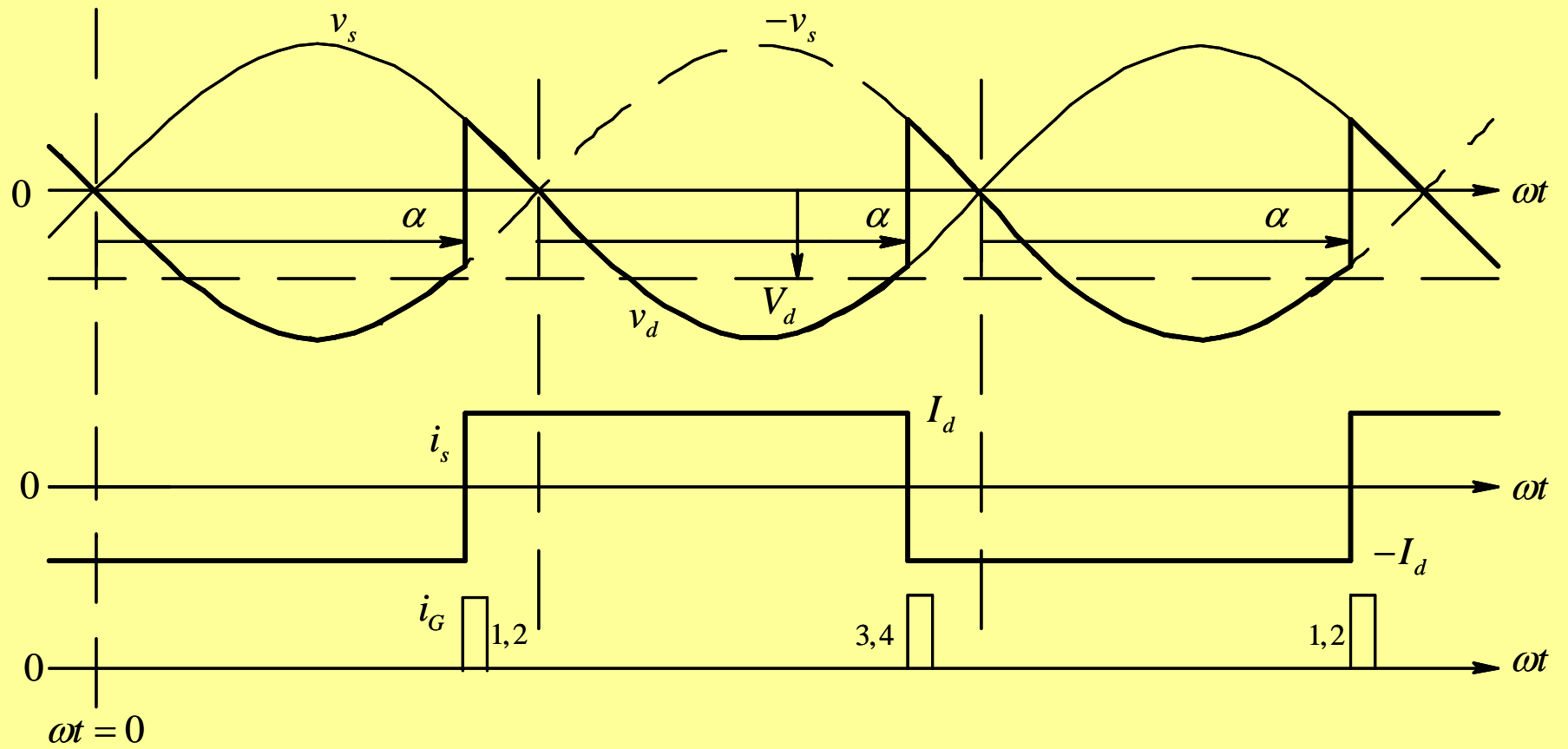
$$V_d = \frac{1}{\pi} \int_{\alpha}^{\alpha+\pi} \hat{V}_s \sin \omega t \cdot d(\omega t) = \frac{2}{\pi} \hat{V}_s \cos \alpha$$




Current Harmonics and the Reactive Power:


$$\hat{I}_{sh} = \frac{\hat{I}_{s1}}{h}$$

$$Q = \frac{1}{2} \hat{V}_s \hat{I}_{s1} \sin \alpha$$

The Effect of L_s on Current Commutation

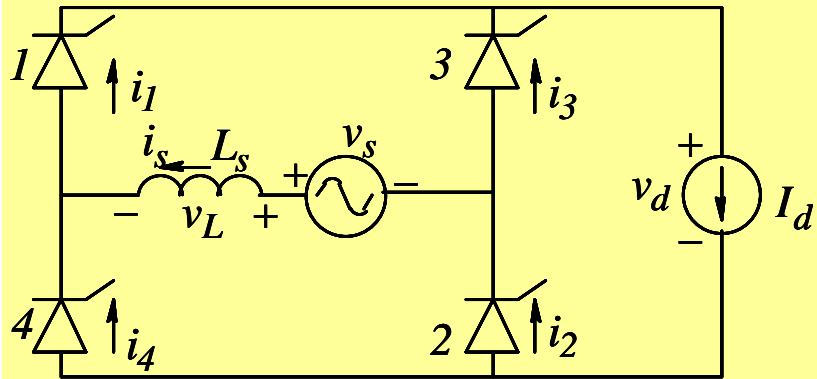

(a)

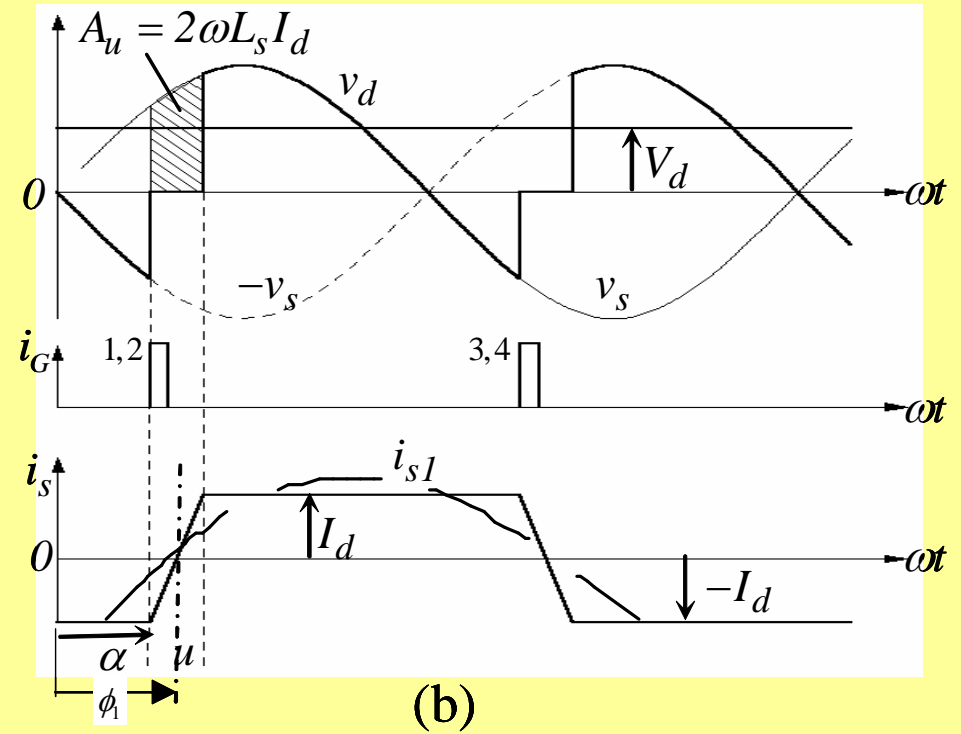

(b)

$$\int_{\alpha}^{\alpha+u} v_L d(\omega t) = L_s \int_{\alpha}^{\alpha+u} \frac{di_s}{dt} d(\omega t) = \omega L_s \int_{-I_d}^{I_d} di_s = \omega L_s (2I_d)$$

$$\Delta V_d = \frac{2}{\pi} \omega L_s I_d \quad V_d = \frac{2}{\pi} V_s \cos \alpha - \frac{2}{\pi} \omega L_s I_d$$

$$\phi_1 = \alpha + \frac{u}{2} \quad Q = \frac{1}{2} \hat{V}_s \hat{I}_{s1} \sin\left(\alpha + \frac{u}{2}\right)$$

Summary

- Single-Phase Thyristor Converters
 - Inverter Mode of Operation
 - Current Commutation