
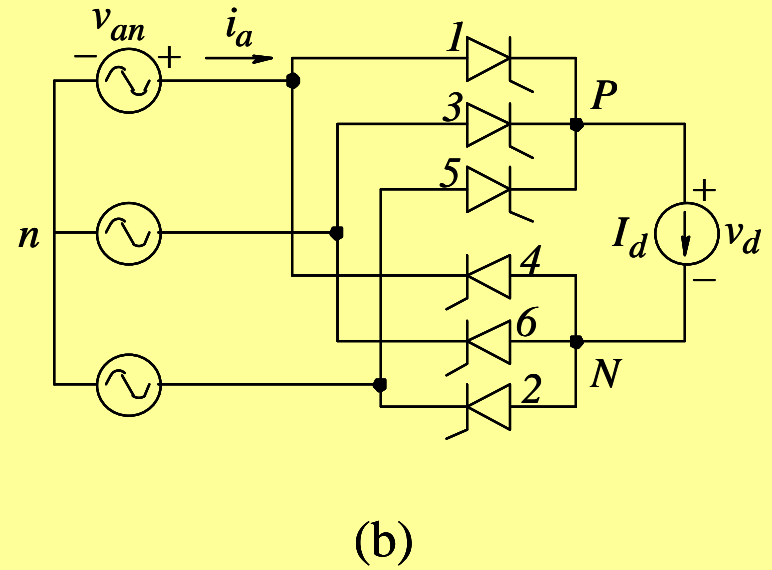





Three-Phase Thyristor Converters





- Applications
- Three-Phase Thyristor Converter Operation
- Applications in HVDC Systems

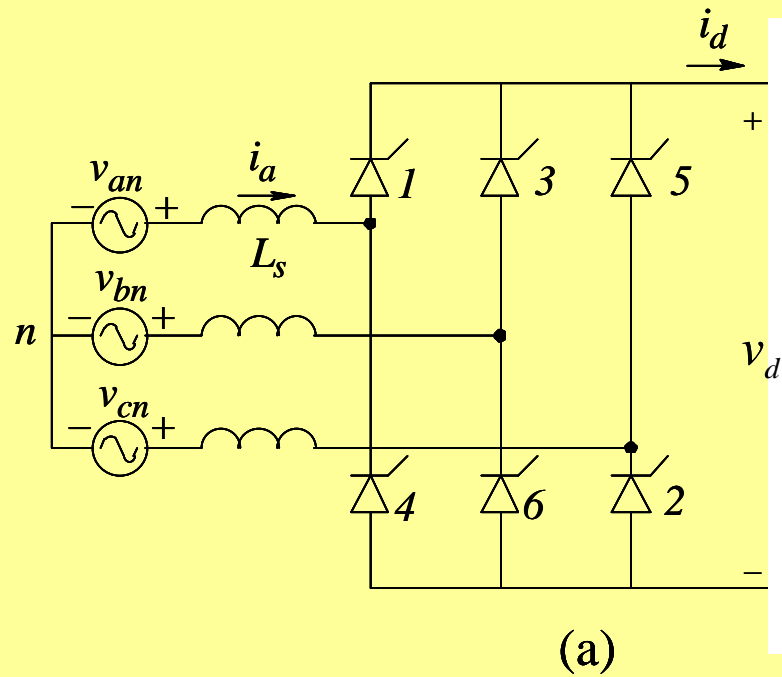
THREE-PHASE, FULL-BRIDGE THYRISTOR CONVERTERS



Three-Phase Diode Rectifier Waveforms

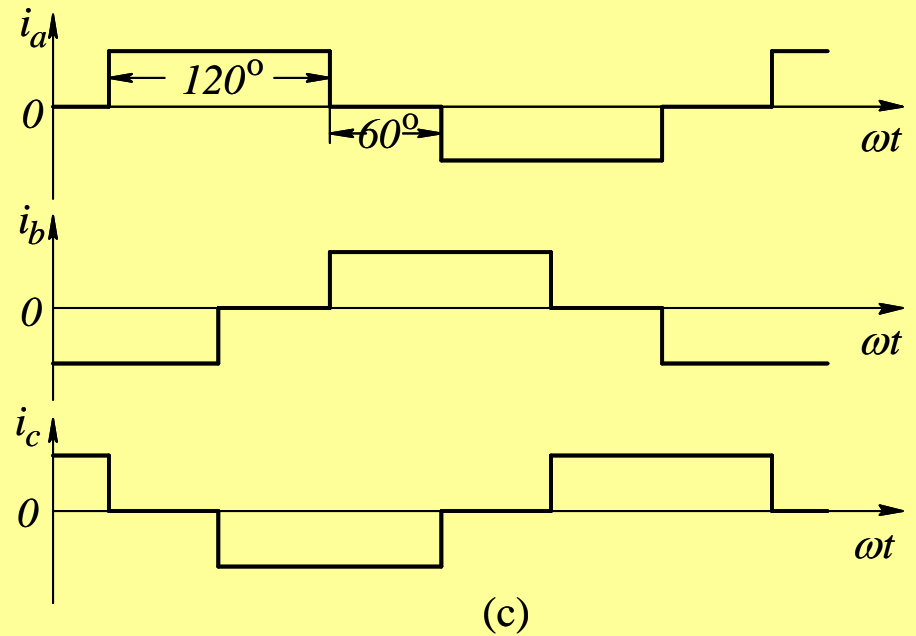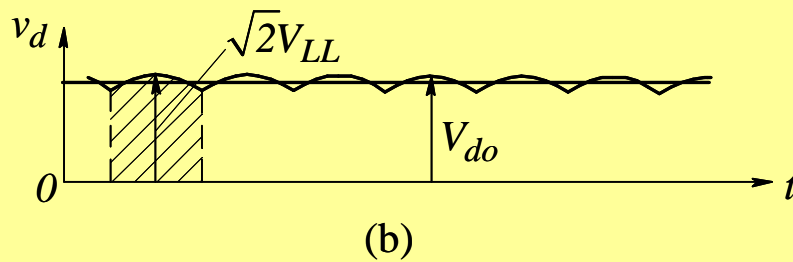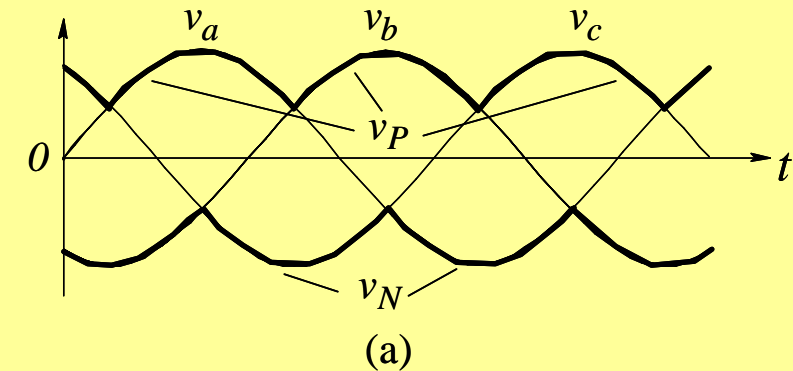

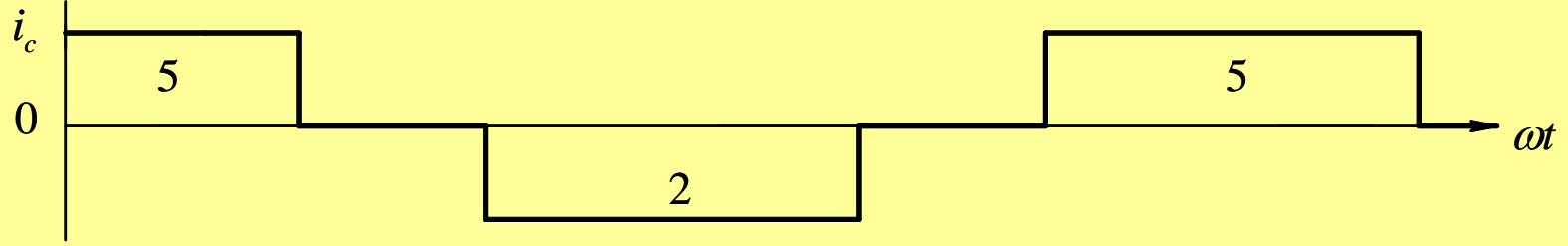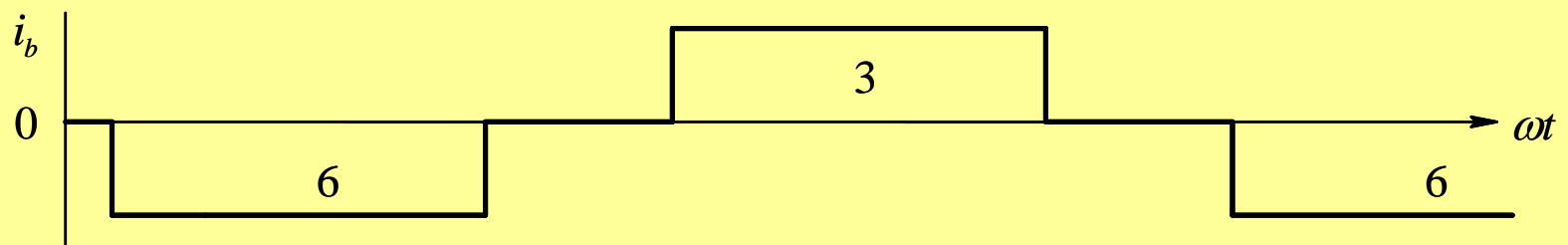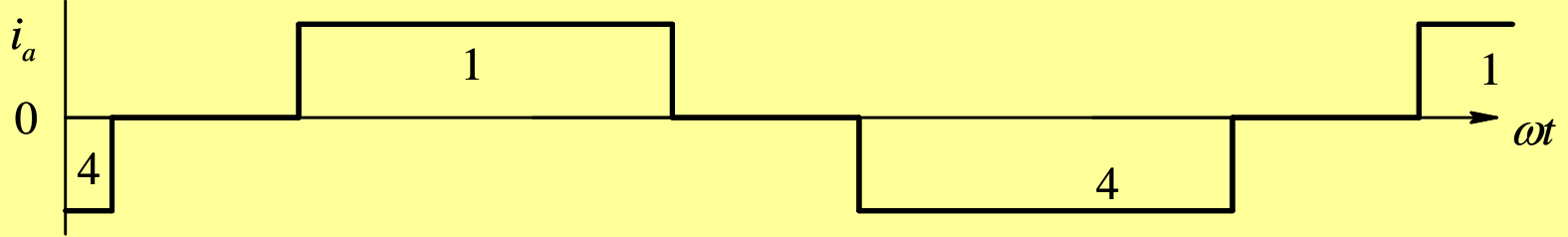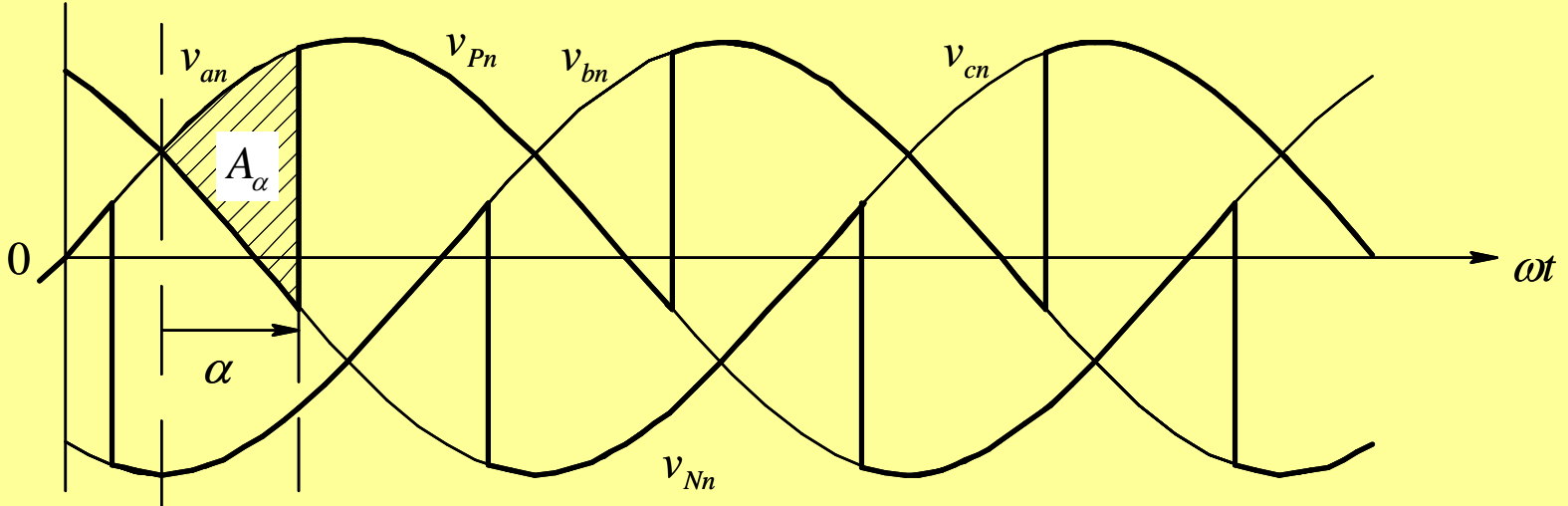


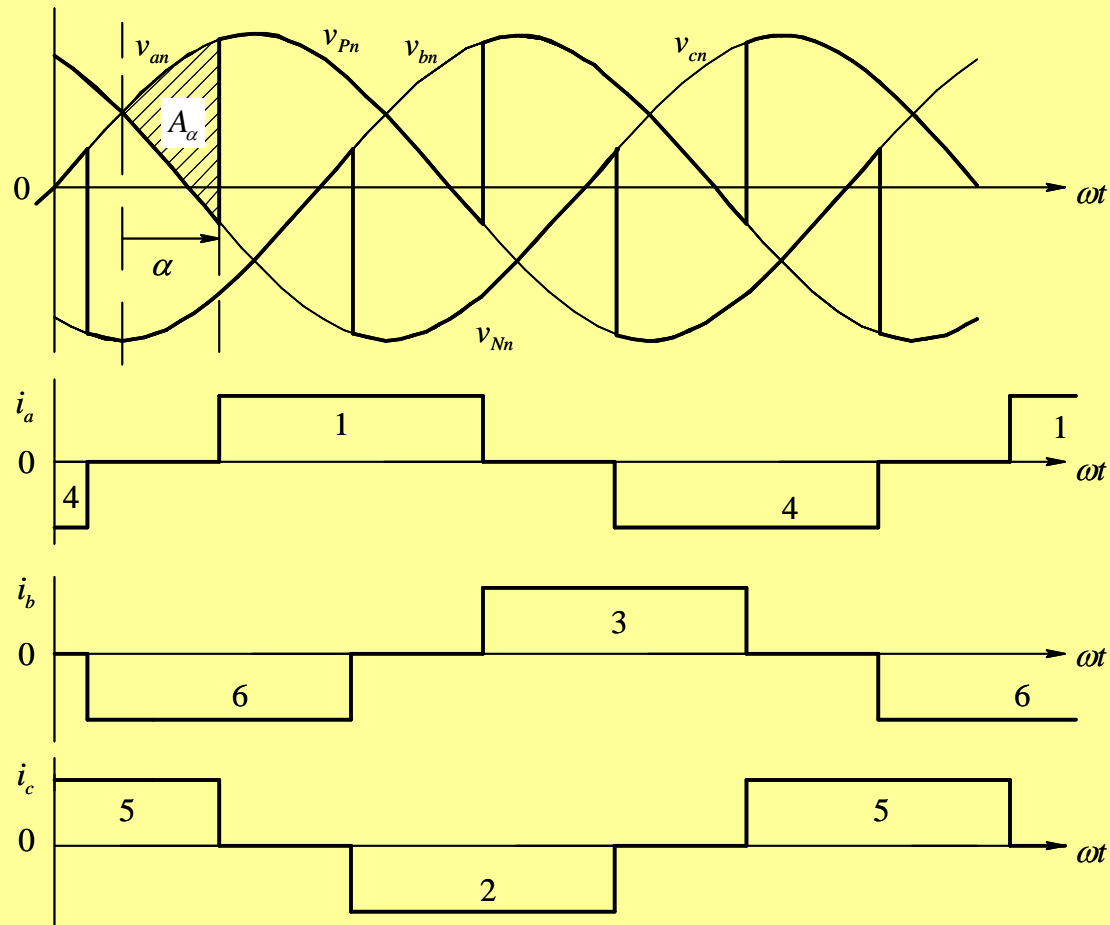


$$V_{do} = \frac{1}{\pi/3} \int_{-\pi/6}^{\pi/6} \hat{V}_{LL} \cos \omega t \cdot d(\omega t) = \frac{3}{\pi} \hat{V}_{LL} \quad \Delta V_{\alpha} = \frac{1}{\pi/3} \int_0^{\alpha} \hat{V}_{LL} \sin \omega t \cdot d(\omega t) = \frac{3}{\pi} \hat{V}_{LL} (1 - \cos \alpha)$$

$$V_{d\alpha} = \frac{3}{\pi} \hat{V}_{LL} \cos \alpha$$

Effect of L_s

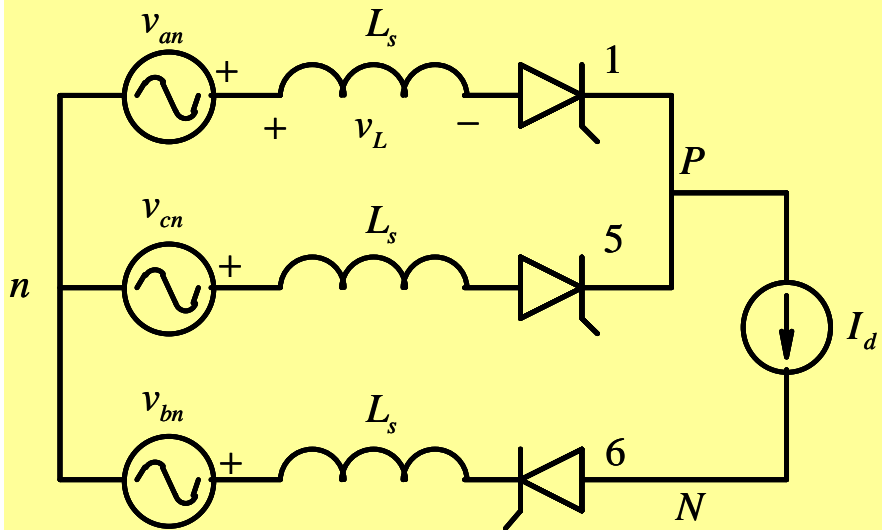


(a)

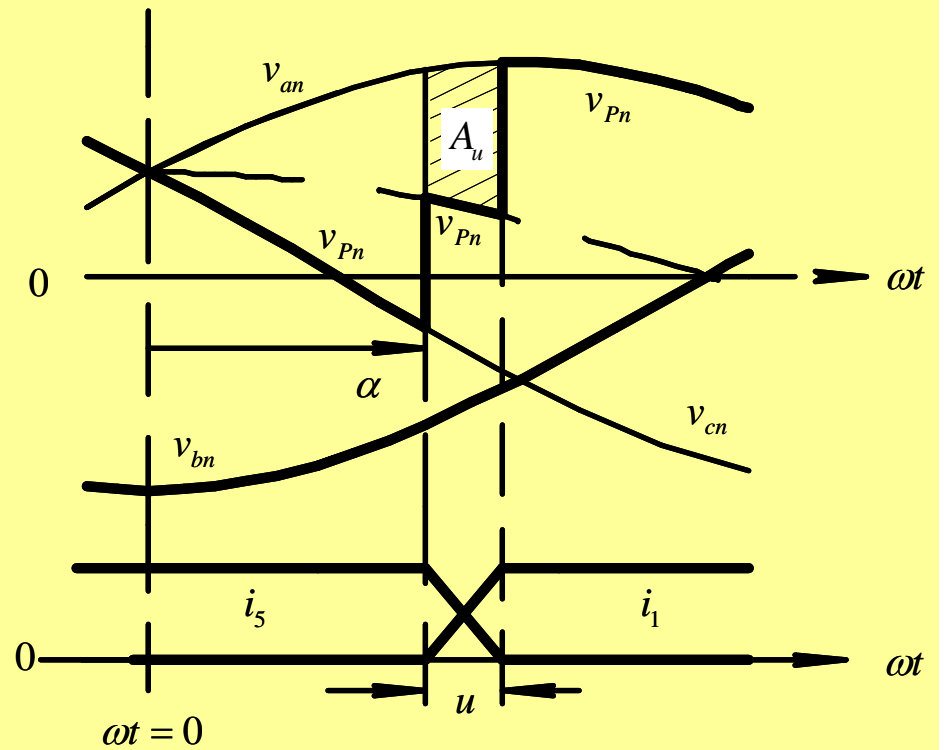

(b)

$$A_u = \int_{\alpha}^{\alpha+u} v_L d(\omega t) = \omega L_s \int_0^{I_d} di_s = \omega L_s I_d$$
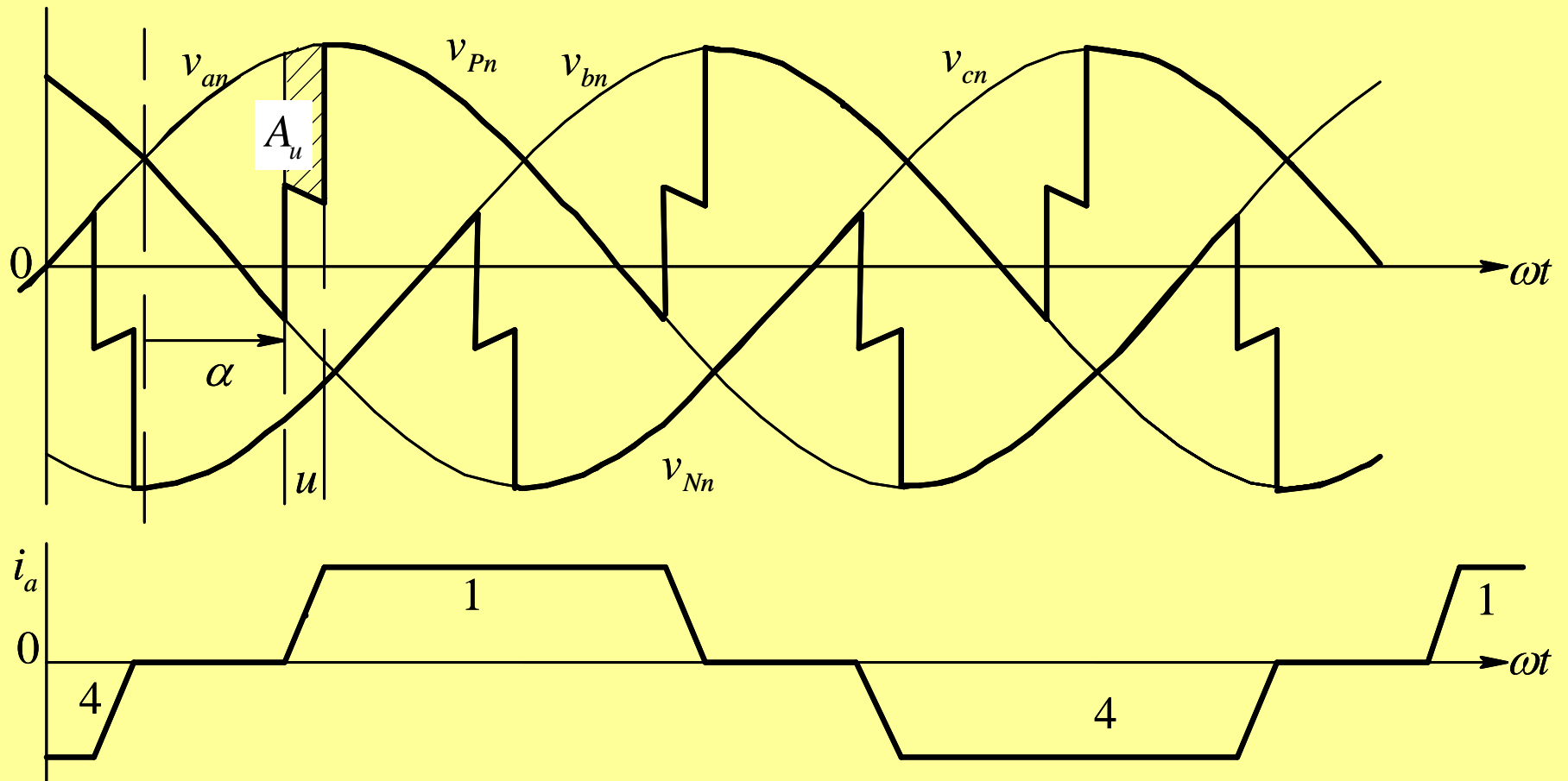
$$\Delta V_u = \frac{A_u}{\pi/3} = \frac{3}{\pi} \omega L_s I_d$$



$$A_u = \int_{\alpha}^{\alpha+u} v_L d(\omega t) = \omega L_s \int_0^{I_d} di_s = \omega L_s I_d \quad \Delta V_u = \frac{A_u}{\pi/3} = \frac{3}{\pi} \omega L_s I_d$$

$$V_d = V_{do} - \Delta V_{\alpha} - \Delta V_u \quad V_d = \frac{3}{\pi} \hat{V}_{LL} \cos \alpha - \frac{3}{\pi} \omega L_s I_d$$


Current Harmonics and the Reactive Power:

$$\hat{I}_{ah} = \frac{\hat{I}_{a1}}{h}$$



$$Q = \frac{3}{2} \hat{V}_{an} \hat{I}_{a1} \sin \phi_1$$

$$\phi_1 = \alpha + \frac{u}{2}$$


HVDC System

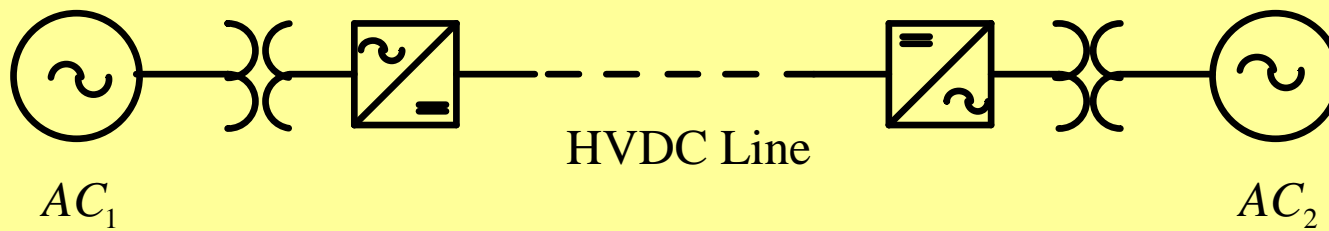

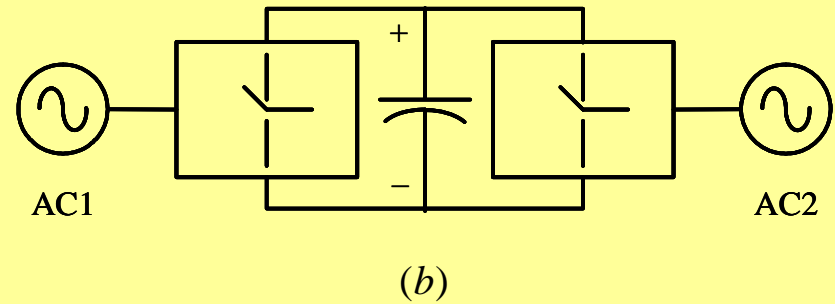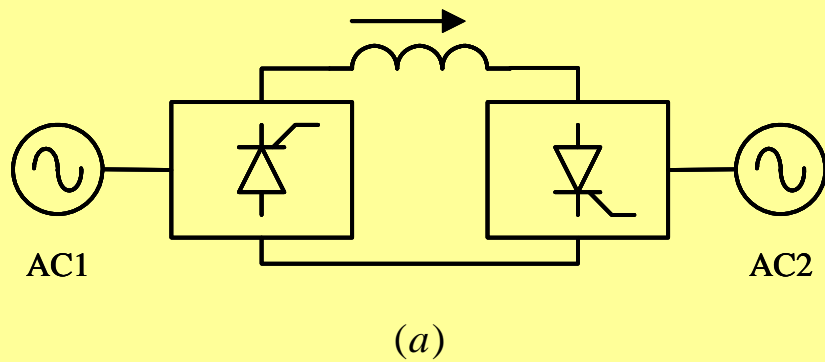
HVDC Systems: Voltage-Link and Current-Link




Current-Link HVDC Systems

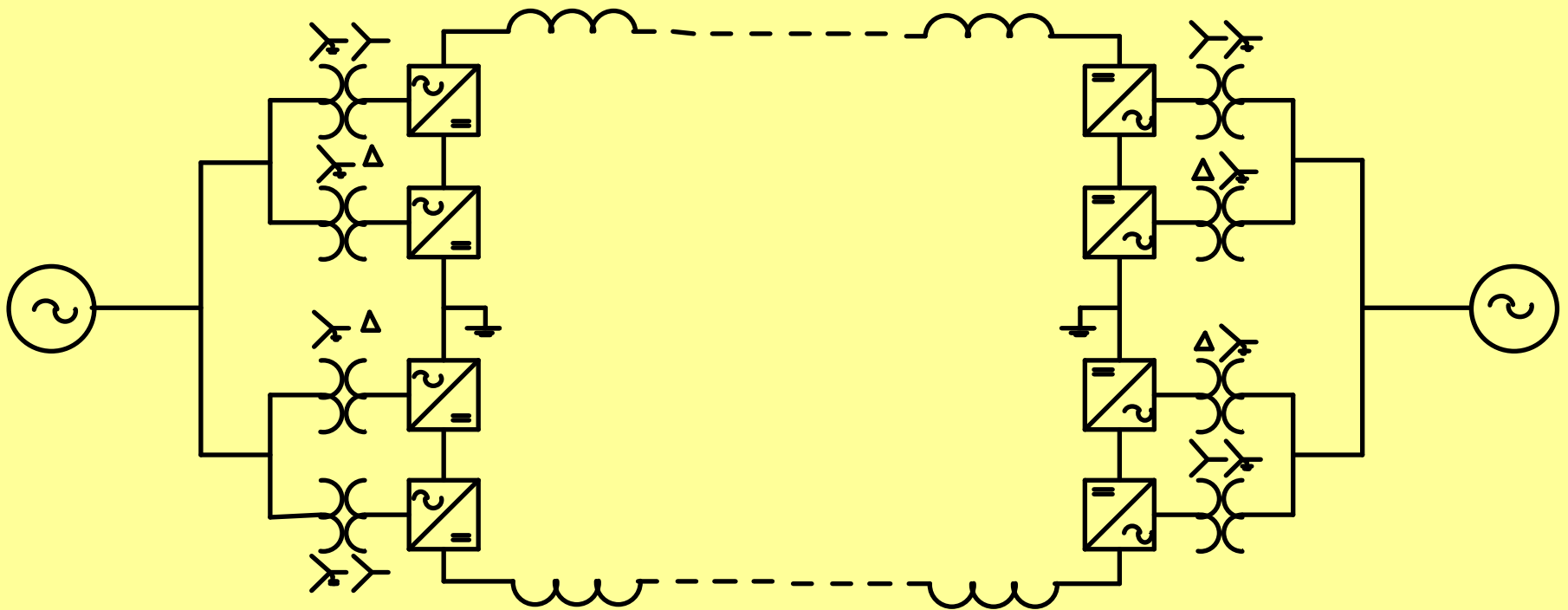

CU One-line Diagram

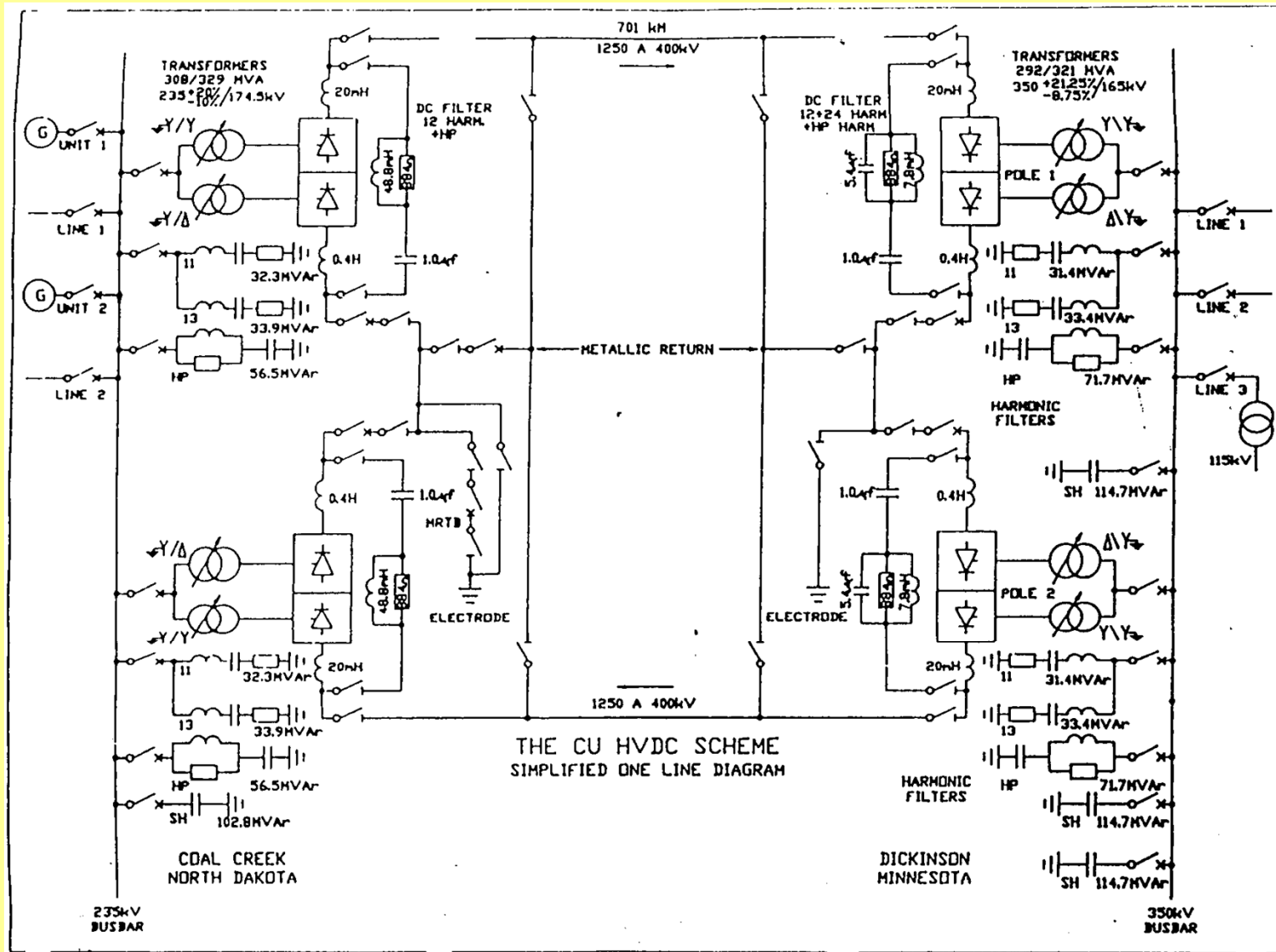

Current-Link Systems

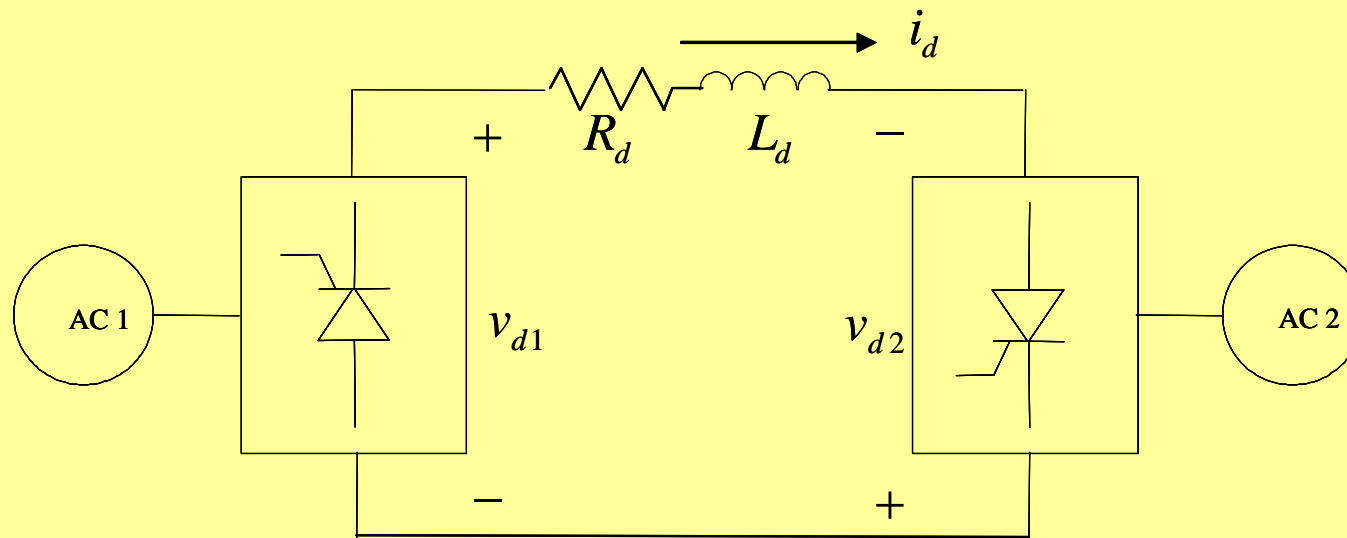

$$V_{d1} = \frac{3}{\pi} \hat{V}_{LL1} \cos \alpha_1 - \frac{3}{\pi} \omega L_{s1} I_d$$

$$V_{d2} = \frac{3}{\pi} \hat{V}_{LL2} \cos \alpha_2 - \frac{3}{\pi} \omega L_{s2} I_d$$

$$I_d = \frac{V_{d1} + V_{d2}}{R_d}$$

Summary

- Three-Phase Thyristor Converters
 - Three-Phase Thyristor Converter Operation
 - Applications in HVDC Systems