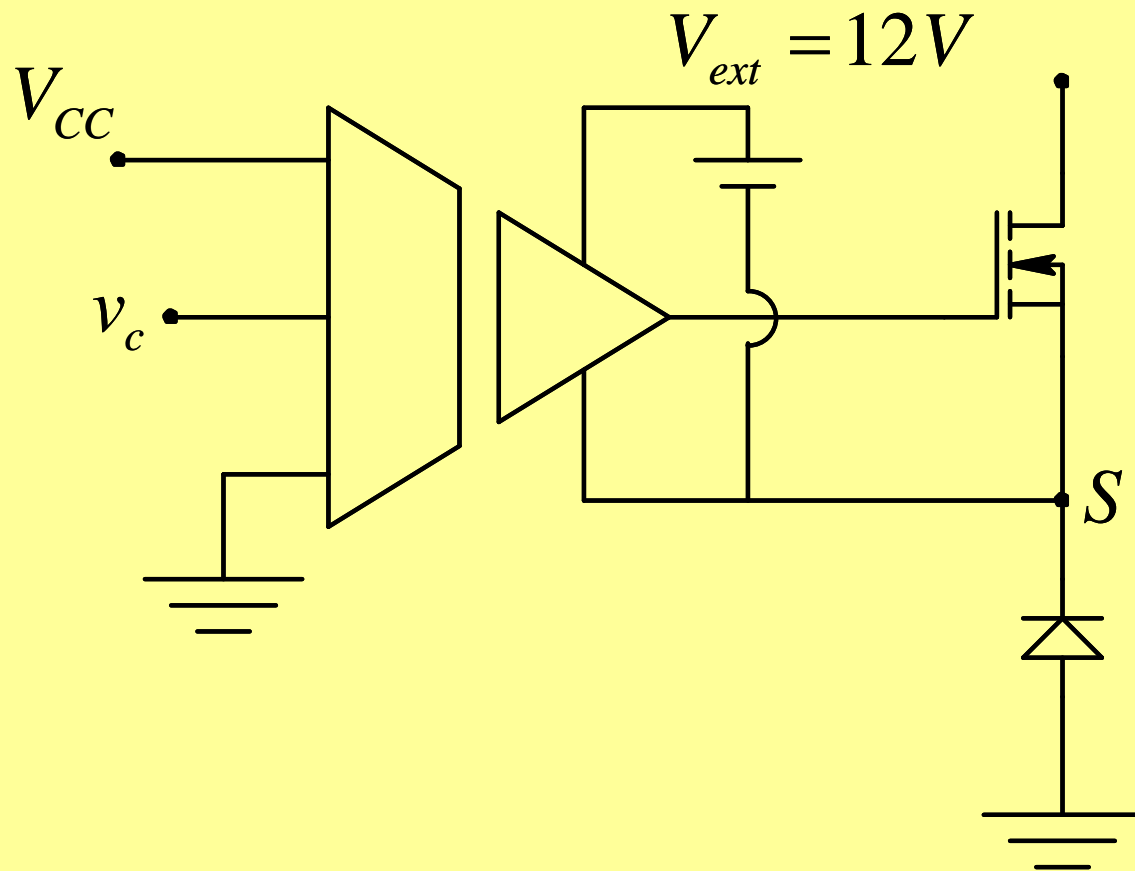


Practical Considerations in Implementing Switching Power-Poles

- Gate Driver ICs
- Design Considerations
 - Thermal Considerations
 - Magnetic Components
 - Capacitors
 - Selection of Switching Frequency
- Diode Reverse Recovery Characteristic
 - Conduction Losses
 - Increase in Switching Losses

Gate Driver Integrated Circuits (ICs) with Built-in Fault Protection



DESIGN CONSIDERATIONS

- Switching Frequency
- Selection of Transistors and Diodes
- Magnetic components
- Capacitor Selection

$$A_p = \frac{L \hat{I}_{rms}}{k_w J_{max} B_{max}} \quad A_p = \frac{k_{conv} \sum V_y I_{y,rms}}{k_w B_{max} J_{max} f_s}$$



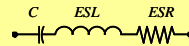


Figure 2-10 Capacitor ESR and ESL.

PSpice Modeling:


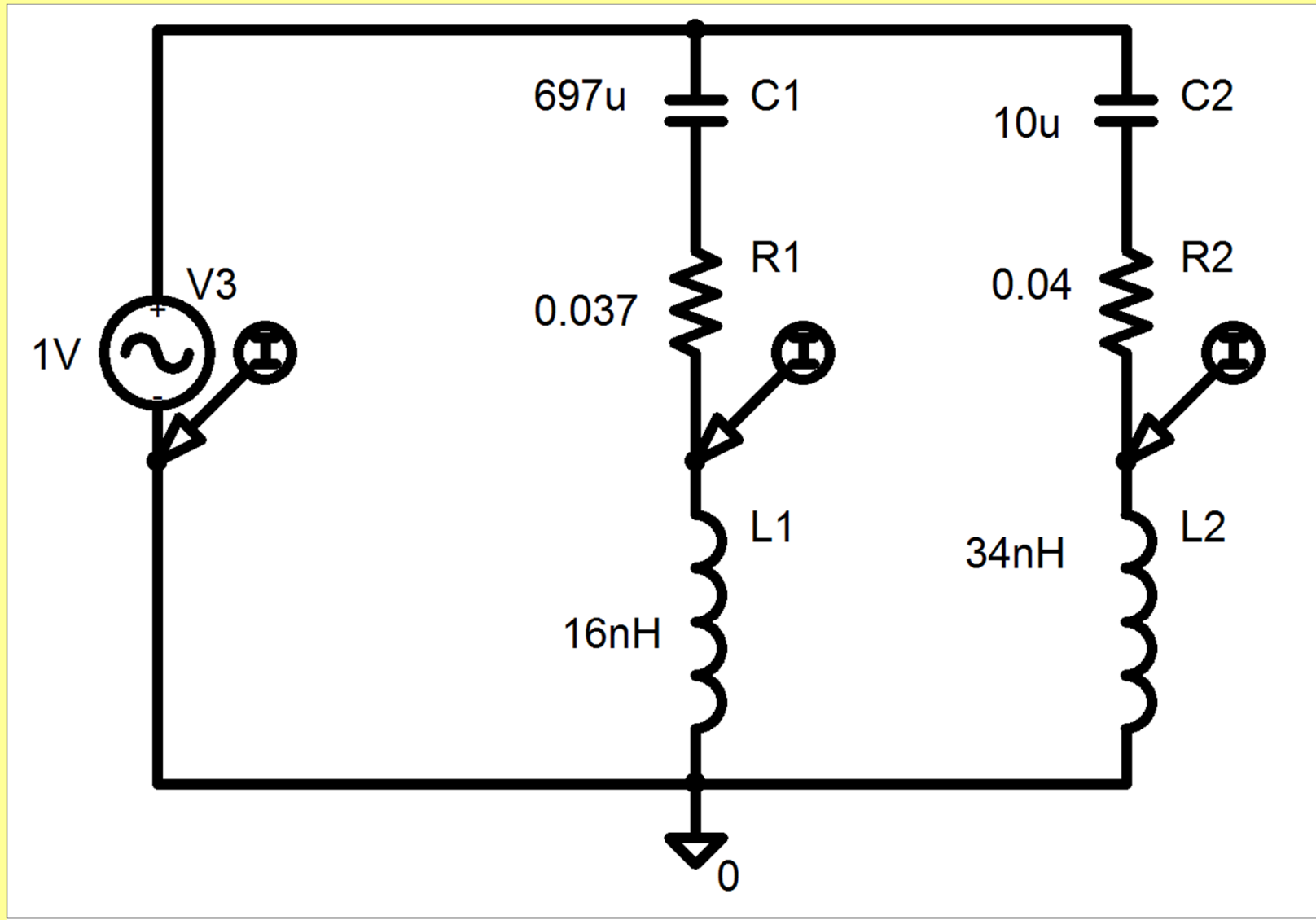


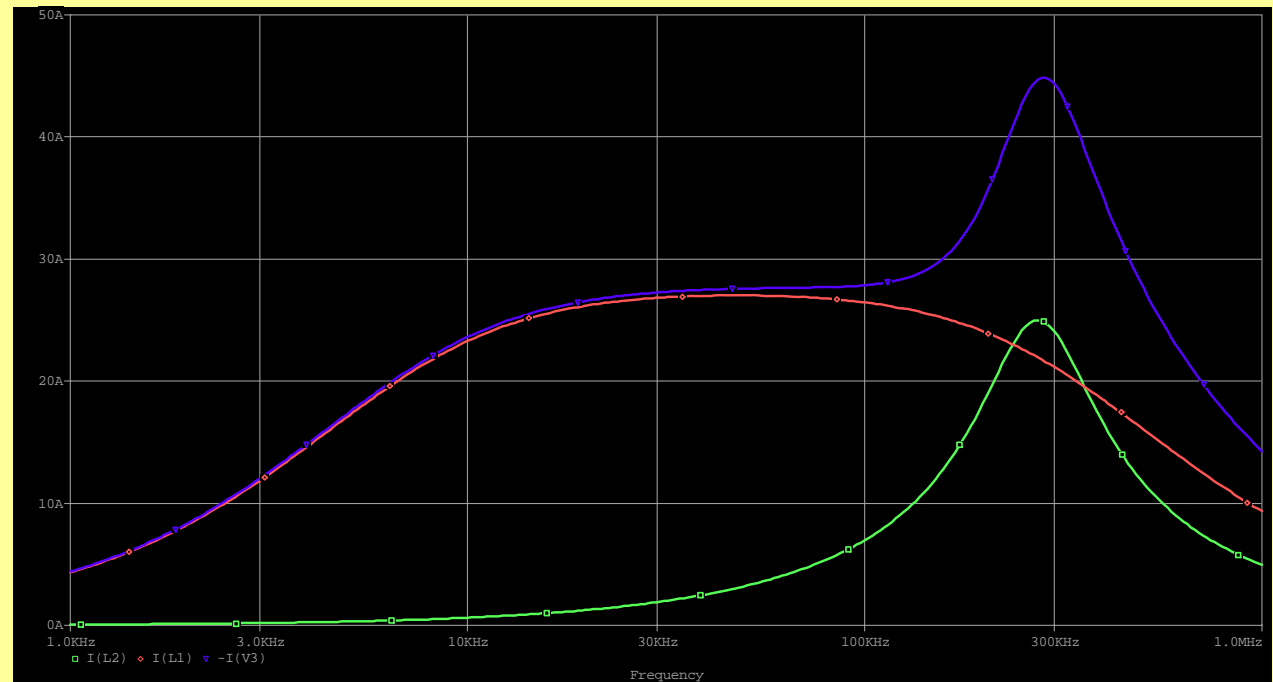Simulation Results: Individual and Total Admittances




Thermal Design
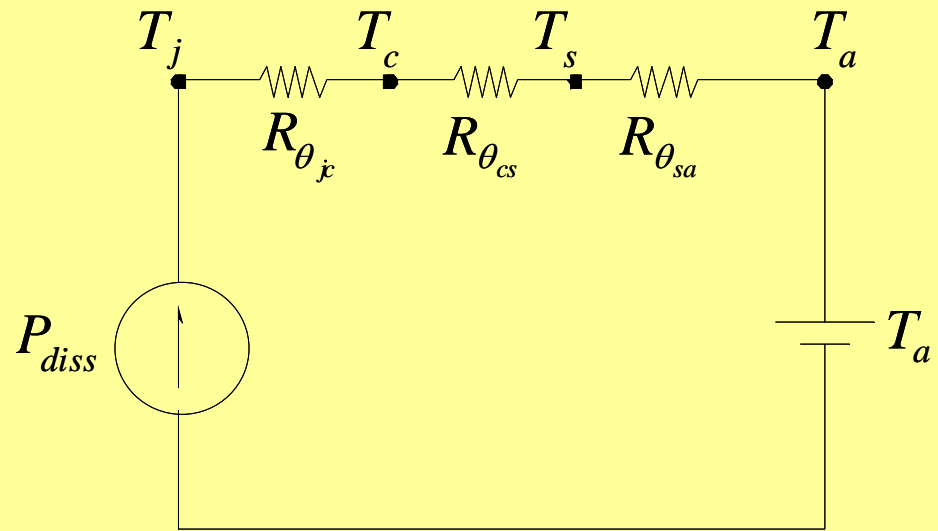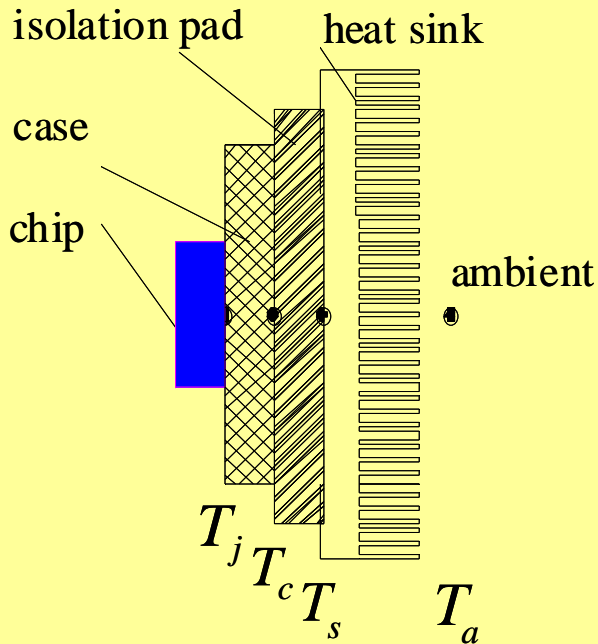
$$T_j = T_a + (R_{\theta jc} + R_{\theta cs} + R_{\theta sa}) P_{diss}$$



Design Tradeoffs


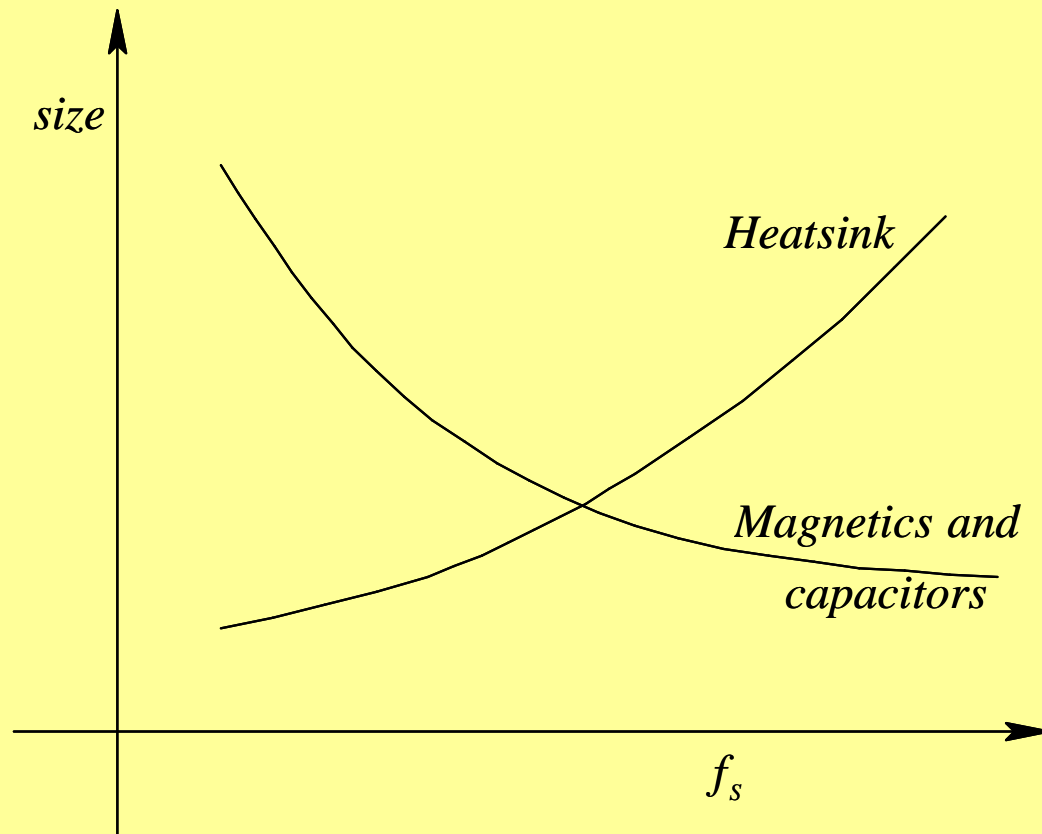


**Size of magnetic components and heat sink
as a function of switching frequency**

Diode Reverse Recovery and Power Losses



Diode Forward Loss: $P_{diode,F} = (1-d) \cdot V_{FM} I_o$

Diode Reverse Recovery Characteristic:

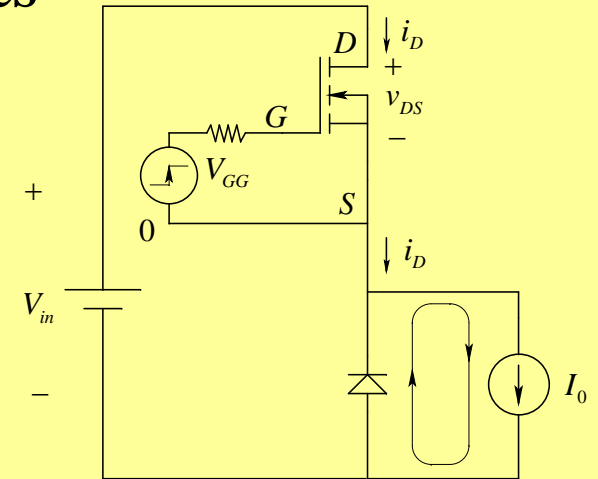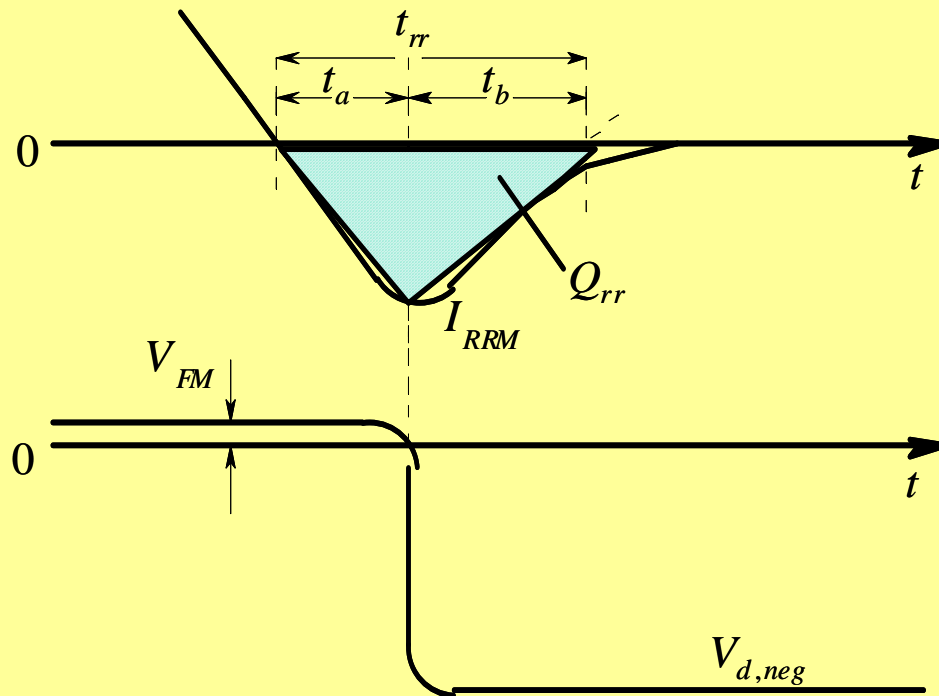

Diode Switching Losses: $P_{diode,sw} = \left(\frac{1}{2} I_{RRM} t_b\right) \cdot V_{d,neg} \cdot f_s$

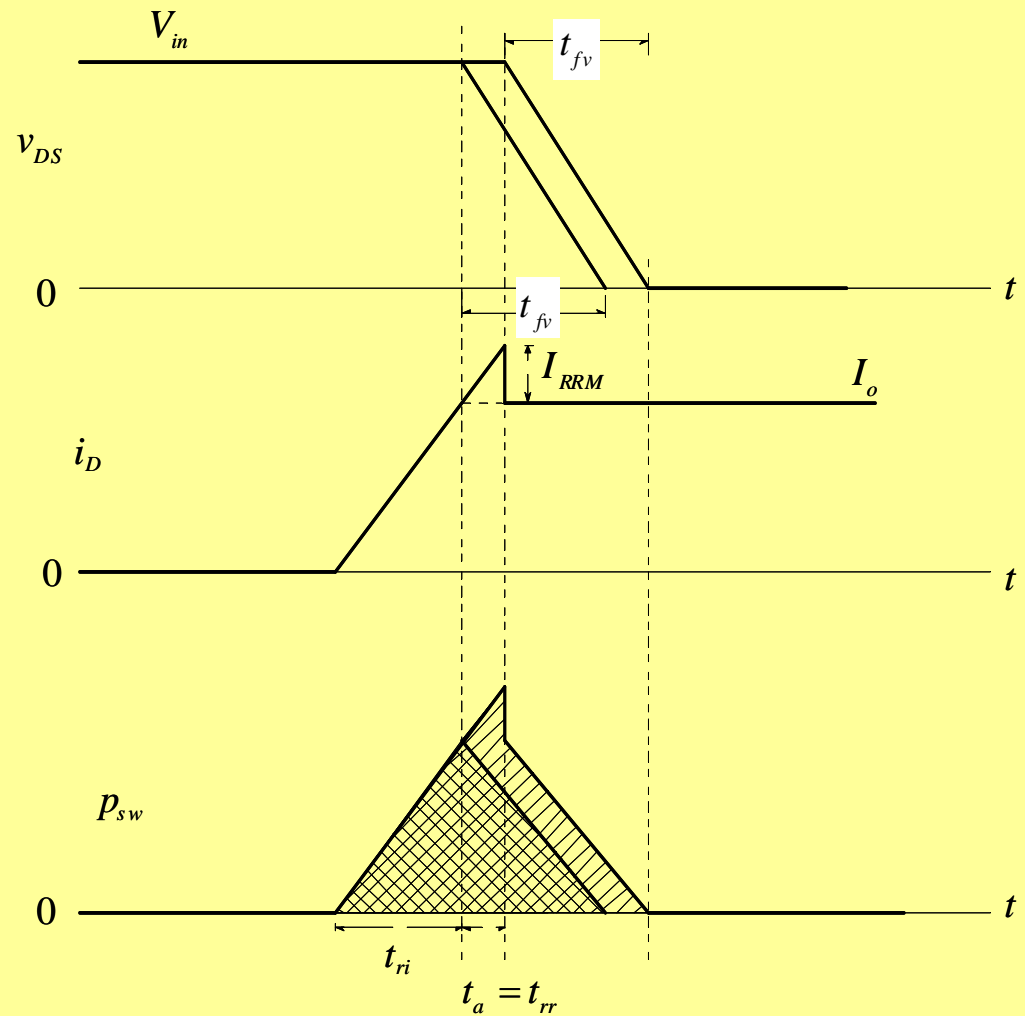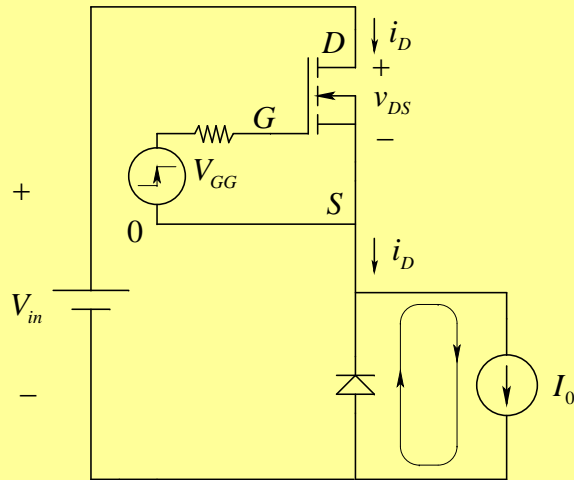Effect of Diode Reverse Recovery Current:



Summary

- Practical Implementation Considerations
 - Gate Driver ICs
 - Design Considerations
 - Thermal Considerations
 - Magnetic Components
 - Capacitors
 - Selection of Switching Frequency
 - Diode Reverse Recovery Characteristics
 - Conduction Losses
 - Increase in Switching Losses