
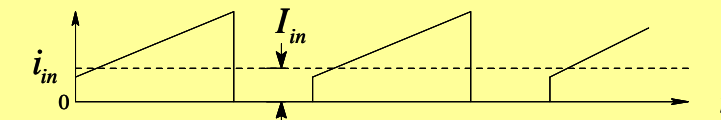
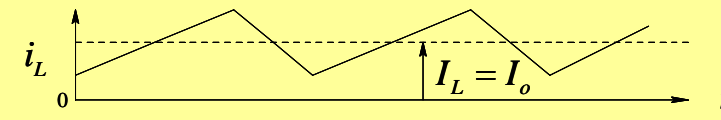
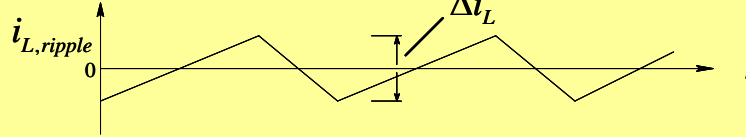
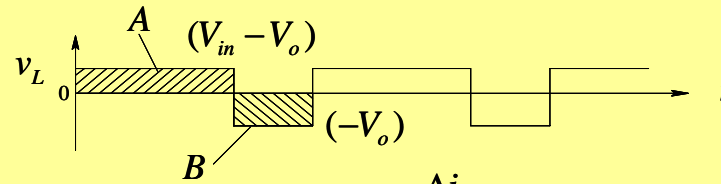
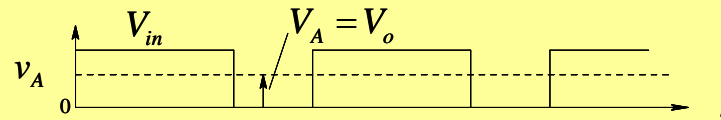
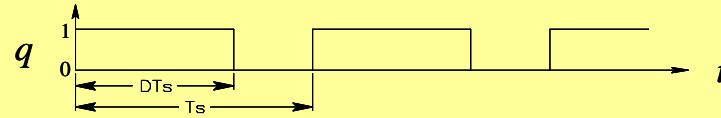
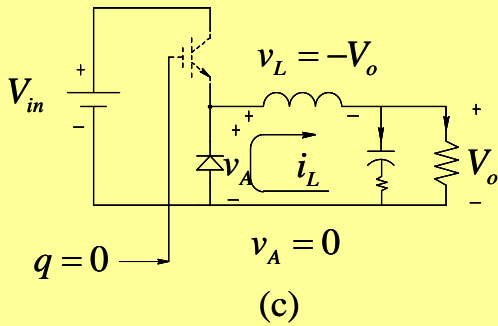
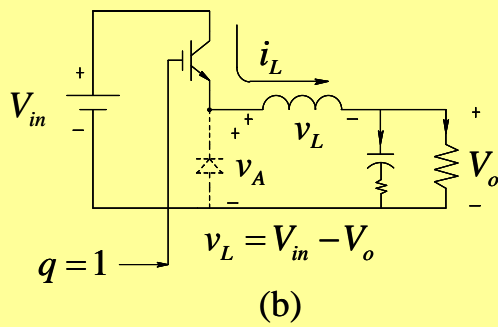


# Buck (Step-Down DC-DC) Converters

- Applications
- Operation in Steady State
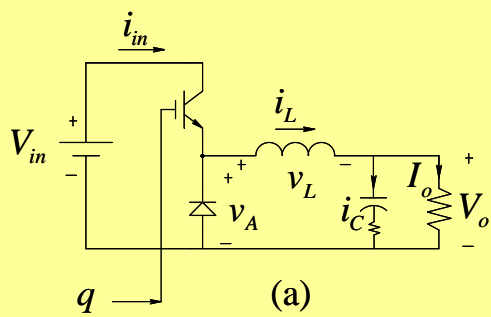
# SWITCHING ANALYSIS IN DC STEADY STATE (CCM)



(d)

$$V_o = V_A = DV_{in}$$

$$\Delta i_L = \frac{V_{in} - V_o}{L} DT_s = \frac{V_o}{L} (1 - D) T_s$$


$$I_L = I_o = \frac{V_o}{R}$$

$$V_{in} I_{in} = V_o I_o$$


$$I_{in} = DI_L = DI_o$$

$$i_C(t) \approx i_{L,ripple}(t)$$

# PSpice Modeling:

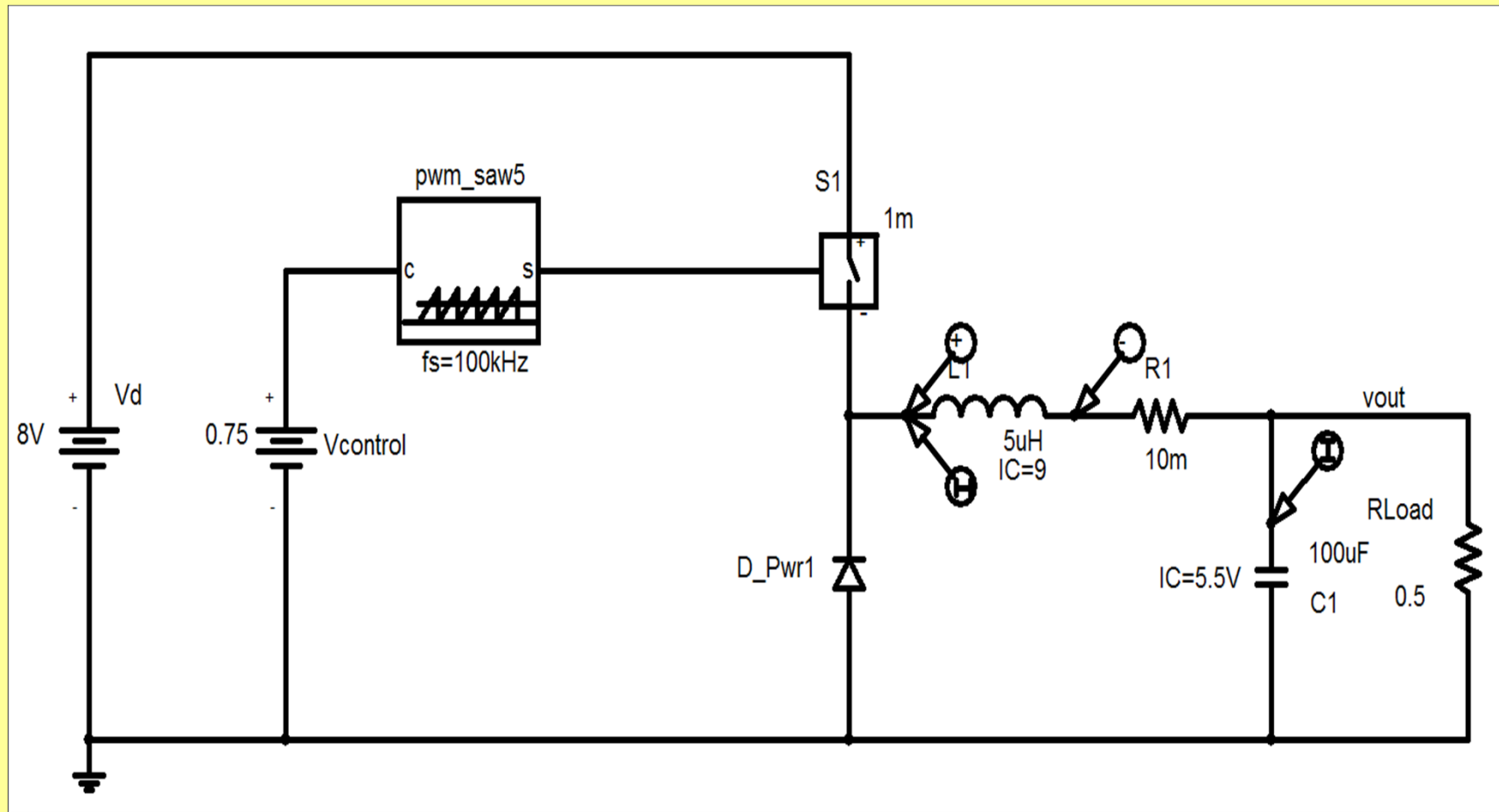

# Simulation Results

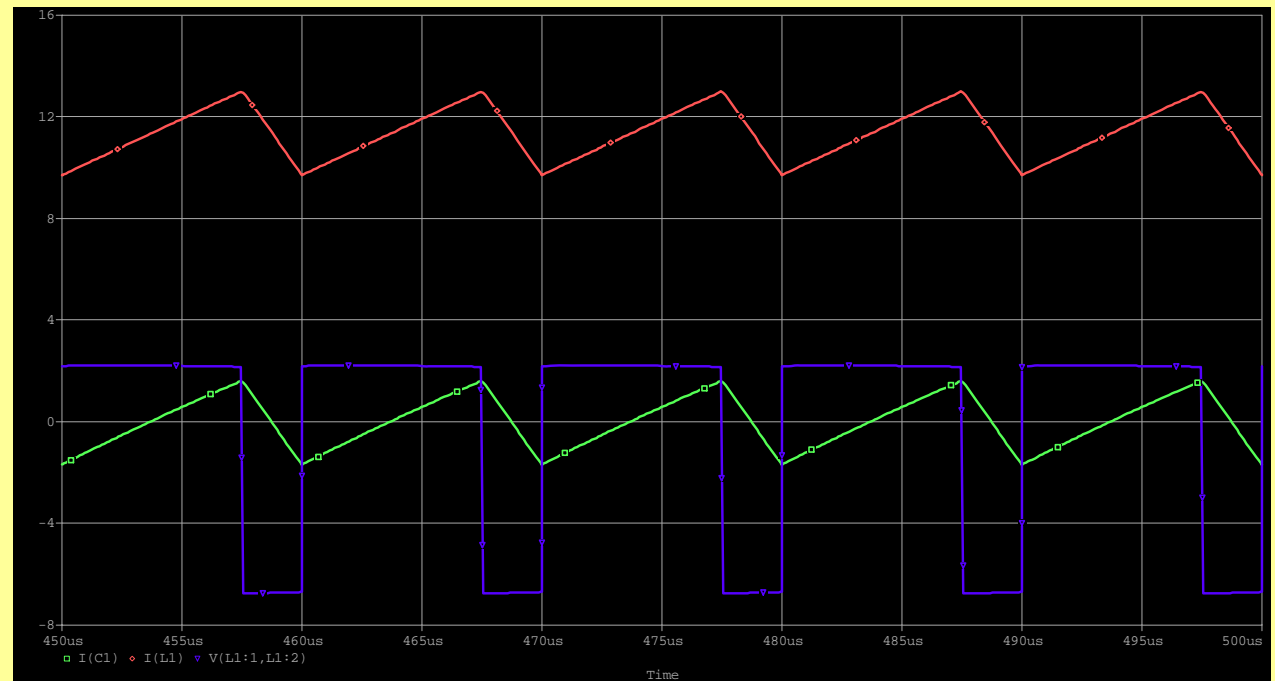

# Summary Buck (Step-Down DC-DC) Converters

- Buck (Step-Down DC-DC) Converters
  - Applications
  - Operation in Steady State