

ELE 2110A Electronic Circuits

Week 5: BJT Biasing and Small Signal Model



Topics to cover ...

- BJT Amplifier Biasing Circuits
- Small Signal Operation and Equivalent Circuits

Reading Assignment:

Chap 13.1 – 13.6 of Jaeger and Blalock , or
Chap 5.5 - 5.7 of Sedra & Smith



BJT as Amplifier: Example 1

- **Problem:** Determine the dc voltage transfer characteristic of the circuit for $0 < v_i < 5 \text{ V}$
- **Analysis:**

For $v_i \leq 0.7 \text{ V}$, Q is cut off and $v_o = 5 \text{ V}$.

For $v_i > 0.7 \text{ V}$, Q turns on and is in the active mode, so that

$$i_B = \frac{v_i - V_{BE}}{R_B} = \frac{v_i - 0.7}{100\text{k}\Omega}$$

The output voltage is

$$v_o = V^+ - i_C R_C = V^+ - \beta i_B R_C$$



or

$$v_o = 5 - (100) \left[\frac{v_i - 0.7}{100\text{k}\Omega} \right] 4\text{k}\Omega$$

This equation is valid for $v_i \geq 0.7 \text{ V}$ and $v_o \geq v_{CE}(\text{sat}) = 0.2 \text{ V}$.



The input voltage for $v_o = 0.2 \text{ V}$ is found to be $v_i = 1.9 \text{ V}$.

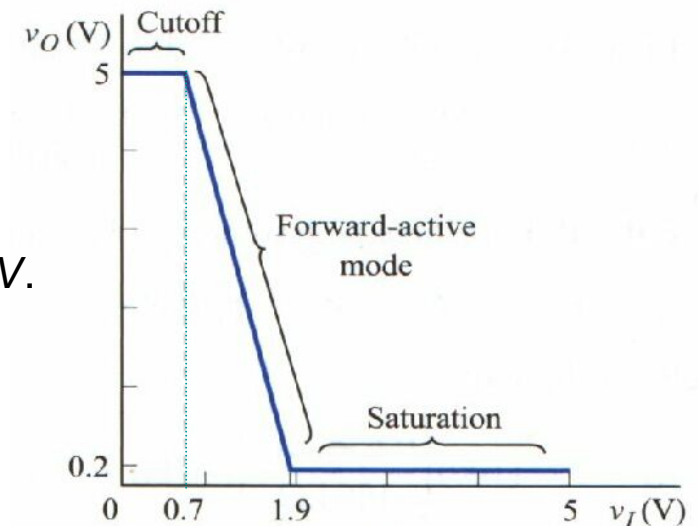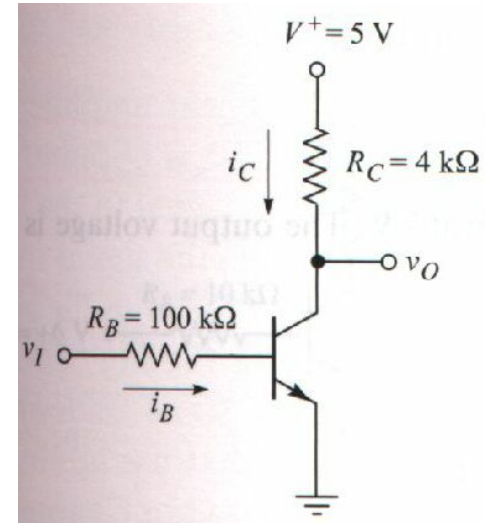Now, for $v_i > 1.9 \text{ V}$, the transistor is in saturation.




Conceptual Bias Circuit for BJT

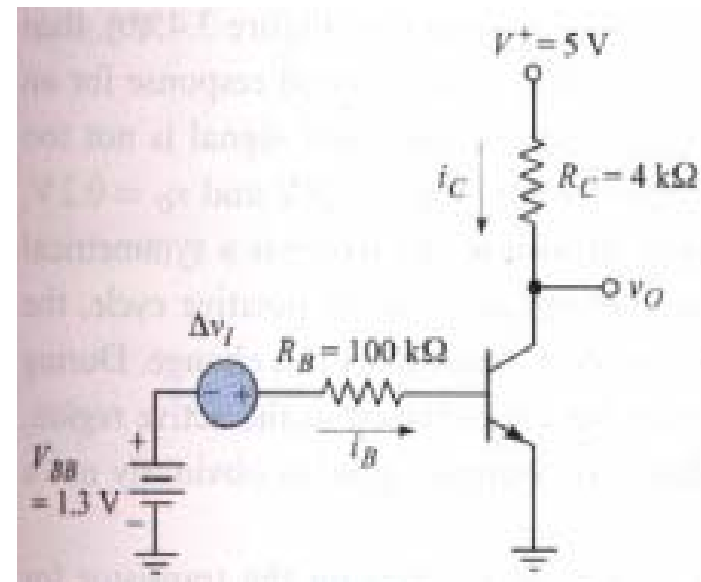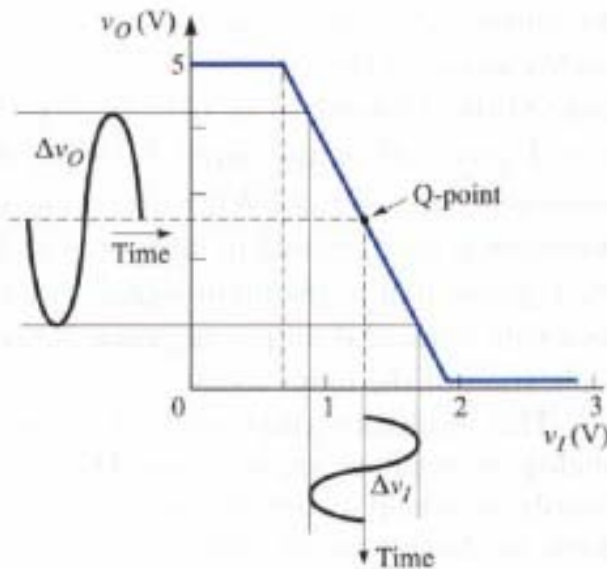- Keep the transistor in the active mode;
- Establish a Q-point near the center of the active region;
- Couple the time-varying signal to the base.




Two Obvious Bias Circuits

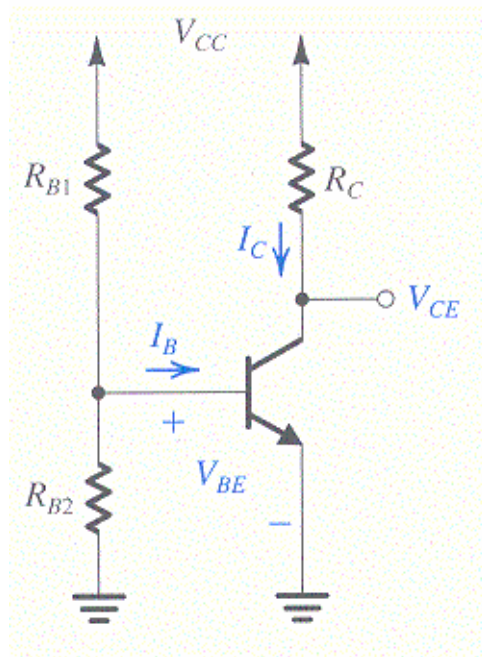

Fix V_{BE}

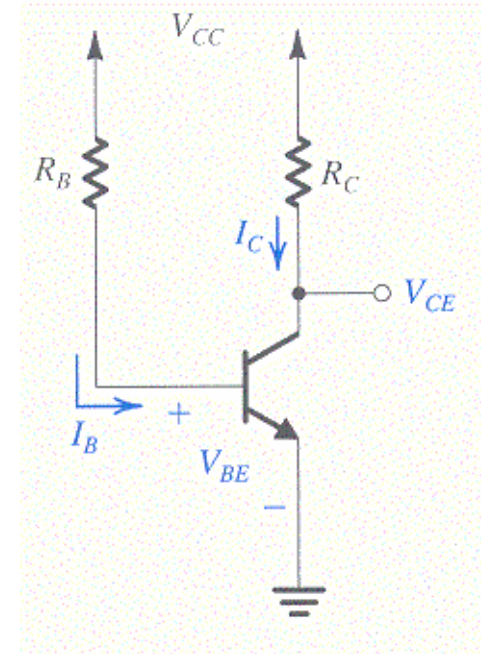→ I_C is an exponential function of V_{BE} and thus V_{CC}




Fix I_B

→ $I_C = \beta I_B$, but β is a poorly controlled parameter

- Wide variations in I_C and hence in V_{CE}
- “Bad” biasing schemes




Biasing Circuit in ERG2810 Experiment A3

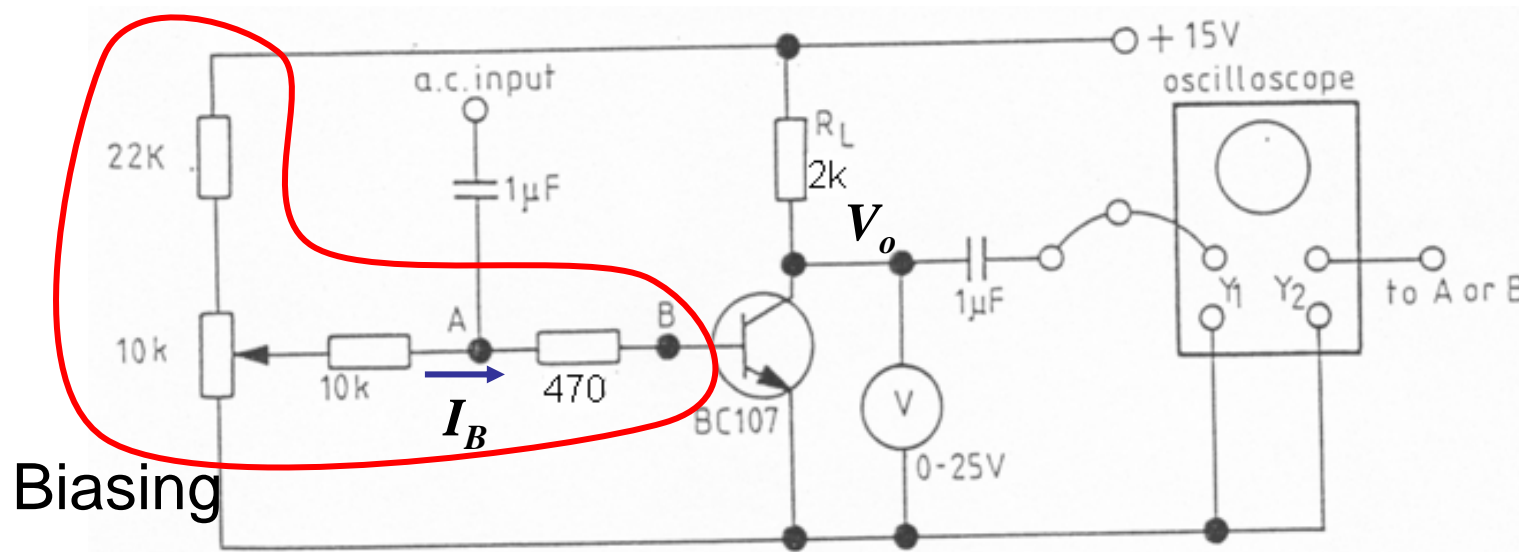

- Adjusting the variable resistor to give a desired amount of I_B such that V_o is at about 8V (half the supply voltage).
- The transistor operates at the middle of active region.



Classical Four-Resistor Bias Circuit

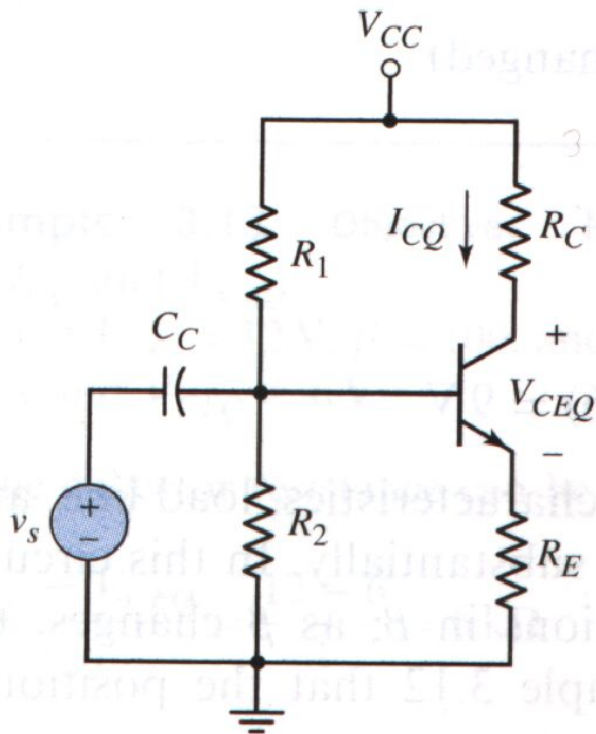


- V_B established by the voltage divider formed by R_1 and R_2 .
- R_E added \rightarrow reduce sensitivity to supply voltage, process, and temperature variations
 \rightarrow to be discussed later
- Coupling capacitor C_C :
 - open circuit to DC, isolating the signal source from the dc biasing current.
 - short circuit to AC signal (if the signal frequency is large enough and C_C is large enough).
- The Q-point is usually specified by (I_C, V_{CE}) for *npn* transistor or (I_C, V_{EC}) for *pnp* transistor.




Example 2

Given $\beta = 200$.

Problem: find Q-point.

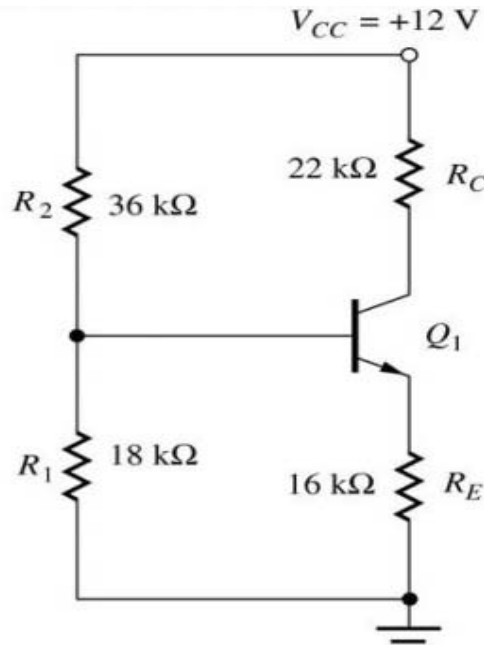

Thevenin equivalent circuit at the base:

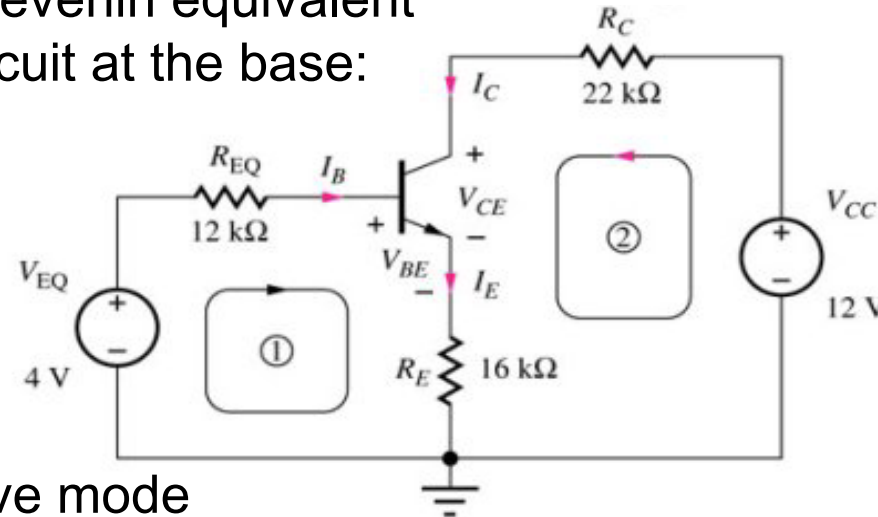

$$V_{EQ} = V_{CC} \frac{R_1}{R_1 + R_2}$$

$$R_{EQ} = \frac{R_1 R_2}{R_1 + R_2}$$

Assume BJT in active mode

$$\text{KVL at loop 1: } V_{EQ} = R_{EQ} I_B + V_{BE} + R_E I_E$$

$$4 = 12,000 I_B + 0.7 + 16,000 (\beta + 1) I_B$$

$$\therefore I_B = \frac{4V - 0.7V}{1.23 \times 10^6 \Omega} = 2.68 \mu A$$

$$I_C = \beta I_B = 201 \mu A \quad I_E = (\beta + 1) I_B = 204 \mu A$$

$$V_{CE} = V_{CC} - R_C I_C - R_E I_E$$



$$= V_{CC} - \left(R_C + \frac{R_E}{\alpha_F} \right) I_C = 4.32 V$$

Q-point is (201 μA , 4.32 V)



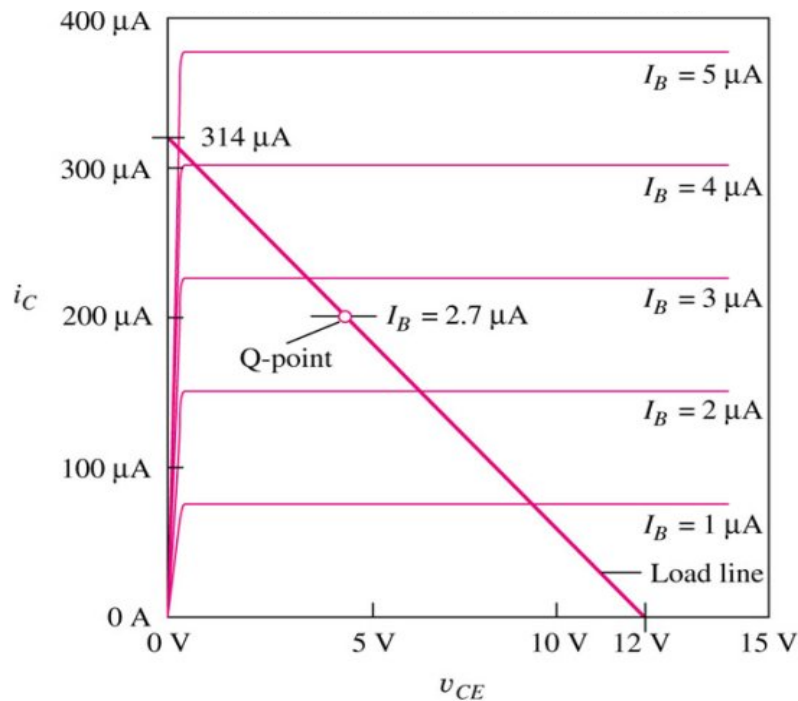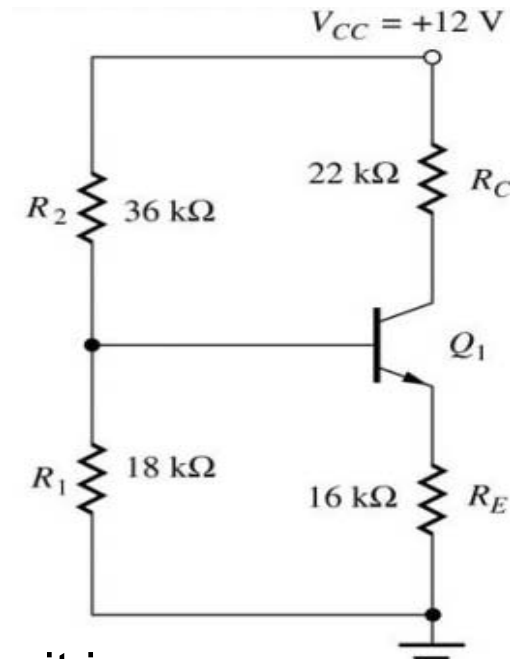Example 2 (Cont')

- All calculated currents > 0 ,
 $V_{BC} = V_{BE} - V_{CE} = 0.7 - 4.32 = -3.62 \text{ V}$
- Hence, base-collector junction is reverse-biased, assumption of active region operation is correct.



- Load-line for the circuit is:



$$V_{CE} = V_{CC} - \left(R_C + \frac{R_E}{\alpha} \right) I_C = 12 - 38,200 I_C$$

$$I_B = 2.7 \mu\text{A}$$

intersection point \rightarrow Q-point.



Example 2 (Cont')

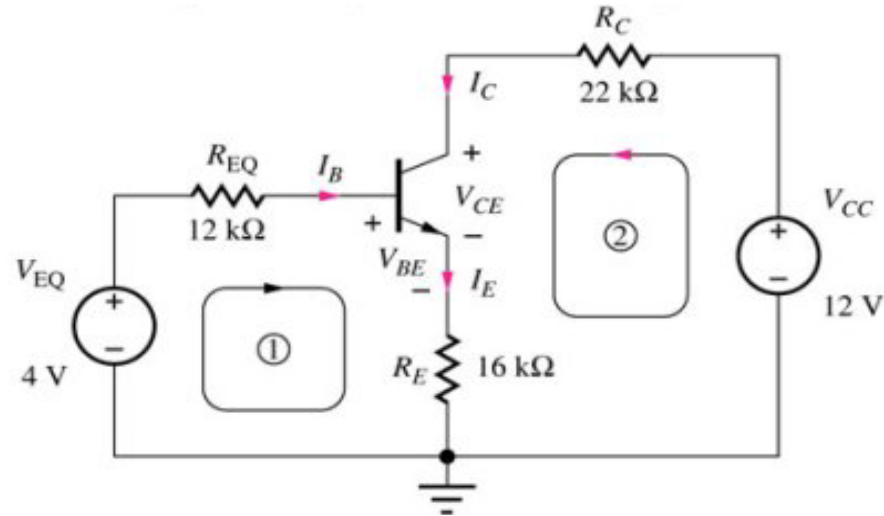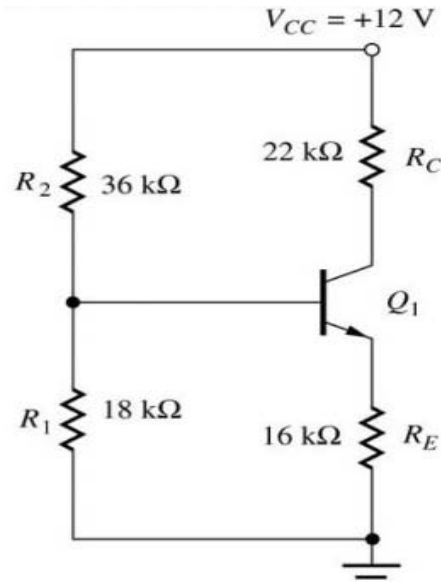

$$V_{EQ} = V_{CC} \frac{R_1}{R_1 + R_2}$$

$$R_{EQ} = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{EQ} = R_{EQ} I_B + V_{BE} + R_E I_E$$


V_{CC} Temp. Process (β)

$$I_E = \frac{V_{EQ} - V_{BE} - R_{EQ} I_B}{R_E}$$



Design Objectives: Q-point Insensitive to PVT Variations

$$I_E = \frac{V_{EQ} - V_{BE} - R_{EQ} I_B}{R_E}$$


- 1) I_E linearly (not exponentially) related to V_{CC} 
- 2) For I_E to be less sensitive to I_B (thus β):
 - $R_{EQ} I_B \ll (V_{EQ} - V_{BE})$
 - Need small R_{eq}
 - Large currents through R_1 and R_2 ($I_2 \gg I_B$)
- 3) For I_E to be less sensitive to V_{BE} (due to temperature change):
 - $V_{EQ} \gg V_{BE}$



Design Objectives: Low Power and Large Signal Swing

But ...

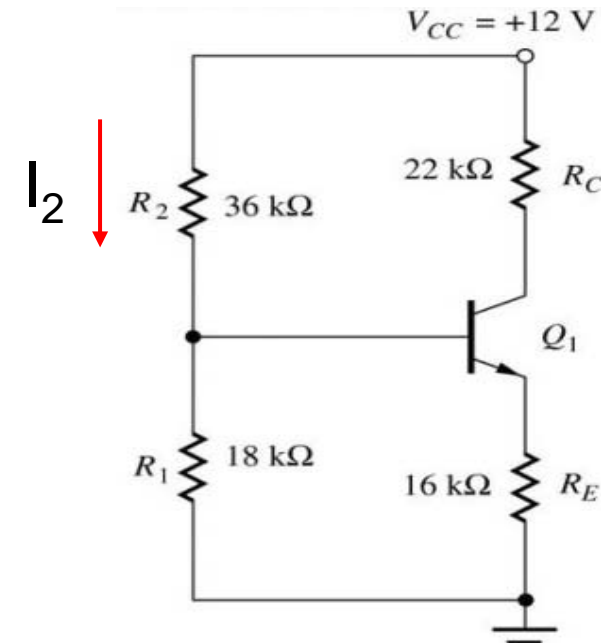- For low power consumption:
 - needs small I_2
 - contradict with constraint (2)
 - set $I_2 = 10I_B$ typically
- For large output signal swing:
 - V_{EQ} cannot be too high (because $V_C \in [V_{EQ}, V_{CC}]$)
 - $V_{EQ} = 1/3 V_{CC}$ typically



Design Guidelines

- Choose Thevenin equivalent base voltage

$$\frac{V_{CC}}{4} \leq V_{EQ} \leq \frac{V_{CC}}{2}$$

- Select R_1 to set $I_1 = 9I_B$ $R_1 = \frac{V_{EQ}}{9I_B}$


- Select R_2 to set $I_2 = 10I_B$ $R_2 = \frac{V_{CC} - V_{EQ}}{10I_B}$

- R_E is determined by V_{EQ} and desired I_C

$$R_E \approx \frac{V_{EQ} - V_{BE}}{I_C}$$

- R_C is determined by desired V_{CE}

$$R_C \approx \frac{V_{CC} - V_{CE}}{I_C} - R_E$$

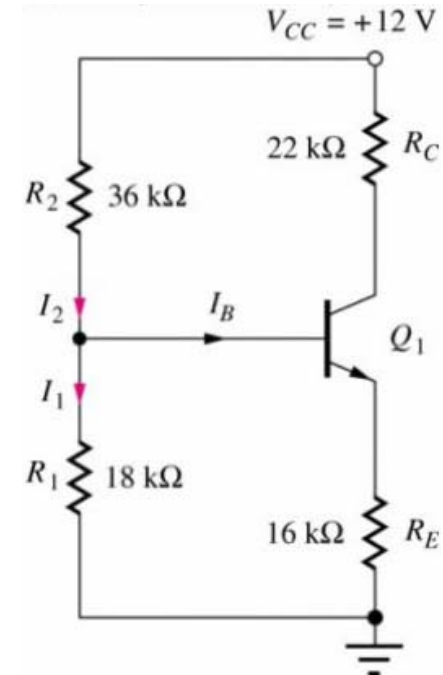

Example 3

- **Problem:** Design a 4-resistor bias circuit with given parameters.
- **Given data:** $I_C = 750 \mu\text{A}$, $V_{CE} = 5 \text{ V}$, $\beta = 100$, $V_{CC} = 15 \text{ V}$, $V_{BE} = 0.7 \text{ V}$
- **Unknowns:** V_B , voltages across R_E and R_C ; values for R_1 , R_2 , R_C and R_E .
- **Analysis:** A common approach is to divide $(V_{CC} - V_{CE})$ equally between R_E and R_C . Thus, $V_E = 5 \text{ V}$ and $V_C = 10 \text{ V}$.

$$R_C = \frac{V_{CC} - V_C}{I_C} = 6.67 \text{ k}\Omega$$

$$R_E = \frac{V_E}{I_E} = 6.60 \text{ k}\Omega$$

$$V_B = V_E + V_{BE} = 5.7 \text{ V}$$

$$I_B = \frac{I_C}{\beta} = 7.5 \mu\text{A}$$


Now choose $I_2 = 10I_B$:

$$I_2 = 10I_B = 75 \mu\text{A}$$

$$I_1 = 9I_B = 67.5 \mu\text{A}$$


$$R_1 = \frac{V_B}{9I_B} = 84.4 \text{ k}\Omega$$

$$R_2 = \frac{V_{CC} - V_B}{10I_B} = 124 \text{ k}\Omega$$

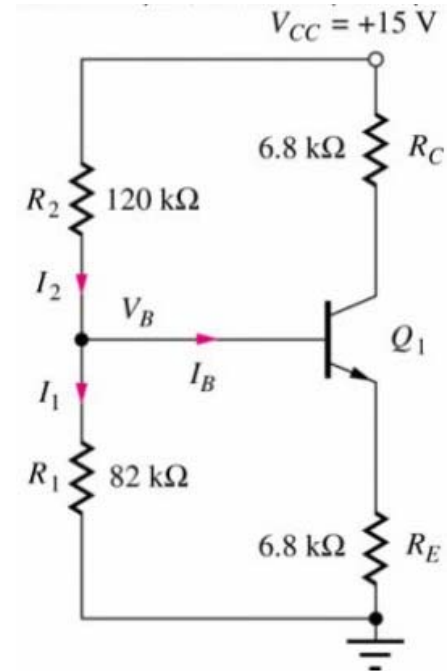

Example 4: Two-Resistor Bias Network

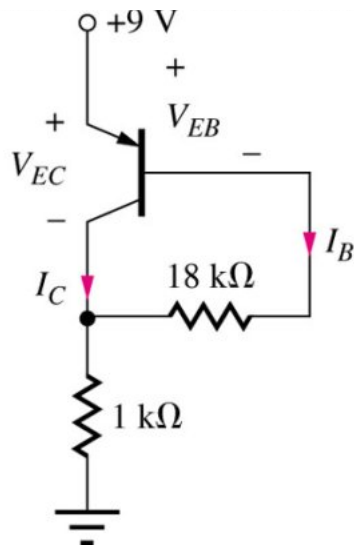- **Problem:** Find Q-point for *pnp* transistor in 2-resistor bias circuit with given parameters.
- **Given data:** $\beta_F = 50$, $V_{CC} = 9\text{ V}$
- **Assumptions:** Forward-active operation region, $V_{EB} = 0.7\text{ V}$
- **Analysis:**



$$9 = V_{EB} + 18,000 I_B + 1000 (I_C + I_B)$$
$$\therefore 9 = V_{EB} + 18,000 I_B + 1000 (51) I_B$$

$$\therefore I_B = \frac{9\text{ V} - 0.7\text{ V}}{69,000\ \Omega} = 120\ \mu\text{A}$$

$$I_C = 50 I_B = 6.01\text{ mA}$$


$$V_{EC} = 9 - 1000 (I_C + I_B) = 2.88\text{ V}$$

$$V_{BC} = 2.18\text{ V}$$

Q-point is : (6.01 mA, 2.88 V)




Current Source Biasing

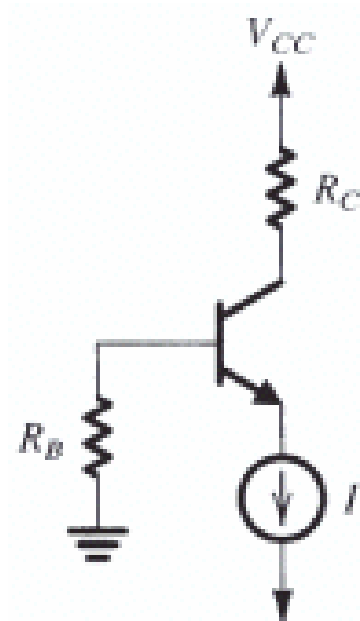


- $I_E = I \rightarrow$ independent of the value of β and temperature



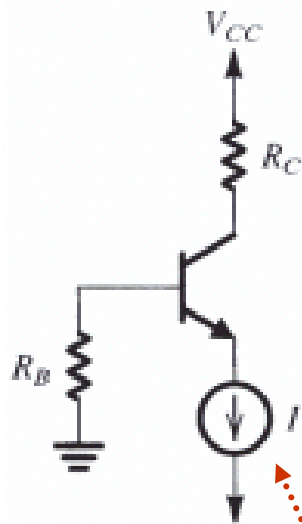Current Source Implementation: Current Mirror



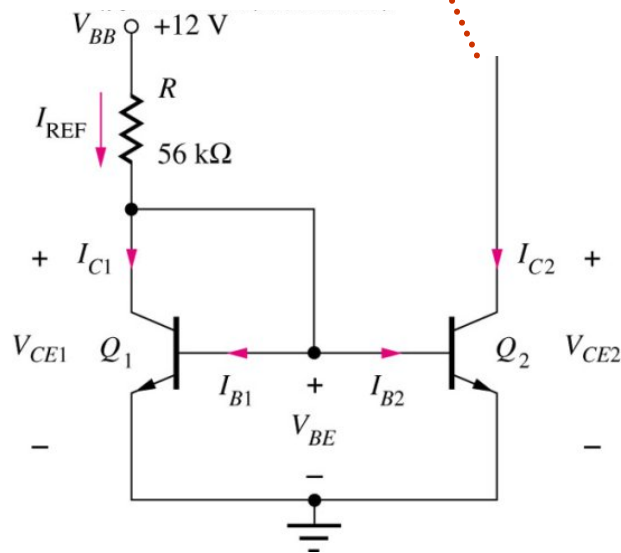- Use collector current of a transistor in active mode
- Neglect Early effect, I_{C2} is independent of V_{CE2} as long as $V_{CE2} > V_{CEsat}$ (i.e. BJT in active mode)
- For matched Q_1 and Q_2 , i.e., having identical I_S, β, V_A , we have



$$I_{C2} = I_{REF}$$

$$I_{REF} = \frac{V_{BB} - V_{BE}}{R}$$



Topics to cover ...


- BJT Amplifier Biasing Circuits

- Small Signal Operation and Equivalent Circuits



BJT as an Amplifier

Conceptual
Amplifier circuit:

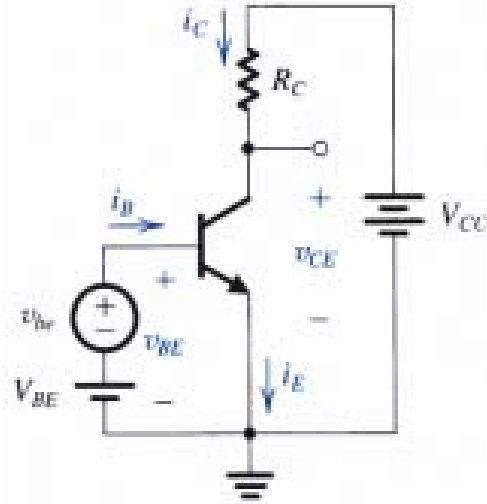

Superposition of DC with AC signal

If an ac+dc input signal the total v_{BE} becomes

$$v_{BE} = V_{BE} + v_{be}$$

The collector current becomes

$$\begin{aligned} i_C &= I_S e^{(V_{BE} + v_{be})/V_T} \\ &= I_S e^{V_{BE}/V_T} e^{v_{be}/V_T} = I_C e^{v_{be}/V_T} \end{aligned}$$



Small-signal Transconductance

For small ac signal, i.e., $v_{be} \ll V_T$:

$$\begin{aligned} i_c &= I_C e^{v_{be}/V_T} \cong I_C (1 + v_{be}/V_T) \\ &= \underbrace{I_C}_{DC} + \underbrace{\frac{I_C}{V_T} v_{be}}_{AC} \end{aligned}$$


The ac (or signal) component of the collector current is:

$$i_c = \frac{I_C}{V_T} v_{be}$$

We define:

$$g_m \equiv \frac{i_c}{v_{be}} = \frac{I_C}{V_T}$$

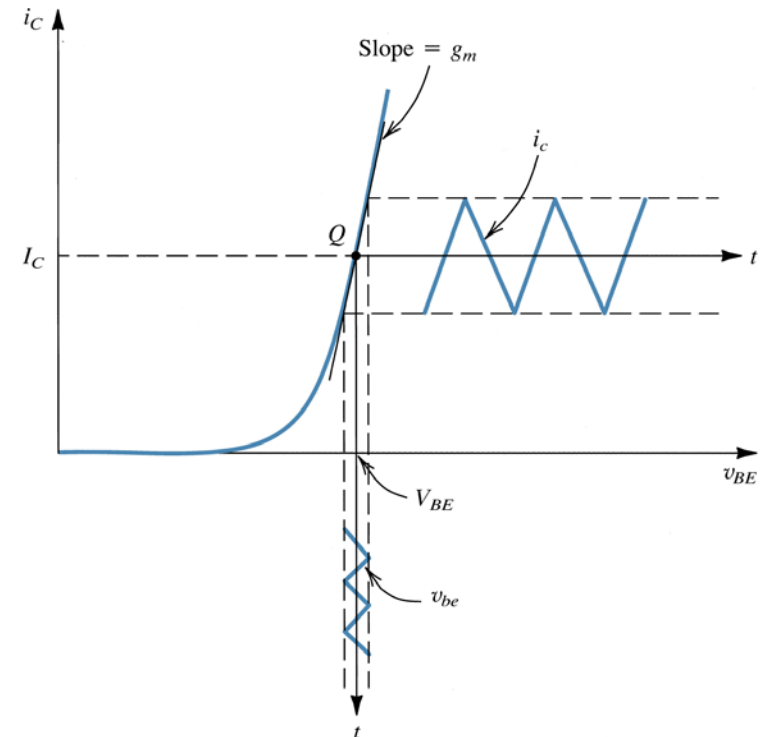g_m is called the small signal **transconductance**. It represents the slope of i_c - v_{BE} curve at the Q-point.



$$g_m \equiv \left. \frac{i_c}{v_{be}} \right|_{v_{be} \rightarrow 0} = \left. \frac{\partial i_c}{\partial v_{BE}} \right|_{i_c = I_C}$$



Signal Component of Base Current

Total base current:
$$i_B = \frac{i_C}{\beta} = \underbrace{\frac{I_C}{\beta}}_{DC} + \underbrace{\frac{1}{\beta} \frac{I_C}{V_T} v_{be}}_{AC}$$

Signal component of base current:
$$i_b = \frac{1}{\beta} \frac{I_C}{V_T} v_{be} = \frac{g_m}{\beta} v_{be}$$

Define:
$$r_\pi \equiv \frac{v_{be}}{i_b} = \frac{\beta}{g_m} \quad \text{or} \quad r_\pi = \frac{V_T}{I_B}$$

r_π is the small-signal input resistance between base and emitter, *looking into the base*.



Signal Component of Emitter Current

The total emitter current i_E :

$$i_E = \frac{i_C}{\alpha} = \underbrace{\frac{I_C}{\alpha}}_{DC} + \underbrace{\frac{1}{\alpha} \frac{I_C}{V_T} v_{be}}_{AC}$$

Signal component of emitter current:

$$i_e = \frac{1}{\alpha} \frac{I_C}{V_T} v_{be} = \frac{I_E}{V_T} v_{be}$$

Define:

$$r_e \equiv \frac{v_{be}}{i_e} = \frac{\alpha}{g_m} \quad \text{or} \quad r_e = \frac{V_T}{I_E}$$

r_e is the small-signal input resistance between base and emitter, *looking into the emitter*.

It is easy to find out that $r_\pi = (i_e / i_b) r_e = (\beta + 1) r_e$




Small Signal I-V Expressions

$$\frac{i_c}{v_{be}} = g_m = \frac{I_C}{V_T}$$

$$\frac{v_{be}}{i_b} = r_\pi = \frac{V_T}{I_B}$$

$$\frac{v_{be}}{i_e} = r_e = \frac{V_T}{I_E}$$

Can be modeled by equivalent circuits:

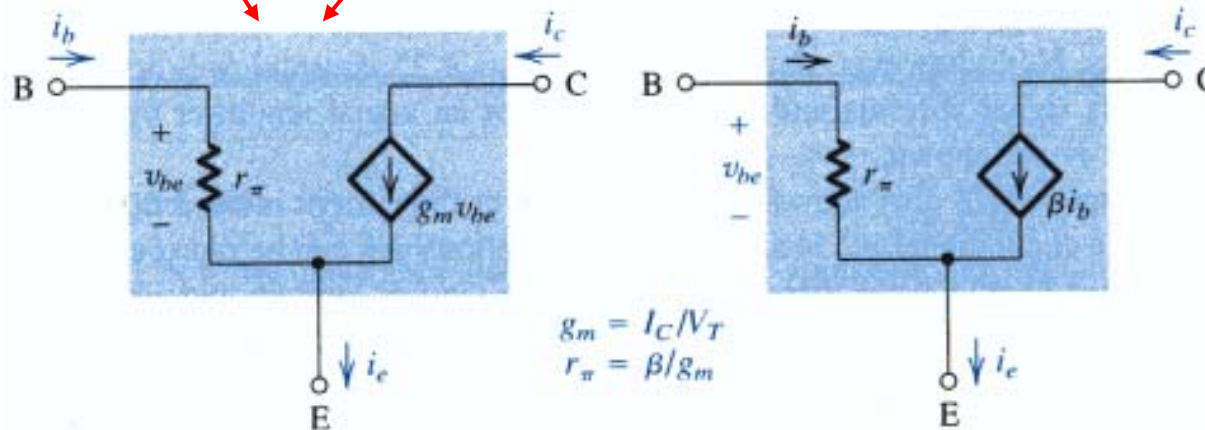

(**Hybrid- π** small signal model of BJT)





Another model: T-model

$$\frac{i_c}{v_{be}} = g_m = \frac{I_C}{V_T}$$


$$\frac{v_{be}}{i_b} = r_\pi = \frac{V_T}{I_B}$$
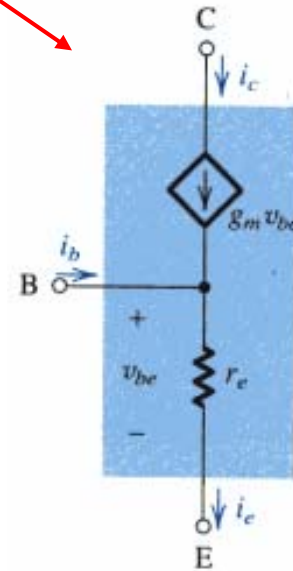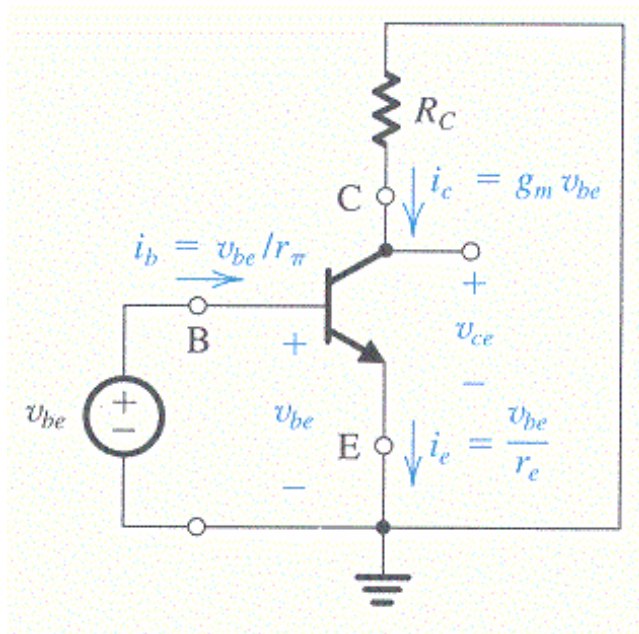
$$\frac{v_{be}}{i_e} = r_e = \frac{V_T}{I_E}$$



$$g_m = I_C / V_T$$

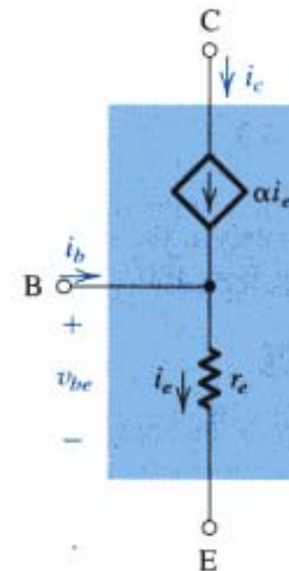
$$r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m}$$



T-model



Hybrid- π model including Early effect

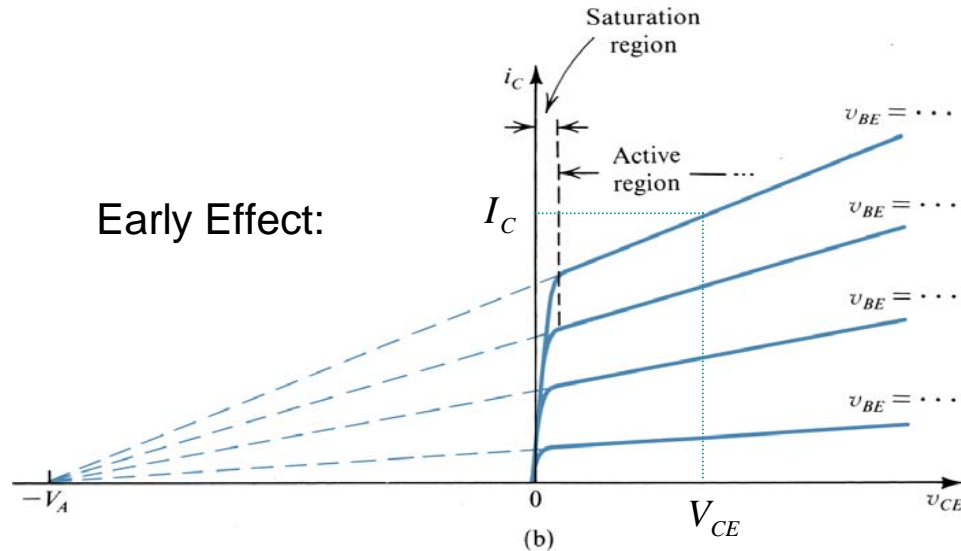


$$i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A}\right)$$


$$\text{Define } r_o = \left(\frac{\partial i_C}{\partial v_{CE}} \Big|_{\text{fixed } v_{BE}} \right)^{-1}$$

$$= \frac{V_A + V_{CE}}{I_C} \approx \frac{V_A}{I_C}$$

Include Early Effect in the model:

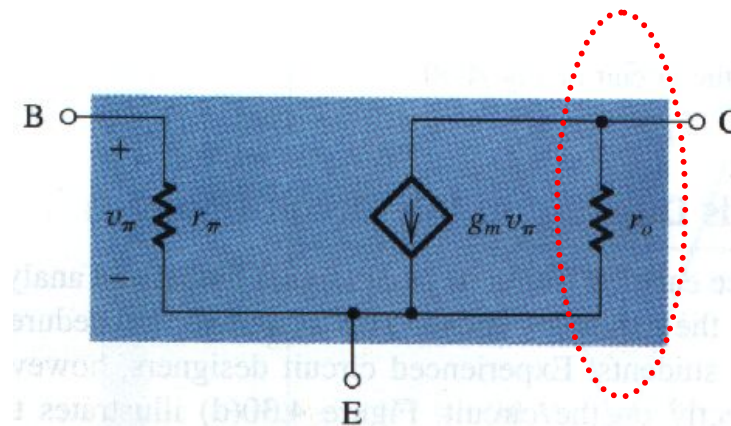

Graphic Analysis

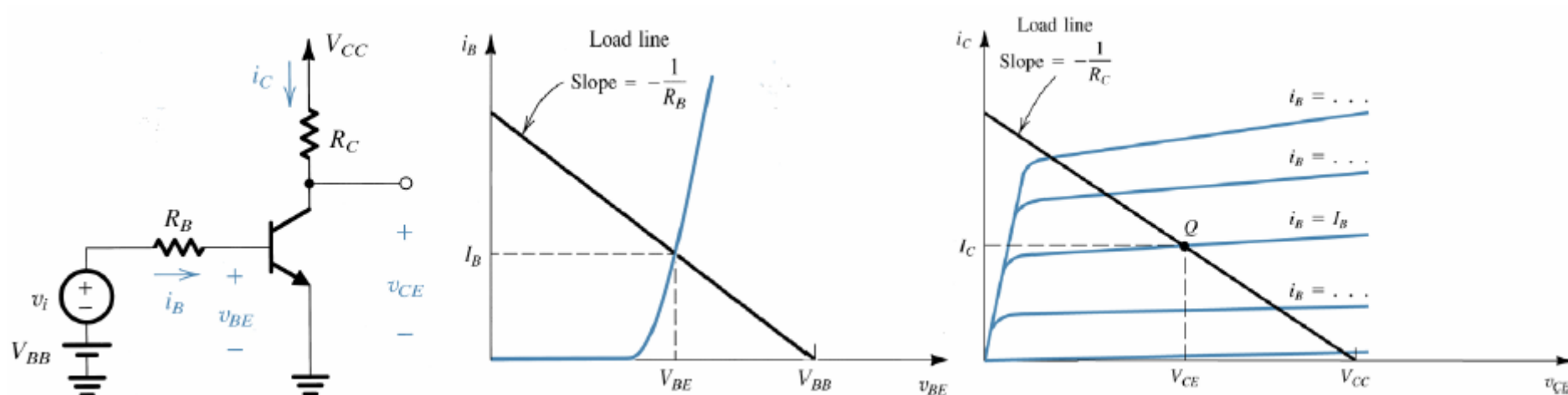


- Can be useful to understand the operation of BJT circuits
- First, establish DC conditions by finding I_B (or V_{BE})
 - Input load line: $v_{BE} = V_{BB} - R_B i_B$
- Second, figure out the DC operating point for I_C
 - Output load line:

$$v_{CE} = V_{CC} - i_C R_C \Rightarrow i_C = \frac{V_{CC}}{R_C} - \frac{1}{R_C} v_{CE}$$



Graphic Analysis (Cont.)

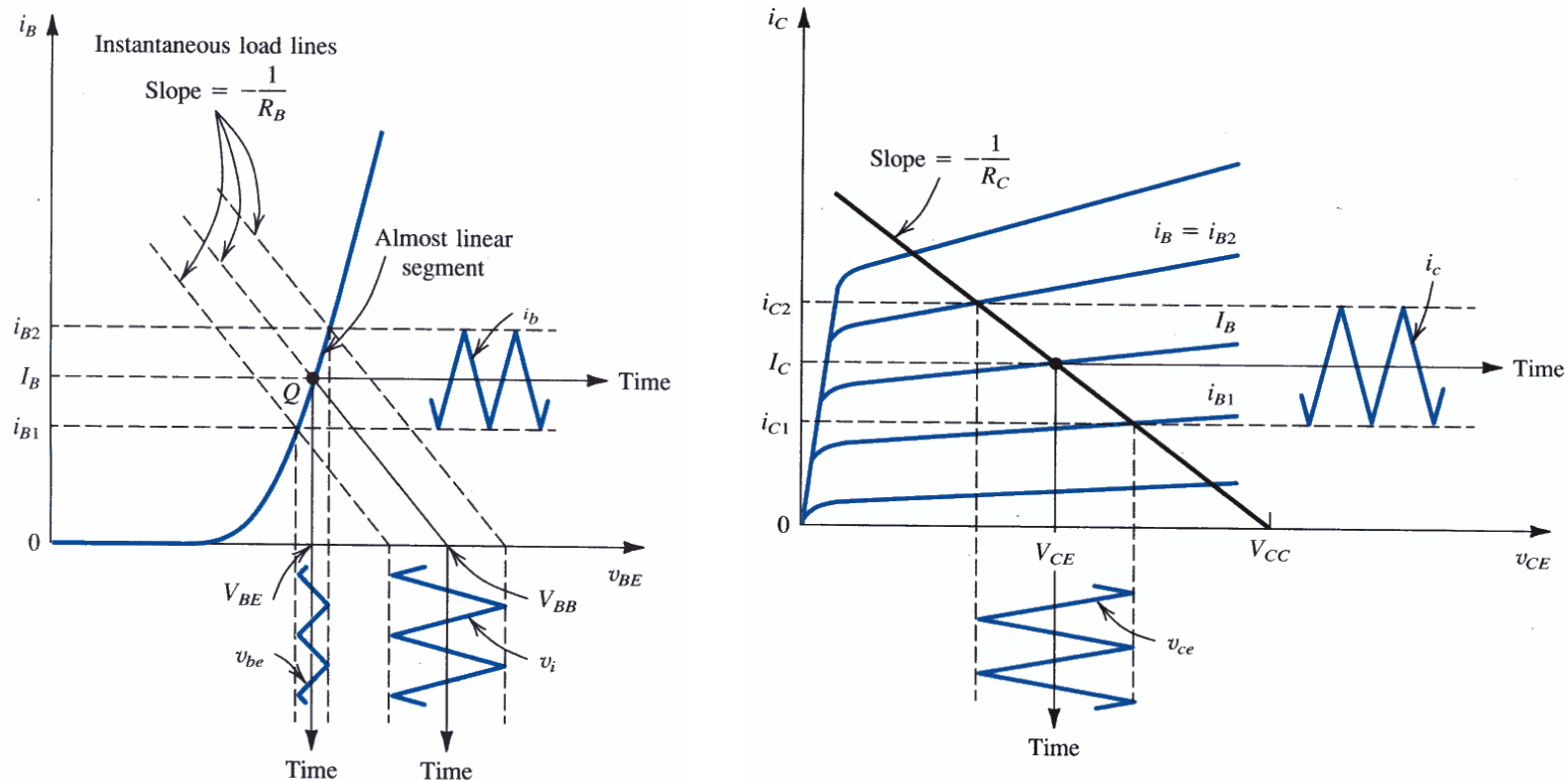

- Apply a small signal input voltage and see i_b
- See how i_b translates into V_{CE}
- Can get a feel for whether the BJT will stay in active region of operation
 - What happens if R_C is larger or smaller?

