

# ECE321 Electronics I: Lecture 1

---

## Chapter 1 Introduction to Electronics

### **Microelectronic Circuit Design**

Richard C. Jaeger  
Travis N. Blalock

---

Jaeger/Blalock  
4/15/07

Microelectronic Circuit Design  
McGraw-Hill

Chap 1 - 1

## Chapter Goals

---

- Explore the history of electronics.
- Quantify the impact of integrated circuit technologies.
- Describe classification of electronic signals.

### REVIEW

- Review circuit notation and theory.
- Introduce tolerance impacts and analysis.
- Describe problem solving approach

---

Jaeger/Blalock  
4/15/07

Microelectronic Circuit Design  
McGraw-Hill

Chap 1 - 2

## Notational Conventions

---

- Total signal = DC bias + time varying signal

$$v_T = V_{DC} + V_{sig}$$


$$i_T = I_{DC} + i_{sig}$$

- Resistance and conductance - R and G with same subscripts will denote reciprocal quantities. Most convenient form will be used within expressions.

$$G_x = \frac{1}{R_x} \quad \text{and} \quad g_\pi = \frac{1}{r_\pi}$$

## Figure 1.10 Controlled Sources

---

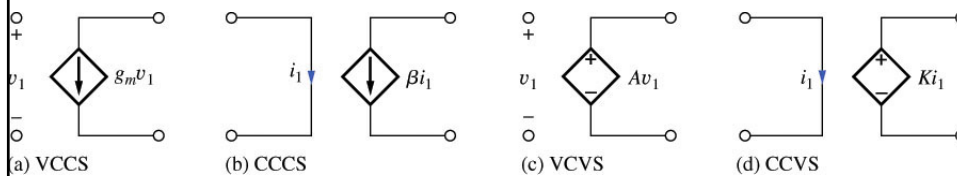

## Problem-Solving Approach

---

- Make a clear **problem** statement.
- List **known information and given data**.
- Define the **unknowns** required to solve the problem.
- List **assumptions**.
- Develop an **approach** to the solution.
- Perform the **analysis** based on the approach.
- **Check the results** and the assumptions.
  - Has the problem been solved? Have all the unknowns been found?
  - Is the math correct? Have the assumptions been satisfied?
- **Evaluate the solution**.
  - Do the results satisfy reasonableness constraints?
  - Are the values realizable?
- Use **computer-aided analysis** to verify hand analysis

## What are Reasonable Numbers?

---

- If the power supply is  $\pm 10$  V, a calculated DC bias value of 15 V (not within the range of the power supply voltages) is unreasonable.
- Generally, our bias current levels will be between 1  $\mu$ A and a few hundred milliamps.
- A calculated bias current of 3.2 amps is probably unreasonable and should be reexamined.
- Peak-to-peak ac voltages should be within the power supply voltage range.
- A calculated component value that is unrealistic should be rechecked. For example, a resistance equal to 0.013 ohms.
- Given the inherent variations in most electronic components, three significant digits are adequate for representation of results. Three significant digits are used throughout the text.


## Circuit Theory Review: Voltage Division

$$v_1 = i_s R_1 \quad \text{and} \quad v_2 = i_s R_2$$

Applying KVL to the loop,

$$v_s = v_1 + v_2 = i_s (R_1 + R_2)$$
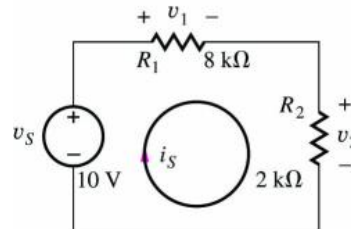
$$\text{and} \quad i_s = \frac{v_s}{R_1 + R_2}$$



Combining these yields the basic voltage division formula:

$$v_1 = v_s \frac{R_1}{R_1 + R_2} \quad v_2 = v_s \frac{R_2}{R_1 + R_2}$$

Jaeger/Blalock  
4/15/07

Microelectronic Circuit Design  
McGraw-Hill


Chap 1 - 7

## Circuit Theory Review: Voltage Division (cont.)

Using the derived equations with the indicated values,

$$v_1 = 10 \text{ V} \frac{8 \text{ k}\Omega}{8 \text{ k}\Omega + 2 \text{ k}\Omega} = 8.00 \text{ V}$$
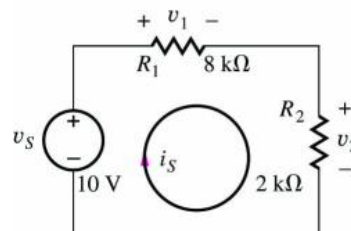
$$v_2 = 10 \text{ V} \frac{2 \text{ k}\Omega}{8 \text{ k}\Omega + 2 \text{ k}\Omega} = 2.00 \text{ V}$$



Design Note: Voltage division only applies when both resistors are carrying the same current.

Jaeger/Blalock  
4/15/07

Microelectronic Circuit Design  
McGraw-Hill


Chap 1 - 8

## Circuit Theory Review: Current Division

$$i_s = i_1 + i_2 \text{ where } i_1 = \frac{v_s}{R_1} \text{ and } i_2 = \frac{v_s}{R_2}$$

Combining and solving for  $v_s$ ,
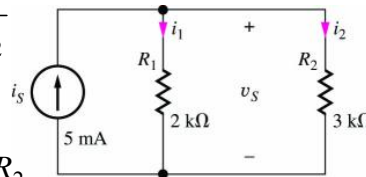
$$v_s = i_s \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = i_s \frac{R_1 R_2}{R_1 + R_2} = i_s R_1 \parallel R_2$$



Combining these yields the basic current division formula:


$$i_1 = i_s \frac{R_2}{R_1 + R_2} \quad i_2 = i_s \frac{R_1}{R_1 + R_2}$$

## Circuit Theory Review: Current Division (cont.)

Using the derived equations with the indicated values,


$$i_1 = 5 \text{ ma} \frac{3 \text{ k}\Omega}{2 \text{ k}\Omega + 3 \text{ k}\Omega} = 3.00 \text{ mA}$$
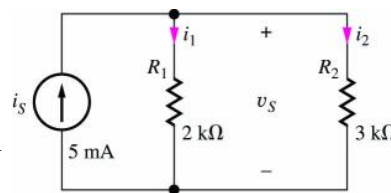
$$i_2 = 5 \text{ ma} \frac{2 \text{ k}\Omega}{2 \text{ k}\Omega + 3 \text{ k}\Omega} = 2.00 \text{ mA}$$



Design Note: Current division only applies when the same voltage appears across both resistors.
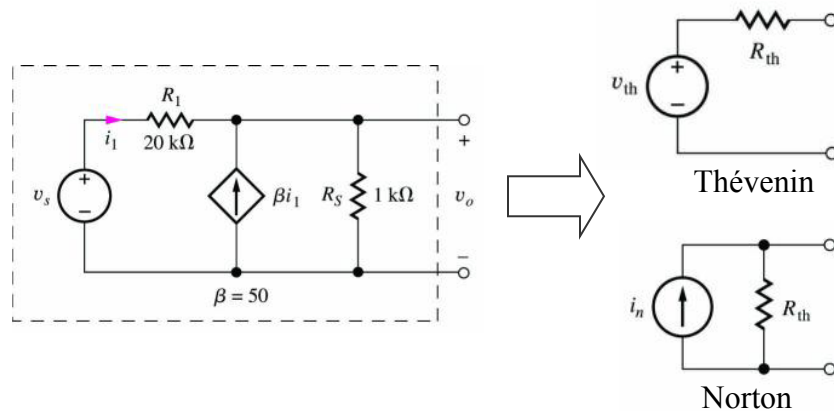
## Circuit Theory Review: Thévenin and Norton Equivalent Circuits



Jaeger/Blalock  
4/15/07

Microelectronic Circuit Design  
McGraw-Hill



Chap 1 - 11

## Circuit Theory Review: Find the Thévenin Equivalent Voltage

**Problem:** Find the Thévenin equivalent voltage at the output.

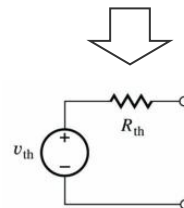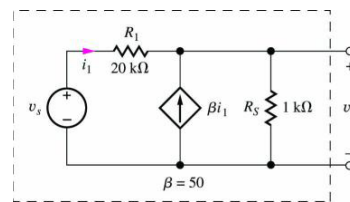**Solution:**

- **Known Information and Given Data:** Circuit topology and values in figure.
- **Unknowns:** Thévenin equivalent voltage  $v_{th}$ .
- **Approach:** Voltage source  $v_{th}$  is defined as the output voltage with no load.
- **Assumptions:** None.
- **Analysis:** Next slide...



Jaeger/Blalock  
4/15/07

Microelectronic Circuit Design  
McGraw-Hill

Chap 1 - 12

## Circuit Theory Review: Find the Thévenin Equivalent Voltage


Applying KCL at the output node,

$$\beta i_1 = \frac{v_o - v_s}{R_1} + \frac{v_o}{R_S} = G_1(v_o - v_s) + G_S v_o$$

Current  $i_1$  can be written as:  $i_1 = G_1(v_o - v_s)$

Combining the previous equations
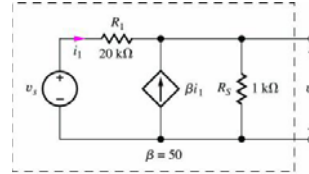
$$G_1(\beta + 1)v_s = [G_1(\beta + 1) + G_S]v_o$$



$$v_o = \frac{G_1(\beta + 1)}{G_1(\beta + 1) + G_S} v_s \times \frac{R_1 R_S}{R_1 R_S} = \frac{(\beta + 1)R_S}{(\beta + 1)R_S + R_1} v_s$$


## Circuit Theory Review: Find the Thévenin Equivalent Voltage (cont.)

Using the given component values:

$$v_o = \frac{(\beta + 1)R_S}{(\beta + 1)R_S + R_1} v_s = \frac{(50 + 1)1 \text{ k}\Omega}{(50 + 1)1 \text{ k}\Omega + 1 \text{ k}\Omega} v_s = 0.718v_s$$

and

$$v_{th} = 0.718v_s$$

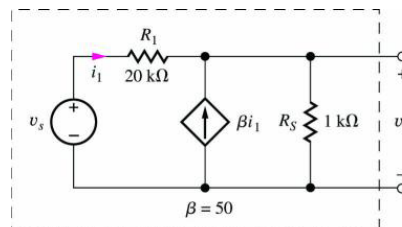


## Circuit Theory Review: Find the Thévenin Equivalent Resistance

**Problem:** Find the Thévenin equivalent resistance.

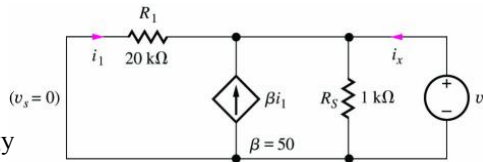**Solution:**

- **Known Information and Given Data:** Circuit topology and values in figure.
- **Unknowns:** Thévenin equivalent resistance  $R_{th}$ .
- **Approach:** Voltage source  $v_{th}$  is defined as the output voltage with no load.
- **Assumptions:** None.
- **Analysis:** Next slide...




Test voltage  $v_x$  has been added to the previous circuit. Applying  $v_x$  and solving for  $i_x$  allows us to find the Thévenin resistance as  $v_x/i_x$ .
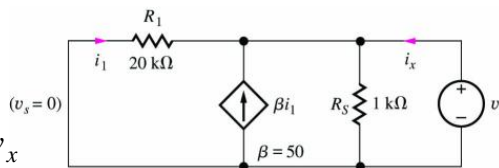
## Circuit Theory Review: Find the Thévenin Equivalent Resistance (cont.)

Applying KCL,

$$\begin{aligned} i_x &= -i_1 - \beta i_1 + G_S v_x \\ &= G_1 v_x + \beta G_1 v_x + G_S v_x \\ &= [G_1(\beta + 1) + G_S] v_x \end{aligned}$$



$$R_{th} = \frac{v_x}{i_x} = \frac{1}{G_1(\beta + 1) + G_S} = R_S \parallel \frac{R_1}{\beta + 1}$$

$$R_{th} = R_S \parallel \frac{R_1}{\beta + 1} = 1 \text{ k}\Omega \parallel \frac{20 \text{ k}\Omega}{50 + 1} = 1 \text{ k}\Omega \parallel 392 \text{ }\Omega = 282 \text{ }\Omega$$




## Circuit Theory Review: Find the Norton Equivalent Circuit

**Problem:** Find the Norton equivalent circuit.

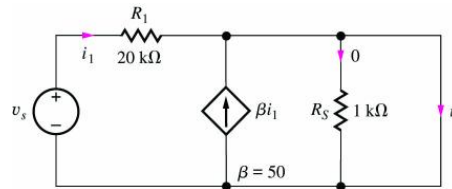**Solution:**

- **Known Information and Given Data:** Circuit topology and values in figure.
- **Unknowns:** Norton equivalent short circuit current  $i_n$ .
- **Approach:** Evaluate current through output short circuit.
- **Assumptions:** None.
- **Analysis:** Next slide...




A short circuit has been applied across the output. The Norton current is the current flowing through the short circuit at the output.
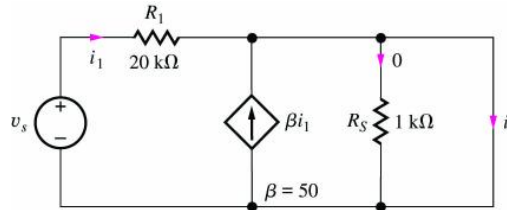
## Circuit Theory Review: Find the Norton Equivalent Circuit (cont.)

Applying KCL,


$$\begin{aligned}
 i_n &= i_1 + \beta i_1 \\
 &= G_1 v_s + \beta G_1 v_s \\
 &= G_1 (\beta + 1) v_s \\
 &= \frac{v_s (\beta + 1)}{R_1}
 \end{aligned}$$



Short circuit at the output causes zero current to flow through  $R_s$ .  $R_{th}$  is equal to  $R_{th}$  found earlier.

$$i_n = \frac{50 + 1}{20 \text{ k}\Omega} v_s = \frac{v_s}{392 \text{ }\Omega} = (2.55 \text{ mS}) v_s$$


## Final Thévenin and Norton Circuits

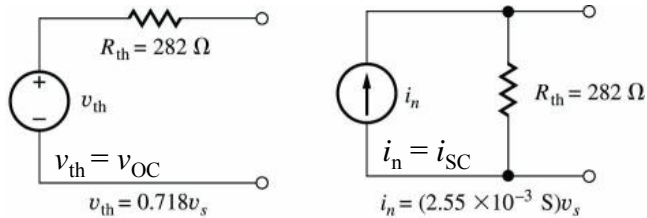

**Check of Results:** Note that  $v_{th} = i_n R_{th}$  and this can be used to check the calculations:  $i_n R_{th} = (2.55 \text{ mS})v_s(282 \Omega) = 0.719v_s$ , accurate within round-off error.

While the two circuits are identical in terms of voltages and currents at the output terminals, there is one difference between the two circuits. With no load connected, the Norton circuit still dissipates power!
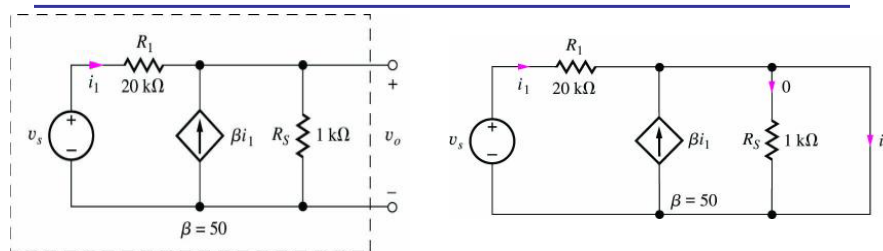
## Alternate Approach: $R_{th} = v_{OC}/i_{SC}$



$$v_{OC}/R_S = (1+\beta)(v_S - v_{OC})/R_1$$

$$v_{OC} = [(1+\beta)v_S/R_1]/[1/R_S + (1+\beta)/R_1]$$

$$= [(1+\beta)R_S]/[R_1 + (1+\beta)R_S]$$

$$= 0.718v_S$$


$$i_{SC} = (1+\beta)i_1 = (1+\beta)v_S/R_1$$

$$= 51v_S/20k\Omega$$

$$R_{th} = v_{OC}/i_{SC}$$

$$= R_1 R_S / [R_1 + (1+\beta)R_S] = 282\Omega$$

Fig. 1.16/Example 1.4 Circuit with VCCS (BJT CE amplifier)

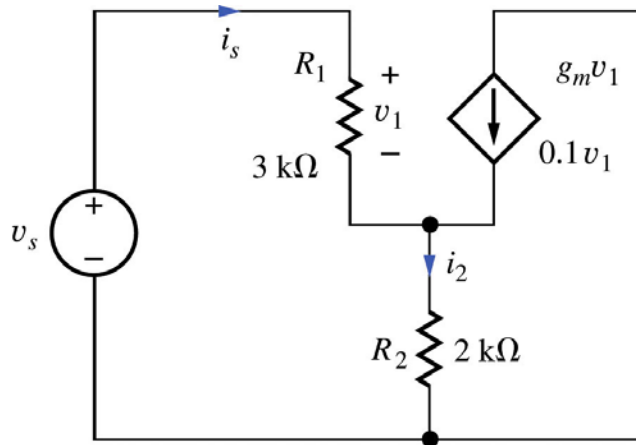

Jaeger/Blalock  
4/15/07

Microelectronic Circuit Design  
McGraw-Hill

Chap 1 - 21

## Amplifier Basics

- Analog signals are typically manipulated with linear amplifiers.
- Although signals may be comprised of several different components, linearity permits us to use the **superposition principle**.
- Superposition allows us to calculate the effect of each of the different components of a signal individually and then add the individual contributions to the output.

Jaeger/Blalock  
4/15/07

Microelectronic Circuit Design  
McGraw-Hill

Chap 1 - 22

## Amplifier Linearity

Given an input sinusoid:

$$v_s = V_s \sin(\omega_s t + \phi)$$

For a linear amplifier, the output is at the same frequency, but different amplitude and phase.


$$v_o = V_o \sin(\omega_s t + \phi + \theta)$$

In phasor notation:

$$\mathbf{v}_s = V_s \angle \phi \quad \mathbf{v}_o = V_o \angle (\phi + \theta)$$

Amplifier gain is:
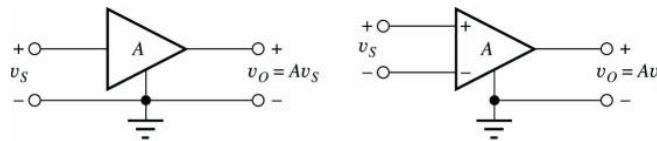
$$A = \frac{\mathbf{v}_o}{\mathbf{v}_s} = \frac{V_o \angle (\phi + \theta)}{V_s \angle \phi} = \frac{V_o}{V_s} \angle \theta$$




Jaeger/Blalock  
4/15/07

Microelectronic Circuit Design  
McGraw-Hill

Chap 1 - 23

## Amplifier Input/Output Response

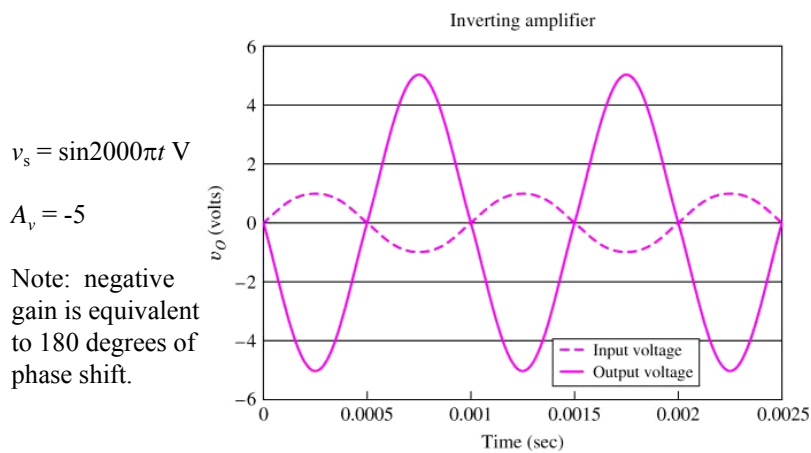

Jaeger/Blalock  
4/15/07

Microelectronic Circuit Design  
McGraw-Hill

Chap 1 - 24

## Ideal Operational Amplifier (Op Amp)

Ideal op amps are assumed to have  
infinite voltage gain, and  
infinite input resistance.

These conditions lead to two assumptions useful in analyzing ideal op-amp circuits:

1. The voltage difference across the input terminals is zero.
2. The input currents are zero.

## Ideal Op Amp Example

Writing a loop equation:

$$v_s - i_s R_1 - i_2 R_2 - v_o = 0$$

From assumption 2, we know that  $i_- = 0$ .

$$i_s = i_2 = \frac{v_s - v_-}{R_1}$$


Assumption 1 requires  $v_- = v_+ = 0$ .

$$i_s = \frac{v_s}{R_1}$$

Combining these equations yields:

$$A_v = \frac{v_o}{v_s} = -\frac{R_2}{R_1}$$

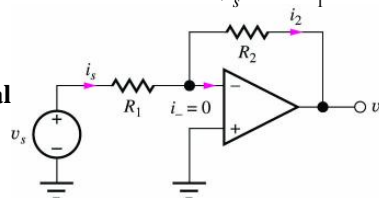Assumption 1 requiring  $v_- = v_+ = 0$  creates what is known as a **virtual ground**, or (more generally) a **virtual short-circuit**.



## Ideal Op Amp Example (Alternative Approach)

From Assumption 2,  $i_2 = i_s$ : 
$$i_s = \frac{v_s - v_-}{R_1} = \frac{v_s}{R_1} = i_2 = \frac{v_- - v_o}{R_2} = \frac{-v_o}{R_2}$$


And Assumption 1,  $v_- \approx 0$

$$\frac{v_s}{R_1} = \frac{-v_o}{R_2}$$

Yielding:

$$A_v = \frac{v_o}{v_s} = -\frac{R_2}{R_1}$$

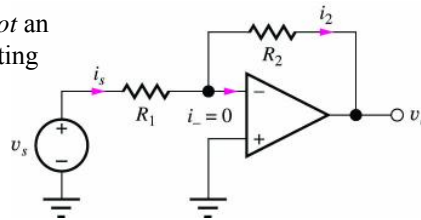Design Note: The virtual ground is *not* an actual ground. Do not short the inverting input to ground to simplify analysis.



Jaeger/Blalock  
4/15/07

Microelectronic Circuit Design  
McGraw-Hill

Chap 1 - 27

## Circuit Element Variations

- All electronic components have manufacturing tolerances.
  - Resistors can be purchased with  $\pm 10\%$ ,  $\pm 5\%$ , and  $\pm 1\%$  tolerance. (IC resistors are often  $\pm 10\%$ .)
  - Capacitors can have asymmetrical tolerances such as  $+20\%/-50\%$ .
  - Power supply voltages typically vary from 1% to 10%.
- Device parameters will also vary with temperature and age.
- Circuits must be designed to accommodate these variations.
- We will use worst-case and Monte Carlo (statistical) analysis to examine the effects of component parameter variations.

Jaeger/Blalock  
4/15/07

Microelectronic Circuit Design  
McGraw-Hill

Chap 1 - 28

## Tolerance Modeling

---

- For symmetrical parameter variations

$$P_{\text{nom}}(1 - \varepsilon) \leq P \leq P_{\text{nom}}(1 + \varepsilon)$$

- For example, a 10K resistor with  $\pm 5\%$  percent tolerance could take on the following range of values:

$$10\text{k}(1 - 0.05) \leq R \leq 10\text{k}(1 + 0.05)$$

$$9,500 \Omega \leq R \leq 10,500 \Omega$$

## Circuit Analysis with Tolerances

---


- Worst-case analysis
  - Parameters are manipulated to produce the worst-case min and max values of desired quantities.
  - This can lead to over design since the worst-case combination of parameters is rare.
  - It may be less expensive to discard a rare failure than to design for 100% yield.
- Monte-Carlo analysis
  - Parameters are randomly varied to generate a set of statistics for desired outputs.
  - The design can be optimized so that failures due to parameter variation are less frequent than failures due to other mechanisms.
  - In this way, the design difficulty is better managed than a worst-case approach.

## Worst Case Analysis Example

**Problem:** Find the nominal and worst-case values for output voltage and source current.

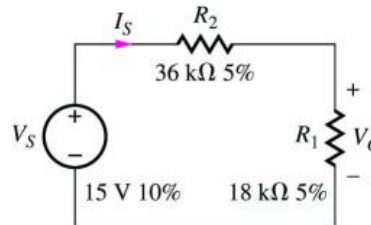**Solution:**

- **Known Information and Given Data:** Circuit topology and values in figure.
- **Unknowns:**  $V_O^{nom}$ ,  $V_O^{min}$ ,  $V_O^{max}$ ,  $I_S^{nom}$ ,  $I_S^{min}$ ,  $I_S^{max}$ .
- **Approach:** Find nominal values and then select  $R_1$ ,  $R_2$ , and  $V_S$  values to generate extreme cases of the unknowns.
- **Assumptions:** None.
- **Analysis:** Next slides...



Nominal voltage solution:


$$V_O^{nom} = V_S^{nom} \frac{R_1^{nom}}{R_1^{nom} + R_2^{nom}}$$

$$= 15V \frac{18k\Omega}{18k\Omega + 36k\Omega} = 5V$$
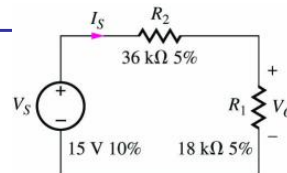
## Worst-Case Analysis Example (cont.)

Nominal Source current:

$$I_S^{nom} = \frac{V_S^{nom}}{R_1^{nom} + R_2^{nom}} = \frac{15V}{18k\Omega + 36k\Omega} = 278\mu A$$



Rewrite  $V_O$  to help us determine how to find the worst-case values.

$$V_O = V_S \frac{R_1}{R_1 + R_2} = \frac{V_S}{1 + \frac{R_2}{R_1}}$$

$V_O$  is maximized for max  $V_S$ ,  $R_1$  and min  $R_2$ .

$V_O$  is minimized for min  $V_S$ ,  $R_1$ , and max  $R_2$ .

$$V_O^{max} = \frac{15V(1.1)}{1 + \frac{36K(0.95)}{18K(1.05)}} = 5.87V$$

$$V_O^{min} = \frac{15V(0.95)}{1 + \frac{36K(1.05)}{18K(0.95)}} = 4.20V$$



## Worst-Case Analysis Example (cont.)

Worst-case source currents:

$$I_S^{\max} = \frac{V_S^{\max}}{R_1^{\min} + R_2^{\min}} = \frac{15V(1.1)}{18k\Omega(0.95) + 36k\Omega(0.95)} = 322\mu A$$


$$I_S^{\min} = \frac{V_S^{\min}}{R_1^{\max} + R_2^{\max}} = \frac{15V(0.9)}{18k\Omega(1.05) + 36k\Omega(1.05)} = 238\mu A$$

**Check of Results:** The worst-case values range from 14-17 percent above and below the nominal values. The sum of the three element tolerances is 20 percent, so our calculated values appear to be reasonable.
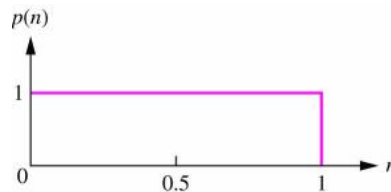
## Monte Carlo Analysis

- Parameters are varied randomly and output statistics are gathered.
- We use programs like MATLAB, Mathcad, SPICE, or a spreadsheet to complete a statistically significant set of calculations.
- For example, with Excel®, a resistor with 5% tolerance can be expressed as:  $R = R_{nom}(1 + 2\varepsilon(RAND() - 0.5))$

The RAND() function returns random numbers uniformly distributed between 0 and 1.




## Monte Carlo Analysis Example

**Problem:** Perform a Monte Carlo analysis and find the mean, standard deviation, min, and max for  $V_O$ ,  $I_S$ , and power delivered from the source.

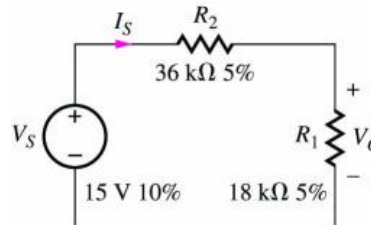**Solution:**

- **Known Information and Given Data:** Circuit topology and values in figure.
- **Unknowns:** The mean, standard deviation, min, and max for  $V_O$ ,  $I_S$ , and  $P_S$ .
- **Approach:** Use a spreadsheet to evaluate the circuit equations with random parameters.
- **Assumptions:** None.
- **Analysis:** Next slides...



Monte Carlo parameter definitions:

$$V_S = 15(1 + 0.2(\text{RAND}() - 0.5))$$

$$R_1 = 18,000(1 + 0.1(\text{RAND}() - 0.5))$$

$$R_2 = 36,000(1 + 0.1(\text{RAND}() - 0.5))$$

Jaeger/Blalock  
4/15/07

Microelectronic Circuit Design  
McGraw-Hill

Chap 1 - 35

## Monte Carlo Analysis Example (cont.)

Monte Carlo parameter definitions:

$$V_S = 15(1 + 0.2(\text{RAND}() - 0.5))$$

$$R_1 = 18,000(1 + 0.1(\text{RAND}() - 0.5))$$

$$R_2 = 36,000(1 + 0.1(\text{RAND}() - 0.5))$$

Circuit equations based on Monte Carlo parameters:

$$V_O = V_S \frac{R_1}{R_1 + R_2} \quad I_S = \frac{V_S}{R_1 + R_2} \quad P_S = V_S I_S$$

Excel Results:

	Avg	Nom.	Stdev	Max	WC-max	Min	WC-Min
$V_O$ (V)	4.96	5.00	0.30	5.70	5.87	4.37	4.20
$I_S$ (mA)	0.276	0.278	0.0173	0.310	0.322	0.242	0.238
$P$ (mW)	4.12	4.17	0.490	5.04	--	3.29	--


Jaeger/Blalock  
4/15/07

Microelectronic Circuit Design  
McGraw-Hill

Chap 1 - 36

## MATLAB Monte Carlo Analysis Result

---

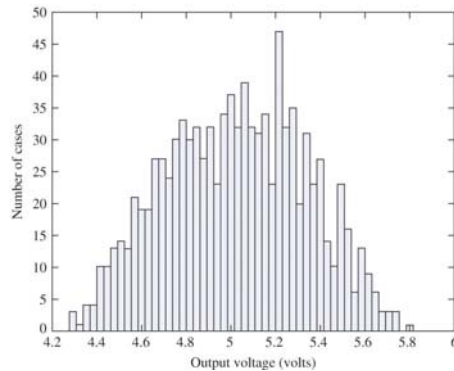

Histogram of output voltage from 1000 case Monte Carlo simulation.

## Temperature Coefficients

---

- Most circuit parameters are temperature sensitive.  
$$P = P_{\text{nom}}(1 + \alpha_1 \Delta T + \alpha_2 \Delta T^2)$$
 where  $\Delta T = T - T_{\text{nom}}$   
 $P_{\text{nom}}$  is defined at  $T_{\text{nom}}$
- Most versions of SPICE allow for the specification of  $T_{\text{NOM}}$ ,  $T$ ,  $TC1(\alpha_1)$ ,  $TC2(\alpha_2)$ .
- SPICE temperature model for resistor:  
$$R(T) = R(T_{\text{NOM}}) * [1 + TC1 * (T - T_{\text{NOM}}) + TC2 * (T - T_{\text{NOM}})^2]$$
- Many other components have similar models.

---

End of Lecture 1