
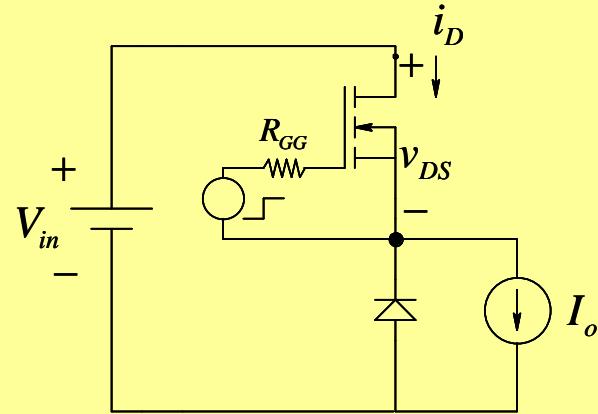


Soft-Switching in DC-DC Converters

HARD-SWITCHING IN SWITCHING POWER-POLES

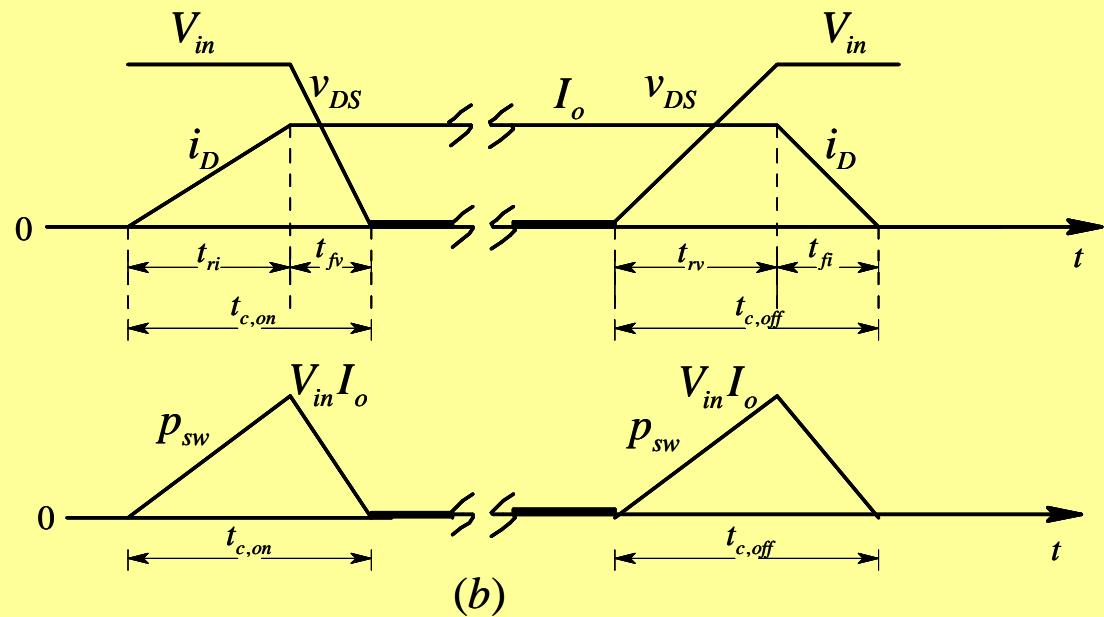

(a)




$$P_{sw} \propto f_s (t_{c(on)} + t_{c(off)})$$


SOFT-SWITCHING IN SWITCHING POWER-POLES

- ZVS (zero voltage switching), and
- ZCS (zero current switching)

Zero Voltage Switching (ZVS)




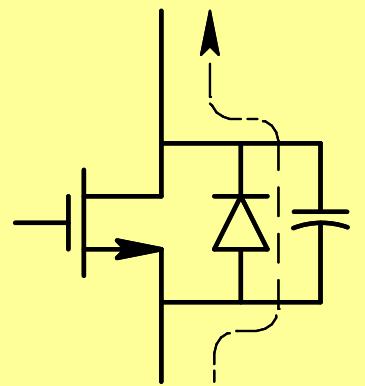



(a)

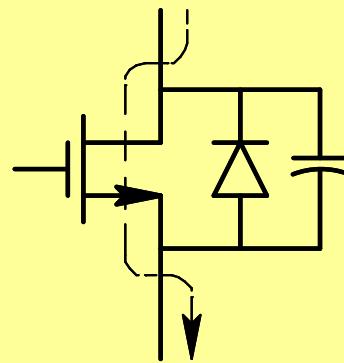

(b)

Synchronous Buck Converter with ZVS

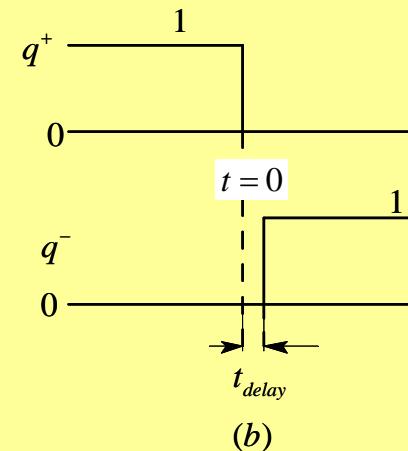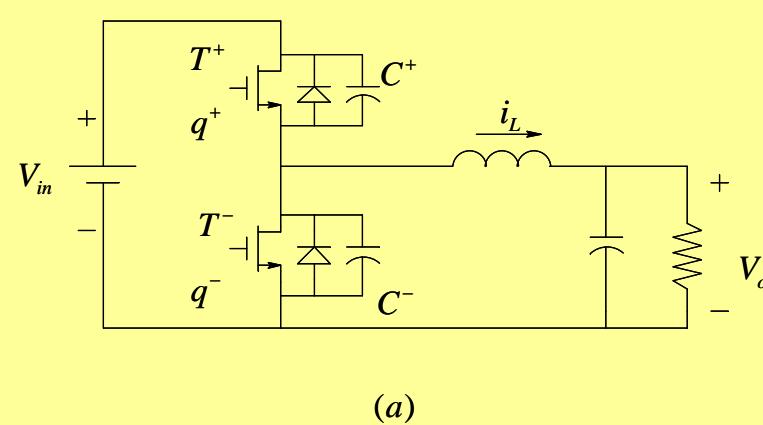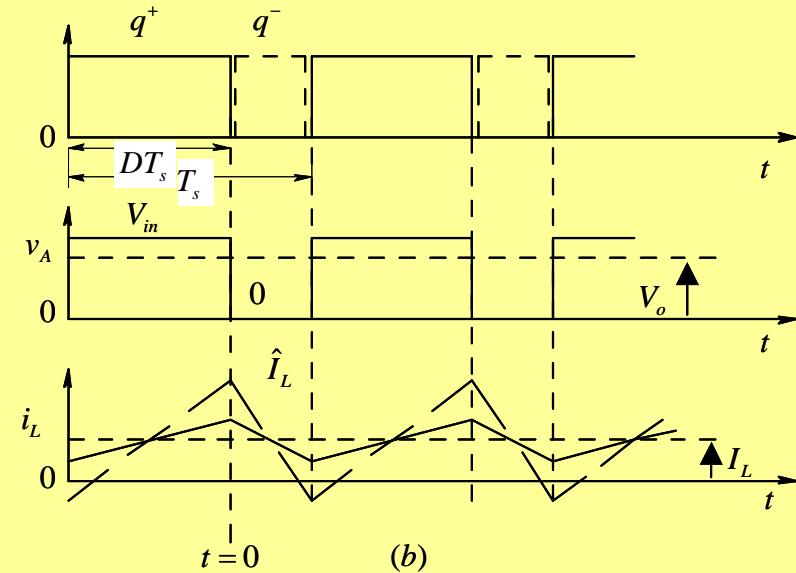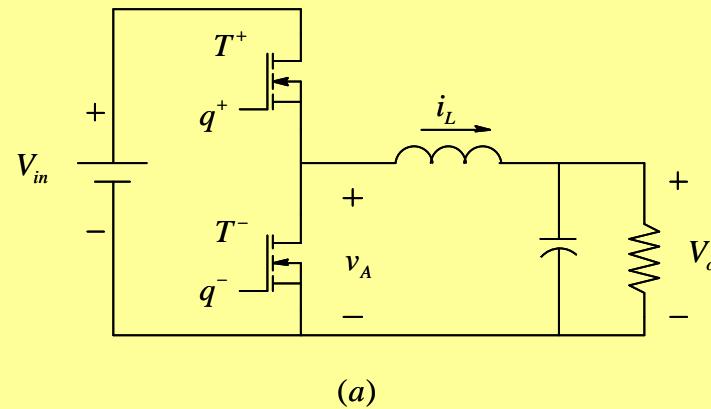

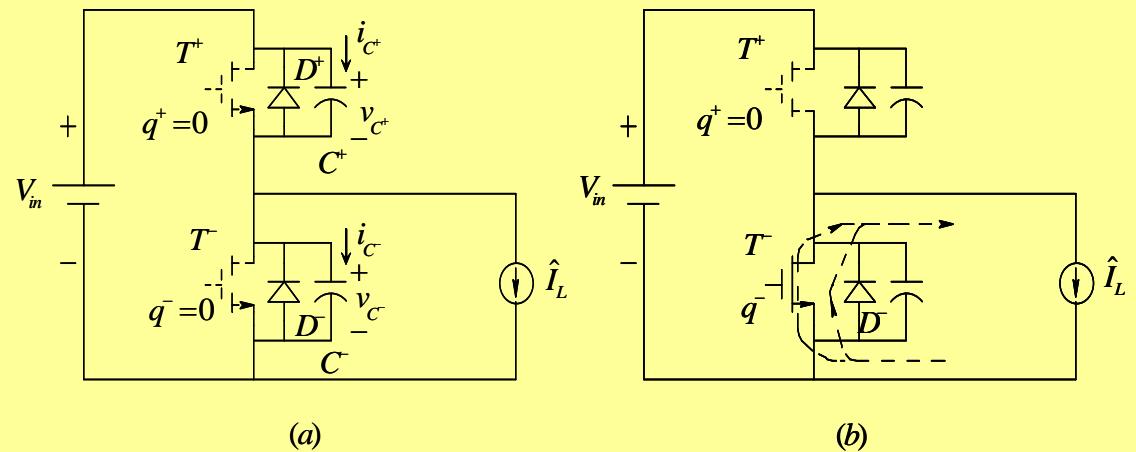


$$v_{C^+} + v_{C^-} = V_{in}$$

$$C \frac{d}{dt} v_{C^+} + C \frac{d}{dt} v_{C^-} = 0$$


$$i_{C^+} + i_{C^-} = 0 \quad \Rightarrow \quad i_{C^+} = -i_{C^-}$$

$$i_{C^+} = -i_{C^-} = \frac{\hat{I}_L}{2}$$


PSpice Modeling:

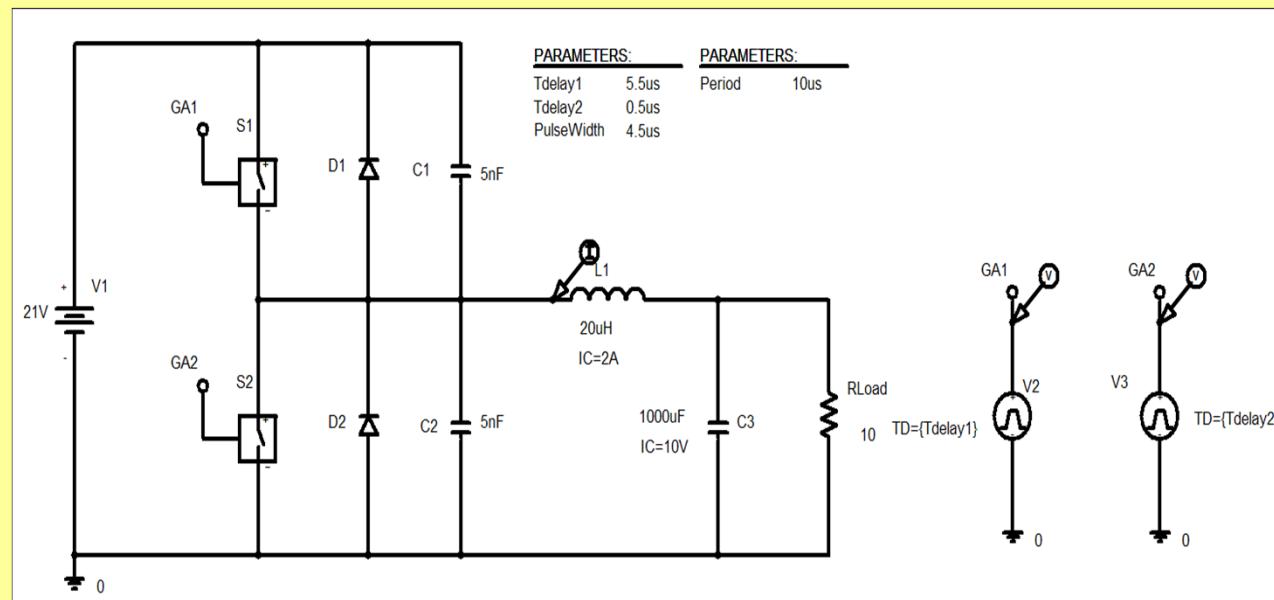

Simulation Results

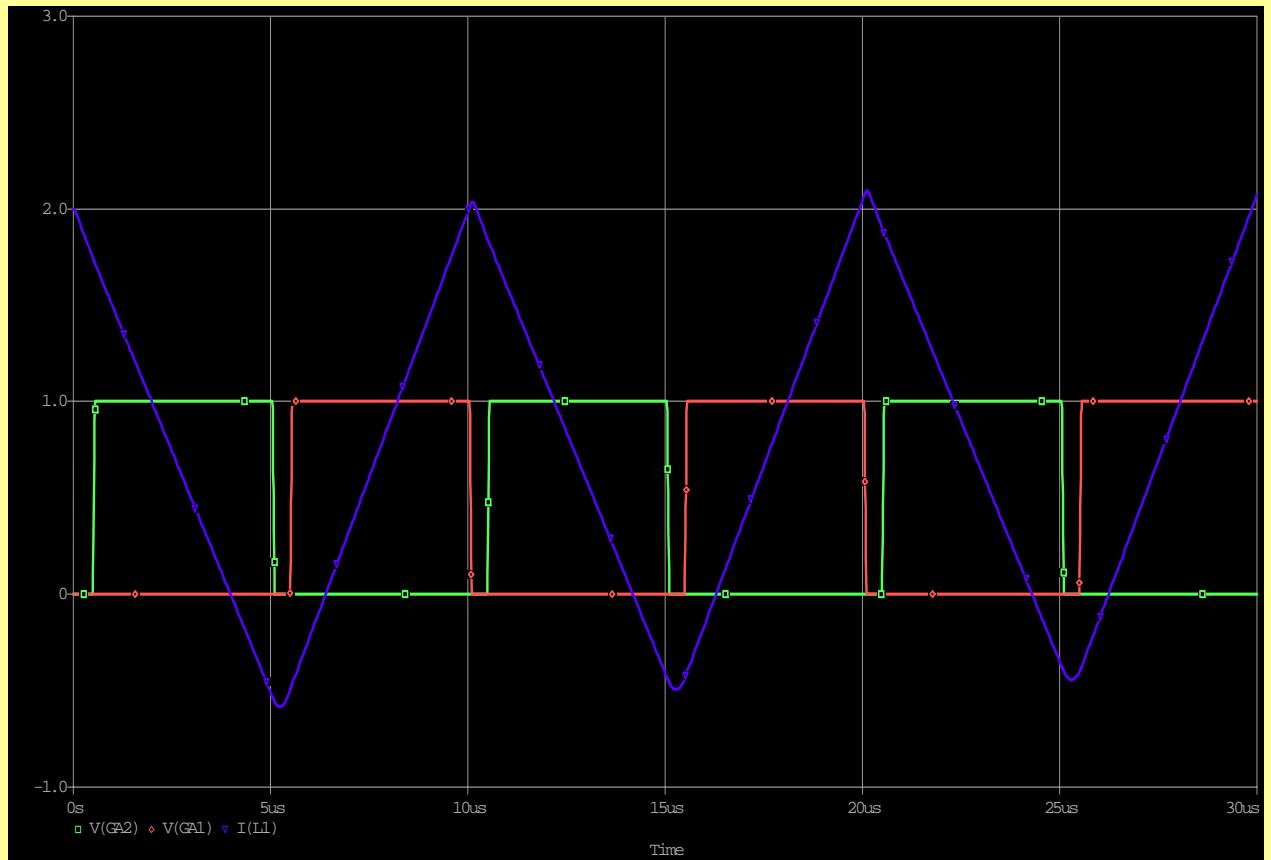

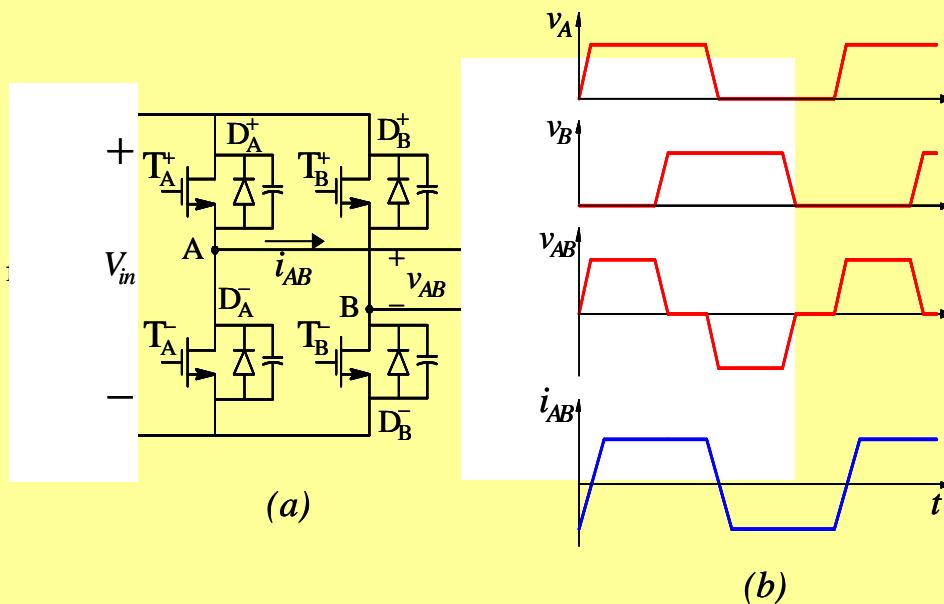Phase-Shift Modulated (PSM) DC-DC Converter



Summary

Soft-Switching in DC-DC Converters