
 


Fig. 5-1 Block Diagram of Sequential Circuit

 


(a) Block diagram



(b) Timing diagram of clock pulses

Fig. 5-2 Synchronous Clocked Sequential Circuit

 


(a) Logic diagram

$S$	$R$	$Q$	$Q'$	
1	0	1	0	
0	0	1	0	(after $S = 1, R = 0$ )
0	1	0	1	
0	0	0	1	(after $S = 0, R = 1$ )
1	1	0	0	

(b) Function table

Fig. 5-3 SR Latch with NOR Gates

 


(a) Logic diagram

<i>S</i>	<i>R</i>	<i>Q</i>	<i>Q'</i>	
1	0	0	1	
1	1	0	1	(after <i>S</i> = 1, <i>R</i> = 0)
0	1	1	0	
1	1	1	0	(after <i>S</i> = 0, <i>R</i> = 1)
0	0	1	1	

(b) Function table

Fig. 5-4 SR Latch with NAND Gates

 


(a) Logic diagram

$C$	$S$	$R$	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; Reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate

(b) Function table

Fig. 5-5 SR Latch with Control Input

 

(a) Logic diagram

$C$	$D$	Next state of $Q$
0	X	No change
1	0	$Q = 0$ ; Reset state
1	1	$Q = 1$ ; Set state

(b) Function table

Fig. 5-6 D Latch

 


Fig. 5-7 Graphic Symbols for Latches



(a) Response to positive level



(b) Positive-edge response



(c) Negative-edge response

Fig. 5-8 Clock Response in Latch and Flip-Flop

 


Fig. 5-9 Master-Slave *D* Flip-Flop



 


Fig. 5-10 *D*-Type Positive-Edge-Triggered Flip-Flop

 


(a) Positive-edge

 


(a) Negative-edge

Fig. 5-11 Graphic Symbol for Edge-Triggered  $D$  Flip-Flop

 


(a) Circuit diagram

 


(b) Graphic symbol


Fig. 5-12 *JK* Flip-Flop

 

(a) From JK flip-flop

 


(b) From D flip-flop

 


(c) Graphic symbol

Fig. 5-13 T Flip-Flop

 


(a) Circuit diagram

 

(b) Graphic symbol

R	C	D	Q	$Q'$
0	X	X	0	1
1	$\uparrow$	0	0	1
1	$\uparrow$	1	1	0

(b) Function table

 


 



Fig. 5-16 State Diagram of the Circuit of Fig. 5-15

 

(a) Circuit diagram

Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(b) State table

 

(c) State diagram

Fig. 5-17 Sequential Circuit with D Flip-Flop

 


Fig. 5-18 Sequential Circuit with *JK* Flip-Flop



 


Fig. 5-19 State Diagram of the Circuit of Fig. 5-18

 

(a) Circuit diagram

 

(b) State diagram

Fig. 5-20 Sequential Circuit with  $T$  Flip-Flops

 


Fig. 5-21 Simulation Output of HDL Example 5-7

 


Fig. 5-22 State Diagram

 


Fig. 5-23 Reduced State Diagram



 



Fig. 5-24 State Diagram for Sequence Detector

 

$$D_A = Ax + Bx$$

 

$$D_B = Ax + B'x$$

 

$$y = AB$$

Fig. 5-25 Maps for Sequence Detector



 



Fig. 5-26 Logic Diagram of Sequence Detector

 


$$J_A = Bx'$$

 

$$K_A = Bx$$

 

$$J_B = x$$

 

$$K_B = (A \oplus x)'$$

 


Fig. 5-28 Logic Diagram for Sequential Circuit with JK Flip-Flops

 


Fig. 5-29 State Diagram of 3-Bit Binary Counter

 


Fig. 5-30 Maps for 3-Bit Binary Counter

 


Fig. 5-31 Logic Diagram of 3-Bit Binary Counter

 


Fig. P5-7

 


Fig. P5-8

 


Fig. P5-19